

# Dependable Computing

A Multilevel Approach



**Behrooz Parhami**

University of California, Santa Barbara

## STRUCTURE AT A GLANCE

<b>Part I — Introduction:</b> Dependable Systems (The Ideal-System View)	Goals	1. Background and Motivation 2. Dependability Attributes 3. Combinational Modeling 4. State-Space Modeling
	Models	
<b>Part II — Defects:</b> Physical Imperfections (The Device-Level View)	Methods	5. Defect Avoidance 6. Defect Circumvention 7. Shielding and Hardening 8. Yield Enhancement
	Examples	
<b>Part III — Faults:</b> Logical Deviations (The Circuit-Level View)	Methods	9. Fault Testing 10. Fault Masking 11. Design for Testability 12. Replication and Voting
	Examples	
<b>Part IV — Errors:</b> Informational Distortions (The State-Level View)	Methods	13. Error Detection 14. Error Correction 15. Self-Checking Modules 16. Redundant Disk Arrays
	Examples	
<b>Part V — Malfunctions:</b> Architectural Anomalies (The Structure-Level View)	Methods	17. Malfunction Diagnosis 18. Malfunction Tolerance 19. Standby Redundancy 20. Resilient Algorithms
	Examples	
<b>Part VI — Degradations:</b> Behavioral Lapses (The Service-Level View)	Methods	21. Degradation Allowance 22. Degradation Management 23. Robust Task Scheduling 24. Software Redundancy
	Examples	
<b>Part VII — Failures:</b> Computational Breaches (The Result-Level View)	Methods	25. Failure Confinement 26. Failure Recovery 27. Agreement and Adjudication 28. Fail-Safe System Design
	Examples	

Appendix: Past, Present, and Future

# About This Presentation

This presentation is intended to support the use of the textbook *Dependable Computing: A Multilevel Approach* (traditional print or on-line open publication, TBD). It is updated regularly by the author as part of his teaching of the graduate course ECE 257A, Fault-Tolerant Computing, at Univ. of California, Santa Barbara. Instructors can use these slides freely in classroom teaching or for other educational purposes. Unauthorized uses, including distribution for profit, are strictly prohibited. © Behrooz Parhami

<b>Edition</b>	<b>Released</b>	<b>Revised</b>	<b>Revised</b>	<b>Revised</b>	<b>Revised</b>
<b>First</b>	<b>Sep. 2006</b>	<b>Oct. 2007</b>	<b>Oct. 2009</b>	<b>Oct. 2012</b>	<b>Oct. 2013</b>
		<b>Jan. 2015</b>	<b>Oct. 2015</b>	<b>Oct. 2018</b>	<b>Oct. 2019</b>
		<b>Oct. 2020</b>			



# 9 Fault Testing








## STRUCTURE AT A GLANCE

<b>Part I — Introduction:</b> Dependable Systems (The Ideal-System View)	Goals	1. Background and Motivation 2. Dependability Attributes 3. Combinational Modeling 4. State-Space Modeling
	Models	
<b>Part II — Defects:</b> Physical Imperfections (The Device-Level View)	Methods	5. Defect Avoidance 6. Defect Circumvention 7. Shielding and Hardening 8. Yield Enhancement
	Examples	
<b>Part III — Faults:</b> Logical Deviations (The Circuit-Level View)	Methods	9. Fault Testing 10. Fault Masking
	Examples	11. Design for Testability 12. Replication and Voting
<b>Part IV — Errors:</b> Informational Distortions (The State-Level View)	Methods	13. Error Detection 14. Error Correction 15. Self-Checking Modules 16. Redundant Disk Arrays
	Examples	
<b>Part V — Malfunctions:</b> Architectural Anomalies (The Structure-Level View)	Methods	17. Malfunction Diagnosis 18. Malfunction Tolerance 19. Standby Redundancy 20. Resilient Algorithms
	Examples	
<b>Part VI — Degradations:</b> Behavioral Lapses (The Service-Level View)	Methods	21. Degradation Allowance 22. Degradation Management 23. Robust Task Scheduling 24. Software Redundancy
	Examples	
<b>Part VII — Failures:</b> Computational Breaches (The Result-Level View)	Methods	25. Failure Confinement 26. Failure Recovery 27. Agreement and Adjudication 28. Fail-Safe System Design
	Examples	

 


Appendix: Past, Present, and Future

# 9.1 Overview and Fault Models

## The faulty state


and transitions into and out of it

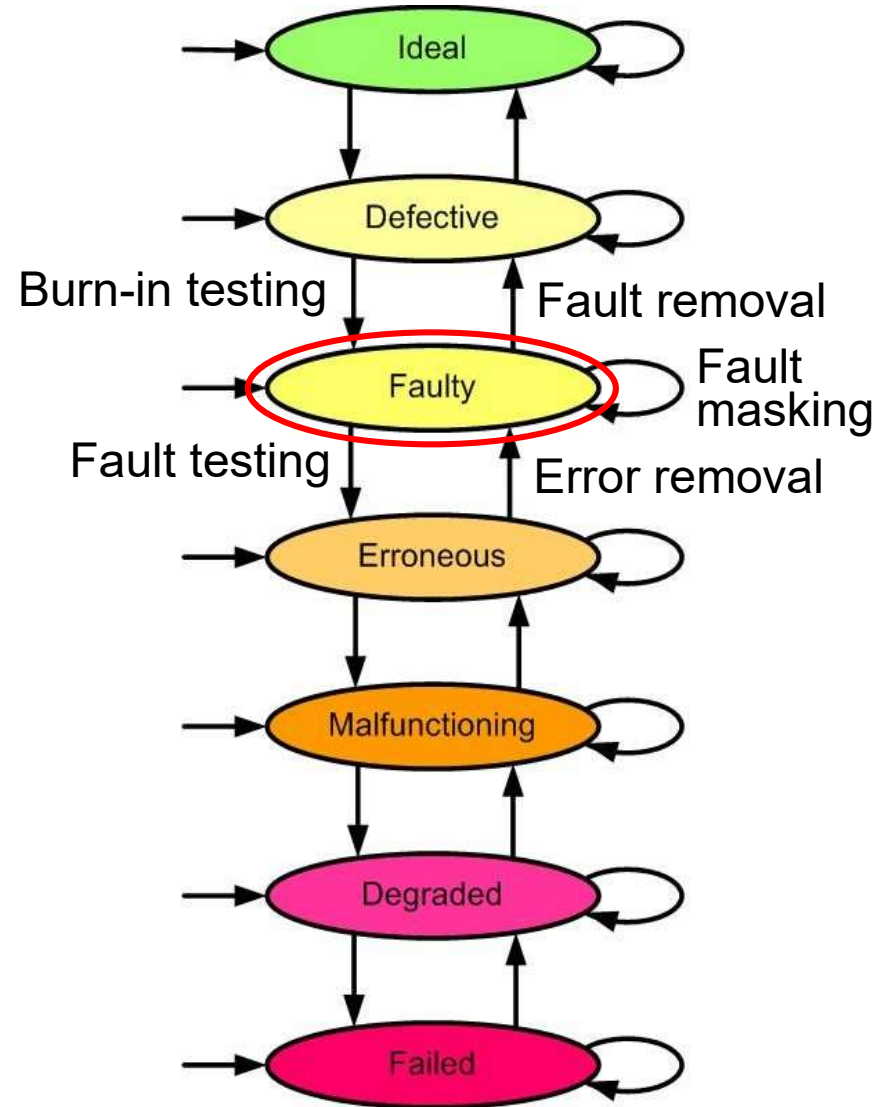

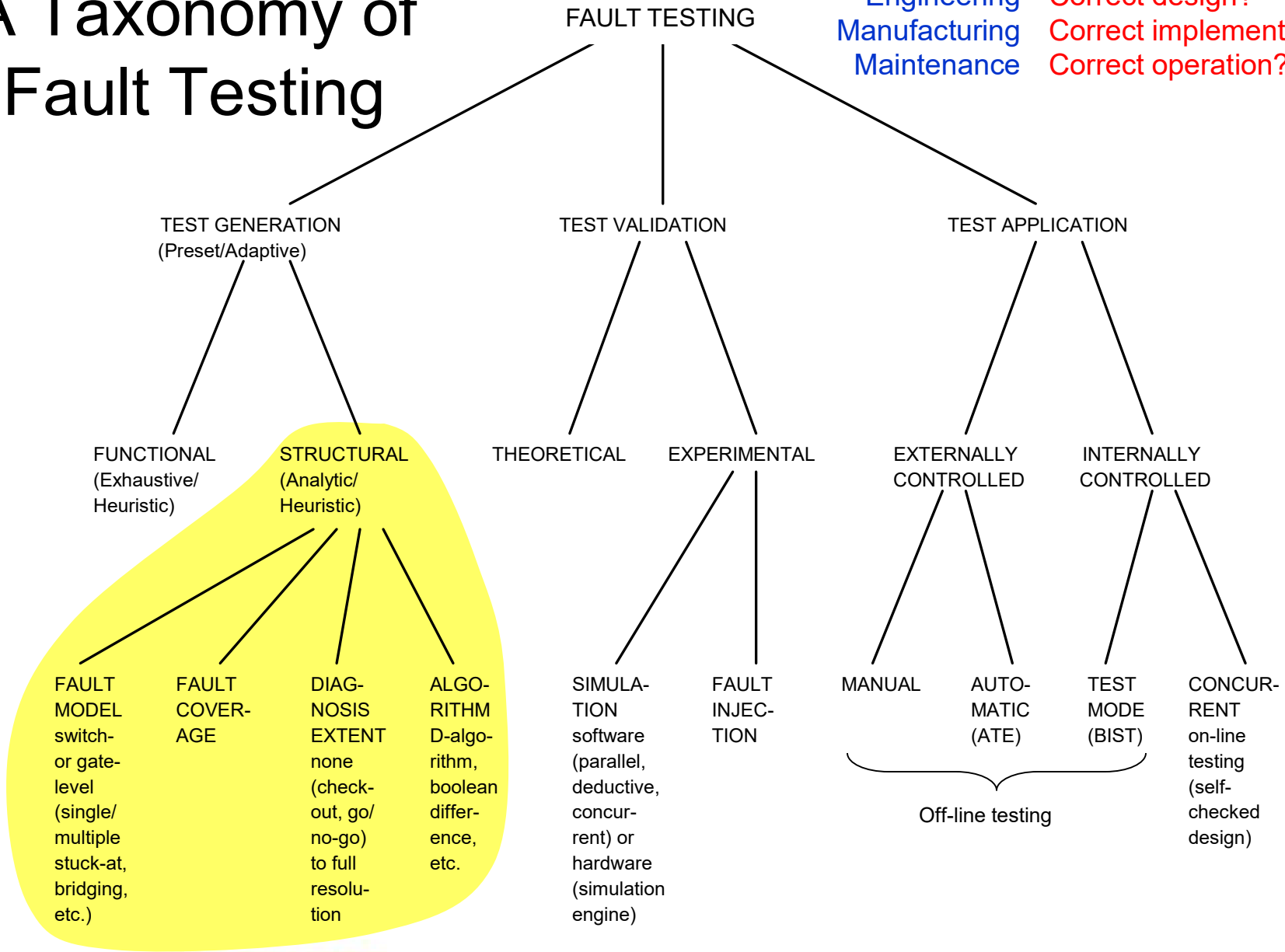
# A Taxonomy of Fault Testing

Engineering  
Manufacturing  
Maintenance

Correct design?  
Correct implementation?  
Correct operation?



# Requirements and Setup for Testing

 

Testability requires **controllability** and **observability** (redundancy may reduce testability if we are not careful; e.g., TMR)

Reference value can come from a “gold” version or from a table

Test patterns may be randomly generated, come from a preset list, or be selected according to previous test outcomes

Test results may be compressed into a “signature” before comparing

Test application may be off-line or on-line (concurrent)



# Importance and Limitations of Testing

Important to detect faults as early as possible

Approximate cost of catching a fault at various levels

Component	\$1
Board	\$10
System	\$100
Field	\$1000

Test coverage may be well below 100% (model inaccuracies and impossibility of dealing with all combinations of the modeled faults)

“Trying to improve software quality by increasing the amount of testing is like trying to lose weight by weighing yourself more often.”

Steve C. McConnell

“Program testing can be used to show the presence of bugs, but never to show their absence!” Edsger W. Dijkstra

# Fault Models at Different Abstraction Levels

Fault model is an abstract specification of the types of deviations in logic values that one expects in the circuit under test

Can be specified at various levels: transistor, **gate**, function, system

## Transistor-level faults

Caused by defects, shorts/opens, electromigration, transients, . . .

May lead to high current, incorrect output, intermediate voltage, . . .

Modeled as stuck-on/off, bridging, delay, coupling, crosstalk faults

Quickly become intractable because of the large model space

## Function-level faults

Selected in an ad hoc manner based on the function of a block  
(decoder, ALU, memory)

## System-level faults (malfunctions, in our terminology)

Will discuss later in Part V

# Gate- or Logic-Level Fault Models

Most popular models (due to their accuracy and relative tractability)

## Line stuck faults

Stuck-at-0 (s-a-0)

Stuck-at-1 (s-a-1)

## Line bridging faults

Unintended connection  
(wired OR/AND)

## Line open faults


Often can be modeled as s-a-0 or s-a-1

## Delay faults (less tractable than the previous fault types)

Signals experience unusual delays

## Other faults

Coupling, crosstalk

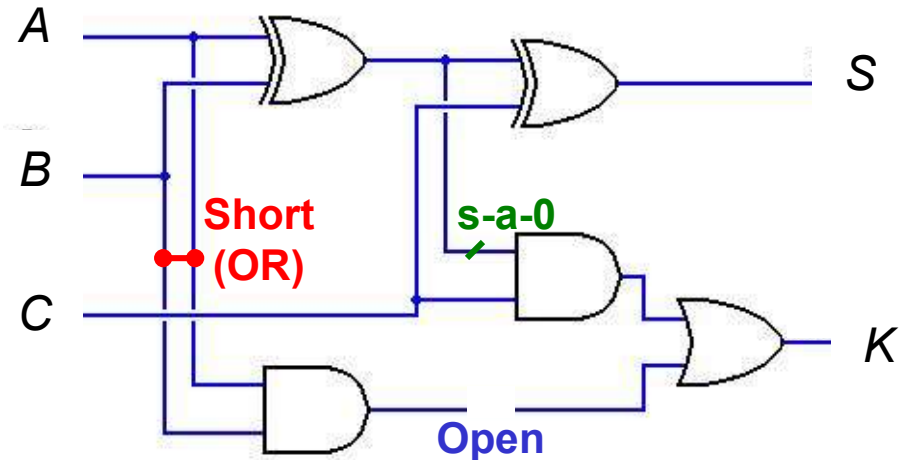




# 9.2 Path Sensitization and D-Algorithm

The main idea behind test design: control the faulty point from inputs and propagate its behavior to some output

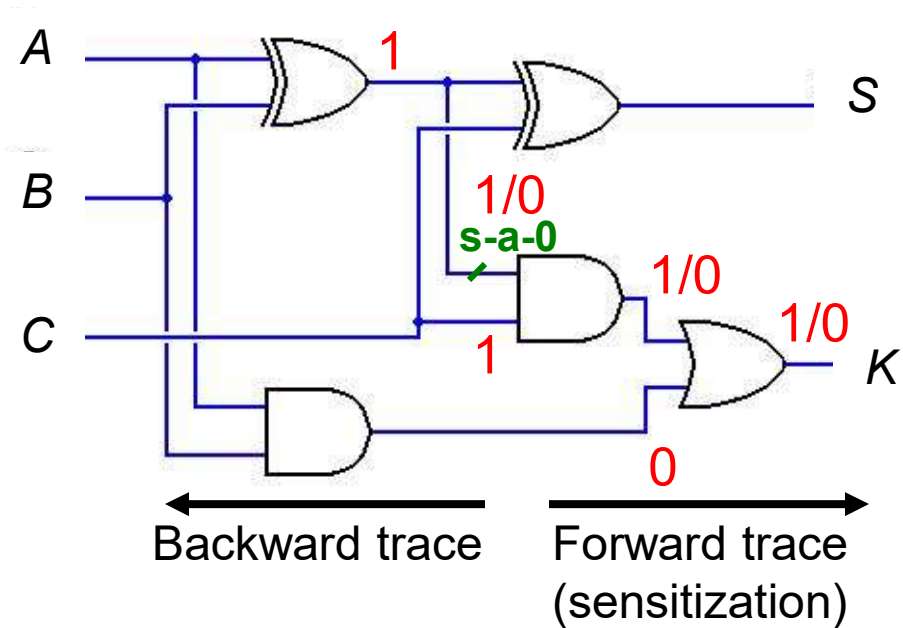Example: s-a-0 fault  
Test must force the line to 1

Two possible tests  
(A, B, C) = (0 1 1) or (1 0 1)

This method is formalized in the *D*-algorithm



## D-calculus

1/0 on the diagram above is represented as *D*


0/1 is represented as  $\bar{D}$

Encounters difficulties with XOR gates (PODEM algorithm fixes this)

# Selection of a Minimal Test Set

Each input pattern detects a subset of all possible faults of interest (according to our fault model)

A	B	C	P		Q	
			s-a-0	s-a-1	s-a-0	s-a-1
0	0	0	-	-	-	X
0	0	1	-	X	-	X
0	1	1	X	-	X	-
1	0	1	X	-	X	-

 

Choosing a minimal test set is a covering problem


Equivalent faults: e.g.,  $P$  s-a-0  $\equiv$   $L$  s-a-0  $\equiv$   $Q$  s-a-0  
 $Q$  s-a-1  $\equiv$   $R$  s-a-1  $\equiv$   $K$  s-a-1

# Capabilities and Complexity of D-Algorithm

Reconvergent fan-out

Consider the s input s-a-0

 Simple path sensitization does not allow us to propagate the fault to the primary output z



PODEM solves the problem by setting y to 0

Worst-case complexity of D-algorithm is exponential in circuit size

Must consider all path combinations

XOR gates cause the behavior to approach the worst case

Average case is much better; quadratic

PODEM: Path-oriented decision making

Developed by Goel in 1981

Also exponential, but in the number of circuit inputs, not its size




## 9.3 Boolean Difference Methods

$$K = f(A, B, C) = AB \vee BC \vee CA$$

$$\begin{aligned} dK/dB &= f(A, 0, C) \oplus f(A, 1, C) \\ &= CA \oplus (A \vee C) \\ &= A \oplus C \end{aligned}$$

$$K = PC \vee AB$$
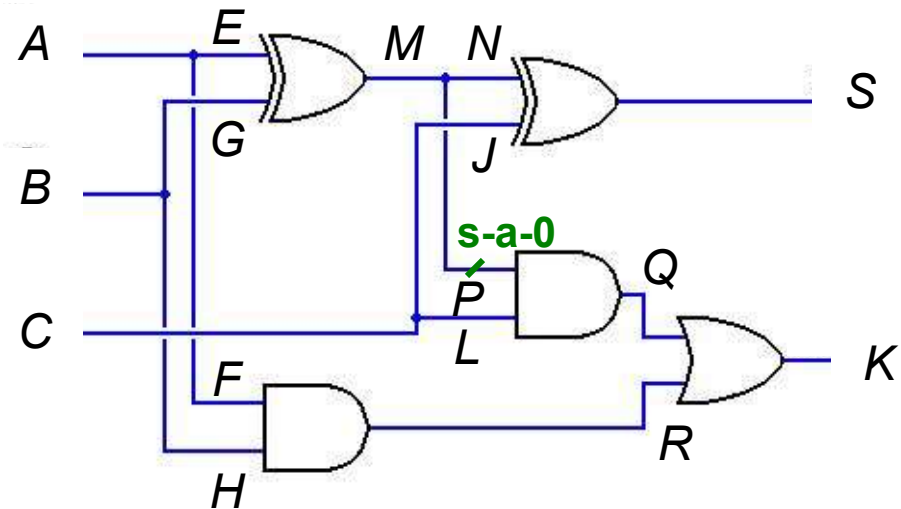
$$dK/dP = AB \oplus (C \vee AB) = C(\overline{AB})$$



Tests that detect  $P$  s-a-0 are solutions to the equation  $P dK/dP = 1$

$$(A \oplus B) C(\overline{AB}) = 1 \quad \Rightarrow \quad C = 1, A \neq B$$

Tests that detect  $\overline{P}$  s-a-1 are solutions to the equation  $\overline{P} dK/dP = 1$

$$(A \oplus B) C(\overline{AB}) = 1 \quad \Rightarrow \quad C = 1, A = B = 0$$

# 9.4 The Complexity of Fault Testing

## The satisfiability problem (SAT)

Decision problem: Is a Boolean expression satisfiable?  
(i.e., can we assign values to the variables to make the result 1?)

Theorem (Cook, 1971): SAT is NP-complete

In fact, even restricted versions of SAT remain NP-complete

Theorem (Cook, 1971): 3SAT is NP-complete

In 3SAT, the logic expression is a product of 3-term OR clauses

According to the Boolean difference formulation, fault detection can be converted to SAT (find the solutions to  $P \text{ d}K/\text{d}P = 1$ )

To prove the NP-completeness of fault detection, we need to show that SAT (or another NP-complete problem) can be converted to it

Proof of NP-completeness is due to Ibarra and Sahni [Ibar75]

A simple alternate proof by Fujiwara [Fuji82] is in the textbook

# Proof that Fault Detection is NP-Complete

Theorem (Cook, 1971): 3SAT is NP-complete

Theorem: Clause-monotone SAT (CM-SAT) is NP-complete

CM-SAT has OR clauses each of which consists entirely of complemented or uncomplemented variables, but not both

3SAT can be converted to CM-SAT by replacing each mixed OR clause with the product of two clauses involving a new variable

Example:  $(x_i \vee x_j \vee x'_k)$  is replaced by  $(x_i \vee x_j \vee v_k)(v'_k \vee x'_k)$

Clause-monotone SAT can be converted to fault detection in a circuit

First level has ANDs for all clauses with complemented variables

Second level has ORs for all clauses with uncomplemented variables, plus an OR gate with level-1 outputs as its inputs (one input to this gate is  $y$ )

Third level has one AND gate that receives all level-2 outputs as its inputs  
A test for  $y$  s-a-1 satisfies the original clause-monotone expression



# 9.5 Testing of Units with Memory

The presence of memory expands the number of required test cases

To test a sequential machine, we may need to apply different input sequences for each possible initial state

Exponentially many possible input sequences

Exponentially many possible machine states

# Testing of Memory

Simple-minded approach: Write 000 . . . 00 and 111 . . . 11 into every memory word and read out to verify proper storage and retrieval

Problems with the simple-minded approach:

- Does not test access/decoding mechanism – How do you know the intended word was written into and read from?
- Many memory faults are pattern-sensitive, where cell operation is affected by the values stored in nearby cells
- Modern high-density memories experience dynamic faults that are exposed only for specific access sequences

Memory testing continues to be an active research area

Built-in self test is the only viable approach in the long term

Challenge: Any run time testing consumes some memory bandwidth

# 9.6 Off-Line vs. Concurrent Testing

This section will be forthcoming.



# 10 Fault Masking








off the mark by Mark Parisi  
www.offthemark.com



ZERO TOLERANCE ON INTOLERANCE...

   

Oct. 2020



Part III – Faults: Logical Deviations




Slide 22




## STRUCTURE AT A GLANCE

<b>Part I — Introduction:</b> Dependable Systems (The Ideal-System View)	Goals	1. Background and Motivation 2. Dependability Attributes 3. Combinational Modeling 4. State-Space Modeling
	Models	
<b>Part II — Defects:</b> Physical Imperfections (The Device-Level View)	Methods	5. Defect Avoidance 6. Defect Circumvention 7. Shielding and Hardening 8. Yield Enhancement
	Examples	
<b>Part III — Faults:</b> Logical Deviations (The Circuit-Level View)	Methods	9. Fault Testing 10. Fault Masking
	Examples	11. Design for Testability 12. Replication and Voting
<b>Part IV — Errors:</b> Informational Distortions (The State-Level View)	Methods	13. Error Detection 14. Error Correction 15. Self-Checking Modules 16. Redundant Disk Arrays
	Examples	
<b>Part V — Malfunctions:</b> Architectural Anomalies (The Structure-Level View)	Methods	17. Malfunction Diagnosis 18. Malfunction Tolerance 19. Standby Redundancy 20. Resilient Algorithms
	Examples	
<b>Part VI — Degradations:</b> Behavioral Lapses (The Service-Level View)	Methods	21. Degradation Allowance 22. Degradation Management 23. Robust Task Scheduling 24. Software Redundancy
	Examples	
<b>Part VII — Failures:</b> Computational Breaches (The Result-Level View)	Methods	25. Failure Confinement 26. Failure Recovery 27. Agreement and Adjudication 28. Fail-Safe System Design
	Examples	

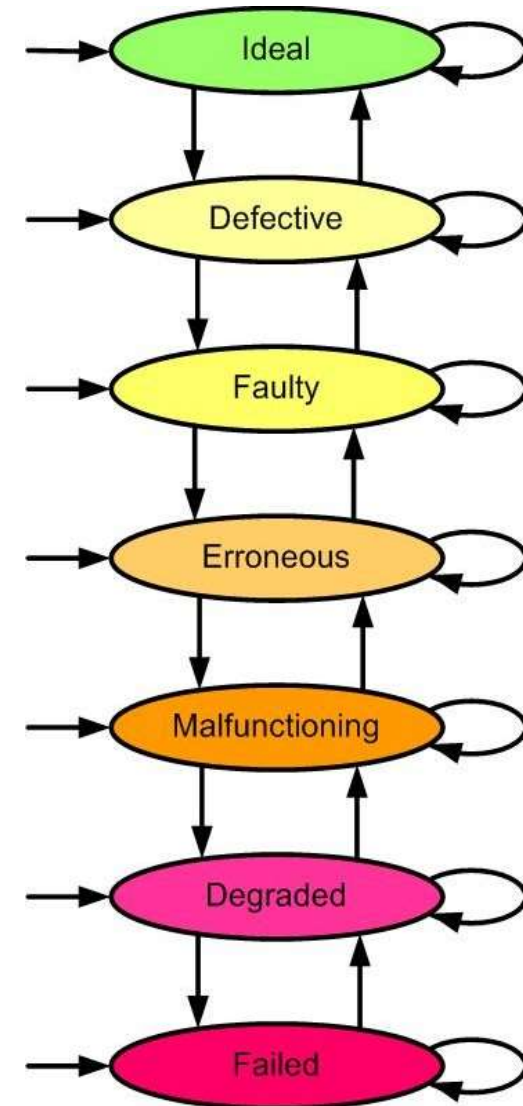


Appendix: Past, Present, and Future

# 10.1 Fault Avoidance vs. Masking

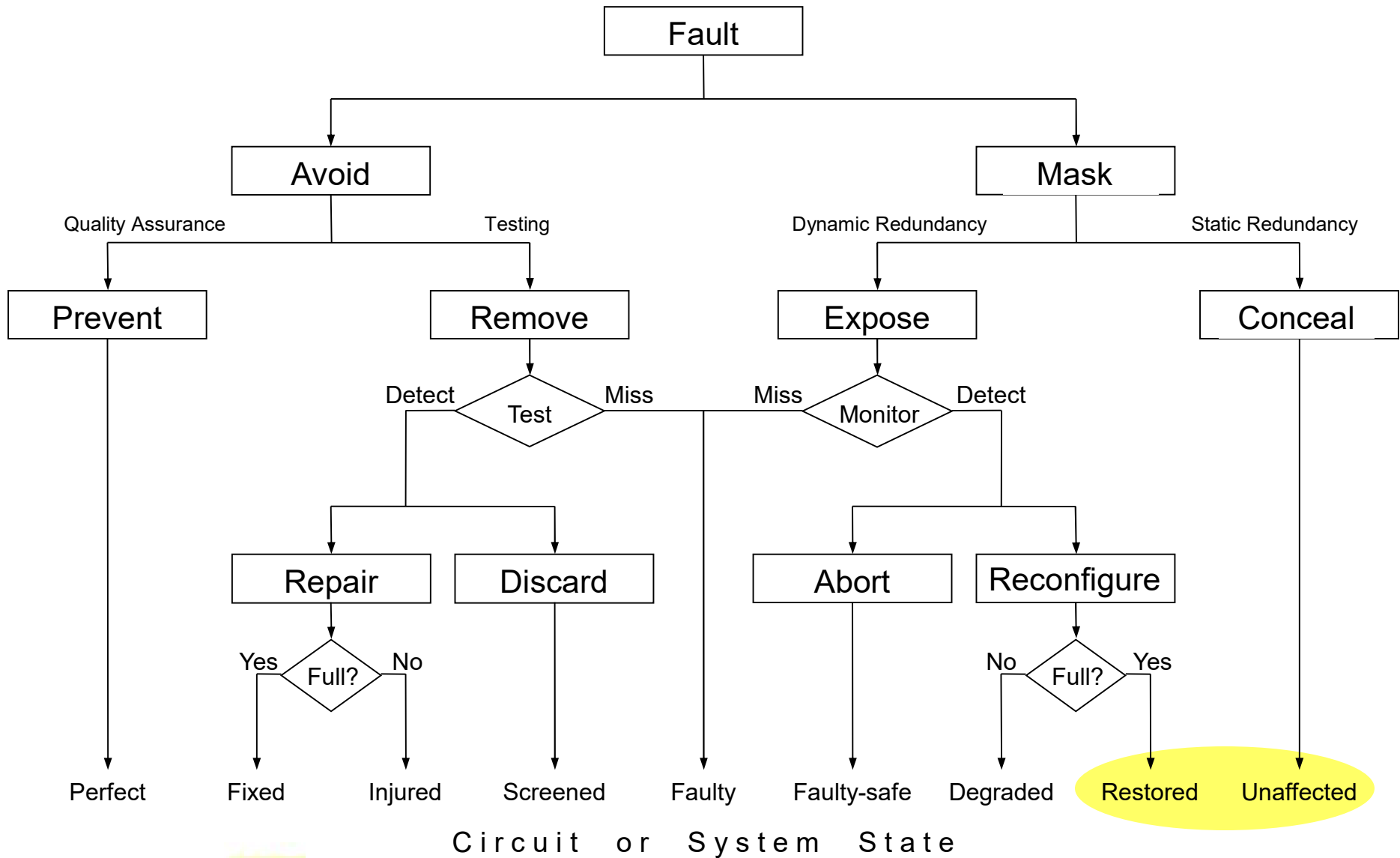



## 10.2 Interwoven Redundant Logic

 

**0 → 1** fault in *b* is critical


**0 → 1** fault in *c* or *d* is not critical (it is masked)

**1 → 0** fault in *a* or *h* is not critical (it is masked)

Even nonredundant circuits have some masking capability

Is there a way to exploit the inherent masking capabilities of logic gates to achieve general fault masking?

# How Interwoven Logic Works

 

Let  $x_1, x_2, x_3,$  and  $x_4$  be 4 copies of the signal  $x$

**1 → 0** change is critical for AND, subcritical for OR

**0 → 1** change is critical for OR, subcritical for AND


Alternating layers of ANDs and ORs can mask each other's critical faults

To mask  $h$  critical faults:

Number of gates multiplied by  $(h + 1)^2$




Gate inputs multiplied by  $h + 1$

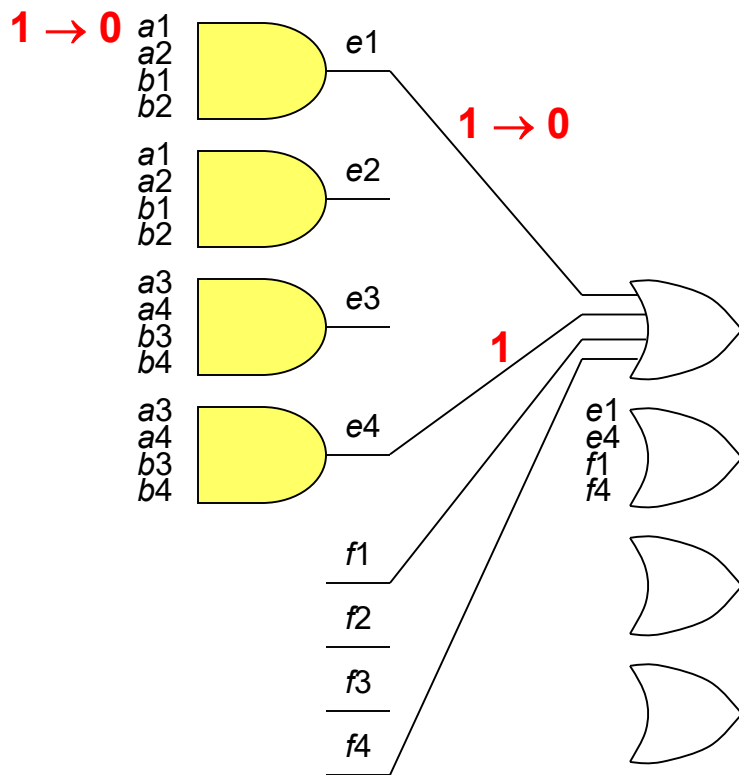For  $h = 1$ , the scheme is known as **Quadded logic**



# Interwoven Logic for Nanoelectronics

Half-adder implemented in quadded logic

  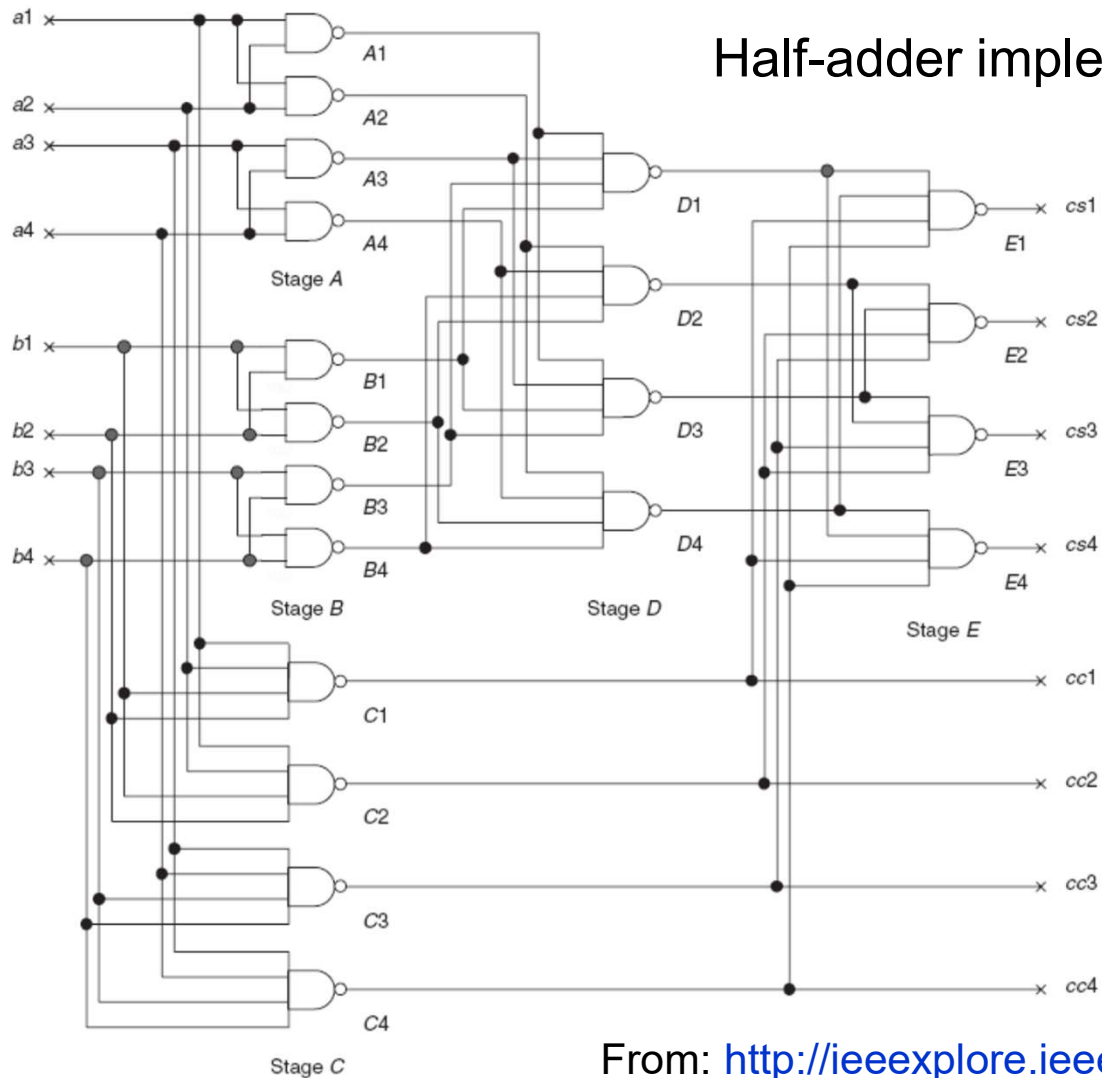


*IEEE D&T*  
 July-Aug. 2005  
 pp. 328-339

From: <http://ieeexplore.ieee.org/iel5/54/32070/01492293.pdf>


# Highly Reliable Logic with “Crummy” Relays

Moore & Shannon, 1956

- $a$ : prob [contact made | energized]
- $1 - a$ : prob [contact open | energized]
- $c$ : prob [contact made | not energized]
- $1 - c$ : prob [contact open | not energized]

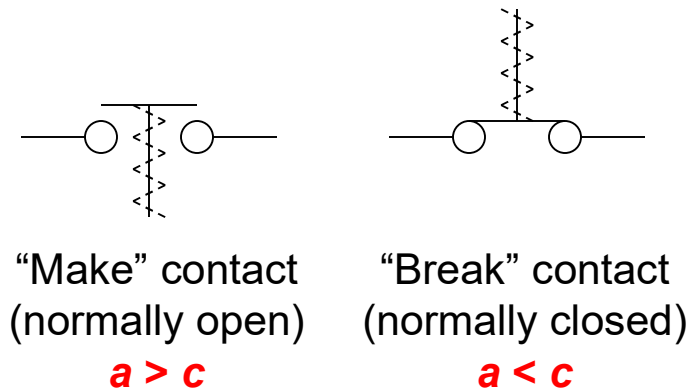


 No matter how crummy the relays (i.e., how close the values of  $a$  and  $c$ ), one can interconnect many of them in a redundant series-parallel structure to achieve arbitrarily high reliability



prob [connection made | energized] =  $2a^2 - a^4$  ( $> a$  if  $a > 0.62$ )

prob [connection made | not energized] =  $2c^2 - c^4$  (always  $< c$ )

 





# 10.3 Static Redundancy with Replication

TMR:  $R = 3R_m^2 - 2R_m^3 \stackrel{?}{>} R_m$


Condition on the module reliability:

$$R = R_m [1 + (1 - R_m)(2R_m - 1)]$$
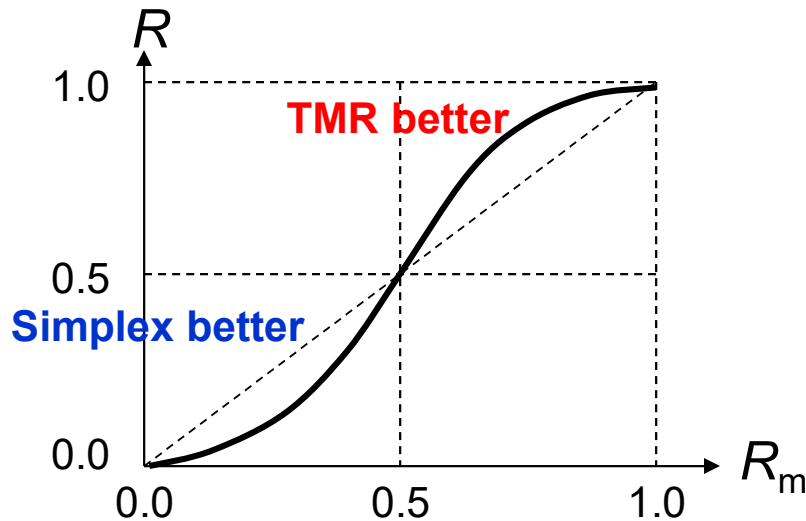 
$$(1 - R_m)(2R_m - 1) > 0 \Rightarrow R_m > 1/2$$


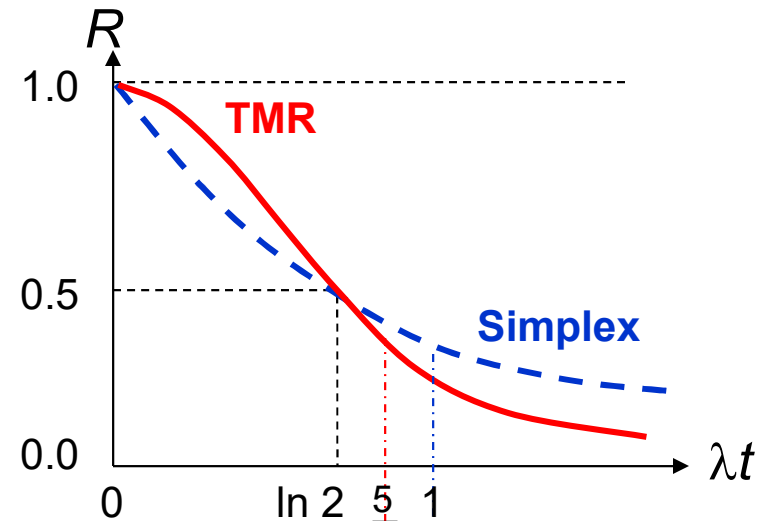
$$\begin{aligned} \text{RIF}_{\text{TMR/Simplex}} &= (1 - R_m)/(1 - R) \\ &= 1/[1 - R_m(2R_m - 1)] \end{aligned}$$




$$\begin{aligned} \text{MTTF: TMR} &= 5/(6\lambda) \\ \text{Simplex} &= 1/\lambda \end{aligned}$$
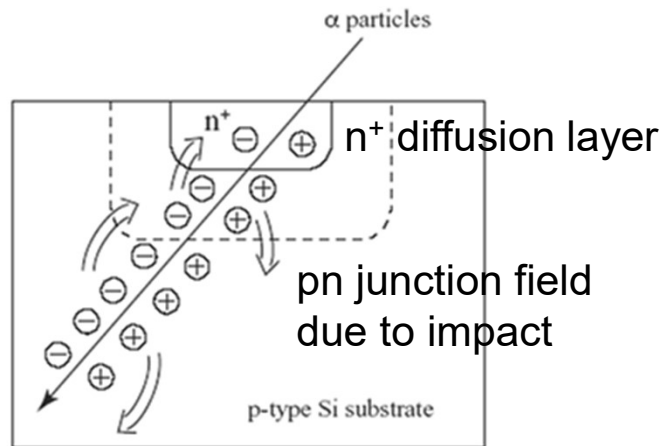
# A TMR Application and Its Bit-Voting Unit


Single-event upset (SEU) = Soft error

Change of state caused by a high-energy particle strike




SEU effect on DRAMs  
(from SANYO website)

TMR flip-flop for SEU tolerance

 

# Example: SEU Hardened Flip-Flop

 

For list of flip-flop hardening methods and their comparison, see:  
[http://klabs.org/richcontent/fpga\\_content/pages/notes/seu\\_hardening.htm](http://klabs.org/richcontent/fpga_content/pages/notes/seu_hardening.htm)

# $N$ -Modular Redundancy (NMR)


Triple-modular redundancy (TMR) can be generalized to  $N$  units

$N$ -modular redundancy (NMR) uses  $N$  modules along with a voter, with  $N$  usually being odd

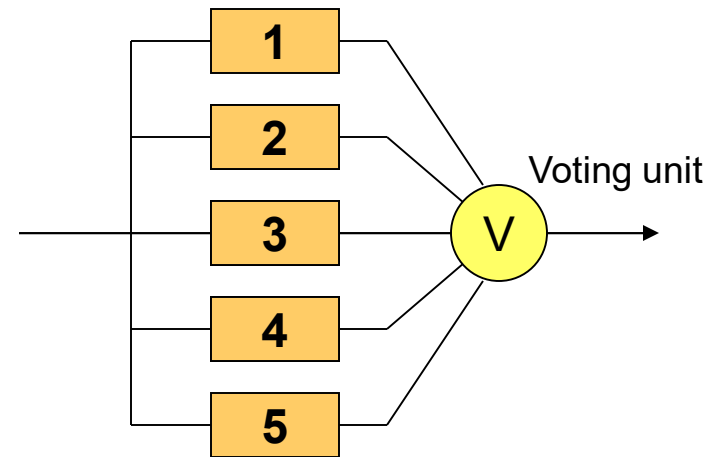Example: 5MR

Operates correctly as long as 3 of the 5 modules are healthy

Voter complexity rises rapidly with increasing  $N$



Even values of  $N$  are also feasible

Example: 4MR, with 3-out-of-4 voting

Voter masks single faults; can be designed to detect double faults


# 10.4 Dynamic and Hybrid Redundancy

## 1. Detect and replace

Dynamic redundancy (cold/hot standby)

Detection via

 - coding, watchdog timer, self-checking
- duplication (pair-and-spare)




## 2. Mask in place

Static redundancy

May revert to simplex instead of duplex

Design challenges include

 - synchronization for voting
- voting on imprecise results



## 3. Mask, diagnose, and reconfigure


Hybrid redundancy

Fault masked at output, but diagnosed

-- e.g., via comparison with voter output

Faulty circuit is replaced by spare

Becomes static upon spare exhaustion

 



# Comparing Replication Schemes

## Advantages

Less power  
(cold standby)  
Long life  
(just add spares)

Immediate masking  
High safety


Immediate masking  
Long life and  
high safety

## Drawbacks

Coverage factor  
Tolerance latency

Power/area penalty  
Voting critical

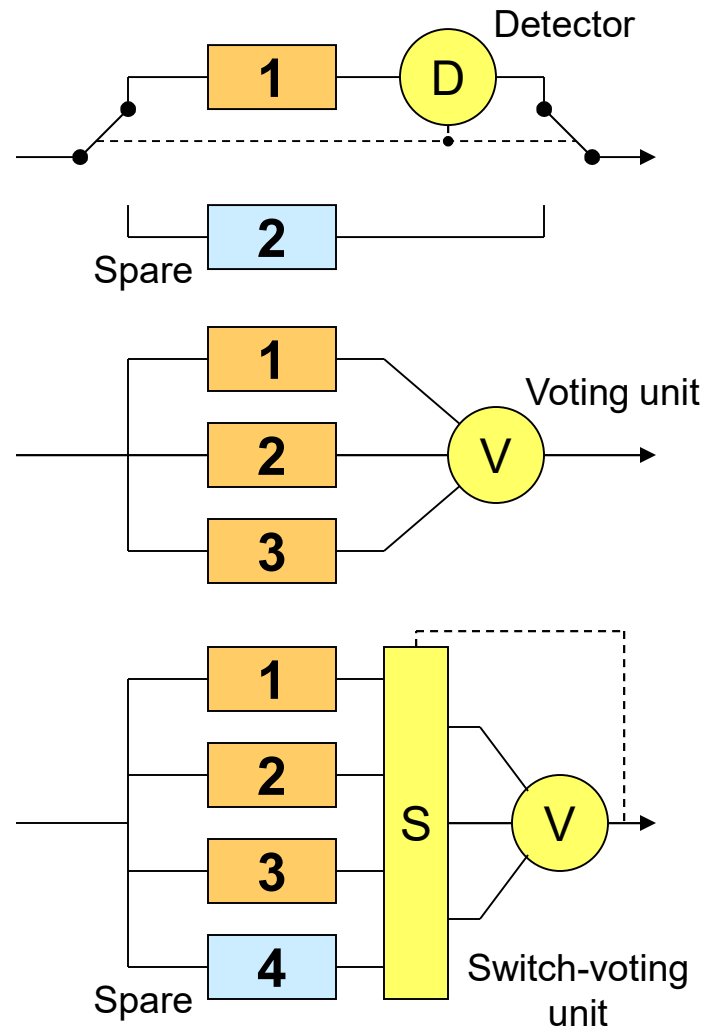Power/area penalty  
Switch-voting critical



# Switch for Standby Redundancy


Standby redundancy requires an  $n$ -to-1 switch to select the output of the currently active module

The detectors use various info to deduce fault conditions

- Error coding
- Reasonableness checks
- Watchdog timer

Once a fault has been detected, the switch reconfigures the system by flagging the faulty unit and activating next spare in sequence

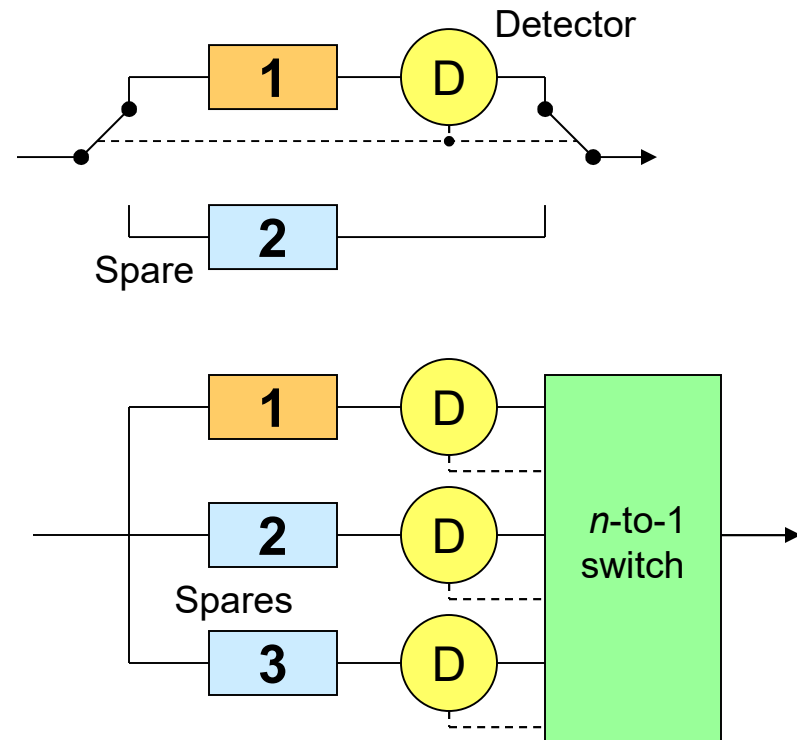If we use an  $n$ -to-2 switch and compare the two selected outputs, the configuration is known as “pair-and-spares”




# Fault Detection in Standby Redundancy

Activity monitoring

Duplication and comparison



Self-checking design

 
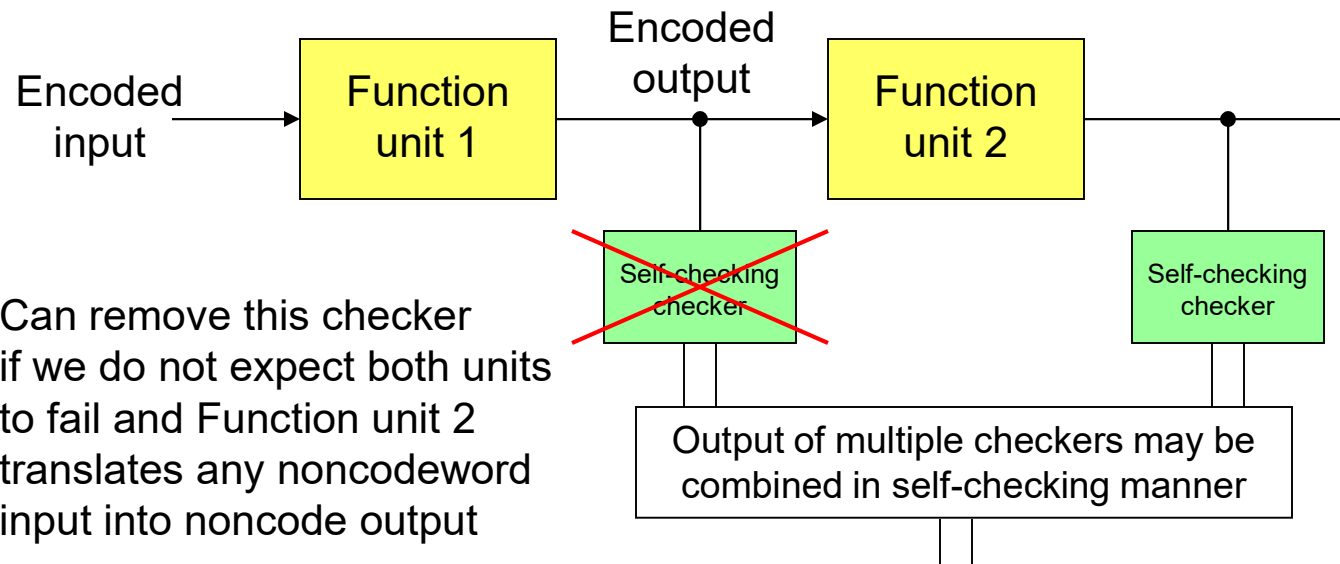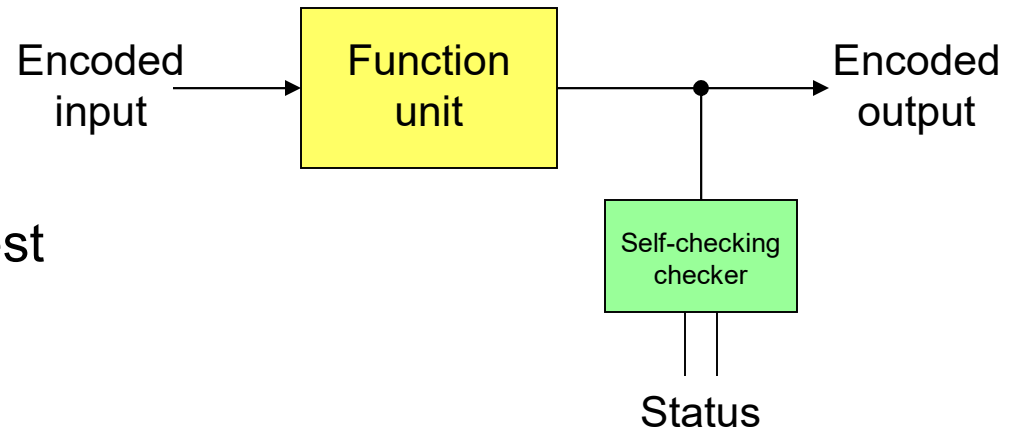
# Preview of Self-Checking Design

Covered in Chapter 15

Function unit designed such that internal faults manifest themselves as invalid outputs





Can remove this checker if we do not expect both units to fail and Function unit 2 translates any noncodeword input into noncode output

# Switch for Hybrid Redundancy

Hybrid redundancy with  $n$  active and  $s$  spare modules requires an  $(n + s)$ -to- $n$  switch to select the outputs of the active modules

Self-purging redundancy is a variant of hybrid redundancy in which all modules are active at the outset, but they are purged as they disagree with the majority output

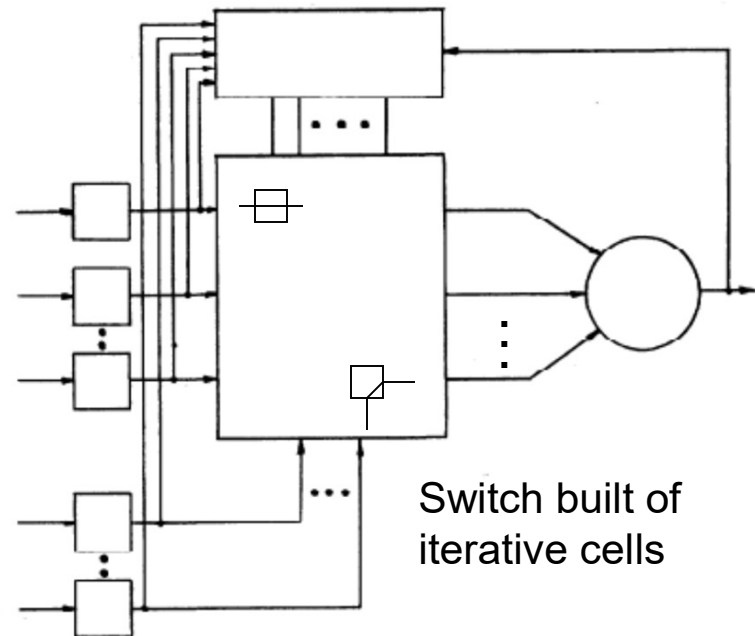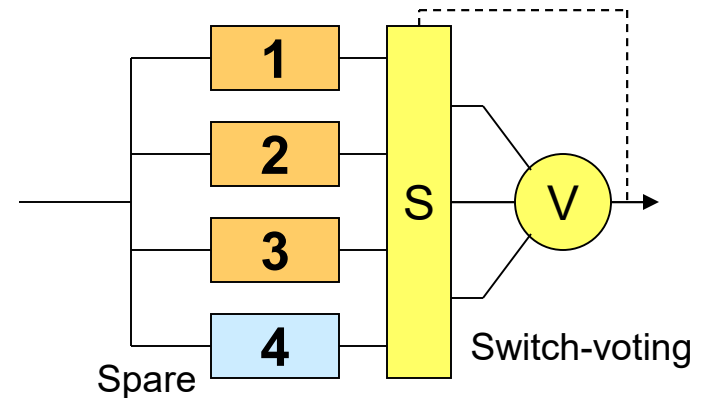Voting unit in self-purging redundancy is a threshold voter that considers the inputs with weights of 1 (active) or 0 (purged)



# 10.5 Time Redundancy

Retry upon a detected fault: particularly useful for transient faults

Recomputation not useful with permanent faults

Can make recomputation work by slightly changing the operands, but this is not always applicable

Compute  $a \times (2b)$  instead of  $(2a) \times b$


Compute  $b + a$  or  $-(-a - b)$  instead of  $a + b$


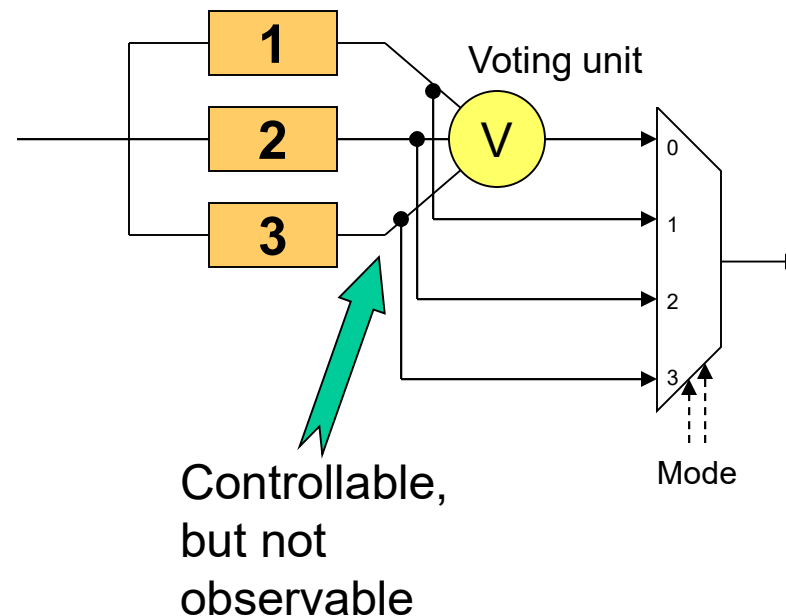
# 10.6 Variations and Complications

Static redundancy makes fault testing more challenging

For static redundancy to be effective, we must ensure that initially all redundant components are fault-free



# Applications of NMR and Hybrid Redundancy

## NASA's Space Shuttle (retired in 2012):

Used 5-way redundancy in hardware

Originally, 3 operational units + 2 spares  
(one warm, one cold)

More recently, 4 operational + 1 spare

Also, uses 2 independently developed  
software systems (Design diversity)



## Japanese Shinkansen “Bullet” Train

Triple-duplex system (6-fold redundancy)

# 11 Design for Testability




Oct. 2020



Part III – Faults: Logical Deviations





Slide 42

 

*Savage Chickens*

by Doug Savage

  

"Someone in this house flunked his earth science test because someone else in this house told him that love makes the world go around!"




**"Algebra class will be important to you later in life because there's going to be a test six weeks from now."**



## STRUCTURE AT A GLANCE

<b>Part I — Introduction:</b> Dependable Systems (The Ideal-System View)	Goals	1. Background and Motivation 2. Dependability Attributes 3. Combinational Modeling 4. State-Space Modeling
	Models	
<b>Part II — Defects:</b> Physical Imperfections (The Device-Level View)	Methods	5. Defect Avoidance 6. Defect Circumvention 7. Shielding and Hardening 8. Yield Enhancement
	Examples	
<b>Part III — Faults:</b> Logical Deviations (The Circuit-Level View)	Methods	9. Fault Testing 10. Fault Masking 11. Design for Testability 12. Replication and Voting
	Examples	
<b>Part IV — Errors:</b> Informational Distortions (The State-Level View)	Methods	13. Error Detection 14. Error Correction 15. Self-Checking Modules 16. Redundant Disk Arrays
	Examples	
<b>Part V — Malfunctions:</b> Architectural Anomalies (The Structure-Level View)	Methods	17. Malfunction Diagnosis 18. Malfunction Tolerance 19. Standby Redundancy 20. Resilient Algorithms
	Examples	
<b>Part VI — Degradations:</b> Behavioral Lapses (The Service-Level View)	Methods	21. Degradation Allowance 22. Degradation Management 23. Robust Task Scheduling 24. Software Redundancy
	Examples	
<b>Part VII — Failures:</b> Computational Breaches (The Result-Level View)	Methods	25. Failure Confinement 26. Failure Recovery 27. Agreement and Adjudication 28. Fail-Safe System Design
	Examples	

 

Appendix: Past, Present, and Future

# 11.1 The Importance of Testability

A small circuit with a limited number of inputs and outputs can be tested with a reasonable amount of effort and time

A complex unit, such as a microprocessor, cannot be tested solely based on its input/output behavior

Hence, the need for provisions in the design to facilitate testing




# 11.2 Testability Modeling

To allow detection of a fault in point A of a logic circuit, we need to:

Be able to control that point from the primary inputs

Be able to observe that point from the primary outputs

 Thus, good **testability** requires  
good **controllability** and  
good **observability**  
for every node in the circuit



# Quantifying Controllability

Controllability  $C$  of a line has a value between 0 and 1

Derive  $C$  values by proceeding from inputs ( $C = 1$ ) to outputs

Controllability transfer factor

$$CTF = 1 - \left| \frac{N(0) - N(1)}{N(0) + N(1)} \right|$$


$$C_{\text{output}} = (\sum_i C_{\text{input } i} / k) \times CTF$$

$f$ -way fan-out


A line with very low controllability is a good test point candidate

$N(0)$ : # input patterns leading to 0 output  
 $N(1)$ : # input patterns leading to 1 output



$k$ -input, 1-output components

 

 $N(0) = 7$   
 $N(1) = 1$   
 $CTF = 0.25$



  $N(0) = 1$   
 $N(1) = 7$   
 $CTF = 0.25$



# Quantifying Observability

Observability  $O$  of a line has a value between 0 and 1


Derive  $O$  values by proceeding from outputs ( $O = 1$ ) to inputs

Observability transfer factor

$$OTF = \frac{N(sp)}{N(sp) + N(ip)}$$

$$O_{\text{input } i} = O_{\text{output}} \times OTF$$


$k$ -input, 1-output components

 

$$N(sp) = 1$$

$$N(ip) = 3$$

$$OTF = 0.25$$

 


$$N(sp) = 1$$

$$N(ip) = 3$$


$$OTF = 0.25$$

$f$ -way fan-out

 

A line with very low observability is a good test point candidate

 
$N(sp)$ : # ways of sensitizing a path to output  
 $N(ip)$ : # ways of inhibiting a path to output




# Quantifying Testability

$$\text{Testability} = \text{Controllability} \times \text{Observability}$$


Controllabilities

 

Observabilities

 


Testabilities

 


Overall testability of a circuit = Average of line testabilities
 
# 11.3 Testpoint Insertion

Increase controllability and observability via the insertion of degating mechanisms and control points



 Design for dual-mode operation  
Normal mode  
Test mode








# 11.4 Sequential Scan Techniques

Increase controllability and observability via provision of mechanisms to set and observe internal flip-flops

Scan design

Shift desired states into FF



Shift out FF states to observe

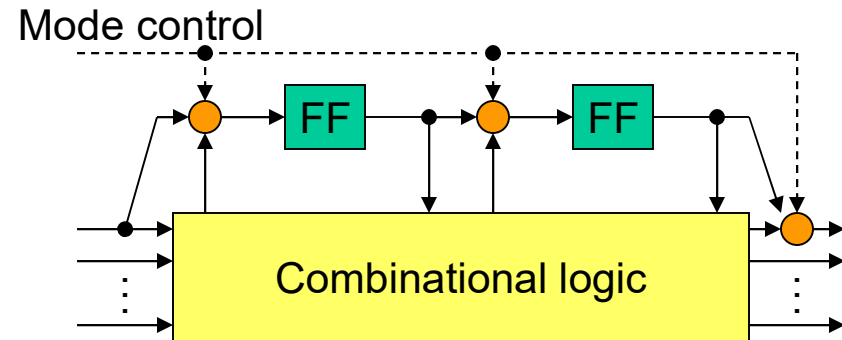  

Partial scan design:  
Mitigates the excessive overhead  
of a full scan design
 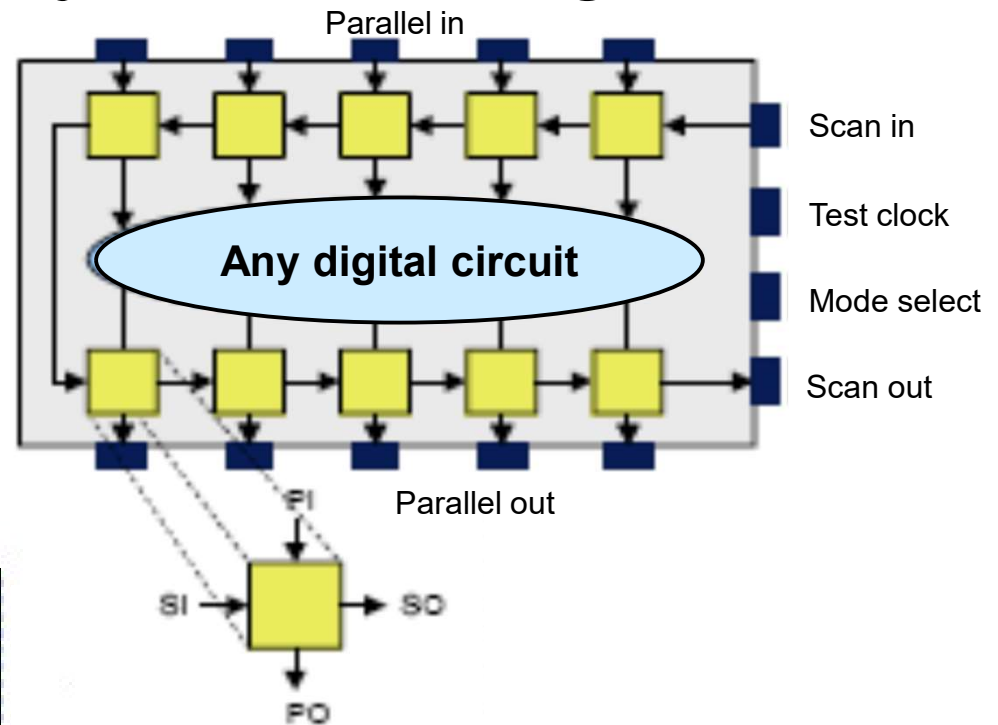
# 11.5 Boundary Scan Design


Allows us to apply arbitrary inputs to circuit parts whose inputs would otherwise not be externally accessible



Boundary scan elements of multiple parts are cascaded together into a scan path


From: [http://www.asset-intertech.com/pdfs/boundaryscan\\_tutorial.pdf](http://www.asset-intertech.com/pdfs/boundaryscan_tutorial.pdf)

# Basic Boundary Scan Cell

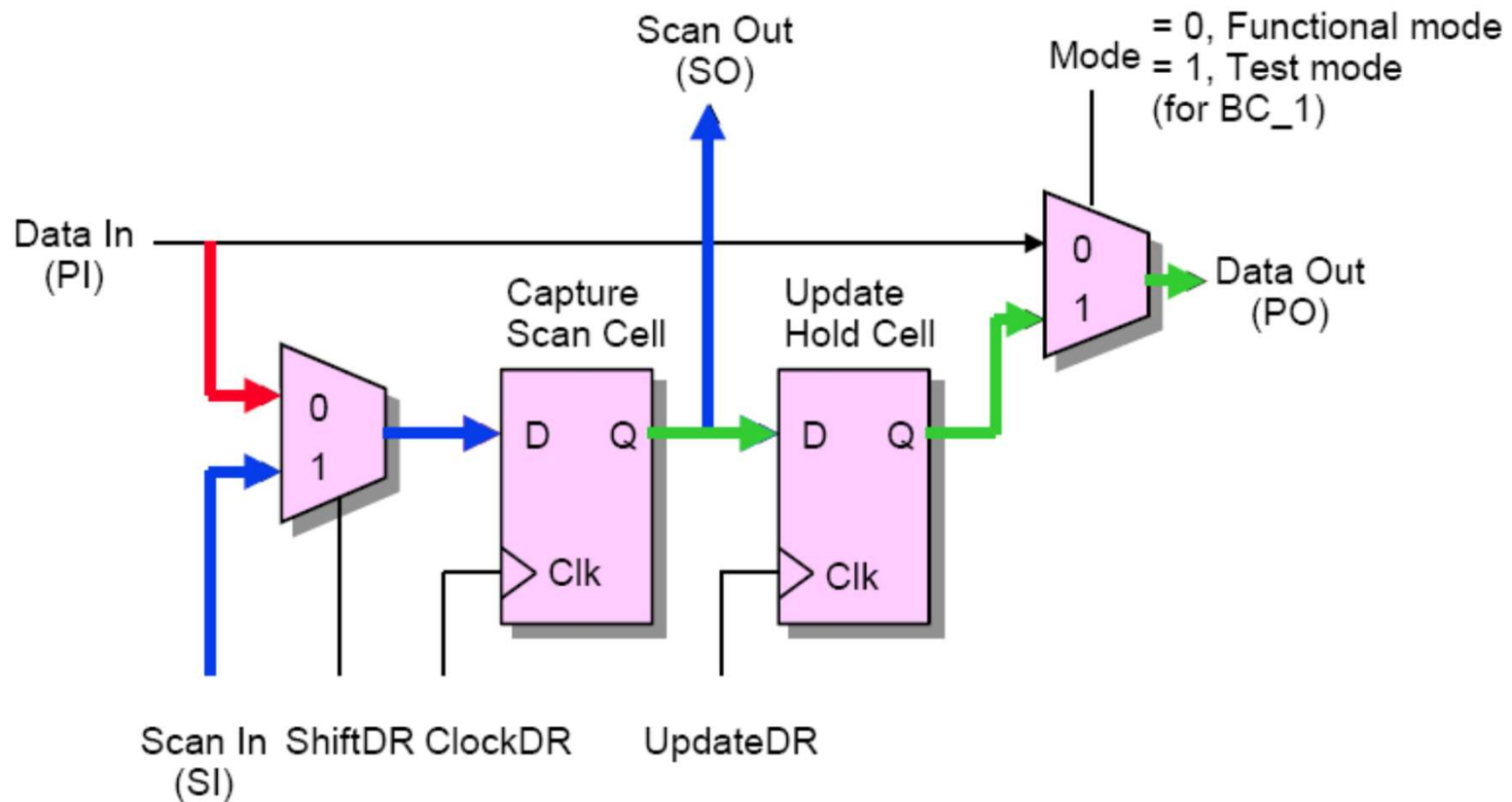

From: [http://www.asset-intertech.com/pdfs/boundaryscan\\_tutorial.pdf](http://www.asset-intertech.com/pdfs/boundaryscan_tutorial.pdf)

# 11.6 Built-in Self-Test (BIST)

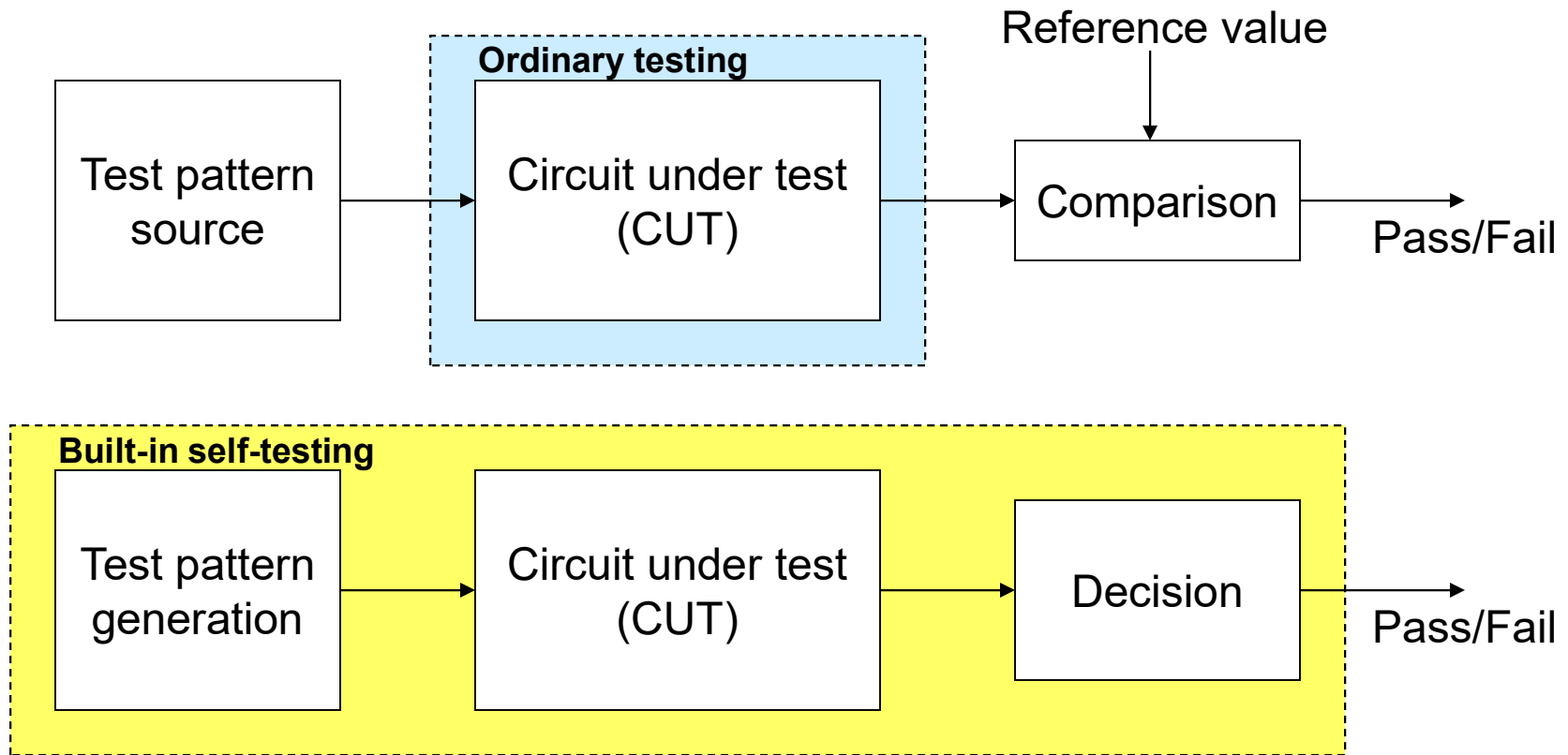

Test patterns may be generated (pseudo)randomly – e.g., via LFSRs

Decision may be based on compressed test results

# 12 Replication and Voting





"Let's try voting for the greater of the two evils this time and see what happens."

© 2000 Randy Glasbergen.  
www.glasbergen.com




"AFTER MONTHS OF SPEECHES, PROMISES, AND ACCUSATIONS, I'VE DECIDED TO JUST VOTE FOR THE GUY WITH THE COOLEST WEB SITE."



Mike Kiefe THE DENVER POST 12/24/07 www.cartoonists.com



"Fire. Bad. Those in favour?"

 


...ARE THERE TOO MANY VOTING PROGRAMMES ON TV?... YOU DECIDE



## STRUCTURE AT A GLANCE

<b>Part I — Introduction:</b> Dependable Systems (The Ideal-System View)	Goals	1. Background and Motivation 2. Dependability Attributes 3. Combinational Modeling 4. State-Space Modeling
	Models	
<b>Part II — Defects:</b> Physical Imperfections (The Device-Level View)	Methods	5. Defect Avoidance 6. Defect Circumvention 7. Shielding and Hardening 8. Yield Enhancement
	Examples	
<b>Part III — Faults:</b> Logical Deviations (The Circuit-Level View)	Methods	9. Fault Testing 10. Fault Masking 11. Design for Testability 12. Replication and Voting
	Examples	
<b>Part IV — Errors:</b> Informational Distortions (The State-Level View)	Methods	13. Error Detection 14. Error Correction 15. Self-Checking Modules 16. Redundant Disk Arrays
	Examples	
<b>Part V — Malfunctions:</b> Architectural Anomalies (The Structure-Level View)	Methods	17. Malfunction Diagnosis 18. Malfunction Tolerance 19. Standby Redundancy 20. Resilient Algorithms
	Examples	
<b>Part VI — Degradations:</b> Behavioral Lapses (The Service-Level View)	Methods	21. Degradation Allowance 22. Degradation Management 23. Robust Task Scheduling 24. Software Redundancy
	Examples	
<b>Part VII — Failures:</b> Computational Breaches (The Result-Level View)	Methods	25. Failure Confinement 26. Failure Recovery 27. Agreement and Adjudication 28. Fail-Safe System Design
	Examples	

 

Appendix: Past, Present, and Future

# 12.1 Hardware Redundancy Overview

## Data path methods:

Replication in space (costly)

- Duplicate and compare

- Triplicate and vote

- Pair-and-spare

- NMR/hybrid

Replication in time (slow?)

- Recompute and compare

- Recompute and vote

- Alternating logic

- Recompute after shift

- Recompute after swap

- Replicate operand segments

Mixed space-time replication

Monitoring (imperfect coverage)

- Watchdog timer

- Activity monitor

Low-redundancy coding

- Parity prediction

- Residue checking

- Self-checking design

## Control unit methods:


- Coding of control signals

- Control-flow watchdog

- Self-checking design


## Glue logic methods:

- Self-checking design

 

 
# 12.2 Replication in Space


The following schemes have already been discussed in connection with fault masking




Duplicate and compare

 

Triplicate and vote

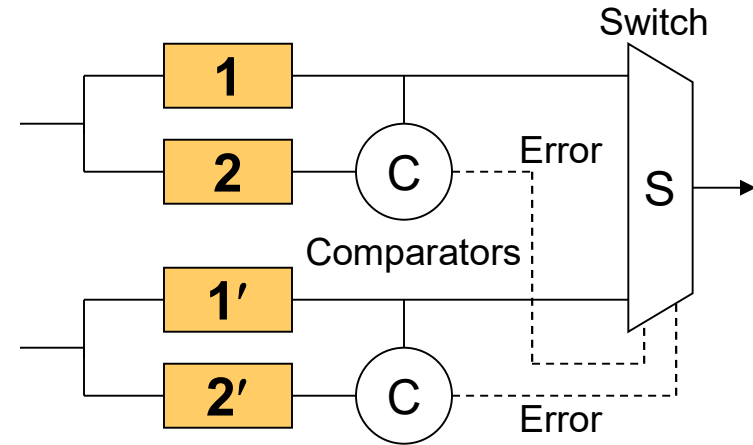

Pair-and-spare

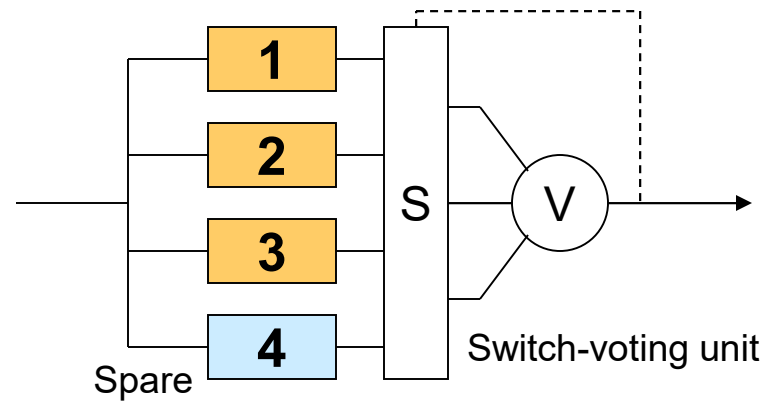

NMR/Hybrid

# TMR with Imperfect Voting Unit

$$R = R_v(3R_m^2 - 2R_m^3) \stackrel{?}{>} R_m$$

Condition on the voting unit reliability

$$R_v > 1 / [3R_m - 2R_m^2]$$

$$dR_v^{\min} / dR_m = (-3 + 4R_m) / (3R_m - 2R_m^2)^2$$

Condition on the module reliability



$$\frac{3 - \sqrt{9 - 8/R_v}}{4} < R_m < \frac{3 + \sqrt{9 - 8/R_v}}{4}$$

Example:  $R_v = 0.95$  requires that

$$0.56 < R_m < 0.94$$

When  $R_v = 1 - \varepsilon$  is close to 1, we have
  
$$1/R_v \approx 1 + \varepsilon \text{ and } (1 - 8\varepsilon)^{0.5} \approx 1 - 4\varepsilon, \text{ leading to } 0.5 + \varepsilon < R_m < 1 - \varepsilon$$



# TMR with Compensating Faults

$R_m = 1 - p_0 - p_1$  (0- and 1-fault probabilities)


$$R = (3R_m^2 - 2R_m^3) + 6p_0p_1R_m$$

Example:  $R_m = 0.998$ ,  $p_0 = p_1 = 0.001$

$$R = \frac{0.999,984}{\text{Basic TMR}} + \frac{0.000,006}{\text{Compensation}} = 0.999,990$$

$$\text{RIF}_{\text{TMR/Simplex}} = 0.002 / 0.000,016 = 125$$

 
$$\text{RIF}_{\text{Compen/TMR}} = 0.000,016 / 0.000,010 = 1.6$$



 
# 12.3 Replication in Time

Can be slow, but in many control applications, extra time is available

Interleaving of the primary and duplicate computations saves time



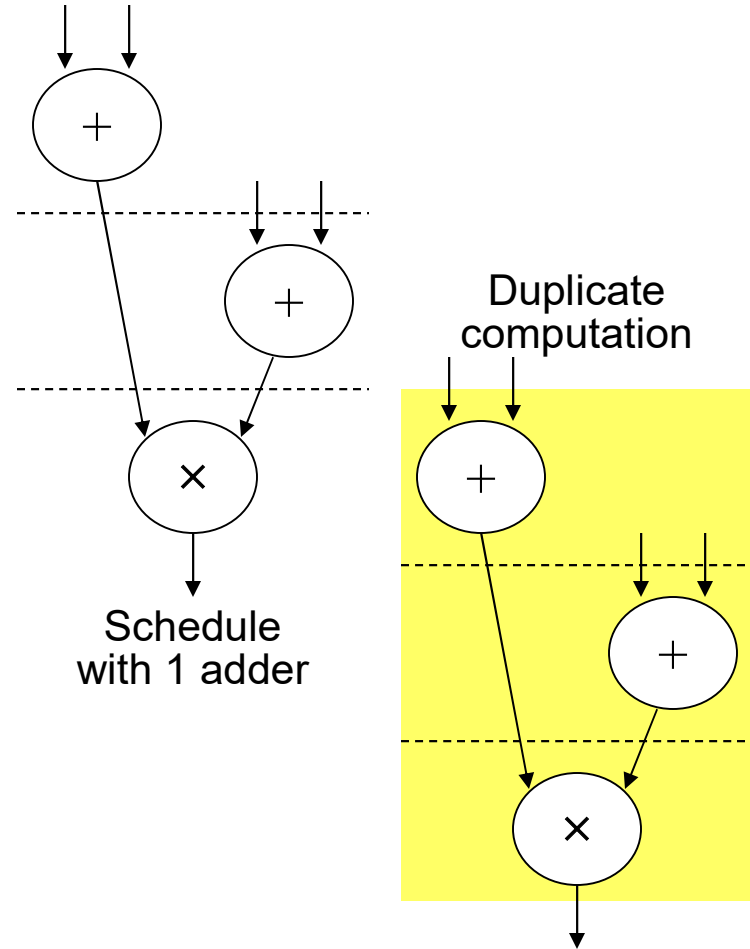Computation flowgraph, and schedule with 2 adders




Schedule with 1 adder
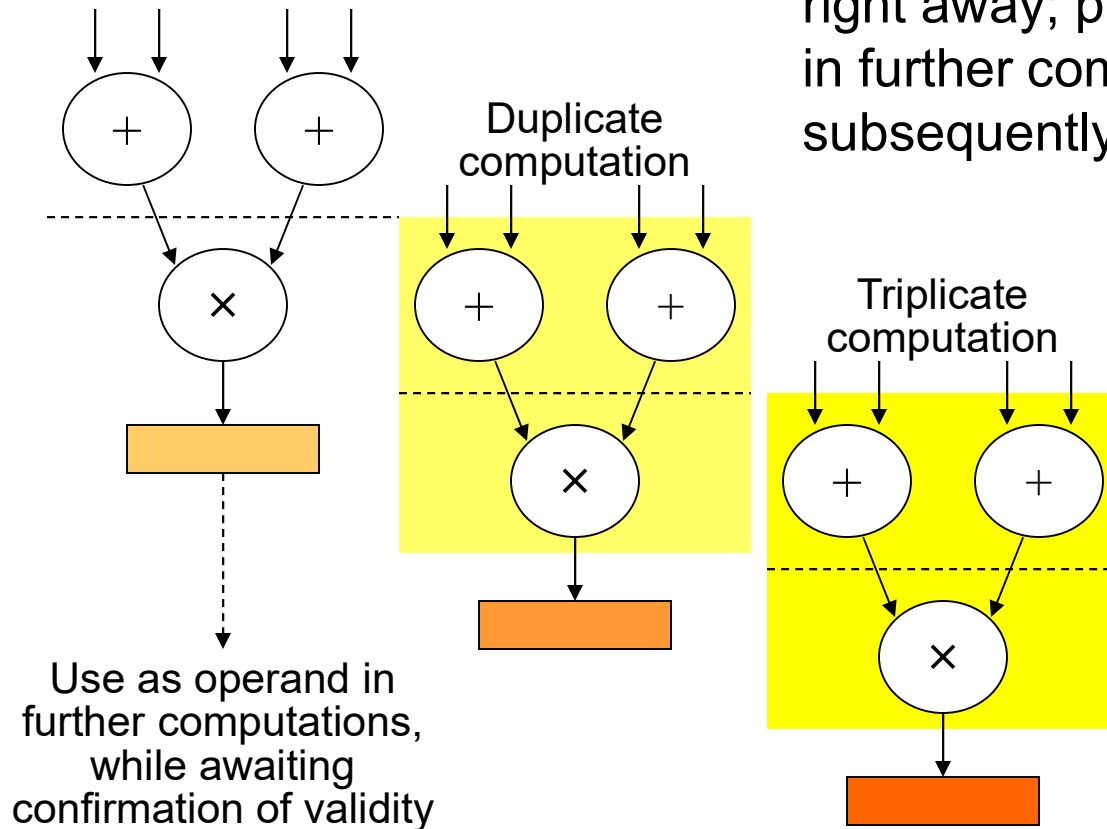
# Recompute and Compare/Vote

Repeat computation and store the results for comparison or voting

Comparison or voting need not be done right away; primary result may be used in further computations, with the result subsequently validated, if appropriate




On a simultaneous multithreading architecture, multiple instruction streams may be interspersed

Some Cray machines take advantage of extensive hardware resources to execute instructions twice



 
# 12.4 Mixed Space/Time Replication


Instead of duplicating the computation with no hardware change (slow) or duplicating the entire hardware (costly), we can add some hardware to make the interleaved recomputations more efficient



 
Recomputation with same hardware resources ( $T = 5$ , excluding compare time)



 Consider the effect of including a second adder



 Recomputation with the inclusion of an extra adder ( $T = 3$ , excluding compare time)




# 12.5 Switching and Voting Units

We begin with some simple voting unit designs:

If in the case of 3-way disagreement any of the inputs can be chosen, then a simple design is possible

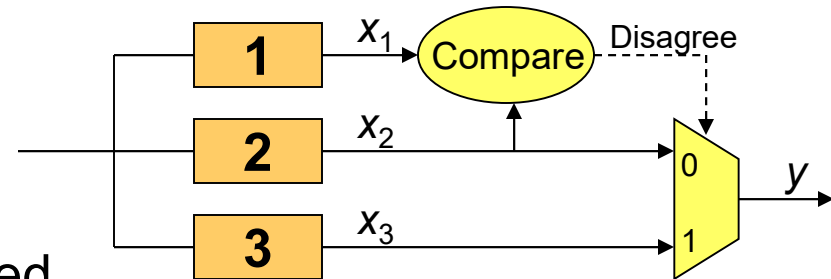This design can be readily generalized to a larger number of inputs



One can perform pseudo voting that yields the median of 3 analog signals (Dennis, N.G., *Microelectronics and Reliability*, Aug. 1974)


Median and mean voting are also possible with digital signals

# Implementing a Bit-Voting Unit

TMR bit-voting:  $y = x_1x_2 \vee x_2x_3 \vee x_3x_1$   
 (carry output of a single-bit full-adder)

What about 5MR, 7MR?

 Gate-level design quickly explodes in size




Other designs are also possible

Arithmetic: add the bits, compare to threshold



Mux-based

Selection-based (majority of bit values is their median)

 
3-out-of-5 voting unit built of 2-input gates



  Two mux-based designs for a 3-out-of-5 bit-voting unit


 
# Complexity of Different Bit-Voting Unit Designs




Cost of majority bit-voting units as a function of the number  $n$  of inputs

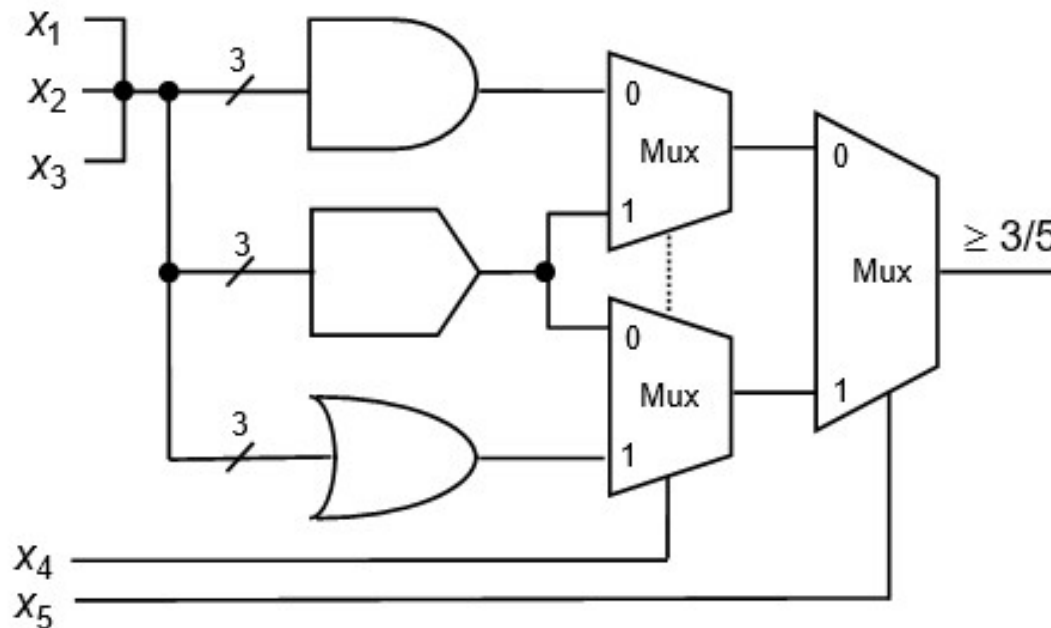
# Majority-Friendly Nanotechnologies

Certain new nanotechnologies offer efficient majority gates

Can we use majority gates as building-blocks in realizing voters?




# Recursive Construction of Large Voters

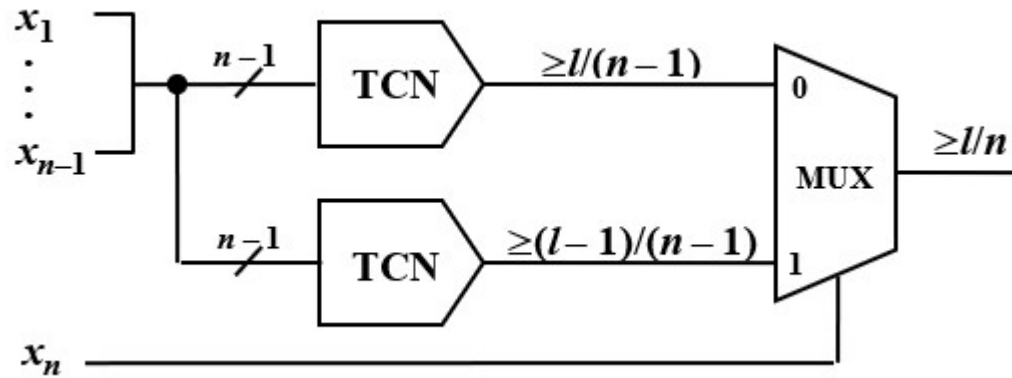

At-least- $l$ -out-of- $n$  threshold counting network built from a multiplexer and two smaller threshold counting networks

Recursively-built 5-out-of-9 voter

 

# Voting at the Word Level

Using bit-by-bit voting may be dangerous

$$x_1 = 0 \ 0$$

$$x_2 = 1 \ 0$$

$$x_3 = 1 \ 1$$

$$\hline y = 1 \ 0$$

One might think that in this example, any of the module outputs could be correct, so that producing 1 0 at the output isn't all that wrong

However, with bit-by-bit voting, the output may be different from all inputs

$$x_1 = 0 \ 0 \ 0$$

$$x_2 = 1 \ 0 \ 1$$

$$x_3 = 1 \ 1 \ 0$$

$$\hline y = 1 \ 0 \ 0$$

Design of bit- and word-voting networks discussed in:  
Parhami, B., "Voting Networks," *IEEE TR*, Aug. 1991




# 12.6 Variations and Design Issues


**NMR/simplex:** Voting unit is replaced with a unit that can also detect disagreements

When a faulty unit is detected, that unit and one other unit are removed from service

 This makes all votes unambiguous and also improves systems lifetime



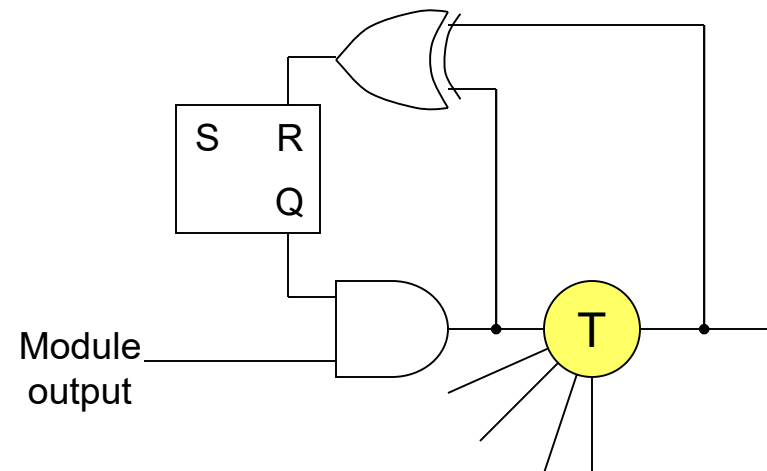**Self-purging redundancy:** Modules purged when they disagree with the output and the threshold of the voting unit is adjusted accordingly (purged modules produce 0 outputs)



# Alternating Logic: Basic Ideas

Transmission of data over unreliable wires or buses

Send data; store at receiving end


Send bitwise complement of data

Compare the two versions

Detects wires s-a-0 or s-a-1, as well as many transients

The *dual* of a Boolean function  $f(x_1, x_2, \dots, x_n)$  is another function  $f_d(x_1, x_2, \dots, x_n)$  such that  $f_d(x_1', x_2', \dots, x_n') = f'(x_1, x_2, \dots, x_n)$

 Fact: Obtain the dual of  $f$  by exchanging AND and OR operators in its logical expression. For example, the dual of  $f = ab \vee c$  is  $f_d = (a \vee b)c$




Advantages of this approach compared with duplication include a smaller probability of common errors
 
# Alternating Logic: Self-Dual Functions

A function  $f$  is self-dual if  $f(x_1, x_2, \dots, x_n) = f_d(x_1, x_2, \dots, x_n)$

For example, both the sum  $a \oplus b \oplus c$  and carry  $ab \vee bc \vee ca$  outputs of a full-adder are self-dual functions



With a self-dual function  $f$ , the functions  $f$  and  $f_d$  in the diagram above can be computed by using the same circuit twice (time redundancy)

Many functions of practical interest are self-dual


**Examples** (proofs left as exercise)

A  $k$ -bit binary adder, with  $2k + 1$  inputs and  $k + 1$  outputs, is self-dual

So are 1's-complement and 2's-complement versions of such an adder
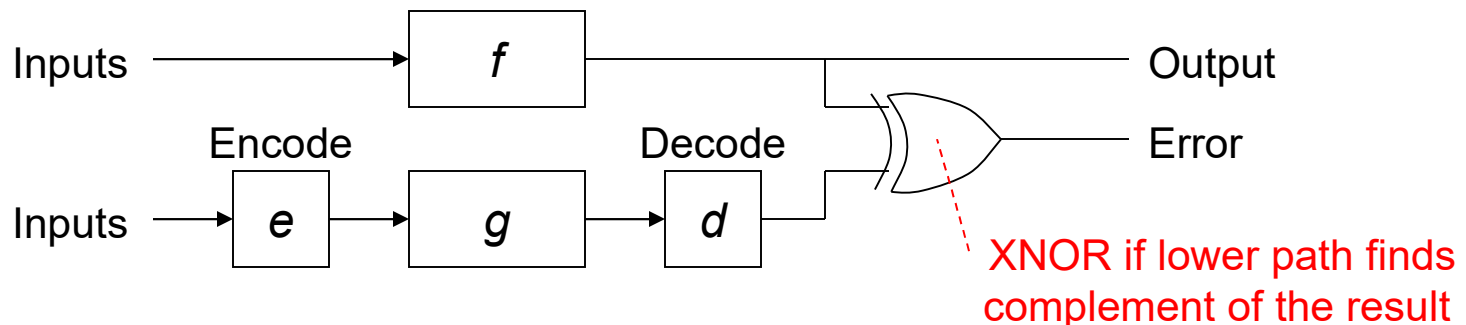
# Recomputing with Transformed Operands

Alternating logic is a special case of the following general scheme, with its encoding and decoding functions being bitwise complementation



## Recompute after shift


When  $f$  is binary addition, we can use shifts for encoding and decoding  
Shifting causes the adder circuits to be exercised differently each time  
Originally proposed for ALUs with bit-slice organization

## Recompute after swap

When  $f$  is binary addition, we can use swaps for encoding and decoding  
Swap the two operands; e.g., compute  $b + a$  instead of  $a + b$   
Swap upper and lower halves of the two operands (modified adder)
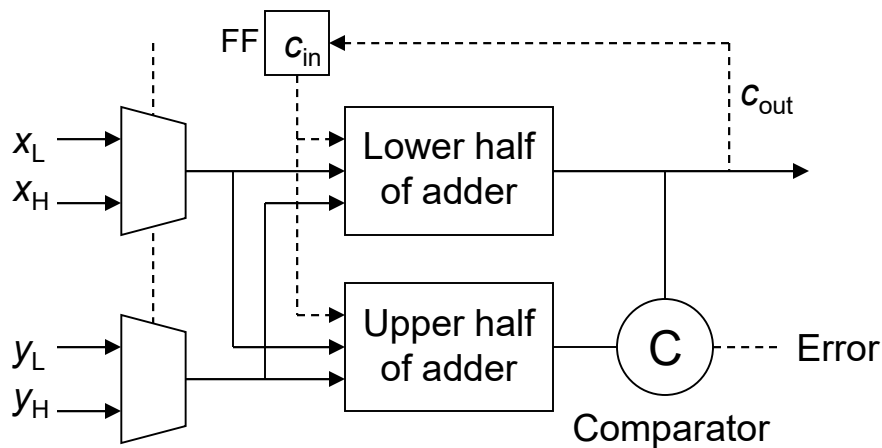
# Time-Redundant, Segmented Addition


Instead of using a  $k$ -bit adder twice for error detection or 3 times for error correction, one can segment the operands into 2 or 3 parts and similarly segment the adder; perform replicated addition on operand segments and use comparison/voting to detect/correct error



Sum computed in two cycles:  
The lower half in cycle 1, and  
the upper half in cycle 2

Various other segmentation schemes have been suggested

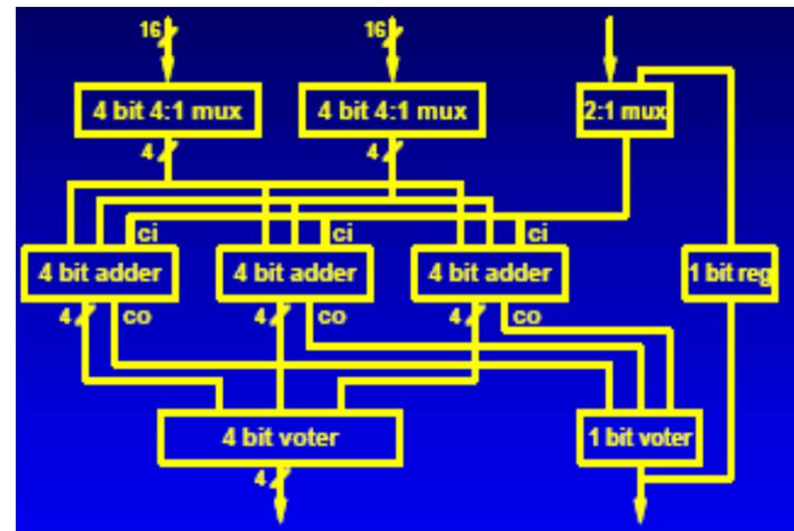**Example:** 16-bit adder with 4-way segmentation and voting



Townsend, Abraham, and Swartzlander, 2003