

Fault-Tolerant Computing

Dealing with
Low-Level
Impairments



About This Presentation

This presentation has been prepared for the graduate course ECE 257A (Fault-Tolerant Computing) by Behrooz Parhami, Professor of Electrical and Computer Engineering at University of California, Santa Barbara. The material contained herein can be used freely in classroom teaching or any other educational setting. Unauthorized uses are prohibited. © Behrooz Parhami




Edition	Released	Revised	Revised
First	Oct. 2006		

Fault Masking





ZERO TOLERANCE ON INTOLERANCE...

   

Multilevel Model

Component



Logic

Information


System

Service

Result

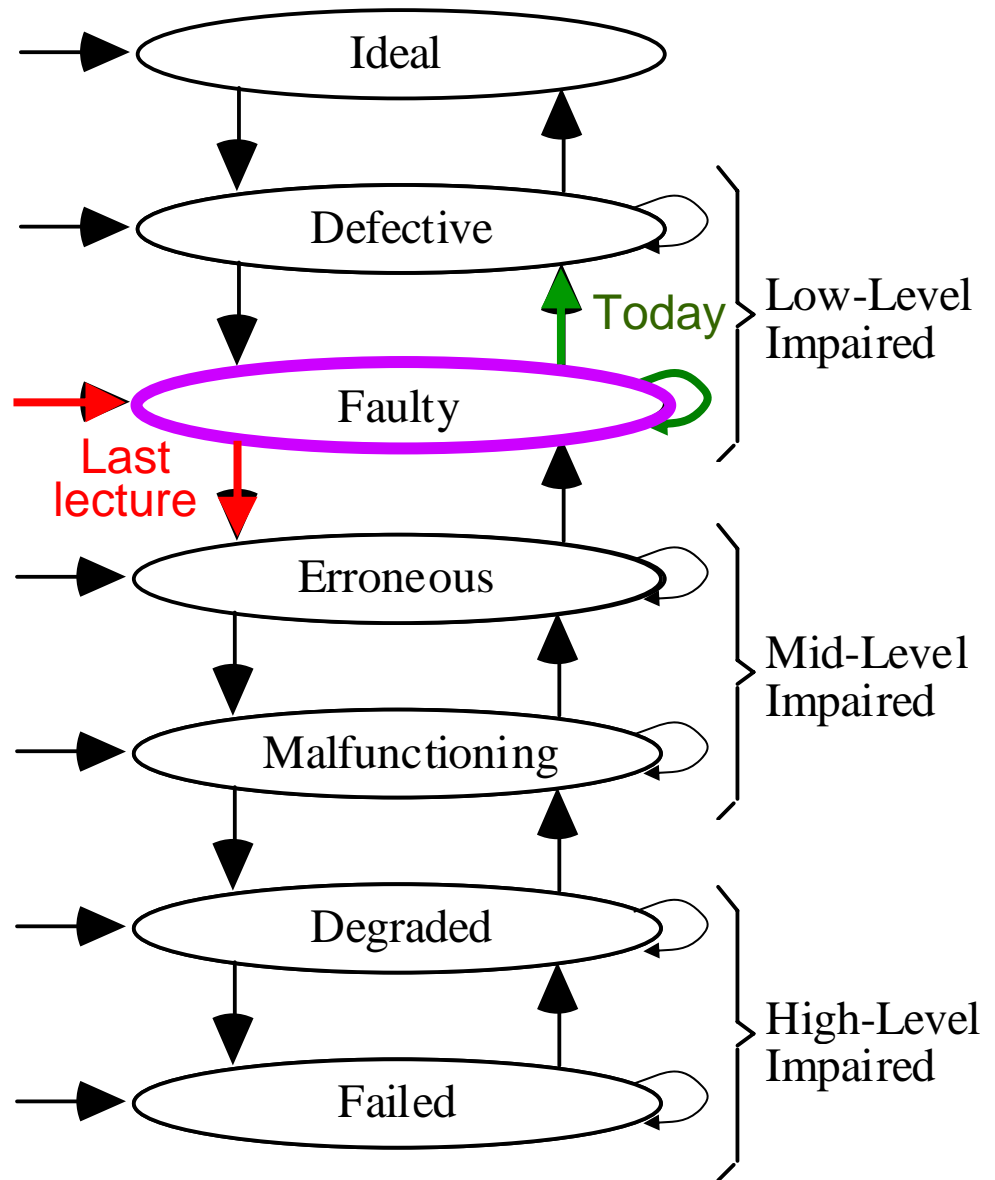 

Handling Faults

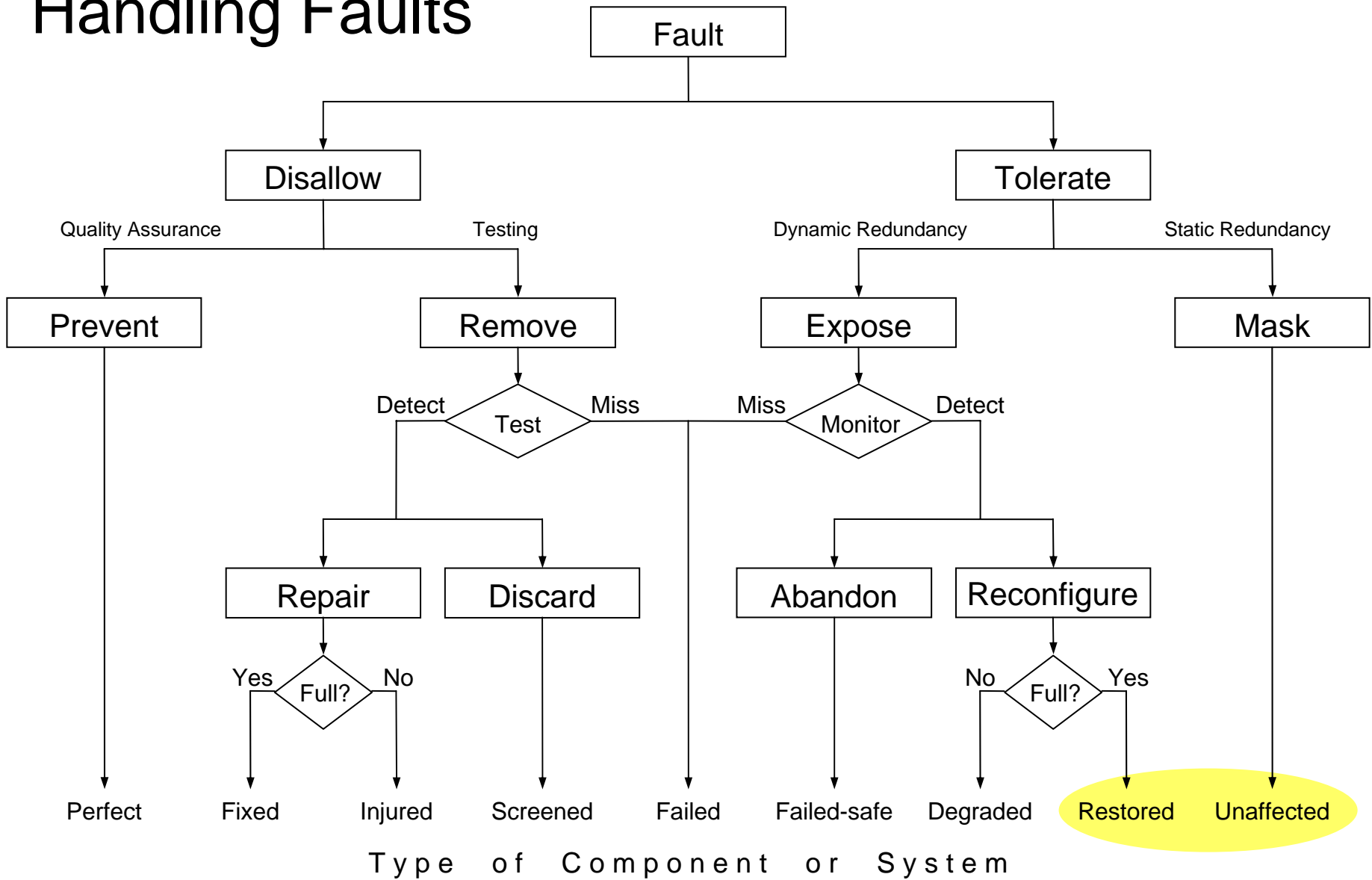

Type of Component or System


Some Options for Fault Tolerance

1. Detect and replace

Dynamic redundancy (cold/hot standby)

Detection via

 - coding, watchdog timer, self-checking
- duplication (pair-and-spare)




2. Mask

Static redundancy

May revert to simplex instead of duplex

Design challenges include

 - synchronization for voting
- voting on imprecise results



3. Mask, diagnose, and reconfigure


Hybrid redundancy

Fault masked at output, but diagnosed

-- e.g., via comparison with voter output

Faulty circuit is replaced by spare

Becomes static upon spare exhaustion

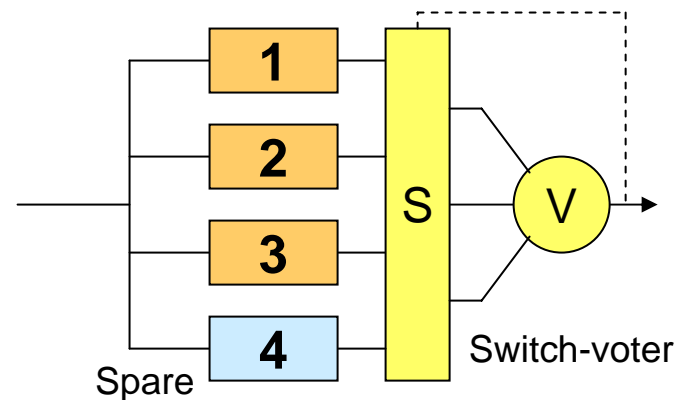

Comparing Fault Tolerance Schemes

Advantages

Less power
(cold standby)
Long life
(just add spares)

Immediate masking

High safety

Immediate masking

Long life and
high safety

Drawbacks

Coverage factor




Tolerance latency

Power/area penalty


Voter critical

Power/area penalty

Switch-voter critical

   

Inherent Fault Masking in Logic Circuits

 

0 → 1 fault in *b* is critical


0 → 1 fault in *c* or *d* is not critical (it is masked)

1 → 0 fault in *a* or *h* is not critical (it is masked)


Even nonredundant circuits have some masking capability

Is there a way to exploit the inherent masking capabilities of logic gates to achieve fault tolerance?

Interwoven Redundant Logic

 

 Let $x_1, x_2, x_3,$ and x_4 be 4 copies of the signal x



1 → 0 change is critical for AND, subcritical for OR

0 → 1 change is critical for OR, subcritical for AND

Alternating layers of ANDs and ORs can mask each other's critical faults

To mask h critical faults:



Number of gates multiplied by $(h + 1)^2$

Gate inputs multiplied by $h + 1$

For $h = 1$, the scheme is known as **Quadded logic**

Interwoven Logic for Nanoelectronics

Half-adder implemented in quadded logic

 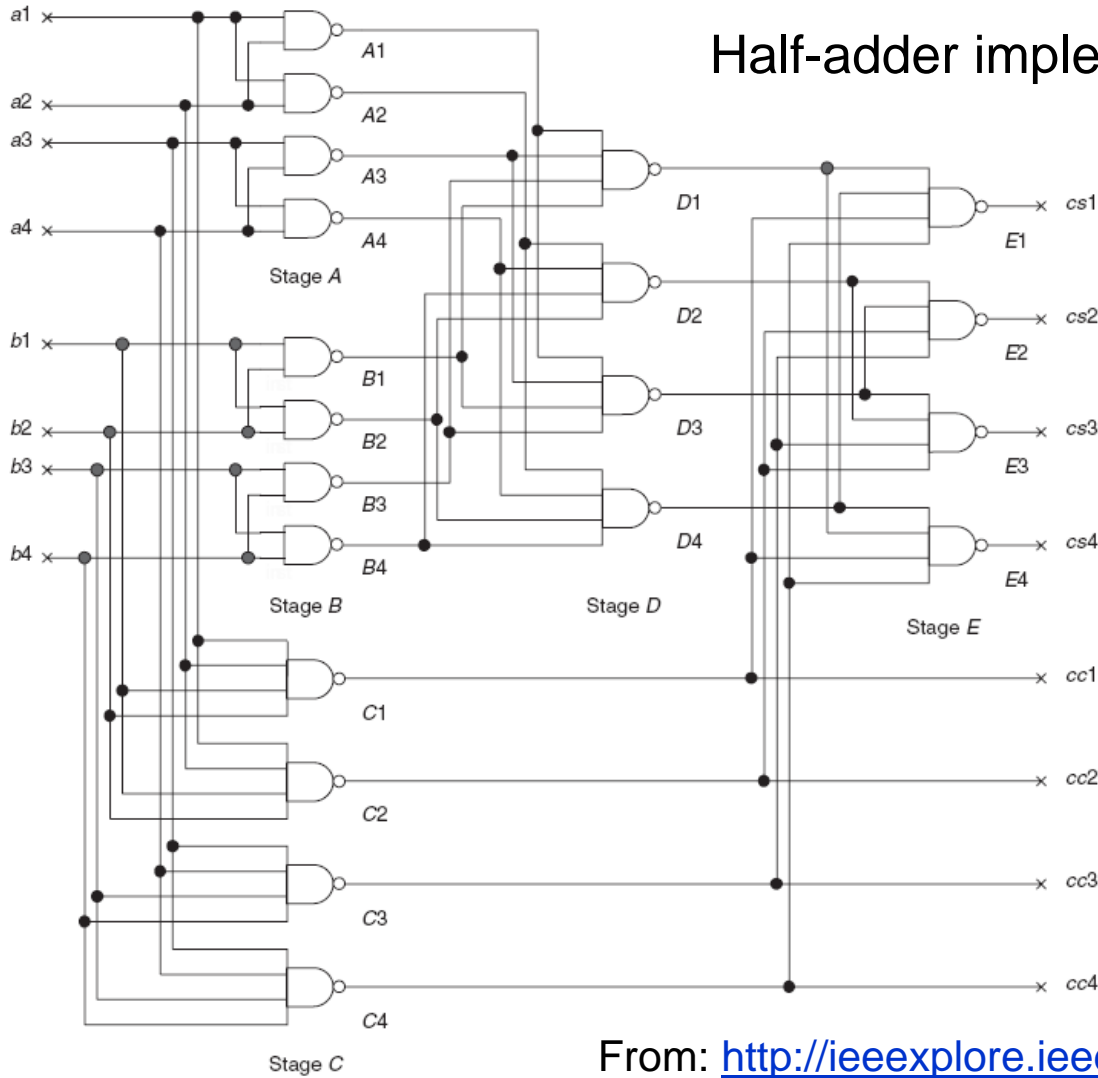

IEEE D&T
 July-Aug. 2005
 pp. 328-339

From: <http://ieeexplore.ieee.org/iel5/54/32070/01492293.pdf>


Highly Reliable Logic with “Crummy” Relays

Moore & Shannon, 1956

a : prob [contact made | energized]

c : prob [contact made | not energized]

 No matter how crummy the relays
(i.e., how close the values of a and c),
one can interconnect many of them in
a redundant series-parallel structure
to achieve arbitrarily high reliability




“Make” contact
(normally open)

$$a > c$$

“Break” contact
(normally closed)

$$a < c$$

 




TMR with Perfect Voter

$$R = 3R_m^2 - 2R_m^3 \stackrel{?}{>} R_m$$

Condition on the module reliability:

$$R = R_m [1 + (1 - R_m)(2R_m - 1)]$$
   
$$(1 - R_m)(2R_m - 1) > 0 \Rightarrow R_m > 1/2$$



$$\begin{aligned} \text{RIF}_{\text{TMR/Simplex}} &= (1 - R_m)/(1 - R) \\ &= 1/[1 - R_m(2R_m - 1)] \end{aligned}$$

$$\begin{aligned} \text{MTTF: TMR} &= 5\lambda/6 \\ \text{Simplex} &= \lambda \end{aligned}$$

TMR with Imperfect Voter

$$R = R_v(3R_m^2 - 2R_m^3) \stackrel{?}{>} R_m$$

Condition on the voter reliability



$$R_v > 1 / [3R_m - 2R_m^2]$$

$$dR_v^{\min} / dR_m = (-3 + 4R_m) / (3R_m - 2R_m^2)^2$$

Condition on the module reliability

$$\frac{3 - \sqrt{9 - 8/R_v}}{4} < R_m < \frac{3 + \sqrt{9 - 8/R_v}}{4}$$

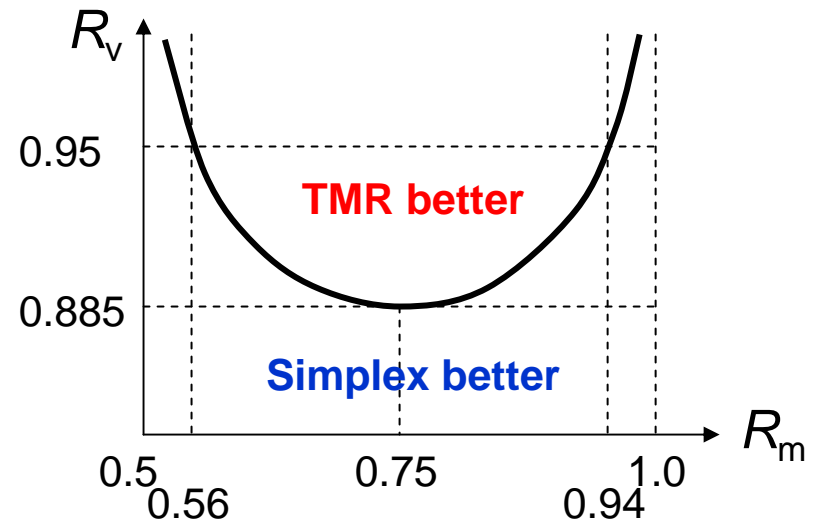 Example: $R_v = 0.95$ requires that
 $0.56 < R_m < 0.94$



TMR with Compensating Faults

$$R_m = 1 - p_0 - p_1 \quad (0\text{- and }1\text{-fault probabilities})$$


$$R = (3R_m^2 - 2R_m^3) + 6p_0p_1R_m$$

Example: $R_m = 0.998$, $p_0 = p_1 = 0.001$

$$R = \frac{0.999,984}{\text{Basic TMR}} + \frac{0.000,006}{\text{Compensation}} = 0.999,990$$

$$\text{RIF}_{\text{TMR/Simplex}} = 0.002 / 0.000,016 = 125$$
 
$$\text{RIF}_{\text{Compen/TMR}} = 0.000,016 / 0.000,010 = 1.6$$



Implementing a Bit-Voter

TMR bit-voting: $y = x_1x_2 \vee x_2x_3 \vee x_3x_1$
 (carry output of a single-bit full-adder)

What about 5MR, 7MR?


Gate-level design quickly explodes in size

Other designs are also possible


Arithmetic: add the bits, compare to threshold

Mux-based


 
Selection-based (majority of bit values is their median)




3-out-of-5 voter built of 2-input gates

 

  Two mux-based designs for a 3-out-of-5 bit-voter



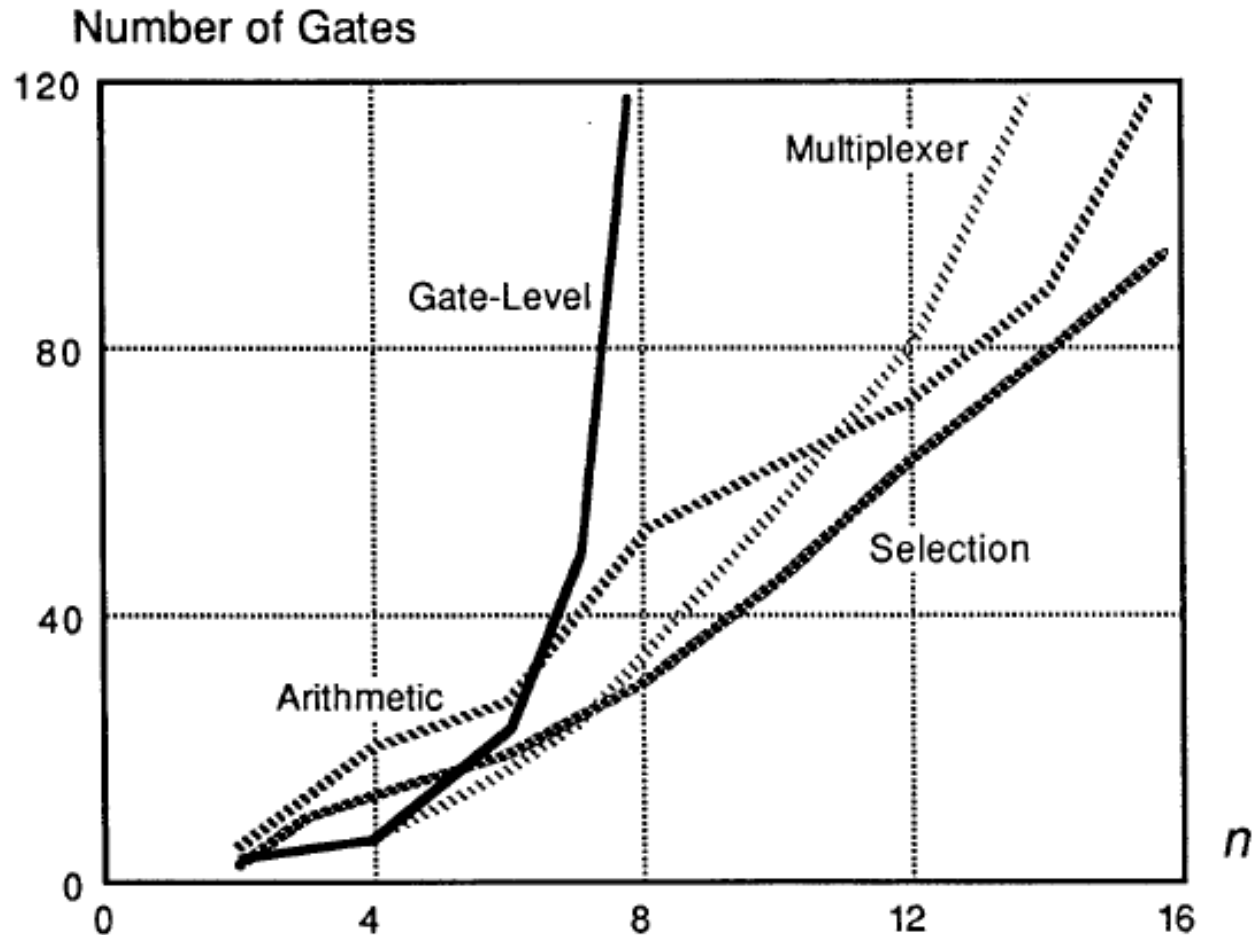Complexity of Different Bit-Voter Designs



Cost of majority bit-voters as a function of the number n of inputs

Voting at the Word Level

Using bit-by-bit voting may be dangerous

$$x_1 = 0 \ 0$$

$$x_2 = 1 \ 0$$

$$x_3 = 1 \ 1$$

$$\hline y = 1 \ 0$$

One might think that in this example, any of the module outputs could be correct, so that producing 1 0 at the output isn't all that wrong

However, with bit-by-bit voting, the output may be different from all inputs

$$x_1 = 0 \ 0 \ 0$$

$$x_2 = 1 \ 0 \ 1$$

$$x_3 = 1 \ 1 \ 0$$

$$\hline y = 1 \ 0 \ 0$$

Design of bit- and word-voting networks discussed in:
Parhami, B., "Voting Networks," *IEEE TR*, Aug. 1991


Some Simple Voter Designs

If in the case of 3-way disagreement any of the inputs can be chosen, then a simple design is possible

This design can be readily generalized to a larger number of inputs

One can perform pseudo voting that yields the median of 3 analog signals (Dennis, N.G., *Microelectronics and Reliability*, Aug. 1974)

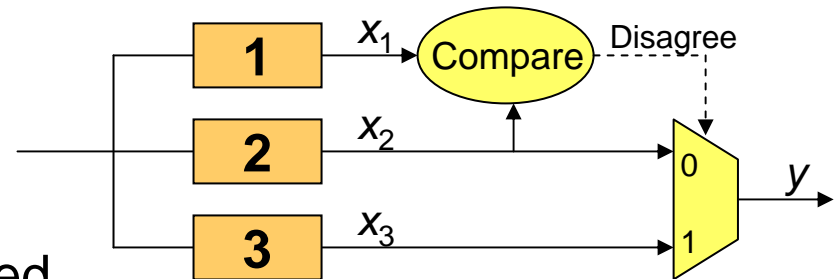Median and mean voting are also possible with digital signals



Switch for Standby Redundancy


Standby redundancy requires an n -to-1 switch to select the output of the currently active module

The detectors use various info to deduce fault conditions

- Error coding
- Reasonableness checks
- Watchdog timer

Once a fault has been detected, the switch reconfigures the system by flagging the faulty unit and activating next spare in sequence

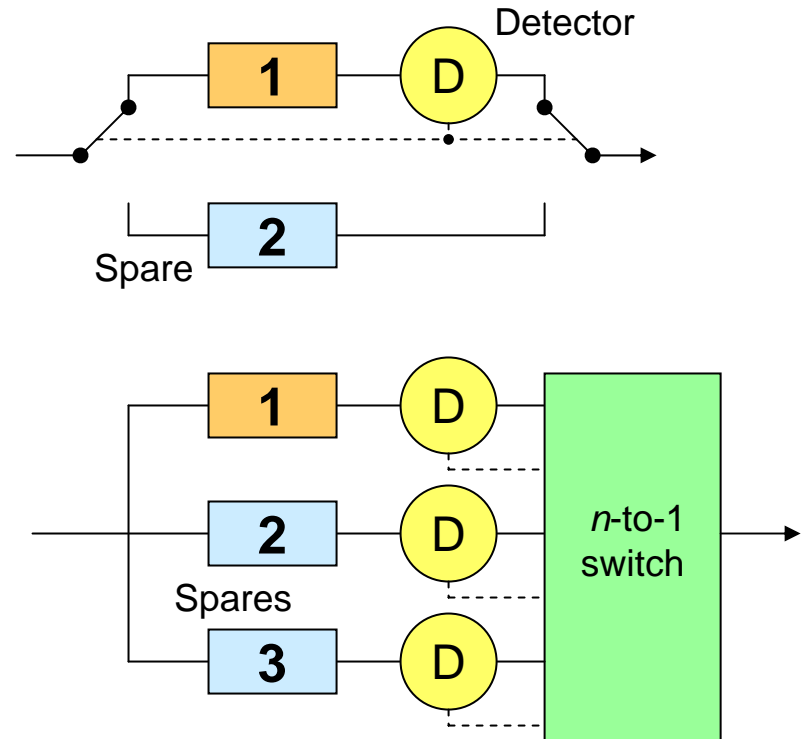If we use an n -to-2 switch and compare the two selected outputs, the configuration is known as “pair-and-spares”





Switch for Hybrid Redundancy

Hybrid redundancy with n active and s spare modules requires an $(n + s)$ -to- n switch to select the outputs of the active modules

Self-purging redundancy is a variant of hybrid redundancy in which all modules are active at the outset, but they are purged as they disagree with the majority output

  Voter in self-purging redundancy is a threshold voter that considers the inputs with weights of 1 (active) or 0 (purged)



Applications of n MR and Hybrid Redundancy

The Space Shuttle:

Uses 5-way redundancy in hardware

Originally, 3 operational units and 2 spares (one warm, one cold)

More recently, 4 operational units and 1 spare

Additionally, uses two independently developed software systems

Japanese Shinkansen “Bullet” Train

Triple-duplex system (6-fold redundancy)

⋮