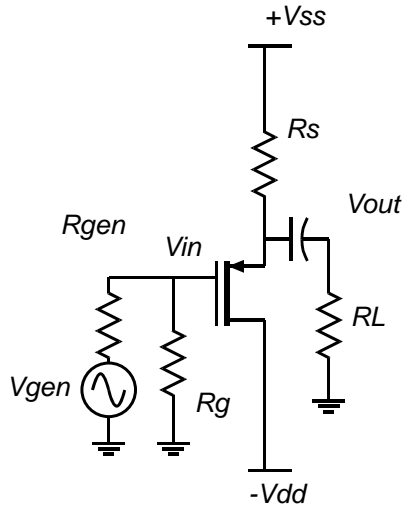



ECE137A Problem set #4



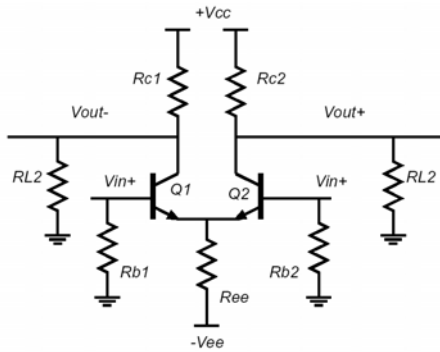
Problem 1 Common-drain stage. The PMOS FET has 1.2 nm oxide thickness, 250 nm gate length, and a -0.4 V threshold. Mobility is $200 \text{ cm}^2/(\text{V}\cdot\text{s})$. $1/\lambda$ is 15 V. Use a constant-mobility model.

Choose the gate width and R_s so that the transistor carries 5 mA and has 0.6 V on the source electrode. The load resistance is 1 kOhm, R_g is 1 MOhm, R_{gen} is 100 kOhm.


Find the bias conditions, the small-signal gains V_{out}/V_{in} , V_{out}/V_{gen} , and V_{out}/V_{in} , and find the input and output impedances.



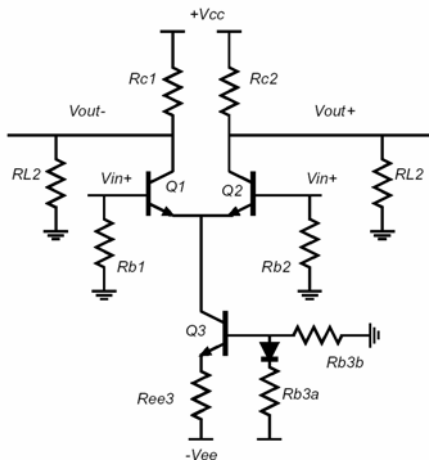Problem 2 The circuit above uses 2N3904 bjts. -- use datasheet values for beta and R_{ce} . For DC bias, V_{in+} and V_{in-} are zero volts. $V_{cc} = +5 \text{ V}$, $V_{ee} = -5 \text{ V}$. The DC emitter currents are each 2 mA, and the DC collector voltages are 2.5 V. $R_{b1} = R_{b2} = 10 \text{ kOhm}$. $R_{L1,2}$ are 10 kOhm. Find all resistor values. Find the bias conditions, the differential input impedance, the differential gain, and the common-mode rejection ratio.




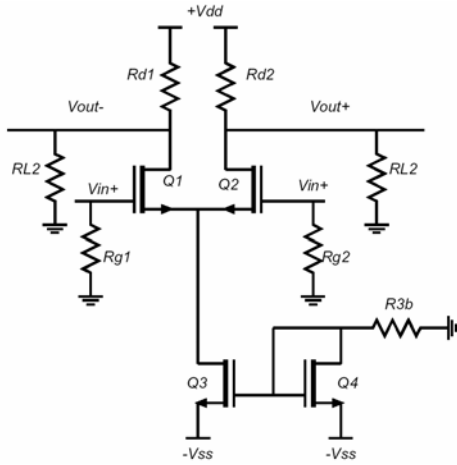Problem 3 The circuit now uses a constant current source to bias the differential amplifier. For Q1 and Q2, the DC emitter currents are each 1 mA, while their DC collector voltages are 2.5 V. There is a 0.2 V IR drop across R_{ee3} , while the DC current in R_{b3a} is 1/10th of the emitter current of Q3. Find all resistor values. Find the bias conditions, the differential and common-mode gains, and the common-mode rejection ratio. The diode has the same "on" voltage as the transistors.



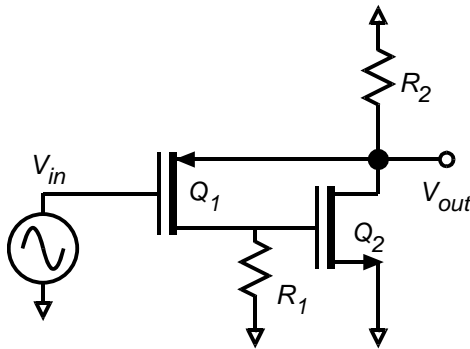Problem 4 The NMOS FET has 1.2 nm oxide thickness, 250 nm gate length, and a 0.4 V threshold. Mobility is $400 \text{ cm}^2/(\text{V}\cdot\text{s})$. $1/\lambda$ is 15 V. Use a constant-mobility model.

The supplies are + and - 1.5 Volts. Q3 and Q4 are to carry 1 mA drain current at $V_{gs}=0.6 \text{ V}$. Q1 and Q2 are to operate at $V_{gs}=0.6 \text{ V}$. The drain voltage is to be 1.0 Volts. The load resistances are 5 kOhm. Find all resistor values. Find the bias conditions, FET widths, the differential and common-mode gains, and the common-mode rejection ratio.



Problem #5. Nodal Analysis exercise. This is a "super-buffer". Ignore DC bias analysis. You don't need it. The two transistors have transconductance g_{m1} and g_{m2} respectively. Their drain-source resistances R_{ds1} and R_{ds2} are both infinity.

- Compute V_{out}/V_{in} by nodal analysis.
- find numerical values of V_{out}/V_{in} given $g_{m1}=10 \text{ mS}$, $g_{m2}=100 \text{ mS}$, $R_1=5\text{kOhm}$, $R_2=500 \text{ Ohms}$.