

## Final Exam, ECE 137A

Wednesday March 18, 2015 7:30-10:30 PM

Name: Solution b

Closed Book Exam: Class Crib-Sheet and 3 pages (6 surfaces) of student notes permitted  
Do not open this exam until instructed to do so. Use any and all reasonable approximations (5% accuracy), *after stating & justifying them.*

**Show your work:**

*Full credit will not be given for correct answers if supporting work is missing.*


Good luck

Time function	LaPlace Transform
$\delta(t)$ impulse	1
$U(t)$ unit step-function	$1/s$
$e^{-\alpha}U(t)$	$\frac{1}{s + \alpha}$
$e^{-\alpha} \cos(\omega_d t)U(t)$	$\frac{s + \alpha}{(s + \alpha)^2 + \omega_d^2}$
$e^{-\alpha} \sin(\omega_d t)U(t)$	$\frac{\omega_d}{(s + \alpha)^2 + \omega_d^2}$

Part	Points Received	Points Possible	Part	Points Received	Points Possible
1a		5	2c		15
1b		6	2d		10
1c		4	3a		7
1d		10	3b		8
1e		10	3c		7
2a		10	3d		8
2b		10			
total		100			

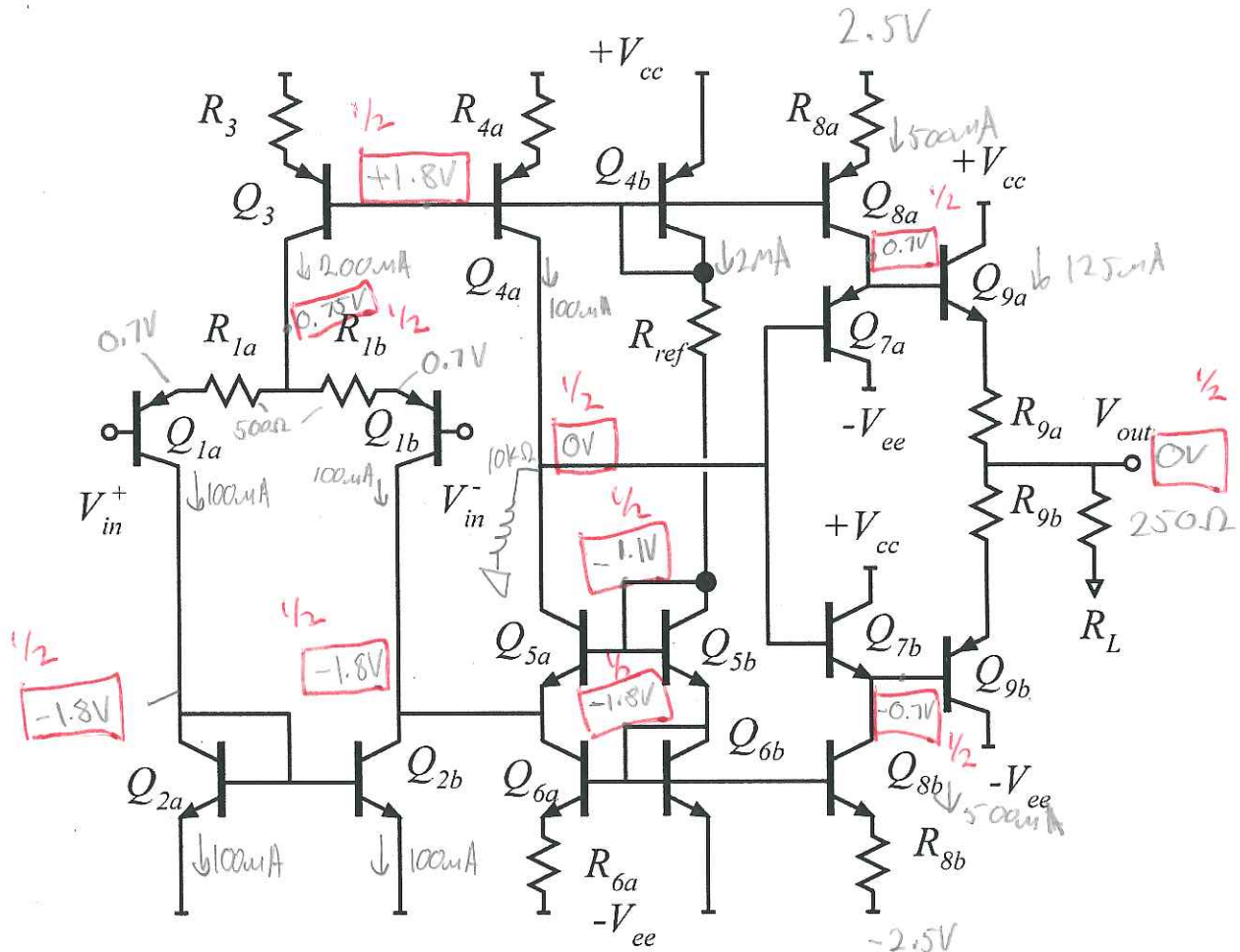Part a, 5 points

DC bias---to simplify, assume  $\beta = \infty$  for the DC analysis only.



On the circuit diagram above, label the DC voltages at ALL nodes, the DC currents through ALL resistors, and the DC collector currents of all transistors.

Part b

$$\textcircled{1} [V_{be6b} - V_{be6a} = \frac{kT}{q} \ln \left[ \frac{2mA}{100\mu A} \right] = 78mV \rightarrow R_{6a} = \frac{78mV}{100\mu A} = \boxed{779\Omega}$$

$$\textcircled{1} [V_{be6b} - V_{be8b} = \frac{kT}{q} \ln \left[ \frac{2mA}{500\mu A} \right] = 36.04mV \rightarrow R_{8b} = \frac{36.04mV}{500\mu A} = \boxed{72.1\Omega}$$

$$\textcircled{1} [V_{be7b} - V_{be9b} = \frac{kT}{q} \ln \left[ \frac{500\mu A}{125\mu A} \right] = 36.04mV \rightarrow R_{9a} = \frac{36.04mV}{125\mu A} = \boxed{288\Omega}$$

by same arguments,  $R_{8a} = \boxed{72\Omega}$   
 $R_{9a} = \boxed{288\Omega}$

$$\textcircled{i} [V_{be4b} - V_{be4a} = \frac{kT}{q} \ln \left[ \frac{2\text{mA}}{100\mu\text{A}} \right] = 78\text{mV} \rightarrow R_{4a} = \frac{78\text{mV}}{100\mu\text{A}} = \boxed{779\Omega}]$$

$$\textcircled{i} [V_{be4b} - V_{be3} = \frac{kT}{q} \ln \left[ \frac{2\text{mA}}{200\mu\text{A}} \right] = 60\text{mV} \rightarrow R_3 = \frac{60\text{mV}}{200\mu\text{A}} = \boxed{299\Omega}]$$

$$\textcircled{i} [R_{ref} = \frac{1.8\text{V} - (-1.1\text{V})}{2\text{mA}} = \boxed{1450\Omega}]$$

Part b, 6 points

DC bias:

Find the value of all resistors.

$$R3 = \underline{299\Omega} \quad R4b = \underline{779\Omega} \quad R6a = \underline{779\Omega} \quad R_{ref} = \underline{\quad} \quad R8a = \underline{72\Omega} \quad R8b = \underline{72\Omega}$$

$$R9a = \underline{288\Omega} \quad R9b = \underline{288\Omega}$$

↑  
1.45kΩ

Part c, 4 points

Find the transconductance of the transistors below:

$$g_{m1a} = 3.85 \text{ mS} \quad g_{m1b} = 3.85 \text{ mS} \quad g_{m5a} = 3.85 \text{ mS} \quad g_{m7a} = 19.2 \text{ mS}$$

$$g_{m7b} = 11.2 \text{ mS} \quad g_{m9a} = 4.8 \text{ mS} \quad g_{m9b} = 4.8 \text{ mS}$$

$$\textcircled{1} [Q_{1a,b}: I_c = 100 \mu\text{A}, \frac{1}{g_m} = 260 \Omega \rightarrow 3.85 \text{ mS}]$$

$$\textcircled{1} [Q_{5a}: I_c = 100 \mu\text{A} \rightarrow \frac{1}{g_m} = 260 \Omega \rightarrow 3.85 \text{ mS}]$$

$$\textcircled{1} [Q_{7a,b}: I_c = 500 \mu\text{A} \rightarrow \frac{1}{g_m} = 52 \Omega \rightarrow 19.23 \text{ mS}]$$

$$\textcircled{1} [Q_{9a,b}: I_c = 125 \mu\text{A} \rightarrow \frac{1}{g_m} = 208 \Omega \rightarrow 4.8 \text{ mS}]$$

Part d, 10 points.

Find the following, using the actual value of  $\beta$ , i.e.  $\beta=250$


	Voltage Gain	Input impedance
Transistor combination Q2a,2b,1a,1b	0.342	190k $\Omega$
Q5a	38.46	260 $\Omega$
Q7a or 7b	1.0	46.6M $\Omega$
Q9a or 9b	0.335	186.5k $\Omega$
Overall differential Vout/Vin	4.4	190k $\Omega$

1 pt.  
each

★ We have a push-pull stage. Gain will vary over signal swing if one transistor or the other or both are on.

★ We will assume either Q9a or Q9b is on, but not both.

Q9a:

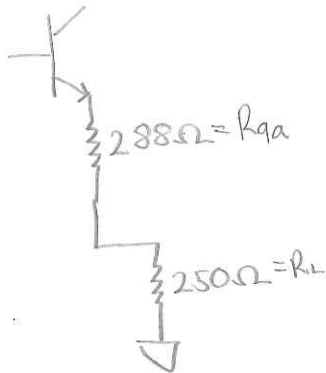

$$1/g_{m9a} = 208 \Omega$$

★ Emitter-follower + Voltage Divider.

Voltage Divider gain:

$$\frac{250}{250+288} = 0.46$$

Emitter Follower gain:

$$R_{L,eq} = 250 + 288 = 538 \Omega$$

$$A_v = \frac{538}{538+208} = 0.72$$

$$\text{Overall: } (0.46)(0.72) = \boxed{0.335}$$

$$R_{in9a} = \beta(208 \Omega + 288 \Omega + 250 \Omega) = \boxed{186.5 k \Omega}$$

$$\underline{Q_{7b}}: R_{Leq7b} = R_{in9b} = 186.5 \text{ k}\Omega \quad (\text{neglect } R_{in,c,8b})$$

$$1/g_{m7b} = 52 \Omega$$

$$A_v = \frac{R_{Leq}}{R_{Leq} + 1/g_m} = \boxed{1.0}$$


$$R_{in7b} = \beta [186 \text{ k}\Omega] = \boxed{46.6 \text{ M}\Omega}$$

$$\underline{Q_{5a}}: R_{Leq5a} = 10 \text{ k}\Omega \parallel R_{in7a} \quad (\text{neglect } R_{in,c,4a})$$
$$\cong 10 \text{ k}\Omega$$

\* Impedance presented to base of  $Q_{5a}$  is that of diodes  $Q_{5b}$  &  $Q_{6b}$ , each  $13 \Omega$ , for a total of  $26 \Omega = R_{base5a}$

$$R_{in5a} = \frac{1}{g_{m5a}} + \frac{R_{base5a}}{\beta} = \boxed{260 \Omega}$$
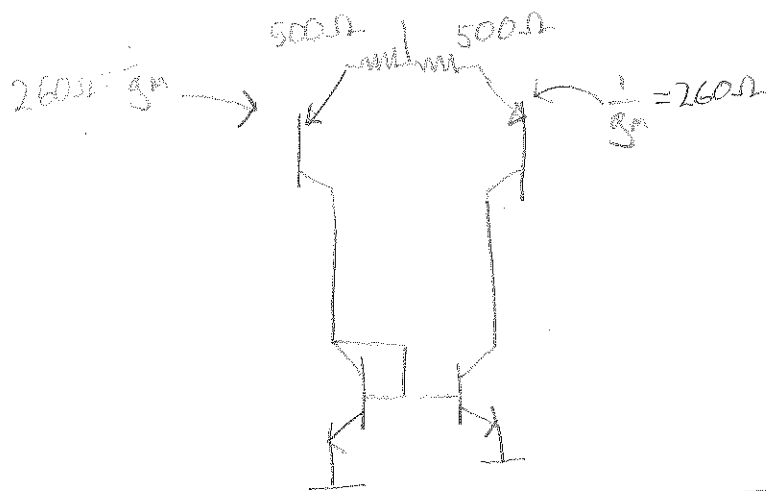
$$A_{v5a} = \frac{10 \text{ k}\Omega}{260 \Omega} = \boxed{38.46}$$



Overall transconductance =  $\frac{1}{\frac{1}{g_{m1a}} + R_{1a}} = \frac{1}{500\Omega + 260\Omega} = (760\Omega)^{-1}$

gain =  $\frac{260\Omega}{760\Omega} = \boxed{0.342}$

Input impedance per side is  $\beta(760\Omega + 260\Omega) = \boxed{190k\Omega}$




Part e, 10 points

Maximum peak-peak output voltage (*show all your work*)

1  
2  
2  
1  
2  
2


	magnitude and sign of maximum output signal swing due to <i>cutoff</i>	magnitude and sign of maximum output signal swing due to <i>saturation</i>
Transistor Q4a	+ 0.66V	Not Relevant
Transistor Q5a	-0.43V	+0.33V
Transistor Q7a	+30V	-0.89V
Transistor Q7b	-30V	+0.89V
Transistor Q9a	Not Relevant	+0.92V
Transistor Q9b	Not Relevant	-0.92V

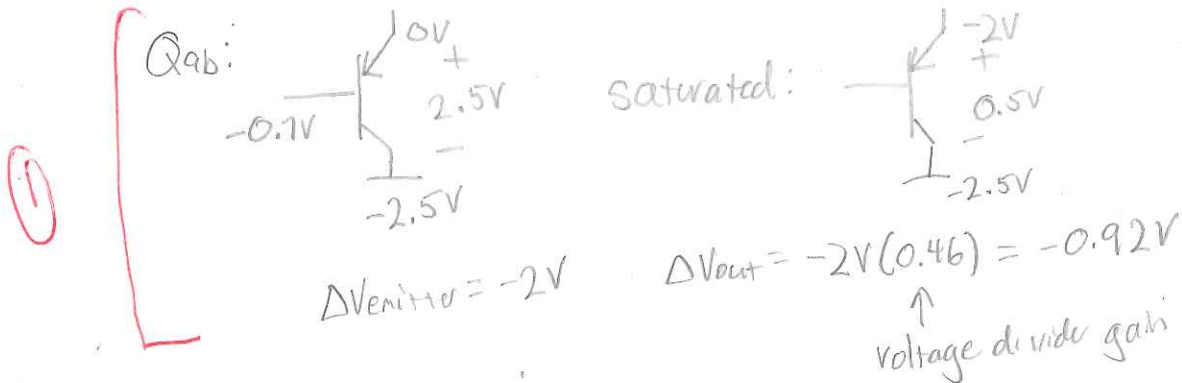Be warned: In some cases a limit is not relevant at all. Mark those answers "not relevant". But, give a 1-sentence statement below as to why it is not relevant. Q7ab and Q9b form a push pull stage, so be careful about your answers here.




- ① [ Cutoff: Not relevant because Q9a takes over push-pull
- ② [ Q9a: Analysis exactly the same but signs are reversed.

①

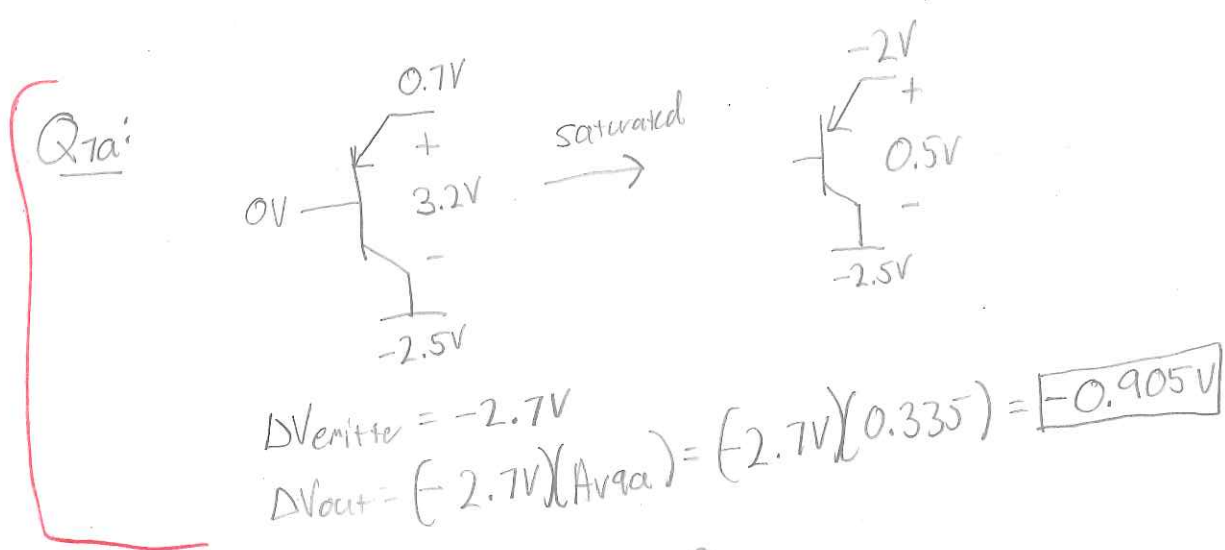


①

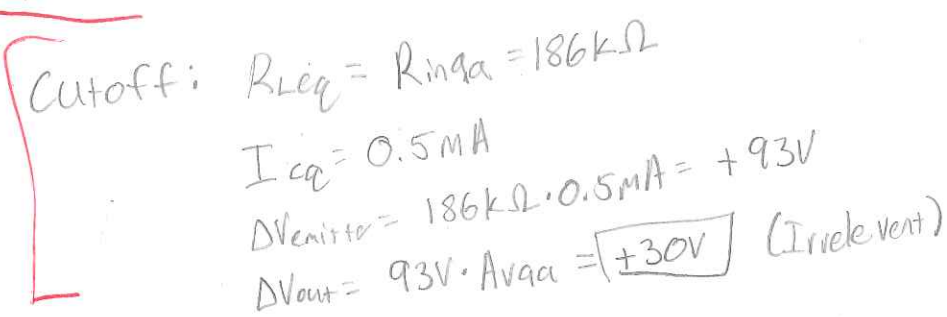


①

Q7b: Mirror-symmetric with Q7a, so answers the same with signs reversed.


①

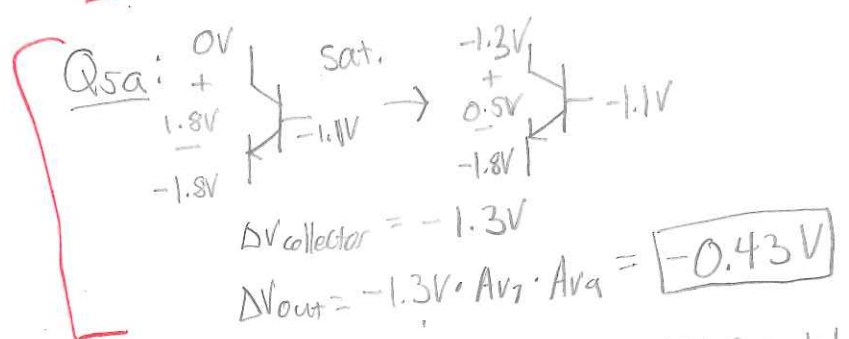

①

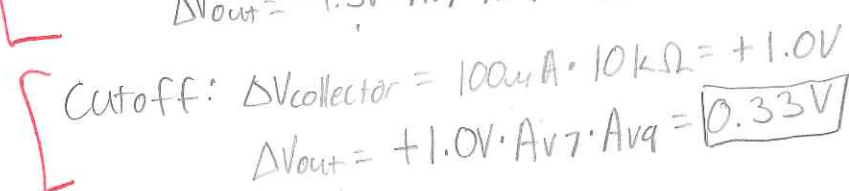


①

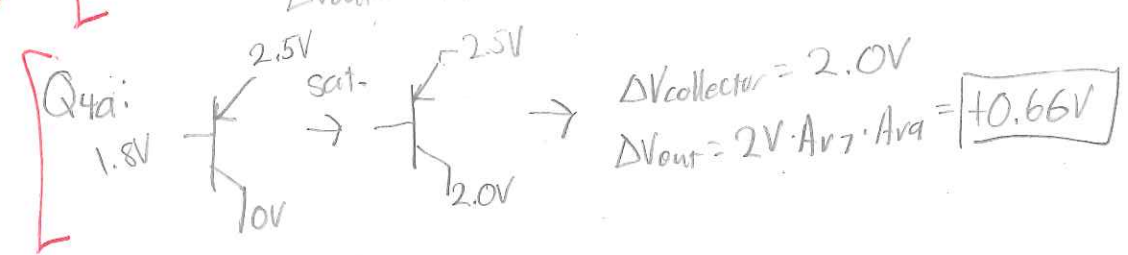

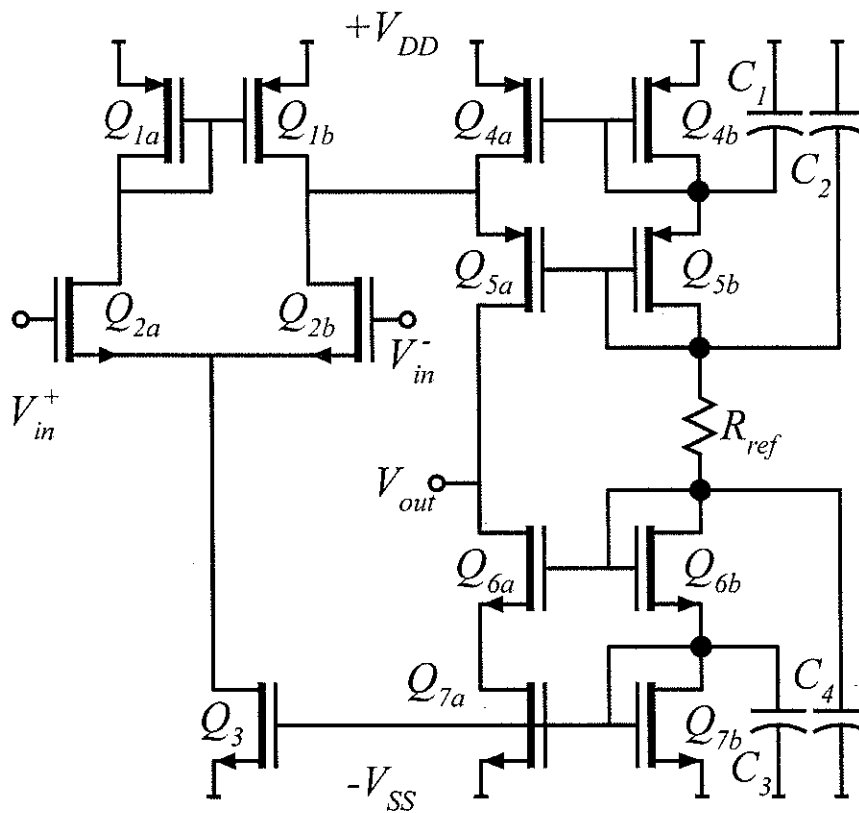**Problem 2, 35 points**

*This is an Op-Amp*---analyze the bias under the assumption that DC output voltage is zero volts, that the positive input  $V_{in+}$  is zero volts, and that we must determine the DC value of the negative input voltage ( $V_{in-}$ ) necessary to obtain this.



The NMOSFETs and the PMOSFETs have a 0.20 V threshold, a 22nm gate length, 300 cm<sup>2</sup>/Vs mobility, a 10<sup>7</sup>cm/s saturation drift velocity, and  $1/\lambda=3$  Volts. The gate oxide thickness is 1.0nm and the dielectric constant is 3.8. This gives

$$\mu c_{ox} W_g / 2L_g = 15 \text{ mA/V}^2 \cdot (W_g / 1\mu\text{m}) \text{ and}$$

$$v_{sat} c_{ox} W_g = 3.36 \text{ mA/V} \cdot (W_g / 1\mu\text{m}) \text{ (both are a bit unrealistic for a real technology).}$$

$$\text{and } v_{sat} L_g / \mu = 0.113 \text{ V}$$

$$V_{DD} = +0.75 \text{ V}, -V_{SS} = -0.75 \text{ V},$$

Part a, 10 points

DC bias.

**Approximation: ignore the term  $(1 + \lambda V_{DS})$  in DC bias analysis.**

Analyze the bias under the assumption that DC output voltage is zero volts, that the positive input  $V_{i+}$  is zero volts, and that we must determine the DC value of the negative input voltage ( $V_{i-}$ ) necessary to obtain this.

Q1ab,2ab are to be biased at  $25 \mu A$  drain current.

Q4ab,5ab,6ab,7ab are to be biased at  $100 \mu A$  drain current

All transistors are to operate with  $|V_{gs}| = 0.25V$ .

Find the gate widths of all transistors.

Find:

Wg1a=\_\_\_\_\_ Wg1b=\_\_\_\_\_ Wg2a=\_\_\_\_\_ Wg2b=\_\_\_\_\_ Wg3=\_\_\_\_\_  
Wg4a=\_\_\_\_\_ Wg4b=\_\_\_\_\_ Wg5a=\_\_\_\_\_ Wg5b=\_\_\_\_\_  
Wg6a=\_\_\_\_\_ Wg6b=\_\_\_\_\_ Wg7a=\_\_\_\_\_ Wg7b=\_\_\_\_\_  
Rref=\_\_\_\_\_

②  $V_{gs} = 0.25V$  so  $V_{gs} - V_{th} = 50mV < \frac{V_{sat} L_g}{\mu}$  so mobility-limited

②  $I_D = [15mA/V^2] \left[ \frac{W_g}{1\mu m} \right] \cdot (V_{gs} - V_{th})^2$

②  $I_D = 37.5\mu A \left( \frac{W_g}{1\mu m} \right) \rightarrow W_g = 1\mu m \cdot \frac{I_D}{37.5\mu A}$


1.33  $[Q_{1a, 2a, 1b, 2b}: I_D = 25\mu A \rightarrow W_g = 0.666\mu m$

1.33  $[Q_3: I_D = 50\mu A \rightarrow W_g = 1.33\mu m$

1.33  $[Q_{4ab, 5ab, 6ab, 7ab}: I_D = 100\mu A \rightarrow W_g = 2.66\mu m$

Part b, 10 points

DC bias

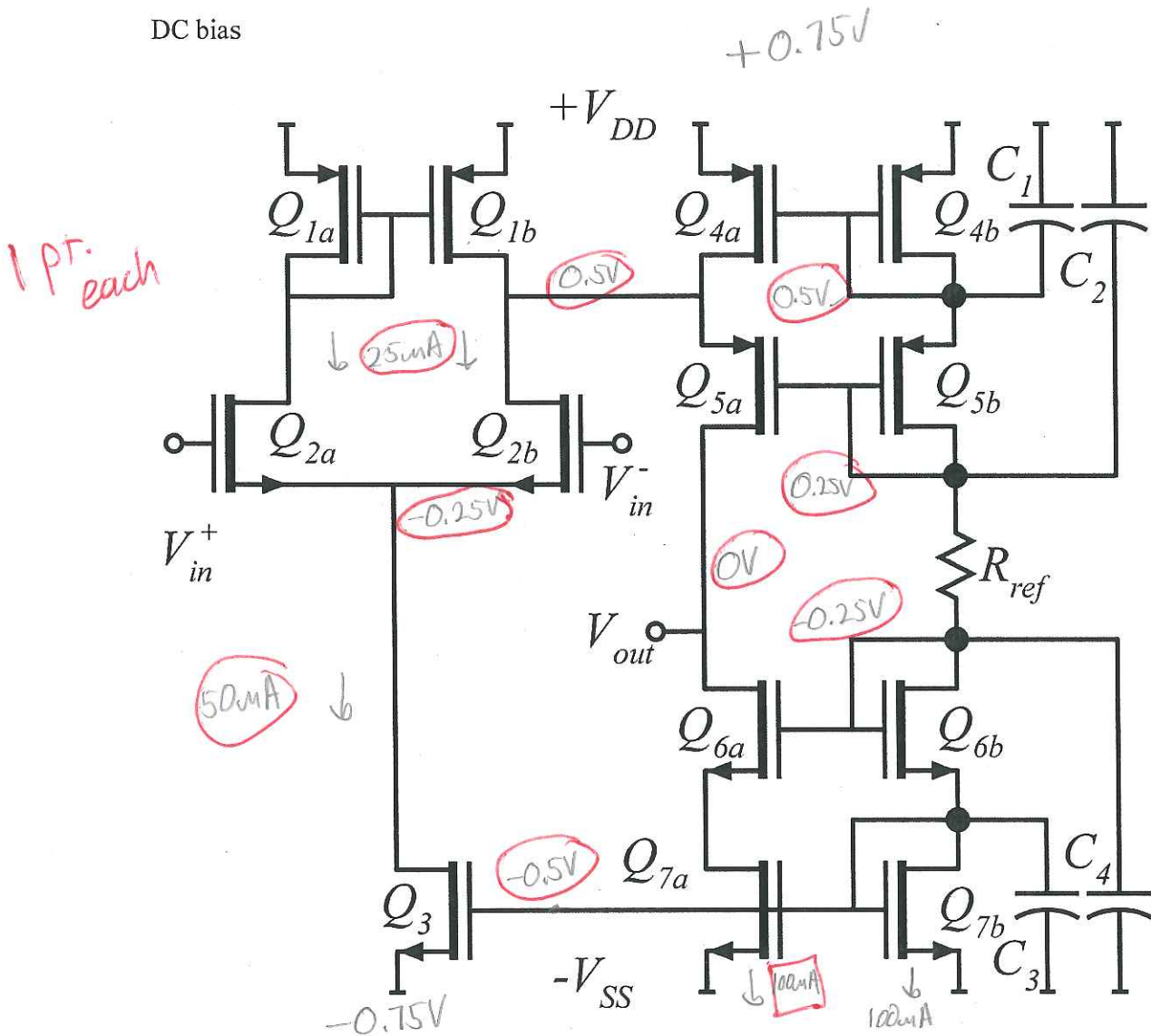

On the circuit diagram above, label the DC voltages at ALL nodes the drain currents of ALL transistors, and the gate widths of ALL transistors

Part c, 15 points.

You will now compute the op-amp differential gain. *You must consider the  $(1 + \lambda V_{DS})$  term in the FET IV characteristics when you do this.*

The capacitors C1-C4 are all zero Ohms AC impedance. (They would not be present in a real design; they are added here to simplify the exam).

Find the following

	Voltage Gain	Input impedance
Transistor combination Q2a,2b,1a,1b	21.3	$\infty$
Q5a	129	33k $\Omega$
Overall differential Vout/Vin	2746	$\infty$

(Alternative----if you very skilled, you might be able to compute the combined gain of Q2a,2b,1a,1b and Q5a, all together, in a single step using Norton or Thevenin methods. If you do so, first, don't ask for hints on how to do this and, second, do please also calculate the input impedance of Q5a.)

①  $\star$  Since  $I_D = \frac{15mA}{V^2} (V_{GS} - V_{th})^2 \cdot \frac{Wg}{L_{min}}$ , so  $g_m = \frac{\delta I_D}{\delta V_{GS}} = \frac{20mA}{V^2} (V_{GS} - V_{th}) \left( \frac{Wg}{L_{min}} \right)$

$g_m = 1.5mS \cdot \frac{Wg}{L_{min}}$

①  $Q_{1ab,2ab}: g_m = 1.0mS$

$Q_3: g_m = 2.0mS$

$Q_{4ab,5ab,6ab,7ab}: g_m = 4.0mS$

1pt

$R_{DS} = \frac{3.25V}{100\mu A} = 32.5k\Omega$

$R_{out, drain 6a} = R_{DS} (1 + g_m R_{DS 7a}) = 4.26 M\Omega = R_{eq 5a}$


2pts

①  $R_{eq} = R_{out drain}$

①  $Q_{5a}$ : common gate:

①  $R_{in 5a} = \frac{1}{g_{m5a}} \left( \frac{R_{eq} + R_{DS}}{R_{DS}} \right) = 33k\Omega$

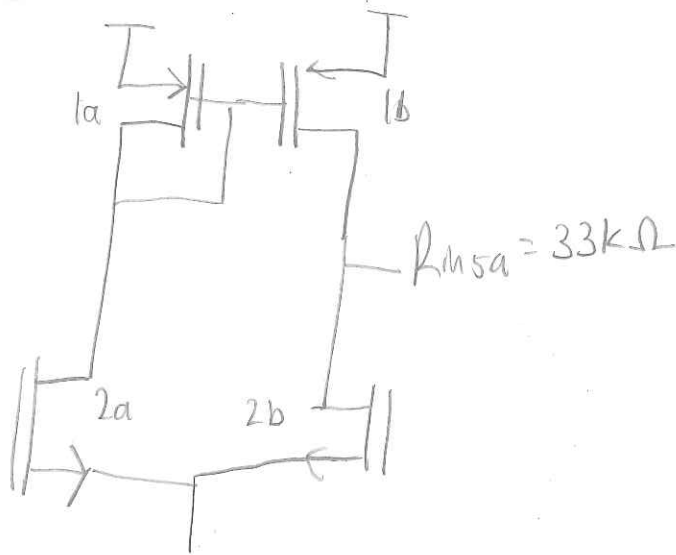①  $A_{v5a} = \frac{R_{eq}}{R_{in 5a}} = 129$



Q1a, 2a, 1b, 2b

① [ all  $g_m = 1.0 \text{ mS}$

① [ all  $R_{os} \approx \frac{3V}{25 \mu\text{A}} = 120 \text{ k}\Omega$

② [ Stage transconductance =  $g_{m1a} = 1 \text{ mS}$

① [  $R_{Leq} = R_{msa} \parallel R_{os1b} \parallel R_{os2b} = 33 \text{ k}\Omega \parallel 120 \text{ k}\Omega \parallel 120 \text{ k}\Omega$   
 $= 21.3 \text{ k}\Omega$

② [  $g_{ah} = 1 \text{ mS} \cdot 21.3 \text{ k}\Omega = \boxed{21.3}$


Part d, 10 points

Maximum peak-peak output voltage at the positive output  $V_{o+}$  (show all your work)

	magnitude and sign of maximum output signal swing due to <i>cutoff</i>	magnitude and sign of maximum output signal swing due to: <i>knee voltage</i> (saturation)
Transistor Q5a	- kilovolts	+0.45V
Transistor Q6a	cannot cut off	-0.45V
Transistor Q2a	+ Huge $\rightarrow$ irrelevant	cannot be reached $\rightarrow$ irrelevant
Transistor Q2b	- Huge $\rightarrow$ irrelevant	- irrelevant

Be warned: in some cases a limit is not relevant. Mark those answers "not relevant". But, give a 1-sentence statement why below.

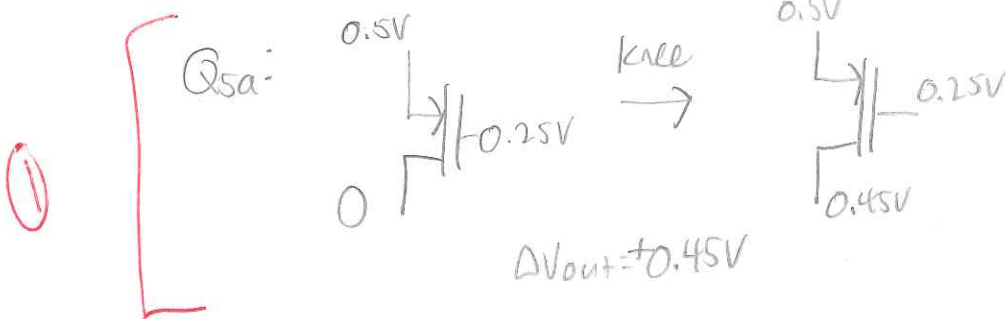②  $\mu$ -limited, so  $V_{ds,sat} = V_{gs} - V_{th} = 50mV$  for all Fets




① [By symmetry, knee voltage of Q6a limits  $\Delta V_{out}$  to  $-0.45V$

① [Cutoff of Q5a  $\cdot \Delta I_d = 100\mu A$ ,  $R_{L,eq} = 4.26M\Omega$   
 $\Delta V_{out} = \text{kilovolts}$



# Cutoff of $Q_{2a}$ & $Q_{2b}$

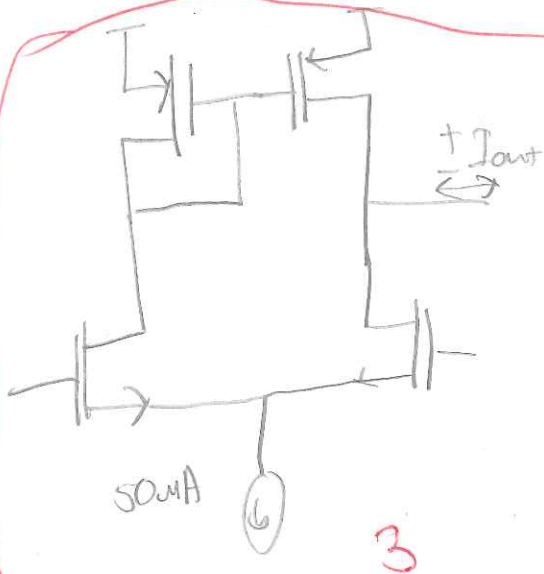

As  $2a$  and  $2b$  are driven, one full-on and the other cut off,  $I_{out}$  varies by  $\pm 50\mu A$


This drives  $\pm 50\mu A$  into effective load of  $4.26 M\Omega$ ;  $(\pm 50\mu A)(4.26 M\Omega) = \pm 2.13 V$

$H_{ge} \rightarrow$  Irrelevant

① knee voltage of  $Q_{2a}$  - cannot be reached until past  $Q_{2b}$  cutoff

irrelevant

② knee voltage of  $Q_{2b}$

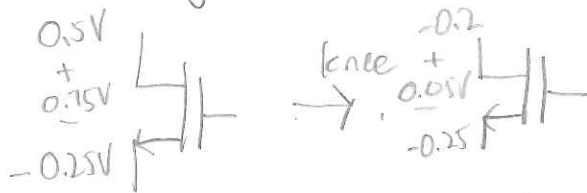


$$\Delta V_{drain} = -0.7V$$

$$\Delta V_{out} = (-0.7V) A_{v_{50\mu A}} = - \text{large number}$$


irrelevant

Problem 3, 30 points

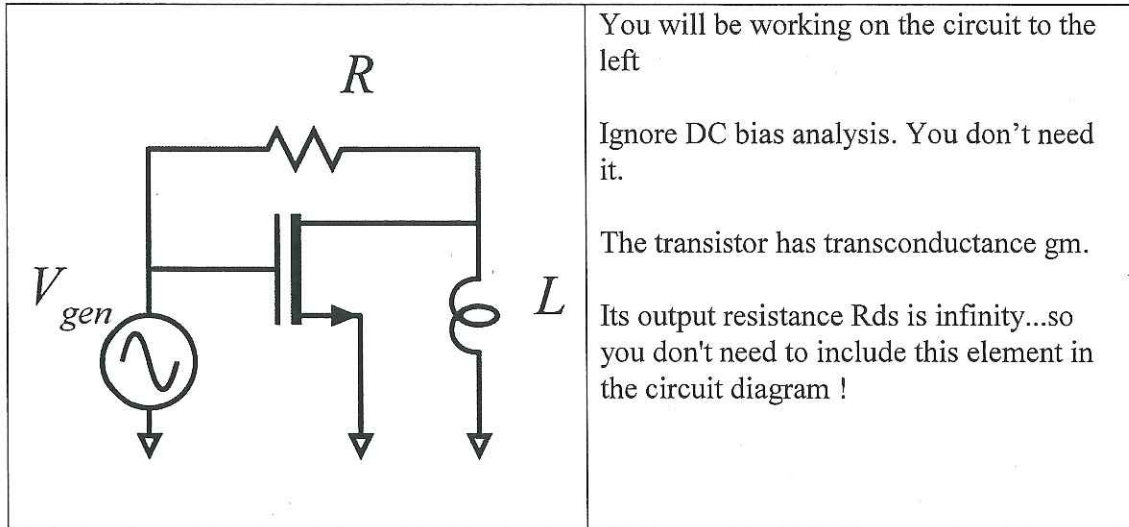

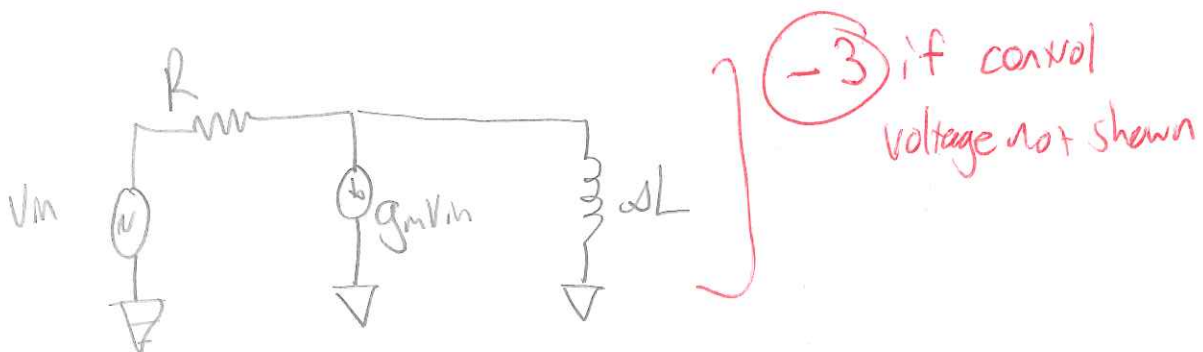Part a, 7 points

Draw a small-signal equivalent circuit of the circuit.



Part b, 8 points

$g_m = 10 \text{ mS}$ ,  $L = 1 \mu\text{H}$ ,  $R = 1000 \text{ Ohms}$

Find, by nodal analysis, a small-signal expression for  $V_{out}/V_{in}$ . Be sure to give the answer with **\*\*correct units\*\*** and in ratio-of-polynomials form, i.e.

$$\frac{V_{out}(s)}{V_{gen}(s)} = K \cdot \frac{1 + b_1s + b_2s^2 + \dots}{1 + a_1s + a_2s^2 + \dots} \text{ or (as appropriate) } \frac{V_{out}(s)}{V_{gen}(s)} = K \cdot (s\tau)^n \cdot \frac{1 + b_1s + b_2s^2 + \dots}{1 + a_1s + a_2s^2 + \dots}$$

Note that an expression like

$$\frac{V_{out}(s)}{V_{gen}(s)} = \frac{1}{1 + (3 \cdot 10^{-6})s} \text{ is dimensionally wrong; } \frac{1}{1 + (3 \cdot 10^{-6} \text{ seconds})s} \text{ is dimensionally correct}$$

$V_{out}(s)/V_{in}(s) = \underline{\hspace{2cm}}$

$$\sum I @ V_{out} = 0 \Rightarrow V_{out} \left( \frac{1}{sL} + \frac{1}{R} \right) + V_{in} \left[ g_m - \frac{1}{R} \right] = 0$$

4 pts For some version of this

$$\frac{V_o}{V_m} = - \left[ g_m R - 1 \right] \frac{sL/R}{1 + sL/R}$$

$$\frac{L}{R} = 10^{-9} \text{ sec} = 1 \text{ ns}$$

$$\frac{V_o}{V_m} = -9 \left[ \frac{s \cdot 1 \text{ ns}}{1 + s \cdot 1 \text{ ns}} \right] \quad 4 \text{ pts}$$


Part c, 7 points

Find any/all pole and zero frequencies of the transfer function, in Hz:

① 0 at DC, pole at 159 MHz ①

Draw a clean Bode Plot of  $V_{out}/V_{in}$ ,

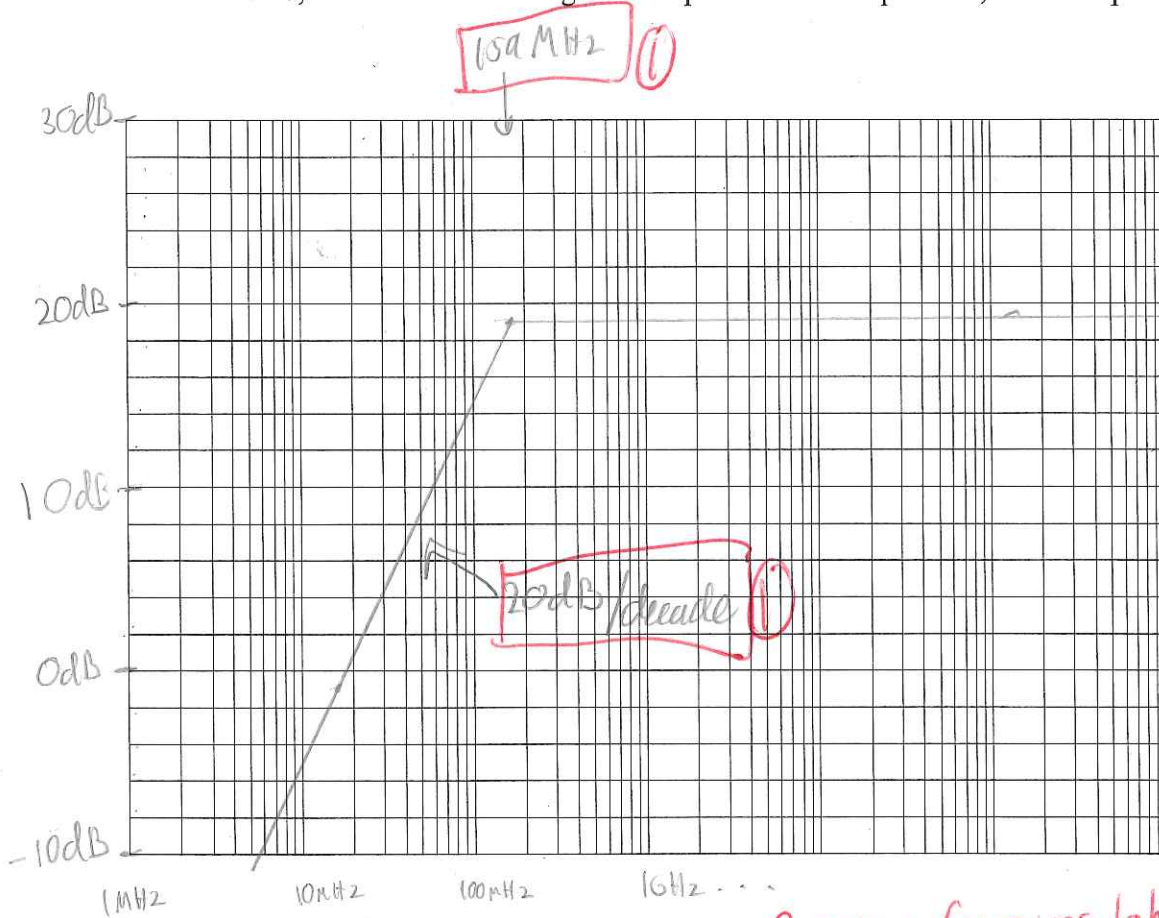LABEL AXES, LABEL all relevant gains and pole or zero frequencies, Label Slopes




2 points for axes labelled  
Sensibly

Part d, 8 points

$V_{in}(t)$  is a 0.1 V amplitude step-function.

Find  $V_{out}(t) =$  \_\_\_\_\_

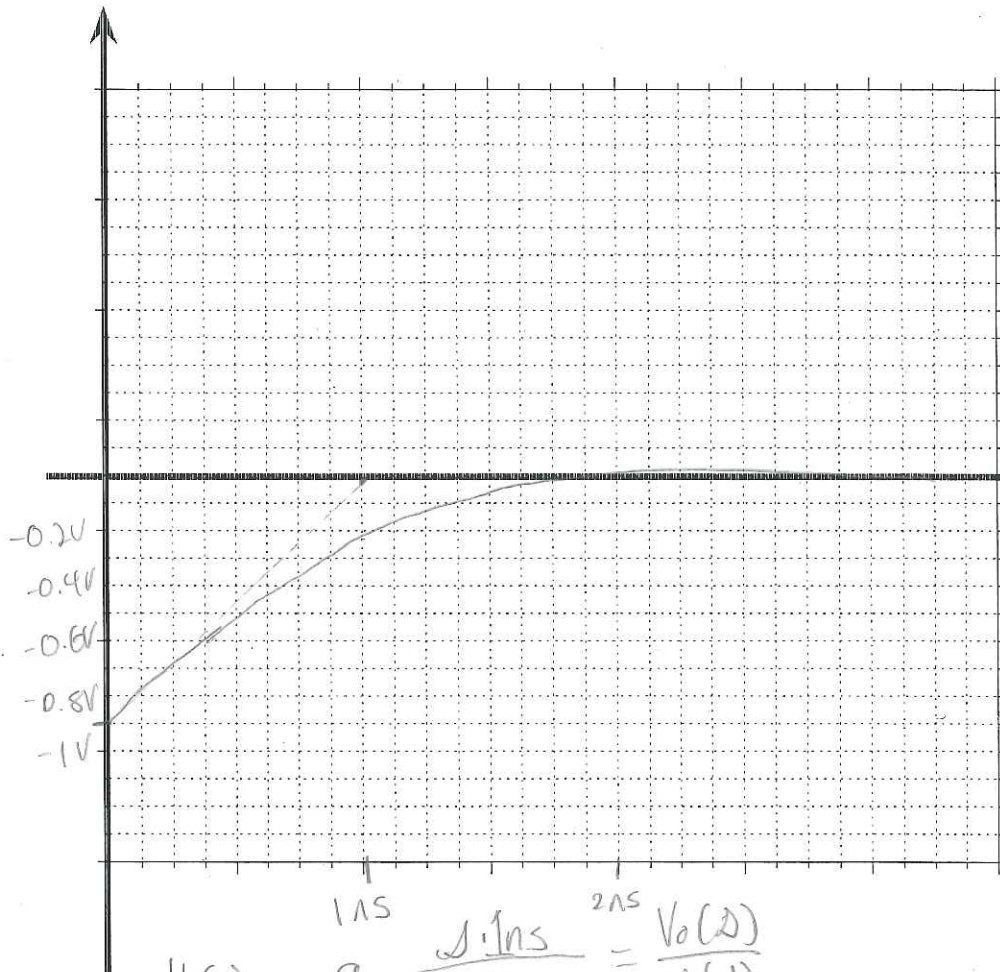Plot it below. Label axes, show initial and final values, show time constants.



2pts  
for  
red scribble  
graph

$$H(\Delta) = -9 \cdot \frac{\Delta \cdot 1ns}{1 + \Delta \cdot 1ns} = \frac{V_o(\Delta)}{V_i(\Delta)}$$

$$\textcircled{2} \left( V_{in}(\Delta) = \frac{0.1V}{\Delta} \right) \text{ so } \left( V_{out}(\Delta) = -0.9V \cdot \frac{1ns}{1 + \Delta \cdot 1ns} \right) 2$$

$$V_{out}(t) = -0.9V \cdot u(t) \cdot e^{-t/1ns}$$