

Final Exam, ECE 137A

Wednesday March 22, 2017, 7:30 - 10:30pm

Name: Solution

Closed Book Exam:

Class Crib-Sheet and 3 pages (6 surfaces) of student notes permitted

Do not open this exam until instructed to do so. Use any and all reasonable approximations (5% accuracy), *after stating & justifying them.*

Show your work:

Full credit will not be given for correct answers if supporting work is missing.


Good luck

Time function	LaPlace Transform
$\delta(t)$ impulse	1
$U(t)$ unit step-function	$1/s$
$e^{-\alpha}U(t)$	$\frac{1}{s + \alpha}$
$e^{-\alpha} \cos(\omega_d t)U(t)$	$\frac{s + \alpha}{(s + \alpha)^2 + \omega_d^2}$
$e^{-\alpha} \sin(\omega_d t)U(t)$	$\frac{\omega_d}{(s + \alpha)^2 + \omega_d^2}$

Part	Points Received	Points Possible	Part	Points Received	Points Possible
1a		5	2c		15
1b		6	2d		10
1c		4	3a		7
1d		10	3b		8
1e		10	3c		7
2a		10	3d		8
2b		10			
total		100			

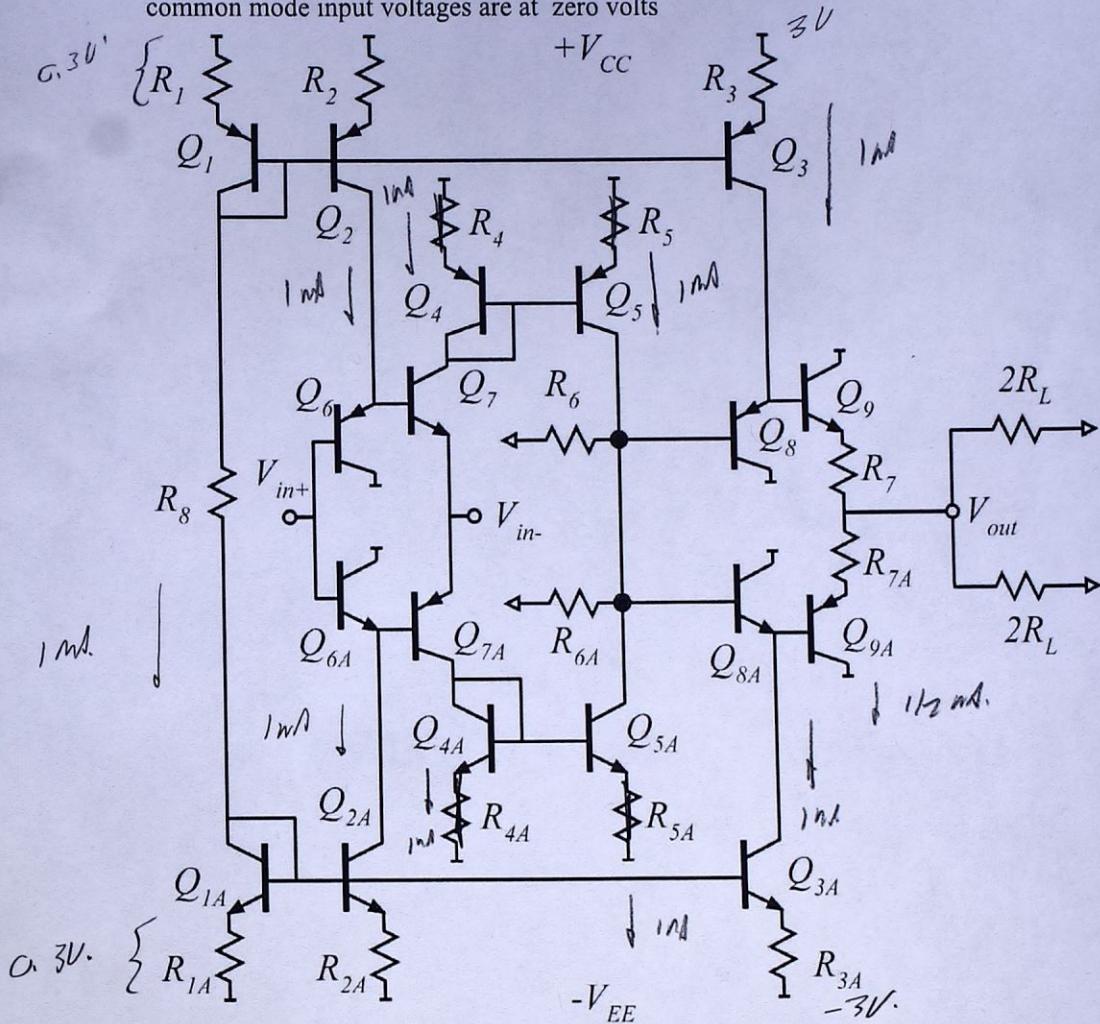Problem 1, 35 points

This is an NOT an Op-Amp: Analyze under the assumption that the differential and common mode input voltages are at zero volts



All the transistors have the same (matched) I_S , have $\beta = 100$, and $V_A = \infty$ Volts.

$V_{CE(sat)} = 0.5V$.

V_{be} is roughly 0.7 V, but use $V_{be} = (kT/q) \ln(I_E / I_S)$ when necessary and appropriate.

The supplies are +3 Volts and -3 Volts.

$R_1 = R_{1A}$, $R_2 = R_{2A}$, $R_3 = R_{3A}$, $R_6 = R_{6A}$, $R_7 = R_{7A}$.

The voltage drops across R_1 and R_{1A} are both 300mV.

$Q_1, Q_{1A}, Q_6, Q_{6A}, Q_7, Q_{7A}, Q_5, Q_{5A}, Q_8, Q_{8A}$: $I_C = 1mA$.


Q_9, Q_{9A} : $I_C = 0.5 mA$.

$R_L = 100$ Ohms, $R_6 = R_{6A} = 1000$ Ohms. $R_4 = R_{4A} = R_5 = R_{5A} = 0$ Ohms.

$$R_7 = \frac{kT}{q(1/2mA)} \ln 2 = 36 \Omega$$

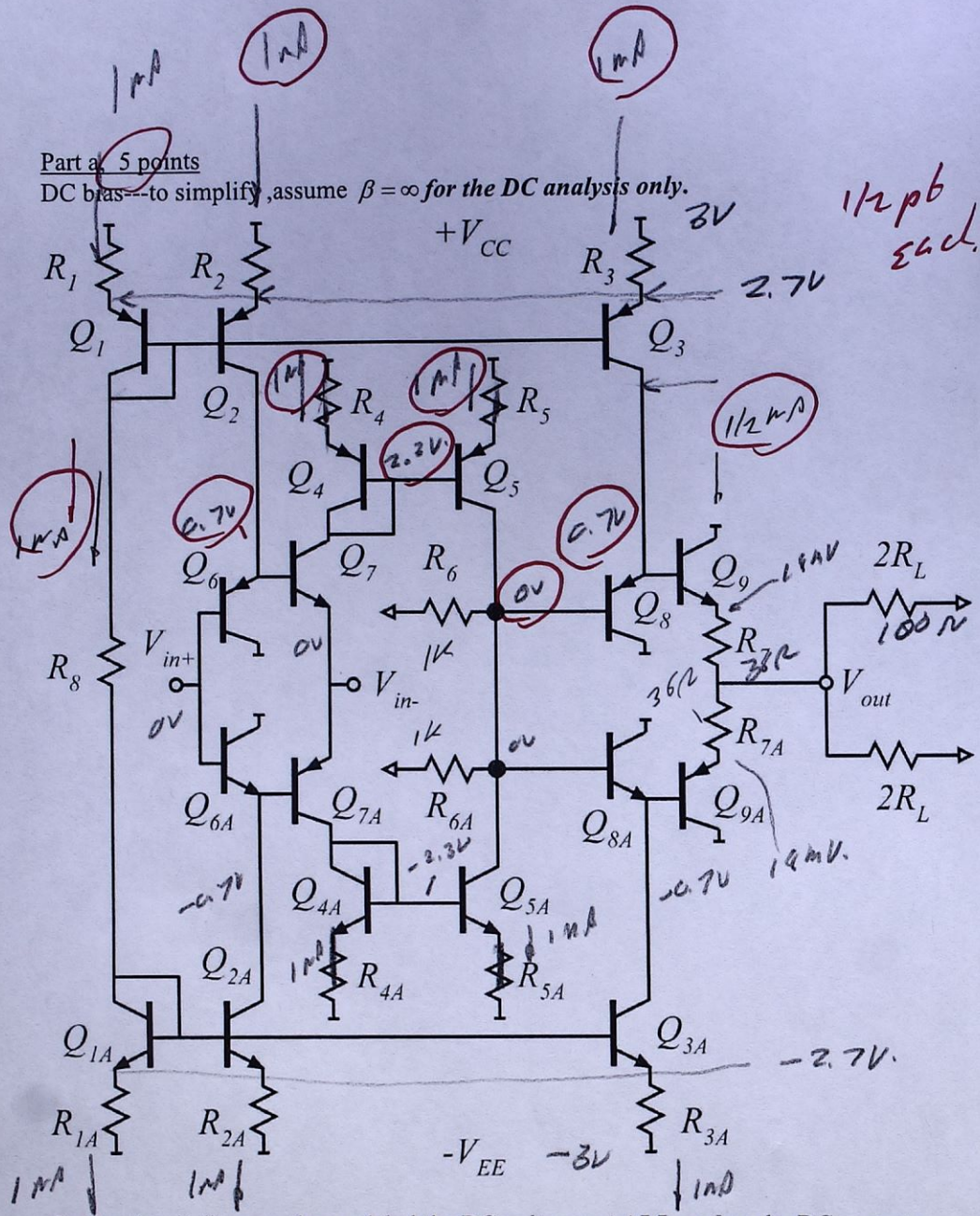Part a 5 points

DC bias--to simplify, assume $\beta = \infty$ for the DC analysis only.



On the circuit diagram above, label the DC voltages at **ALL nodes**, the DC currents through **ALL resistors**, and the DC collector currents of **all transistors**.

Part b, 6 points

DC bias:

Find the value of all resistors.

$$\begin{aligned} R1/R1A &= 300 & R2/R2A &= 320 & R3/R3A &= 300 & R4/R4A &= 0 \\ R5/R5A &= 0 & R6/R6A &= 1\mu\Omega & R7/R7A &= 36 & R8 &= 5.4\mu\Omega \end{aligned}$$

$$2 \left[R1/1A/2/2A/3/3A \right] \quad R5 = \frac{0.3V}{1mA} = 300\Omega$$

$$2 \left[R7/7A \right] \quad V_{be8} + V_{be8A} - V_{be9} - V_{be9A} = 2 \cdot R7 \cdot 0.5mA$$
$$2 \cdot \frac{4T}{5} \cdot 1A(2) = 2 \cdot R7 \cdot 0.5mA$$
$$R7 = 36\Omega$$

$$2 \left[R8 \right] \quad V_{drop} \text{ is } (3V - 0.3V) \cdot 2, \text{ current is } 1mA$$
$$R = \frac{2(2.7V)}{1mA} = 5.4\mu\Omega$$

Part c, 4 points

find the following

device	Q1/1A	2/2A	3/3A	4/4a	5/5A	6/6A	7/7A	8/8A	9/9A
gm, S									
Rce, Ω									

$$1 \left[R_{ce} = \frac{V_o + V_{ce}}{I_c} \rightarrow \infty \Omega$$

$$1.5 \left[\text{all } K_a \text{ except } Q9/9A \\ I_c = 1 \text{ mA} \rightarrow 1/g_m = 25 \Omega$$


$$\rightarrow g_m = 38.5 \text{ mS}$$

$$1.5 \left[\underline{9/9A} \\ I_c = 1/2 \text{ mA} \rightarrow 1/g_m = 50 \Omega$$

$$\rightarrow g_m = 19.2 \text{ mS}$$

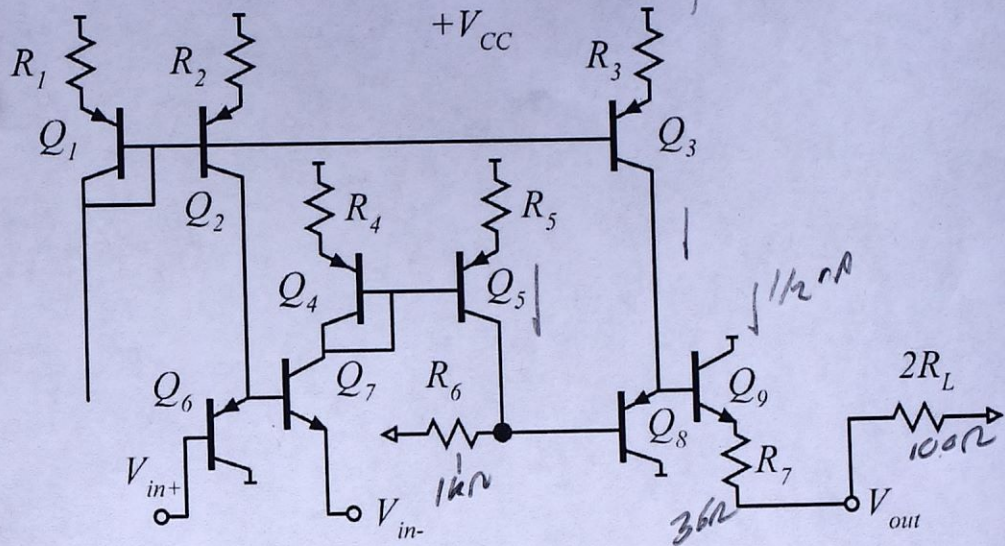Part d, 10 points.

The circuit is 100% symmetric, and can be represented by the simpler small-signal diagram below;



Find the following, using the actual value of β , i.e. $\beta=100$

	Voltage Gain	Input impedance
Q9	0.53	15.8 k Ω
Q8	1	1.88 M Ω
Q5	-3.805	2.6 k Ω
Q7	-1	2.6 k Ω
Q6	1	260 k Ω
Overall differential Vout/Vin	20.38	260 k Ω

Note: with some insight, you can find the combined gain of Q7/Q4/Q5 in a single step. If you would like to do so, omit the separate answers for Q5 and Q7 in the table above, and instead fill in the table below,

	Voltage Gain	Input impedance
Q7/Q4/Q5 combination.		

Q4

$$\left. \begin{array}{l} R_7 / 2R_L \text{ divider} \\ V_{out} / V_{S9} = \frac{100\Omega}{136\Omega} = 0.735 \\ Q9 A_v = \frac{136\Omega}{136\Omega + 1/g_m} = \frac{136\Omega}{136\Omega + 52\Omega} = 0.72 \end{array} \right\} 0.53$$

$$\frac{1}{2} [R_{i1} = \beta(188\Omega) = 18.8\text{k}\Omega]$$

Q8 $\frac{1}{2} [R_{eq} = R_{i9} = 18.8\text{k}\Omega]$

$$\frac{1}{2} [A_v = \frac{18.8\text{k}\Omega}{18.8\text{k}\Omega + 26\Omega} \approx 1 \text{ to } 1\% \text{ precision.}]$$

$$\frac{1}{2} [R_{i8} = \beta(18.8\text{k}\Omega) = 1.88\text{M}\Omega]$$

Q5 $\frac{1}{2} [R_{eq5} = 1\text{k}\Omega // 1.88\text{M}\Omega \approx 1\text{k}\Omega \text{ to } 1\% \text{ precision!}]$

$$\frac{1}{2} [A_{v5} = -g_m R_{eq5} = -1\text{k}\Omega / 26\Omega = -38.5]$$

$$\frac{1}{2} [R_{i5} = \beta / g_m = 2.6\text{k}\Omega]$$

Q7 $\frac{1}{2} [R_{eq} = 1/g_m // R_{i5} = 1/g_m \text{ to } 1\%]$
 $= 26\Omega$


$$1 [A_{v5} = -g_m R_{eq} = -26 / 26 = -1]$$

$$1 [R_{i7} = \beta / g_m = 2.6\text{k}\Omega]$$

Q6 $\frac{1}{2} [R_{eq} = R_{i7} = 2.6\text{k}\Omega]$ $1 [A_v = \frac{2.6\text{k}\Omega}{2.6\text{k}\Omega + 26\Omega} \approx 0.99 \approx 1]$

$$1 [R_{i6} \approx \beta R_{eq} = 260\text{k}\Omega]$$

Alternative for Q5/7

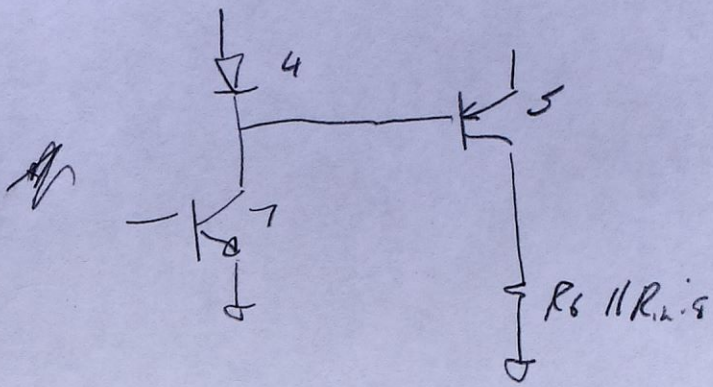

$$\begin{aligned} A_v &= -g_{m7} \cdot R_6 \parallel R_{in8} \\ &= \frac{1000 \mu\text{S}}{20 \Omega} = -39.5 \end{aligned}$$

2/1.

Note Q9A answers are the negative of Q9 answers.




Part e, 10 points

Maximum peak-peak output voltage (show all your work)

For this, you must use the full circuit diagram, not the half circuit diagram.

	magnitude and sign of maximum output signal swing due to <i>cutoff</i>	magnitude and sign of maximum output signal swing due to <i>saturation</i>
Transistor Q9	1.45V	N/A
Transistor Q9A	-1.45V	N/A
Transistor Q8	-2.03	+5V
Transistor Q8A	+2.03	-5V
Transistor Q5	+1.45V	N/A
Transistor Q5A	-1.45V	N/A
Transistor Q7	N/A	N/A
Transistor Q7A	N/A	N/A

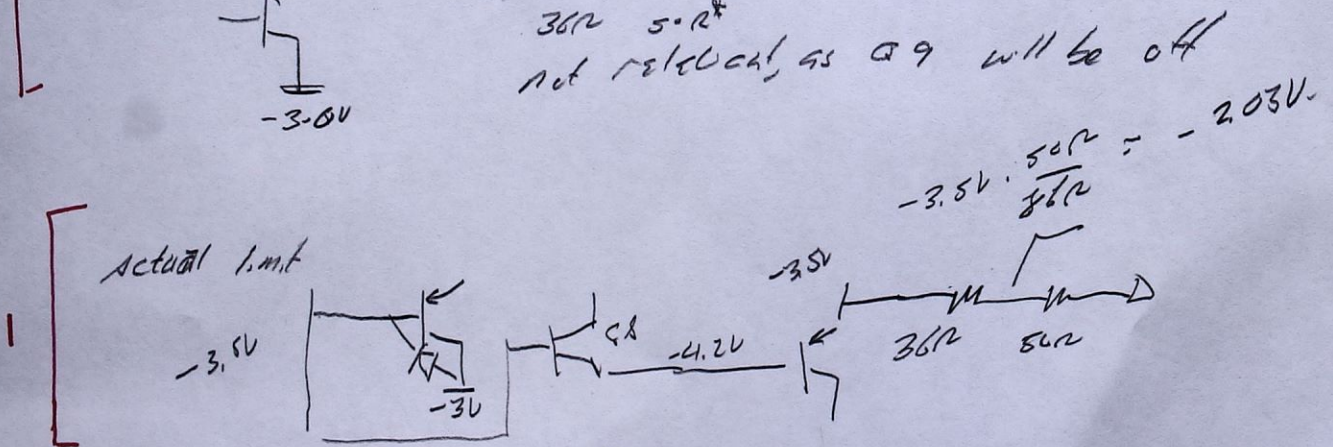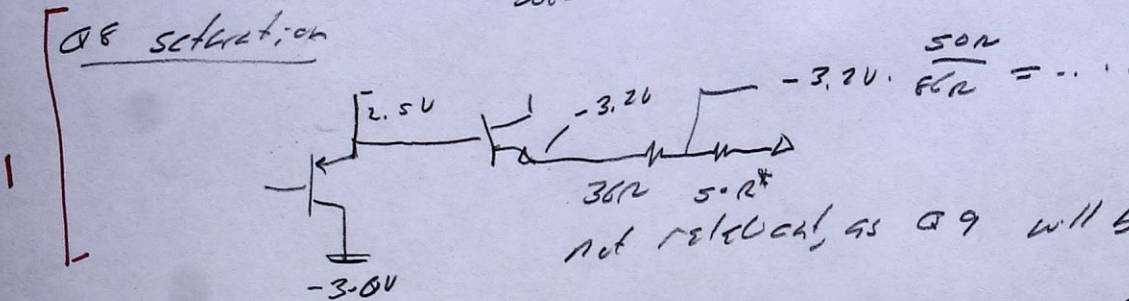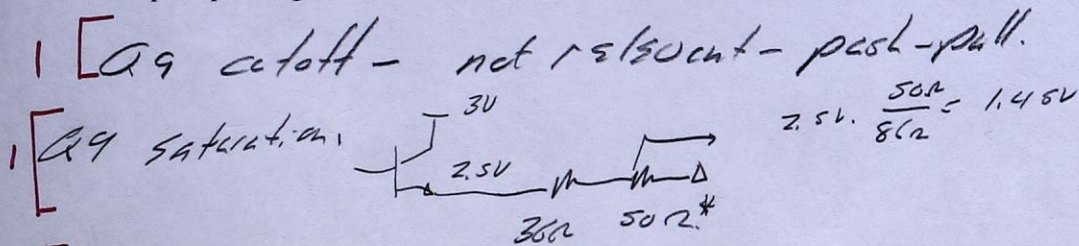Be warned: In some cases a limit is not relevant at all. Mark those answers "not relevant". But, give a 1-sentence statement below as to why it is not relevant. Q9/9A form a push pull stage, so be careful about your answer there. **Hint:** There is, effectively, another push-pull stage in the circuit, which will affect two of the other answers.




11

b


[note - we will accept use of $R_e = 100\Omega$ throughout this part]

1 [Cutoff Q8

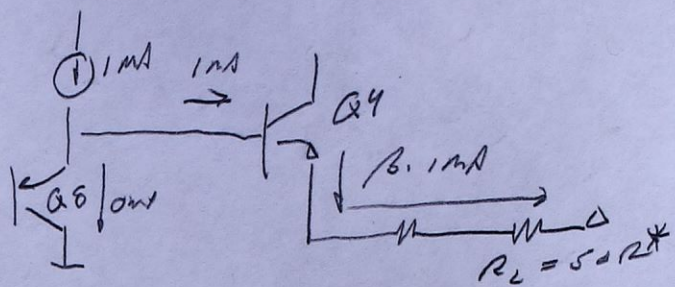

$$V_{out} = \beta \cdot 1mA \cdot R_L = 100mA \cdot 50\Omega = +5V$$

2 [Sat Q5:

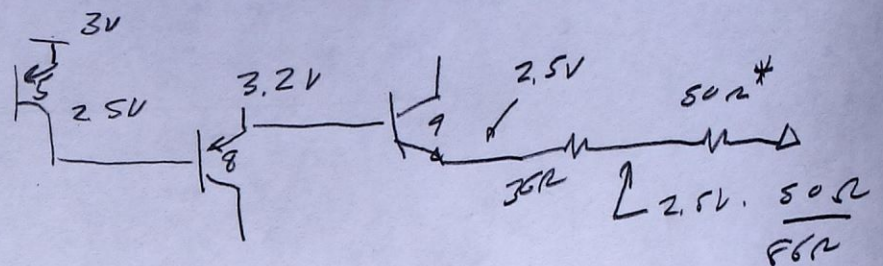

$$I_C = \frac{2.5V}{50\Omega} = 50\mu A$$

$$V_{CE} = 2.5V - I_C \cdot R_L = 2.5V - 50\mu A \cdot 50\Omega = 1.45V$$

1 [Cutoff Q5:

not relevant, as Q5/5A form a push-pull pair

1 [Sat Q7:

not relevant, as when $V_{CE7} = 0.5V$ V_{BE5} would be $2.5V$, giving a very large I_C for Q5.

1 [Cutoff Q7 -


not relevant, as Q7/7A and Q5/5A form a push pull pair

03V.

out]

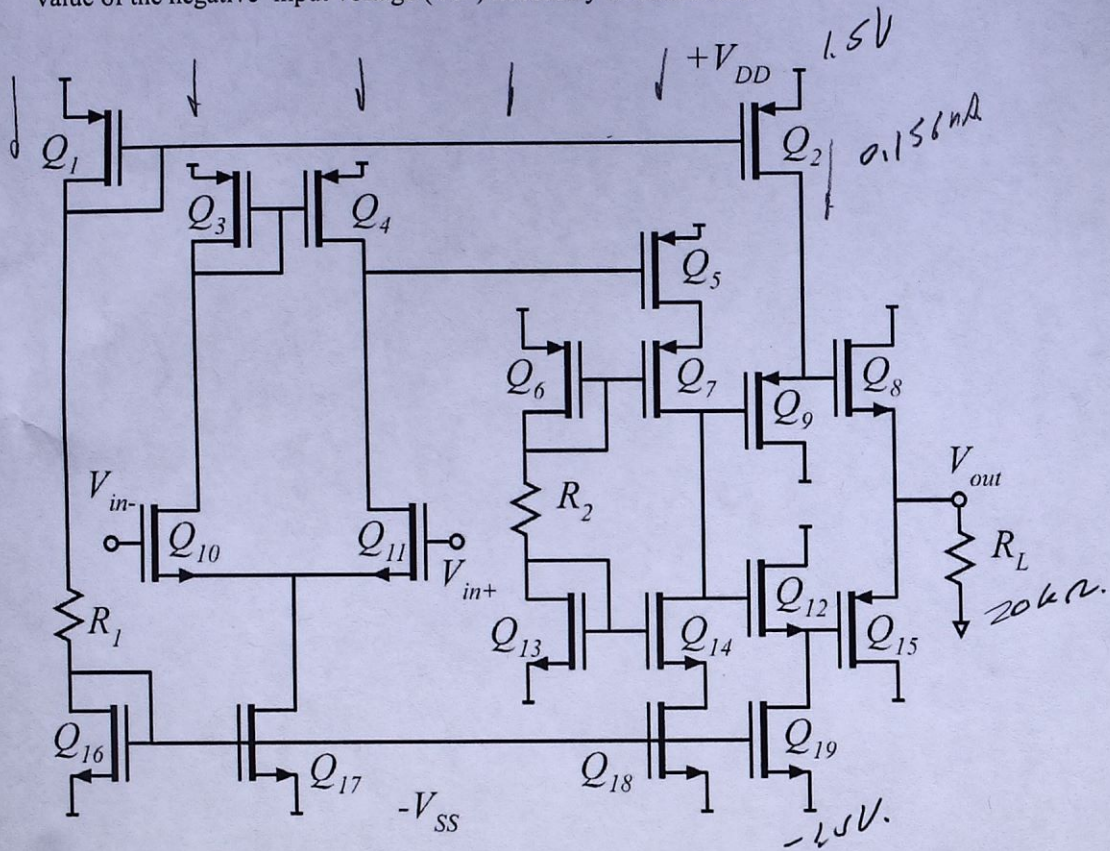Problem 2, 35 points

This is an Op-Amp---analyze the bias under the assumption that DC output voltage is zero volts, that the positive input V_{i+} is zero volts, and that we must determine the DC value of the negative input voltage (V_{i-}) necessary to obtain this.



The NMOSFETs and the PMOSFETS have a 0.20 V threshold, a 22nm gate length, 200 cm^2/Vs mobility, a 10^7cm/s injection velocity, and $1/\lambda = 6 \text{Volts}$. The gate oxide thickness is 1.0nm and the dielectric constant is 3.8. This gives

$$\mu c_{ox} W_g / 2L_g = 15.3 \text{ mA/V}^2 \cdot (W_g / 1\mu\text{m}) \text{ and}$$

$$v_{sat} c_{ox} W_g = 3.36 \text{ mA/V} \cdot (W_g / 1\mu\text{m}) \text{ (both are a bit unrealistic for a real technology).}$$

$$\text{and } v_{sat} L_g / \mu = 0.110 \text{ V}$$

$$V_{DD} = +1.5 \text{ V}, \quad -V_{SS} = -1.5 \text{ V}, \quad R_L = 20 \text{ kOhm}$$

Part a, 10 points

DC bias.

Approximation: ignore the term $(1 + \lambda V_{DS})$ in DC bias analysis.

Analyze the bias under the assumption that DC output voltage is zero volts, that the positive input V_{i+} is zero volts, and that we must determine the DC value of the negative input voltage (V_{i-}) necessary to obtain this.

All transistors **except Q6, Q13** have $|V_{gs}| = 0.3V$.

Q6 and Q13 have $V_{gs} = 0.35V$.

All transistors **except Q8, Q15, Q17** have $|I_D| = 0.156mA$.

Q8 and Q15 have $|I_D| = 1.56mA$.

You can figure out $|I_D|$ for Q17.

Find the gate widths of all transistors, plus R1 and R2.

Find:

Wg1= _____ Wg2= _____ Wg3= _____ Wg4= _____
 Wg5= _____ Wg6= _____ Wg7= _____ Wg8= _____
 Wg9= _____ Wg10= _____ Wg11= _____ Wg12= _____
 Wg13= _____ Wg14= _____ Wg15= _____ Wg16= _____
 Wg17= _____ Wg18= _____ Wg19= _____
 R1= _____ R2= _____

1 [$|V_{gs}| = 0.3V \rightarrow$ less than $V_{TL} + \Delta V \rightarrow$ mobility limit.

2 [$0.156mA = 15.3 \mu A \cdot \frac{W_9}{1\mu m} (0.3V - 0.2V)^2$
 $\rightarrow W_9 = 1.02 \mu m \approx 1 \mu m$
 for all T_n except Q17, Q8, Q15, 6, 13.

1 [Q8, 15 $\rightarrow W_9 = 10 \mu m$ (10:1 more I_D , same V_{gs})

2 [Q17: $0.312mA = 15.3 \mu A \cdot \frac{W_9}{1\mu m} (0.3V - 0.2V)$
 $\rightarrow W_9 = 2 \mu m$

1 [$R_1 \parallel I_1 = 0.156 \mu A, V = 2(1.5V - 0.3V) \Rightarrow R = 15.4 k\Omega$

1 [$R_2 \parallel I = 0.156 \mu A, V^{14} = 2(1.5V - 0.35V)$
 $\Rightarrow R = 14.7 k\Omega$

Q6, Q13

$$V_{gs} = 0.35V, \quad I_D = 0.156 \mu A$$


↳ more than $V_{th} + V_{ov} = 0.2V + 0.1V$

$$I_D = 0.156 \mu A = 3.36 \frac{\mu A}{V} \left(0.35V - 0.2V - \frac{0.11V}{2} \right) \cdot \frac{W_9}{L_9}$$

$$\Rightarrow W_9 = 0.490 \mu m$$

Part b, 10 points

DC bias

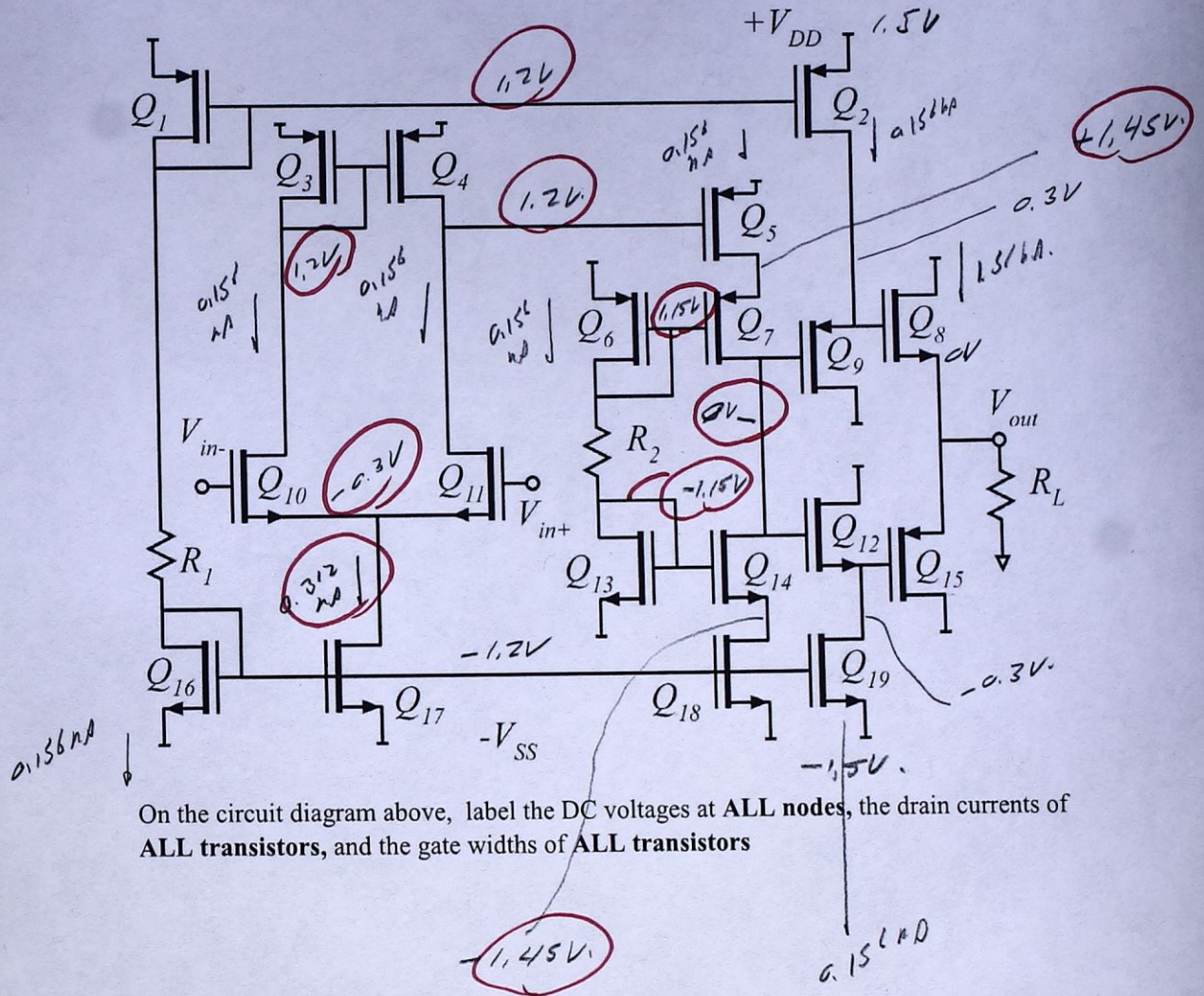

On the circuit diagram above, label the DC voltages at ALL nodes, the drain currents of ALL transistors, and the gate widths of ALL transistors

Part c, 15 points.

You will now compute the op-amp differential gain. *You must consider the $(1 + \lambda V_{DS})$ term in the FET IV characteristics when you do this.*

Find the following

	Voltage Gain	Input impedance
Transistor combination Q3,4,10,11	58.9	$\infty \Omega$
Q5,7	6940	∞
Q9 or Q12.	0.98	$\infty \Omega$
Q8 or Q15	0.99	$\infty \Omega$
Overall differential Vout/Vin	396000	$\infty \Omega$

Notes:

1) You can analyse Q5 and Q7 as separate stages, or as a combined stage using Norton/Thevenin methods. Don't ask for hints as to how to do this.

2) For Q9/12 and for Q8/15, you can assume that Q9 and Q12 are on for the positive signal swing and Q8 and Q15 are on for the negative signal swing. More accurately, you can assume, for the signal swing near zero volts, that all are on. If you take the latter approach (and do it correctly), you will receive a couple of extra credit points. One hint (don't ask for any other hints): use symmetry.

$$\begin{aligned}
 2 \quad & \tau_n = 2 \frac{C_{gs} - C_{gd}}{\sqrt{2}} \cdot \frac{W_g}{v} \\
 & = 3.06 \text{ ns for all } \tau_{L_n} \text{ except } Q_8, Q_{15}. \\
 & = 30.6 \text{ ns for } Q_8, Q_{15}.
 \end{aligned}$$


$$\begin{aligned}
 1 \quad & R_{DS} = 1 / I_D = 50 / 0.156 \text{ mA} = 38.5 \text{ k}\Omega \text{ all } \tau_{L_n} \text{ except } Q_8, Q_{15} \\
 & = 3.85 \text{ k}\Omega \quad Q_8, Q_{15}.
 \end{aligned}$$

$$\begin{aligned}
 \underline{Q_8} \quad & 1 \quad R_{L_{eq}} = R_L \parallel R_{DS8} = 20 \text{ k}\Omega \parallel 3.85 \text{ k}\Omega \\
 & = 3.22 \text{ k}\Omega \\
 & 1 \quad A_v = \frac{3.22 \text{ k}\Omega}{3.22 \text{ k}\Omega + \underbrace{1/g_m}_{32.6 \Omega}} = 0.990 \\
 & 1 \quad R_{i_n} = \underline{\underline{\infty}}
 \end{aligned}$$

$$\begin{aligned}
 \underline{Q_9} \quad & 1 \quad R_{L_{eq}} = R_{DS9} \parallel R_{DS2} = \frac{38.5 \text{ k}\Omega}{2} = 19.25 \text{ k}\Omega \\
 & 1 \quad A_v = \frac{19.25 \text{ k}\Omega}{19.25 \text{ k}\Omega + \underbrace{1/g_m}_{32.6 \Omega}} = 0.983 \\
 & 1 \quad R_{i_n} = \underline{\underline{\infty}}
 \end{aligned}$$

Q5/7/14/15

Use Norton method.

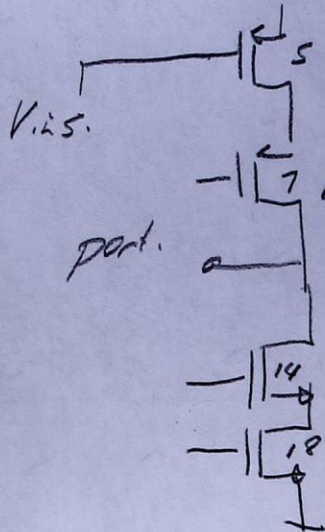

$R = (\text{some calculation}) = 4.57 \text{ M}\Omega$

$R = R_{DS14} (1 + g_{m14} R_{DS18}) = 4.57 \text{ M}\Omega$

Total impedance @ node = $\frac{4.57 \text{ M}\Omega}{2} = 2.28 \text{ M}\Omega$

short-circuit current = $g_{m5} \cdot V_{i5} \cdot \frac{R_{DS5}}{R_{DS5} + 1/g_{m7}}$

$g_{oi} \text{ of } Q5/7 = \frac{-g_{m5} \cdot 2.28 \text{ M}\Omega \cdot R_{DS5}}{R_{DS5} + 1/g_{m7}} = \frac{-6940}{0.99} \approx -7000$

g_{oi} of Q3/4/10/11

$R_{leg} = R_{DS4} \parallel R_{DS11} = \frac{38.5 \text{ k}\Omega}{2} = 19.25 \text{ k}\Omega$

$A_v = g_{m10} R_{leg} = 19.25 \text{ k}\Omega (3.06 \text{ mS}) = 58\%$

Q5/7/14/15

Part d, 10 points


Maximum peak-peak output voltage at the positive output V_{o+} (show all your work)

	magnitude and sign of maximum output signal swing due to <i>cutoff</i>	magnitude and sign of maximum output signal swing due to: <i>knee voltage</i> (saturation)
Transistor Q8	N/A	1.4V
Transistor Q15	N/A	-1.4V
Transistor Q9	+6V or large ignore	-1.7V
Transistor Q12	+6V or large ignore	+1.7V
Transistor Q2	N/A	+1.1V
Transistor Q19	N/A	-1.1V
Transistor Q7	-3.5V or N/A	1.35V
Transistor Q14	N/A	-1.35V

Be warned: in some cases a limit is not relevant. Mark those answers "not relevant"...

- 1 [Q8, 15 - cutoff not relevant - push pull.]
- 1 [Q5 knee voltage $+0.2V$ \uparrow \downarrow $+0.1V$ \downarrow $0.3V$ knee @ $V_{DS} = 0.1V$. $V_{out} = 1.5V - 0.1V = 1.4V$]
- 1/2 [Q15 knee voltage - identical calculation]
- 1/2 [Q9 cutoff $\Delta I_D = 0.15mA$ but $R_{DS(on)}$ is large \rightarrow large. $\Delta V = 0.15mA \cdot R_{DS(on)} = +6V \rightarrow$ large \rightarrow ignore.]
- 1/2 [Q12 cutoff - identical calculation.]
- 1 [Q9 knee voltage. $-1.4V$ \downarrow $+0.1V$ \downarrow $+0.3$ $-1.7V$ - beyond supply]
- 1/2 [Q12 knee voltage $-1.5V$ identical calculation $\rightarrow +1.7V$.]


Q2 knee voltage

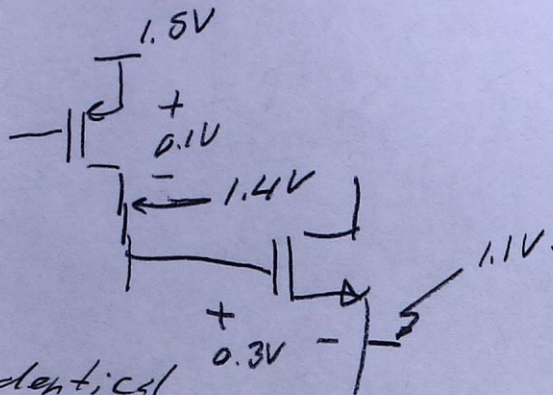

1/2 [Q19 knee - identical calculation \rightarrow -1.1V.

1/2 [Q2/19 cutoff - not relevant - I_d does not vary.

Q7 knee voltage

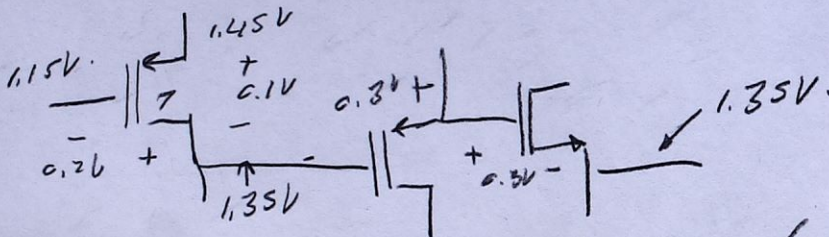


1/2 [Q14 knee voltage - identical calculation.

Q7 cutoff

$$\Delta I = 0.156 \text{ mA}, R_{eq} \parallel R_{out7} = 2.28 \text{ M}\Omega$$
$$\Delta V = \text{product} = -355 \text{ V} \rightarrow \text{Very large, not relevant}$$


1/2 [Q14 cutoff - not relevant

Problem 3, 30 points

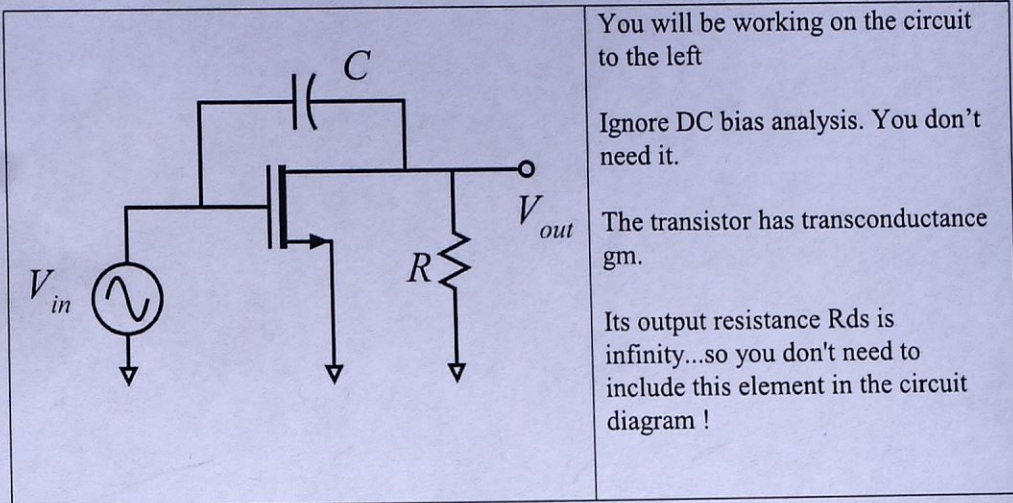

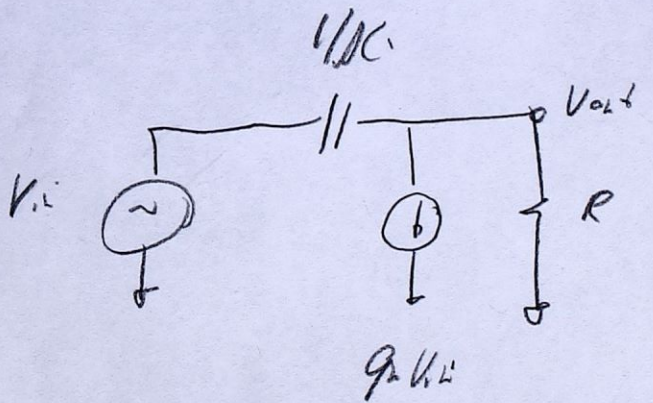Part a, 7 points

Draw a small-signal equivalent circuit of the circuit.



all elements must be labelled

*↑
control must be identical*

Part b, 8 points

$g_m = 10 \text{ mS}$, $C = 1 \text{ nF}$, $R = 1000 \text{ Ohms}$

Find, by nodal analysis, a small-signal expression for V_{out}/V_{in} . Be sure to give the answer with ****correct units**** and in ratio-of-polynomials form, i.e.

$$\frac{V_{out}(s)}{V_{gen}(s)} = K \cdot \frac{1 + b_1s + b_2s^2 + \dots}{1 + a_1s + a_2s^2 + \dots} \text{ or (as appropriate) } \frac{V_{out}(s)}{V_{gen}(s)} = K \cdot (s\tau)^n \cdot \frac{1 + b_1s + b_2s^2 + \dots}{1 + a_1s + a_2s^2 + \dots}$$

Note that an expression like

$$\frac{V_{out}(s)}{V_{gen}(s)} = \frac{1}{1 + (3 \cdot 10^{-6})s} \text{ is dimensionally wrong; } \frac{1}{1 + (3 \cdot 10^{-6} \text{ seconds})s} \text{ is dimensionally correct}$$

$V_{out}(s)/V_{in}(s) =$ _____

$\sum I = 0 \text{ @ } V_{out}$

$$4 \left[V_{out} \left(\frac{1}{R} \right) + g_m V_{in} + (V_{out} - V_{in}) (sC) = 0 \right]$$

$$V_{out} \left(\frac{1}{R} + sC \right) = V_{in} (sC - g_m)$$

$$\frac{V_o/V_{in}}{s} = \frac{sC - g_m}{sC + 1/R} = \frac{-(g_m - sC)}{sC + 1/R} = -g_m R \frac{1 - sC/g_m}{1 + sCR}$$

$$\frac{V_o(s)}{V_{in}(s)} = -g_m R \cdot \frac{1 - sC/g_m}{1 + sCR}$$


$$= -10 \cdot \frac{1 - s \frac{1000 \text{ nS}}{10}}{1 + s \frac{1 \mu\text{S}}{10}}$$

Part c, 7 points

Find any/all pole and zero frequencies of the transfer function, in Hz:

points deducted if these are not correctly located

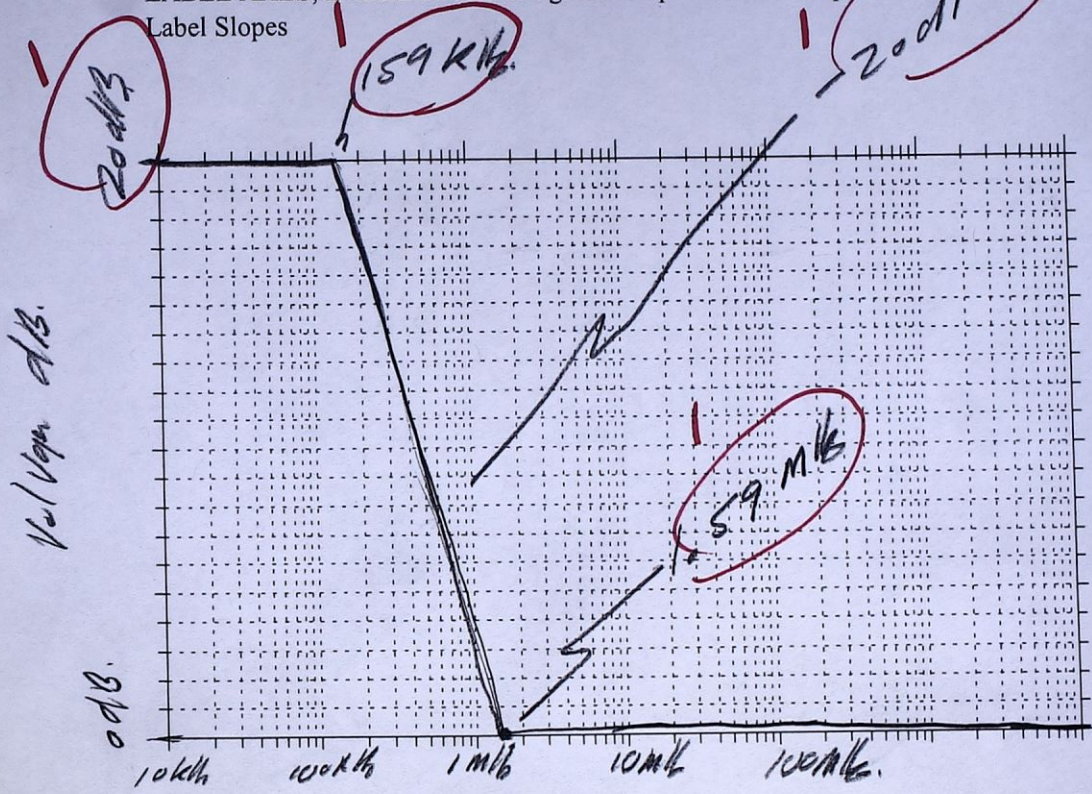Draw a clean Bode Plot of V_{out}/V_{in} , LABEL AXES, LABEL all relevant gains and pole or zero frequencies, Label Slopes



$$f_p = \frac{1}{2\pi RC} = 159 \text{ kHz}$$

$$f_z = \frac{f_m}{2\pi C} = 1.59 \text{ MHz}$$


$$f_m R = 10 \text{ ms} \cdot 1000 \Omega = 10 \rightarrow 20 \text{ dB/dec}$$

Part d, 8 points

$V_{in}(t)$ is a 0.1 V amplitude step-function.

Find $V_{out}(t) =$ _____

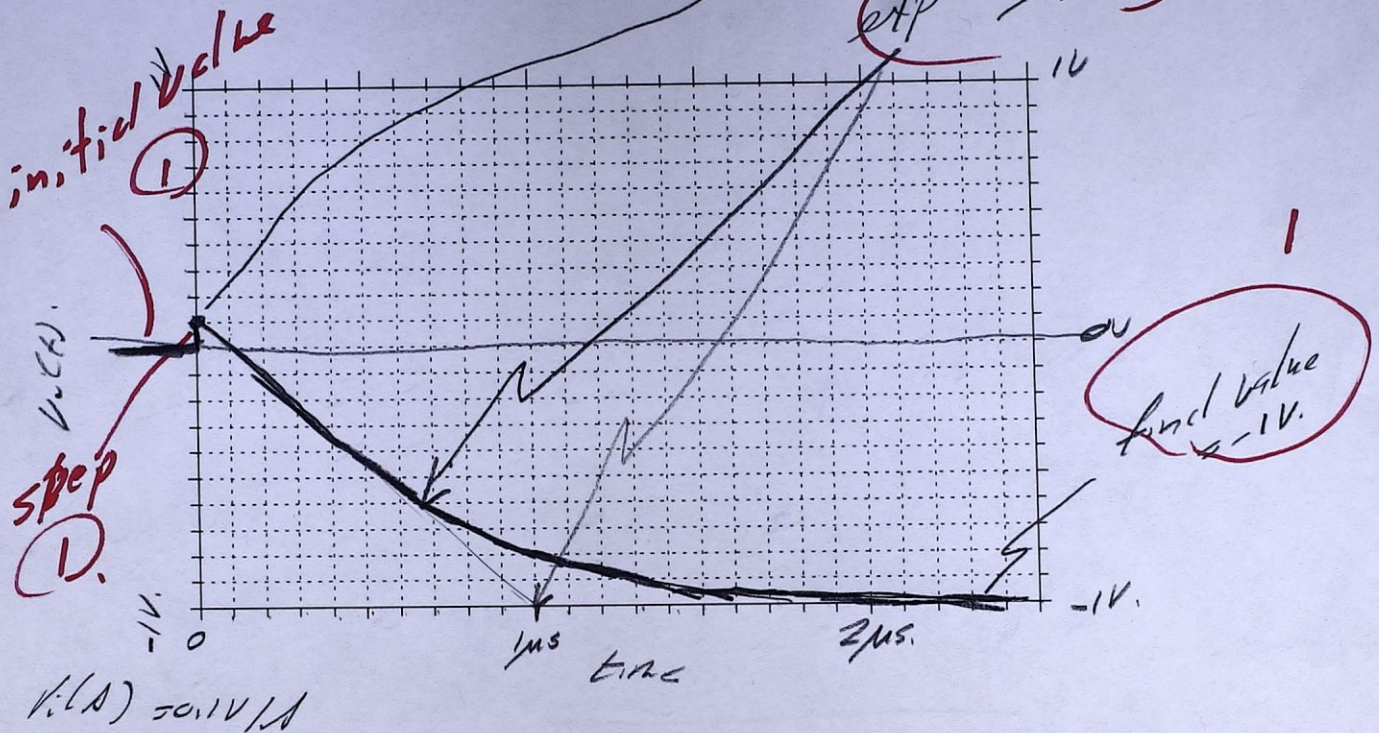Plot it below. Label axes, show initial and final values, show time constants.



$$\begin{aligned}
 V_o(s) &= \frac{0.1V}{s} (-g_m R_L) \frac{1 - sT_f}{1 + sT_p} = \frac{0.1V (-g_m R_L)}{s} \left[1 - \frac{s(T_f + T_p)}{1 + sT_p} \right] \\
 &= \frac{0.1V (-g_m R_L)}{s} + (g_m R_L) 0.1V \cdot \frac{T_f + T_p}{T_p} \frac{s T_p}{1 + s T_p} \\
 &= \underline{\underline{-\frac{1V}{s} + 1.1V \frac{s T_p}{1 + s T_p}}} \rightarrow \underline{\underline{V_o(t) = -1V \cdot u(t) + 1.1V u(t) e^{-t/1\mu s}}}
 \end{aligned}$$