

Final Exam, ECE 137A

Thursday March 17, 12 - 3 p.m.

Name: *solution.*

Closed Book Exam:

Class Crib-Sheet and 4 pages (4 surfaces) of student notes permitted

Do not open this exam until instructed to do so. Use any and all reasonable approximations (5% accuracy), *after stating & justifying them.*

Show your work:


Full credit will not be given for correct answers if supporting work is missing.

Good luck

Part	Points Received	Points Possible	Part	Points Received	Points Possible
1a		6	2c		10
1b		5	2d		10
1c		4	3a		10
1d		10	3b		10
1e		10	3c		10
2a		10			
2b		5			
total		100			

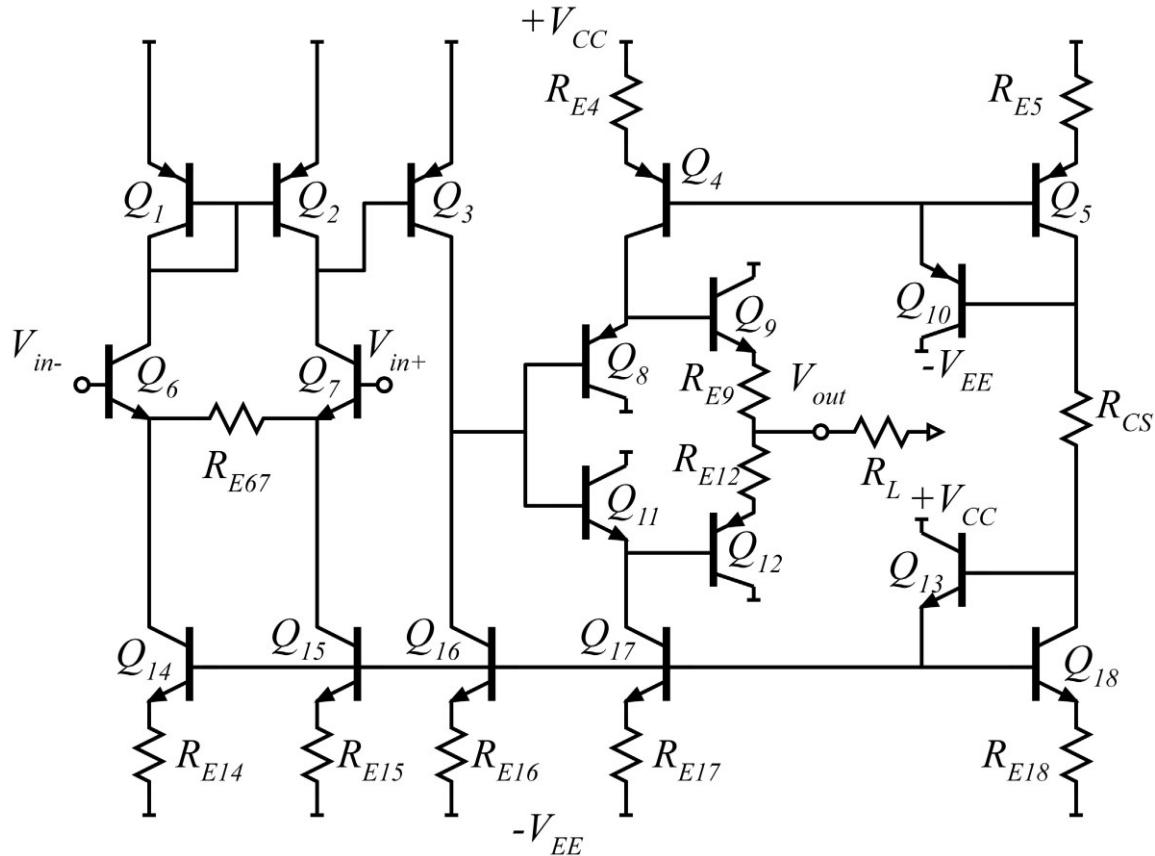Problem 1, 35 points

This is an Op-Amp---analyze the bias under the assumption that DC output voltage is zero volts, that the positive input V_{in+} is zero volts, and that we must determine the DC value of the negative input voltage (V_{in-}) necessary to obtain this.



All the transistors have the same (matched) I_S , have $\beta = 100$, and $V_A = \text{*infinity*}$ Volts.

$V_{CE(sat)} = 0.5\text{V}$. V_{be} is approximately 0.7V , but use $V_{be} = (kT/q) \ln(I_E/I_S)$ when necessary or appropriate. The supplies are $+3\text{Volts}$ and -3Volts .

All transistors have the same I_S .

The resistors R_E5 and R_E18 have a 300mV DC voltage drop across them.

$R_E67=100\text{ Ohms}$, $R_L=1000\text{ Ohms}$.

DC bias currents: $I_{C6}=I_{C7}=I_{C9}=I_{C12}=I_{C18}=0.1\text{ mA}$. $I_{C3}=I_{C8}=I_{C11}=0.2\text{mA}$

Part a, 6 points

DC bias---to simplify ,assume $\beta = \infty$ for the DC analysis only.

Analyze the bias under the assumption that DC output voltage is zero volts, that the positive input V_{i+} is zero volts, and that we must determine the DC value of the negative input voltage (V_{i-}) necessary to obtain this.

(Hint, this should give $V_{i-} = 0V$)

Find the value of the following resistors:

$$R_{e4} = \underline{1.4\text{k}\Omega}, R_{e5} = \underline{3\text{k}\Omega}, R_{e9} = \underline{180\text{\Omega}}, R_{e12} = \underline{180\text{\Omega}}, R_{e14} = \underline{3\text{k}\Omega}, \\ R_{e15} = \underline{3\text{k}\Omega}, R_{e16} = \underline{1.4\text{k}\Omega}, R_{e17} = \underline{1.4\text{k}\Omega}, R_{e18} = \underline{3\text{k}\Omega}, R_{cs} = \underline{26\text{k}\Omega}.$$

$$\frac{1}{2} [R_{e14} = R_{e15} = R_{e18} = \frac{0.8V}{100\mu A} = 3\text{k}\Omega]$$

$$V_{e16} = V_{e17} = V_{e18} + V_T \ln \frac{200\mu A}{100\mu A} \\ = V_{e18} + 18mV$$

| so the voltage drops across R_{e16} & R_{e17}
are $200mV - 18mV = 282mV$

$$\frac{1}{2} [R_{e16} = R_{e17} = \frac{282mV}{200\mu A} = \underline{\underline{1.41\text{k}\Omega}}]$$

$$\frac{1}{2} [\text{Some calculation for } R_{e4} \rightarrow 1.41\text{k}\Omega]$$

$$\frac{1}{2} [\text{similar calculation for } R_{e5} = \frac{300mV}{100\mu A} = 3\text{k}\Omega]$$

$$\frac{1}{2} [R_{eq} = R_{e12} = \frac{V_T}{100\mu A} \ln \left(\frac{200\mu A}{100\mu A} \right) = \frac{18mV}{0.1mA} = 180\Omega]$$


$$\frac{1}{2} [R_{cs} = \frac{2(1.3V)}{0.1mA} = \frac{2.6V}{0.1mA} = \underline{\underline{26\text{k}\Omega}}]$$

Part b, 5 points

114 μ A each
for yellow

$$\beta = 100 \quad V_A = \infty V$$

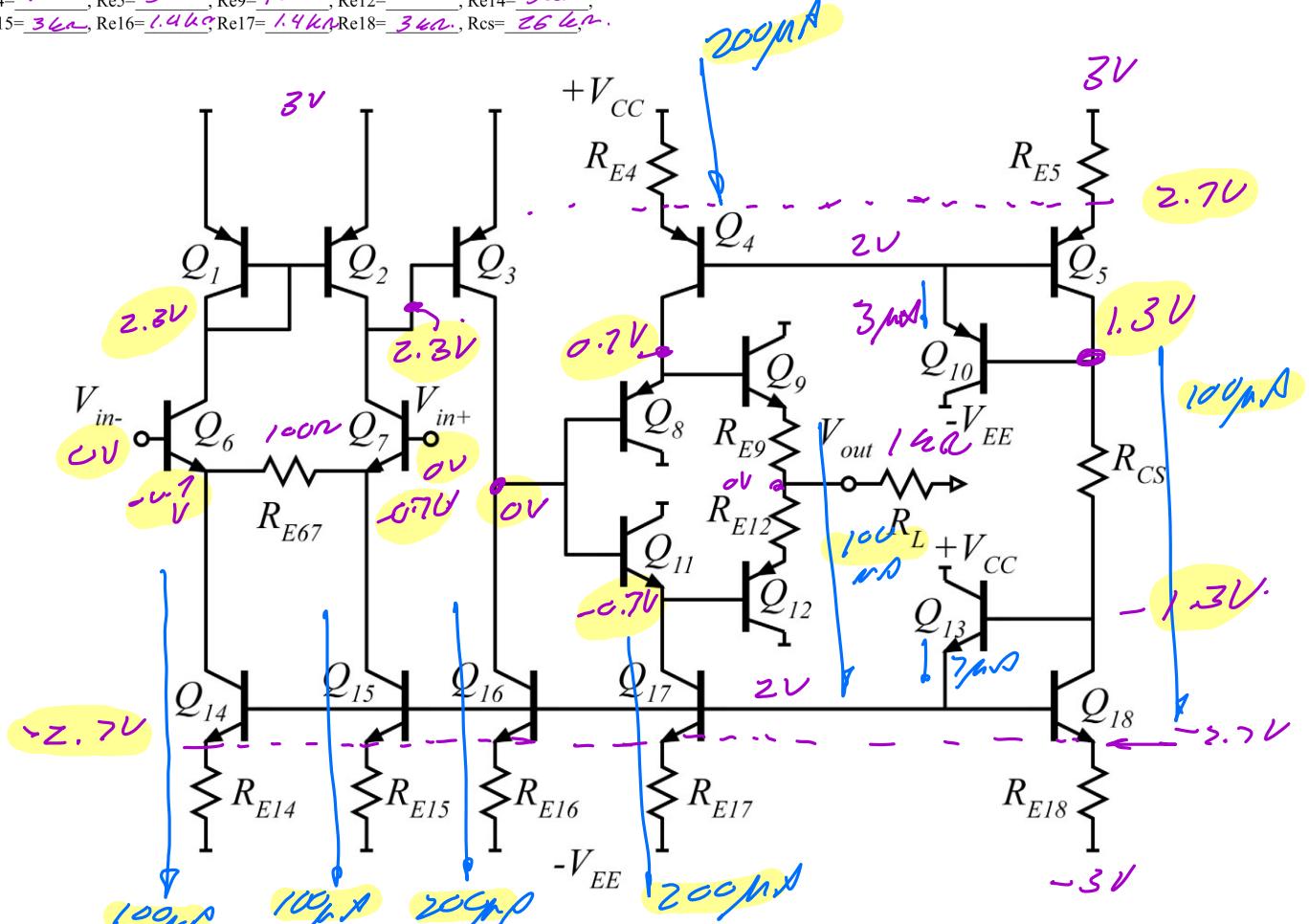Find the value of the following resistors:
 $R_{E4} = 1.4 \text{ k}\Omega$, $R_{E5} = 3 \text{ k}\Omega$, $R_{E9} = 180 \text{ }\mu\text{A}$, $R_{E12} = 180 \text{ }\mu\text{A}$, $R_{E14} = 3 \text{ k}\Omega$,
 $R_{E15} = 3 \text{ k}\Omega$, $R_{E16} = 1.4 \text{ k}\Omega$, $R_{E17} = 1.4 \text{ k}\Omega$, $R_{E18} = 3 \text{ k}\Omega$, $R_{CS} = 26 \text{ k}\Omega$.



On the circuit diagram above, label the DC voltages at ALL nodes, and the DC collector currents of all transistors. Label the values of all resistors.

$$I_{E13} = \frac{I_{C14} + I_{C15} + I_{C18} + I_{C17} + I_{C16}}{\beta}$$

$$\Rightarrow \frac{700 \mu\text{A}}{100} = 7 \mu\text{A}$$

$$I_{E10} = \frac{I_{C4} + I_{C5}}{\beta} = \frac{300 \mu\text{A}}{100} = 3 \mu\text{A}$$

Part c, 4 points

find the following

device	Q1	Q2	Q3	Q4	Q5	Q6	Q7	Q8
gm, mS	3.85	3.85	7.7	7.7	3.85	3.85	3.85	7.7

device	Q9	Q10	Q11	Q12	Q13	Q14	Q15	Q16
gm, mS	3.85	don't bother*	7.7	3.85	don't bother*	3.85	3.85	7.7

device	Q17	Q18
gm, mS	7.7	3.85

*don't bother calculating these

2 $I_C = 100\mu A$ for Q1, 2, 6, 7, 14, 15, 9, 12, 5, 18

$$g_m = \frac{1}{260\Omega} = 3.85 \text{ mS}$$

2 $I_C = 200\mu A$ for Q3, 16, 4, 6, 11, 17

$$g_m = \frac{1}{130\Omega} = 7.7 \text{ mS}$$


Note that all R_{ce} are $\infty \Omega$

Part d, 10 points.

Find the following, *using the actual value of β , i.e. $\beta=100$*

	Voltage Gain	Input impedance
Q9 or Q12	0.694	144 kΩ
Q8 or Q11	0.999 ≈ 1	14.4 MΩ
Q3	-111,000	13 kΩ.
Q1,2,6,7 combination.	-41.9	62 kΩ
Overall differential Vout/Vin	$3.2 \cdot 10^6$	62 kΩ

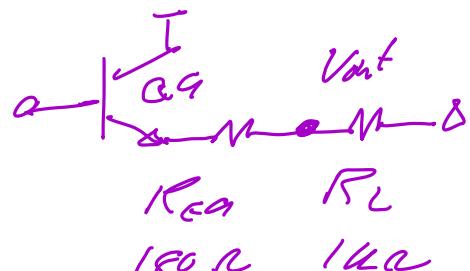Assume that either Q9 or Q12 is on; here I assume Q9



Q9: EF

$$1/2 \left[R_{\text{eqg}} = (R_{\text{EQ}} + R_2) = 1.18 \text{ kN} \right]$$

$$| \left[\text{Avg} = \frac{1400}{1400 + 1800} \cdot \frac{1400 + 1800}{1400 + 1800 + 2600} = 0.694 \right]$$

$$R_{ring} = \frac{\beta(140n + 180n + 260n)}{s_{100}} = 144 \text{ kN}$$

Q8: EK

$$1/2 \left[R_{\text{eq} \infty} = R_{L9} = 144 \text{ k}\Omega \right] \rightarrow 130 \Omega$$

$$1 \left[N_{0.8} = 144k_2 / (144k_2 + 1/q_{0.8}) = 0.999 \right] = 1$$

13082

$$1 \left[R_{in} = \beta (144 kR + 1/g_m) \right] \stackrel{9}{=} \beta \cdot \frac{144 kR}{100} = 14.4 M\Omega$$


Q3: CE $\frac{1}{2}$ $R_{leg3} = R_{in8} = 14.4 \text{ M}\Omega$

| $A_{v3} = -g_m3 R_{leg3} = -\frac{R_{leg3}}{r_{e3}} = \frac{14.4 \text{ M}\Omega}{130\Omega} = -111,000$

| $R_{in3} = \beta 1/g_m3 = 100 \cdot 130\Omega = 13 \text{ k}\Omega$.

Q1, 2, 6, 7 $\frac{1}{2}$ $R_{leg7} = R_{in3} = 13 \text{ k}\Omega$.

| $A_v = \frac{R_{leg7}}{50\Omega + 1/g_m7}$
 $= \frac{13 \text{ k}\Omega}{50\Omega + 260\Omega} = -41.9$

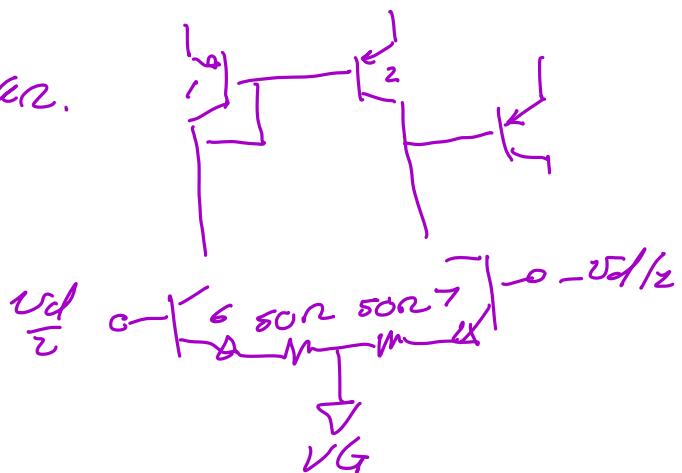

| Differential input impedance between $V^+ \text{ and } V^-$
 $R_{in \text{ diff}} = \beta (R_{leg7} + 1/g_m6 + 1/g_m7)$
 $= 100 (100\Omega + 260\Omega + 260\Omega)$
 $= 100 \cdot 620\Omega = 62 \text{ k}\Omega$

Part e, 10 points

Maximum peak-peak output voltage (**show all your work**)



For this, you must use the full circuit diagram, not the half circuit diagram.

	magnitude and sign of maximum output signal swing due to <i>cutoff</i>	magnitude and sign of maximum output signal swing due to <i>saturation</i>
Transistor Q9	not relevant	+2.12V ↑
Transistor Q12	not relevant	-2.12V ↓
Transistor Q8	+2.0V ↑	-2.2V ↓
Transistor Q11	-2.0V ↓	+2.2V ↑
Transistor Q4	not relevant	+1.04V ↑
Transistor Q17	not relevant	-1.04V ↓

Be warned: In some cases a limit is not relevant at all. Mark those answers "not relevant". But, give a 1-sentence statement below as to why it is not relevant. Q9/12 form a push pull stage, so be careful about your answer there.



Q12, Q9 cutoff - not relevant - push-pull

Q9 saturation:

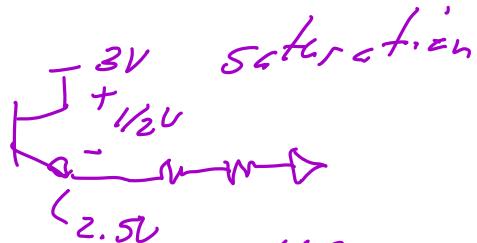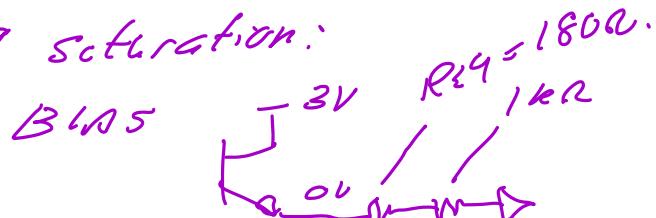



$$\Delta V_{emitter} = +2.5V \quad \Delta V_{out} = 2.5V \cdot \frac{1k\Omega}{1.18k\Omega} = +2.12V$$

Q12 saturation:

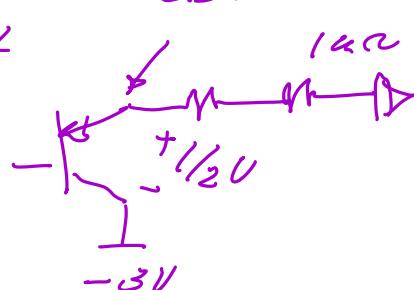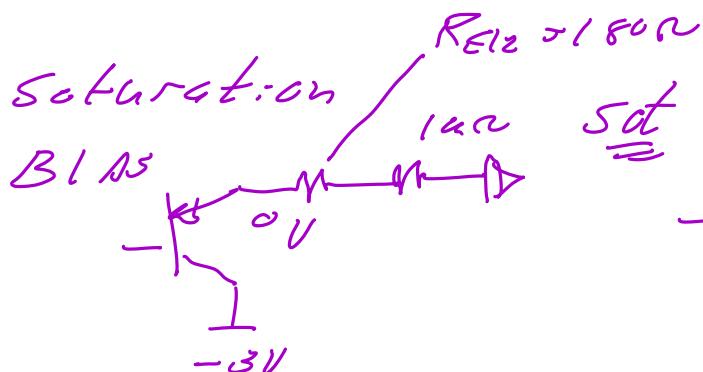

$$\Delta V_{emitter} = -2.5V \quad \Delta V_{out} = -2.5V \cdot \frac{1k\Omega}{1.18k\Omega} = -2.12V$$

Q_8 saturation.

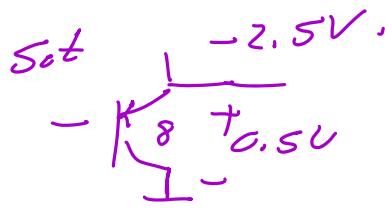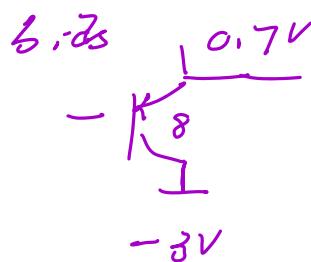



$$\Delta V_{\text{Emitter}} = -3.2V \quad \Delta V_{\text{out}} = -3.2V \cdot N_{\text{eq}} = -2.2V.$$

Q_{11} saturation.

This is +/- symmetric with Q_8 saturation
 $\rightarrow \Delta V_{\text{out}} = +2.2V$

Q_8 cutoff bias
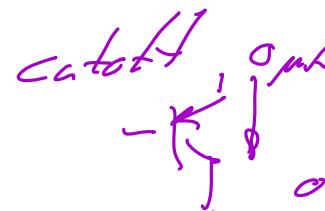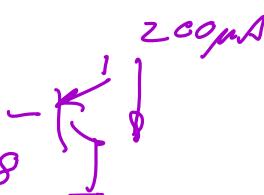
$$V_{\text{Emitter}} = 200\mu A \cdot R_{L\text{eq} 8} \\ = 200\mu A \cdot 144k\Omega \\ = 28.8V$$




$$\Delta V_{\text{out}} = 28.8V \cdot N_{\text{eq}} = 20V$$


Q_{11} cutoff

This is +/- symmetric with Q_8 cutoff
 $\rightarrow \Delta V_{\text{out}} = -20V$

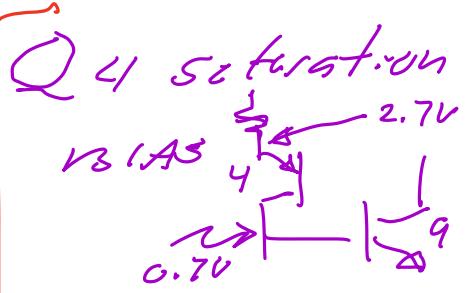Q_4 and Q_{17} cutoff - not relevant; I_C not modulated.


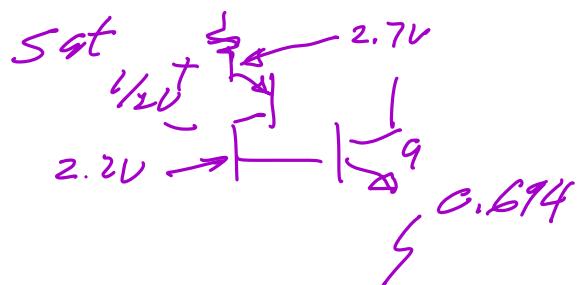
$$\Delta V_{\text{Collector}} = 1.5V \quad \Delta V_{\text{out}} = 1.5V \cdot N_A q = +1.04V$$




$Q17$ saturation.

This is \pm symmetric with $Q4$ saturation
 $\rightarrow \Delta V_{\text{out}} = -1.04V$

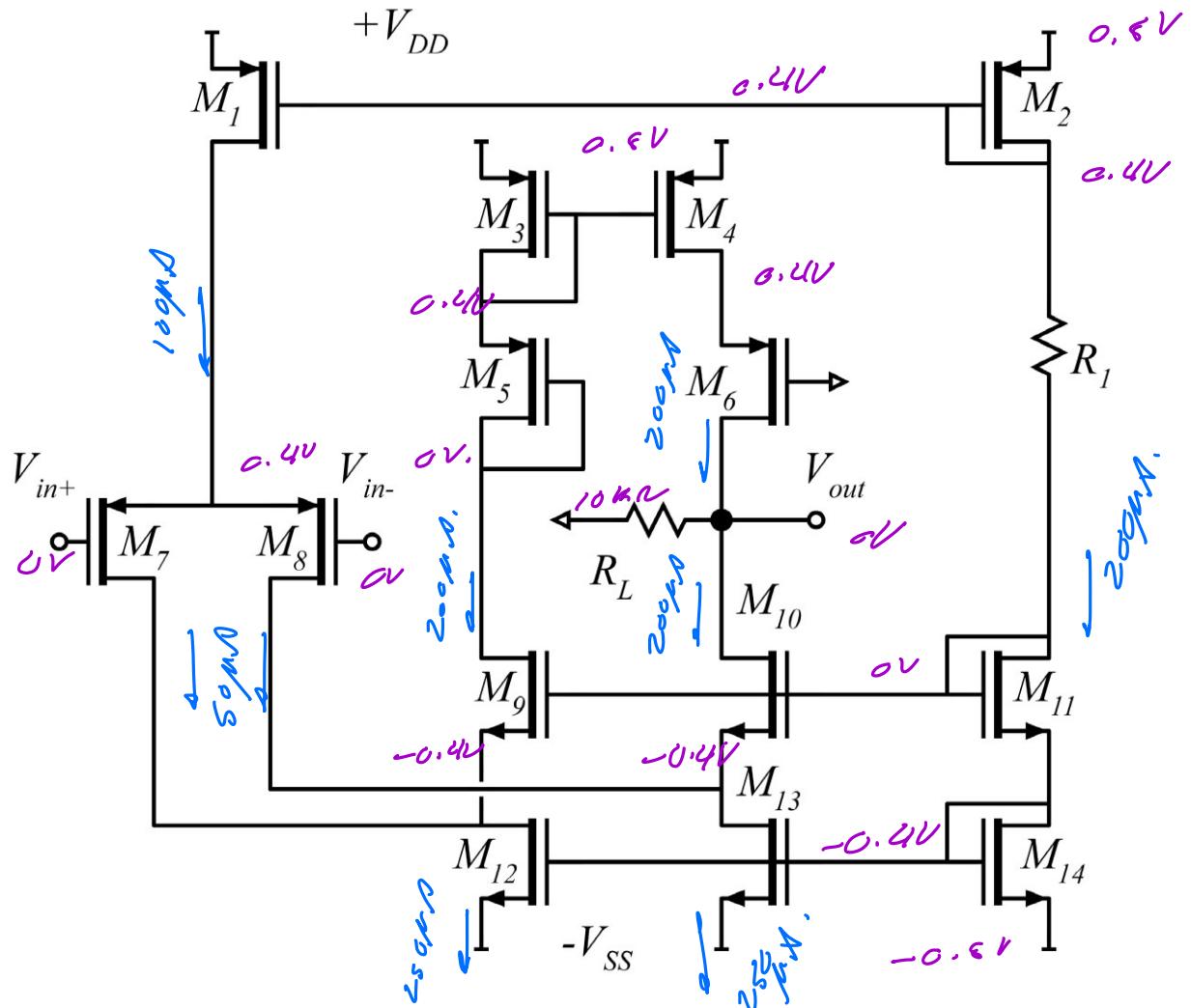Problem 2, 35 points

This is an NOT an Op-Amp: Analyze under the assumption that the differential and common mode input voltages are at zero volts



The NMOSFETs have $K_\mu = \mu C_{gs} W_g / 2L_g = 10 \text{ mA/V}^2 \cdot (W_g / 1\mu\text{m})$

$K_v = c_{gs} v_{inj} W_g = 2.0 \text{ mA/V} \cdot (W_g / 1\mu\text{m})$, $\Delta V = v_{inj} L_g / \mu = 0.10 \text{ V}$, $V_{th} = 0.3 \text{ V}$,

$1/\lambda = 5 \text{ V}$

The PMOS have identical parameters, except, of course, V_{th} is negative.

$V_{DD} = +0.8 \text{ V}$, $-V_{SS} = -0.8 \text{ V}$, $R_L = 10 \text{ k}\Omega$

All transistors have $|V_{gs}| = 0.4 \text{ V}$

M7,8 are biased at $I_D = 50 \mu\text{A}$.

M5,6,9,10,11 are biased at $I_D = 200 \mu\text{A}$

Part a, 10 points

DC bias.

Find the Gate widths, in μm , of
M1 $0.43\mu\text{m}$, M7 $0.43\mu\text{m}$

Note that, by using the mobility-limited formula $g_m = 2I_D / (V_{gs} - V_{th})$, we can solve the exam without calculating any of the FET widths. **So, there's no reason to spend time calculating other FET widths.**

FETs M7 & M8: $\left[V_{BS} = 0.8V, V_{GS} = 0.4V \right]_2$


5 $\left[I_D = \frac{10\text{mA}}{\sqrt{2}} \underbrace{(V_{GS} - V_{BS})^2}_{0.1V} \frac{W_g}{1\mu\text{m}} \left(1 + \frac{V_{BS}}{V_A} \right) \right]$
 $50\mu\text{A}$

3 $\rightarrow W_g = 0.43\mu\text{m}$

1/61 pt each

Part b, 5 points

DC bias

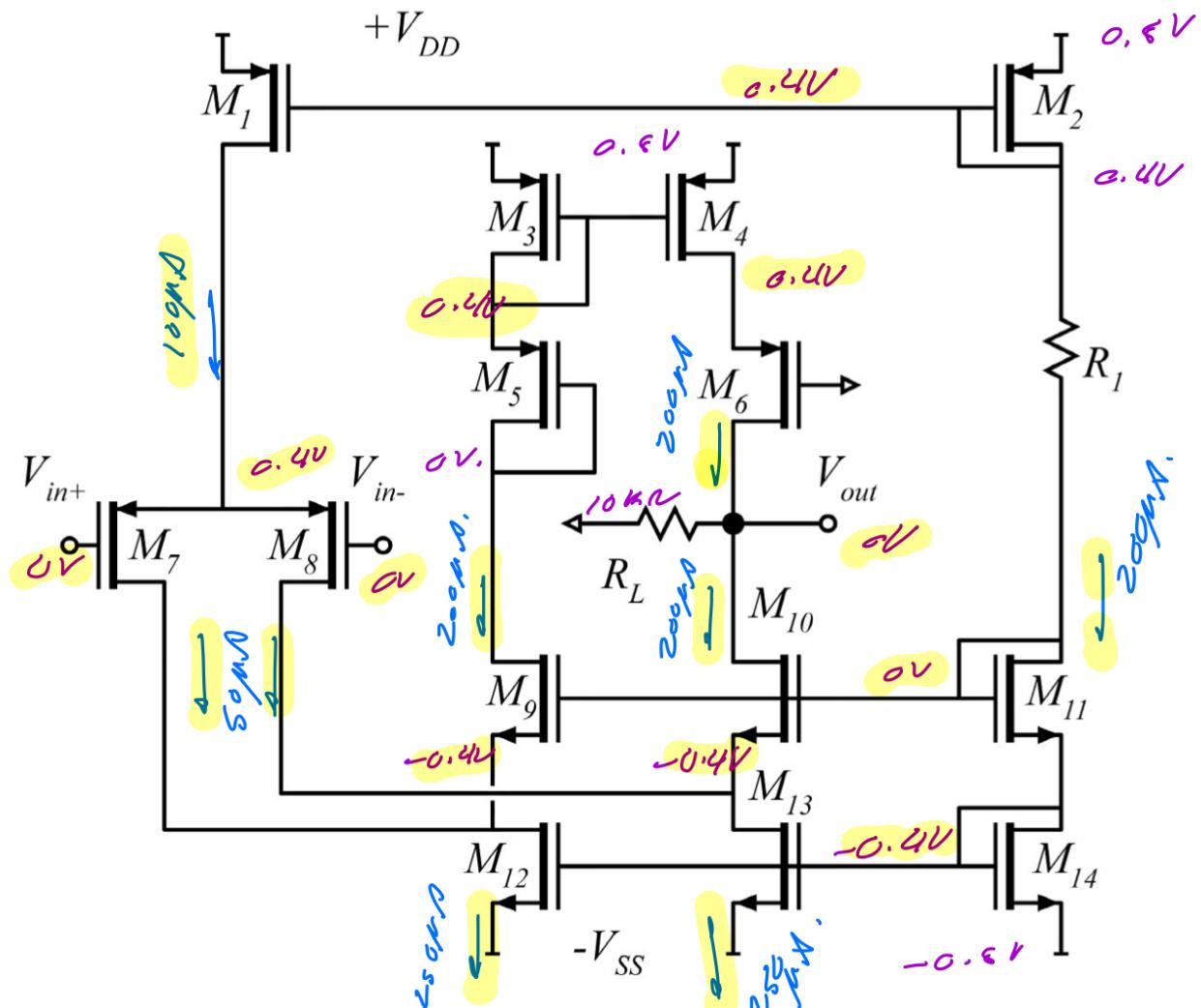

On the circuit diagram above, label the DC voltages at **ALL nodes**, the drain currents of **ALL transistors**

Part c, 10 points.

This amplifier has *two* signal paths between input and output.
 One is the path (M7 and M8, M9, M3, M4, M6, output).
 The other is the path (M7 and M8, M10, output).

You will now compute the differential gain for the path (M7 and M8, M10, output).

Find the following

	Voltage Gain	Input impedance
Transistor M10	28.6	350Ω
M7-M8 differential pair	0.1715	$\infty \Omega$
Overall differential Vout/Vin for this path	4.90	$\infty \Omega$

$$R_{out4} = R_{DS} = 1/I_D = 5V/200\mu A = 25k\Omega$$

$$g_{m6} = \frac{2I_D}{(V_{GS}-V_{TH})} = \frac{2(0.2mA)}{0.1V} = \frac{0.4mA}{0.1V} = 4ms = \frac{1}{250\Omega}$$

$$R_{out6} = R_{DS6}(1 + g_{m6}R_{out4})$$

$$= 25k\Omega (1 + 25k\Omega \cdot 4ms) = 25k\Omega (101)$$

$$= 2.52 M\Omega$$

$$R_{Ceq10} = R_c || R_{out6} = 10k\Omega || 2.5M\Omega = 9.98k\Omega \approx 10k\Omega$$

$$A_{D1510} = R_{DS6} = 25k\Omega ; g_{m10} = g_{m6} = 4ms$$

$$R_{i2,10} = 1/g_{m10} (1 + R_{Ceq6}/R_{DS10})$$

$$= 250\Omega (1 + 10k\Omega /25k\Omega) = 350\Omega$$

$$A_{v10} = R_{Ceq10} / R_{i2,10} = \frac{10k\Omega}{350\Omega} = 28.6$$

$$R_{Ceq8} = R_{DS8} || R_{DS13} || R_{in10}$$

$$= \frac{5V}{50\mu A} || \frac{5V}{250\mu A} || 350\Omega =$$

$$= 100k\Omega // 20k\Omega // 360\Omega = 343\Omega$$

$$g_{m8} = \frac{2(50mA)}{0.1V} = \frac{0.1mA}{0.1V} = 1mA$$

$$A_{v8,2} = \frac{1}{2} \cdot g_{m8} \cdot R_{c8,2} = \underline{\underline{0.1715}}$$

↓ ↓ ↓
 diff 1mA 343Ω

$Z_{8,2}$

$$\frac{Z_{8,2}}{= 4.9\Omega} \leftarrow \text{total gain}$$

Comment... In the limit of $R_{c8} \gg R_L$,
 the overall gain is $\frac{g_{m7,8} \cdot R_L}{2} = 5$.
 for each path, giving a total
 differential gain of 10.0

Part d, 10 points

This amplifier has *two* signal paths between input and output.

One is the path (M7 and M8, M9, M3, M4, M6, output).

The other is the path (M7 and M8, M10, output).

You will now compute the differential gain for the path (M7 and M8, M9, M3, M4, M6, output). Find the following

	Voltage Gain	Input impedance
Transistor M6	28.6	350Ω
Transistor M4	1.38	∞Ω
Transistor M9	1.0	25kΩ
M7-M8 differential pair	0.125	∞Ω
Overall differential Vout/Vin for this path	4.93	∞Ω

(the overall amplifier gain is the sum of the answers for parts c and d, but you are not asked to calculate this.)

$$1 \quad \left[R_{\text{leg 6}} = R_L \parallel R_{\text{sub 10}} \quad \text{but} \quad R_{\text{sub 10}} \gg R_L \right] \approx 10k\Omega$$

$$\frac{1}{2} \quad \left[g_{m6} = \frac{2I_D}{V_{GS}-V_{th}} = \frac{2(0.2mA)}{0.1V} = 4mA \right]$$

$$\frac{1}{2} \quad \left[R_{o6} = \frac{1}{g_m} = \frac{5V}{0.2mA} = 25k\Omega \right]$$

$$\frac{1}{2} \quad \left[R_{i6} = \frac{1}{g_{m6}} \left(1 + \frac{R_{\text{leg 6}}}{R_{o6}} \right) = 250\Omega \left(1 + \frac{10k\Omega}{25k\Omega} \right) = 350\Omega \right]$$

$$\frac{1}{2} \quad \left[A_{v6} = R_{\text{leg 6}} / R_{i6} = \frac{10k\Omega}{350\Omega} \approx 28.6 \right]$$

$$\frac{1}{2} \quad \left[R_{\text{leg 4}} = R_{o4} \parallel R_{i6} = 25k\Omega \parallel 350\Omega = 345\Omega \right]$$

$$\frac{1}{2} \quad \left[A_{v4} = -g_{m4} \cdot R_{\text{leg 4}} = -4mA \cdot 345\Omega \approx -1.38 \right]$$

$$\frac{1}{2} \left[\text{For } M_9, \text{ the FETs } M_3 \text{ & } M_5 \text{ act as resistors} = 1/g_m \right]$$

$$\frac{1}{2} \left[\text{There's a 2:1 voltage divider between } M_3 \text{ & } M_5 = 250\Omega \right]$$

$$\frac{1}{2} [R_{eq4} = 1/g_{m3} + 1/g_{m5} = 500\Omega]$$

$$\frac{1}{2} [R_{DS9} = 250\Omega, g_{mg} = 4mS]$$

$$1 \left[R_{iog} = \frac{1/g_{mg} (1 + \frac{R_{eq9}}{R_{DS9}})}{R_{DS9}} = 250\Omega (1 + \frac{500\Omega}{250\Omega}) \right]$$

$$\frac{1}{2} \left[\frac{A_{og}}{\sqrt{2}} = \frac{R_{eq9}}{R_{iog}} = \frac{1}{2} \frac{500\Omega}{250\Omega} = 1.0 \right]$$

due to M_3/M_5 resistive divider

$$1 \left[R_{eq7,8} = R_{DS7} // R_{DS12} // R_{mg} = \frac{5V}{80\mu A} // \frac{5V}{250\mu A} // 250\Omega \right]$$

$$= 100\Omega // 20\Omega // 250\Omega = 24\Omega \approx 25\Omega$$

$$\frac{1}{2} \left[g_{m7} = g_{m8} = \frac{2ID}{V_{GS}-V_{BL}} = \frac{2(50\mu A)}{0.1V} = \frac{0.1mA}{0.1V} = 1mS \right]$$

$$\frac{1}{2} \left[\Delta V_{7,8} = \frac{1}{2} g_{m7} \cdot R_{eq7} = \frac{1}{2} \cdot 1mS \cdot 25\Omega = \frac{1}{8} = 0.125 \right]$$

↑ diff

$$\begin{aligned} & 2.86 \\ & \times 1.38 \\ & \times 1.0 \\ & \underline{\times 0.125} \\ & = 4.93 \end{aligned}$$

Problem 3, 30 points

Nodal analysis: optical receiver preamplifier as real-world example.

Part a, 10 points

	<p>You will be working on the circuit to the left</p> <p>Ignore DC bias analysis. You don't need it.</p> <p>The NFET and the PFET each have transconductance g_m.</p> <p>The NFET and the PFET each have output resistance R_{ds} of infinity...so you don't need to include this element in the circuit diagram !</p> <p>$g_m = 0.5 \text{ mS}$ $R_F = 11 \text{ kOhm}$</p>
--	---


Compute, from nodal analysis, the small-signal gain V_{out}/I_{in} . This is called a transimpedance gain.

$$V_{out}/I_{in} = -10 \text{ k}\Omega$$


$$\begin{aligned} & \vdots \\ 3 & \left[\begin{aligned} zgmV_{in} &= I_{in} \\ \rightarrow V_{in} &= I_{in}/zgm \end{aligned} \right] \end{aligned}$$

$$\begin{aligned} 3 & \left[\begin{aligned} \text{Also } I_{in}R_F &= V_{in} - V_{out} = I_{in}/zgm - V_{out} \\ \rightarrow I_{in}(R_F + 1/zgm) &= -V_{out} \end{aligned} \right] \end{aligned}$$
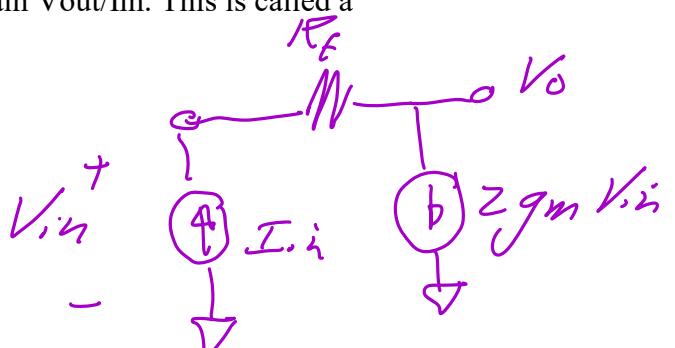
$$\begin{aligned} 4 & \left[\begin{aligned} \frac{V_{out}}{I_{in}} &= 1/zgm - R_F = 1000\Omega - 11k\Omega = -10k\Omega \end{aligned} \right] \end{aligned}$$




Part b, 10 points

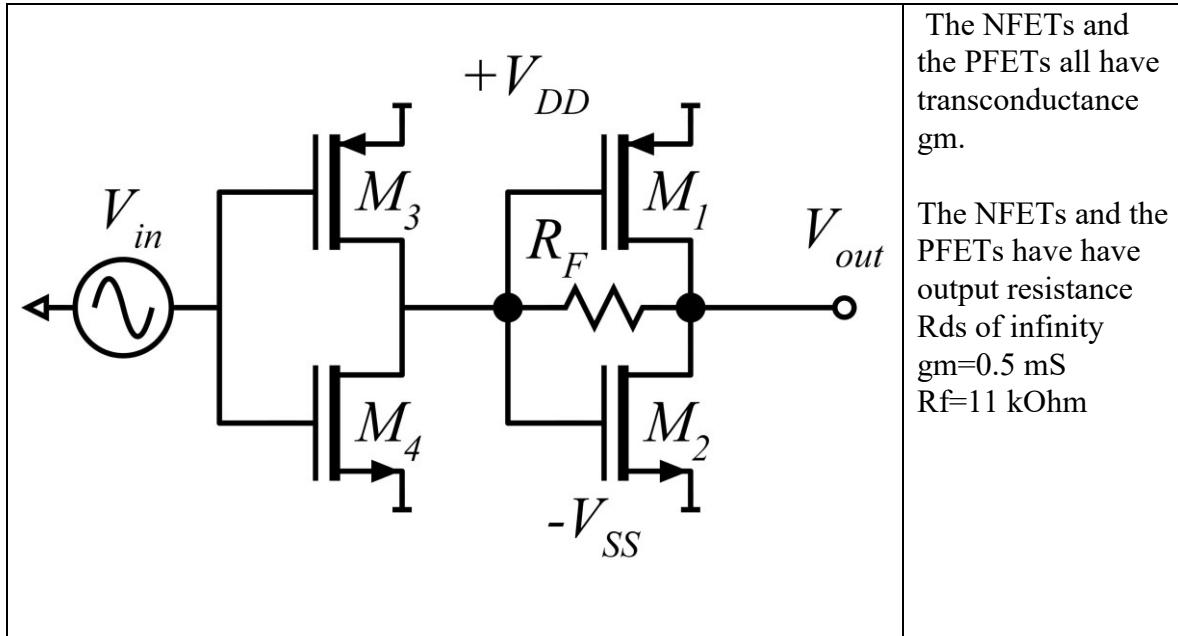

Compute, from nodal analysis, the small-signal gain V_{out}/V_{in} . This is a voltage gain.
 Hint: you can save some work by using the result from part A.


$$V_{out}/V_{in} = +10$$

from part A,

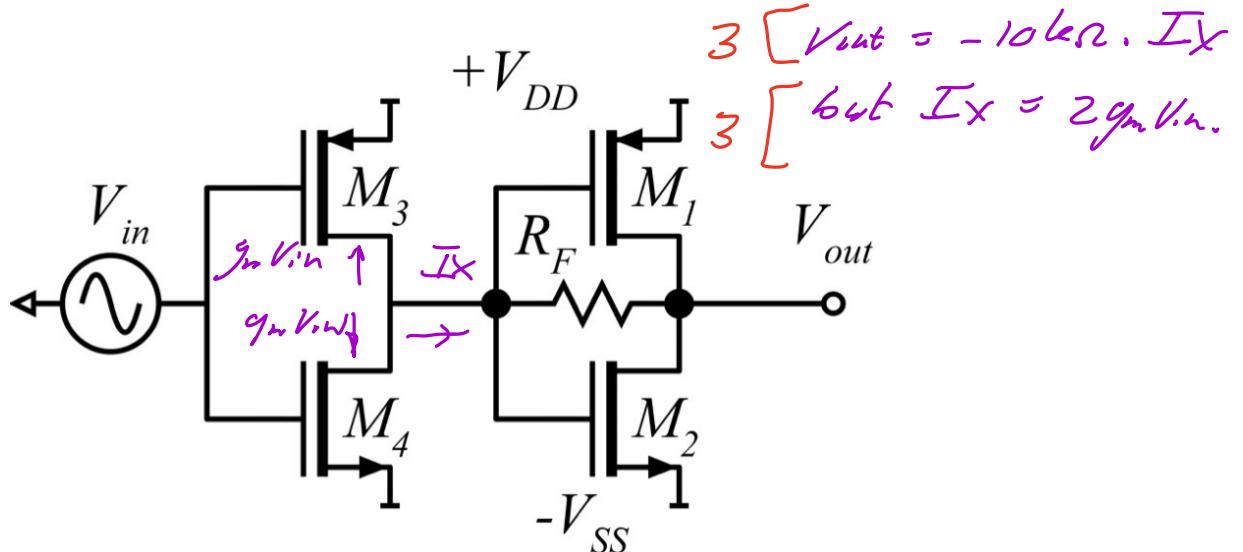

$$\Rightarrow \frac{V_{out}}{V_{in}} = 2 \cdot g_m \cdot 10k\Omega = 1 \text{ mS} \cdot 10k\Omega = 10.$$

Part c, 10 points

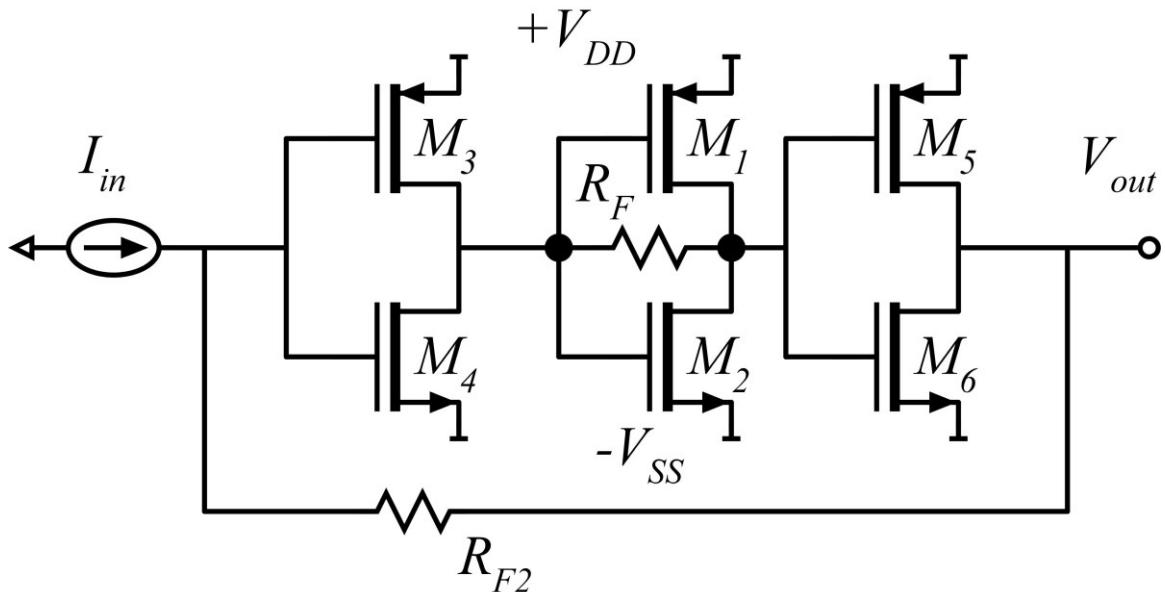


The NFETs and the PFETs all have transconductance gm . The NFETs and the PFETs have have output resistance R_{ds} of infinity.

$gm = 0.5 \text{ mS}$, $R_f = 11 \text{ kOhm}$, $R_{f2} = 1 \text{ kOhm}$.

Compute, from nodal analysis, the small-signal gain V_{out}/I_{in} . This is a transimpedance gain. Hint: you can save a great deal of work by using the results from parts A and B.
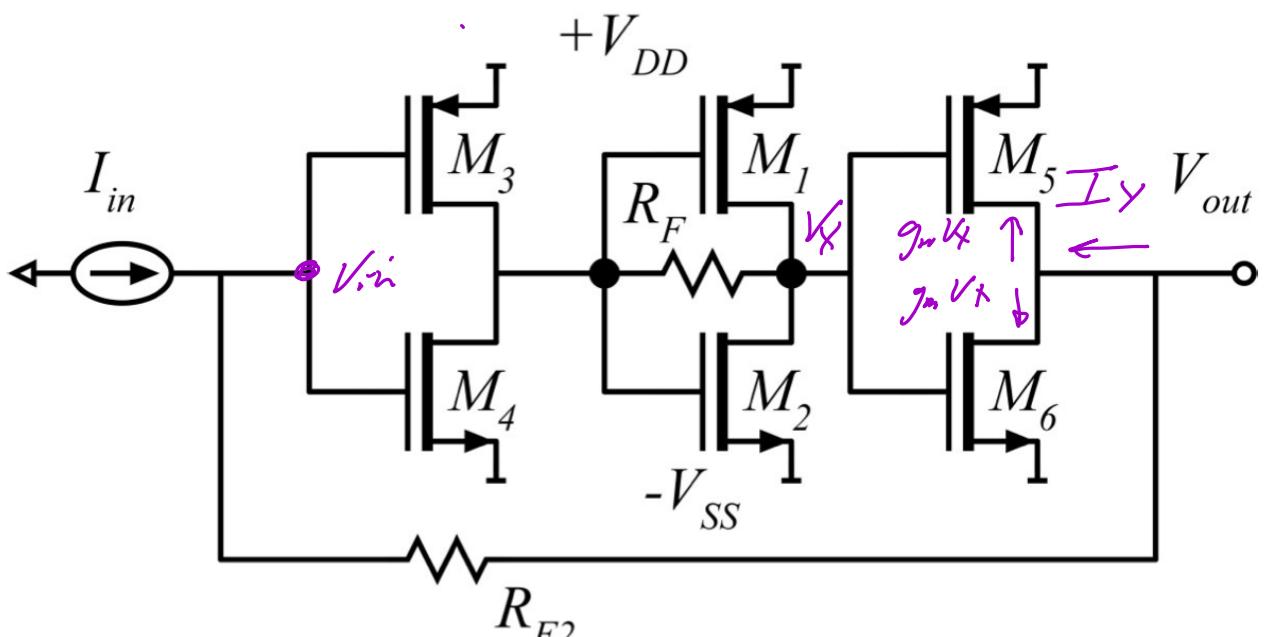
$$V_{out}/I_{in} = \underline{-900 \text{ } \Omega}$$



$$2 \quad \text{from part B, } V_x = 10V_{in}.$$

$$2 \quad \text{so } I_y = 2gm \cdot V_x = 2 \cdot 0.5ms \cdot 10V_{in}$$

$$= 10ms \cdot V_{in}$$

$$2 \quad \text{but } I_y = I_{in} \rightarrow V_{in} = \frac{I_{in}}{10ms}$$

$$2 \quad \text{and } V_{in} - V_{out} = I_{in} R_{f2}$$

$$\frac{I_{in}}{10ms} - V_{out} = I_{in} R_{f2}$$

$$2 \quad \frac{V_{out}}{I_{in}} = \frac{1}{10ms} - R_{f2}$$

$$= 100\Omega - 1k\Omega$$

$$= \underline{-900\Omega}$$