

ECE 137 A Mid-Term Exam

Wednesday February 9, 2022

Do not open exam until instructed to.

Closed book: Crib sheet and 1 page personal notes permitted

There are 2 problems on this exam, and you have 75 minutes.


Use any and all reasonable approximations (5% accuracy is fine.), ***AFTER STATING and approximately Justifying them.***

Name: Sabatini

Part	Points Received	Points Possible
1a		7
1b		7
1c		6
1d		15
1e		15
1f		6
1g		14
2a		12
2b		13
2c		5
TOTAL		100

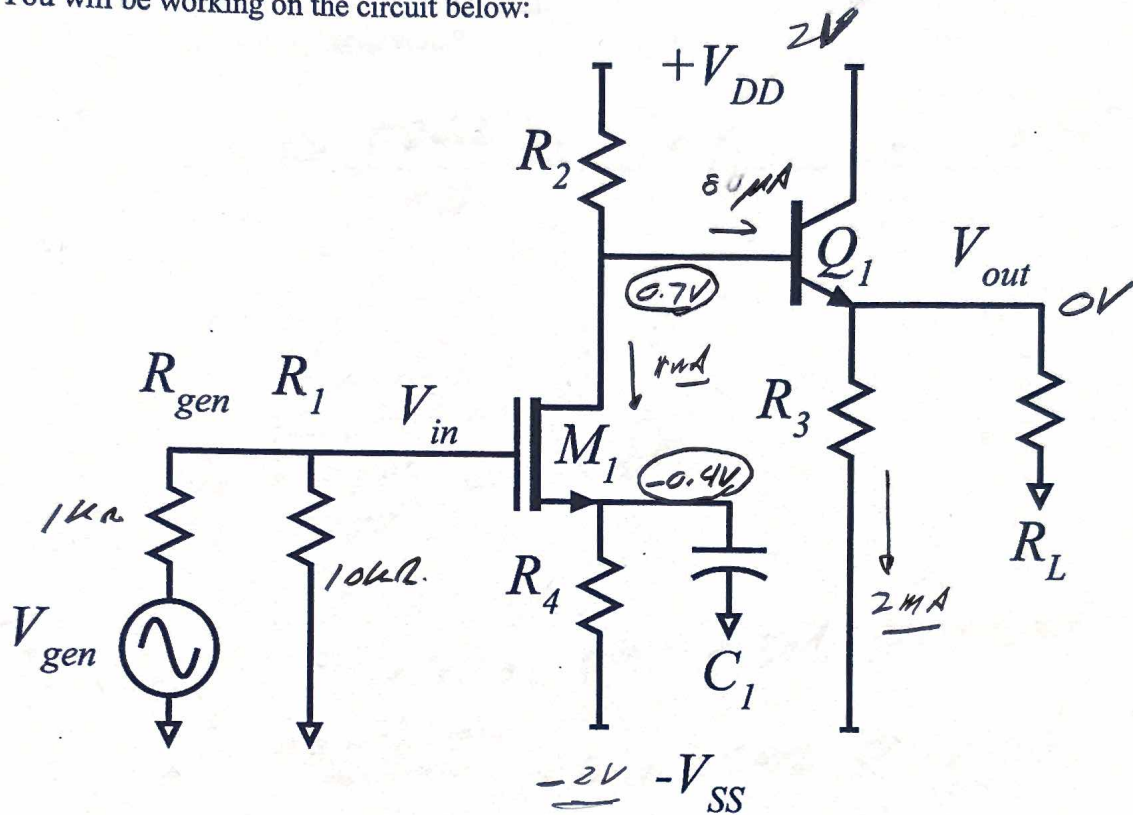Problem 1, 70 points

You will be working on the circuit below:



$$M1: K_{\mu} = \mu c_{gs} W_g / 2L_g = 10 \text{mA/V}^2 \cdot (W_g / 1\mu\text{m})$$

$$K_v = c_{gs} v_{in} W_g = 2 \text{mA/V} \cdot (W_g / 1\mu\text{m})$$

$$\Delta V = v_{in} L_g / \mu = 0.1 \text{V}, V_{th} = 0.3 \text{V}, 1/\lambda = 4 \text{V}$$

$$Q2: \beta = 250, V_A = 100 \text{V}$$

The supplies are +2V and -2V

$R_{gen} = 1000 \text{ Ohms}$, $R_L = 1,000 \text{ Ohms}$. $R_1 = 10 \text{ kOhms}$,

C_1 is very large (AC short-circuit)

Part a, 7 points

DC bias.

M1 is to be biased at 1 mA drain current and $V_{gs}=0.4$ Volts.

Q1 is to be biased at 2 mA collector current.

The DC value of V_{out} is *zero volts*.

Find the following:

$$Wg1 = \underline{7.84 \mu m} \quad R2 = \underline{1.3 k\Omega} \quad R3 = \underline{1 k\Omega} \quad R4 = \underline{1.6 k\Omega}$$

$$I_{SQ1} = \frac{2 \text{ mA}}{250} = 8 \mu A$$

$$\text{Current in } R_2 = 1 \text{ mA} + 8 \mu A = 1.008 \text{ mA}$$

$$R_2 = \frac{2V - 0.7V}{1.008 \text{ mA}} = 1.29 k\Omega \approx \underline{\underline{1.3 k\Omega}}$$

$$R_3 = \frac{2V}{2 \text{ mA}} = 1 k\Omega$$

$$R_4 = \frac{2V - 0.4V}{1 \text{ mA}} = \frac{1.6V}{1 \text{ mA}} = \underline{\underline{1.6 k\Omega}}$$

Note \rightarrow M1 is at boundary of μ & V limits \rightarrow either expression


$$I_{D1} = 1 \text{ mA} = 10 \frac{\text{mA}}{\mu m} \frac{Wg}{L} \frac{1}{2} (V_{gs} - V_{th})^2 (1 + \lambda V_{ds})$$

$\frac{1}{2} (0.1V)^2 (1 + \frac{1.1V}{4V})$

$$1 \text{ mA} = 10 \frac{\text{mA}}{\mu m} \frac{Wg}{L} (0.1V)^2 (1 + \frac{1.1V}{4V}) \rightarrow Wg = 7.84 \mu m$$

Part b, 7 points

DC bias

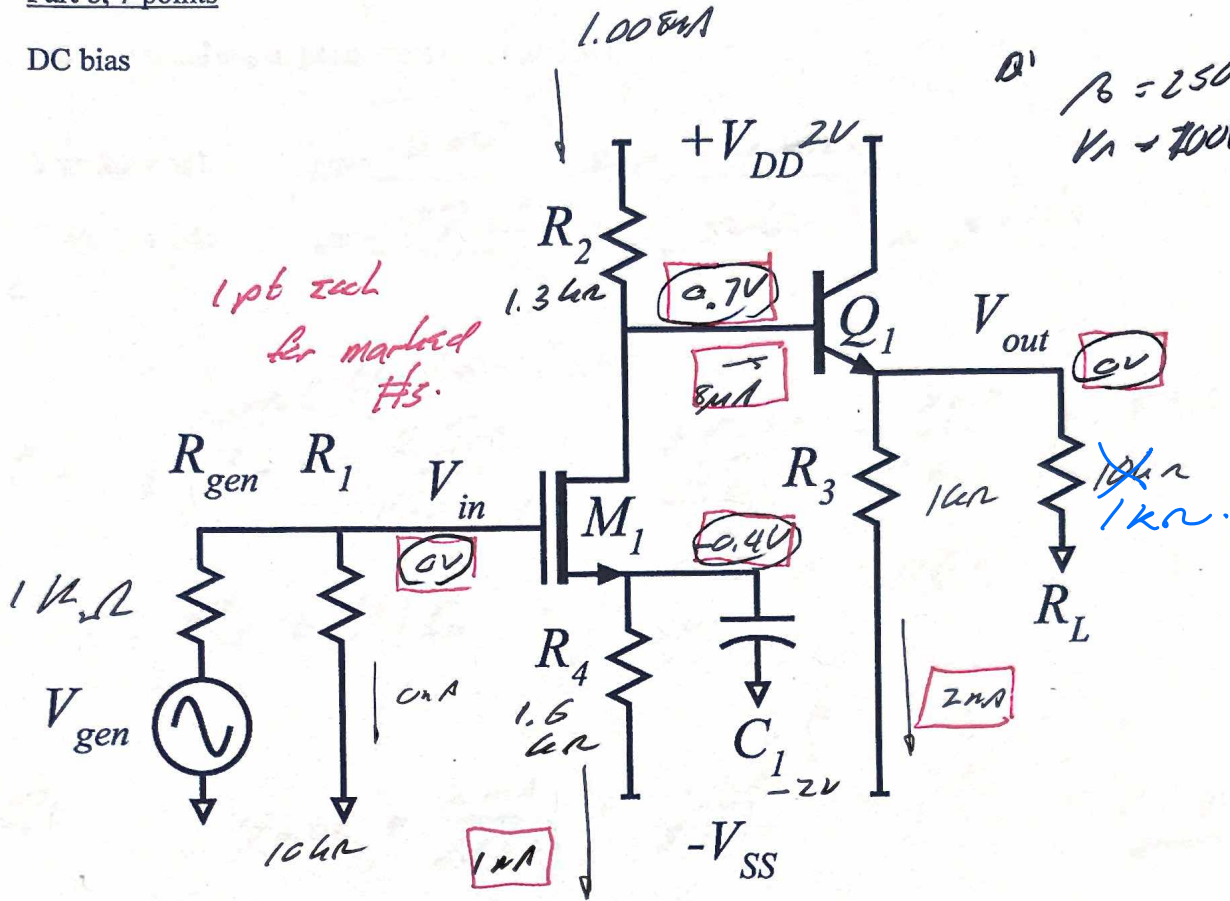

$m_1 \cdot \frac{1}{1} = 4V$
 $\beta = 250$
 $V_A = 100V$

On the circuit diagram above, label the DC voltages at ALL nodes and the DC currents through ALL resistors

$g_{mM1} = 5mS$
 $R_{DSM1} = 4k\Omega$

$g_{mQ1} = 77mS = 4/13k\Omega$
 $R_{eQ1} = 50k\Omega$
 $R_{LQ1} = 3.25k\Omega$

Part c, 6 points

Find the small signal parameters of Q1 and M1.

Transistor M1: $g_m = \underline{5 \text{ mS}}$ $R_{ds} = \underline{4 \text{ k}\Omega}$

Transistor Q1: $g_m = \underline{77 \text{ mS}}$ $R_{ce} = \underline{50 \text{ k}\Omega}$ $R_{be} = \underline{3.25 \text{ k}\Omega}$

M1 $\left[\begin{array}{l} \text{mobility limited, so} \\ g_m = \frac{2 I_{d1}}{V_{gs} - V_{t1}} = \frac{2 (1 \text{ mA})}{0.4 \text{ V}} = \frac{2 \text{ mA}}{0.4 \text{ V}} = 5 \text{ mS} \\ R_{Ds} = \frac{1}{I_{D1}} = \frac{4 \text{ V}}{1 \text{ mA}} = 4 \text{ k}\Omega \end{array} \right.$

Q1 $\left[\begin{array}{l} g_{mQ1} = \frac{2 \text{ mA}}{26 \text{ mV}} = \frac{1 \text{ mA}}{13 \text{ mV}} = \frac{1}{13 \Omega} = 77 \text{ mS} \\ R_{ce} = \frac{V_{CE} + V_A}{I_C} \approx \frac{V_A}{I_C} = \frac{100 \text{ V}}{2 \text{ mA}} = 50 \text{ k}\Omega \\ R_{be} = \frac{\beta}{g_m} = 250 (13 \Omega) = 3.25 \text{ k}\Omega \end{array} \right.$

Part d, 15 points.

Find the small signal voltage gain (V_{e1}/V_{b1}) of Q1 and Q1's small-signal input resistance.

$V_{e1}/V_{b1} = \underline{0.974}$

$R_{in,q1} = \underline{127\text{ k}\Omega}$

Q1:

$$\begin{aligned} 3 \quad [R_{eq} &= R_3 \parallel R_2 \parallel R_e \\ 2 \quad [&= 1\text{ k}\Omega \parallel 1\text{ k}\Omega \parallel 50\text{ k}\Omega \\ &= 495\Omega \end{aligned}$$

$$\begin{aligned} 3 \quad [A_{v1} &= \frac{v_{e1}}{v_b} = \frac{R_{eq1}}{R_{eq1} + 13\Omega} \\ 2 \quad [&= \frac{495\Omega}{495\Omega + 13\Omega} = 0.974. \end{aligned}$$


$$\begin{aligned} 3 \quad [R_{in1} &= \beta (R_{eq1} + 13\Omega) \\ 2 \quad [&= 250 (495\Omega + 13\Omega) = 127\text{ k}\Omega \end{aligned}$$

Part e, 15 points

Find the small signal voltage gain (V_{d1}/V_{g1}) of M_1 and the resistance. ***

$V_{d1}/V_{g1} = \underline{\underline{-4.86}}$

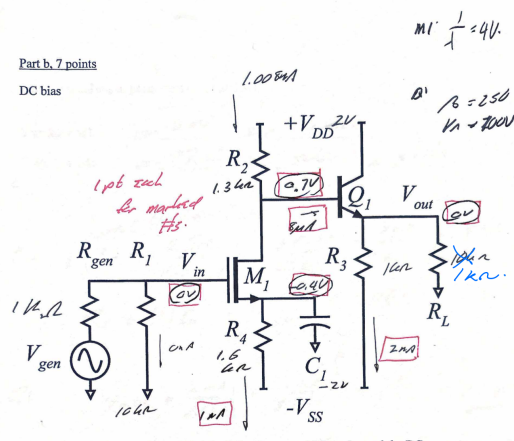$R_{in, amplifier} = \underline{\underline{10k\Omega}}$



On the circuit diagram above, label the DC voltages at ALL nodes and the DC currents through ALL resistors

$I_{DQ1} = 77\mu S = 1/13\mu$
 $g_{m1} = 5mS$
 $R_{DS1} = 4k\Omega$
 $R_{eq1} = 50k\Omega$
 $R_{L1} = 3.25k\Omega$

3 $R_{eq1} = R_{in2} \parallel R_2 \parallel R_{DS1}$
 2 $= 127k\Omega \parallel 1.3k\Omega \parallel 4k\Omega$
 $= 974\Omega$

3 $A_{v1} = \frac{V_{d1}}{V_{g1}} = -g_{m1} R_{eq}$
 2 $= -5mS \cdot 974\Omega$
 $= -4.86$

3 $R_{in1} = \infty$
 $R_{in} = R_{in1} \parallel R_1 = 10k\Omega$
 2

Part f, 6 points

Find (V_{out}/V_{in}) , (V_{in}/V_{gen}) and (V_{out}/V_{gen})

$$(V_{out}/V_{in}) = \underline{\underline{-4.74}}$$

$$(V_{in}/V_{gen}) = \underline{\underline{0.909}}$$

$$(V_{out}/V_{gen}) = \underline{\underline{-4.32}}$$

$$\begin{aligned} \boxed{V_o/V_i} &= A_{v_{mid}} A_{v_{o1}} = -4.86 \cdot 0.974 \\ &= \underline{\underline{-4.74}} \end{aligned}$$

$$\begin{aligned} V_i/V_{g_1} &= \frac{R_{i1}}{R_{i1} + R_{g_1}} = \frac{10k\Omega}{10k\Omega + 1k\Omega} = 0.909 \end{aligned}$$

$$\begin{aligned} \frac{V_o}{V_{g_1}} &= \frac{V_o}{V_i} \cdot \frac{V_i}{V_{g_1}} = -4.32 \end{aligned}$$

Part g, 14 points

Now you must find the maximum signal swings. Find the output voltage due to saturation and cutoff in Q1, and saturation and the knee voltage of M1. Give the sign (+ or -) in your answers below.

Cutoff of Q1; Maximum ΔV_{out} resulting = $\frac{-0.99V \downarrow}{}$

Saturation of Q1; Maximum ΔV_{out} resulting = $\frac{1.5V \uparrow}{}$

Cutoff of M1; Maximum ΔV_{out} resulting = $\frac{0.949V \uparrow}{}$

Knee voltage of M1; Maximum ΔV_{out} resulting = $\frac{0.986V \downarrow}{}$

Q1 cutoff

$R_{eq} = R_3 \parallel R_L \parallel R_{ce} = 495 \Omega$

$I_{ce1} = 2 \text{ mA}$

$\Delta V_{out} = 2 \text{ mA} \cdot 495 \Omega = -0.99V \downarrow$

Q1 sat

$V_{ce,sat} = 2V - 0V = 2V$

$V_{ce,sat Q1} = 0.5V$

$\Delta V_{out} = 2V - 0.5V = 1.5V \uparrow$

974

M1 cutoff

$R_{eq M1} = 974 \Omega$



$I_{DM1} = 1 \text{ mA}$

$\Delta V_{DRAIN1} = 1 \text{ mA} \cdot 974 \Omega = 974 \text{ mV}$

Multiply by A_{v01} to get ΔV_{out} :

$974 \text{ mV} \cdot 0.974 = 0.949V \uparrow$


M1 knee voltage

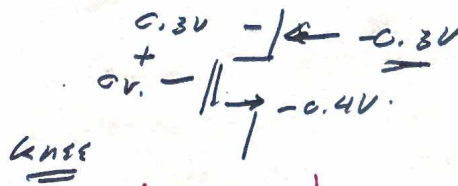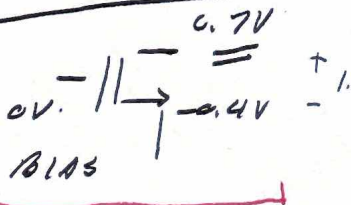

knee

$\Delta V_{DRAIN} = 1V \downarrow$
 $\Delta V_{out} = 1V \cdot A_{v01}$
 $= 1V \cdot 0.986$
 $= 0.986V \downarrow$

Problem 2, 30 points
nodal analysis

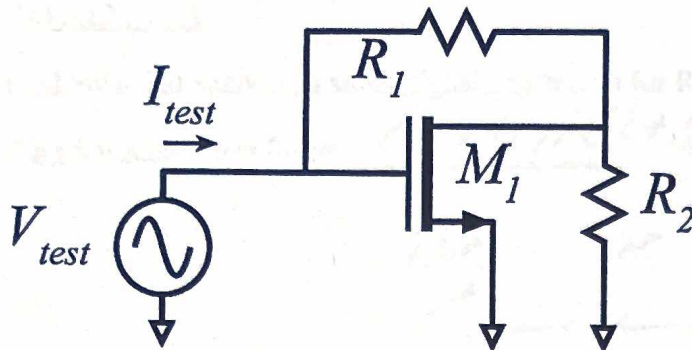

You will be working on the circuit to the left.


Ignore DC bias analysis. You don't need it.

Transistor M1 has transconductance g_m .

The drain-source resistance R_{ds} of M1 is infinity (so you don't need to draw it!)

Part a, 12 points

Draw the small-signal equivalent circuit

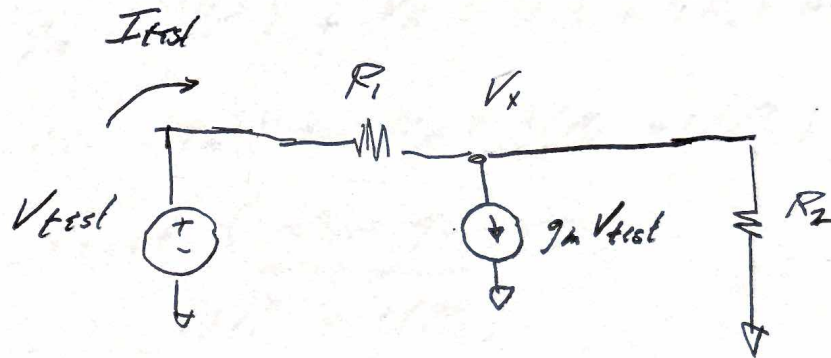


*Hard to give partial credit
deduct points if*

- topology is wrong
- elements are missing
- elements are not labelled
- location of voltage controlling g_m source is not labelled.

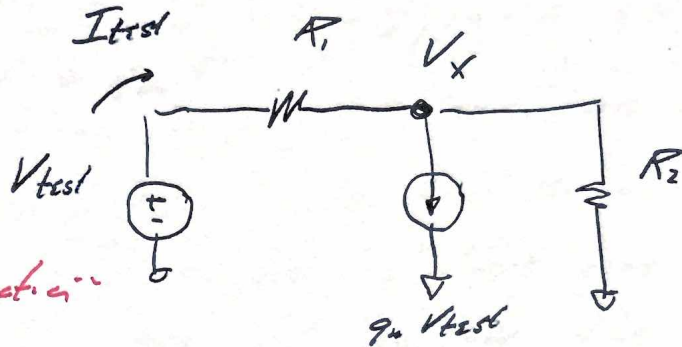Part b, 13 points

Find, by nodal analysis, a small-signal expression for $R_{in,transistor} = V_{test}/I_{test}$

$R_{in,transistor} = V_{test}/I_{test} = \frac{(R_1 + R_2)}{(1 + g_m R_2)}$



5 points for correct equation

$\sum I = 0 @ V_x$

$g_m V_{test} + V_x / R_2 + (V_x - V_{test}) / R_1 = 0$

$V_{test} (g_m - 1/R_1) + V_x (1/R_1 + 1/R_2) = 0$

$V_{test} (1/R_1 - g_m) = V_x (1/R_1 + 1/R_2)$

$V_x = V_{test} \frac{(1/R_1 - g_m)}{(1/R_1 + 1/R_2)}$

$I_{test} = \frac{V_{test} - V_x}{R_1} = \frac{1}{R_1} [V_{test}] \left[1 - \frac{V_x}{V_{test}} \right]$

$R_1 \frac{I_{test}}{V_{test}} = \frac{1}{R_1} - \frac{1/R_1 - g_m}{1/R_1 + 1/R_2} = \frac{1/R_1 + 1/R_2 - 1/R_1 + g_m}{1/R_1 + 1/R_2}$

$R_1 \frac{I_{test}}{V_{test}} = \frac{1/R_2 + g_m}{1/R_1 + 1/R_2}$

this is correct.

this is correct

$$\frac{V_{test}}{I_{test}} = R_1 \cdot \frac{1/R_1 + 1/R_2}{1/R_2 + g_m} = \frac{1 + R_1/R_2}{1/R_2 + g_m}$$

$$\frac{V_{test}}{I_{test}} = \frac{R_1 + R_2}{1 + g_m R_2}$$

← 7 points for correct answer

grader - be sure that answer is correct ... there are several ways of writing the correct answer.

Part c, 5 points

$g_{m1} = 1 \text{ mS}$, $R_1 = 2 \text{ k}\Omega$, $R_2 = 1 \text{ k}\Omega$
Give a numerical value for $R_{in, \text{transistor}}$

$$R_{in, \text{transistor}} = V_{\text{test}} / I_{\text{test}} = \underline{1.5 \text{ k}\Omega}$$

5.
$$R_{in} = \frac{R_1 + R_2}{1 + g_{m1} R_2} = \frac{1 \text{ k}\Omega + 2 \text{ k}\Omega}{1 + 1 \text{ mS} \cdot 1 \text{ k}\Omega}$$
$$= \frac{1 \text{ k}\Omega + 2 \text{ k}\Omega}{2} = 1.5 \text{ k}\Omega$$