

**ECE 137 A Mid-Term Exam**

**February 15, 2002**

Do not open exam until instructed to.

Closed book: Crib sheet and 1 page personal notes permitted


There is one problem on this exam (parts A-F) , and your have 50 minutes.

Use any and all reasonable approximations (5% accuracy is fine. ) , ***AFTER STATING THEM.***

**Name:** \_\_\_\_\_

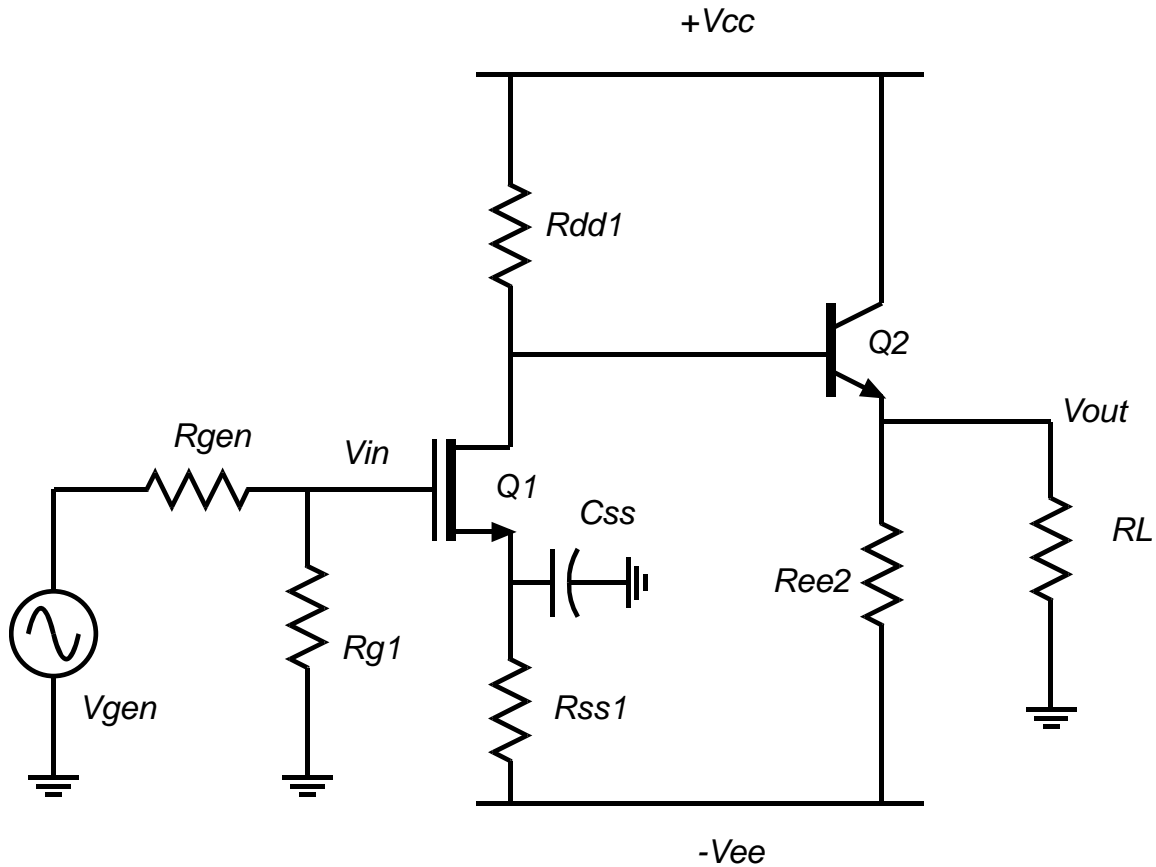**Problem 1, 100 points**

You will be working on the circuit below:



Q1 :  $V_{th} = 0.5$  Volts.  $v_{sat} C_{ox} W_g = 3$  mA/V,  $\lambda = 1/(20 \text{ Volts})$

Q2:  $\beta = 100$ ,  $V_a = 200$  Volts.

$V_{cc} = +3.3$  volts.

$-V_{ee} = -3.3$  volts

$R_{gen} = 1$  MegOhm

$R_L = 1000$  Ohm

$R_{g1} = 10$  MegOhm

$R_{ss1} = ???$

$R_{dd1} = ???$

$R_{ee2} = ???$

$C_{oss}$  is very big and has negligible AC impedance.

Part a, 10 points

DC bias.

Q1 is to be biased with 2 mA source current.


Q2 is to be biased with 10 mA collector current

The circuit is to be biased such that the DC emitter voltage of Q2 is zero volts.

Find:  $R_{ss1} =$  \_\_\_\_\_  $R_{dd1} =$  \_\_\_\_\_  $R_{ee2} =$  \_\_\_\_\_

Part b, 10 points

DC bias

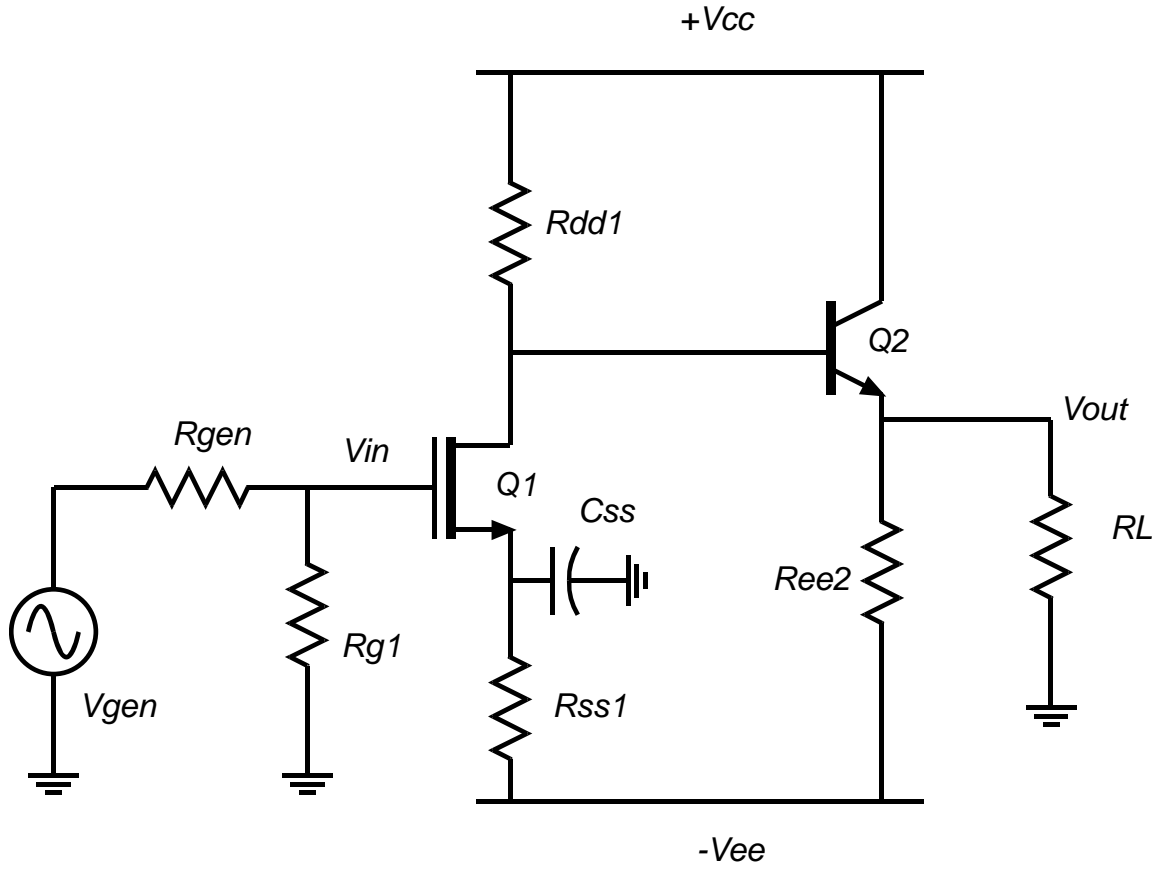

On the circuit diagram above, label the DC voltages at **ALL nodes** and the DC currents through **ALL resistors**

Part b, 10 points

Find the small signal parameters of Q1 and Q2.

Transistor Q1:  $g_m =$  \_\_\_\_\_  $R_o =$  \_\_\_\_\_

Transistor Q2:  $r_e =$  \_\_\_\_\_  $g_m =$  \_\_\_\_\_  $r_\pi =$  \_\_\_\_\_  $R_o =$  \_\_\_\_\_

Part c, 20 points.

Find the small signal voltage gain ( $v_{e2}/v_{b2}$ ) of Q2 and Q2's small-signal input resistance.

$v_{e2}/v_{b2} =$  \_\_\_\_\_

$R_{in,q2} =$  \_\_\_\_\_

Part d, 20 points

Find the small signal voltage gain ( $v_{d1}/v_{g1}$ ) of Q1 and the \*\*\* amplifier \*\*\* input resistance.

$v_{d1}/v_{g1} =$  \_\_\_\_\_

$R_{in, amplifier} =$  \_\_\_\_\_

Part e, 10 points

Find  $(V_{out}/V_{in})$ ,  $(V_{in}/V_{gen})$  and  $(V_{out}/V_{gen})$

$$(V_{out}/V_{in}) = \underline{\hspace{10em}}$$

$$(V_{in}/V_{gen}) = \underline{\hspace{10em}}$$

$$(V_{out}/V_{gen}) = \underline{\hspace{10em}}$$

Part f, 20 points

Find the maximum peak-peak output voltage (show all your work, specifically show the limits of the output swing arising from cutoff and saturation of Q1 and Q2)

**COMMONSENSE POINT: NOTE THAT THE MAXIMUM SWINGS of Q1 must be multiplied by the voltage gain of Q2 in order to find their corresponding limit on output voltage.**

Cutoff of Q1; Maximum  $\Delta V_{out}$  resulting = \_\_\_\_\_

Knee voltage of Q1; Maximum  $\Delta V_{out}$  resulting = \_\_\_\_\_

Cutoff of Q2; Maximum  $\Delta V_{out}$  resulting = \_\_\_\_\_

Saturation of Q2; Maximum  $\Delta V_{out}$  resulting = \_\_\_\_\_

Maximum Peak-Peak output = \_\_\_\_\_

