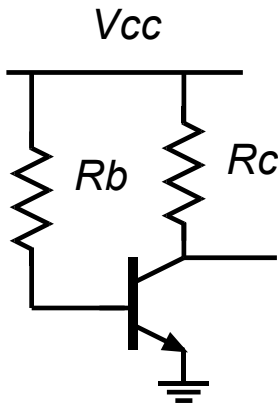



**ECE137A Problem set #1**

**Problem 1.** bipolar transistor biasing. Assume a  $V_{be(on)}$  of 0.7 volts.



- a)  
 $\beta = 75$   
 $V_{cc} = 15$  volts  
 We want 0.5mA collector current,  
 and  $V_{ce} = 3$  Volts  
 Find  $R_c$  and  $R_b$

(this biasing circuit *not* recommended)

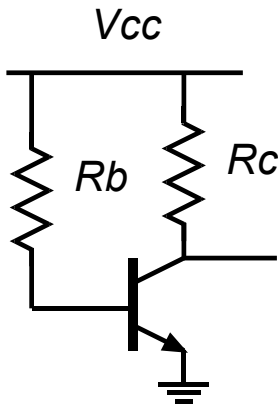


- b) Bias stability of the circuit of problem 1(a).

First, keeping the same values for  $R_b$  and  $R_c$  you found above, compute the collector current and the collector voltage if  $\beta$  is increased to 200.


Second, keeping the same values for  $R_b$  and  $R_c$  you found above, compute collector current and the collector voltage if  $\beta$  is returned back to its original value but  $V_{cc}$  is increased 10%.

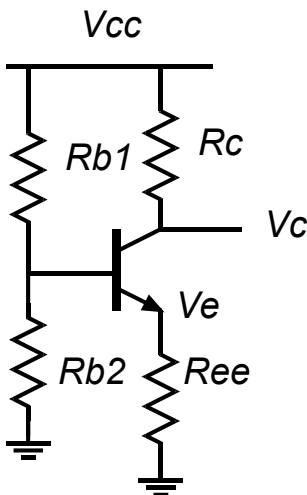Caution: You *must* consider the possibility of saturation.



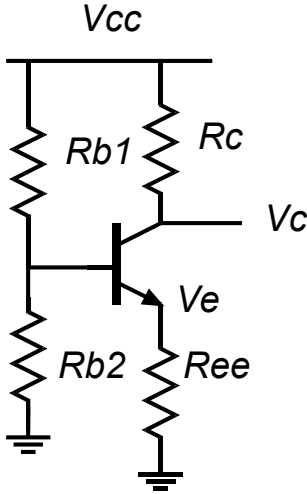- c)  
 $\beta = 75$   
 $V_{cc} = 15$  volts  
 collector current = 0.5 mA  
 Collector voltage  $V_c = 2$  Volts  
 Emitter voltage  $V_e = 0.5$  volts  
 current in  $R_{b2} = 100$  microamps

Find  $R_{b1}$ ,  $R_{b2}$ ,  $R_{ee}$ ,  $R_c$




d) Bias stability of the circuit of problem 1(c).

First, keeping the same values for  $R_{b1}$ ,  $R_{b2}$ ,  $R_{ee}$  and  $R_c$  you found above, compute the collector current and the collector voltage if  $\beta$  is increased by a factor of two.

Second, keeping the same values for  $R_{b1}$ ,  $R_{b2}$ ,  $R_{ee}$  and  $R_c$  you found above, compute the collector current and the collector voltage if  $\beta$  is returned back to its original value but  $V_{cc}$  is increased 10%.

Caution: You *must* consider the possibility of saturation.

Problem 2 MOS Biasing:

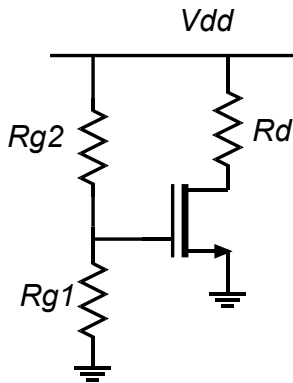

a)

The MOSFET has a 0.3V threshold,

$$K_{\mu} = \mu c_{gs} W_g / 2L_g = 10\text{mA/V}^2 \cdot (W_g / 1\mu\text{m}),$$

$$K_v = c_{gs} v_{inj} W_g = 2.0\text{mA/V} \cdot (W_g / 1\mu\text{m})$$


$$\Delta V = v_{inj} L_g / \mu = 100\text{mV}, \text{ and}$$

$$W_g = 1\mu\text{m}. \text{ Rg1 is } 100\text{ k}\Omega. \text{ Vdd is } 1.0\text{ Volts.}$$

$\lambda = 0$ . We would like to bias the MOSFET at 0.5 mA drain current and 0.5 volts between drain and source.

Please find the required values of  $R_{g2}$  and  $R_d$ .

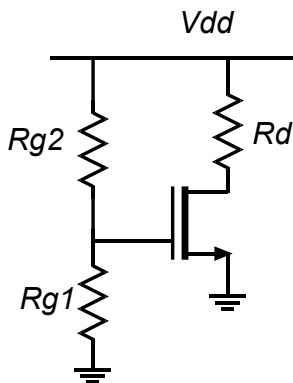b) Bias stability of the circuit of problem 2(a).



First, keeping the same values for  $R_{g1}$ ,  $R_{g2}$ , and  $R_d$  you found above, compute the drain current and the drain voltage if  $K_{\mu}$  and  $K_v$  are both increased 10%.

Second, using the original value of  $K_{\mu}$  and  $K_v$ , and keeping the same values for  $R_{g1}$ ,  $R_{g2}$ , and  $R_d$  you found in 2(a), compute the drain current and the drain voltage if the power supply voltage is increased 10%.