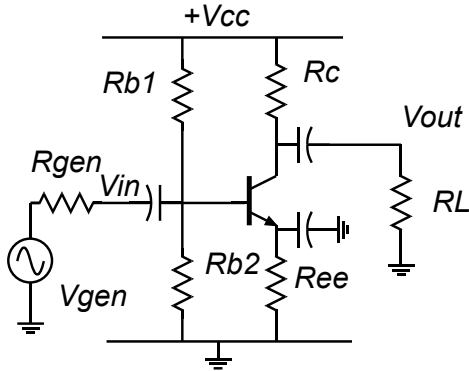


ECE137A Problem set #2

Problem 1. Simple common-emitter amplifier



a) The transistor has $\beta = 150$.

V_{cc} is +15.0 Volts. $R_L = 2000 \text{ Ohm}$. $R_{gen} = 1 \text{ kOhm}$. The transistor has $V_a = 50 \text{ V}$ and $V_{cesat} = 0.5 \text{ volts}$

We want the emitter to be biased at +1.0 volts and the collector to be biased at +5.0 volts. The DC collector current is to be 1 mA, and the DC current through R_{b2} is to be 0.1 mA.

Find R_{b1} , R_{b2} , R_c , R_{ee}


b) Find the following small signal transistor parameters: g_m , r_e , R_{be} , R_{ce}

d) find the ac small signal input impedance, and the AC voltage gains V_{out}/V_{in} , V_{in}/V_{gen} and V_{out}/V_{gen} .

c) draw the small-signal equivalent circuit of the amplifier, taking all capacitors as AC shorts and supplies as AC ground.

e) find the maximum AC peak-peak amplifier output before clipping.

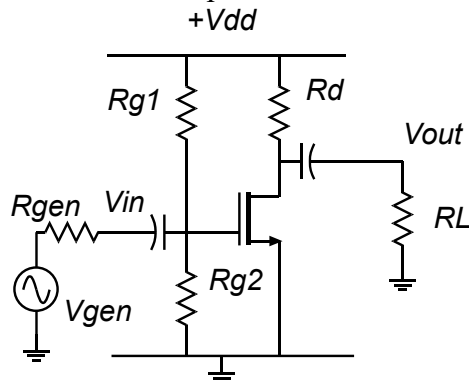Problem 2. Simple common-source amplifier



a) The MOSFET has $v_{th} = 0.3 \text{ Volt}$,

$$K_{\mu} = 0.55 \text{ mA/V}^2 \cdot (W_g / 1 \mu\text{m}),$$

$$K_v = 0.69 \text{ mA/V} \cdot (W_g / 1 \mu\text{m})$$

$$\Delta V = 0.625 \text{ V}$$

$$\text{and } 1/\lambda = 10 \text{ Volts}$$

Find the gate width necessary to carry 0.3 mA drain current at $V_{gs} = 0.5 \text{ V}$.

V_{dd} is +1.5 volts. $R_{gen} = 25 \text{ kOhm}$, $R_L = 100 \text{ kOhm}$

Find the drain resistance R_d necessary to obtain $V_d = 1 \text{ V}$.

We want the *input impedance to be 1 MOhm.

Find R_{g1} , R_{g2}

b) Find the following small signal transistor parameters: g_m , R_{ds}

d) find the ac small signal input


c) draw the small-signal equivalent circuit of the amplifier, taking all capacitors as AC shorts and supplies as AC ground.

e) find the maximum AC peak-peak amplifier

impedance, and the AC voltage gains V_{out}/V_{in} , V_{in}/V_{gen} and V_{out}/V_{gen} .

output before clipping.

Problem 3. Nodal Analysis

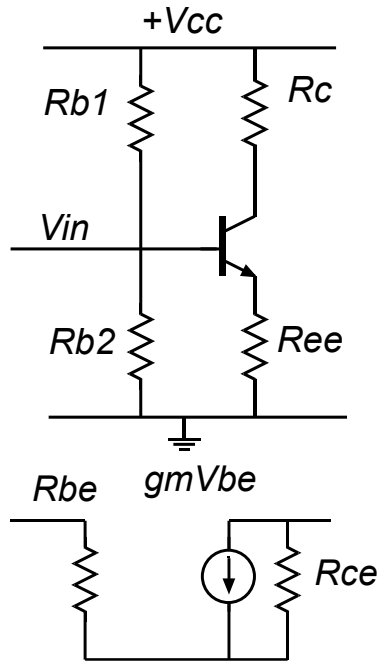


We will frequently need to analyze circuits with resistance in the emitter or source lead.

So, this problem is both a tutorial in how these work, and an exercise in nodal analysis, for which much practice is needed.

The overall circuit and the transistor small-signal model are as indicated on the right....

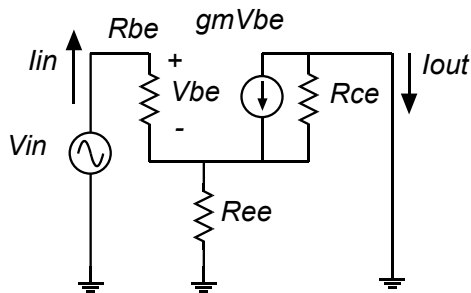
but the problem can be broken into the units below, which is what you must work this week



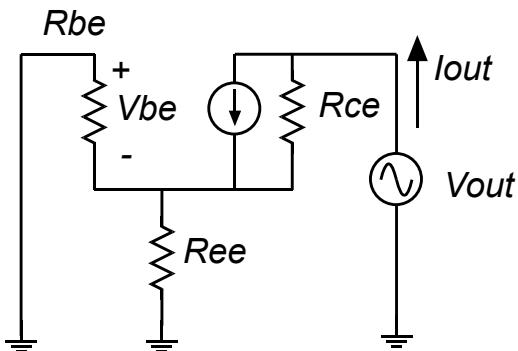a) with the network to the left, derive **by nodal analysis**

...the input impedance V_{in}/I_{in}

...the *extrinsic* transconductance I_{out}/V_{in}



b) with the network to the left, derive **by nodal analysis**

...the output resistance V_{out}/I_{out}