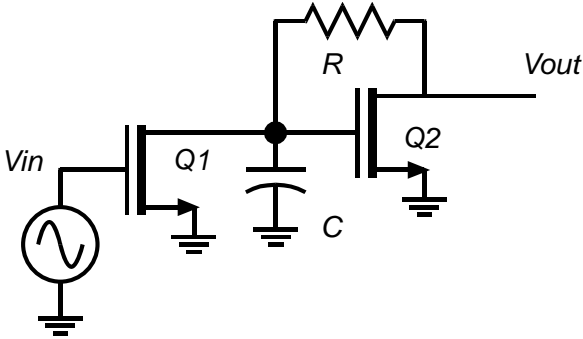
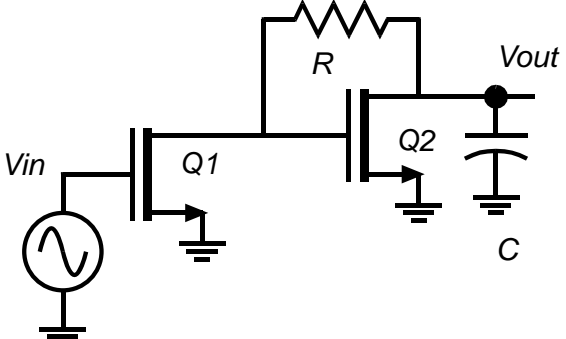
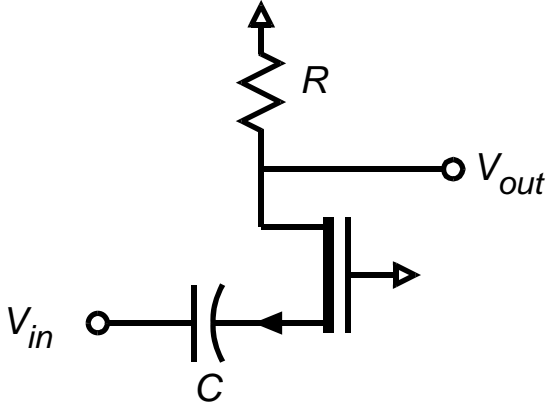
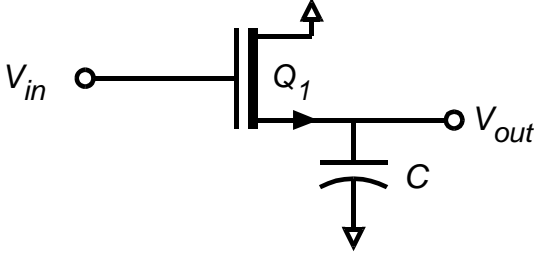
	<p>The problems below will use the following small signal model for the mosfet.</p>
	<p>Problem 1: This is a transconductance-transimpedance amplifier. Ignore DC bias analysis. You don't need it. The two transistors have transconductance <math>gm1</math> and <math>gm2</math> respectively. Their output resistances <math>Rds1</math> and <math>Rds2</math> are both infinity. <math>gm1=10</math> mS. <math>gm2=20</math> mS. <math>R=1k\Omega</math>. <math>C=20</math> pF, <math>Cgs=0</math> fF</p> <p>a) Draw a small-signal equivalent circuit of the circuit</p> <p>b) Find, by nodal analysis, a small-signal expression for <math>Vout(s)/Vin(s)</math></p> <p>c) Find any/all pole and zero frequencies of the transfer function, in Hz:</p> <p>d) Draw a clean Bode Plot of <math>Vout/Vin</math>, LABEL AXES, LABEL all relevant gains and pole or zero frequencies, Label Slopes</p>
	<p>Problem 2: Here again is a transconductance-transimpedance amplifier. Ignore DC bias analysis. You don't need it. The two transistors have transconductance <math>gm1</math> and <math>gm2</math> respectively. Their output resistances <math>Rds1</math> and <math>Rds2</math> are both infinity. <math>gm1=10</math> mS. <math>gm2=20</math> mS. <math>R=1k\Omega</math>. <math>C=20</math> pF. <math>Cgs=0</math> fF</p> <p>(a) Draw a small-signal equivalent circuit of the circuit</p> <p>b) Find, by nodal analysis, a small-signal expression for <math>Vout(s)/Vin(s)</math></p> <p>c) Find any/all pole and zero frequencies of the transfer function, in Hz:</p> <p>d) Draw a clean Bode Plot of <math>Vout/Vin</math>, LABEL AXES, LABEL all relevant gains and pole or zero frequencies, Label</p>

	Slopes
	<p>Problem 3: Ignore DC bias analysis. You don't need it. The transistor has transconductance <math>g_m</math>. Its output resistance <math>R_{ds}</math> is infinity. (a) Draw a small-signal equivalent circuit of the circuit. (b) <math>g_m=5</math> mS. <math>C=50</math> pF. <math>R=200</math> Ohms Find, by nodal analysis, a small-signal expression for <math>V_{out}(s)/V_{in}(s)</math> (c) Find any/all pole and zero frequencies of the transfer function, in Hz: Draw a clean Bode Plot on semilog paper of <math>V_{out}/V_{in}</math>, LABEL AXES, LABEL all relevant gains and pole or zero frequencies, Label Slopes (d) <math>V_{in}(t)</math> is a 100 mV amplitude step-function Find <math>V_{out}(t)</math>, and plot it below. Label axes, show initial and final values, show time constants</p>
	<p>Problem 4: Ignore DC bias analysis. You don't need it. The transistor has transconductance <math>g_m</math>. Its output resistance <math>R_{ds}</math> is infinity. (a) Draw a small-signal equivalent circuit of the circuit. (b) <math>g_m=5</math> mS. <math>C=50</math> pF. <math>R=200</math> Ohms Find, by nodal analysis, a small-signal expression for <math>V_{out}(s)/V_{in}(s)</math> (c) Find any/all pole and zero frequencies of the transfer function, in Hz: Draw a clean Bode Plot on semilog paper of <math>V_{out}/V_{in}</math>, LABEL AXES, LABEL all relevant gains and pole or zero frequencies, Label Slopes (d) <math>V_{in}(t)</math> is a 100 mV amplitude step-function Find <math>V_{out}(t)</math>, and plot it below. Label axes, show initial and final values, show time constants</p>

	<p>Problem 5: Ignore DC bias analysis. You don't need it. The two transistors have transconductance <math>g_{m1}</math> and <math>g_{m2}</math> respectively. Their drain-source resistances <math>R_{ds1}</math> and <math>R_{ds2}</math> are both infinity. (a) Draw a small-signal equivalent circuit of the circuit (t) Find, by nodal analysis, a small-signal expression for <math>V_{out}/V_{in}</math></p>
	<p>Problem 6: Ignore DC bias analysis. You don't need it. The two transistors have transconductance <math>g_{m1}</math> and <math>g_{m2}</math> respectively. Their drain-source resistances <math>R_{ds1}</math> and <math>R_{ds2}</math> are both infinity. (a) Draw a small-signal equivalent circuit of the circuit (t) Find, by nodal analysis, a small-signal expression for <math>V_{out}/V_{in}</math></p>
	<p>Problem 7: <math>R_1=2\text{ KOhm}</math> <math>R_2=2\text{ KOhm}</math>  <math>R_3=1\text{ KOhm}</math> <math>R_4=6\text{ KOhm}</math>  <math>C_1=2\text{ nF}</math> <math>C_2=4\text{ nF}</math> <math>C_3=6\text{ nF}</math>  Using Nodal analysis, find the transfer function <math>V_{out}(s)/V_{gen}(s)</math>. Give the answer in standard form</p> $\frac{V_{out}(s)}{V_{gen}(s)} = \frac{V_{out}}{V_{gen}} \bigg _{DC} \frac{1 + b_1s + b_2s^2 + \dots}{1 + a_1s + a_2s^2 + \dots}$