

ECE ECE145A (undergrad) and ECE218A (graduate)

Final Exam. December 6, 2011

Do not open exam until instructed to.

Open notes, open books, etc

You have 3 hrs.

Use all reasonable approximations (5% accuracy is fine.), ***AFTER STATING THEM.***

Hint: Stop and think before doing complicated calculations. For some problems, there is an easier way.

Problem	Points Received	Points Possible
1a		5
1b		5
1c		5
1d		5
1e		5
1f		5
2		10
3a		10
3a		5
4		10
5		10
6		5
7a		10
7b		10

Name: Solution

$$G_T = \frac{|S_{21}|^2 (1 - |\Gamma_s|^2)(1 - |\Gamma_L|^2)}{|(1 - \Gamma_s S_{11})(1 - \Gamma_L S_{22}) - S_{21} S_{12} \Gamma_s \Gamma_L|^2} \quad G_P = \frac{1}{1 - \Gamma_{in}^2} \cdot |S_{21}|^2 \cdot \frac{1 - |\Gamma_L|^2}{|1 - \Gamma_L S_{22}|^2}$$

$$G_a = \frac{1 - |\Gamma_s|^2}{|1 - \Gamma_s S_{11}|^2} \cdot |S_{21}|^2 \cdot \frac{1}{1 - \Gamma_{out}^2} \quad G_{max} = \frac{|S_{21}|}{|S_{12}|} \cdot [K - \sqrt{K^2 - 1}] \text{ if } K > 1$$

$$G_{MS} = \frac{|S_{21}|}{|S_{12}|} \cdot \text{if } K < 1$$


$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2 |S_{21} S_{12}|} \quad \text{where } \Delta = \det[S]$$

IPN

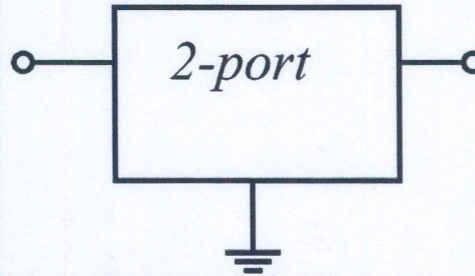Problem 1, 30 points

Gain definitions

At a signal frequency of 1 GHz, a two-port has $S_{11} = 0.7071$, $S_{12} = 0.1$, $S_{21} = 10$ and $S_{22} = 0.316$, as defined with a 50 Ohm impedance reference.



part a, 5 points

If the 2-port were directly connected to 50 Ohm load, and a 50 Ohm generator with 1 mW available power, what would be the power dissipated in the load?

First, is it potentially unstable?

FOR Part B. ←

$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2 |S_{21} S_{12}|} = \frac{1.003}{2(0.1)(10)} = 0.5$$

$$\Delta = S_{11}S_{22} - S_{12}S_{21} = 11 \cdot 0.7766$$

potentially unstable

Here the gain is the insertion gain S_{21}

$$P_{\text{load}} = |S_{21}|^2 \cdot 1 \text{ mW} = 100 \cdot 1 \text{ mW} = \underline{\underline{100 \text{ mW}}}$$

part b, 5 points

If you were to first stabilize (if necessary) and then impedance match the input and output to 50 Ohms, what would be the gain S_{21} of the resulting amplifier?

Calculation of K is first needed

- SEE previous page
- $K < 1$ \rightarrow potentially unstable
- we must first stabilize then match.

Gain, if we stabilize the minimum amount, will be MSG

Transistor S-parameters

$$MSG = \frac{|S_{21}^T|}{|S_{12}^T|} = \frac{10}{0.1} = 100 \quad \text{in units of } \frac{P_{out}}{P_{in}}$$

After matching & stabilizing, $S_{ij}^A \leftarrow$ amplifier

$$|S_{21}^A|^2 = \text{transistor MSG} = 100$$

$$\boxed{|S_{21}^A| = 10}$$

$$\vec{S} = \begin{bmatrix} 0.7071 & 0.1 \\ 10 & 0.316 \end{bmatrix}$$

part c, 5 points

If you were to load the 2-port, without matching or stabilization elements, with a 500 Ohm load, is it possible to select a generator impedance which would cause the 2-port to oscillate?

0.5

$$\Gamma_L = \frac{500/50 - 1}{500/50 + 1} = \frac{10 - 1}{10 + 1} = \frac{9}{11} = \dots$$

2

$$\Gamma_{in} = S_{11} + \frac{S_{12} S_{21} \Gamma_L}{1 - S_{22} \Gamma_L}$$

0.5

$$= 0.7071 + \frac{10 \cdot 0.1 \cdot 9/11}{1 - 0.316 (9/11)}$$

$$= 0.7071 + 1.103$$

$$= 1.81$$

2

$|\Gamma_{in}| > 1$, so some source impedances will result in oscillation.

$$\begin{bmatrix} 0.7071 & 0.1 \\ 10 & 0.316 \end{bmatrix}$$

part d. 5 points

If you were to load the 2-port, without stabilization elements, in 50 Ohms, and then impedance-match the input to a 50 Ohm generator with 1 mW available source power, what would be the power in the load?

Match on input, not on output

→ [operating Gain of transistor] is gain of amplifier.

$$\Gamma_L = 0 \quad (50 \Omega \text{ load})$$

$$\Gamma_{in}^T = S_{11}^T + \frac{S_{12}^T S_{22}^T \Gamma_L}{1 - S_{22}^T \Gamma_L} = S_{11}^T$$

$$G_{TP}^T = \frac{1}{1 - |\Gamma_{in}^T|^2} |S_{21}^T|^2 \frac{1 - |\Gamma_L|^2}{|1 - \Gamma_L S_{22}^T|^2}$$

$$= \frac{1}{1 - |S_{11}^T|^2} |S_{21}^T|^2 = \frac{100}{1 - 1/2} = 200$$

$$G_{TP}^T = |S_{21}^T|^2 = 200$$

$$\text{Power in Load} = 1 \text{ mW} \cdot 200 = \underline{\underline{200 \text{ mW}}}$$

0.7071

0.1

10

0.316

part e, 5 points

If you were to take the 2-port, without stabilization elements, connect the input directly to a 50 Ohm generator with 1 mW available source power, and then impedance-match the output to a 50 Ohm load, what would be the power in the load ?

Match on output, not on input.

Circuit gain $|S_{21}^A|^2 = \text{transistor available gain}$

$$G_A^T = \frac{1 - |\Gamma_s|^2}{|1 - \Gamma_s S_{11}|^2} \cdot |S_{21}^T|^2 \cdot \frac{1}{1 - |\Gamma_{out}|^2}$$

$$\Gamma_s = 0 \text{ (50 } \Omega) \rightarrow$$

$$\Gamma_{out} = S_{22}^T + \frac{S_{12}^T S_{21}^T \Gamma_s}{1 - S_{11}^T \Gamma_s} = S_{22}^T$$

$$G_A^T = 1 \cdot (100) \cdot \frac{1}{1 - (0.316)} = \frac{100}{0.9} = 111.1$$

$$|S_{21}^A|^2 = G_A^T = 111.1$$

$$\text{power in load} = 1 \text{ mW} \cdot 111.1 = \underline{\underline{111.1 \text{ mW}}}$$

$$\begin{bmatrix} 0.7071 & a_1 \\ 10 & 0.316 \end{bmatrix}$$

part f, 5 points

If you were to take the 2-port, without stabilization elements, connect the input directly to a 500 Ohm generator with 1 mW available source power, connect the output directly to a 50 Ohm load. what would be the power in the load?

$$\frac{P_L}{P_{AVG}} = G_T = \text{transducer gain}$$

$$\Gamma_L = 0 \quad \Gamma_S = \frac{10-1}{10+1} = 9/11$$

$$G_T = \frac{|S_{21}|^2 (1 - |\Gamma_S|^2) (1 - |\Gamma_L|^2)}{|(1 - \Gamma_S S_{11})(1 - \Gamma_L S_{22}) - S_{21} S_{12} \Gamma_S \Gamma_L|^2}$$

$$= \frac{|S_{21}|^2 (1 - |\Gamma_S|^2)}{|1 - \Gamma_S S_{11}|^2}$$

$$|1 - \Gamma_S S_{11}|^2$$

9/11 0.7071

$$= \frac{|1 - (0.421)|^2}{(0.421)^2} = \frac{0.579^2}{0.177} = 1.86$$

$$P_{L \text{ of } H} = 2 \text{ dB} / 5 \text{ mW} = 2.8115 \text{ mW}$$

$$= 186 \text{ mW}$$

7


5

Problem 2, 10 points

Gain definitions

A bipolar transistor is shown at right. $R_{be} = 1000$ Ohms, $g_m = 100$ mS, $R_{ce} = 10,000$ Ohms, $C_{be} = 100$ fF.

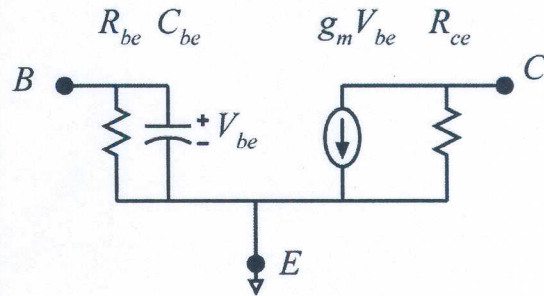The device is impedance-matched to a 50 Ohm generator and a 50 Ohm load at a 10 GHz signal frequency. Find the **magnitude** of S_{21} of the resulting **amplifier** at that frequency.




device is unilateral $\rightarrow S_{12} = 0$

$$\rightarrow G_{max} = \frac{1}{1 - |S_{11}|^2} |S_{21}|^2 \frac{1}{1 - |S_{22}|^2}$$

but S_{11} is hard to compute - try another approach.

If impedance matched at both ports
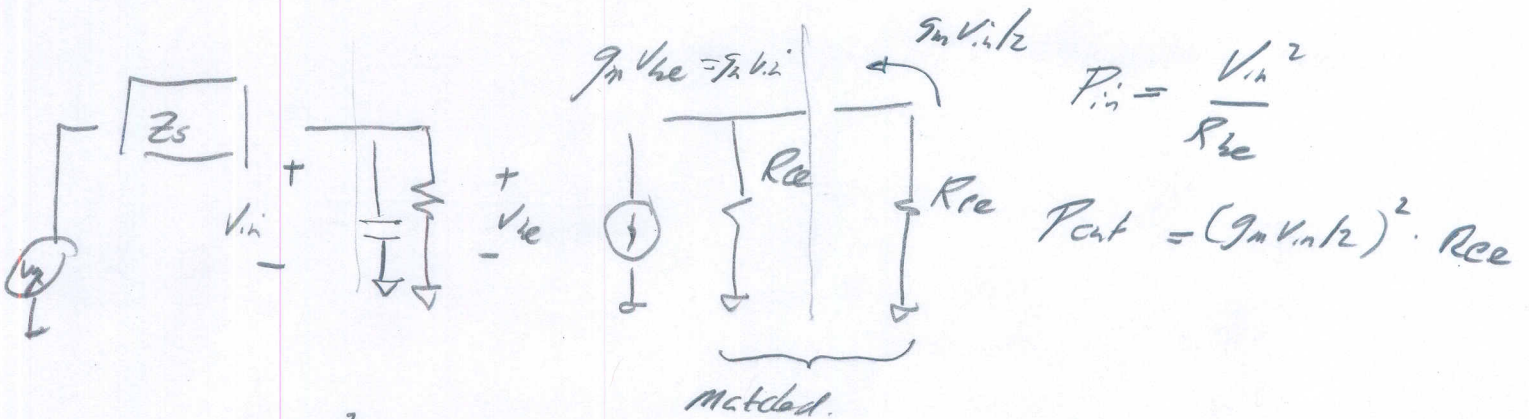
$$\text{Power Gain} = G_{max} = \frac{P_{out}}{P_{in}}$$



$$P_{in} = \frac{V_{in}^2}{R_{be}}$$

$$P_{out} = (g_m V_{in}/2)^2 \cdot R_{ce}$$

$$\frac{P_{out}}{P_{in}} = \frac{(g_m/2)^2 R_{ce}}{1/R_{be}} = \frac{g_m^2}{4} R_{ce} R_{be} = \frac{(0.15)^2}{4} 1k\Omega \cdot 10k\Omega = \underline{\underline{25,000}}$$


$$\text{ckt power gain} = |S_{21}|^2 = 25000 \rightarrow |S_{21}| = \underline{\underline{158}}$$

Problem 3, 15 points

Gain definitions, computation of Y-parameters


A bipolar transistor is shown at right. $C_{cb} = 100$ fF, $g_m = 100$ mS.

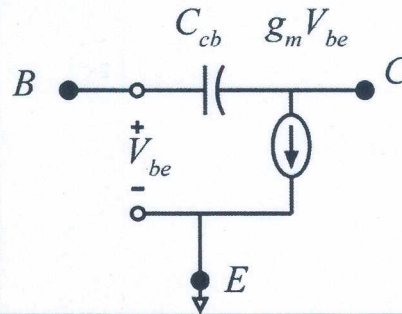It can be shown that $S_{21}/S_{12} = Y_{21}/Y_{12}$



part a, 10 points


compute Y_{21} and Y_{12}

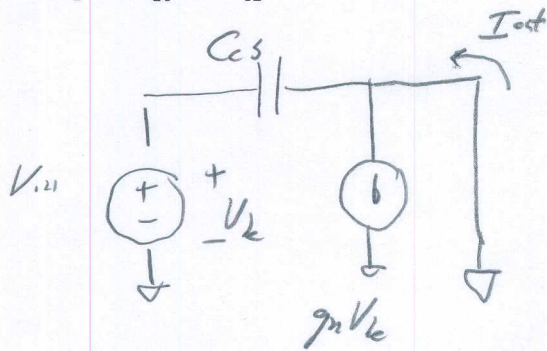

$$I_{out} = g_m V_{be} - j\omega C_{cb} V_{be}$$

$$= g_m - j\omega C_{cb}$$

$$Y_{21} = g_m - j\omega C_{cb}$$

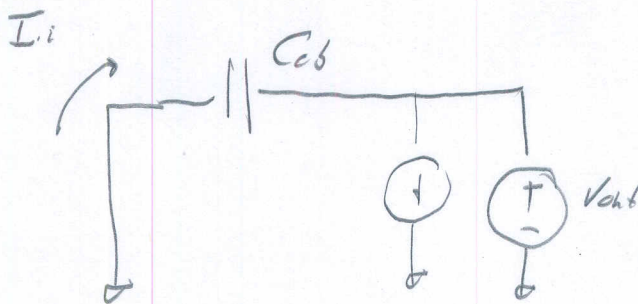

$$I_{in} = -j\omega C_{cb} \cdot V_{out}$$

$$Y_{12} = -j\omega C_{cb}$$

part b, 5 points

The transistor is first stabilized and then impedance-matched to 50 Ohm generator and load. Find the resulting amplifier gain magnitude $\|S_{21}\|$

$$\begin{aligned} \text{AMP. Gain} &= \text{MSG} = \frac{\|S_{21}^T\|}{\|S_{12}^T\|} = \frac{\|Y_{21}^T\|}{\|Y_{12}^T\|} \\ \text{Power} &= \frac{\|S_{21}^A\|^2}{\|S_{21}\|^2} \\ &= \frac{\frac{0.15}{N} \cdot 6.28 \cdot 10^{-3}}{\|1 - j\omega C_{cb}\|} \approx \frac{1}{\|1 - j\omega C_{cb}\| \cdot 6.28 \cdot 10^{-3}} \\ &= 159 = (10^4 / 2\pi) \end{aligned}$$


$$\|S_{21}^A\| = \sqrt{159} = 12.6$$

Problem 4, 10 points

Computation of S-parameters


A bipolar transistor is shown at right. $R_{be} = 25$ Ohms, $g_m = 100$ mS, $R_{ce} = \text{infinity}$ Ohms.

Find S_{11} and S_{21}

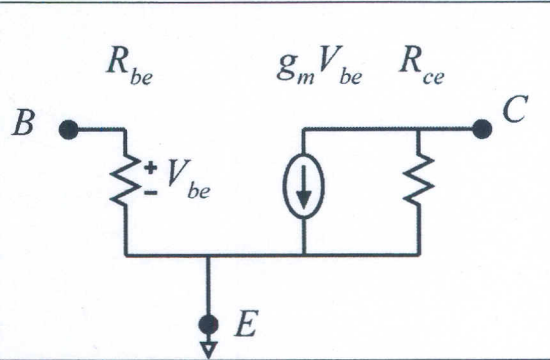

$$S_{11} = \frac{Z_{in}/Z_0 - 1}{Z_{in}/Z_0 + 1} = \frac{1/2 - 1}{1/2 + 1} = -1/3$$

$$S_{21} = 2 \frac{V_o}{V_a} \Big|_{Z_L = Z_0 = Z_a}$$

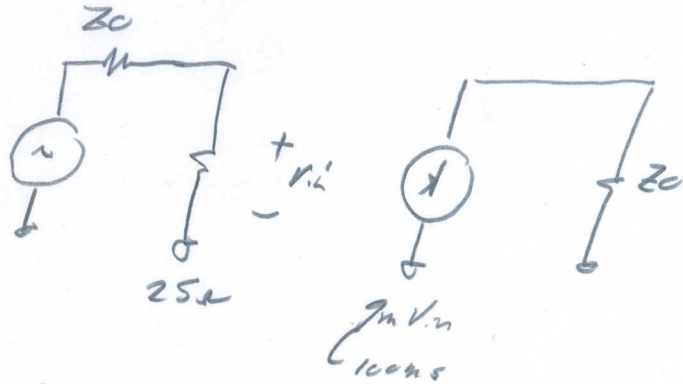

$$= 2 \cdot \frac{25}{25 + 50} \cdot (-g_m Z_0)$$

↑ ↑
100mS 50 Ohm


$$= 2 \cdot \frac{1}{3} \cdot (-5) = -\frac{10}{3}$$

$$S_{21} = -\frac{10}{3}$$

Problem 5, 10 points
Stabilization

stable here
because $|S_{22}| < 1$

stable here because
 $|S_{11}| < 1$

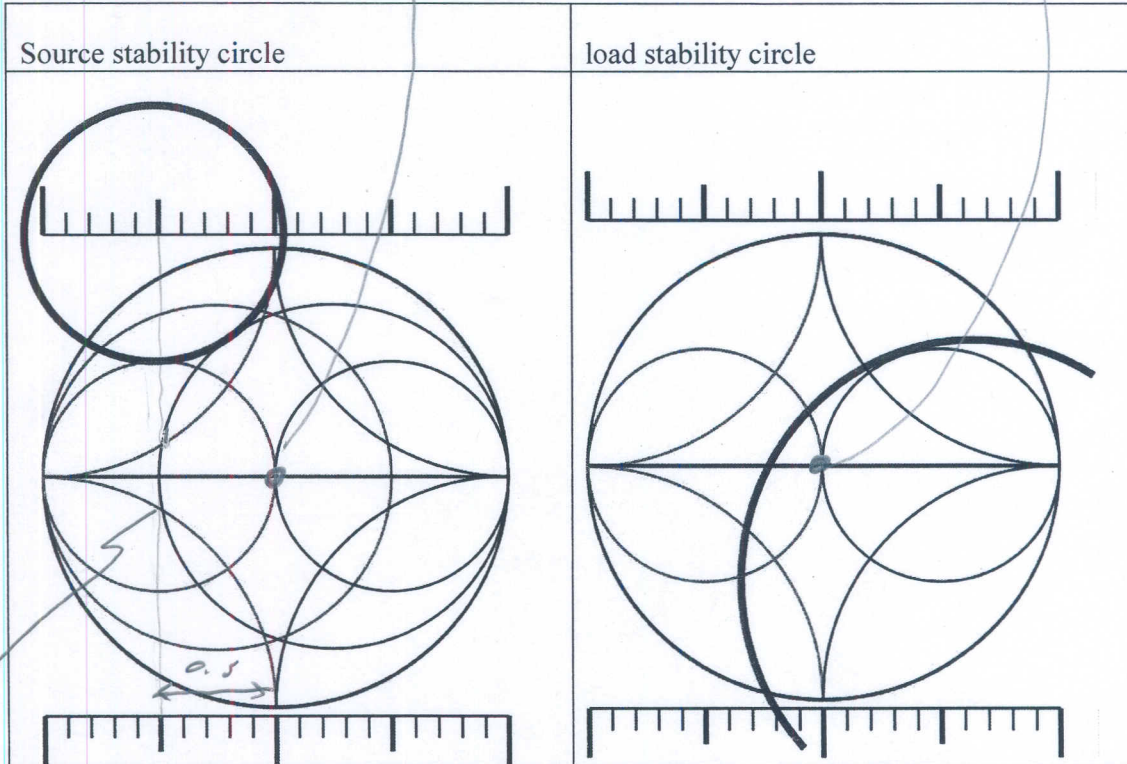


A MOSFET in common-source mode has $S_{11} = 0.5$ and $S_{22} = 0.3$. Source and load stability circles are as shown. Draw **3** circuit diagrams, giving resistor values, of methods of stabilizing the transistor.

Source: the indicated circle has $\frac{R}{Z_0} = \frac{1 - |S_{11}|^2}{1 + |S_{11}|^2} = \frac{1 - 1/4}{1 + 1/4} = 1/3$

$$\text{i.e. } R = \frac{50 \Omega}{3} = 16.6 \Omega$$

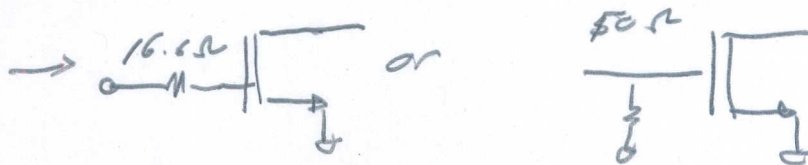the stability circle touches the $R = 16.6 \Omega$ circle
and the $G = (1/50 \Omega)$ circle



Load

$\Gamma_L = 0$ is stable because $|S_{11}| < 1$

$$\text{from } \Gamma_{in} = S_{11} + \frac{S_{12} S_{21} \Gamma_L}{1 - S_{22} \Gamma_L}$$

so inside of stability circle is stable

Circle touches the 50Ω series resistance circle


so 50Ω in series will stabilize

A short-circuit on the output is potentially unstable
so parallel stabilization does not work.



Problem 6, 5 points

Gain circles

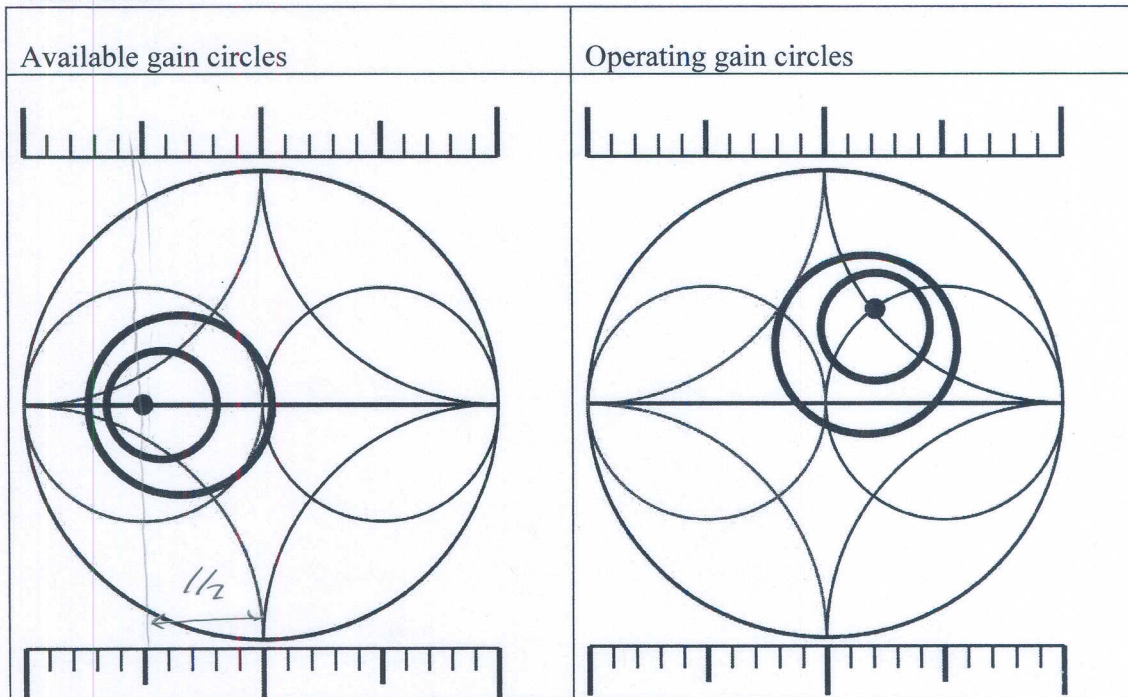

At 10 GHz, a MOSFET in common-source mode operating and available gain circles as shown. Find the optimum generator and load impedances (in complex Ohms).

Available gain - source match

$$\Gamma_S^{opt} = -1/2 \rightarrow Z_{opt} = Z_0 \frac{1 - \Gamma^{opt}}{1 + \Gamma^{opt}} = Z_0/3 = \underline{16.7 \Omega} + \underline{j0 \Omega}$$

operating gain - load match

optimum impedance, as shown, is $\frac{Z_L}{Z_0} = 1 + j \cdot 1$


$$Z_{L,opt} = Z_0 + jZ_0 = \underline{50 \Omega} + \underline{j50 \Omega}$$

Problem 7, 20 points

Amplifier design

A bipolar transistor is shown at right. $R_{be} = 25 \text{ Ohms}$, $g_m = 100 \text{ mS}$, $R_{ce} = 50 \text{ Ohms}$.

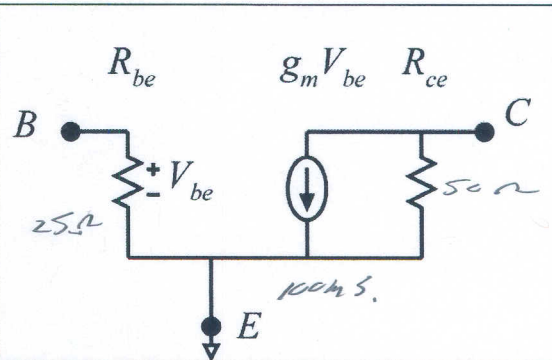The amplifier is to be impedance-matched, using ONLY lumped-element ****series**** inductors and shunt capacitors.



part a, 10 points.


Design on the attached Smith chart the input matching network. Give values of all elements.

output needs no matching network

input $\rightarrow Z_{in}/Z_0 = 25/50 = 1/2$

point "A" $\Rightarrow Z/Z_0 = 1/2 + j0$

point "B" $= Z/Z_0 = 0.5 + j0.5$

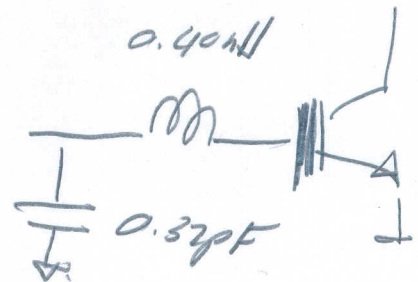

\rightarrow must add series element $\frac{Z}{Z_0} = j0.5 \rightarrow j\omega L = j0.5 \cdot 50 \Omega$

$$L = \frac{0.5 \cdot 50 \Omega}{2\pi (10 \text{ GHz})} = 0.40 \text{ nH}$$

point "B" $\Rightarrow Y/Y_0 = 1.0 - j1.0$


point "C" $\Rightarrow Y/Y_0 = 1.0 + j0$

\rightarrow must add shunt element $Y/Y_0 = j1.0 \rightarrow j\omega C = j1.0/50 \Omega$

$$\Rightarrow C = \frac{1}{50 \Omega (2\pi)(10 \text{ GHz})} = 0.318 \text{ pF}$$

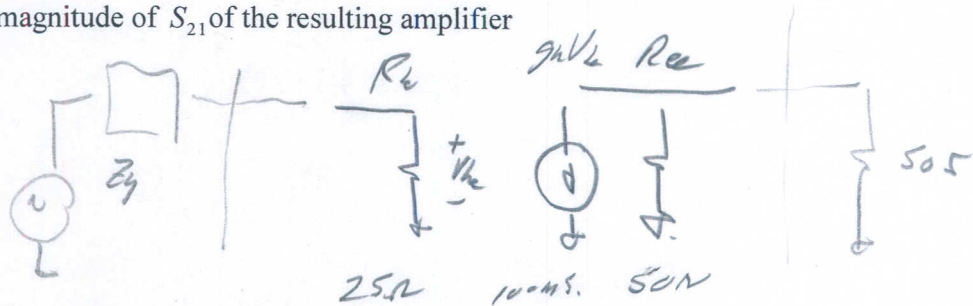part b, 10 points.

Determine the magnitude of S_{21} of the resulting amplifier



what is the transistor G_{max} ?

Match output & compute P_{out}/P_{in} , because with a matched input, $P_{in} = P_{AVG}$.

$$P_{in} = V_{be}^2 / R_{be}$$

$$P_{out} = (g_m V_{be})^2 (1/2)^2 \cdot \overbrace{50\Omega}^{R_{ce} = R_L}$$

$$\frac{P_{out}}{P_{in}} = \frac{(g_m/2)^2 R_{ce}}{1/R_{be}} = \frac{g_m^2 R_{ce} R_{be}}{4} = \underline{\underline{3.125}}$$


$\begin{matrix} 100mS & 50\Omega & 25\Omega \\ \swarrow & \searrow & \swarrow \\ & & \end{matrix}$

$$|S_{21}^{AMP}|^2 = \overset{\text{transistor}}{G_{max}} = 3.125$$

$$|S_{21}^{AMP}| = \sqrt{3.125} = 1.77$$

NAME	TITLE	DWG. NO.
SMITH CHART FORM ZY-01-N	Microwave Circuit Design - EE523 - Fall 2000	DATE

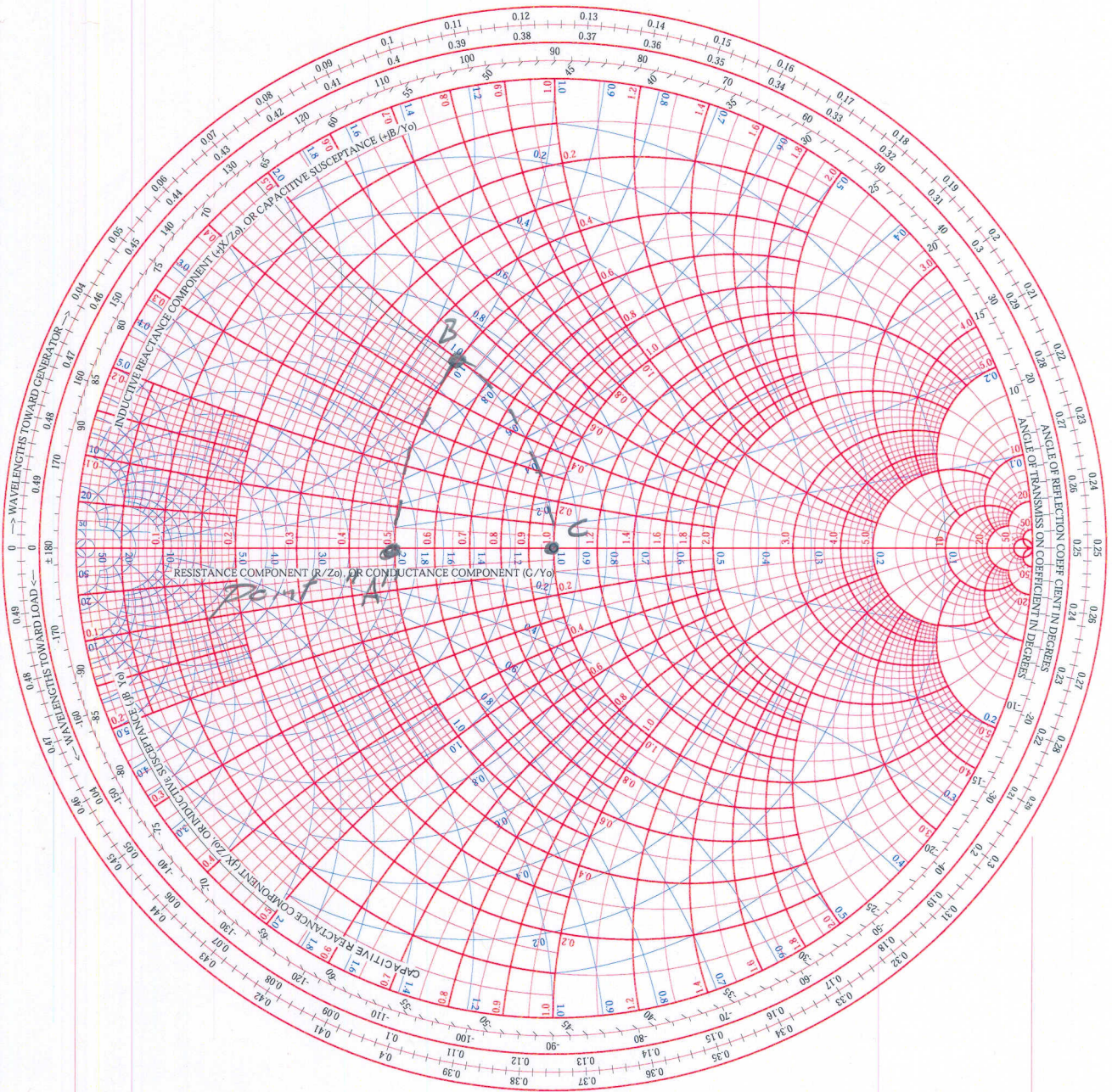NORMALIZED IMPEDANCE AND ADMITTANCE COORDINATES



Part A

RADIALLY SCALED PARAMETERS

