

ECE ECE145A (undergrad) and ECE218A (graduate)

Mid-Term Exam. October 30, 2018

Do not open exam until instructed to.

Open notes, open books, etc.

You have 1 hour and 15 minutes.

Use any and all reasonable approximations (5% accuracy is fine.), ***AFTER STATING THEM.***


Problem	Points Received	Points Possible
1		15
2a		10
2b		7
2c		8
2d (218 only)		15 (218A only)
3a		7.5
3b		7.5
4		15
5a		5
5b		5
5c		5
5d (218 only)		7.5 (218A only)
total		85 (145), 107.5 (218A)


Name: sdutton

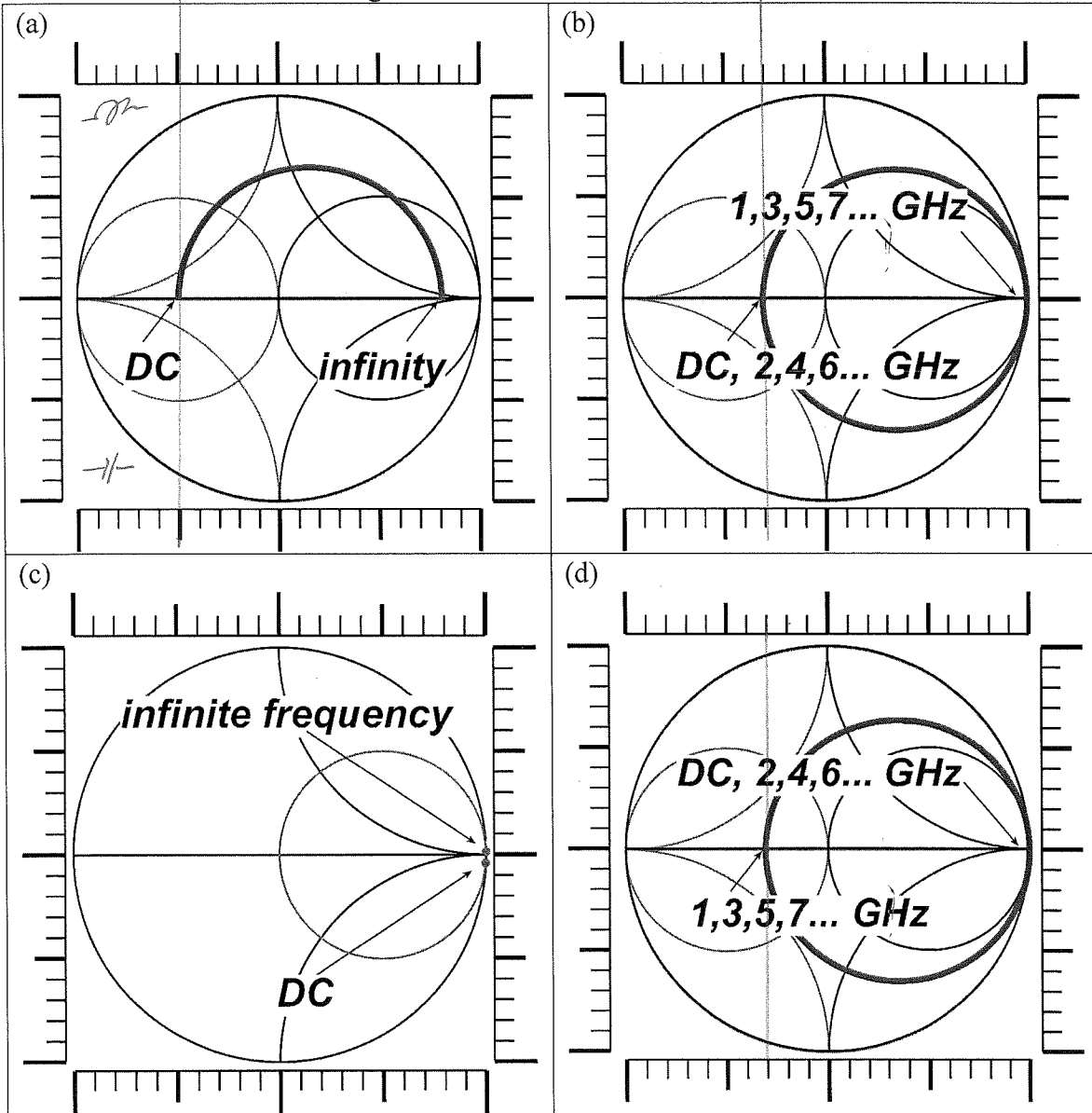
Problem 1, 15 points

The Smith Chart and Frequency-Dependent Impedances.

HINT: use the scales on the figures to measure distances as needed.



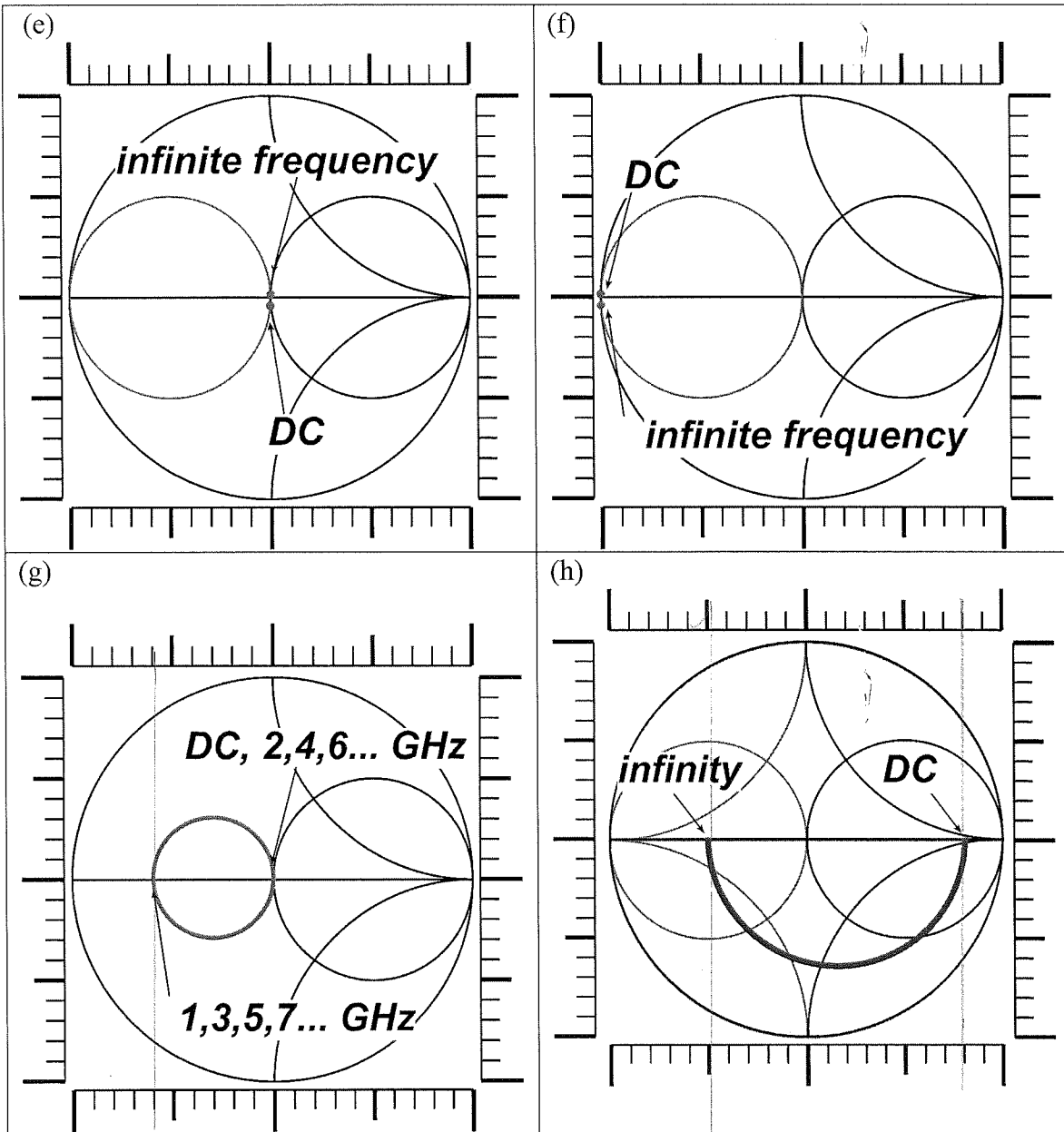

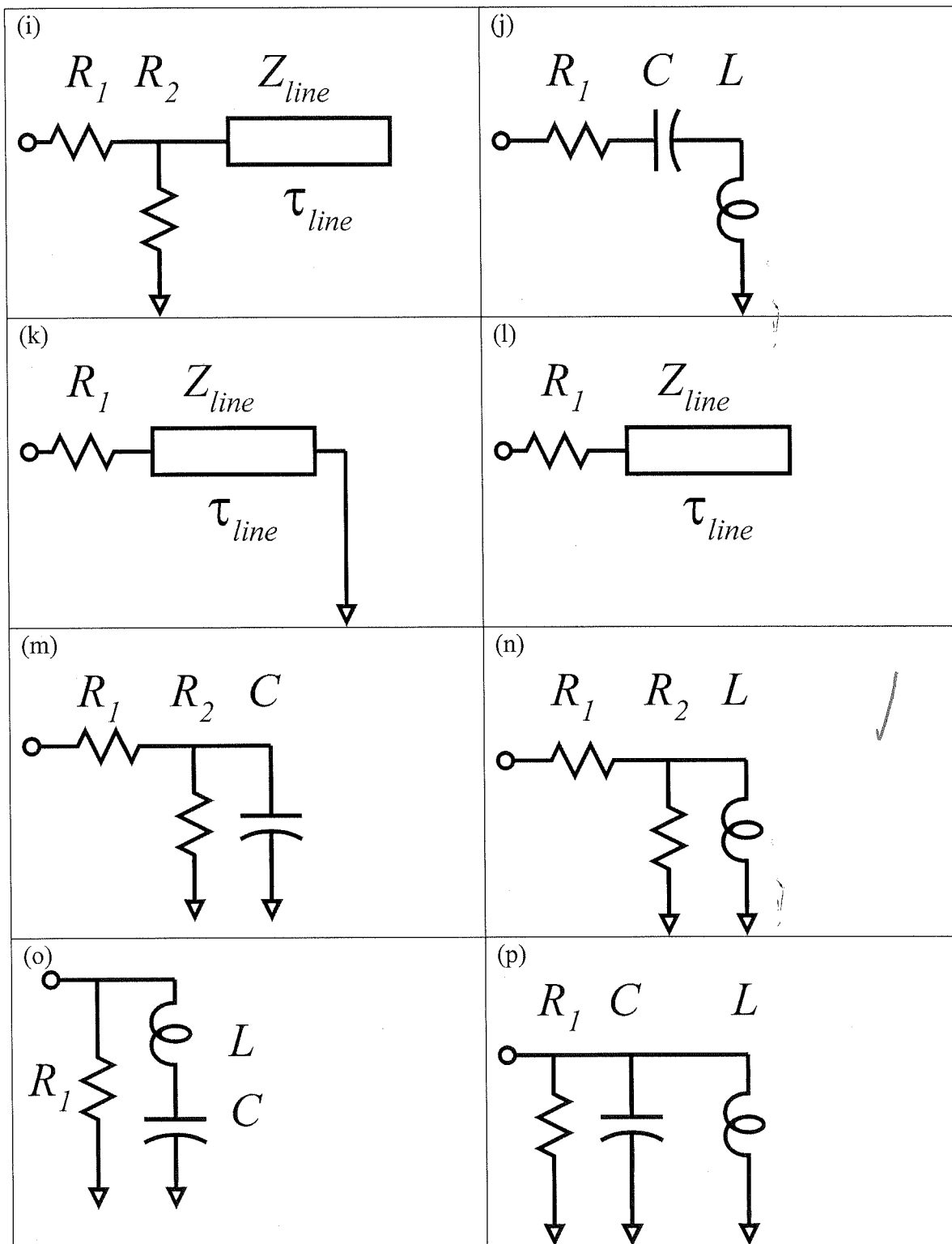

First match each Smith Chart with each circuit. *Then determine as many component values as is possible* (RLC values, transmission line delays and characteristic impedances)...note that some values cannot be determined with the information given. The charts all use 50 Ohm normalization:

- Smith chart (a). Circuit = N^1 .
Component values: $R_1 = 17\Omega$, $R_2 = 433\Omega$, _____,
- Smith chart (b). Circuit = K .
Component values: $R_1 = 27\Omega$, _____, _____,
- Smith chart (c). Circuit = (i) .
Component values: $R = 50\Omega$, _____, _____,
- Smith chart (d). Circuit = l .
Component values: $R = 27\Omega$, _____, _____,
- Smith chart (e). Circuit = ~~ERROR!~~.
Component values: _____, _____, _____,
- Smith chart (f). Circuit = (j) .
Component values: $R = 50\Omega$, _____, _____,
- Smith chart (g). Circuit = (L) .
Component values: $R_1 = 12.5\Omega$, $R_2 = 37.5\Omega$, _____,
- Smith chart (h). Circuit = h .
Component values: $R_1 = 433\Omega$, $R_2 = 17\Omega$, _____,

2 a) goes from $\Gamma = -1/2 @ DC \rightarrow 50\Omega \cdot \frac{1-1/2}{1+1/2} = \frac{50\Omega}{3} = 17\Omega$
to $\Gamma = 0.8 @ f \rightarrow \infty \rightarrow 50\Omega \cdot \frac{1.8}{0.2} = 50\Omega \cdot 9 = 450\Omega$
trajectory is inductive $\rightarrow (n)$
 $R_1 = 17\Omega$, $R_2 = 450 - 17\Omega = 433\Omega$


2 b) goes between $\Gamma = -0.3 \Rightarrow 50\Omega \cdot \frac{1-0.3}{1+0.3} = 27\Omega$
and an open circuit - does so repeatedly.
(K)

2 c) goes from open @ DC, to 50Ω , then to open.
 $\rightarrow (i)$ $R_1 = 50\Omega$

2 [D) goes between open & $50\Omega \cdot \frac{1-0.3}{1+0.3} = 27\Omega$
 does so repetitively
 $\rightarrow (l)$

0 [(E) goes from 50Ω @ DC to open
 & then 50Ω @ $f = \infty$.

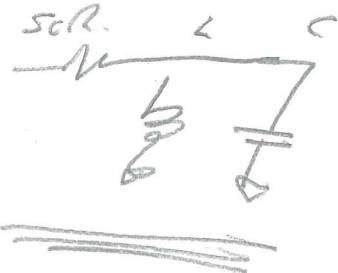(i) oh no! I've made a mistake!
 the right solution is



3 [(F) goes from 0Ω @ DC
 to 50Ω @ resonance, to 0Ω @ $f = \infty$
 $\rightarrow (P) \quad R_1 = 50\Omega$

2 [(G) goes repetitively between 50Ω @ DC
 and $50\Omega \left(\frac{1-0.6}{1+0.5} \right) = 12.5\Omega$ starting

(i) with $R_1 = 12.5\Omega$

$$\text{and } R_2 = 50\Omega - 12.5\Omega = 37.5\Omega$$

2 [(h) goes from $50\Omega \frac{1+0.8}{1-0.7} = 450\Omega$ @ DC
 to $50\Omega \left(\frac{1-0.3}{1+0.5} \right) = 17\Omega$ @ $f = \infty$
 Trajectory is capacitive $\Rightarrow (m)$


$$R_2 = 17\Omega$$

$$R_1 = 450\Omega - 17\Omega = 433\Omega$$


Problem 2, 25 points (ece145A), 40 points (ece218A)
 2-port parameters and Transistor models

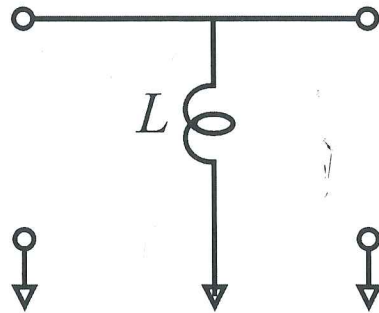Part a, 10 points

For the network at the right, give numerical values for the four S-parameters. Assume that the reference Z_0 is 50 Ohms. The signal frequency is 1GHz and the inductance is 8.0nH.



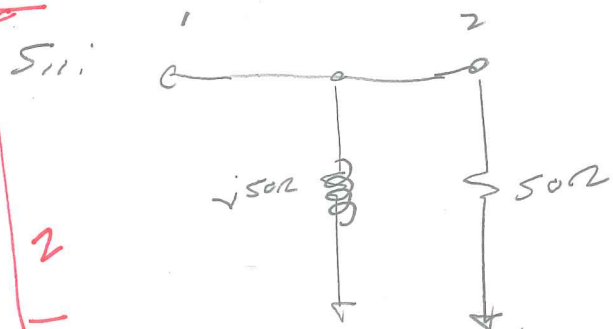1 [inductive reactance $= j\omega L = j2\pi(1\text{GHz})(8\text{nH})$
 $= j50\Omega$]



$$\begin{aligned} Z_{in} / Z_0 = 50\Omega &= 50\Omega \parallel j50\Omega \\ &= 50\Omega \left(\frac{1 \cdot j}{1+j} \right) \end{aligned}$$


2

$$S_{11} = \frac{Z_{in} / Z_0 - 1}{Z_{in} / Z_0 + 1} = \frac{\frac{j50\Omega}{50\Omega} - 1}{\frac{j50\Omega}{50\Omega} + 1} = \frac{j - 1}{j + 1}$$

$$= \frac{-1}{1 + 2j} = \frac{1 \angle 180^\circ}{\sqrt{5} \angle 63.4^\circ} = \frac{1}{\sqrt{5}} \angle 117^\circ$$

all ok.

1/2 [by symmetry, $S_{22} = S_{11}$]

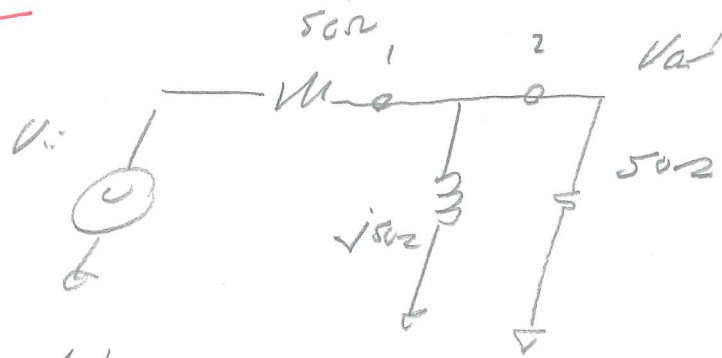

$$\frac{V_{out}}{V_i} = \frac{50\Omega \parallel j50\Omega}{50\Omega + 50\Omega \parallel j50\Omega} = \frac{1 \parallel j}{1 + 1 \parallel j}$$

$$= \frac{\frac{j}{1+j}}{1 + \frac{j}{1+j}} = \frac{j}{1+2j}$$

$$= \frac{1 \angle 90^\circ}{\sqrt{5} \angle 63^\circ} = \frac{1}{\sqrt{5}} \angle 27^\circ$$


$$S_{11} = 2 \cdot \frac{V_c}{V_{gen}} \Big|_{Z_L = Z_S = Z_0} = \frac{2}{\sqrt{5}} \angle 27^\circ \text{ or } = \frac{2j}{1+2j}$$

either ok.

1/2. [and, by symmetry, $S_{11} = S_{12}$]

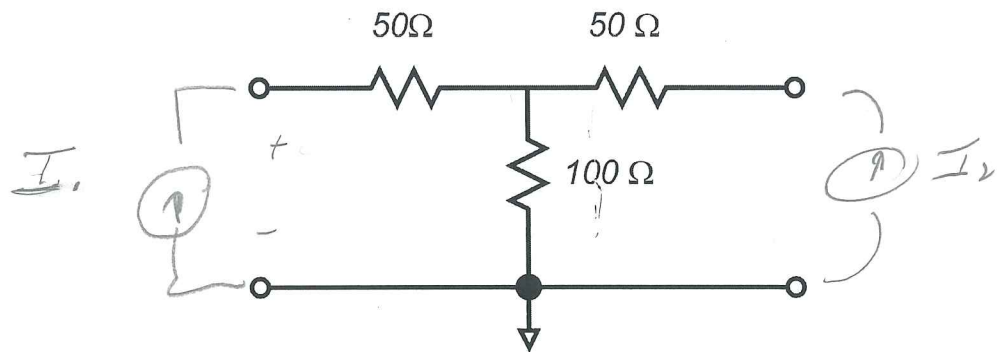Part b, 7 points

Compute the Z parameters for this network



$$Z_{11} = Z_{22} = 150 \Omega$$

$$Z_{21} = Z_{12} = 100 \Omega$$


[by inspection, $V_1 = I_1 (150 \Omega) + I_2 (100 \Omega)$] 5
[so this gives Z_{11} and Z_{12}] !

[Z_{22} and Z_{21} by symmetry.] !

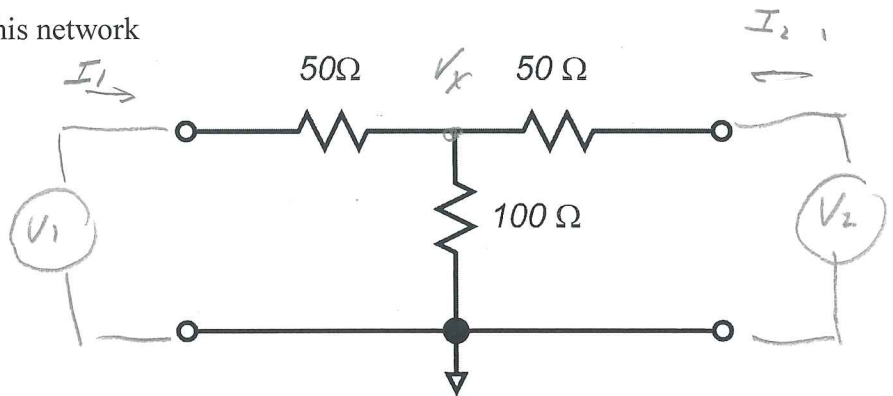Part c, 7 points

Compute the Y parameters for this network

We could just
invert the Z matrix...
... or ...



we don't know V_x , so:

$$2 \left[\frac{V_x - V_1}{50\Omega} + \frac{V_x - V_2}{50\Omega} + \frac{V_x}{100\Omega} = 0 \right]$$

$$V_x (5ms) = V_1 (2ms) + V_2 (2ms)$$

$$1 \left[V_x = 0.4 \cdot V_1 + 0.4 \cdot V_2 \right]$$

$$50 \left[I_1 = \frac{V_1 - V_x}{50\Omega} = (V_1 - V_x) 2ms = 2ms(V_1 - 0.4V_1 - 0.4V_2) \right]$$

$$1 \left[I_1 = 2ms(0.6V_1 - 0.4V_2) = 1.2ms \cdot V_1 - 0.8ms \cdot V_2 \right]$$

$$1 \left[I_1 = Y_{11}V_1 + Y_{12}V_2 = 1.2ms \cdot V_1 - 0.8ms \cdot V_2 \right]$$


$$1 \left[\begin{array}{l} \text{so } Y_{11} = 1.2ms, \quad Y_{12} = -0.8ms \\ \text{by symmetry, } Y_{22} = Y_{11} \text{ and } Y_{21} = Y_{12} \end{array} \right]$$

Part d, ECE218A students only 15 points

For the network at the right, give an algebraic expressions for Y_{11} and Y_{21} .

Please write as a Taylor series in $j\omega$, omitting terms of power $(j\omega)^3$ and higher.

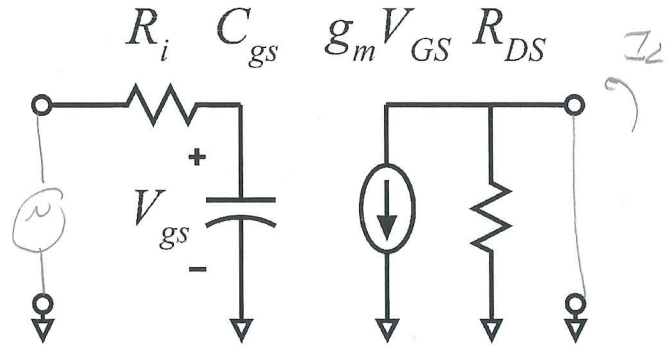This is an exercise in device model extraction from measured S/Y/Z parameters.



If $V_1 \neq 0, V_2 = 0$ then

$$2 \quad I_1 = Y_{11} V_1 = \frac{V_1}{R_i + \frac{1}{j\omega C_{gs}}} = V_1 \frac{j\omega C_{gs}}{1 + j\omega C_{gs} R_i}$$

$$3 \quad \text{so } Y_{11} = \frac{j\omega C_{gs}}{1 + j\omega C_{gs} R_i} \approx j\omega C_{gs} (1 - j\omega C_{gs} R_i + O(\omega^2))$$

$$3 \quad Y_{11} = j\omega C_{gs} + \omega^2 C_{gs}^2 R_i + O(\omega^3)$$

$$2 \quad \frac{V_{gs}}{V_1} = \frac{1/j\omega C_{gs}}{R_i + 1/j\omega C_{gs}} = \frac{1}{1 + j\omega C_{gs} R_i}$$

$$2 \quad \left[\frac{I_2}{V_1} = Y_{21} = \frac{g_m}{1 + j\omega C_{gs} R_i} \right] = \frac{g_m (1 - j\omega C_{gs} R_i)}{1 + \omega^2 C_{gs}^2 R_i^2}$$

$$4 \quad = g_m (1 - j\omega C_{gs} R_i) (1 - \omega^2 C_{gs}^2 R_i^2 + O(\omega^4))$$

$$4 \quad Y_{21} = g_m (1 - j\omega C_{gs} R_i - \omega^2 C_{gs}^2 R_i^2 + O(\omega^3))$$

Problem 3, 15 points

Transmission lines in the time domain.

Part a, 7.5 points



V_{gen} is a 1 V step-function.

R_{gen} is zero Ohms and R_L is 50 Ohms.

τ is 1 ns.

Z_{line} is 50 Ohms.

Plot below $V_{out}(t)$ and $V_{in}(t)$

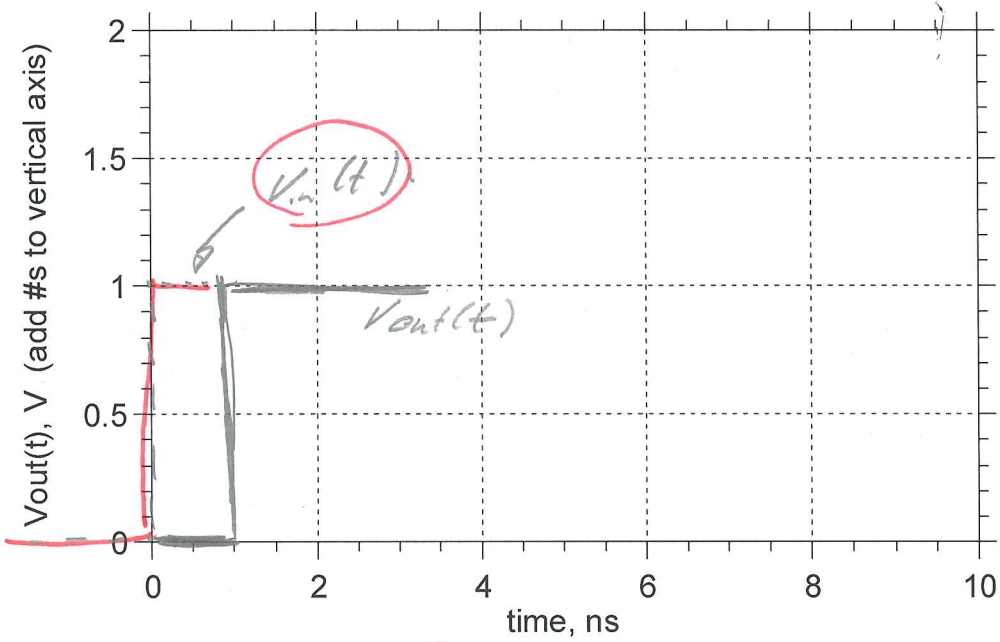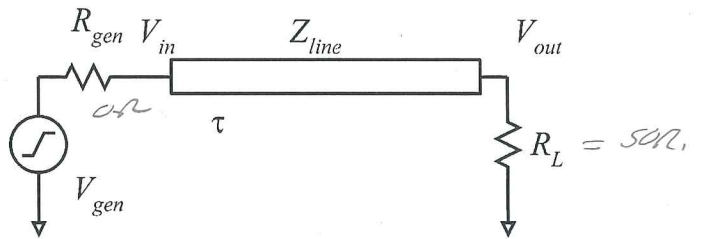

3.7 spTs each...


Part b, 7.5 points

V_{gen} is a 1 V step-function.

R_{gen} is 50 Ohms and R_L is infinite.


τ is 1 ns.

Z_{line} is 50 Ohms.

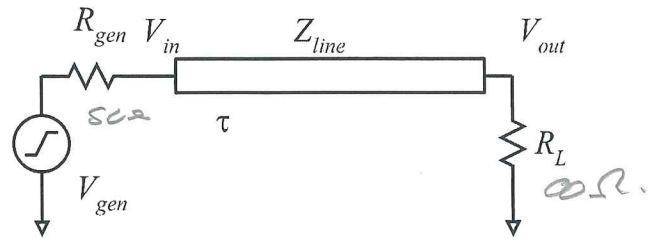

Plot below $V_{out}(t)$ and $V_{in}(t)$

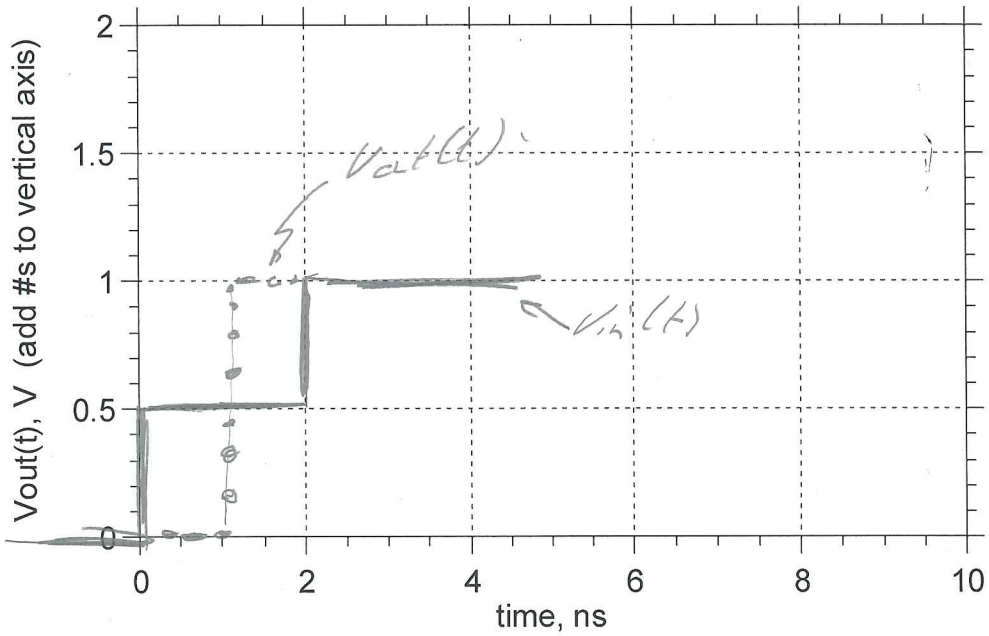Please comment on the pulse response of this circuit and that of part a.




Q.5

$$\Gamma_L = \frac{\infty - 1}{\infty + 1} = 1$$

$$\Gamma_S = 0$$

$$\tau_S = \frac{\tau_0}{Z_0 + R_{gen}} = 1/2$$

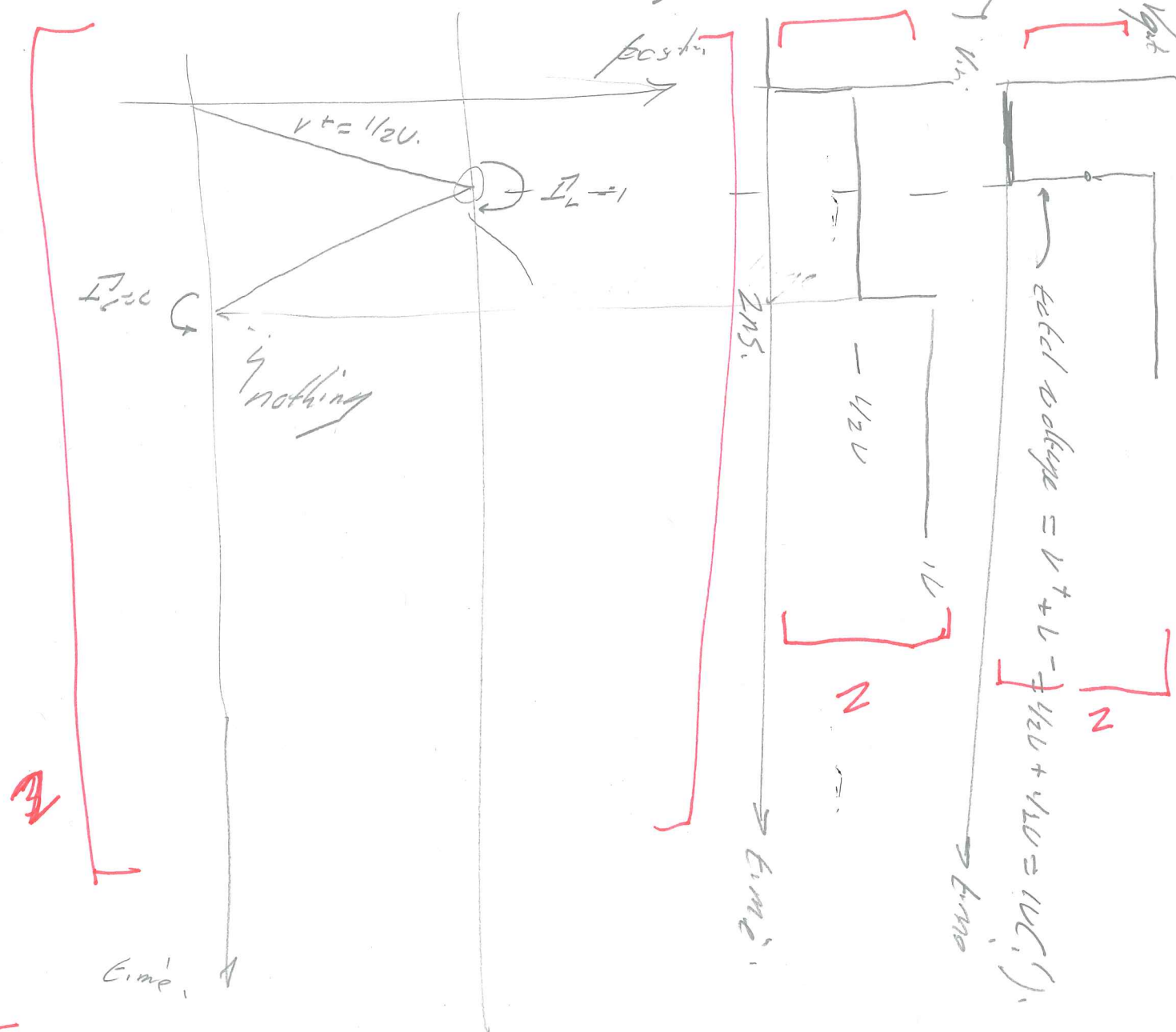$P_c = \frac{1}{2}$, $T_s = 1/2$, $I_s = 0$.




Comment

part (a) is called receiving end termination.
 signal is and started at both ends of line.

part (b) is called sending end termination.
 signal is and started only at receiving
end of line.

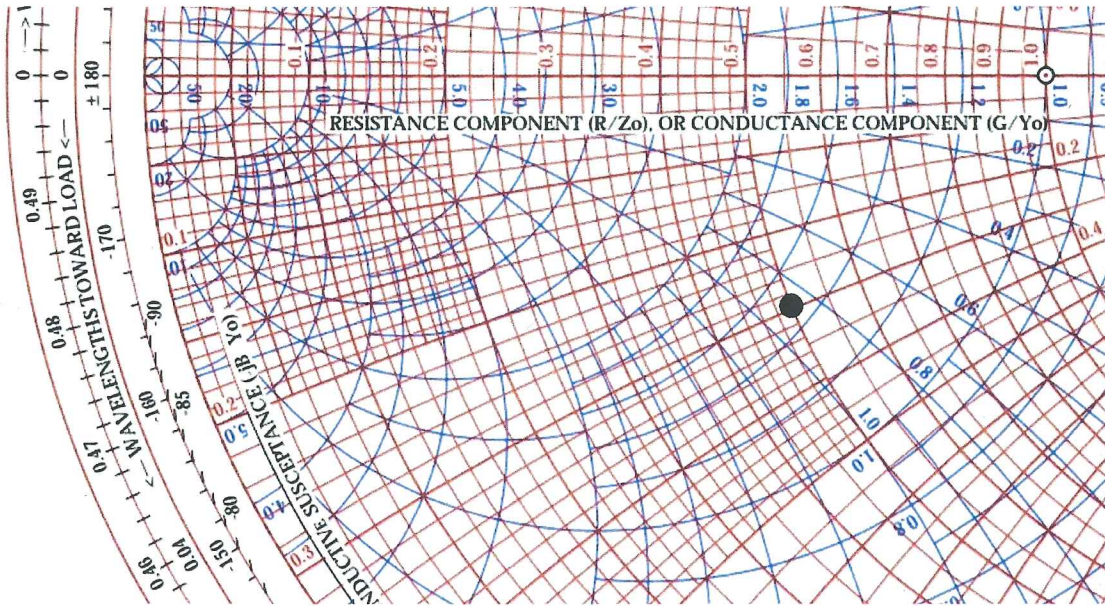Problem 4, 15 points
Impedance-matching exercise.

The (50 Ohm normalization) Smith chart gives the input impedance of a circuit at 1 GHz signal frequency. Design a lumped-element matching network which converts this impedance to **50 Ohms**. Give all element values. Use the full impedance-admittance chart which has been provided to you.



There are two different
lumped element solutions

Both are shown

either one is acceptable.

First soln.

2. Point "A" is at an impedance, normalized
of $Z_A = 0.5 - j0.3$.

2. We move to point "B", which has a normalized
impedance of $Z_B = 0.5 + j0.5$

2. This movement from "A" to "B" corresponds to the addition
of $\Delta Z = j0.5 - (-0.3j) = 0.8j$
an un-normalized impedance of $\Delta Z = 0.8 \cdot 50 \Omega \cdot j$
 $= j40 \Omega$

This is an inductor $\Delta Z = j\omega L = j40 \Omega$
 $\rightarrow L = \frac{40 \Omega}{\omega} = \frac{40 \Omega}{2\pi(16 \text{ kHz})} \approx 6.37 \text{ nH}$.

2. Point "B" has a normalized admittance of
 $Y_B = 1.0 - j1.0$




2. Point "C" has a normalized admittance of
 $Y_C = 1.0 + j0$.

3. This movement from "B" to "C" corresponds to
the addition of
 $\Delta Y = j0 - (-j1) = j1$
an un-normalized admittance of $\Delta Y = \frac{j1}{50 \Omega} = +j(20 \text{ mS})$.

2. This is a capacitor $\Delta Y = j\omega C = j20 \text{ mS}$
 $C = \frac{20 \text{ mS}}{2\pi(16 \text{ kHz})} = 3.18 \text{ pF}$

NAME	TITLE <i>Second solution</i>	DWG. NO.
SMITH CHART FORM ZY-01-N	Microwave Circuit Design - EE523 - Fall 2000	DATE

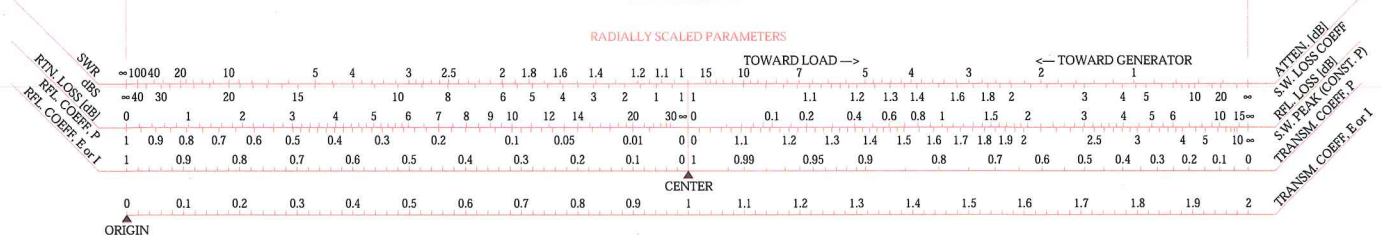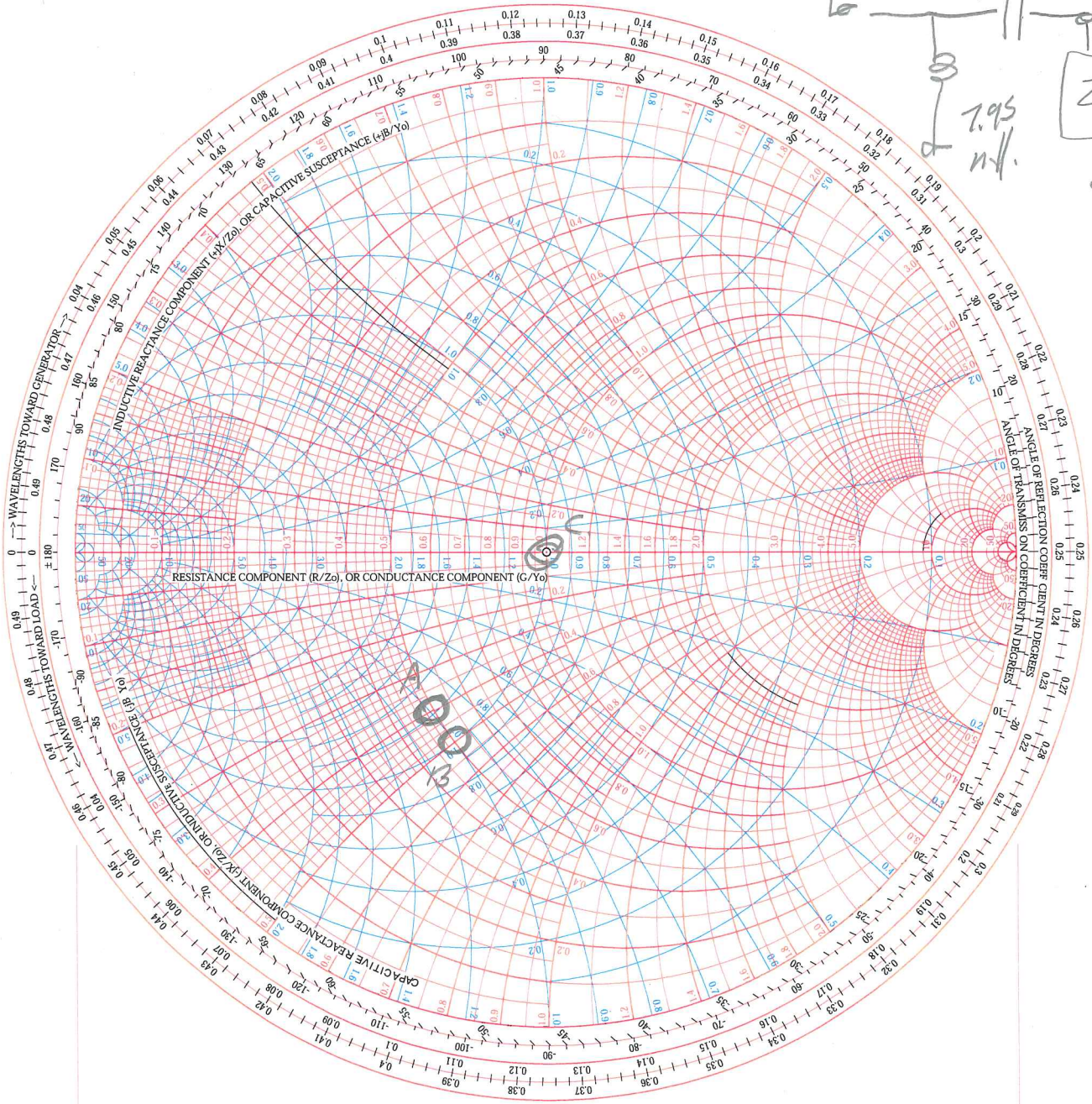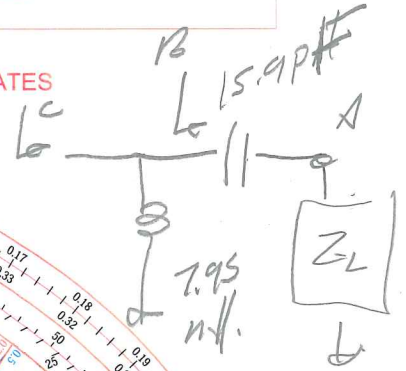NORMALIZED IMPEDANCE AND ADMITTANCE COORDINATES



Second solution

2 [point "a" is at the normalized impedance
 $z_A = 0.5 - j0.3$

2 [we move to point "B", a normalized impedance of
 $z_B = 0.5 - j0.5$

2 [This movement from "A" to "B" corresponds to the
addition of $\Delta z = -j0.5 - (-j0.3) = -j0.2$
an an-normalized impedance of

$$\Delta B = -j0.2 \cdot 50\Omega = -j10\Omega$$

This is a series capacitor $\Delta Z = \frac{1}{j\omega C} = -j10\Omega$

$$\Rightarrow C = \frac{1}{10\Omega \cdot 2\pi(16\text{kHz})} = 15.9\text{pF}$$

2 [Point "B" has a normalized admittance of
 $y_B = 1 + j1$

2 [point "c" has a normalized admittance of
 $y_c = 1 + j0$

3 [The movement from "B" to "c" corresponds to
the addition of $\Delta y = j0 - (j1) = -j1$ g
an an-normalized admittance of $\Delta Y = \frac{-j1}{50\Omega} = -j(20\text{ms})$

2 [This is an inductor $\Delta Y = \frac{1}{j\omega L} = -j(20\text{ms})$

20

$$L = \frac{50\Omega}{2\pi(16\text{kHz})} = 7.95\text{nH}$$

Problem 5, 15 points (ece145A), 20 points (218A)
 Transmission-line properties.

Part a, 5 points

Z_{in}




In an undergraduate class, a 1 meter length of 50 Ohm cable connects a circuit under test to an oscilloscope. The input impedance to the oscilloscope is extremely high. The propagation velocity of the transmission line is $2 \cdot 10^8$ m/s. At a signal frequency of 1 MHz, what would the input impedance be, approximately?

speed of light delay = $\tau = \frac{l}{v} = \frac{1\text{m}}{2 \cdot 10^8 \text{ m/s}}$

$\tau = 5\text{ns}$

The period of 1MHz is $1\mu\text{s}$, so $\tau \ll T$, or equivalently, $l \ll \lambda$

use lumped element model: T-section

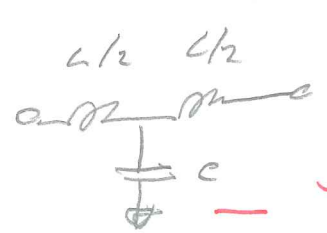

$C = \frac{l}{v} \epsilon_0 = \frac{5\text{ns}}{500} = 10\text{pF}$
 $L = \tau \cdot Z_0 = 5\text{ns} \cdot 50\Omega = 0.25\mu\text{H}$

$Z_{in} = j\omega \frac{L}{2} + \frac{1}{j\omega C} = +j(1.6\Omega) - j1590\Omega$

$\approx \frac{1}{j\omega C} = -j1590\Omega$

Part b, 5 points


Z_{in}



At 1 MHz, if we short-circuit the far end of the cable, what would be the approximate input impedance?

2.5

now use a π -section

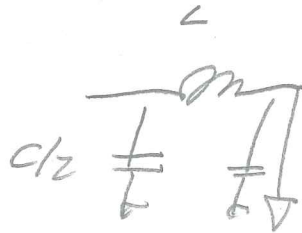

2.5

$$Z = j\omega L \parallel \frac{1}{j\omega C/2} = j(1.6\Omega) \parallel (-j31.8\Omega)$$
$$\approx \underline{\underline{j1.6\Omega}}$$

Part c, 5 points

Z_{in}



At what frequencies is the input impedance infinite?

At what frequencies is the input impedance zero?

1 [line has $v = 5 \text{ m/s}$


1 [so line is one wavelength long @ $f = \frac{v}{\lambda} = 200 \text{ MHz}$

1 [line is $\frac{1}{4}$ λ long @ $f = 50 \text{ MHz}$
line is $\frac{3}{4}$ λ long @ $f = 150 \text{ MHz}$

1 [Input impedance will be zero @
 $f = 0, 100 \text{ MHz}, 200 \text{ MHz}, 300 \text{ MHz}, \dots$

1 [Input impedance will be infinite when
 $f = 50 \text{ MHz}, 150 \text{ MHz}, 250 \text{ MHz}, 350 \text{ MHz}, \dots$

Part d, 7.5 points ECE 218 students only

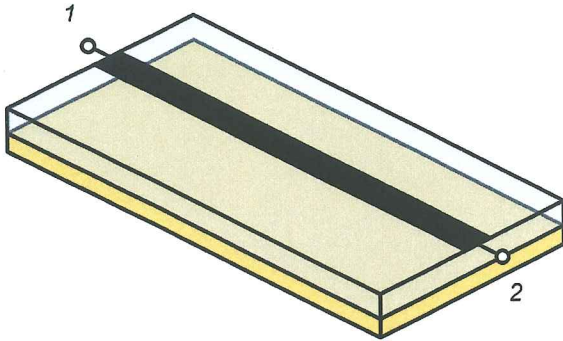

Denyer - confusion of

L = inductance

and L = length

I've written L_m for inductance

-We will make a 50 Ohm microstrip line on a circuit board of 1mm thickness having a dielectric constant of 4. If we ignore fringing fields, how wide must the conductor be?

-Using transmission-line relationships, and ignoring the fringing fields, derive expressions for the inductance and capacitance of a conductor of length L and width W , on a circuit board of thickness T , where the circuit board has a ground plane on the back surface.

if we ignore fringing fields, then

$$Z_0 \cong 377 \Omega \frac{1}{\sqrt{\epsilon_r}} \frac{H}{W} = 50 \Omega$$

$$377 \Omega = \sqrt{\frac{\mu_0}{\epsilon_0}}$$

$$\Rightarrow H/W = \frac{50 \Omega}{377 \Omega} \cdot 147 = 0.265$$

$$W = \frac{H}{0.265} = \frac{1 \text{ mm}}{0.265} = 3.77 \text{ mm}$$

if we ignore fringing fields, then the capacitance must be

$$C = \epsilon_0 \epsilon_r \frac{W \cdot L}{v H L}$$

$$\text{But } Z_0 = \sqrt{\frac{L}{C}} = \sqrt{\frac{\mu_0 \mu_r}{\epsilon_0 \epsilon_r}} \frac{H}{W} \rightarrow$$

$$L = \left(\frac{\mu_0 \mu_r}{\epsilon_0 \epsilon_r} \right) \frac{H^2}{W^2} \cdot C$$

$$L_m = \frac{\mu_0 \mu_r}{\epsilon_0 \epsilon_r} \frac{H^2}{W^2} \cdot \epsilon_0 \epsilon_r \frac{W \cdot L}{H} \rightarrow$$

$$L_m = \mu_0 \mu_r \frac{H}{W} \cdot L$$