

ECE ECE145A (undergrad) and ECE218A (graduate)

Mid-Term Exam. November 14, 2019

Do not open exam until instructed to.

Open notes, open books, etc.

You have 1 hour and 15 minutes.

Use any and all reasonable approximations (5% accuracy is fine.), ***AFTER STATING THEM.***


Problem	Points Received	Points Possible
1		15
2a		10
2b		7
2c		8
2d (218 only)		15 (218A only)
3a		7.5
3b		7.5
4		15
5a		5
5b		5
5c		5
5d (218 only)		15 (218A only)
total		85 (145), 115 (218A)


Name: Solution

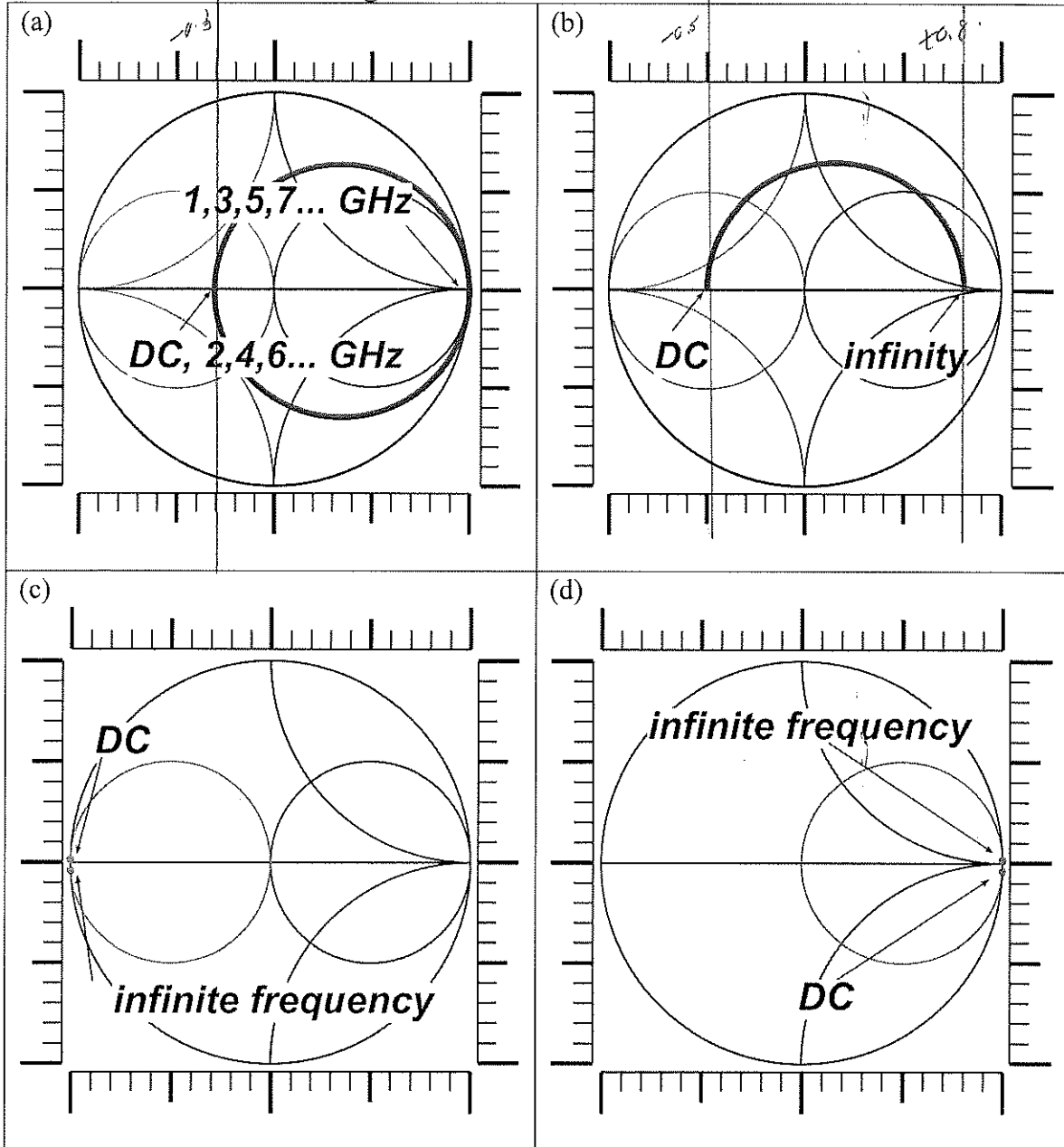
Problem 1, 15 points

The Smith Chart and Frequency-Dependent Impedances.

HINT: use the scales on the figures to measure distances as needed.



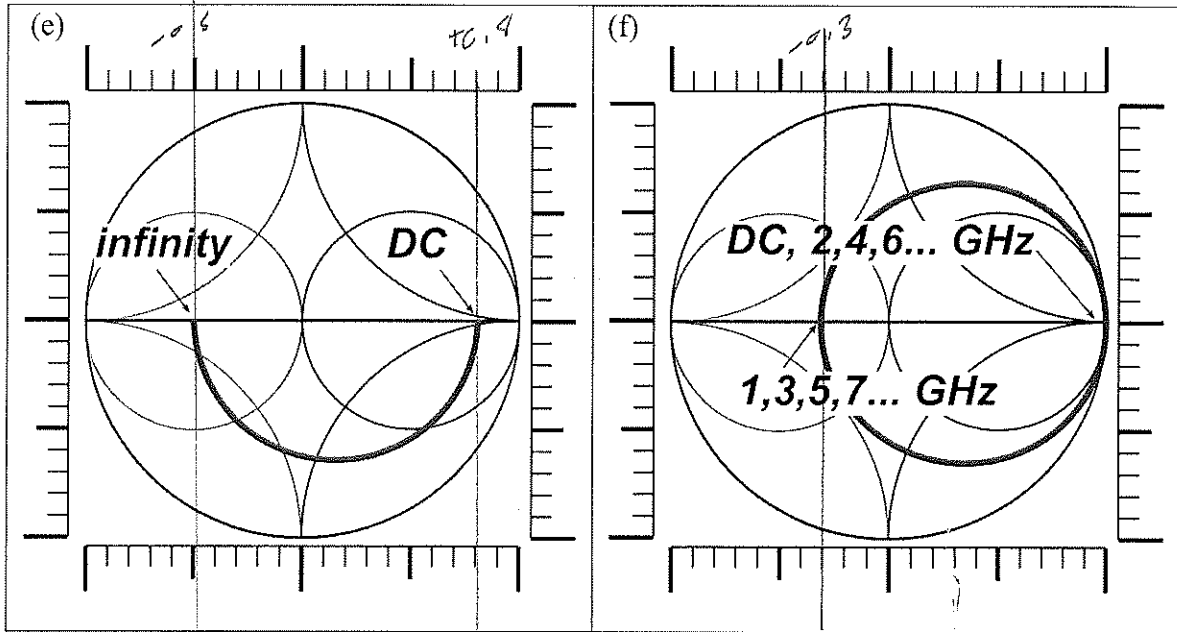

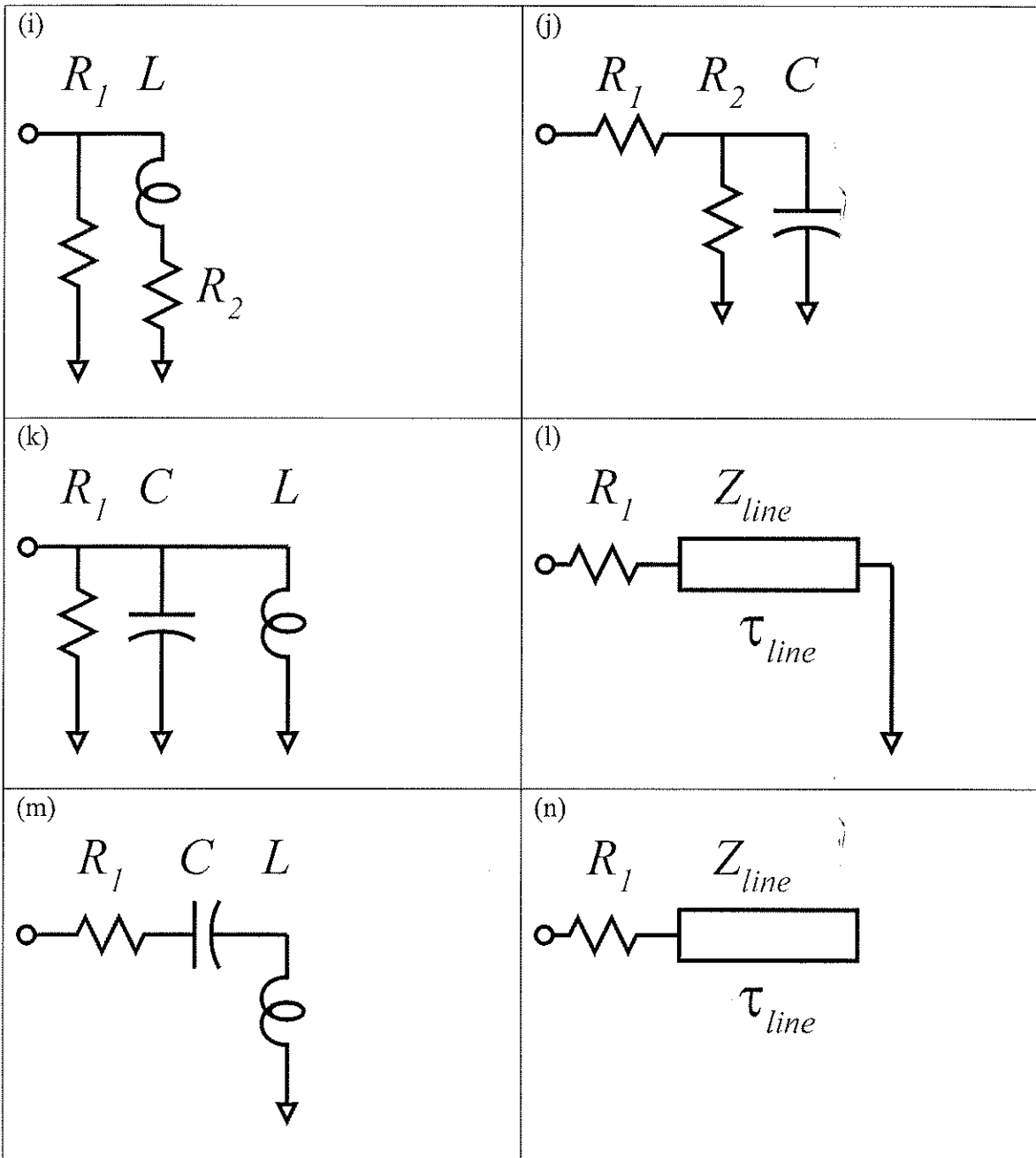


First match each Smith Chart with each circuit. **Then determine as many component values as is possible** (RLC values, transmission line delays and characteristic impedances)...note that some values cannot be determined with the information given. The charts all use 50 Ohm normalization:

- Smith chart (a). Circuit= ℓ .
 Component values: $R = 26.9 \Omega$, $\gamma = 114 \text{ ns}$, _____,
 Smith chart (b). Circuit= L .
 Component values: $R_1 = 450 \Omega$, $R_2 = 17.3 \Omega$, _____,
 Smith chart (c). Circuit= K .
 Component values: $R = 50 \Omega$, _____,
 Smith chart (d). Circuit= M .
 Component values: $R = 50 \Omega$, _____,
 Smith chart (e). Circuit= J .
 Component values: $R_1 = 16.7 \Omega$, $R_2 = 433 \Omega$, _____,
 Smith chart (f). Circuit= N .
 Component values: $R = 27 \Omega$, $\gamma = 44 \text{ ns}$, _____,

a) $\Gamma = -0.3 \rightarrow Z = Z_0 \frac{1 - \Gamma}{1 + \Gamma} = 26.9 \Omega$ (a)
 impedance is ∞ at $1, 3, 5, \dots$ $\lambda/8$.
 \rightarrow network ℓ with $R = 26.9 \Omega$. !
 line is $\lambda/4$ @ $16 \text{ GHz} \rightarrow$ is λ @ $4 \text{ GHz} \rightarrow \gamma = 114 \text{ ns}$
 $= 250 \text{ ps}$!


b) impedance increases with frequency \rightarrow (b)
 $R = 50 \Omega (1 - 0.5) / (1 + 0.5) = 16.7 \Omega$
 $\infty \rightarrow R = 50 \Omega (1 + 0.5) / (1 - 0.5) = 450 \Omega$!
 $R_1 = 450 \Omega$
 $R_2 = (1 / 16.7 \Omega - 1 / 450 \Omega)^{-1} = 17.3 \Omega$

c) impedance increases from 0Ω @ DC (c)
 then reaches 50Ω , drops to 0Ω as $f \rightarrow \infty$.

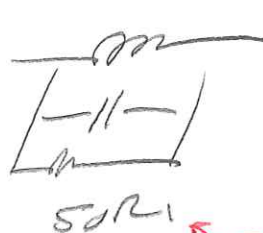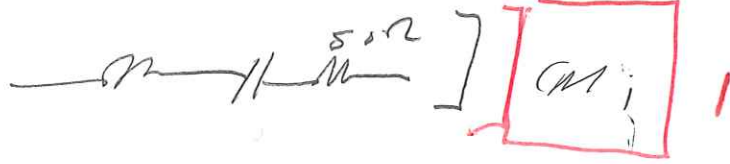
 (c) (c)
5

D)

goes from open @ DC to open @ $f = \infty$.
 1 [50Ω at some intermediate frequency]



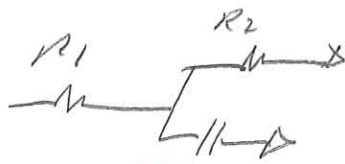5] goes from $\Gamma = +0.8 \Rightarrow R = 50\Omega \frac{1+0.8}{1-0.8} = 450\Omega @ DC$
 to $\Gamma = -0.5 \Rightarrow R = 50\Omega \frac{1-0.5}{1+0.5} = 16.6\Omega @ f = \infty$



(i)] 1

$$R_1 + R_2 = 450\Omega$$

$$R_1 = 16.6\Omega$$

$$R_2 = 450\Omega - 16.6\Omega = 433.4\Omega$$

2

Q.

Impedance is infinity @ 2, 4, 6 GHz

Line is 1/4 @ 15 GHz \rightarrow 1 @ 45 GHz $\rightarrow \tau = 25495$


1 [@ 15 GHz, $\Gamma = -0.3, \Rightarrow R = 50\Omega \frac{1-0.3}{1+0.3} = 26.9\Omega$

net to $\frac{1}{N}$] 1

Problem 2, 25 points (ece145A), 40 points (ece218A)
 2-port parameters and Transistor models

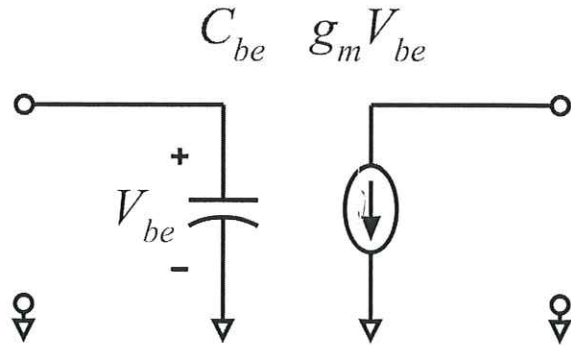Part a, 10 points

For the network at the right, give numerical values for the four S-parameters. Assume that the reference Z_0 is 50 Ohms. The signal frequency is 10GHz, $g_m=1$ mS, and $C_{be}=1$ fF.



$$S_{11} = \frac{Z_{in}/Z_0 - 1}{Z_{in}/Z_0 + 1} \Big|_{Z_L=Z_0}$$

$$= \frac{1/j\omega C Z_0 - 1}{1/j\omega C Z_0 + 1}$$


$$Z_{in}|_{Z_L=Z_0} = 1/j\omega C$$

$$= \frac{1 - j\omega C Z_0}{1 + j\omega C Z_0} = \frac{(1 - j\omega C Z_0)^2}{(1 + \omega^2 C^2 Z_0^2)}$$

by inspection, $|S_{11}| = 1$

and $\angle S_{11} = 2 \cdot (-1) \cdot \arctan(\omega C Z_0)$
 $= -2 \cdot (89.8^\circ) = -179.6^\circ$

$S_{22} = 1, S_{12} = 0$

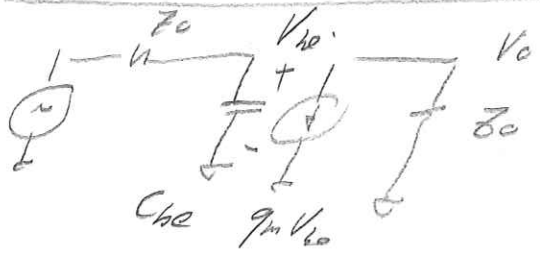

$$S_{21} = \frac{2V_o}{V_{gen}} \Big|_{Z_L=Z_0=Z_{gen}}$$

$$= \frac{-g_m Z_0 \cdot 2}{1 + j\omega C Z_0}$$


$$= \frac{-2g_m Z_0}{1 + \omega^2 C^2 Z_0^2} (1 - j\omega C Z_0)$$

(1) $S_{21} = \frac{-50 \Omega \cdot 1 \text{ mS} \cdot 2}{1 + 9.9 \cdot 10^{-6}} \cdot (1 - j 3.1 \cdot 10^{-2})$
 $= 0.01$

$$Y_0 = 1/50\Omega.$$

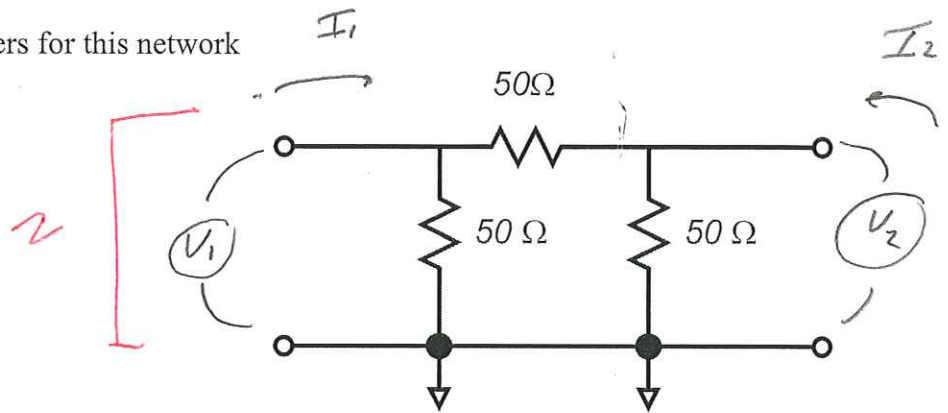Part b, 7 points

Compute the Y parameters for this network



$$2 \left[I_1 = V_1 (2Y_0) - V_2 Y_0. \right]$$


$$2 \left[\begin{aligned} Y_{11} &= 2Y_0 = 2/50\Omega = 40\text{mS} \\ Y_{12} &= -Y_0 = -20\text{mS}. \end{aligned} \right]$$

$$1 \left[\begin{aligned} \text{by Symmetry } Y_{22} &= Y_{11} = 40\text{mS} \\ Y_{21} &= Y_{12} = -20\text{mS}. \end{aligned} \right]$$

Part c, 7 points

Compute the ***Z*** parameters for this network

$$Z_0 = 50\Omega$$

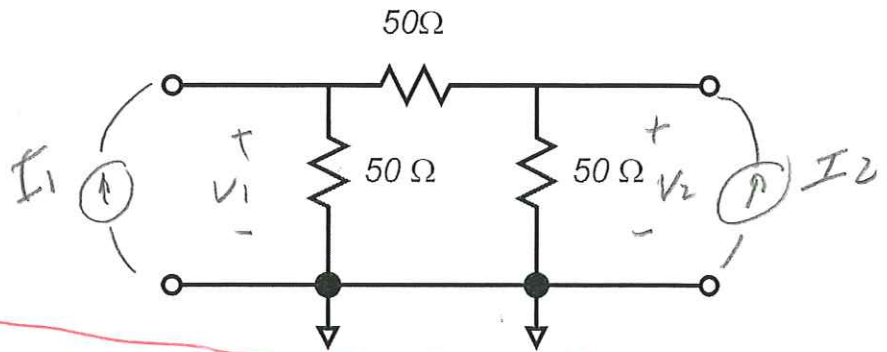

problem is matrix
invers

We know thd.

$$\begin{cases} I_1 = Y_{11} V_1 + Y_{12} V_2 \\ I_2 = Y_{21} V_1 + Y_{22} V_2 \end{cases}$$

So

$$Y_{22} I_1 = Y_{22} Y_{11} V_1 + Y_{22} Y_{12} V_2$$

$$Y_{12} I_2 = Y_{12} Y_{21} V_1 + Y_{12} Y_{22} V_2$$

subtract these:

$$Y_{22} I_1 - Y_{12} I_2 = (Y_{22} Y_{11} - Y_{12} Y_{21}) V_1$$

$$V_1 = \frac{Y_{22}}{\Delta Y} I_1 - \frac{Y_{12}}{\Delta Y} I_2$$

$\Delta Y = (Y_{11}^2) - (Y_{12}^2) = 4Y_0^2 - Y_0^2 = 3Y_0^2$

$$Z_{11} = \frac{Y_{22}}{\Delta Y} = \frac{2Y_0}{3Y_0^2} = \frac{2}{3} \frac{1}{Y_0} = \frac{2}{3} Z_0 = \frac{2}{3} \cdot 50\Omega = 33.33\Omega$$

$$Z_{12} = \frac{-Y_{12}}{\Delta Y} = \frac{+Y_0}{3Y_0^2} = \frac{1}{3} Z_0 = \frac{1}{3} \cdot 50\Omega = 16.6\Omega$$


by symmetry, $Z_{22} = Z_{11} = 33.3\Omega$

$$Z_{21} = Z_{12} = 16.6\Omega$$

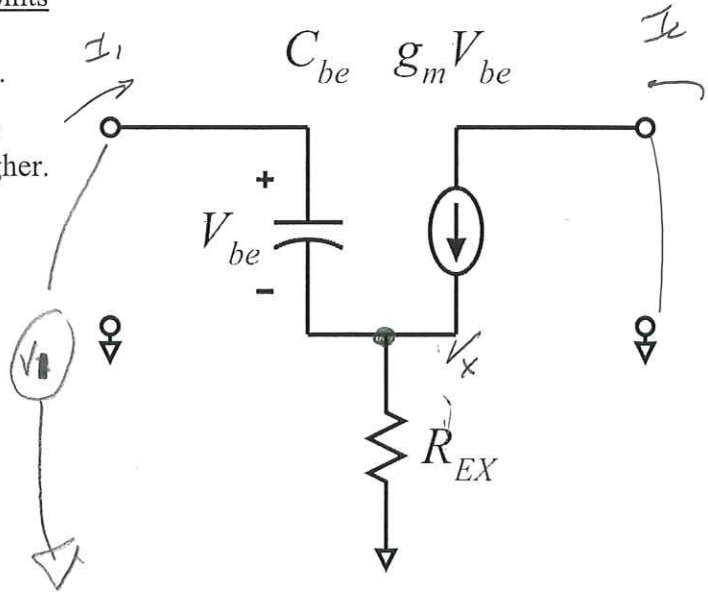Part d, ECE218A students only 15 points

For the network at the right, give an algebraic expressions for Y_{11} and Y_{21} . Please write as a Taylor series in $j\omega$, omitting terms of power $(j\omega)^3$ and higher.

This is an exercise in device model extraction from measured S/Y/Z parameters.



take V_2 as the only unknown:

$I_2 @ V_2 = 0$

spts for correct circuit solution

$$(V_x - V_1) j\omega C_{be} + V_x / R_{EX} + g_m (V_x - V_1) = 0$$

$$V_x (g_m + 1/R_{EX} + j\omega C_{be}) = V_1 (g_m + j\omega C_{be})$$

$$V_x = V_1 \frac{g_m + j\omega C_{be}}{g_m + 1/R_{EX} + j\omega C_{be}}$$

$$(V_1 - V_x) = \frac{1/R_{EX}}{g_m + 1/R_{EX} + j\omega C_{be}} \cdot V_1$$

$$I_1 = j\omega C_{be} (V_1 - V_x) = \frac{j\omega C_{be} / R_{EX}}{g_m + 1/R_{EX} + j\omega C_{be}} \cdot V_1$$

5pts

$$\frac{I_1}{v_1} = Y_{11} = \frac{j\omega C_{be}/R_{ex}}{g_m + 1/R_{ex} + j\omega C_{be}}$$

$$= j\omega \left(\frac{C_{be}}{1 + g_m R_{ex}} \right) \frac{1}{1 + j\omega \frac{C_{be}}{1 + g_m R_{ex}}}$$

but

$$\begin{aligned} \frac{1}{1 + j\epsilon} &= \frac{1}{1 + j\epsilon} \frac{1 - j\epsilon}{1 - j\epsilon} = \frac{1 - j\epsilon}{1 + \epsilon^2} \\ &= (1 - j\epsilon)(1 - \epsilon^2 + O(\epsilon^4)) \\ &= 1 - j\epsilon - \epsilon^2 + j\epsilon^3 + O(\epsilon^4) \\ &= 1 - j\epsilon - \epsilon^2 + O(j\epsilon^3) \end{aligned}$$

so

$$Y_{11} = j\omega \frac{C_{be}}{1 + g_m R_{ex}} \left[\frac{1 - j\omega C_{be}}{1 + g_m R_{ex}} - \frac{\omega^2 C_{be}^2}{(1 + g_m R_{ex})^2} + O(\omega^3) \right]$$

$$Y_{11} = \frac{j\omega C_{be}}{1 + g_m R_{ex}} + \frac{\omega^2 C_{be}^2}{(1 + g_m R_{ex})^2} + O(j\omega^3)$$

* we can see that this is $C_{be}/(1 + g_m R_{ex})$ in series with R_{ex}

$$5 \quad Y_2 = I_1 \cdot \frac{g_m}{j\omega C_{be}}$$

$$\text{So } Y_{21} = Y_{11} = \frac{g_m}{j\omega C_{be}}$$

$$Y_{21} = \frac{g_m}{j\omega C_{be}} \left[\frac{j\omega C_{be}}{1 + g_m R_{ex}} \right] \left[1 - \frac{j\omega C_{be}}{1 + g_m R_{ex}} - \frac{\omega^2 C_{be}^2}{(1 + g_m R_{ex})^2} + O(\omega^3) \right]$$

$$Y_{21} = \frac{g_m}{1 + g_m R_{ex}} \left[1 - \frac{j\omega C_{be}}{1 + g_m R_{ex}} - \frac{\omega^2 C_{be}^2}{(1 + g_m R_{ex})^2} + O(\omega^3) \right]$$

spls for Y_{21}

Problem 3, 15 points


Available source power relationships, lumped/distributed relationships.

Part a, 7.5 points

V_s is 0.1V RMS at 2GHz

R_s is 10 Ohms, L_s is 1nH.

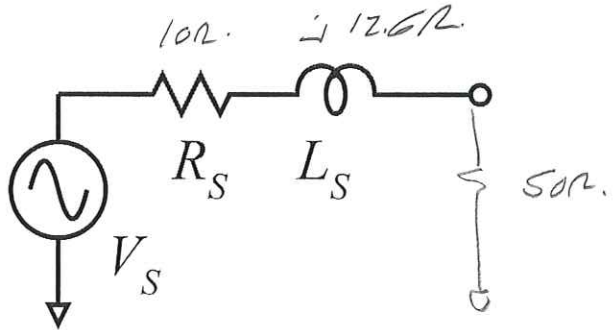At 2GHz, what power would be delivered into a 50 Ohm load? What is the available signal power?



$$1 \quad [X_L = \omega L = 2\pi f \cdot L = 12.57\Omega]$$

4.5

$$V_L = 0.1V \cdot \frac{50\Omega}{60 + j12.6\Omega} \Rightarrow \|V_L\| = 0.1V \cdot \frac{50\Omega}{\|60 + j12.6\|}$$

$$\|V_L\| = 0.1V \cdot \frac{50\Omega}{\sqrt{60^2 + 12.6^2}} = 0.1V \cdot 0.8155 = 0.08155V$$


$$P_L = \frac{\|V_L\|^2}{50\Omega} = 0.133\mu W \quad \text{into } 50\Omega$$

2

$$P_{avg} = \frac{(0.1V)^2}{4(10\Omega)} = 0.25\mu W$$

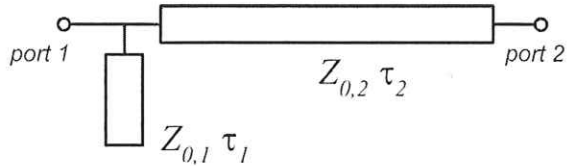Part b, 7.5 points

In the network to the right, $Z_{o2}=100 \text{ Ohm}$,
 $Z_{o1}=25 \text{ Ohms}$, $\tau_2=50 \text{ ps}$, $\tau_1=50 \text{ ps}$.




Representing line #2 as a pi-section and line #1 as a T-section, give an approximate lumped equivalent circuit model, with element values, for the network.

Approximately what would be the highest frequency at which the lumped network might reasonably approximate the distributed network (rough answer only)?

Line 2:

$$L = \tau_2 Z_{o2} = 50 \text{ ps} \cdot 100 \Omega = 5000 \text{ pH}$$


$$C = \tau_2 / Z_{o2} = 50 \text{ ps} / 100 \Omega = 0.5 \text{ pF}$$

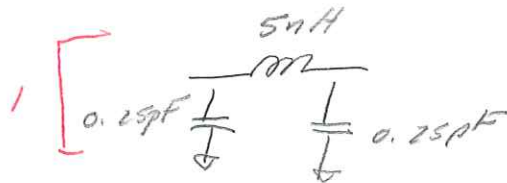


Line 1:

$$L = \tau_1 Z_{o1} = 50 \text{ ps} \cdot 25 \Omega = 1250 \text{ pH} = 1.25 \text{ nH}$$
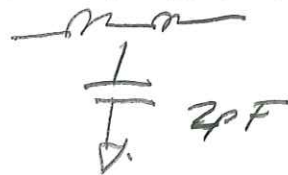
$$C = \tau_1 / Z_{o1} = 50 \text{ ps} / 25 \Omega = 2 \text{ pF}$$



Combined network:

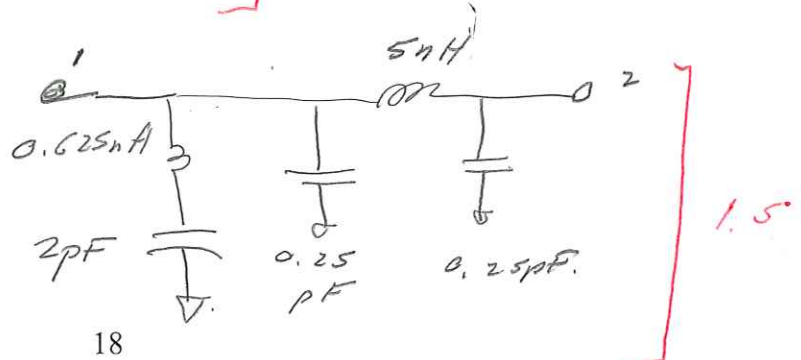

T and π equivalent crats are approximate
for any ratio of l to λ . The approximations
become extremely poor for $l > \lambda/4$.


$$l = \lambda/4 \text{ corresponds to } f = 1/4\lambda$$

$$\textcircled{1} \quad f = 1/4\lambda = \frac{1}{4 \text{ (sec)}} = 5 \text{ c/s}$$

$\textcircled{1}$ 5 c/s would be the upper useful

frequency of this approximate model.

For even rough approximation

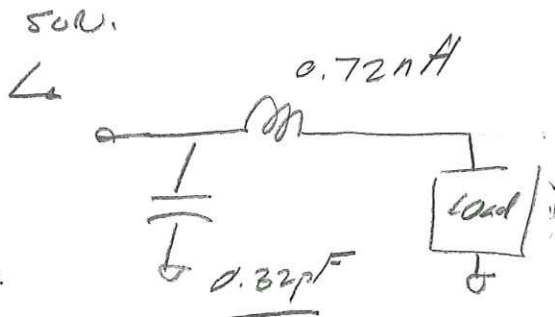

Problem 4, 15 points
Impedance-matching exercise.

At 10GHz signal frequency, an antenna has an input impedance of $25-j20$ Ohms. Design a matching network, using a series inductor and a shunt capacitor, which matches this impedance to 50 Ohms at 10GHz.

Give all element values. Use the full impedance-admittance chart which has been provided to you.

2 [Normalized $Z_L = \frac{25 - j20}{50} = 0.5 - j0.4$

2 [We then move to point "x" on the Smith chart
at point x, $Y = 0.5 + j0.5$

2 [So, change in $Y = (0.5 + j0.5) - (0.5 - j0.4) = j0.9$
change in $\Delta Z = j0.9 \cdot 50 \Omega = j45 \Omega$.

2 [This is a series inductor $\Delta Z = j45 \Omega = j\omega L$
 $\Rightarrow L = 45 \Omega / 2\pi f = 45 \Omega / 2\pi(10 \text{ GHz})$
 $= 0.716 \text{ nH}$.

2 [We then move to point "y"; $Y = 1 + j0$, $Y = 1 + j0$.

2
$$\left. \begin{aligned} Y_y &= 1 + j0 \\ Y_x &= 1 - j1 \end{aligned} \right\} \Delta Y = (1 + j0) - (1 - j1) = j1$$


This is a shunt capacitor $\Delta Y = \Delta Y / Z_0 = \frac{j1}{50 \Omega} = j20 \text{ mS}$

3.
$$\Rightarrow C = \frac{20 \text{ mS}}{2\pi f} = \frac{20 \text{ mS}}{2\pi(10 \text{ GHz})} = 0.318 \text{ pF}$$


NAME	TITLE <i>problem 4.</i>	DWG. NO.
SMITH CHART FORM ZY-01-N	Microwave Circuit Design - EE523 - Fall 2000	DATE

NORMALIZED IMPEDANCE AND ADMITTANCE COORDINATES

part "x"
part "y"

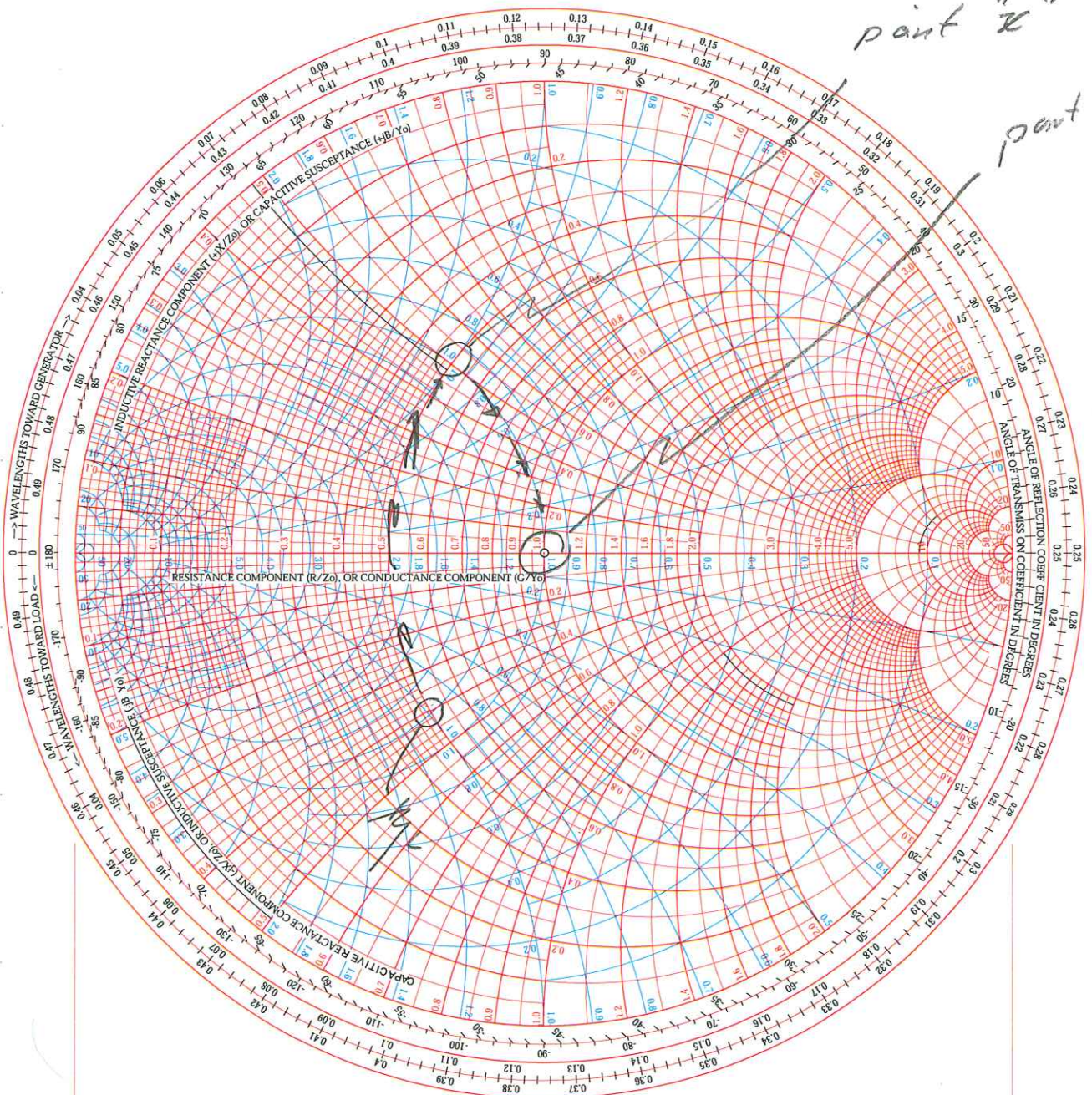


RADIALLY SCALED PARAMETERS

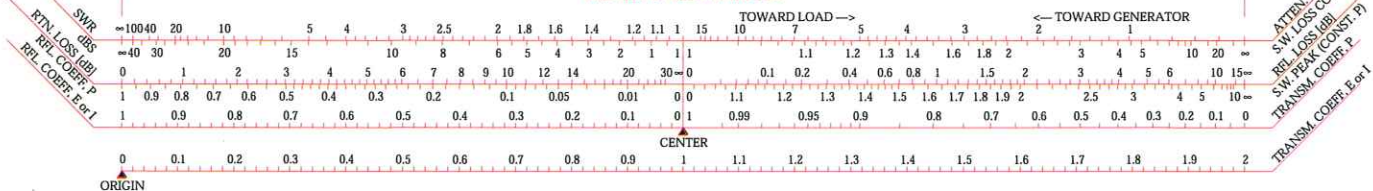


ORIGIN

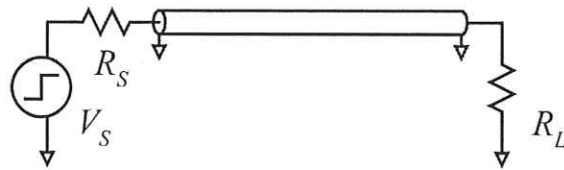Part b, 5 points


Using the parameters from part a, if we drive the cable with a step-function and with $R_s = R_L = 1 \text{ Ohm}$, what will be, approximately, the 10%-90% risetime of the voltage waveform at the load?



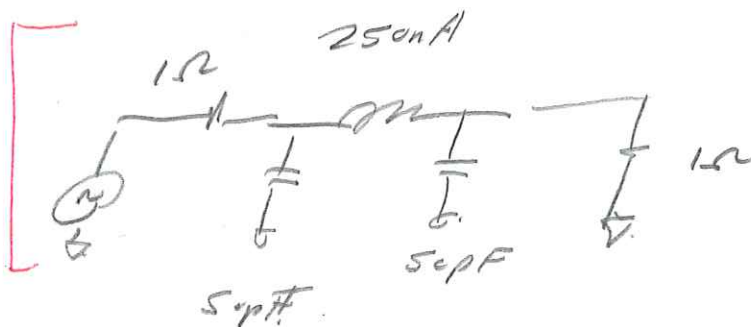with $R_s = R_L \rightarrow Z_0$
 Let's treat the line as a lumped approx. mode
 use a π section:



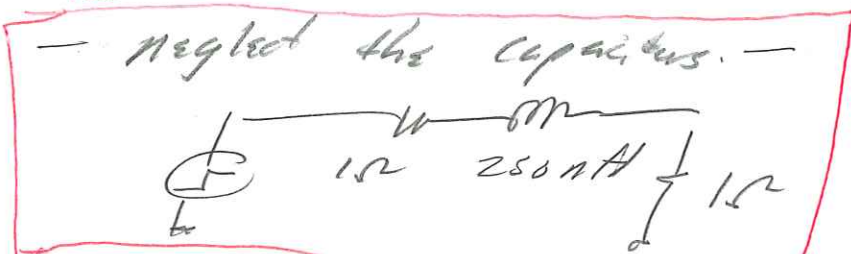but the RC time constants are $R \cdot C = 1 \Omega \cdot 5 \text{ pF} = 5 \text{ pS}$,
 while the L/R time constants are $L/R = \frac{250 \text{ nH}}{2 \Omega} = 125 \text{ nS}$.
 so the RC time constants are negligible \rightarrow




$$L/R = 125 \text{ nS} \Rightarrow \tau_{10-90} = 2.2 \tau$$

$$= 2.2 (250 \text{ nS})$$


$$= \underline{\underline{550 \text{ nS}}}$$

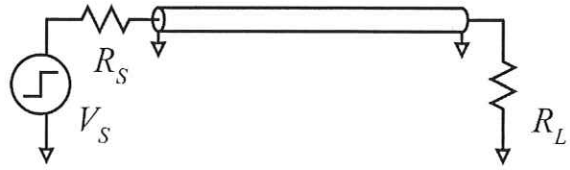Part c, 5 points

Using the parameters from part a, if we drive the cable with a step-function and with $R_s = R_L = 10 \text{ k}\Omega$, what will be, approximately, the 10%-90% risetime of the voltage waveform at the load?



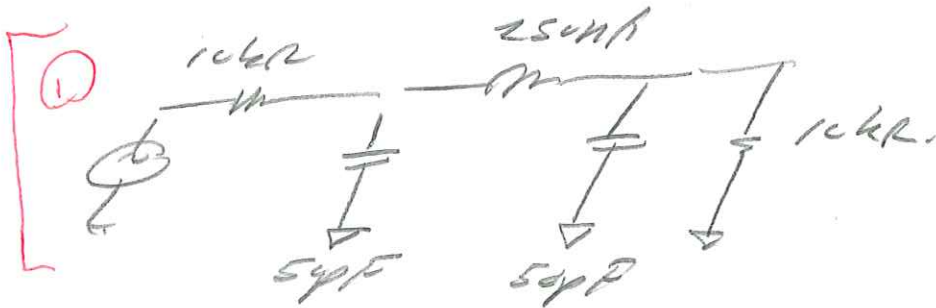
① $R_s = R_L \gg Z_0$
 let's treat the line as a lumped approximation
 use a π section



Now the $\tau_{rc} \approx 50 \text{ pF} \cdot 10 \text{ k}\Omega = 500 \text{ ns}$.

② Now the $\tau_{LR} = \frac{250 \text{ m}\Omega}{20 \text{ k}\Omega} = 12.5 \text{ ps}$

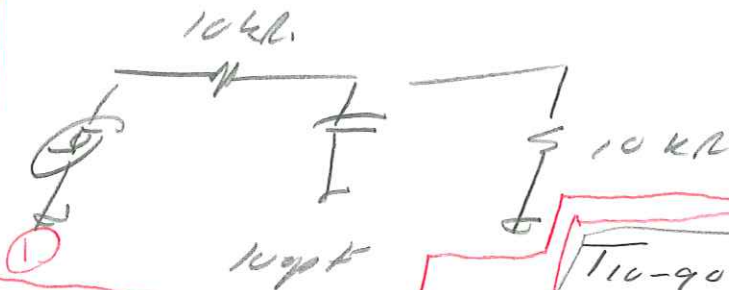\Rightarrow inductive effects are negligible.



$$\tau_{rc} = 10 \text{ pF} \cdot 5 \text{ k}\Omega = 500 \text{ ns}$$

$$\tau_{10-90} = 2.2 \tau = 1.1 \mu\text{s}$$

Problem 5, 15 points (ece145A), 20 points (218A)*Transmission-line properties.*Part a, 5 points

Coaxial cable uses a signal conductor of round cross-section with an insulating dielectric and a ground conductor both wrapped around it. The characteristic impedance is

$$Z_0 = (1/2\pi)(\mu_0 / \epsilon_r \epsilon_0)^{1/2} \ln(D/d)$$

where $(\mu_0 / \epsilon_0)^{1/2} = 377\Omega$, ϵ_r is the insulator dielectric constant, and d and D are the diameters of the inner and outer conductors.

The velocity is $v = c / \epsilon_r^{1/2}$, where c is the speed of light.



Suppose that the dielectric is Polyethylene, which has $\epsilon_r = 2.25$, and that the inner conductor is 1mm diameter.

✓ For 50 Ohms characteristic impedance, what must be the outer conductor diameter?

✓ What is the wave velocity on the transmission line?

If the cable is 1 meter long, what is the total line capacitance and inductance?

$$50\Omega = \frac{377\Omega}{2\pi \epsilon_r^{1/2}} \ln\left(\frac{D}{d}\right)$$

$$\ln\left(\frac{D}{d}\right) = \frac{2\pi \cdot \epsilon_r^{1/2} \cdot 50\Omega}{377\Omega} = 1.25$$

$$\Rightarrow \frac{D}{d} = e^{1.25} = 3.50 \rightarrow D = 3.5 \cdot (1\text{mm}) = \underline{\underline{3.5\text{mm}}}$$


$$v = \frac{c}{\sqrt{\epsilon_r}} = \frac{3 \cdot 10^8 \text{ m/s}}{1.5} = 2 \cdot 10^8 \text{ m/s}$$

$$\ell = 1\text{m}; \quad \tau = \ell/v = 1\text{m} / 2 \cdot 10^8 \text{ m/s} = 5\text{ns}$$

$$C = \tau/Z_0 = \frac{5\text{ns}}{50\Omega} = 0.1\text{nF} = 100\text{pF}$$

$$L = \tau Z_0 = 5\text{ns} \cdot 50\Omega = 250\text{nH}$$

Part d, 15 points ECE 218 students only

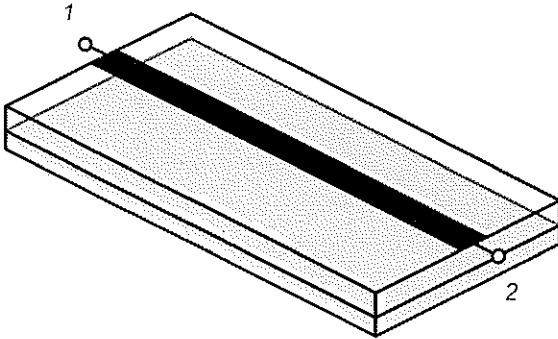

We will make a 50 Ohm microstrip line on commercial board material (like that used in the class) with a dielectric constant of 2.2.

The design frequency is 140GHz.

You are to design a 50 Ohm transmission-line. To approximately model the effect of fringing fields, assume that

$$Z_0 \cong (\mu_0 / \epsilon_r \epsilon_0)^{1/2} (H / (H + W))$$

where W is physical conductor width and H is the board thickness.

To adequately suppress coupling to dielectric slab modes, keep the board thickness less than or equal to the 1/4 of a wavelength *in the dielectric* at the design frequency.

To adequately suppress lateral transmission-line modes, keep the conductor width less than or equal to 1/4 of a wavelength *in the dielectric* at the design frequency.

The conductivity of (very pure) copper is 5.96×10^7 (1/Ohm/meter) at 20C.

-Determine the board thickness and the conductor width.

-Determine the skin effect loss, in dB/mm, at 140GHz.

(hint: the skin depth is $\delta = (2 / \omega \mu_0 \sigma)^{1/2}$, where $\mu_0 = 4\pi \cdot 10^{-7}$ H/m)

$$\sqrt{\epsilon_0} = \frac{377 \Omega}{\sqrt{\epsilon_r}} \cdot \frac{H}{H+W} = 50 \Omega, \quad \epsilon_r = 2.2.$$

$$\Rightarrow \frac{H}{H+W} = \frac{50 \Omega \cdot \sqrt{2.2}}{377 \Omega} = 0.197 \quad \frac{H+W}{H} = 5.08$$

$$\Rightarrow \boxed{W/H = 4.08}$$


We need $H \leq \lambda_d/4$, but also need $W \leq \lambda_d/4$.
 Since $H < W$, clearly we set $W = \lambda_d/4$

$$\lambda_d = \frac{c}{f \sqrt{\epsilon_r}} = \frac{3 \cdot 10^8 \text{ m/s}}{140 \text{ GHz} \cdot \sqrt{2.2}} = 1.44 \text{ mm}.$$

$$\Rightarrow \begin{cases} W = \lambda_d/4 = 1.44 \text{ mm}/4 = 361 \mu\text{m} \\ H = W/4.08 = 88 \mu\text{m} \end{cases}$$

$$\text{skin depth} = \delta = \sqrt{\frac{2}{\omega \mu_0 \sigma}} = \sqrt{\frac{2}{2\pi(140 \text{ GHz}) \cdot 4\pi \cdot 10^{-7} \text{ H/m} \cdot 6 \cdot 10^7 \frac{\text{A}}{\Omega}}}$$

$$= 0.174 \mu\text{m}.$$

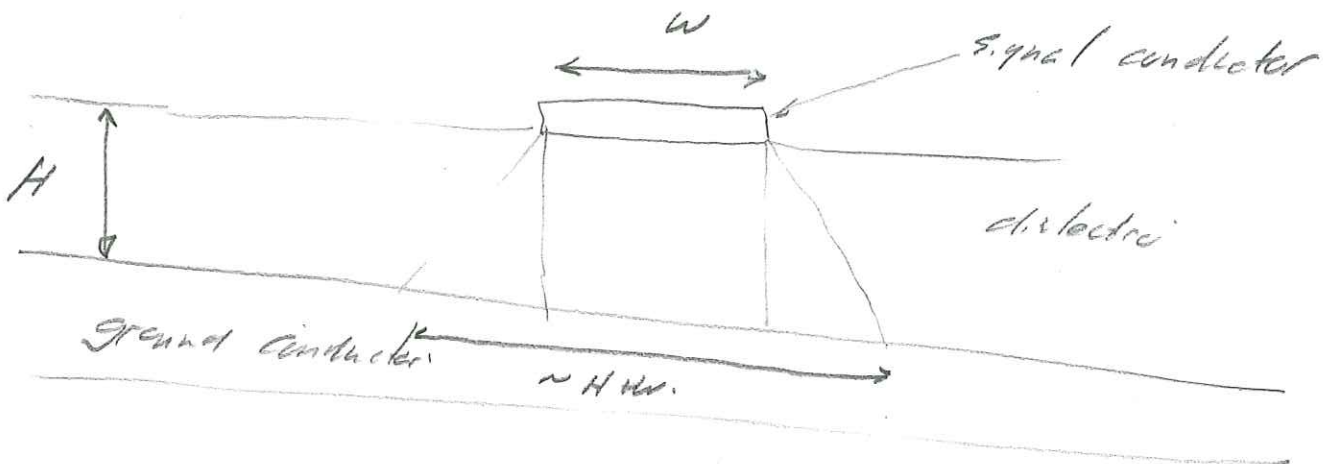

Now, the signal current is carried across the full conductor width w .

$$\Rightarrow \text{Signal conductor resistance per unit length} \\ = R_{\text{sig}} (\Omega/\text{m}) \approx \frac{1}{\sqrt{5} w} = 267 \Omega/\text{m}.$$

While the ground current is carried over an effective conductor width of $\sim (w+h)$

$$\Rightarrow \text{ground conductor resistance per unit length} \\ = R_{\text{ground}} (\Omega/\text{m}) \approx \frac{1}{\sqrt{5} (w+h)} = 215 \Omega/\text{mm}$$

Total resistance per unit length

$$R_{\text{tot}} (\Omega/\text{m}) \approx \frac{1}{\sqrt{5}} \left(\frac{1}{w} + \frac{1}{w+h} \right) = 482 \Omega/\text{mm}$$

waves decay in voltage as $e^{-\alpha z}$ where $\alpha = \frac{R_{\text{tot}}}{2Z_0}$

$$\alpha = \frac{R_{\text{tot}}}{2Z_0} = \frac{482 \Omega/\text{m}}{100 \Omega} = 4.82 \text{ m}^{-1}$$

In one meter, the signal has attenuated in voltage by

$$e^{-\alpha L} = e^{-4.82}$$

$$\text{In dB, this is dB loss} = 20 \cdot \log_{10} [e^{-4.82}] \\ = -41.9 \text{ dB}$$

\Rightarrow Loss is 41.9 dB/meter or 0.04 dB/mm.