

ECE ECE145A (undergrad) and ECE218A (graduate)

Mid-Term Exam. November 14, 2012

Do not open exam until instructed to.

Open notes, open books, etc

You have 1 hr and 15 minutes.

Use any and all reasonable approximations (5% accuracy is fine.), ***AFTER STATING THEM.***


Problem	Points Received	Points Possible
1		20
2a		20
2b		10
3a		10
3b		10
4a		5
4b		5
4c		5
5		15
total		100


Name: Solution

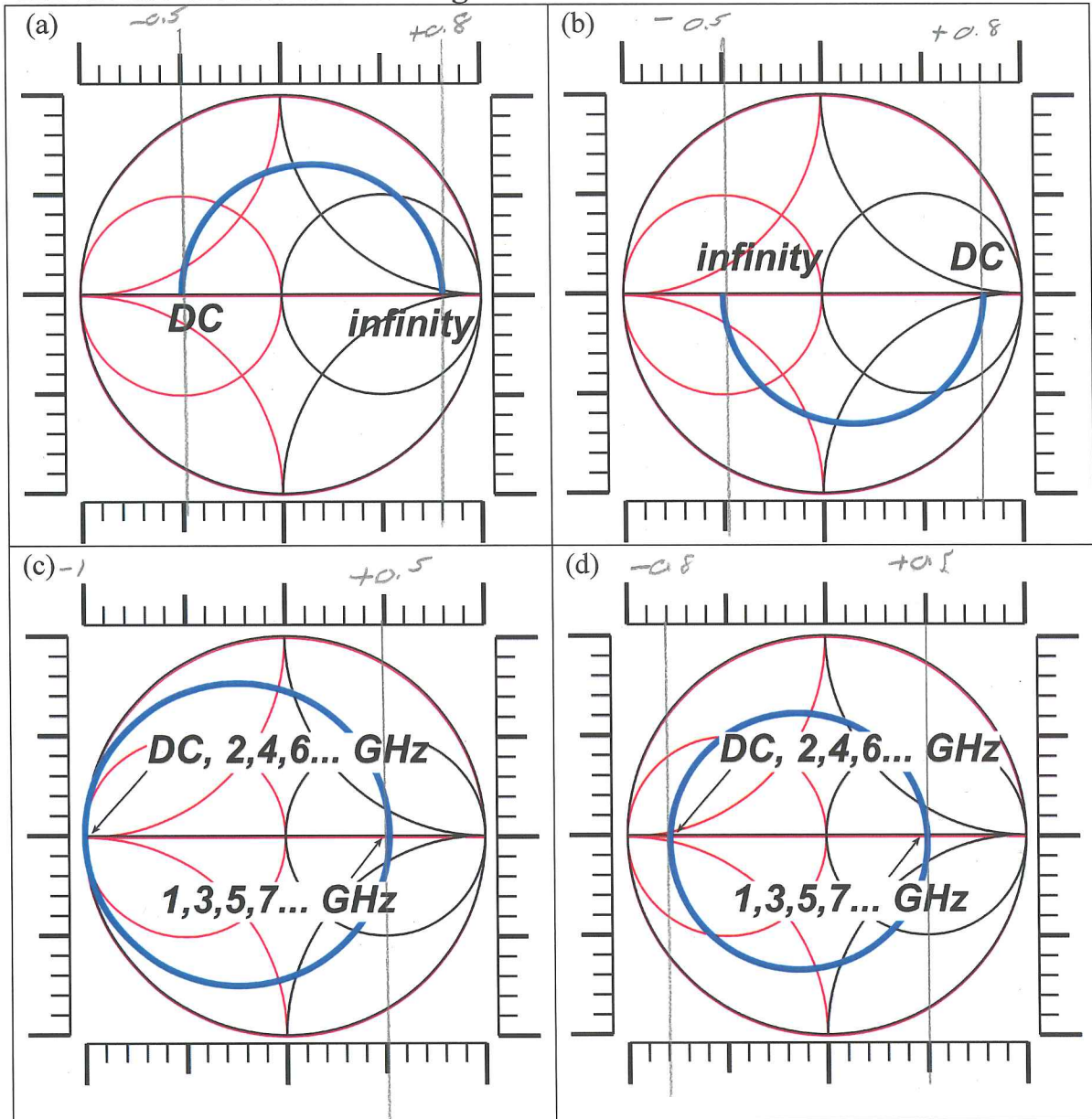Problem 1, 20 points

The Smith Chart and Frequency-Dependent Impedances.

HINT: use the scales on the figures to measure distances as needed.



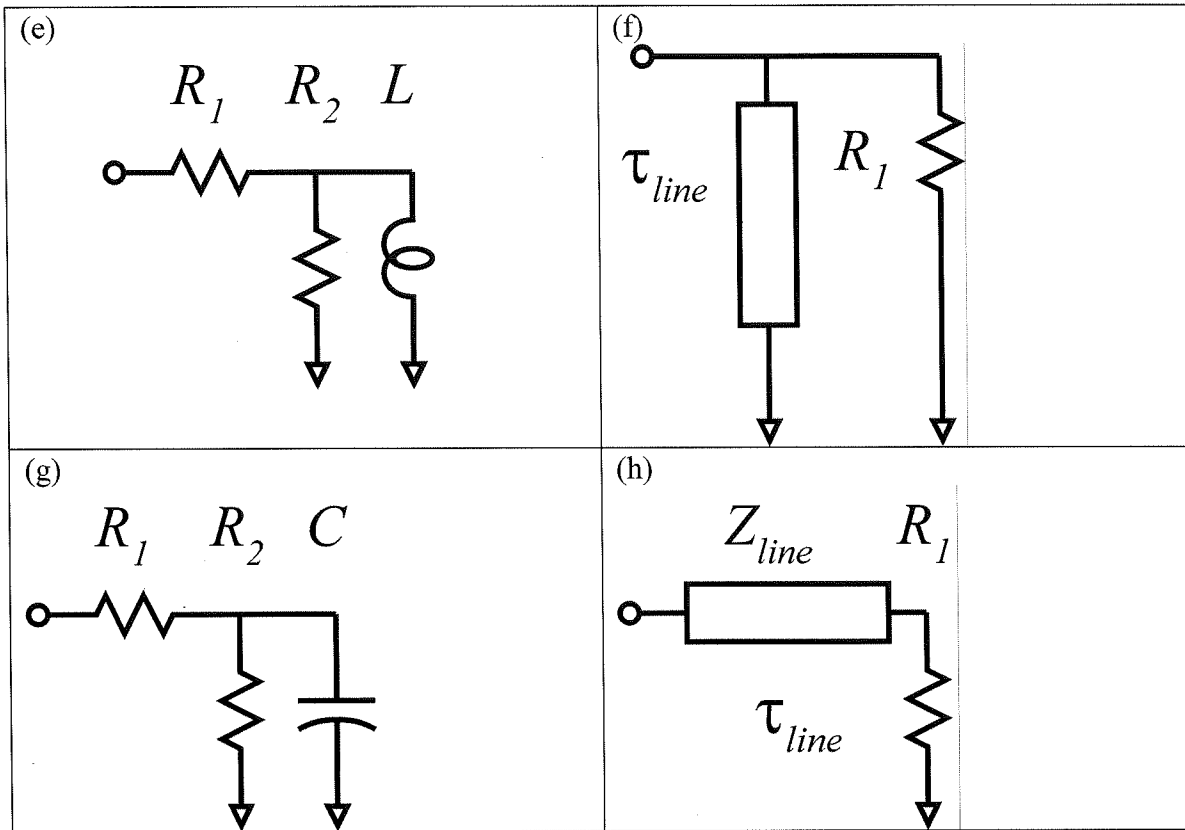


Match each Smith Chart with each circuit, and give all resistor values, and all transmission line delays and characteristic impedances. The charts all use 50 Ohm normalization:

- Smith chart (a). Circuit= E. Component values= $R_1 = 17\Omega, R_2 = 433.3\Omega$
- Smith chart (b). Circuit= B G. Component values= $R_2 = 433\Omega, R_1 = 17\Omega$
- Smith chart (c). Circuit= F. Component values= $R_1 = 150\Omega, \tau = 250\text{ps}$
- Smith chart (d). Circuit= H. Component values= $R_1 = 5.5\Omega, \tau = 250\text{ps}, Z_0 = 29\Omega$

Smith chart a

this is network (E)

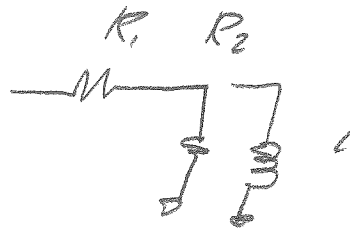


(2) at DC, $Z = R_1$ and $\frac{R}{Z_0} - 1 = \Gamma \rightarrow R_1 = Z_0 \frac{1 + \Gamma}{1 - \Gamma}$
 $= 50 \Omega \left(\frac{1 - 0.5}{1 + 0.5} \right) = 16.7 \Omega$

(2) at $\omega \rightarrow \infty$, $Z = R_1 + R_2 \rightarrow R_1 + R_2 = Z_0 \frac{1 + \Gamma}{1 - \Gamma} = 50 \Omega \frac{1 + 0.8}{1 - 0.8}$
 $R_1 + R_2 = 450 \Omega$
 $R_2 = 433.3 \Omega$

Smith chart B

this is network (G)

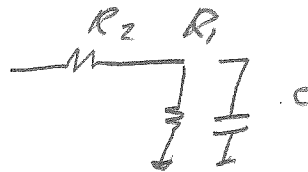

at DC $Z = R_1 + R_2 \rightarrow R_1 + R_2 = Z_0 \frac{1 + \Gamma}{1 - \Gamma} = 50 \Omega \frac{1.8}{0.2} = 450 \Omega$

at $\omega \rightarrow \infty$ $Z = R_2$
 $R_2 = Z_0 \frac{1 + \Gamma}{1 - \Gamma} = 50 \Omega \frac{1 - 0.5}{1 + 0.5} = 17 \Omega$
 $R_1 = 433 \Omega$


Smith chart (C) this is network (F)

$R_1 = Z_0 \frac{1 + \Gamma}{1 - \Gamma} = 50 \Omega \frac{1 + 1/2}{1 - 1/2} = 150 \Omega$

it is not possible to find the Z_0 of the line
 line is $\lambda/4$ @ 1 GHz , so Γ is λ @ 4 GHz ,
 so $T = 1/(4 \text{ GHz}) = 25 \text{ ps}$

Smith chart (h) this is network (h).

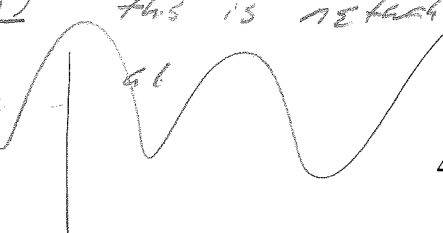at DC
 $R_1 = Z_0 \frac{1 + \Gamma}{1 - \Gamma} = 50 \Omega \frac{1 - 0.8}{1 + 0.8} = 5.55 \Omega$



Smith chart D

this is network(h)

at DC, $\Gamma = -0.8$

$$\begin{aligned} \text{at DC } R_1 &= Z_0 \frac{1 + \Gamma}{1 - \Gamma} \\ &= 50 \Omega \frac{1 - 0.8}{1 + 0.8} \\ &= 5.55 \Omega \end{aligned}$$

At 1 GHz, line is $\lambda/4$ long. so line is λ long @ 4 GHz

$$\rightarrow \Gamma = 250\%$$

At 1 GHz, the line input impedance is $Z_i = Z_0 \frac{1 + \Gamma}{1 - \Gamma} = \underline{\underline{150 \Omega}}$
this is the quarter-wave condition,


$$\begin{aligned} \text{so } Z_{\text{line}} &= \sqrt{R_1 Z_i} = \sqrt{5.55 \Omega \cdot 150 \Omega} \\ &= 28.9 \Omega \end{aligned}$$

Problem 2, 30 points

2-port parameters and Transistor models

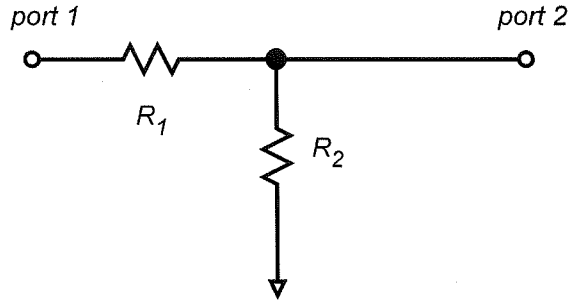Part a, 20 points

For the network at the right, give algebraic expressions for the four Z-parameters and for the four S-parameters.




Then using $R_1=25\text{ Ohms}$, $R_2=50\text{ Ohms}$, , give numerical values.

By inspection:

$$\mathbf{Z} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} R_1 + R_2 & R_2 \\ R_2 & R_2 \end{bmatrix} \quad (3)$$


$$= \begin{bmatrix} 75\Omega & 50\Omega \\ 50\Omega & 50\Omega \end{bmatrix} \quad (1)$$

S_{11} :

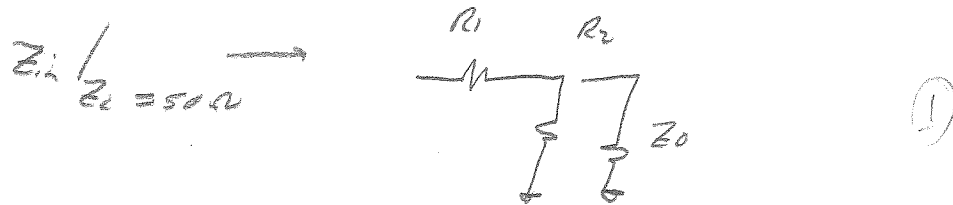

$$= R_2 \parallel Z_0 + R_1 = 50\Omega \parallel 50\Omega + 25\Omega = 50\Omega \quad (1)$$

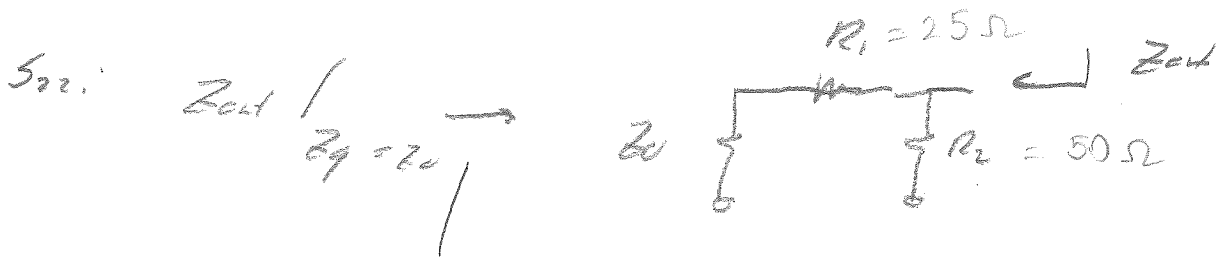
$$S_{11} = \frac{\frac{R_2 \parallel Z_0 + R_1}{Z_0} - 1}{\frac{R_2 \parallel Z_0 + R_1}{Z_0} + 1} = \frac{1 - 1}{1 + 1} = 0 \quad (2) + (1)$$



$$= R_2 \parallel (R_1 + Z_0) = 50 \Omega \parallel 75 \Omega = 30 \Omega$$

$$S_{22} = \frac{R_2 \parallel (R_1 + Z_0)}{Z_0} - 1 = \frac{0.6 - 1}{0.6 + 1} = -0.25$$

(1) + (4)

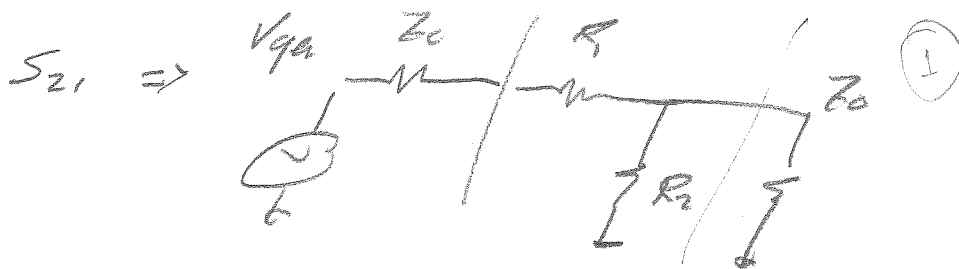

$$S_{21} = 2 \frac{V_o}{V_{in}} \Big|_{Z_L = Z_0 = Z_{in}} = \frac{(Z_0 \parallel R_2) \cdot 2}{(Z_0 \parallel R_2) + R_1 + Z_0}$$

$S_{12} \Rightarrow$

$$= \frac{(25 \Omega) \cdot 2}{25 \Omega + 25 \Omega + 50 \Omega} = 1/2$$

(2)

$$S_{12} = 2 \left(\frac{Z_0}{Z_0 + R_1} \right) \cdot \frac{[(Z_0 + R_1) \parallel R_2]}{(Z_0 + R_1) \parallel R_2 + Z_0}$$


(1)

$$= 2 \left(\frac{50 \Omega}{50 \Omega + 25 \Omega} \right) \frac{(50 \Omega + 25 \Omega) \parallel 50 \Omega}{(50 \Omega + 25 \Omega) \parallel 50 \Omega + 50 \Omega} = 1/2 \quad (\Rightarrow S_{12} = S_{21} \text{ as is required.})$$

(2)

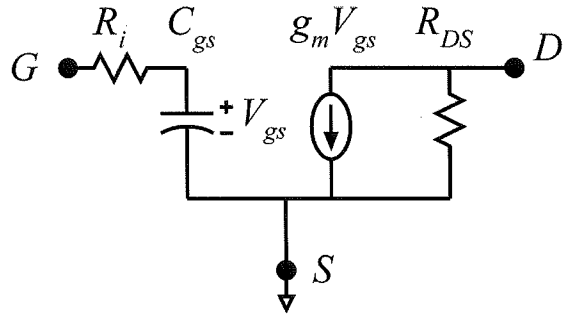Part b, 10 points

To the right is the equivalent circuit of a FET.



First give algebraic expressions for S11 and S21 as a function of frequency.

Then set the transconductance to 100 mS, Ri=5 Ohms, Cgs=50 fF, RDS=infinity, and calculate S21 at 10GHz.

$$S_{11}: \left. \begin{aligned} Z_{in} &= R_i + 1/j\omega C_{gs} \\ Z_{in}/Z_0 &= R_i/Z_0 + 1/j\omega C_{gs} Z_0 \end{aligned} \right\} \textcircled{2}$$

$$\rightarrow S_{11} = \frac{(R_i/Z_0 + 1/j\omega C_{gs} Z_0) - 1}{(R_i/Z_0 + 1/j\omega C_{gs} Z_0) + 1} = \dots \textcircled{2}$$

$$S_{21} = \frac{2V_o}{V_{gs} Z_0 + Z_{in}} = \frac{2(1/j\omega C_{gs}) - g_m (R_{DS}/Z_0)}{1/j\omega C_{gs} + R_i + Z_0} \textcircled{2}$$

$$= \frac{-2g_m (R_{DS}/Z_0)}{1 + j\omega C_{gs} (R_i + Z_0)} = \frac{-2(100\text{mS})(50\Omega)}{1 + j 2\pi f (5\Omega + 50\Omega) 50\text{fF}}$$

$$= \frac{-10}{1 + j 0.173} = \frac{-10(1 - j0.173)}{1 + (0.173)^2}$$

$$S_{21} = -9.71 + j1.68 \textcircled{2}$$

Problem 3, 20 points*Elementary impedance matching network design.*

You are going to design an impedance-matching network to match a 20 Ohm resistor to a 50 Ohm generator at a frequency of 2 GHz.

Part (a), 10 points.

Using the impedance-admittance charts that have been passed out, design a lumped-element matching network. Use a series inductor and a shunt capacitor. Give the circuit diagram and the element values.

Point "A" $20\Omega \rightarrow \frac{Z_L}{Z_0} = \frac{20\Omega}{50\Omega} = 0.4 = \frac{1}{2.5} \quad (1)$

Point "B"

$$\frac{1}{\Gamma_B} = 0.4 + j0.5$$

added normalized reactance.

$$jX = j0.5 \Rightarrow jX = j(0.5)50\Omega = j25\Omega$$

$$\Rightarrow L = \frac{25\Omega}{2\pi(2\text{GHz})} = 1.99\text{ nH} \quad (2) + (4/2)$$

$$y_B = 1.0 - j1.2$$

Point "C"

$$y_C = 1.0 - j0$$


$$\Rightarrow jB = j1.2 \Rightarrow jB = j \frac{1.2}{50\Omega} = j0.024\text{ S} \quad (2) + (4/2)$$

$$jB = j\omega C \rightarrow C = \frac{1.2}{50\Omega(2\pi f)} = 1.91\text{ pF}$$



NAME	TITLE <i>Problem 3(a)</i>	DWG. NO.
SMITH CHART FORM ZY-01-N	Microwave Circuit Design - EE523 - Fall 2000	DATE

NORMALIZED IMPEDANCE AND ADMITTANCE COORDINATES

50 ohm normalization

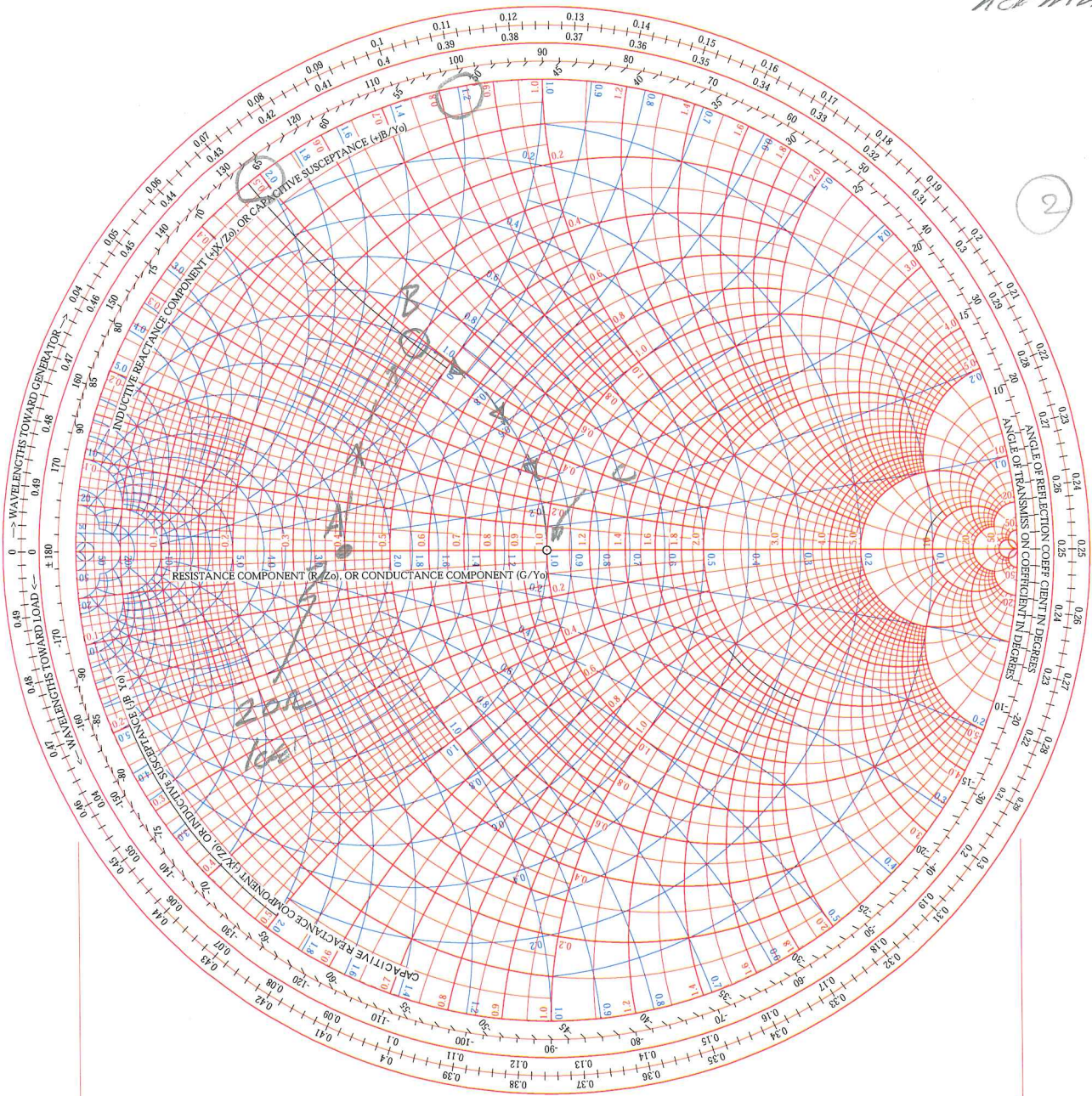

RADIALLY SCALED PARAMETERS

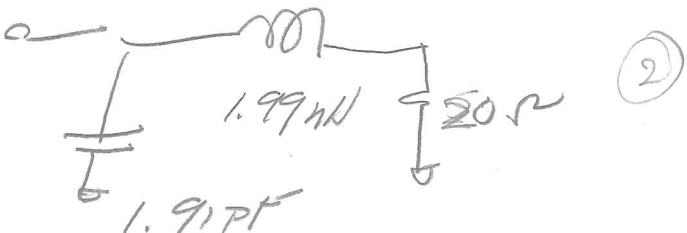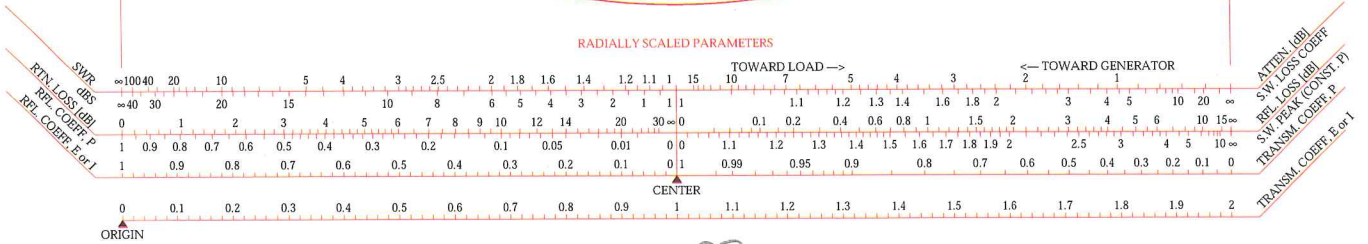

50

Part (b), 10 points.

Lumped inductors are not available to you. **Using the impedance-admittance charts that have been passed out**, design a second matching network using a series transmission-line of 100 Ohms characteristic impedance and a shunt capacitor. The propagation velocity on the transmission line is $2/3$ the speed of light. Give the circuit diagram and the element values (capacitance, length of line).

from smith chart: $A \rightarrow B$

line of 63° length \Rightarrow

$$\text{Length} = \frac{63}{360} \cdot \frac{(2/3 \cdot c)/2}{2c(10^9)/1/2} = \underline{18.5 \text{ mm}}$$

point B

$$y = 1 - j1$$

"point C"

$$y = 1 + j0$$



$$jB = -j1 \Rightarrow jB = j \frac{1}{50 \Omega} = j\omega C$$

$$\Rightarrow C = \frac{1}{\omega 50 \Omega} = \frac{1}{2\pi f 50 \Omega} = 1.6 \text{ pF}$$

\uparrow
200 MHz

NAME	TITLE <i>problem 3(s)</i>	DWG. NO.
SMITH CHART FORM ZY-01-N	Microwave Circuit Design - EE523 - Fall 2000	DATE

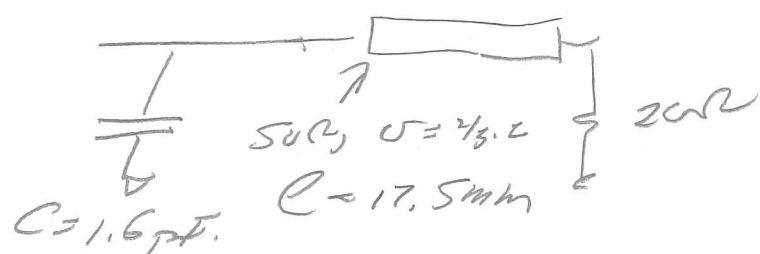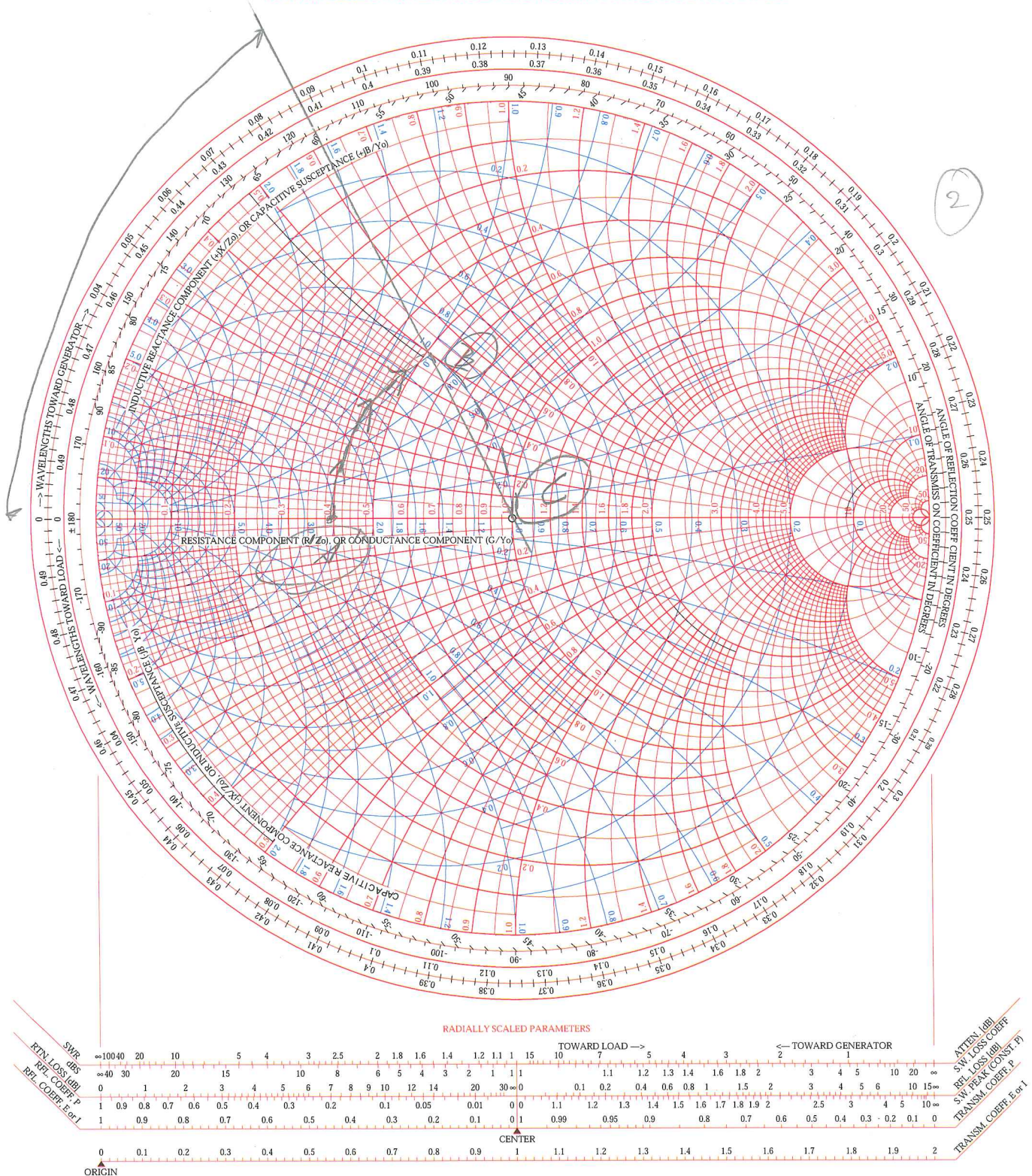NORMALIZED IMPEDANCE AND ADMITTANCE COORDINATES



Problem 4, 15 points

Transmission-lines and lumped elements

Part a: 5 points

A transmission-line has propagation velocity of $2/3$ the speed of light. Its characteristic impedance is 75 Ohms. It is one meter long. Find the total inductance and total capacitance in this cable.

①

$$L = Z_0 \tau = Z_0 \cdot l/v$$
$$= 75 \Omega \cdot \frac{1 \text{ m}}{2 \cdot 10^8 \text{ m/s}} = 75 \Omega \cdot 5 \text{ ns} = \underline{\underline{0.375 \mu\text{H}}}$$

②


$$C = \tau/Z_0 = 5 \text{ ns}/75 \Omega = 66.6 \text{ pF}$$

②

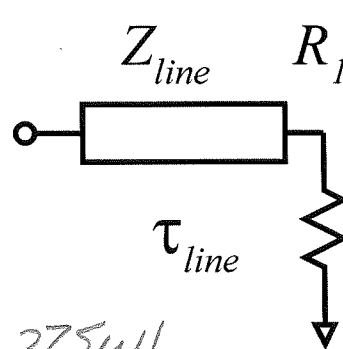
Part b: 5 points

The above cable is loaded in a resistor $R_1 = 10$ kOhm. Find the input impedance of the cable at a frequency of 1 MHz.

Critical hint: use any and all reasonable approximations. Do not carry terms in the calculation which are negligible.



$$L = 0.375 \mu\text{H}$$

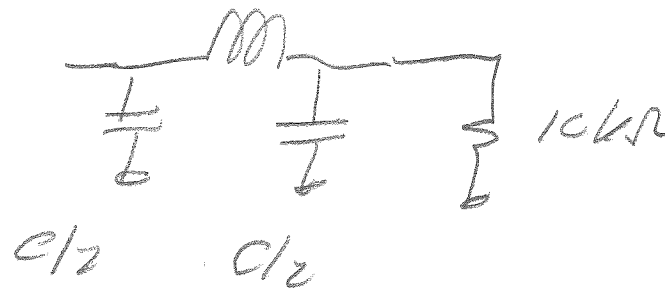

$$C = 67 \text{ pF}$$

$$j\omega L = j2.35 \Omega \ll 10 \text{ k}\Omega \rightarrow j\omega L \text{ is negligible}$$

$$1/j\omega C = -j2.37 \text{ k}\Omega$$

$$Z \approx 10 \text{ k}\Omega \parallel -j2.37 \text{ k}\Omega = \frac{-j23.7 \text{ k}\Omega}{(10 - j23.7)}$$


$$= \frac{56.169 - j237 \text{ k}\Omega}{10^2 + (2.37)^2}$$

$$Z_{in} = 531.81 - j2244 \Omega$$

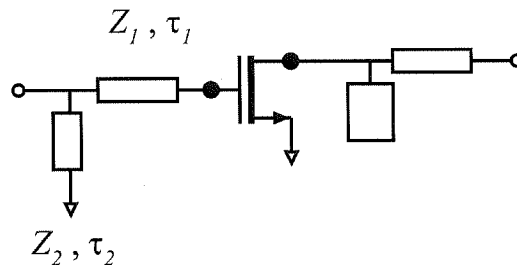Part b: 5 points

You are now going to design a physical matching network for the input to a transistor amplifier. The design frequency is 10 GHz.

The series line #1 must have 100-Ohm characteristic impedance and is $\frac{1}{8}$ (guide) wavelength long at the design frequency.



The shunt line #2 must have 50 Ohm characteristic impedance and is 0.1 (guide) wavelength long at the design frequency.

The lines are microstrip lines. The substrate is 75 micrometer thick and has a dielectric constant of 12. Use the approximations $v = c/\sqrt{\epsilon_r}$ and

$Z_0 = 377\Omega \cdot (\epsilon_r)^{-1/2} \cdot H/(H+W)$, where H is the substrate thickness and W the conductor width.

Compute the length and width of lines 1 and line 2

- line 1 length (m): 1.0825 mm
- line 1 width (m): 33.2303 μm
- line 2 length (m): 0.866 mm
- line 2 width (m): 28.245 μm

Series line (width) (1)

$$Z_0 = \frac{377}{\sqrt{\epsilon_r}} \cdot \frac{H}{H+W} = 75 \Omega$$

$$\frac{H}{H+W} = 0.62915$$

$$0.31085 \cdot H = 0.62915 \cdot W$$

$$W = 33.2303 \mu\text{m}$$

$$W = 33.2303 \mu\text{m}$$

Shunt line (width) (2)

$$Z_0 = \frac{377}{\sqrt{\epsilon_r}} \cdot \frac{H}{H+W} = 50$$

$$\frac{H}{H+W} = 0.45943$$

$$0.54057 \cdot H = 0.45943 \cdot W$$

$$W = 28.245 \mu\text{m}$$

$$W = 28.245 \mu\text{m}$$

Series line (length) (1)

$$v = \frac{c}{\sqrt{\epsilon_r}} = 86.6025 \times 10^5 \text{ m/s}$$

$$\lambda_d f = v$$

$$\lambda_d = 2.66 \text{ mm}$$


$$\begin{aligned} \text{length of series line} &= \frac{1}{2} \cdot \lambda_d \\ &= 1.0825 \text{ mm} \end{aligned}$$

Shunt line (length) (1)


$$\begin{aligned} \text{length of shunt line} &= 0.1 \lambda_d \\ &= 0.266 \text{ mm} \end{aligned}$$

Please make a well-scaled sketch (top view) the matching network below with dimensions indicated.

①

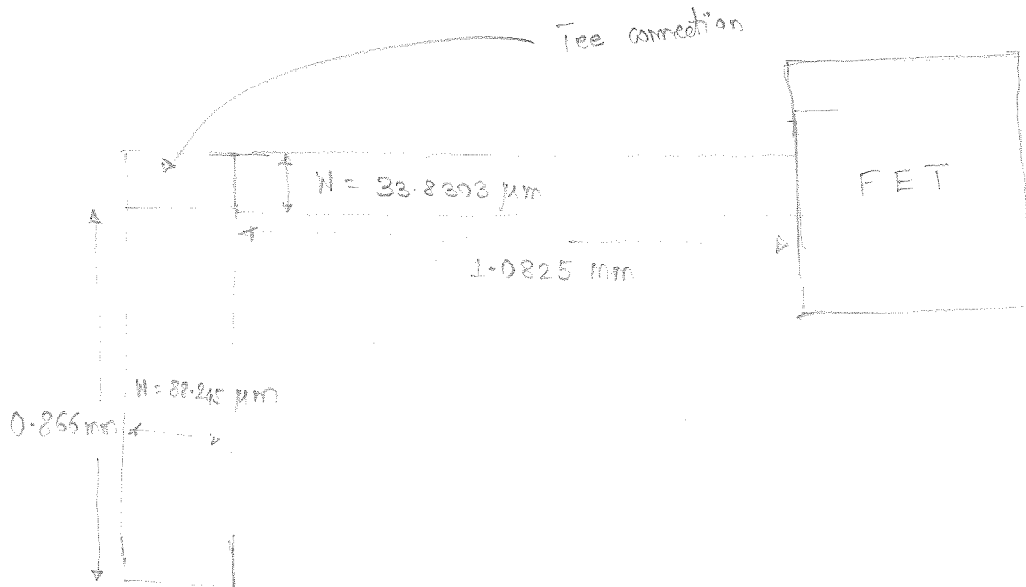

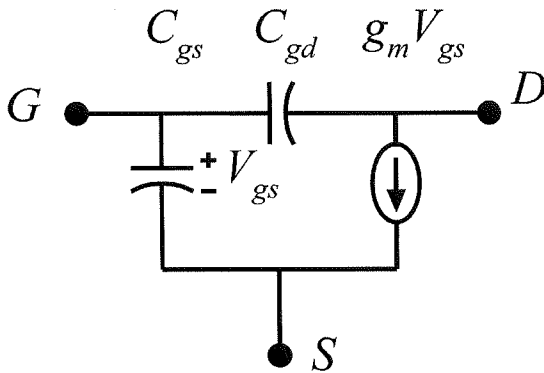Problem 5, 15 points
resistive feedback amplifiers



A FET has a transconductance of 1 mS per micron of gate width. C_{gs} is 1 fF per micron of gate width, and C_{gd} is 0.1 fF per micron of gate width

Design a resistive feedback amplifier with 20 dB gain S21 for a 75 Ohm system using this FET. Draw the circuit diagram with all element values and determine the following:

FET width = 146.7 μm
 transconductance = 0.1467 S
 $C_{gs} =$ 146.7 fF
 $C_{dg} =$ 14.67 fF

amplifier 3-dB bandwidth (from nodal analysis or the time constant method).

$(A_v)_{dB} = 20 \Rightarrow A_v = 10$ $Z_o = 75 \Omega$

To avoid reflections, $(S_{11} = 0)$

$R_f = (1 + A_v) Z_o$
 $R_f = 825 \Omega$ (2)

$g_m = (1 + A_v) / Z_o = 0.1467 \text{ S}$

$g_m = 0.1467 \text{ S}$ (2)

$\Rightarrow 10^{-3} \cdot W_g = 0.1467$


$W_g = 146.7 \mu\text{m}$ (2)

$$C_{gs} = 1 \text{ fF} * W_g = 146.7 \text{ fF}$$

$$C_{gd} = 0.1 \text{ fF} * W_g = 14.67 \text{ fF}$$

(2)

Circuit

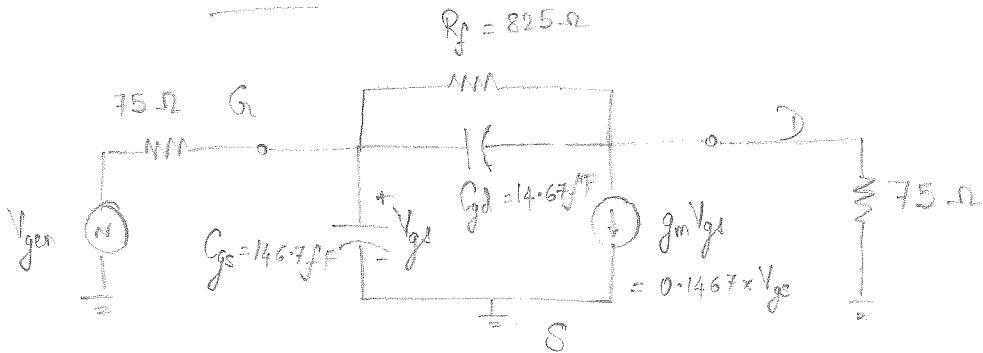

(2)

By NORTC method,

$$R_{11} = (75 \parallel 75) = 37.5 \Omega$$

(1)

R_{22} is calculated as follows. First remove R_f .

$$V_{gs} = I_{in} R_{gen}$$

$$V_{in} = V_{gs} + (g_m V_{gs} + I_{in}) * R_L$$

$$= I_{in} [R_{gen} + (g_m R_{gen} + 1) * R_L]$$

$$R_{in} = \frac{V_{in}}{I_{in}} = [Z_0 + (1 + g_m Z_0) * Z_0]$$

$$R_{22} = R_f \parallel R_{in} \quad (\text{Now add } R_f \text{ back again})$$

$$R_{22} = R_f \parallel [Z_0 + (1 + g_m Z_0) * Z_0] = 825 \parallel [75 + 900 * 1875]$$

$$R_{22} = 446.9 \Omega$$

(3)

$$a_1 = R_{11} C_{gs} + R_{22} C_{gd} = (5.501 + 6.55) \text{ ps}$$

$$a_1 = 12.051 \text{ ps}$$

$$\frac{1}{a_1} = \omega_{3dB} \Rightarrow f_{3dB} = \frac{1}{2\pi a_1} = 13.2 \text{ GHz}$$

$$f_{3dB} = 13.2 \text{ GHz}$$

①

NAME	TITLE	DWG. NO.
SMITH CHART FORM ZY-01-N	Microwave Circuit Design - EE523 - Fall 2000	DATE

NORMALIZED IMPEDANCE AND ADMITTANCE COORDINATES

