

**ECE ECE145A (undergrad) and ECE218A (graduate)**  
**TAKE HOME Final Exam. Return before Friday December 15, 2017**

HONOR SYSTEM: Open book. You have 3 hrs. WORK WITHOUT HELP.

Use all reasonable approximations (5% accuracy is fine. ),

***AFTER STATING and justifying THEM.***

***Think before doing complex calculations. Sometimes there is an easier way.***

Problem	Points Received	Points Possible
1A		5
1B		5
1C		5
1D		10
1E		10
1F		10 (218A only)
2A		10
2B		5
2C		5
2D		5
3A		10
3B		10
4A		5
4B		10
4C		10 (218A only)
total		95 (145A), 115 (218A)

**I certify that**

- 1) I have taken no more than 3 hours to work the exam. (or DSP) limits.**
- 2) I have help from no one**
- 3) I did not read the exam until the time I took the exam.**

**Signed:** \_\_\_\_\_

$$G_T = \frac{|S_{21}|^2 (1-|\Gamma_s|^2)(1-|\Gamma_L|^2)}{|(1-\Gamma_s S_{11})(1-\Gamma_L S_{22}) - S_{21} S_{12} \Gamma_s \Gamma_L|^2} \quad G_P = \frac{1}{1-|\Gamma_{in}|^2} \cdot |S_{21}|^2 \cdot \frac{1-|\Gamma_L|^2}{|1-\Gamma_L S_{22}|^2}$$

$$G_a = \frac{1-|\Gamma_s|^2}{|1-\Gamma_s S_{11}|^2} \cdot |S_{21}|^2 \cdot \frac{1}{1-|\Gamma_{out}|^2} \quad G_{max} = \frac{|S_{21}|}{|S_{12}|} \cdot [K - \sqrt{K^2 - 1}] \text{ if } K > 1$$


$$G_{MS} = \frac{|S_{21}|}{|S_{12}|} \cdot \text{if } K < 1 \quad K = \frac{1-|S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2|S_{21} S_{12}|} \quad \text{where } \Delta = \det[S]$$

Unconditionally stable if : (1)  $K > 1$  and (2)  $\|\det[S]\| < 1$

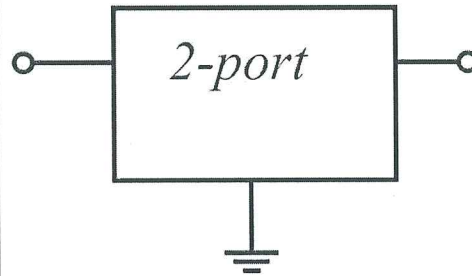**Problem 1, 35 points (145A), 45 points (218A)**

Two-port properties, Power gain definitions

At a signal frequency of 10 GHz, a transistor has  $S_{11} = 0$ ,  $S_{12} = 0.2$ ,  $S_{21} = 2$  and  $S_{22} = 0.8$ , as defined with a 50 Ohm impedance reference.



part a, 5 points

Is the circuit unconditionally stable? Hint: examine the expressions for  $\Gamma_{in}$  and  $\Gamma_{out}$

Yes/No: ? NO

2

$$\Gamma_{out} = S_{22} + \frac{S_{12} S_{21} \Gamma_S}{1 - S_{11} \Gamma_S}$$

2

$$= 0.8 + \frac{(0.2)(2) \Gamma_S}{1 - (0) \Gamma_S} = 0.8 + 0.4 \Gamma_S$$


1

clearly, if  $\Gamma_S = 1$ ,  $\Gamma_{out} = 1.2$

so the 2-port is potentially unstable.

part b, 5 points

Please draw a SOURCE stability circle

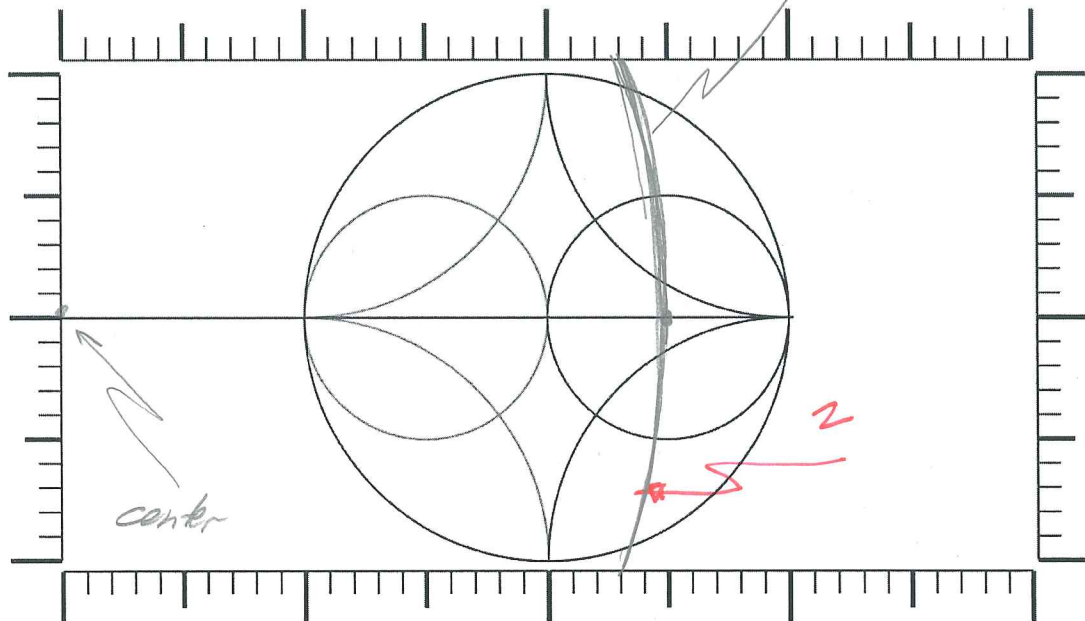

1 [ source stability circle is values of  $\Gamma_B$   
 which give  $|\Gamma_{out}| = 1$

1 [ If  $|\Gamma_{out}| = 1$  then  $\Gamma_{out} = e^{-j\theta}$

1 [  $\Gamma_{out} = e^{-j\theta} = 0.8 + 0.4 \Gamma_B$

$0.4 \Gamma_B = e^{-j\theta} - 0.8$

1 [  $\Gamma_B = 2.5 \cdot e^{-j\theta} - 2$

circle of radius = 2.5  
 centered at  $\Gamma_B = -2$

$\theta$	$e^{-j\theta}$	$\Gamma_B$
0	1	0.5
-180°	-1	-4.5

part c, 5 points

The transistor is connected to a 100 Ohm generator with 1mW available power. The output of the transistor is impedance matched to the load. How much power will be delivered to the load?

load power = 1.9 mW

$$|\Gamma_S| = \frac{100/50 - 1}{100/50 + 1} = \frac{1}{3}$$

$$S_{11} = 0 \quad S_{12} = 0.2$$

$$S_{21} = 2 \quad S_{22} = 0.8$$

this is the available gain

$$G_c = \frac{1 - |\Gamma_S|^2}{|1 - \Gamma_S S_{11}|^2} \cdot \frac{1}{|1 - \Gamma_{out}|^2} \cdot |S_{21}|^2$$

$$\Gamma_{out} = \frac{S_{22} + S_{21} S_{12} \Gamma_S}{1 - S_{11} \Gamma_S}$$

$$= 0.8 + 0.4 \Gamma_S = 0.8 + 0.4(1/3) = 0.9333$$

$$G_c = \frac{1 - |1/3|^2}{|1 - 1/3 \cdot 0|^2} \cdot \frac{0.4}{|1 - |0.9333||^2} = \frac{0.8888}{1} \cdot \frac{4}{1.871}$$

$$= 1.90$$

$$P_{out} = G_c \cdot P_{avg} = 1.9 \text{ mW}$$

part d, 10 points

IF necessary, the transistor is stabilized, and is then impedance-matched to a 50 Ohm generator and a 50 Ohm load? If the generator has 1mW available power, how much power will be delivered to the load?

load power = 10 mW

- 1 [ - transistor is probably available
- 2 [ - so after stabilization a matching, our gain will be the MSG.
- 1 [ -  $MSG = \frac{|S_{21}|}{|S_{12}|} = \frac{2}{0.2} = 10$ .
- 1 [  $P_{load} = 10 \cdot 1mW = 10mW$

part e, 10points

In the case of part D, above, if we consider the transistor, the possible stabilization network, and the matching networks to be, in combination, an amplifier, what are  $\|S_{21}\|$ ,  $\|S_{11}\|$ ,  $\|S_{22}\|$ ,  $\|S_{12}\|$  of the amplifier?

$$\begin{aligned}\|S_{11}\| &= \frac{0}{1} \\ \|S_{12}\| &= \frac{0.316}{1} \\ \|S_{21}\| &= \frac{3.16}{1} \\ \|S_{22}\| &= \frac{0.0}{1}\end{aligned}$$

2 [ - the amplifier has been matched  
so  $|S_{11}| = |S_{22}| = 0$

4 [ - the amplifier <sup>power</sup> gain is  $|S_{21}|^2$  and is equal  
to the K stab. MSB = 10  
 $|S_{21}|^2 = 10 \rightarrow |S_{21}| = 3.16$

4 [ - and (tricky) the matching and stab. network  
are reciprocal, so  
 $\frac{|S_{21}|}{|S_{12}|} = \frac{|S_{21}^T|}{|S_{12}^T|} = \frac{2}{0.2} = 10$   
 $\Rightarrow |S_{12}| = \frac{|S_{21}|}{10} = \frac{3.16}{10} = 0.316$

part f, 10 points (somewhat tricky, ece218c students only)

I now connect the amplifier of parts D and E to a 100 Ohm generator of 1 mW available power. The load is 25 Ohms. What is the power delivered to the load?

Power = \_\_\_\_\_

Sorry, I have messed up.

Can't be solved!

$$G_T = \frac{|S_{21}|^2 (1 - |\Gamma_S|^2) (1 - \|\Gamma_L\|^2)}{|(1 - S_{11}\Gamma_S)(1 - S_{22}\Gamma_L) - S_{12}S_{21}\Gamma_S\Gamma_L|^2}$$

$$S_{11} + S_{22} = 0 \quad |S_{21}| = 3.16 \quad |S_{12}| = 0.316$$

$$G_T = \frac{|S_{21}|^2 (1 - |\Gamma_S|^2) (1 - \|\Gamma_L\|^2)}{|1 - S_{12}S_{21}\Gamma_S\Gamma_L|^2}$$

$$|1 - S_{12}S_{21}\Gamma_S\Gamma_L|^2$$

Unfortunately, though we know  $|S_{21}|, |\Gamma_S|, |\Gamma_L|$

and though we know  $|S_{21}S_{12}|$ , we don't know  $S_{21}S_{12}$ !

8

cannot answer (!).

10 pts  
for noting  
that  
we can't solve



**Problem 2, 25 points**

Unconditionally stable and Potentially unstable amplifier design, gain circles

part a, 10 points

A MOSFET in common-source mode has  $\|S_{11}\| < 1$  and  $\|S_{22}\| > 1$ , and has stability circles (50 Ohm reference impedance) as below.

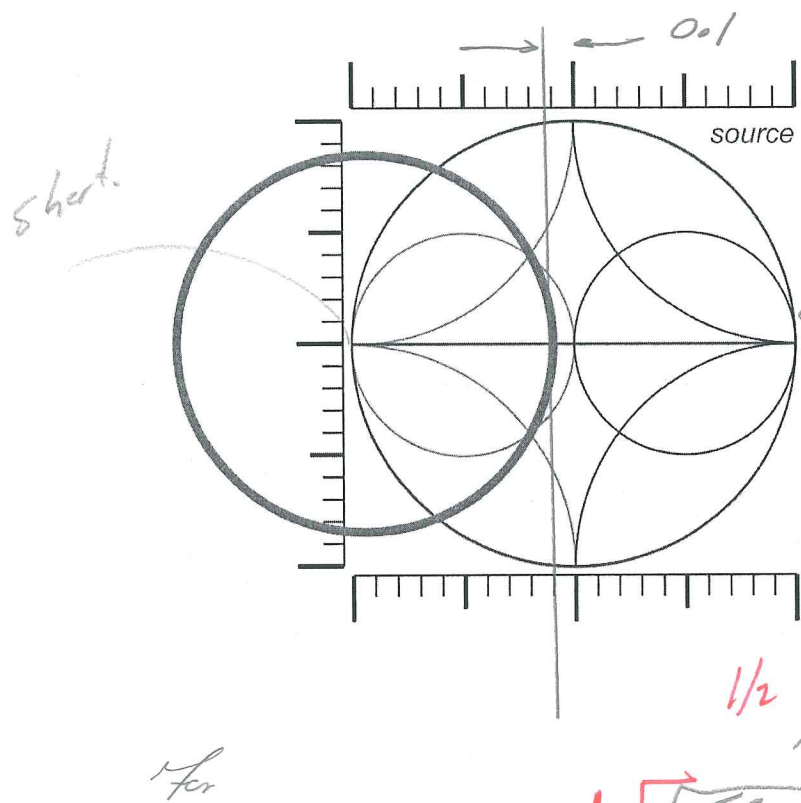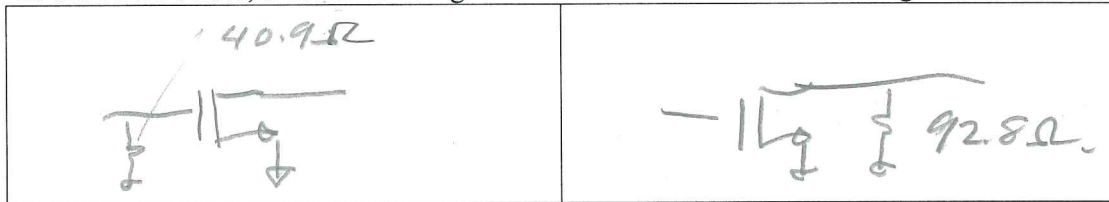In the boxes below, draw circuit diagrams of \*two\* methods of stabilizing the transistor.



source stability circle:  
values of  $\Gamma_{in}$  giving  
 $|\Gamma_{out}| = 1$


$$\Gamma_{out} = S_{22} + \frac{S_{12}S_{21}\Gamma_{in}}{1 - S_{11}\Gamma_{in}}$$

$$= S_{22} \text{ if } \Gamma_{in} = 0$$

Now  $\|S_{22}\| > 1$  so the  
point ( $\Gamma_{in} = 0$ ) is unstable

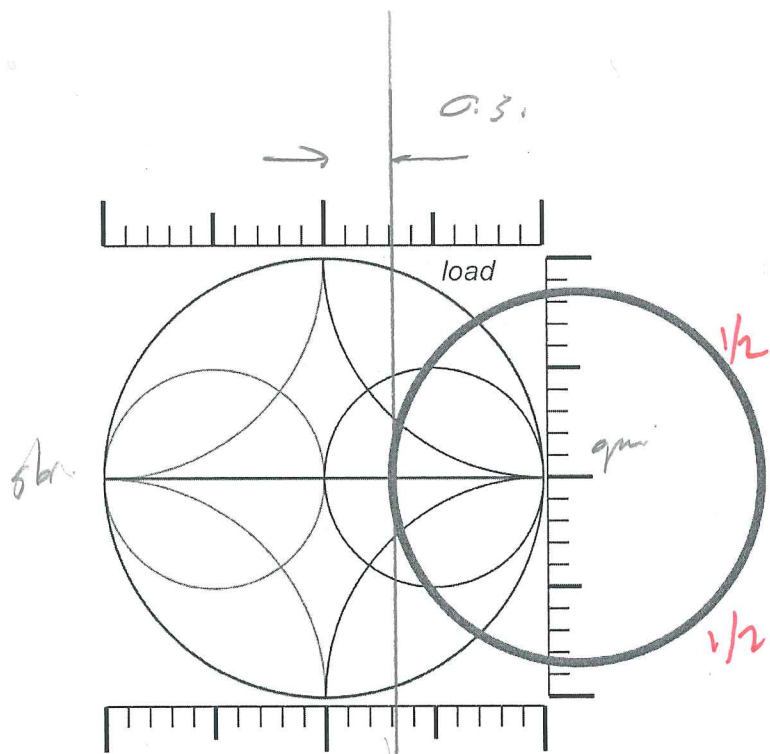50 - ~~center~~ inside of circle is stable





Load stability circle.  
 Values of  $\Gamma_L$  giving  
 $|\Gamma_{in}| = 1$

$$\Gamma_{in} = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L}$$


$$= S_{11} \text{ if } \Gamma_L = 0$$

1/2 [ Now  $|S_{11}| < 1$  so  
 the point  $\Gamma_L = 0$  is stable.  
 1 [ so - outside of circle is stable

Source

I [ stability circle is tangent to  $\Gamma = -0.1$   
 $\Rightarrow R = 50\Omega \cdot \frac{1-0.1}{1+0.1} = 50\Omega \cdot \frac{9}{11} = 40.9\Omega$

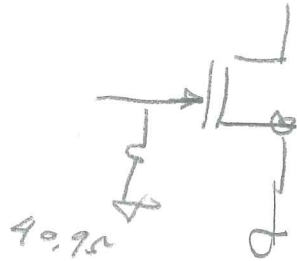
~~we need to~~  
we can stabilize by adding a shunt  $40.9\Omega$   $\downarrow$



Load


I [ stability circle is tangent to  $\Gamma = 0.3$   
 $R = 50\Omega \cdot \frac{1+0.3}{1-0.3} = 50\Omega \cdot \frac{13}{7} = 92.8\Omega$

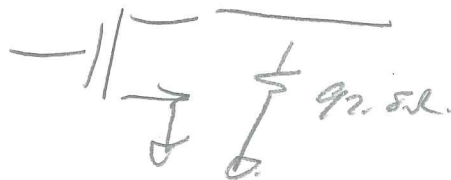I [ we need to keep  $Z_L$  less than this, so  
we need a shunt connection.



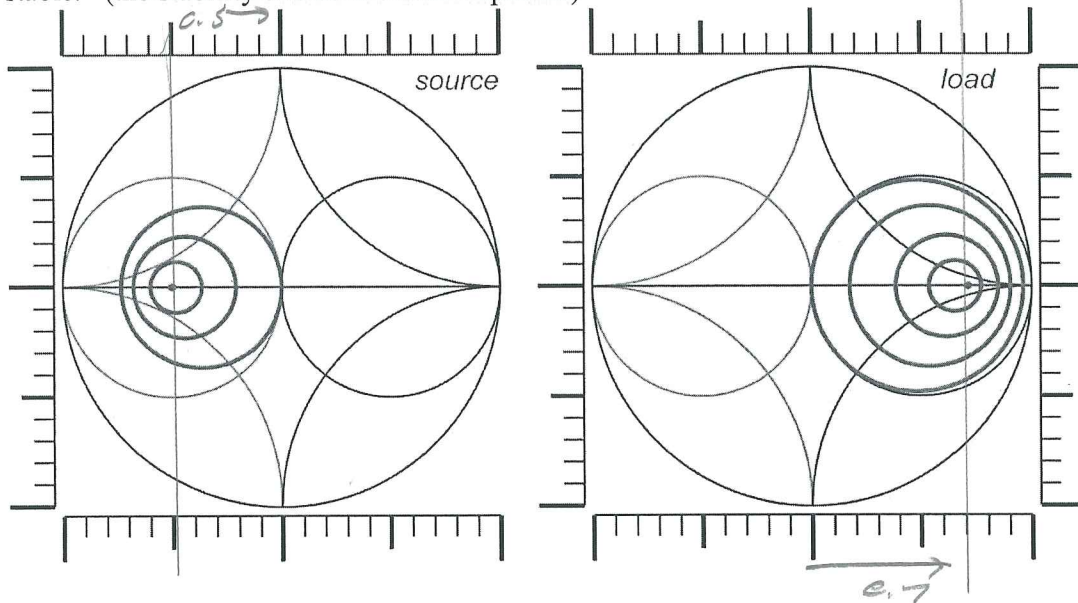part b, 5 points

A transistor has available and operating gain circles as below. These are graphed in 1dB gain increments. The transistor MAG is 10dB, and the transistor is unconditionally stable. (the stability circles have been updated)



What source and load impedances are required for 10dB gain?

$Z_s = 16.7 \Omega$        $Z_L = 283.3 \Omega$

2.5 [  $Z_s = 50 \Omega \frac{1 - 0.5}{1 + 0.5} = 50 \Omega \cdot \frac{1}{3} = 16.7 \Omega$  ]

2.5 [  $Z_L = 50 \Omega \frac{1 + 0.7}{1 - 0.7} = 50 \Omega \frac{17}{3} = 283.3 \Omega$  ]

part c, 5 points

We continue with the transistor of part B. If the generator impedance is 50 Ohms, and the load impedance is matched to the transistor output impedance, then what power gain will the transistor have?

Power gain = 7 dB

3 [ A 50  $\Omega$  generator is 3 steps (circles) away from  $Z_{opt}$ .  $\rightarrow$  3 dB gain decrease ] 2  
7 dB gain

part d, 5 points

We continue with the transistor of part B. If the load impedance is 50 Ohms, and the generator impedance is matched to the transistor input impedance, then what power gain will the transistor have?

Power gain = 6 dB


3 [  $\frac{P_L}{P_{in}}$  50  $\Omega$  load is 4 circles away  
From  $Z_{in} \rightarrow$  4 dB gain decrease ] 2

**Problem 3, 20 points**

*S parameters and Signal flow graphs*

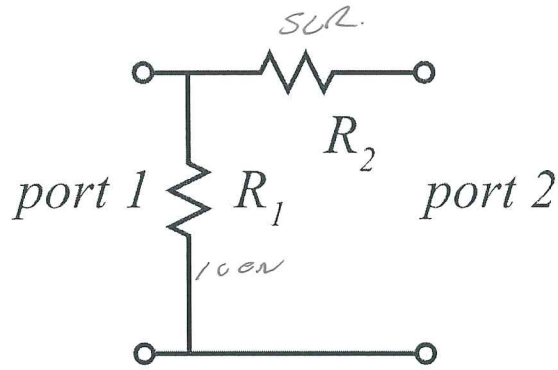
part a, 10 points

We have  $R_1=100$  Ohms and  $R_2=50$  Ohms  
 Given a 50 Ohm impedance reference,  
 Find the four S-parameters of this network



$S_{11} = 0$ ,  $S_{12} = 1/2$ ,  $S_{21} = 1/2$ ,  $S_{22} = 1/4$ .

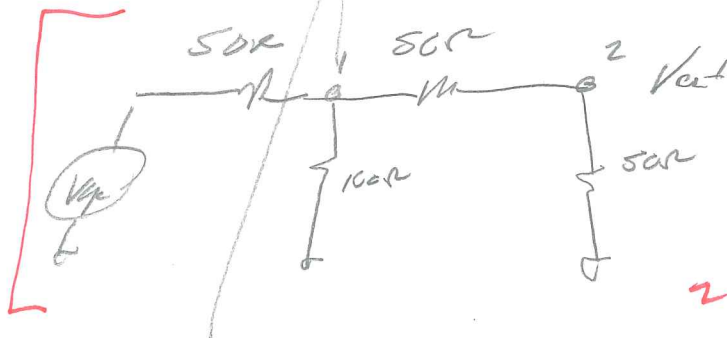1  $[Z_L = 100 \Omega \parallel (100 \Omega) = 50 \Omega]$




2  $\left[ \frac{V_{out}}{V_{gs}} = \frac{50 \Omega}{50 \Omega + 50 \Omega} \frac{Z_L}{Z_L + 50 \Omega} \right]$   
 $= \frac{1}{2} \cdot \frac{1}{2} = 1/4$

2  $\left[ S_{21} = 2 \frac{V_o}{V_{gs}} \Big|_{Z_L = Z_0 = 50} = 1/2 \right]$

1  $\left[ \text{Since } Z_L / Z_0 = 50 \Omega / 50 \Omega = 1, S_{11} = 0 \right]$

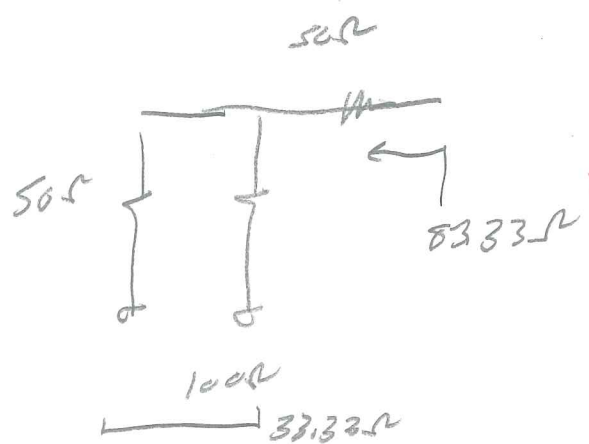2  $\left[ S_{12} = S_{21} \text{ reciprocity} \right]$   
 $= 1/2$




2  $\left[ S_{22} = \frac{83.33/50 - 1}{83.33/50 + 1} = \frac{5/3 - 1}{5/3 + 1} = \frac{5-3}{5+3} \right]$   
 $= \frac{2}{8} = 1/4$

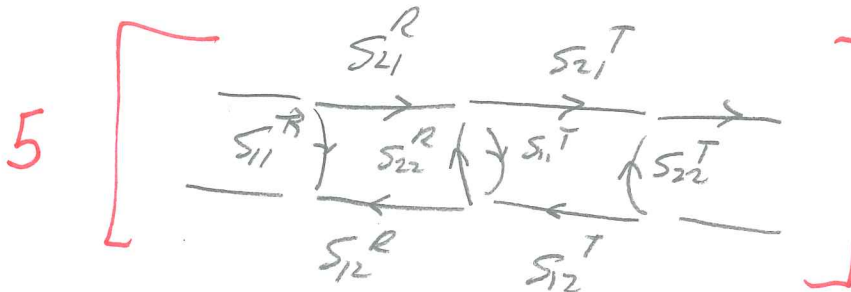part b, 10 points

We have a transistor having  $S_{11}=0.5$ ,  $S_{12}=0.1$ ,  $S_{21}=3$ ,  $S_{22}=0.5$ . We connect the network of part a to the transistor's INPUT. Please find  $S_{21}$  of the combined network

$S_{21}$  of the combined network = 1.714



4

$$S_{21 \text{ overall}} = \frac{S_{21}^R S_{21}^T}{1 - S_{22}^R S_{11}^T}$$


1

$$= \frac{(1/2)(3)}{1 - (1/4)(1/2)} = \frac{3/2}{1 - 1/8} = \frac{3/2}{7/8}$$

$$= \frac{3 \cdot 4}{7} = \frac{12}{7} = 1.714$$

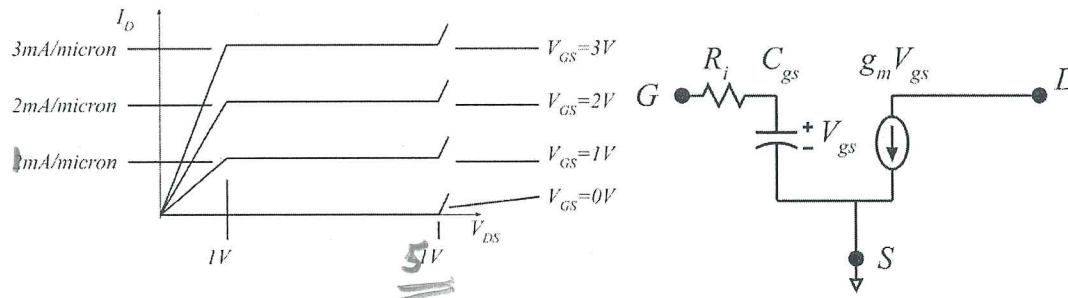**Problem 4, 15 points (145A), 25 points (218A)**

Power amplifier design (the graph is updated)



A FET has the common-source characteristics above, normalize to FET gate width. You can infer  $g_m$  from the data above. We have  $R_i = 1/g_m$ , and  $f_T$  is 200 GHz. The signal frequency is 50 GHz

part a, 5 points

Assuming TEMPORARILY a 1 micron FET width, give the following.

$g_m = \underline{1\text{ mS}}$ ,  $C_{gs} = \underline{0.795\text{ fF}}$   $R_i = \underline{1\text{ k}\Omega}$

2  $\left[ g_m = \frac{3\text{ mA}/\mu\text{m} \cdot 1\mu\text{m}}{3\text{ V}} = \frac{3\text{ mA}}{3\text{ V}} = 1\text{ mS} \right]$

2  $\left[ f_T = \frac{g_m}{2\pi C_{gs}} \rightarrow C_{gs} = \frac{g_m}{2\pi f_T} = 0.795\text{ fF} \right]$

1  $\left[ R_i = 1/g_m = 1\text{ k}\Omega \right]$



$$f = 50 \text{ kHz}$$

part b, 10 points

When we attempt to design impedance-transformation networks, we have found that the minimum load impedance we can synthesize is 10 Ohms.

What FET width should we select?  $W_g = \underline{133.3 \mu\text{m}}$

What maximum undistorted output power will we obtain?  $P_{out} = \underline{200 \text{ mW}}$

What input power does this require?  $P_{in} = \underline{7.38 \text{ mW}}$


$$1 \quad \left[ 5V - 1V = 4V \text{ swing} \right]$$

$$1 \quad \left[ R_L = 10 \Omega \rightarrow I_{max} = \frac{4V}{10 \Omega} = 400 \text{ mA} \right]$$

$$1 \quad \left[ \text{max } C_{gs} = 3 \text{ nA}/\mu\text{m} \rightarrow \text{width} = \frac{400 \text{ mA}}{3 \text{ nA}/\mu\text{m}} = 133.3 \mu\text{m} \right]$$

$$2 \quad \left[ \Delta V = 4V, \quad \Delta I = 400 \text{ mA} \right]$$
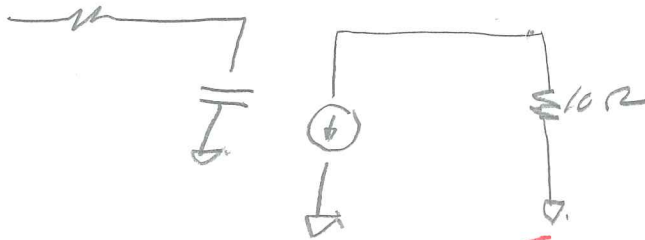
$$P_{max} = \frac{1}{8} \cdot \Delta V \cdot \Delta I = \frac{4V \cdot 400 \text{ mA}}{8} = \underline{200 \text{ mW}}$$



$$f_c = 1 \text{ nS}/\mu\text{m} \cdot 133 \mu\text{m} = 133 \text{ nS}$$

$$R_i = 1/f_c = 7.5 \Omega$$

$$C_{gs} = \frac{f_c}{2\pi f} = 0.1057 \text{ pF}$$

$$P_{out} = I_{out}^2 \cdot R_L$$

$$I_{in} = I_{out} \cdot \frac{2\pi f C_{gs}}{g_m} = I_{out} \cdot \frac{f}{f_T}$$

$$P_{in} = I_{in}^2 \cdot R_i = I_{out}^2 \cdot \left(\frac{f}{f_T}\right)^2 \cdot R_i$$

$$\frac{P_{out}}{P_{in}} = \frac{R_L}{R_i} \cdot \left(\frac{f_T}{f}\right)^2 = \frac{10 \Omega}{7.5 \Omega} \cdot \left(\frac{200 \text{ MHz}}{50 \text{ MHz}}\right)^2$$
$$= \frac{4}{3} (4)^2 = \frac{4^3}{3}$$

$$P_{in} = \frac{P_{out}}{4^3/3} = \frac{200 \text{ mW}}{4^3/3} = \frac{200 \text{ mW}}{21.3} = 9.38 \text{ mW}$$