
ECE145a / 218a ***Bilateral Tuned Amplifier Design***

Mark Rodwell

University of California, Santa Barbara

rodwell@ece.ucsb.edu 805-893-3244, 805-893-3262 fax

Stability

Unconditionally stable if $\|\Gamma_{in}\| < 1$ for all possible Γ_L .

Equivalently : unconditionally stable if $\|\Gamma_{out}\| < 1$ for all possible Γ_S .

A 2 - port is unconditionally stable if the Rollet stability factor $K > 1$, where

$$1) K = \frac{1 - \|S_{11}\|^2 - \|S_{22}\|^2 + \|S_{11}S_{22} - S_{12}S_{21}\|^2}{2 \cdot \|S_{12}S_{21}\|}$$


and

$$2a) \|S_{11}S_{22} - S_{12}S_{21}\| < 1.$$

An alternative 2nd condition is that the stability measure B_1 be positive, where



$$2b) B_1 = 1 + \|S_{11}\|^2 - \|S_{22}\|^2 + \|S_{11}S_{22} - S_{12}S_{21}\|^2$$

Potentially Unstable Amplifier

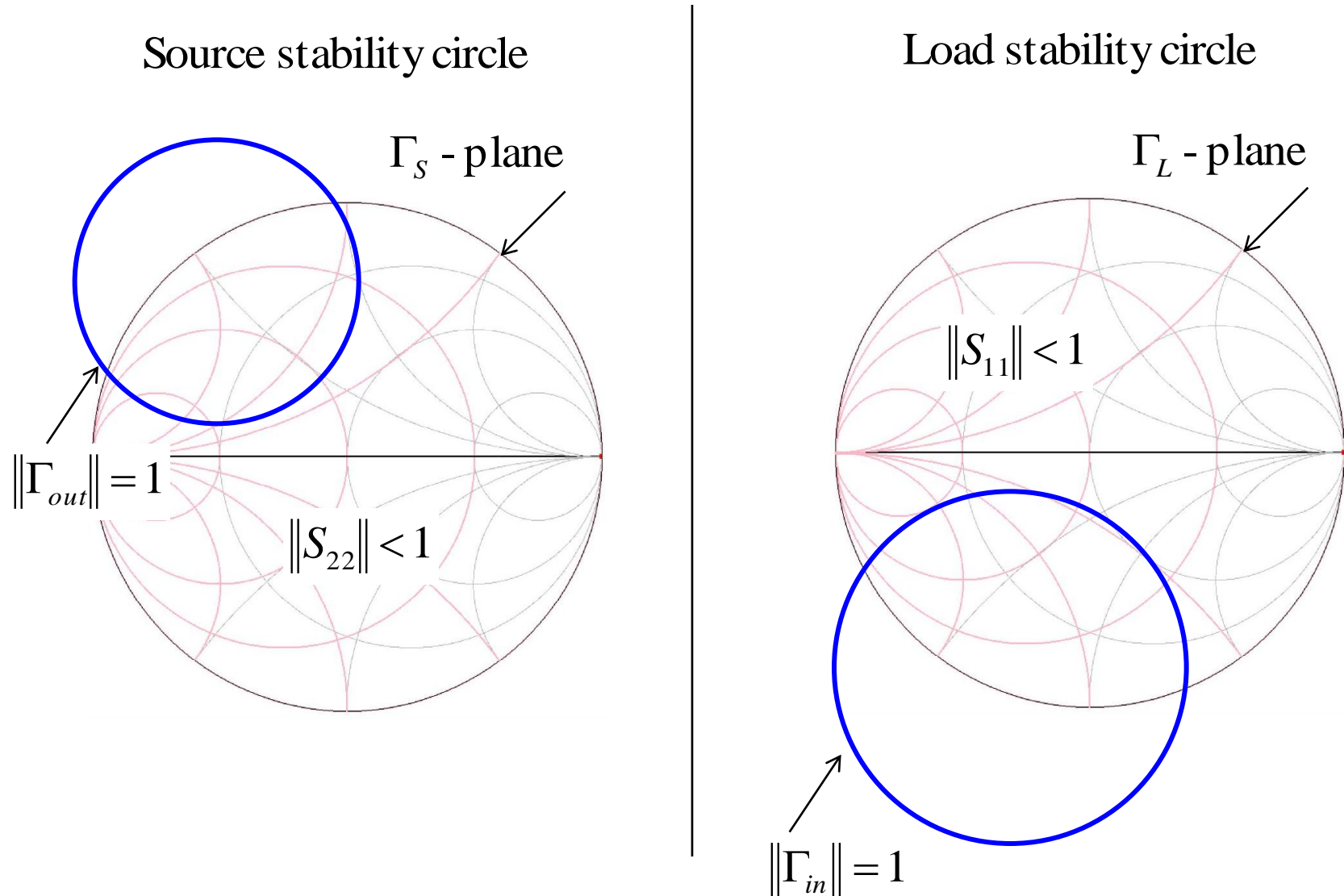



This is a test at one specific frequency; must test at all frequencies.

Unconditionally stable Amplifier

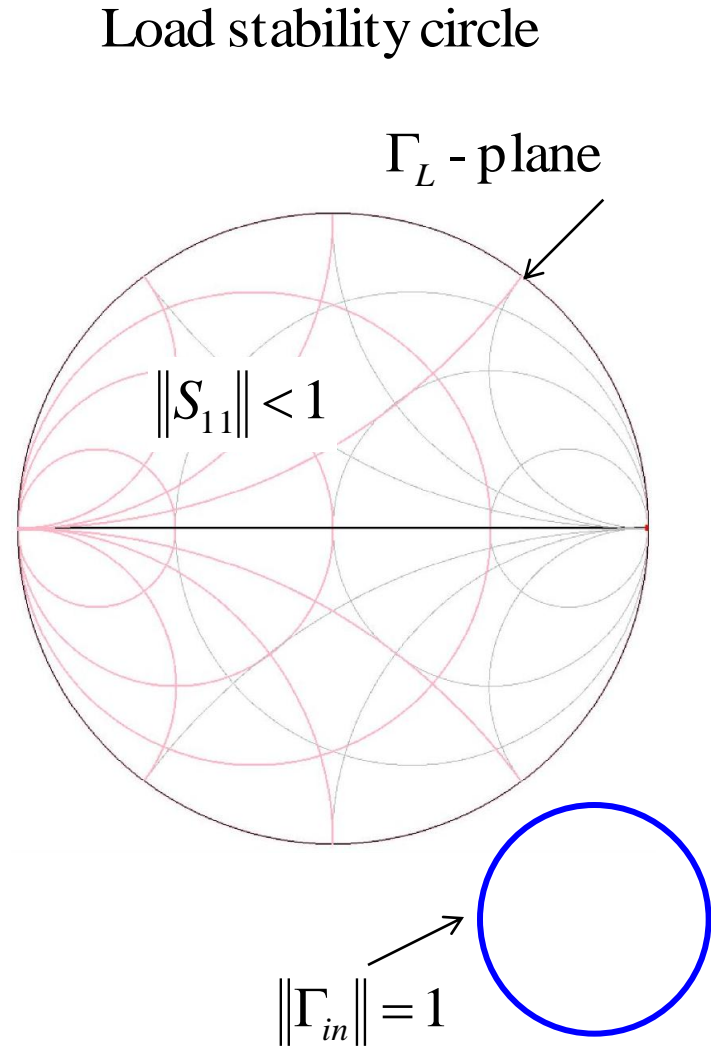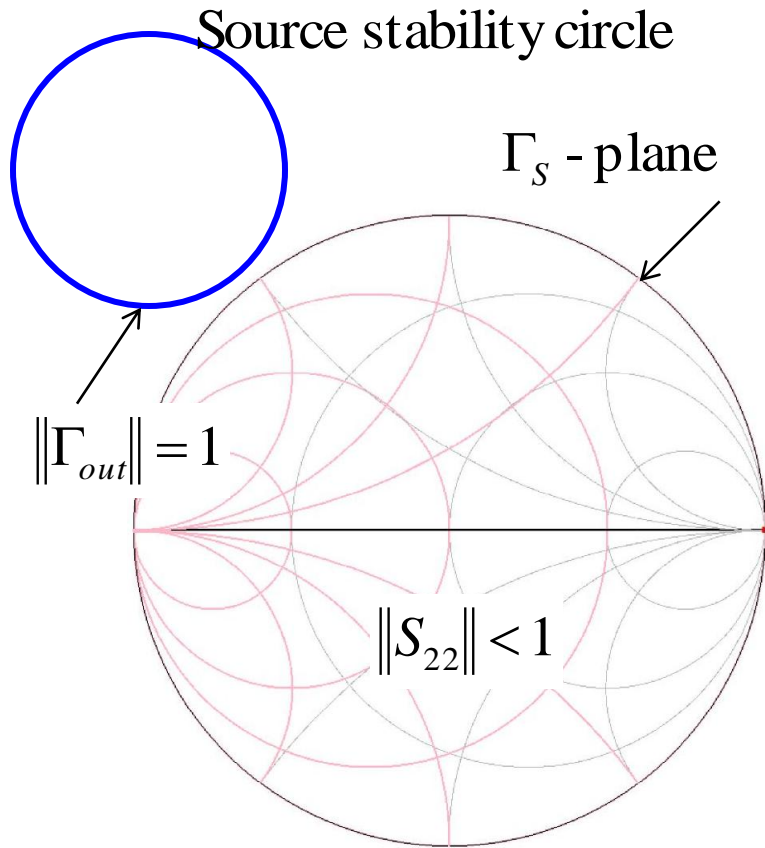

This is a test at one specific frequency; must test at all frequencies.

Why Might MAG Not Exist ?

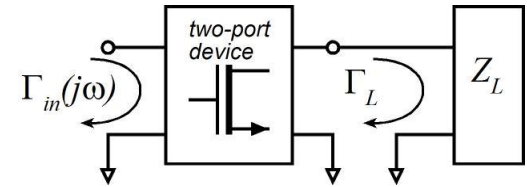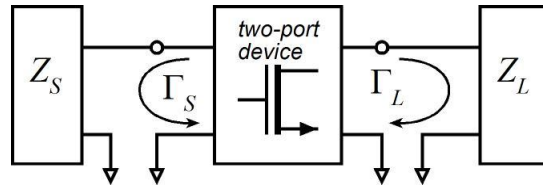

If the network is potentially unstable,
then by placing Γ_L within the load stability circle,
we force $\|\Gamma_{out}\| > 1$.


The device then has negative input resistance.

Appropriate choice of source impedance
will then cause oscillation.

If we adjust Γ_S and Γ_L to obtain
the highest possible gain,
we will instead obtain infinite gain (oscillation).

The maximum available gain is infinite. This is *not* good.

Load stability circle

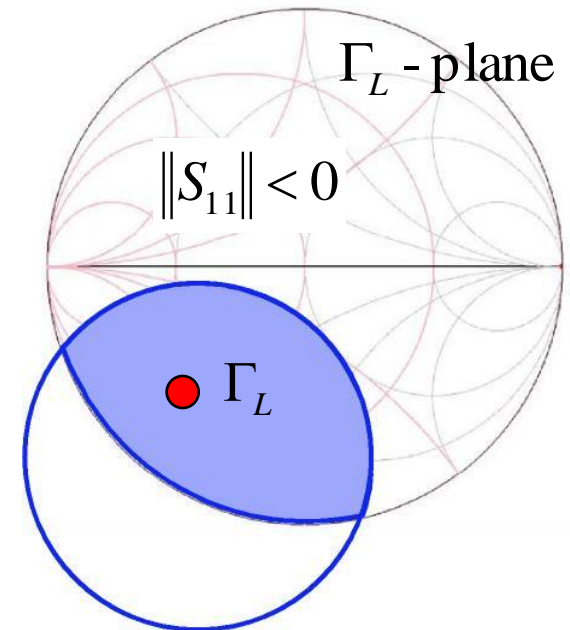

Computing Maximum Available Gain

$$G_{\max} = \frac{P_{AVA}}{P_{in}} \xrightarrow{\text{iff } P_{AVA}=P_{load} \text{ and } P_{in}=P_{AVG}} \frac{P_{load}}{P_{AVG}} = G_T$$

we now need $\Gamma_L = \Gamma_{out}^*$ and $\Gamma_s = \Gamma_{in}^*$

we must simultaneously solve

$$\Gamma_{in} = S_{11} + \Gamma_L \frac{S_{21}S_{12}}{1 - S_{22}\Gamma_L} = \Gamma_s^* \text{ and } \Gamma_{out} = S_{22} + \Gamma_s \frac{S_{21}S_{12}}{1 - S_{11}\Gamma_s} = \Gamma_L^*$$

and then substitute into

$$G_T = \frac{1 - \|\Gamma_s\|^2}{\|1 - \Gamma_{in}\Gamma_s\|^2} \cdot \|S_{21}\|^2 \cdot \frac{1 - \|\Gamma_L\|^2}{\|1 - S_{22}\Gamma_L\|^2}$$

The calculations are long, and will not be shown.



Maximum Available Gain

$$G_{\max} = \left\| \frac{S_{21}}{S_{12}} \right\| \cdot \left(K - \sqrt{K^2 - 1} \right)$$

$$\text{where } K = \frac{1 - \|S_{11}\|^2 - \|S_{22}\|^2 + \|S_{11}S_{22} - S_{12}S_{21}\|^2}{2 \cdot \|S_{12}S_{21}\|} \text{ (Rollet stability factor).}$$



Note that G_{\max} is only defined for an unconditionally stable network, i.e. $K > 1$ and $B_1 > 0$.

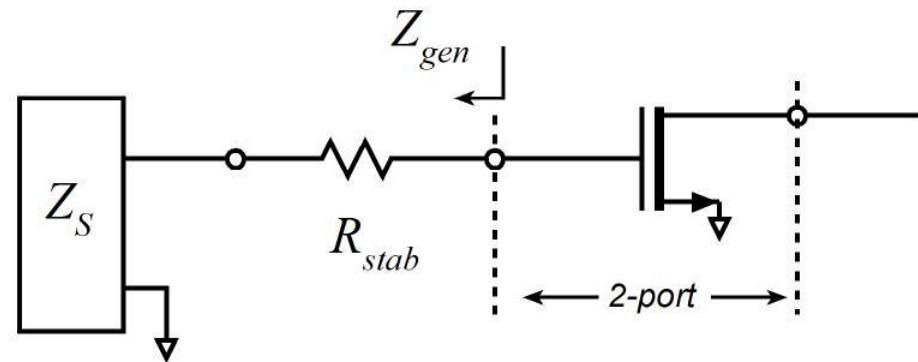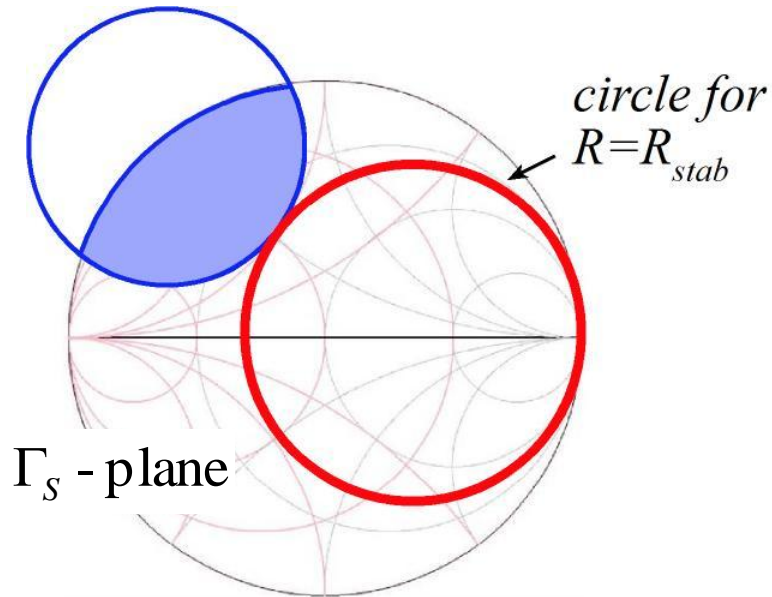Stabilization: if device is potentially unstable




Adding series resistance R_{stab} as shown constains Z_{gen} to lie within stable region.

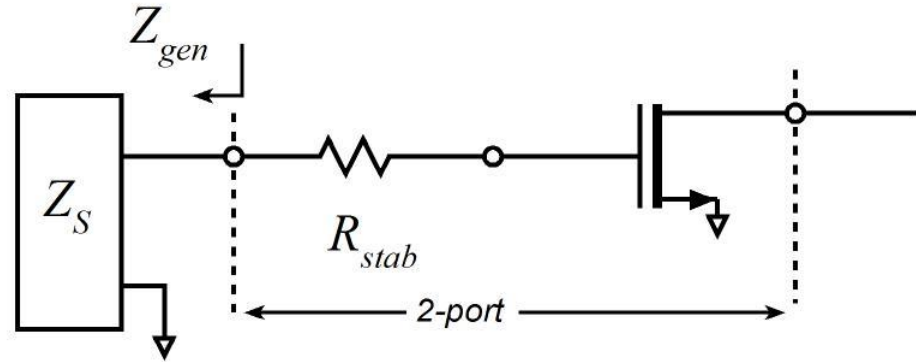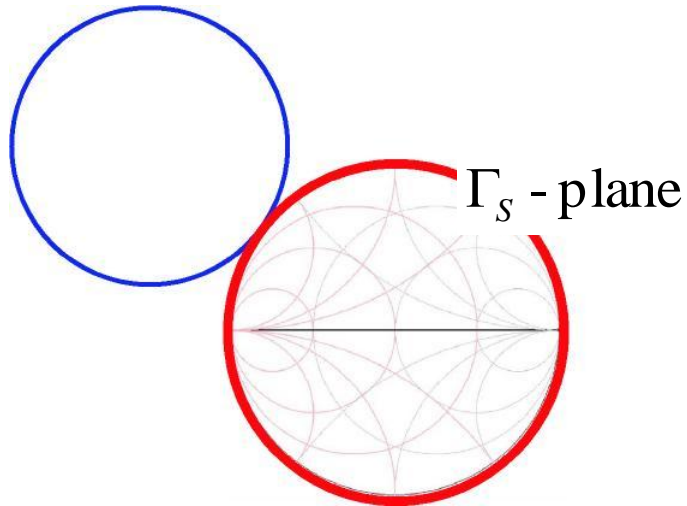Stabilization: if device is potentially unstable






If we include R_{stab} in the 2-port being simulated in the CAD software, the stability circle moves outwards as shown..

4 Obvious Stabilization Methods




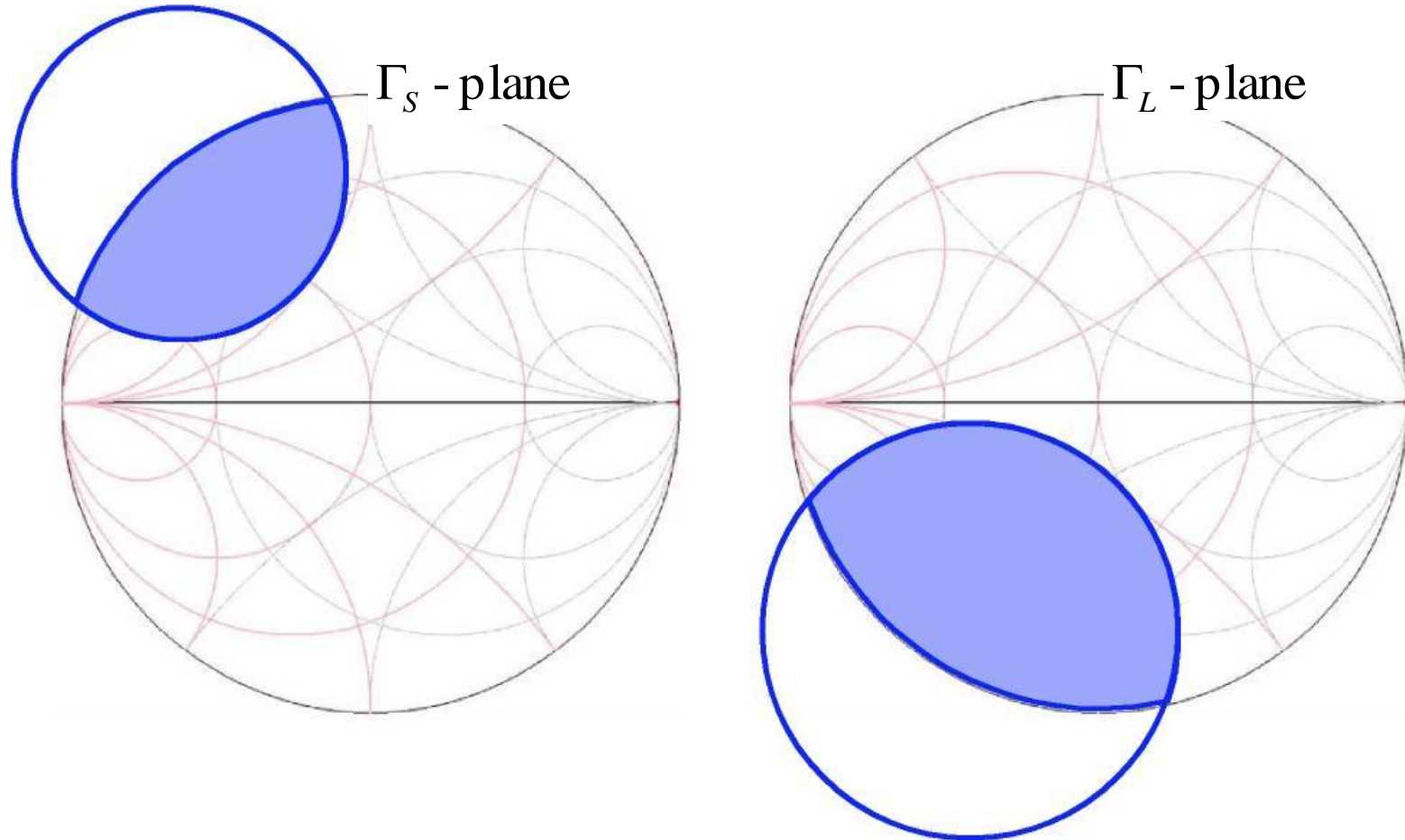


Given these stability circles, four stabilization methods are immediately apparent.




Series Stabilization On Input

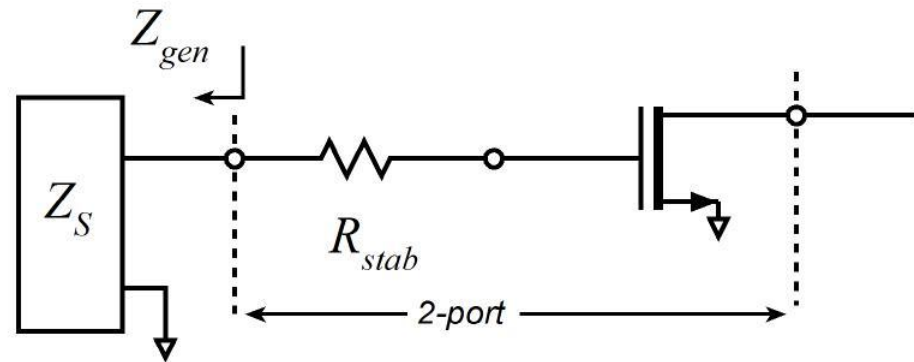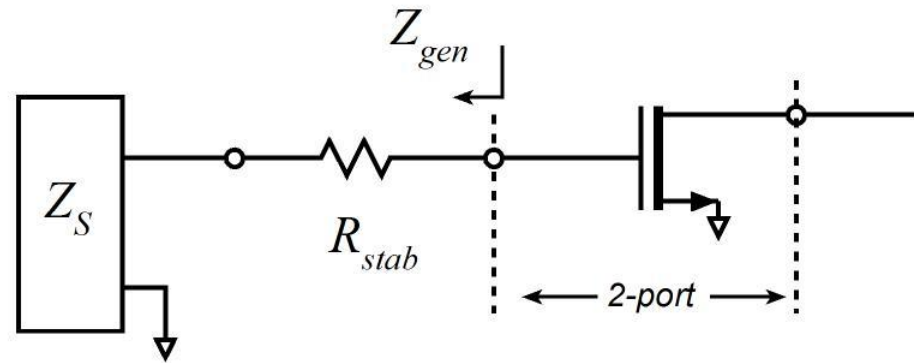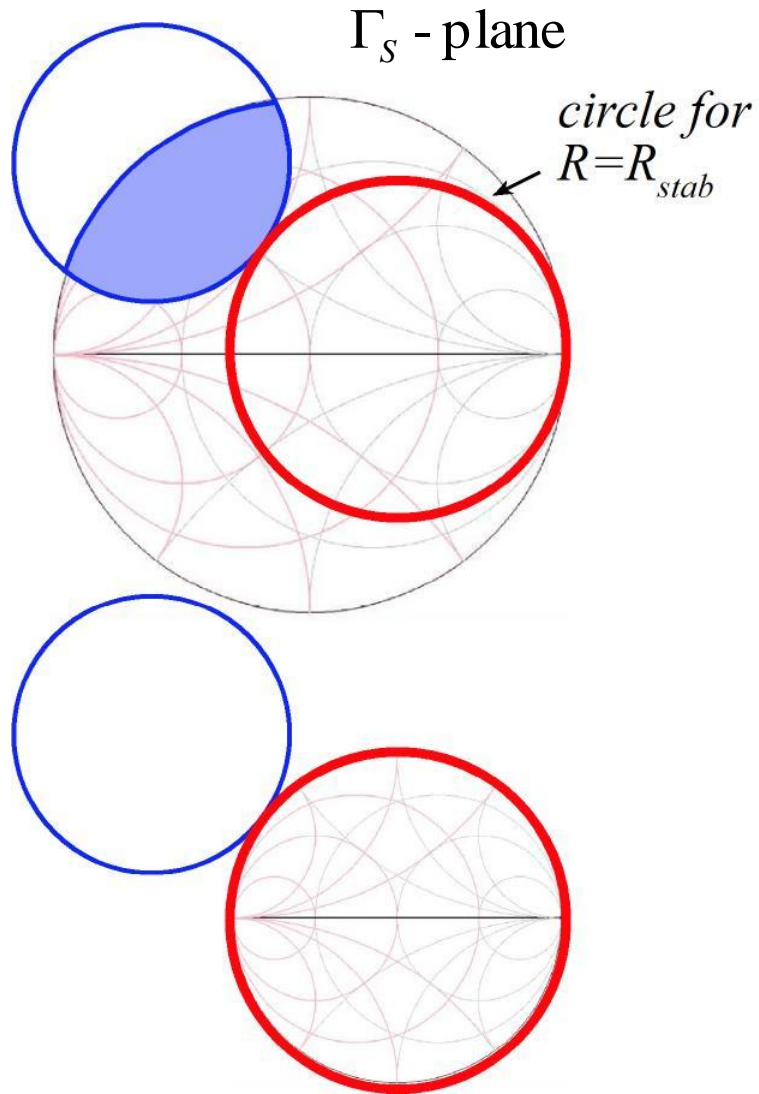




Shunt Stabilization On Input

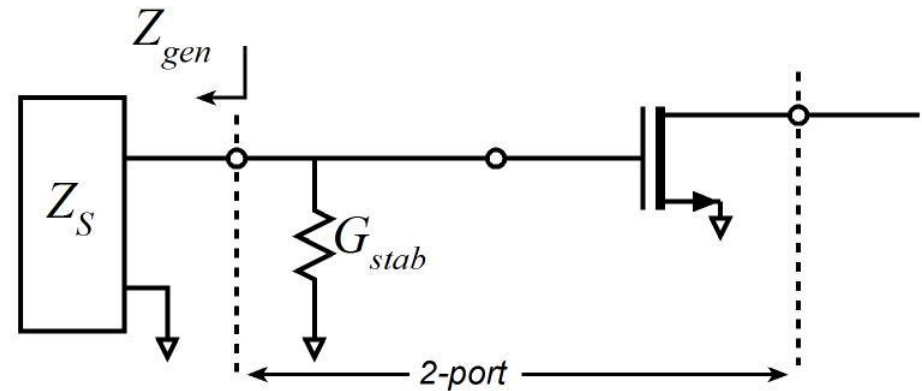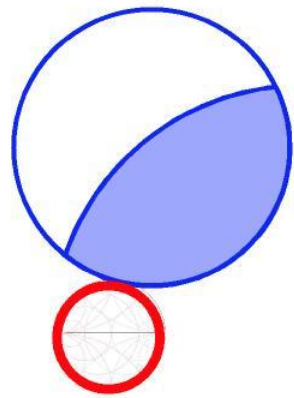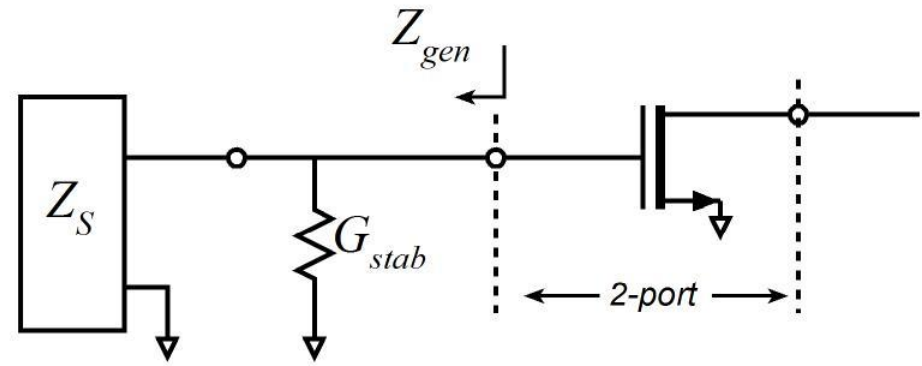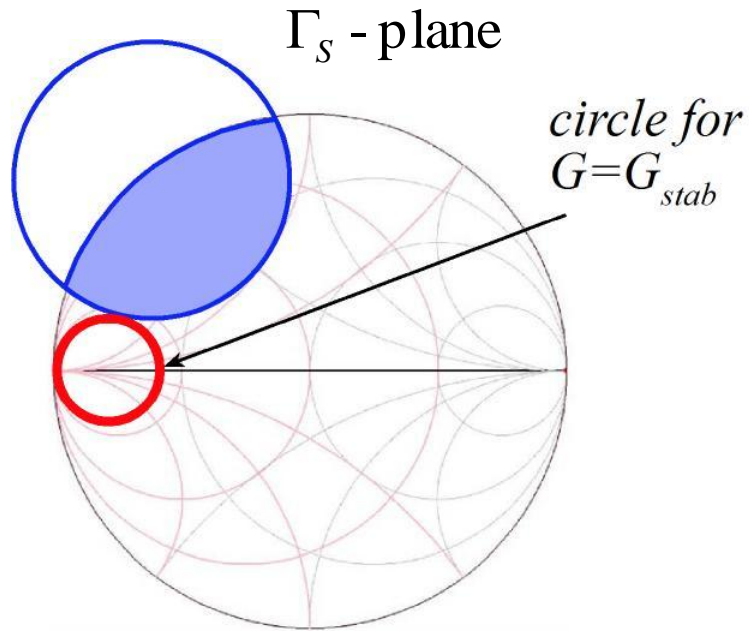

Series Stabilization On Output

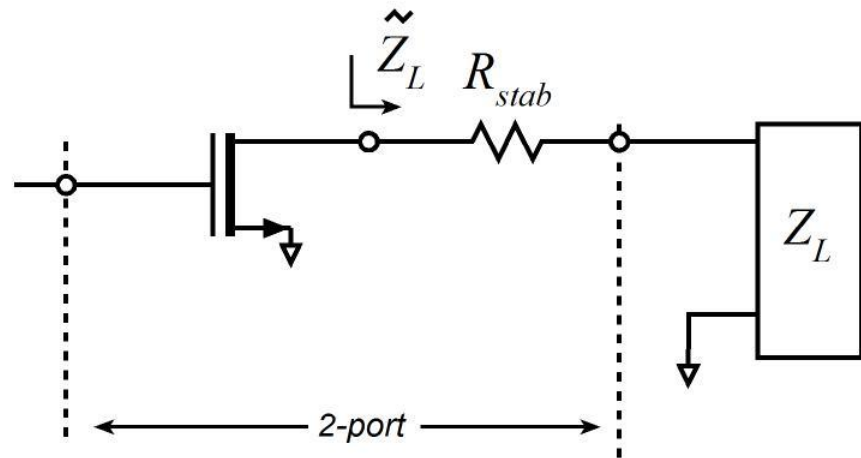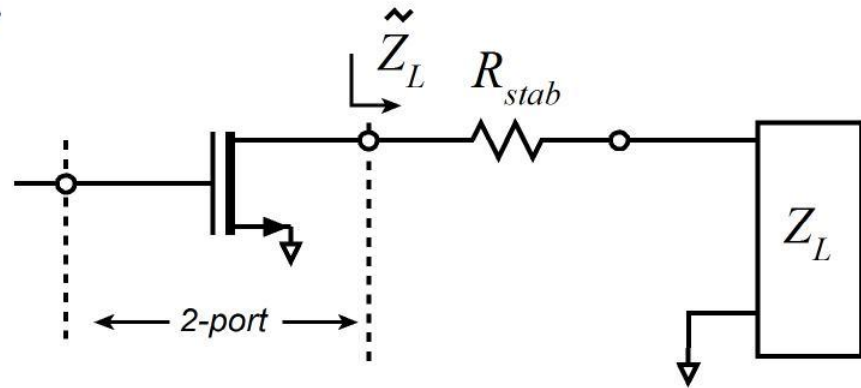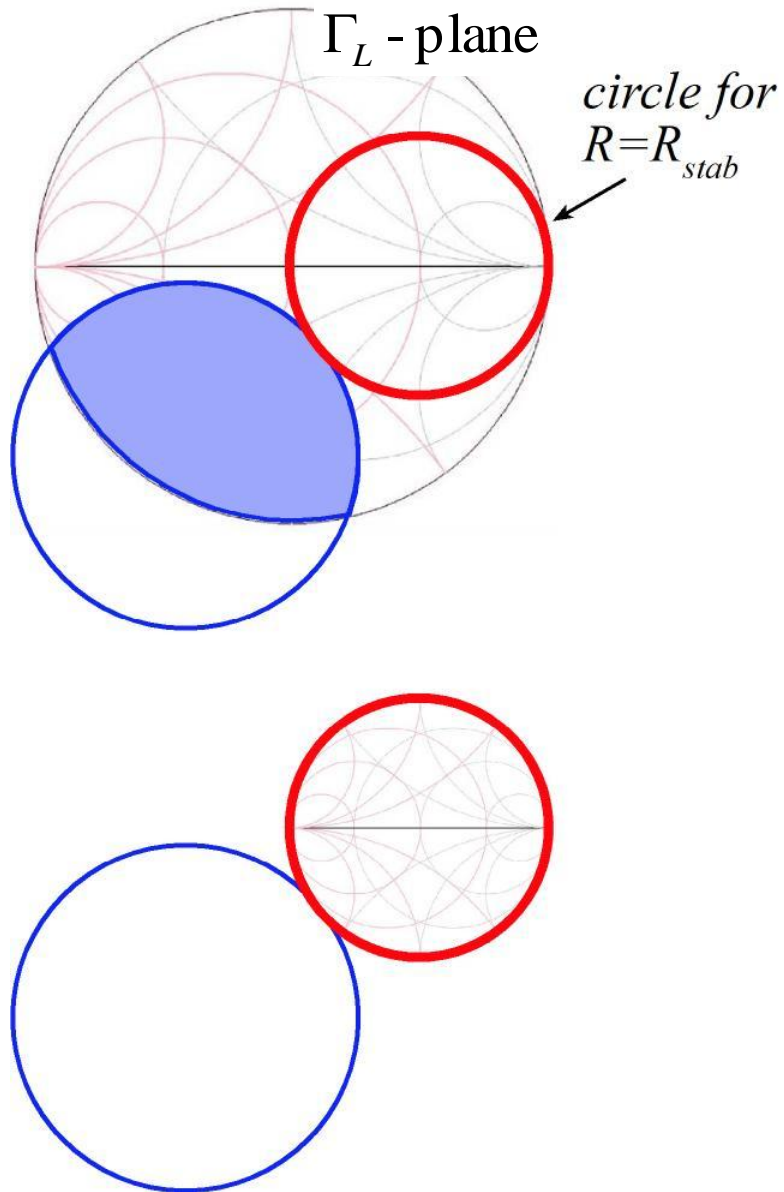


Shunt Stabilization On Output

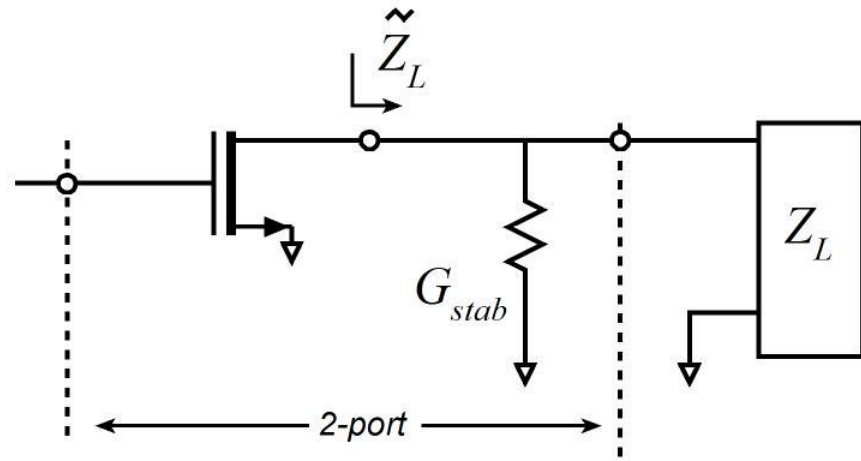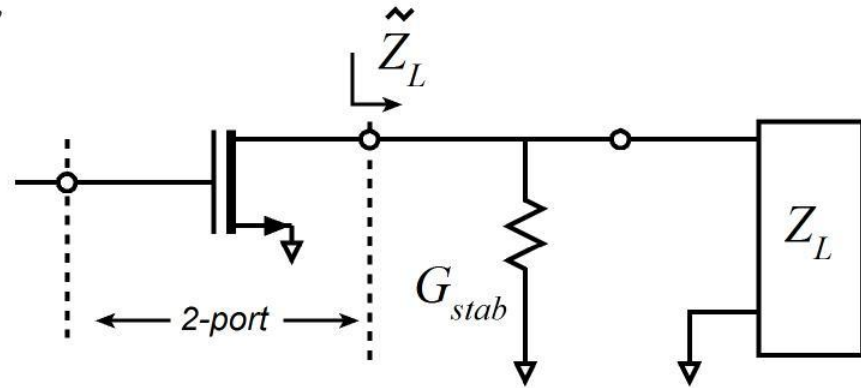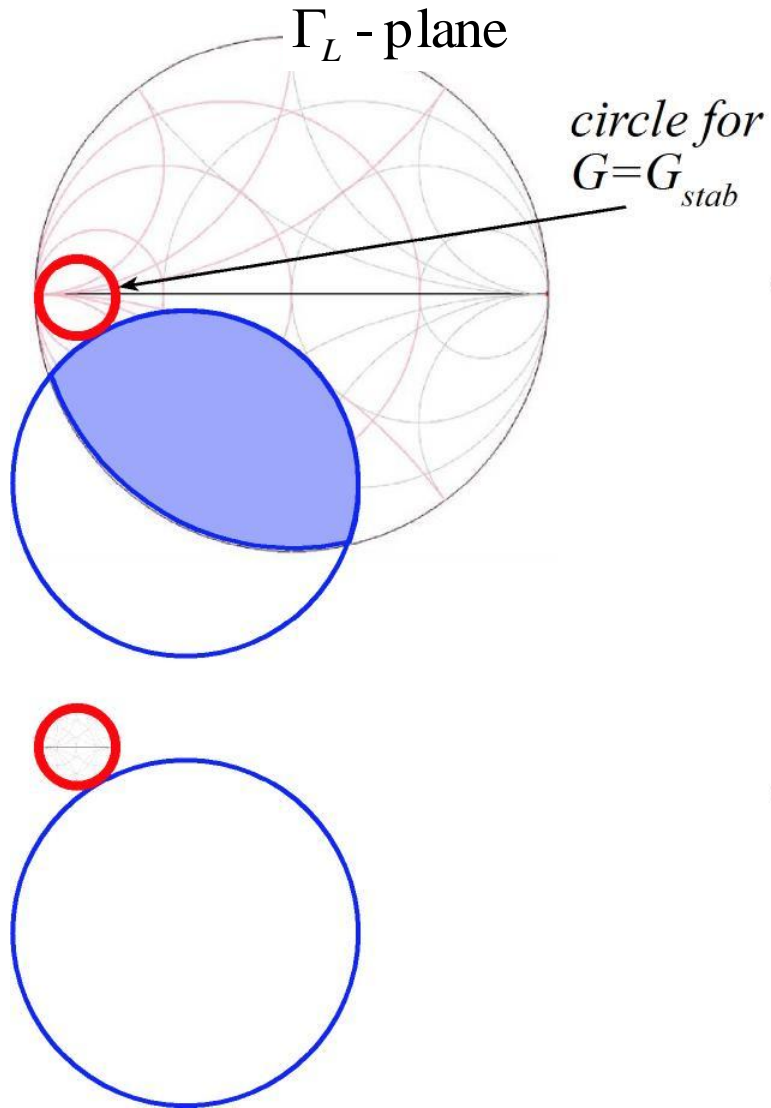

What Gain Do We Get After Stabilization ?

Before stabilization

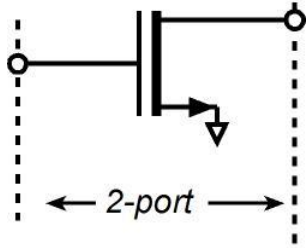


* original * S - parameters : S_{ij}

$$G_{\max} = \left\| \frac{S_{21}}{S_{12}} \right\| \cdot \left(K - \sqrt{K^2 - 1} \right)$$

= undefined (unstable)

After stabilization

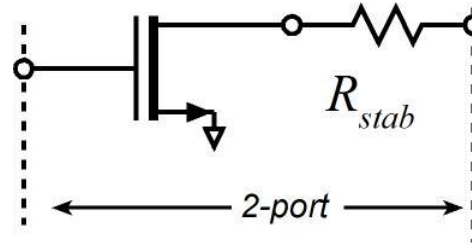

* changed * S - parameters : \tilde{S}_{ij}


$$G_{\max \text{ stable}} = \left\| \frac{\tilde{S}_{21}}{\tilde{S}_{12}} \right\| \cdot \left(\tilde{K} - \sqrt{\tilde{K}^2 - 1} \right)$$

but $\tilde{K} = 1$ (just stable)

$$G_{\max \text{ stable}} = \left\| \frac{\tilde{S}_{21}}{\tilde{S}_{12}} \right\|$$

How do \tilde{S}_{21} and \tilde{S}_{12} compare to S_{21} and S_{12} ?

Consider First The Stabilization Network

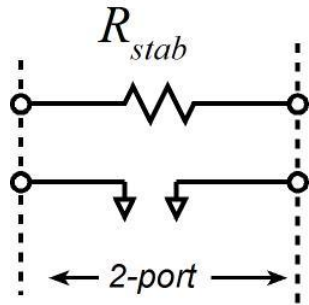


* stabilizer * S - parameters : S_{ij}^R

$$[S_{ij}^R] = \begin{bmatrix} S_{11}^R & S_{12}^R \\ S_{21}^R & S_{22}^R \end{bmatrix}$$

$$S_{11}^R = S_{22}^R = \frac{(R_{stab} + Z_0) - Z_0}{(R_{stab} + Z_0) + Z_0}$$
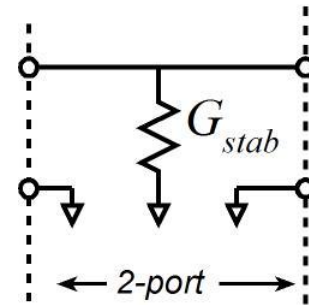
$$S_{21}^R = S_{12}^R = \frac{2Z_0}{R_{stab} + 2Z_0}$$



* stabilizer * S - parameters : S_{ij}^G

$$[S_{ij}^G] = \begin{bmatrix} S_{11}^G & S_{12}^G \\ S_{21}^G & S_{22}^G \end{bmatrix}$$

$$S_{11}^G = S_{22}^G = \frac{(G_{stab} + Y_0) - Y_0}{(G_{stab} + Y_0) + Y_0}$$

$$S_{21}^G = S_{12}^G = \frac{2Y_0}{G_{stab} + 2Y_0}$$

Key point is reciprocity : $S_{12}^R = S_{21}^R$ and $S_{12}^G = S_{21}^G$

What Gain Do We Get After Stabilization ?

S_{ij}^T : transistor S - parameters



S_{ij}^R : stabilizer S - parameters

\tilde{S}_{ij} : stabilized transistor S - parameters

by inspection (Mason's gain rules) :

$$\tilde{S}_{21} = \frac{b_2}{a_1} = \frac{S_{21}^R S_{21}^T}{1 - S_{22}^R S_{11}^T} \quad \tilde{S}_{12} = \frac{b_1}{a_2} = \frac{S_{12}^R S_{12}^T}{1 - S_{22}^R S_{11}^T}$$

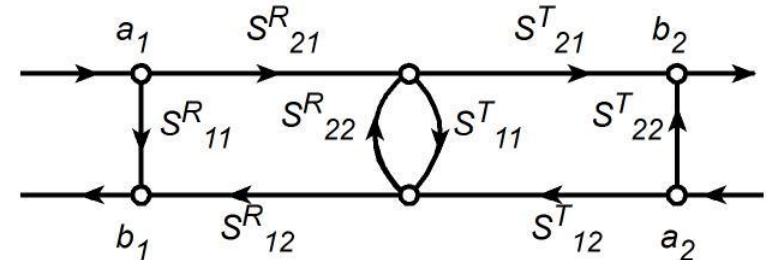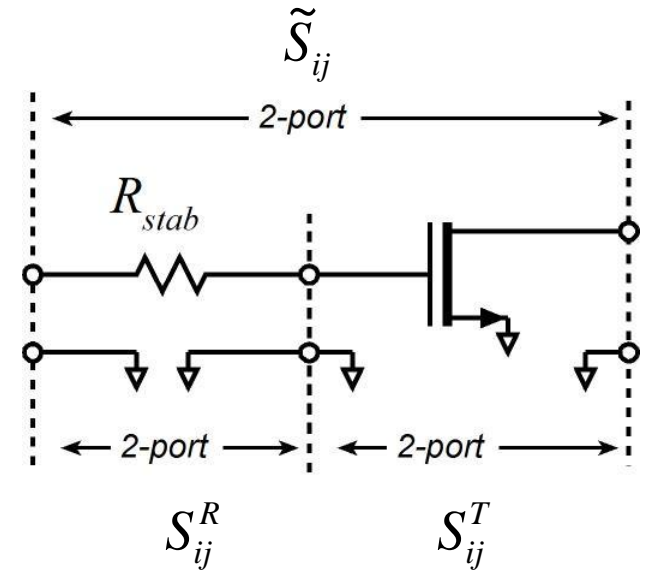
$$\frac{\tilde{S}_{21}}{\tilde{S}_{12}} = \frac{S_{21}^R}{S_{12}^R} \cdot \frac{S_{21}^T}{S_{12}^T} = \frac{S_{21}^T}{S_{12}^T} !!!$$



Consider More Carefully

Any 2 cascaded blocks follow this relationship :
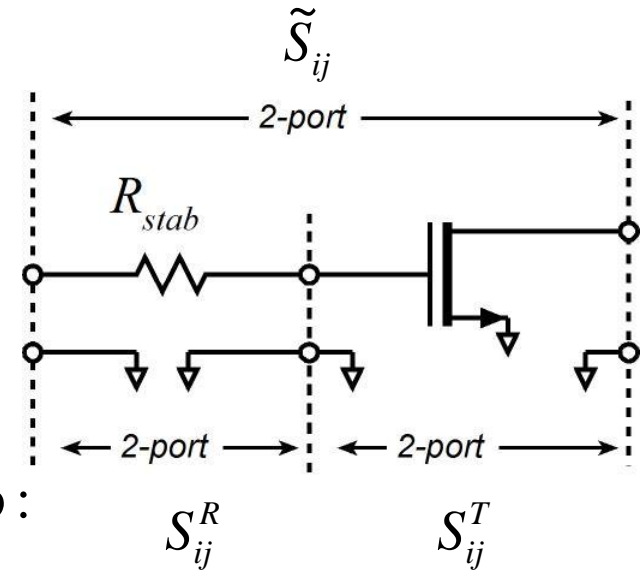
$$\frac{\tilde{S}_{21}}{\tilde{S}_{12}} = \frac{S_{21}^R}{S_{12}^R} \cdot \frac{S_{21}^T}{S_{12}^T}$$



Passive reciprocal networks follow this relationship :

$$\frac{S_{21}^R}{S_{12}^R} = 1$$


We therefore find :

$$\frac{\tilde{S}_{21}}{\tilde{S}_{12}} = \frac{S_{21}^T}{S_{12}^T}$$

Stabilizing does not change the ratio of S_{21} to S_{12} .

What Gain Do We Get After Stabilization ?

Before stabilization

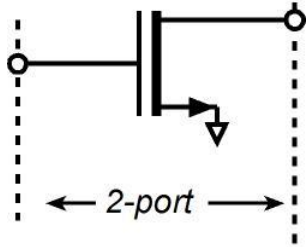


* original * S - parameters : S_{ij}

$$G_{\max} = \left\| \frac{S_{21}}{S_{12}} \right\| \cdot \left(K - \sqrt{K^2 - 1} \right)$$

= undefined (unstable)

After stabilization

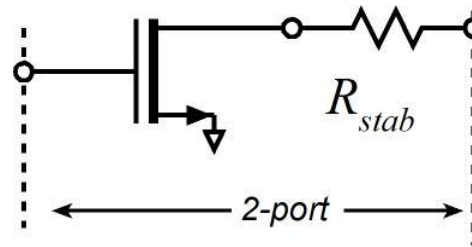

* changed * S - parameters : \tilde{S}_{ij}

$$G_{\max} = \left\| \frac{\tilde{S}_{21}}{\tilde{S}_{12}} \right\| \cdot \left(\tilde{K} - \sqrt{\tilde{K}^2 - 1} \right)$$

but $\tilde{K} = 1$ (just stable)
and $\tilde{S}_{21} / \tilde{S}_{12} = S_{21} / S_{12}$

$$G_{\max_stable} = \left\| \frac{S_{21}}{S_{12}} \right\|$$

Maximum stable gain = $G_{\max_stable} = \left\| S_{21} \right\| / \left\| S_{12} \right\|$

What Does Maximum Stable Gain Mean ???

The term : " Maximum stable gain" is too short to be precise.


Maximum stable gain is the maximum gain we can obtain

if we also guarantee that changing Z_S and Z_L

will not make the amplifier oscillate.

Design Tools: Power Gain Definitions

Transducer Gain

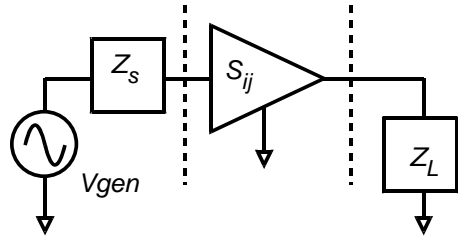


$$G_T = P_{load} / P_{av,gen}$$

$$= \frac{\text{load power}}{\text{power available from generator}}$$

= general - case gain

Available Gain

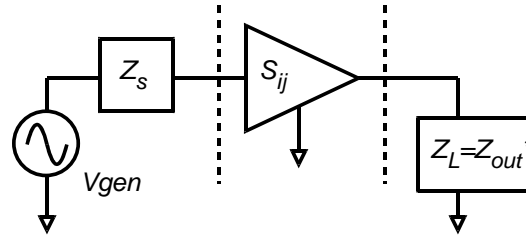


$$G_A = P_{av,a} / P_{av,gen}$$

$$= \frac{\text{power available from amplifier}}{\text{power available from generator}}$$

= gain with output matched

Insertion Gain

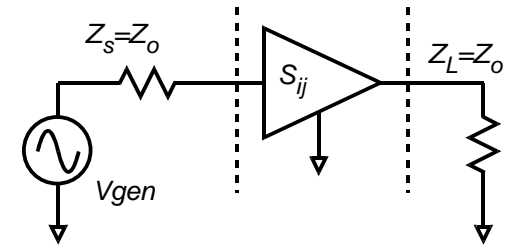


$$\|S_{21}\|^2 = P_{av,a} / P_{av,gen}$$

$$= \frac{\text{power delivered to } Z_o \text{ load}}{\text{power available from } Z_o \text{ generator}}$$

= gain in a 50 Ohm environment

Operating Gain

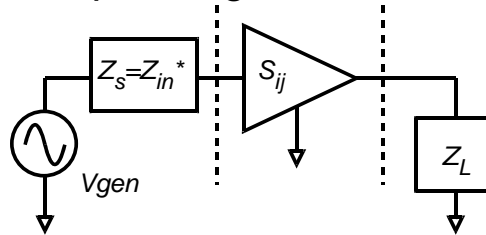


$$G_P = P_{load} / P_{gen,delivered}$$

$$= \frac{\text{load power}}{\text{power delivered from generator}}$$

= gain with input matched

Maximum Available Gain

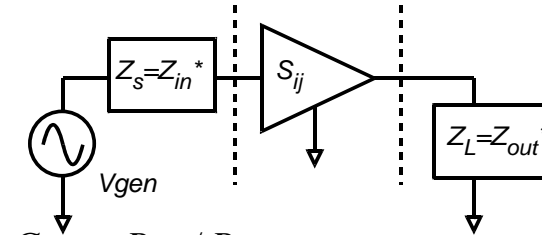


$$G_{Max} = P_{av,a} / P_{gen,delivered}$$

$$= \frac{\text{power available from amplifier}}{\text{power delivered from generator}}$$

= gain with both ports matched
...MAG may not exist...

After impedance-matching:

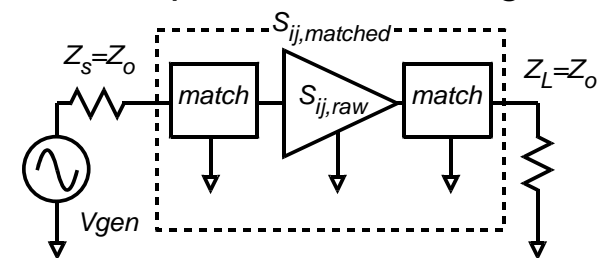

$$\|S_{21,matched}\|^2 = G_{max,raw}$$

$$S_{11,matched} = S_{22,matched} = 0$$

...but only if unconditionally stable...

Unilateral Power Gain


1) Cancel device feedback with external lossless feedback

$$\rightarrow Y_{12} = S_{12} = 0$$

2) Match input and output

Resulting power gain is Mason's Unilateral Gain

$$U = \frac{|Y_{21} - Y_{12}|^2}{4(G_{11}G_{22} - G_{21}G_{12})}$$

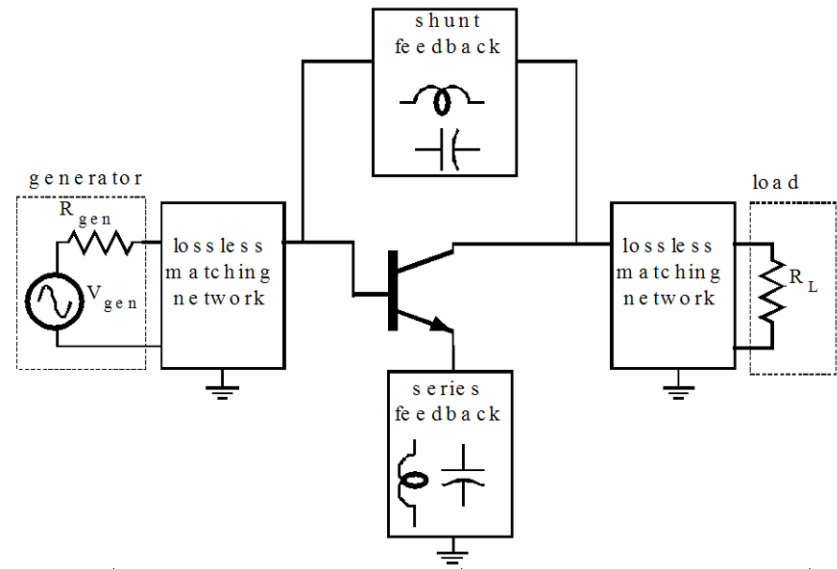

Monolithic amplifiers are not easily made unilateral

→ U mostly of historical relevance to IC design

For simple BJT model, U rolls off at -20 dB/decade


→ U useful for extrapolation to find f_{\max}

In III - V FETs, U shows peak from $C_{ds} - R_s - R_d$ interaction

→ U hard to use for f_{\max} extrapolation


For bulk CMOS, C_{ds} is shielded by substrate

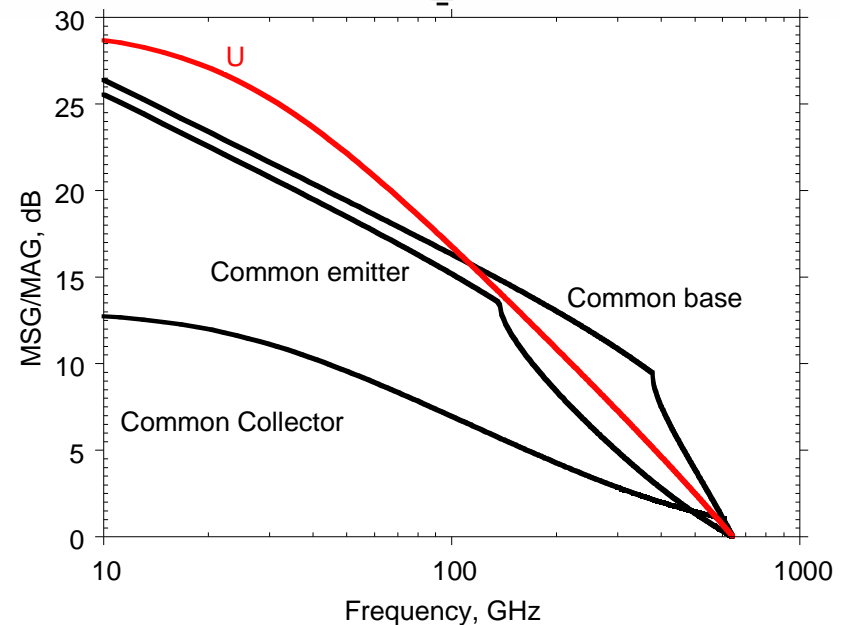→ U should be OK for f_{\max} extrapolation




Design Tools: Stability Factors, Stability Circles
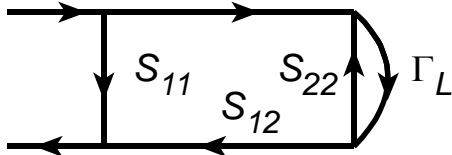
$$\Gamma_{in} = S_{11} + \Gamma_L \frac{S_{12}S_{21}}{1 - S_{22}\Gamma_L}$$




Load Stability Circle

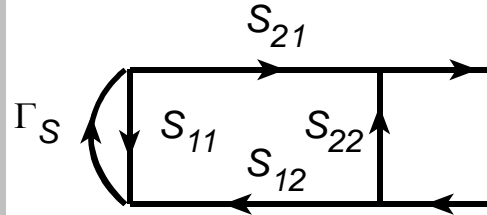
$$\Gamma_{out} = S_{22} + \Gamma_S \frac{S_{12}S_{21}}{1 - S_{11}\Gamma_S}$$



Source Stability Circle

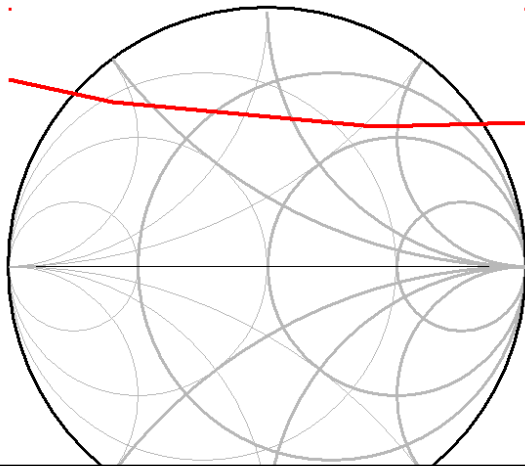

Values of Γ_L which make
 $\|\Gamma_{in}\| = 1 \rightarrow$ beyond lies negative R_{in}

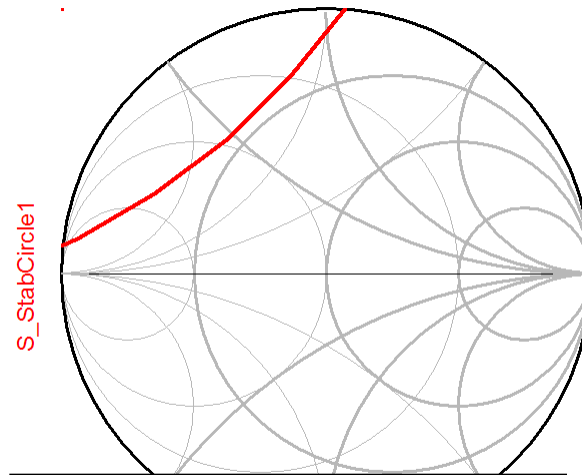

Values of Γ_S which make
 $\|\Gamma_{out}\| = 1 \rightarrow$ beyond lies negative R_{out}

Unconditionally stable


(stable with all (Γ_L, Γ_S) if :

K = Rollet stability factor

$$= \frac{1 - |S_{11}|^2 - |S_{22}|^2 + \det^2[S]}{2|S_{21}S_{12}|} > 1$$

and B = stability measure

$$= 1 - |S_{11}|^2 - |S_{22}|^2 - \det^2[S] > 0$$


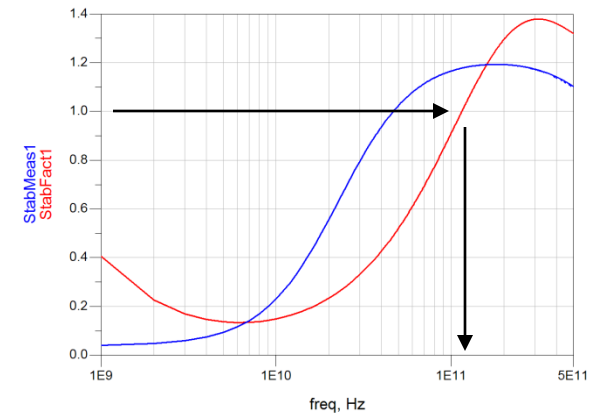


Negative port impedance \rightarrow negative- R oscillator
 Tuning for highest gain \rightarrow infinite gain (oscillation)

Design Tools: Maximum Stable Gain


Maximum stable gain = MSG

$$= \frac{|S_{21}|}{|S_{12}|} = \frac{|Y_{21}|}{|Y_{12}|} = \frac{|Z_{21}|}{|Z_{12}|}$$


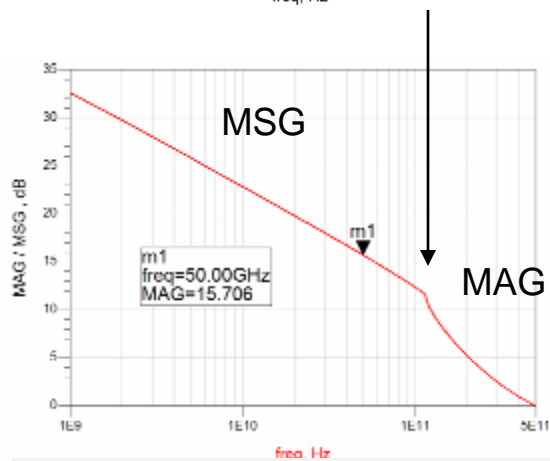
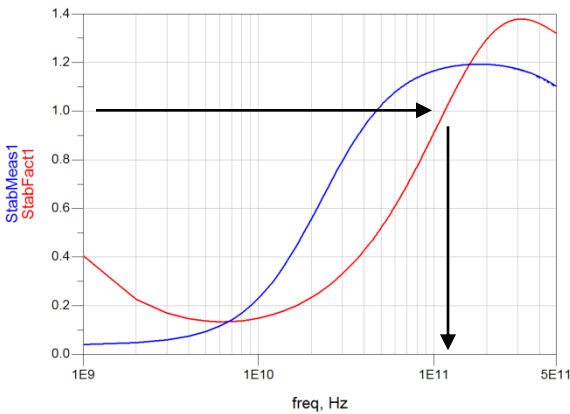


Adding series/shunt resistance
excludes source or load
from unstable regions → stabilizes



circles at 50 GHz

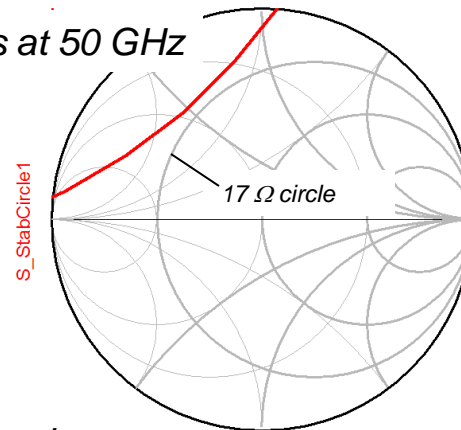

stabilization
methods

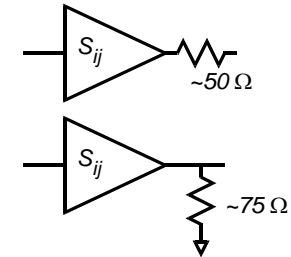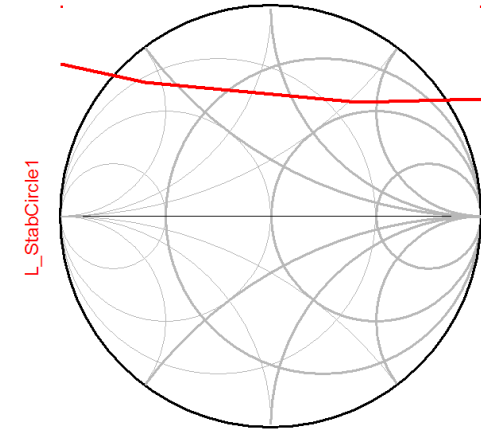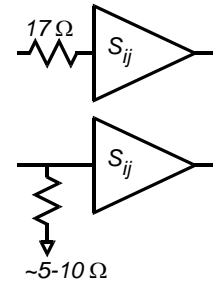



results

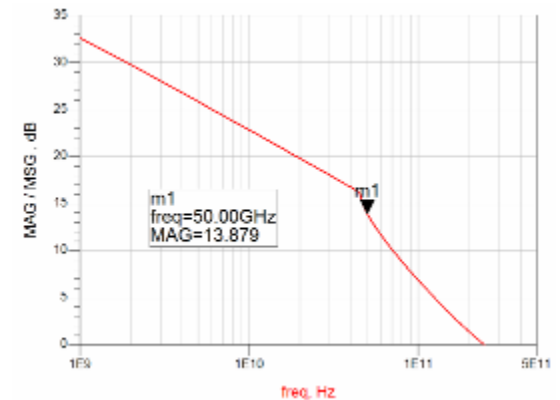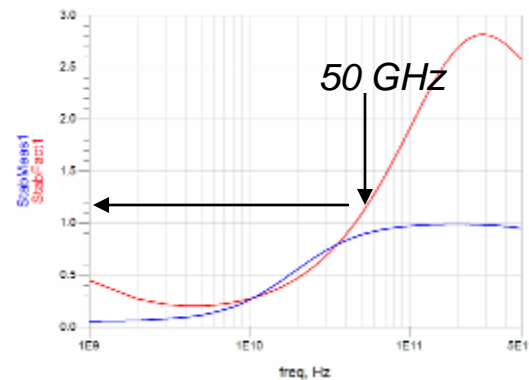



Design Procedure: Simple Gain-Matched Amplifier

First:
stabilize at the design frequency


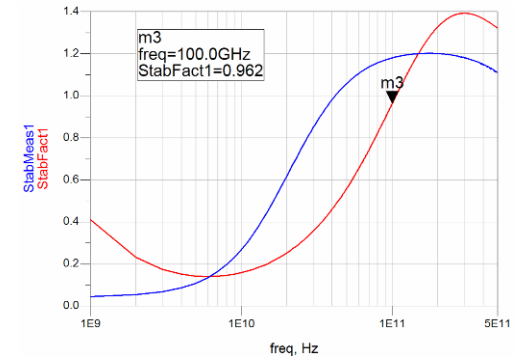
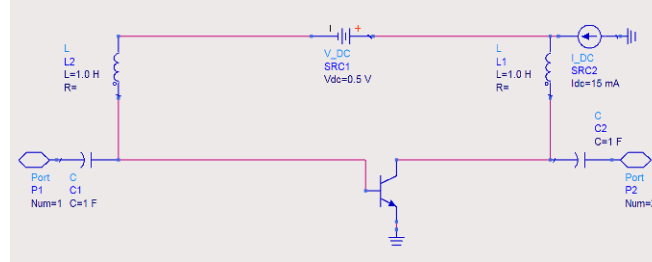
---device is potentially unstable
at 100 GHz design frequency



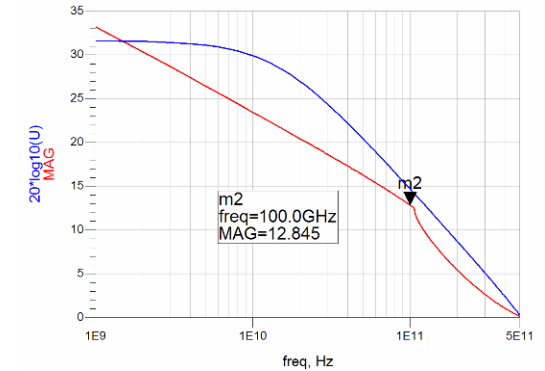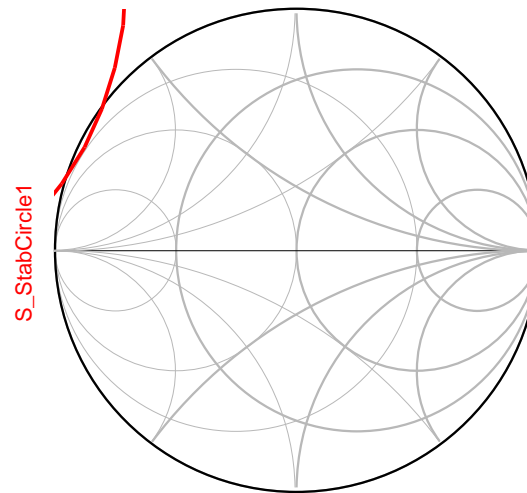source stability circle:
~5 Ohm on input will
overstabilize the device



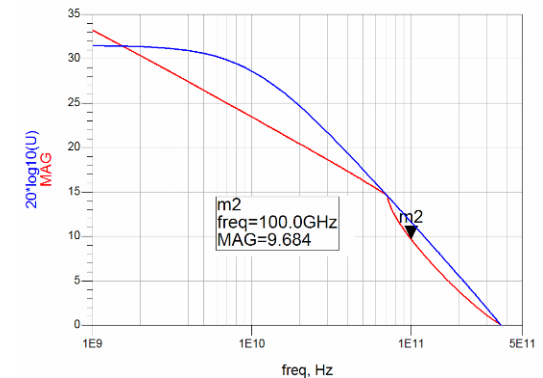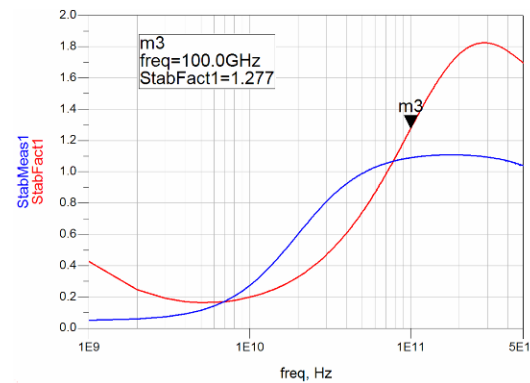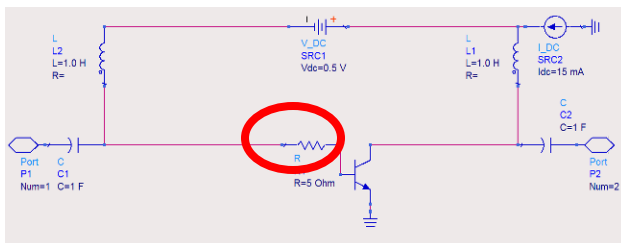After stabilizing
(slightly over-stabilizing)




Design Procedure: Simple Gain-Matched Amplifier

Second:

Determine required interface impedances

The G_a & G_p circles define the source & load impedances which the transistor must see

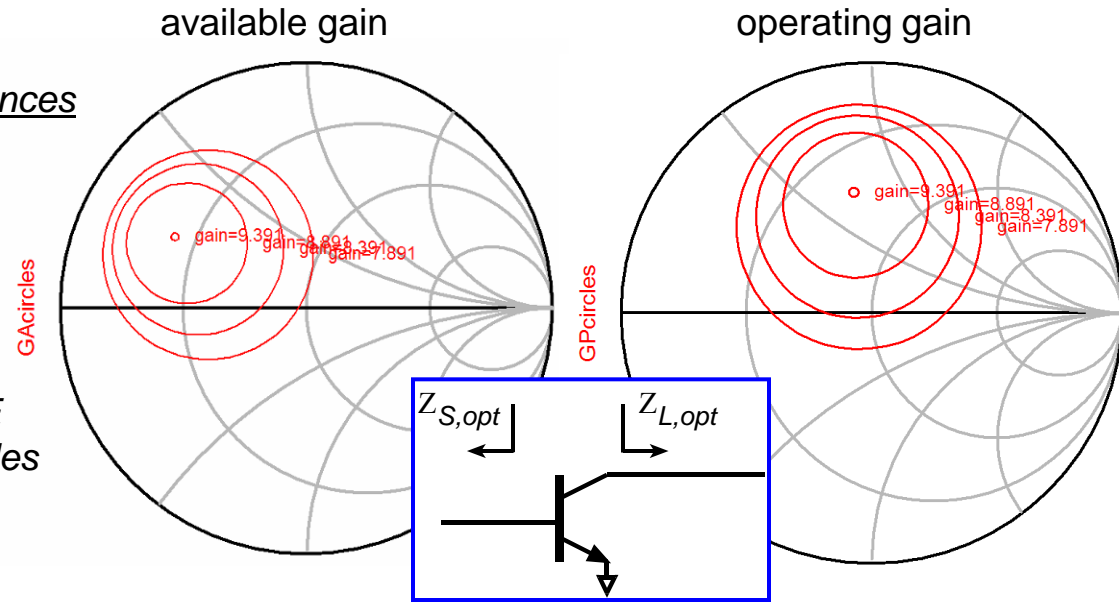
...it is necessary to **OVERSTABILIZE** the device to move the G_a & G_p circles towards the Smith chart center




Third:

Design Input & Output Tuning Networks

...to provide these impedances...

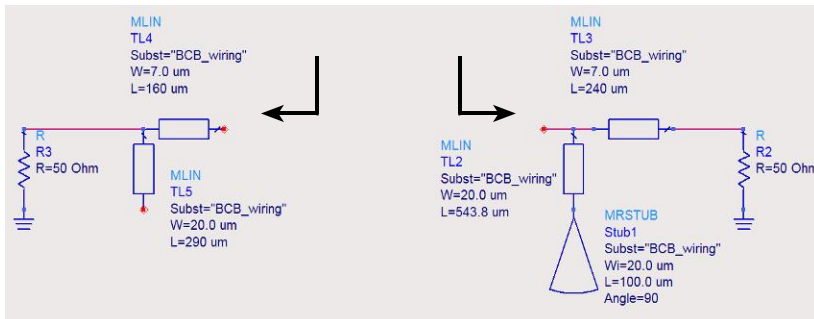


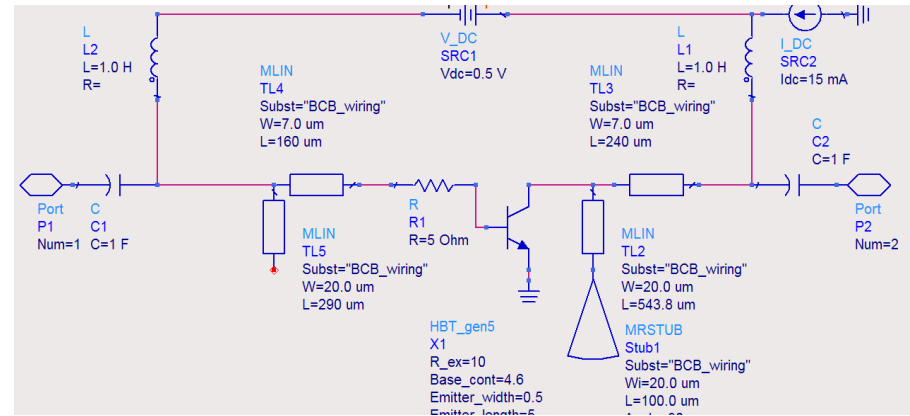...added to device, the amplifier is not yet complete...




Design Procedure: Simple Gain-Matched Amplifier


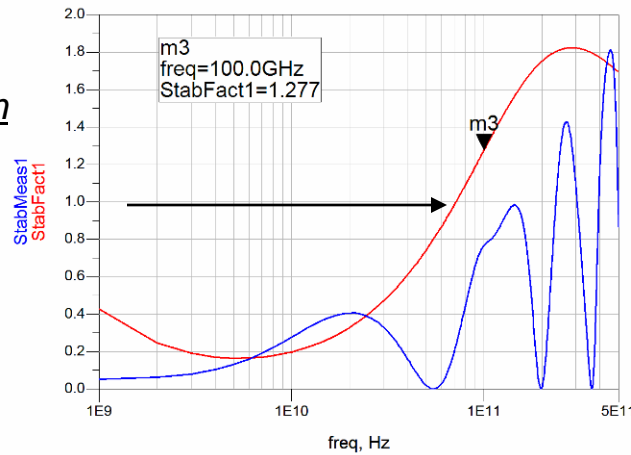
Forth:
Add out-of-band stabilization
 potentially unstable
 below 75 GHz



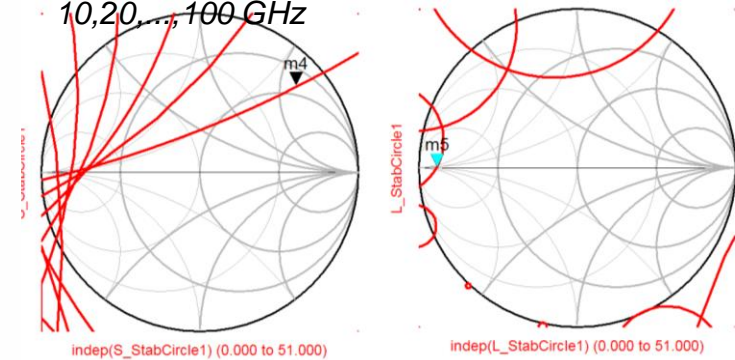
source & load stability circles &
 10,20,...,100 GHz



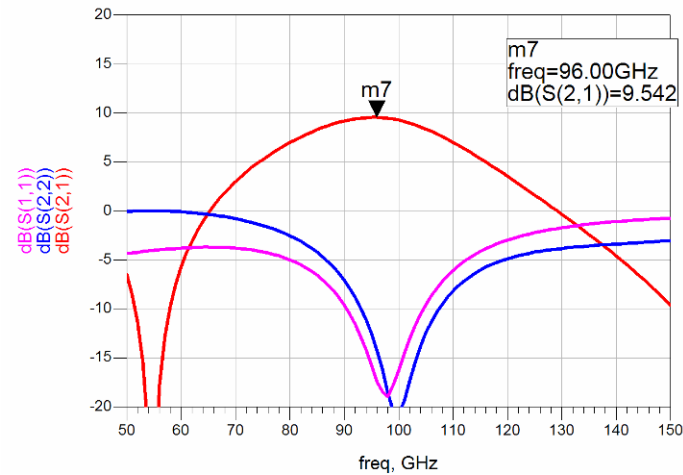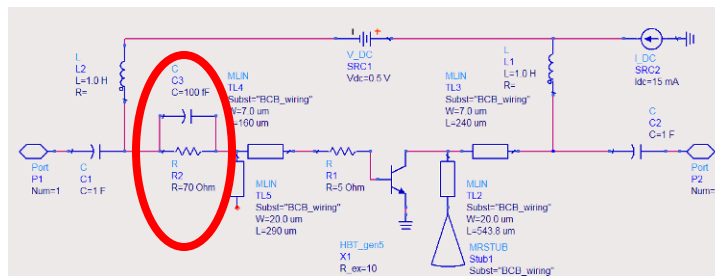with frequency-selective
 series stabilization



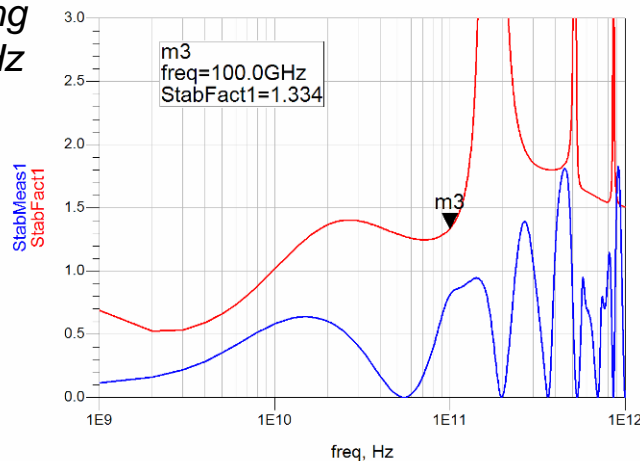...caused only slight mistuning
 & slight gain drop @ 100 GHz



...and is unconditionally
 stable above 10 GHz

Design Procedure: Effect of Line Losses



Finally:
adjusting for line losses

high line skin effect losses → reduced gain


but line losses also increase stability factor

loss in gain are partly recovered
by reducing stabilization resistance &
re-tuning the design

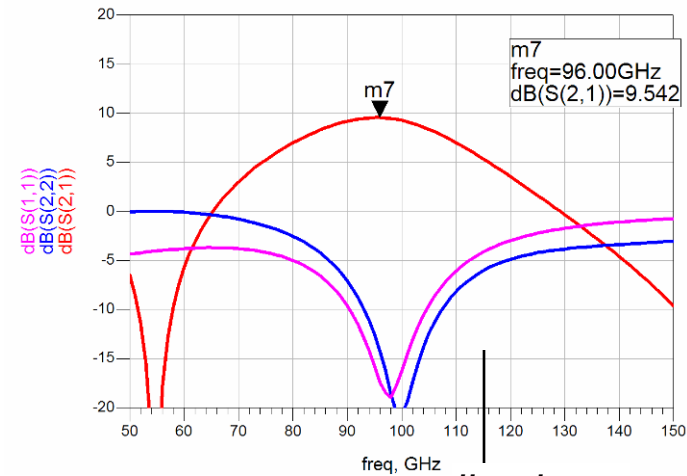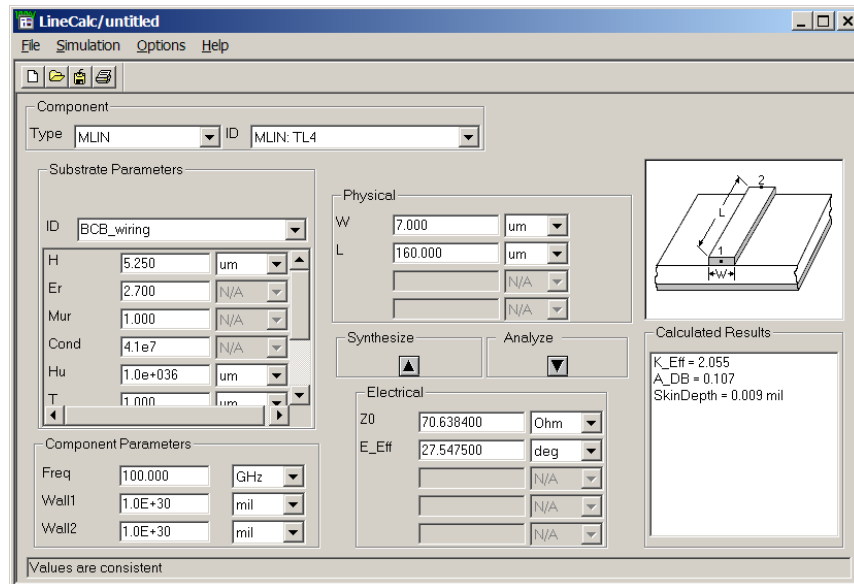--no analytical procedure; just component tweaking





line losses

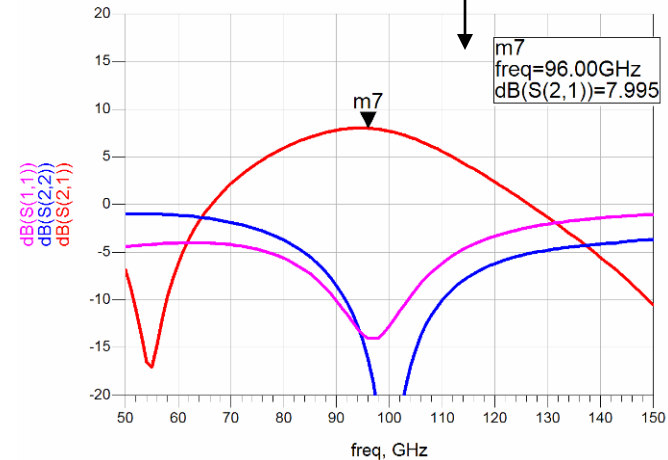





line losses have severe impact
...in VLSI wiring environment
...particularly at 50 + GHz
...particularly with high-power amplifiers

Tuned Amplifier Examples

3-stage cascode in 180 nm CMOS

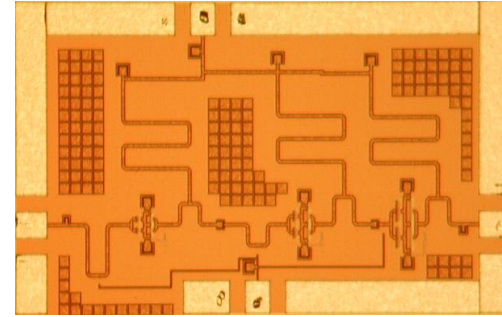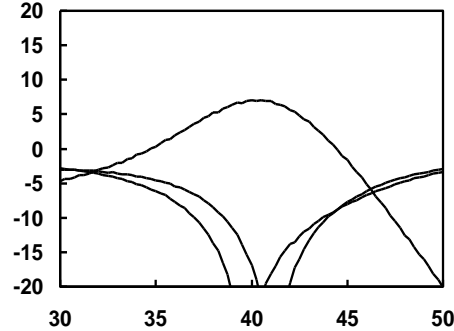

III-V HBT small-signal amplifiers

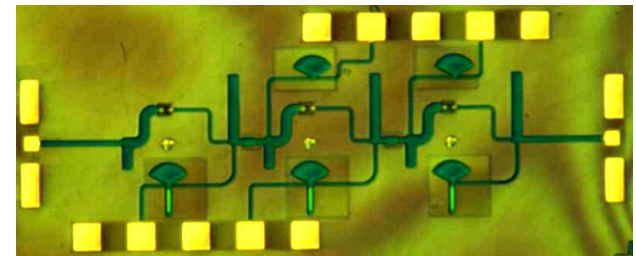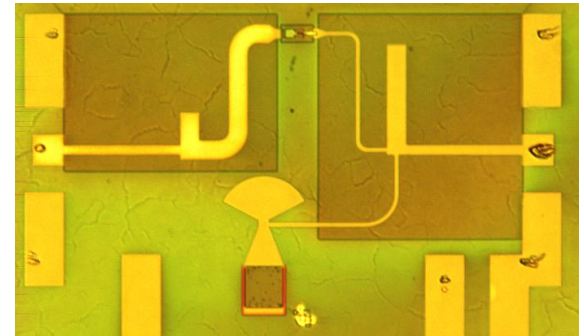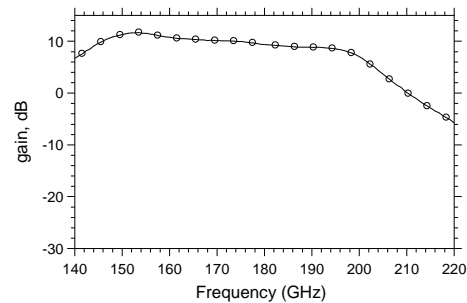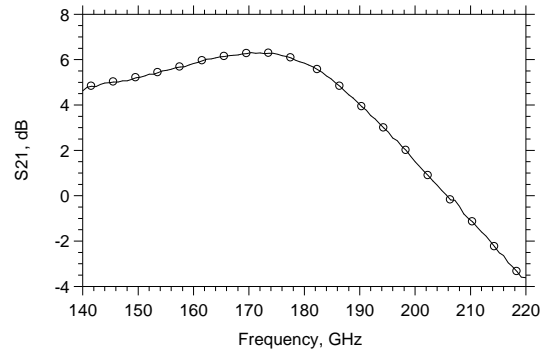

Note: simple gain-tuned amplifiers → limited applications

Transmitters need power amplifiers: need output loadline-match, not gain-match

Receivers need low-noise amplifiers: need input noise-match, not gain-match