

---

# ***ECE 145A / 218 C, notes set 1: Transmission Line Properties and Analysis***

***Mark Rodwell***

***University of California, Santa Barbara***

# Transmission Line Analysis

---

Geometries

Characteristic Impedances

Time Domain Analysis

Lattice Diagrams

Frequency Domain analysis

Reflection coefficients

Movement of Reference Plane

Impedance vs Position

Smith Chart




Standing Waves

Solving wave equations quickly




# **types of transmission lines**

# Transmission Lines for On-Wafer Wiring

microstrip line

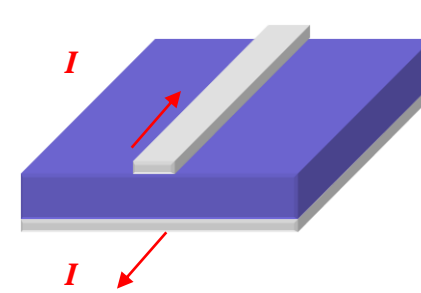
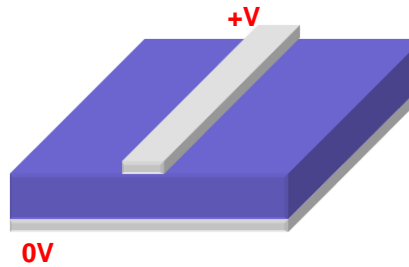
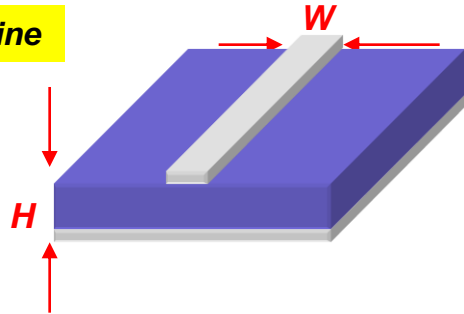


coplanar waveguide

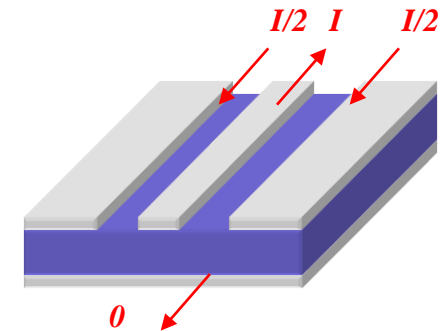
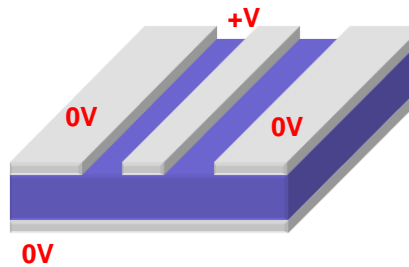
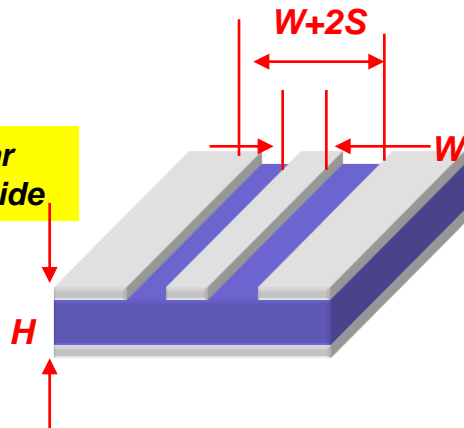


# Transmission Lines for On-Wafer Wiring


coplanar  
strips

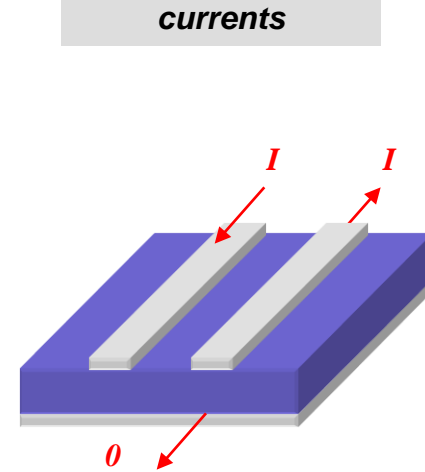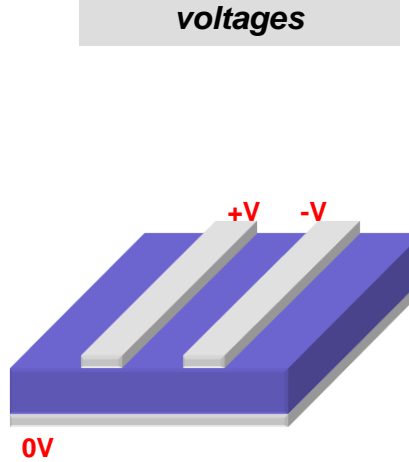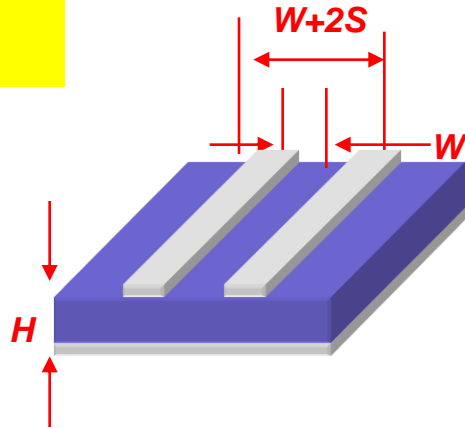

slotline

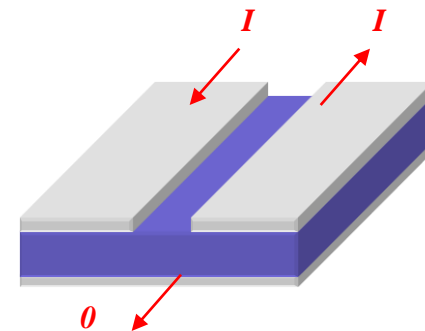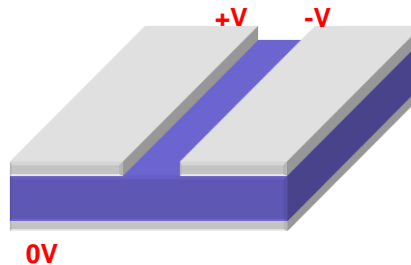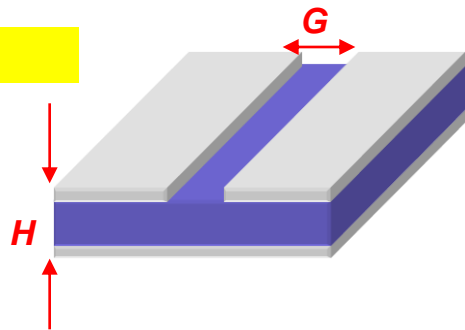


# Substrate Microstrip Line

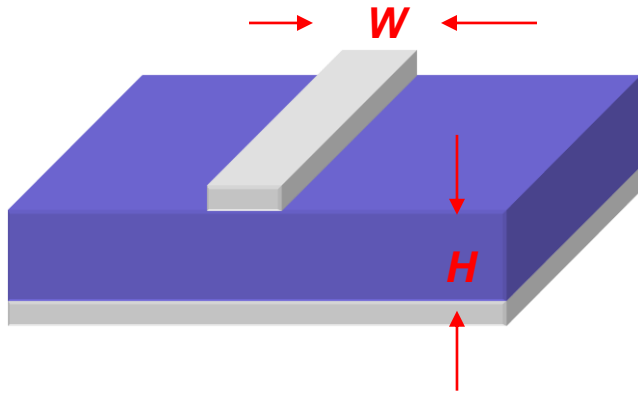

Dominant Transmission medium in  
III-V microwave & mm-wave ICs


Key advantage: IC interconnects  
have very low ground-lead  
inductance

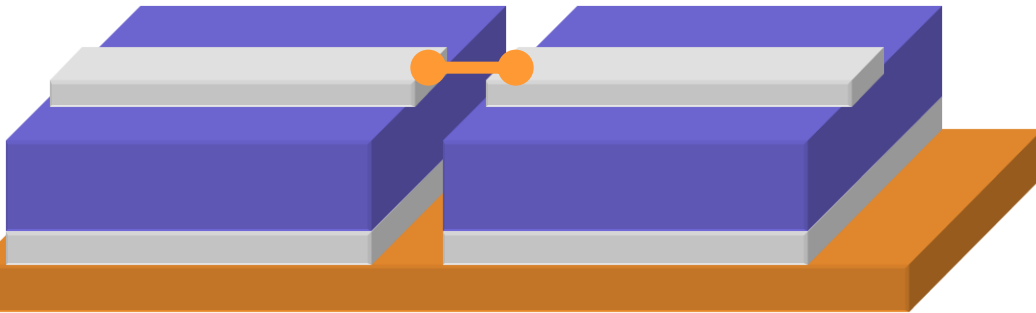Ground-lead inductance:  
-leads to ground-bounce  
-is Miller-multiplied by IC gain



Key problems:  
through-wafer grounding holes (vias)  
coupling to TM modes in substrate

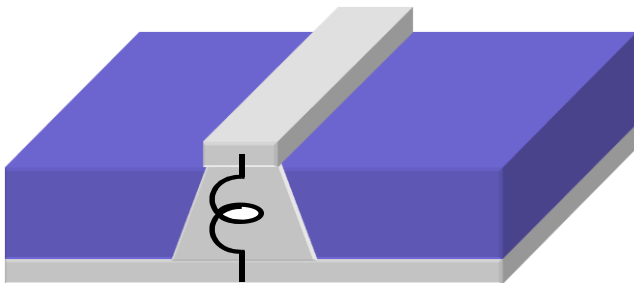Via inductance forces progressively  
thinner wafers at higher frequencies.



**basic theory**

**L, C, Zo, velocity, Gamma**

# Transmission Lines


---

A pair of wires with *regular spacing, dielectric loading* along the length.

These have inductance per unit length and capacitance per unit length.


Forward and reverse waves propagate.

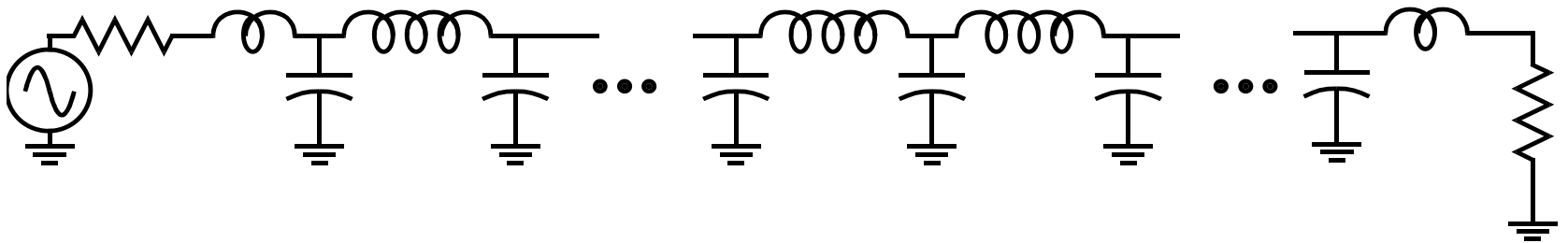Reflections will occur if lines are not correctly terminated





# Transmission Lines: Basic Theory

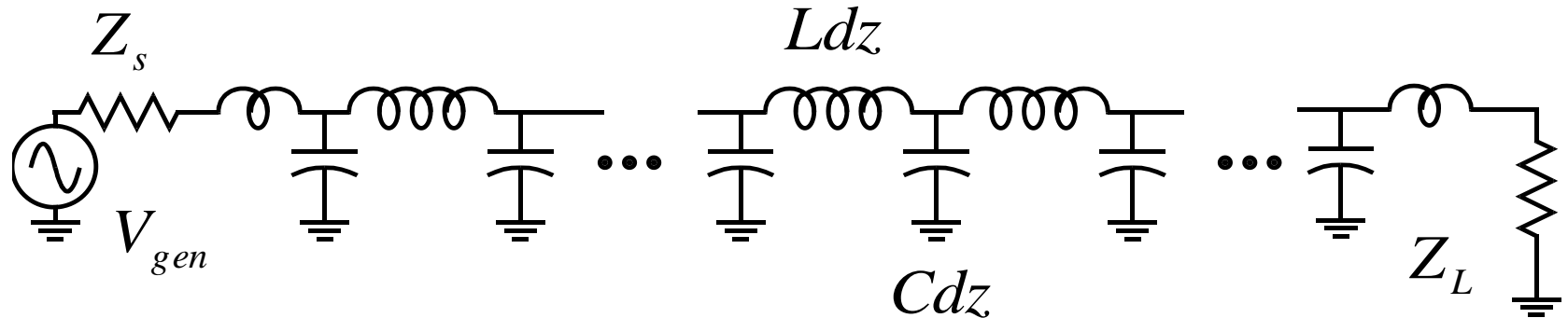

From basic nodal analysis of line :

$$(dV / dz) = -L(dI / dt) \quad \text{and}$$

$$(dI / dz) = -C(dV / dt) \quad \text{from which we find}$$


$$V(z, t) = V^+(t - z/v) + V^-(t + z/v)$$

$$I(z, t) = \frac{V^+(t - z/v)}{Z_o} - \frac{V^-(t + z/v)}{Z_o}$$

where

$$Z_o = \sqrt{L/C} \quad \text{and} \quad v = 1/\sqrt{LC}$$

# Forward and Reverse Waves

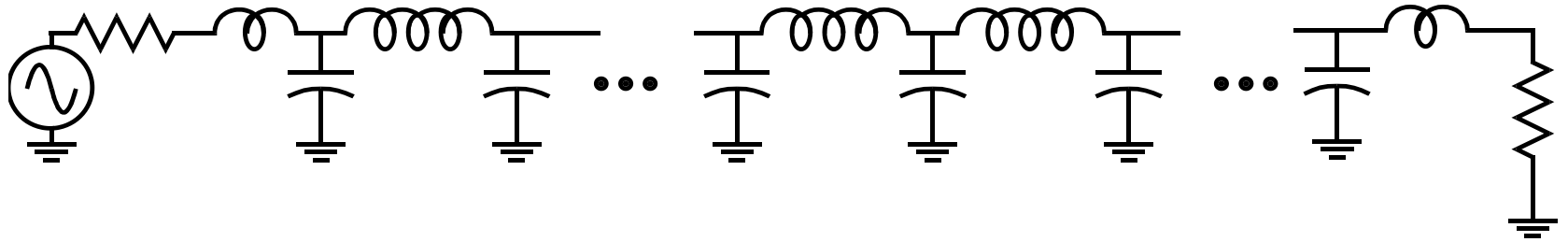


$V^+(t - z/v)$  voltage in forward wave

$+ V^-(t + z/v)$  voltage in reverse wave

$\frac{V^+(t - z/v)}{Z_o}$  current in forward wave

$-\frac{V^-(t + z/v)}{Z_o}$  current in reverse wave

# Velocity and Characteristic Impedance

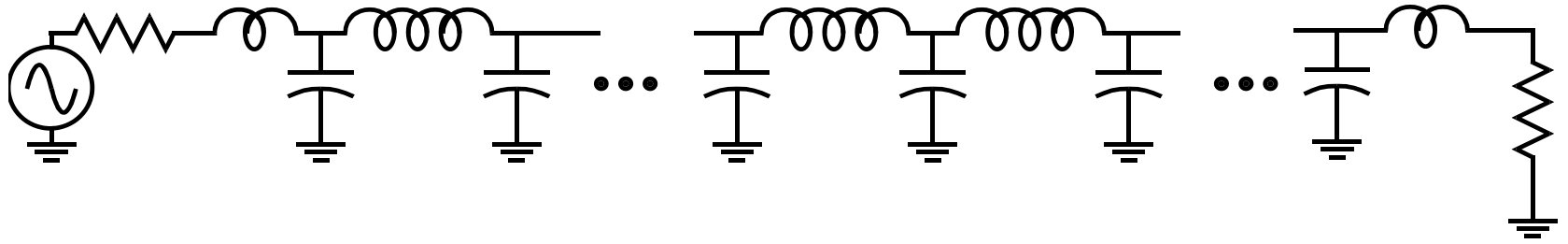

$$Z_o = \sqrt{L/C} \quad \text{and} \quad v = 1/\sqrt{LC}$$


$L$  and  $C$  are here quantities per unit length.

$$v = c / \sqrt{\epsilon_{r,eff}}$$

where  $c$  is the speed of light and

$\epsilon_{r,eff}$  is the effective dielectric constant of the line

# Reflections

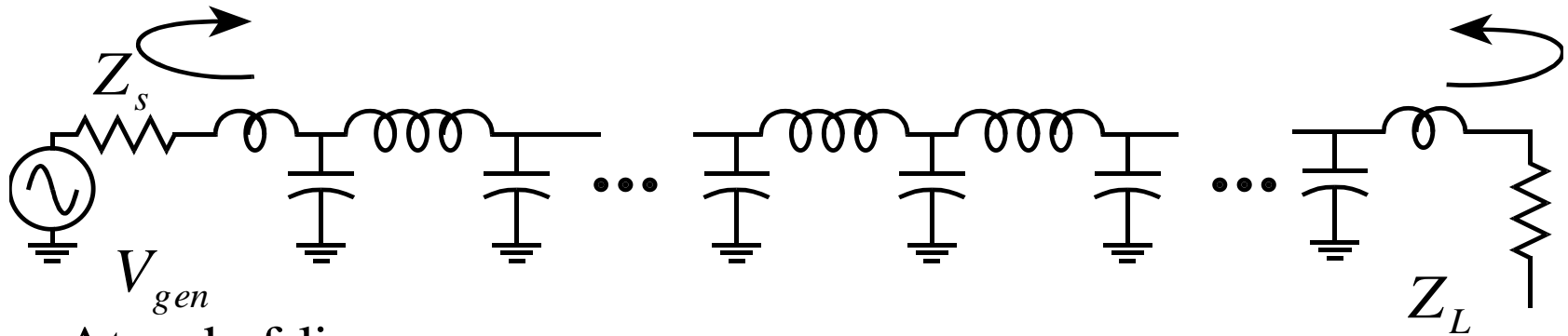

At end of line :

$$V^- = \Gamma_l V^+ \quad \text{where } \Gamma_l = \frac{(Z_l/Z_o) - 1}{(Z_l/Z_o) + 1}$$


At beginning of line :

$$V^+ = \Gamma_s V^- + T_s V_{gen} \quad \text{where } \Gamma_s = \frac{(Z_s/Z_o) - 1}{(Z_s/Z_o) + 1}$$

$$\text{and } T_s = \frac{Z_o}{Z_o + Z_s}$$

Need good terminations to prevent line reflections and ringing
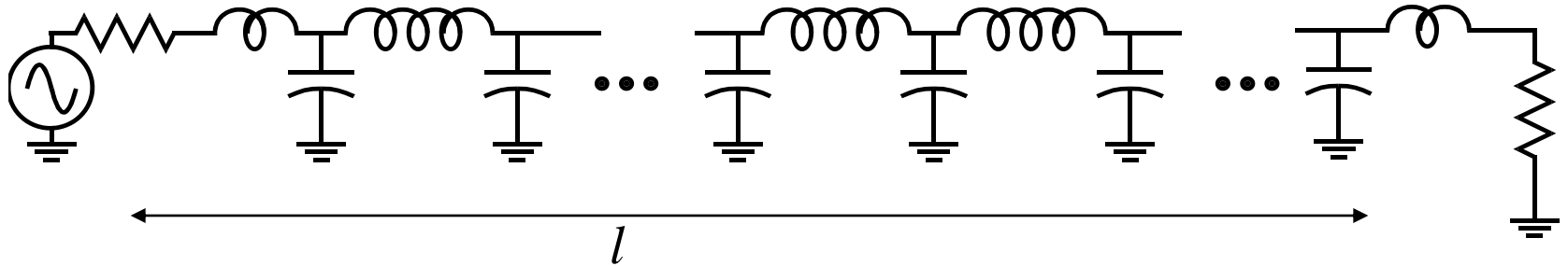
# Total inductance & capacitance in a length of line



If total line length is  $l_{length}$

Then total capacitance in that length is


$$C_{length} = \frac{\tau}{Z_o}$$

and total inductance in that length is

$$L_{length} = \tau Z_o$$

where  $\tau = l_{length} / v$  = "speed of light delay" on the line
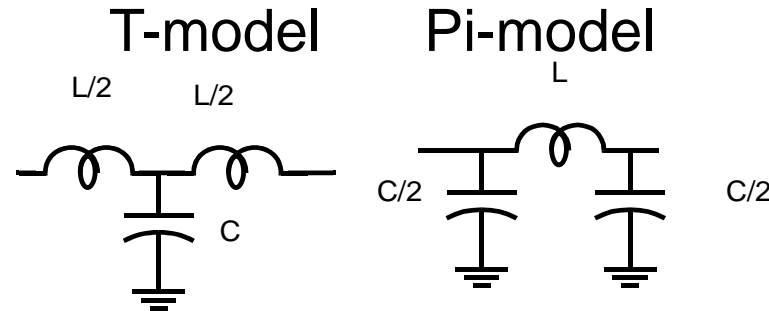
# Lumped models of very short transmission lines




If total line length  $l_{length}$  is much less than a wavelength  
 or total line delay  $\tau = l_{length}/v$  is much less than  $1/f_{signal}$   
 or total line delay  $\tau$  is much less than pulse risetime  
 then the line can be approximated as a T or  $\pi$  section

$$C_{length} = \frac{\tau}{Z_o}$$


$$L_{length} = \tau Z_o$$

# Ladder models of moderately short transmission lines

## Pi-model synthesis

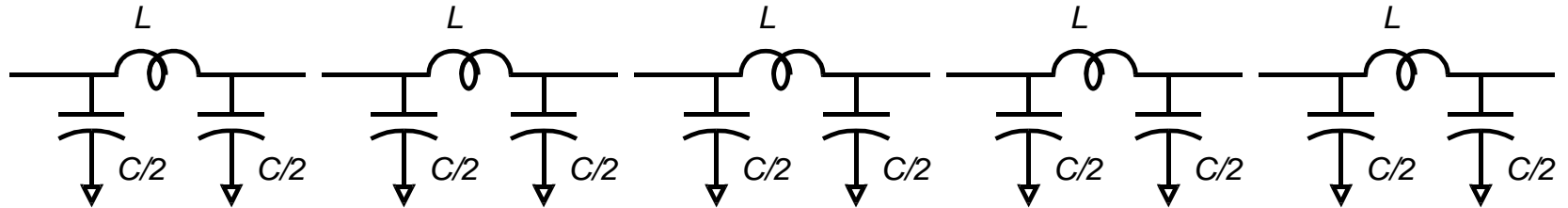

## T-model synthesis

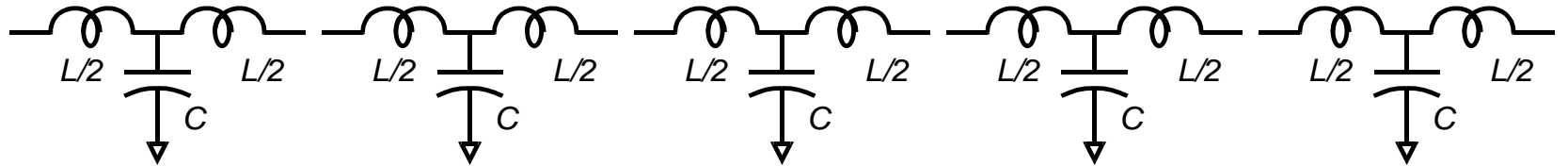

Clearly, we can break a line of any length into sections of length  $l_{line}$  such that  $\tau_{line} = l_{line} / v$  is much less than a signal period.


In this fashion a transmission - line can be modelled by an LC filter.

This is a frequent substitution in circuit simulations

# Microstrip Lines


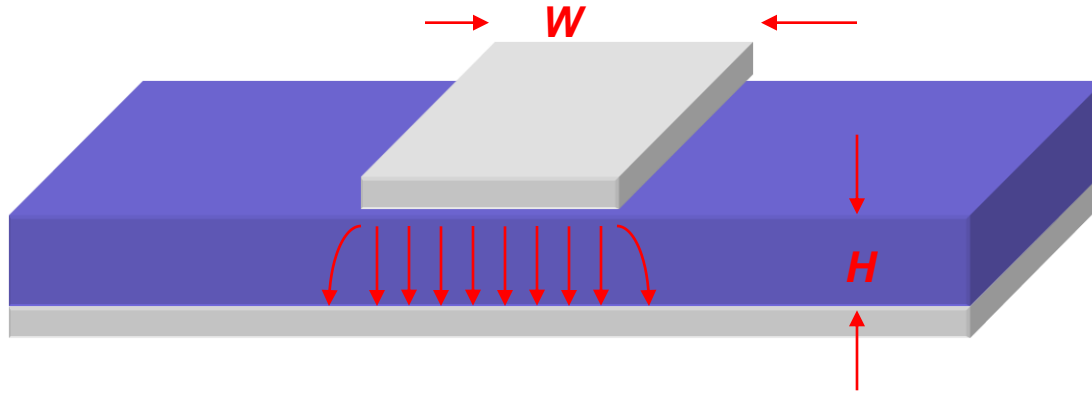
# Microstrip Line: Approximate Properties (1)




Wide line  $\rightarrow$  field mostly in dielectric. This gives :

$v = c / \epsilon_r^{1/2}$ , where  $c = 1 / \sqrt{\mu\epsilon}$  is the speed of light

$Z_0 = \eta_0 H / \epsilon_r^{1/2} W$ , where  $\eta_0 = \sqrt{\frac{\mu}{\epsilon}}$  is the free space wave impedance

(note: wide lines have problems)
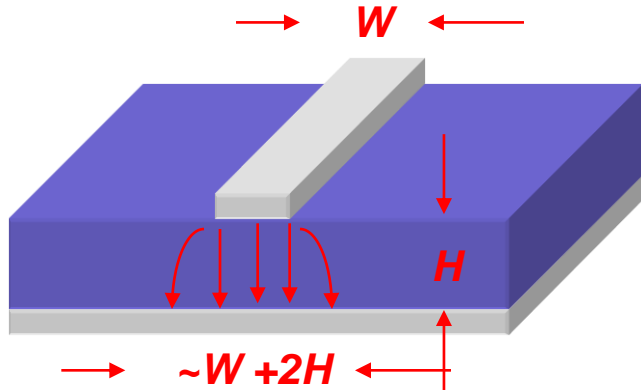
# Microstrip Line: Approximate Properties (2)



If the line is narrower, hand analysis only approximate

Effective width  $\approx W + 2H$

$Z_0 \cong \eta_0 H / \epsilon_r^{1/2} (W + 2H)$  only very approximately

$$v = c / \epsilon_{r,eff}^{1/2}$$

$\epsilon_{r,eff}$  lies somewhere between that of air and of the dielectric,

depending upon what proportion of the field is in air.

# **Lines in Time Domain**


# Lattice Diagrams = Echo Diagrams

First :

Analyze for impulse response

Then :

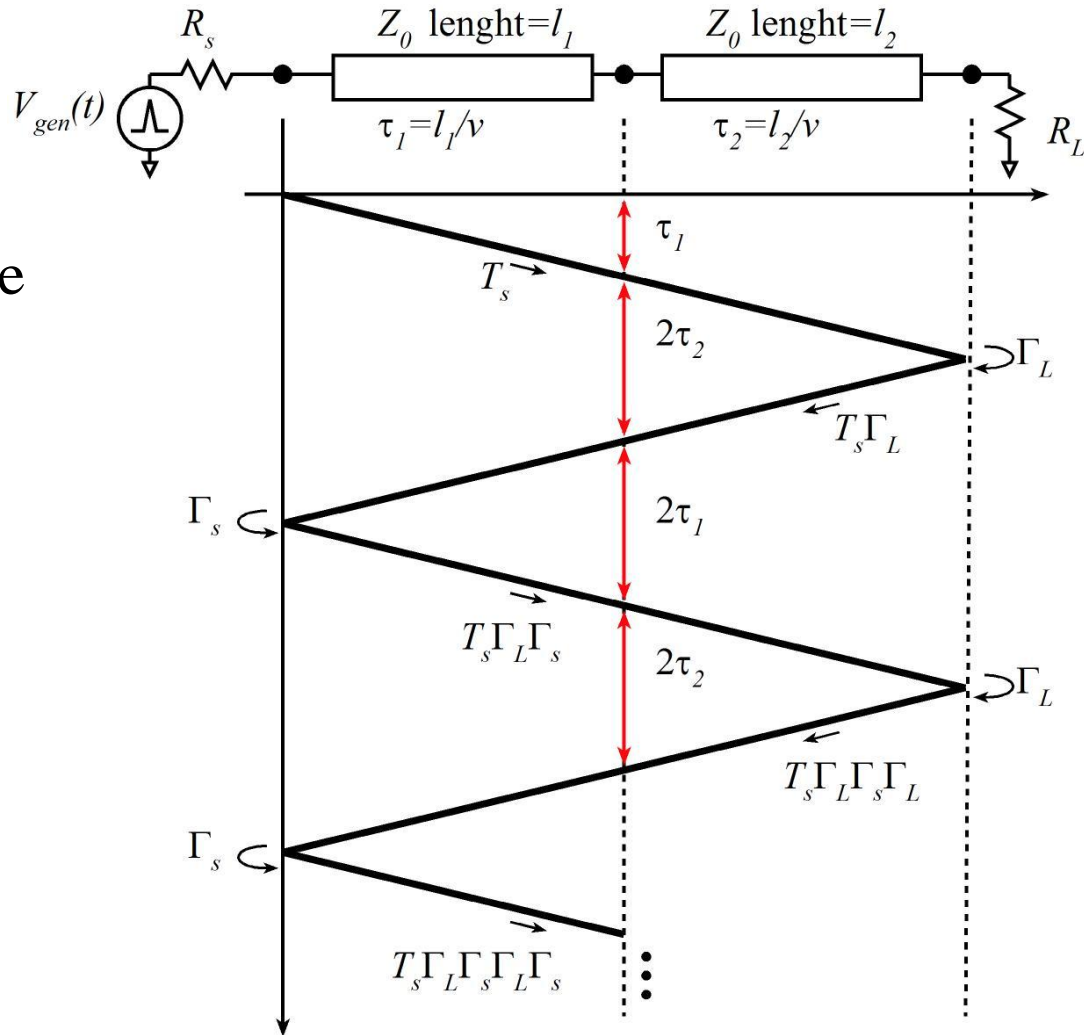Use convolution to find  
general response.




Recall : At end of line :

$$V^- = \Gamma_L V^+ \quad \text{where } \Gamma_L = \frac{(R_L/Z_o) - 1}{(R_L/Z_o) + 1}$$


At beginning of line :

$$V^+ = \Gamma_s V^- + T_s V_{gen} \quad \text{where } \Gamma_s = \frac{(R_s/Z_o) - 1}{(R_s/Z_o) + 1} \quad \text{and } T_s = \frac{Z_o}{Z_o + R_s}$$

# Lattice Diagrams = Echo Diagrams

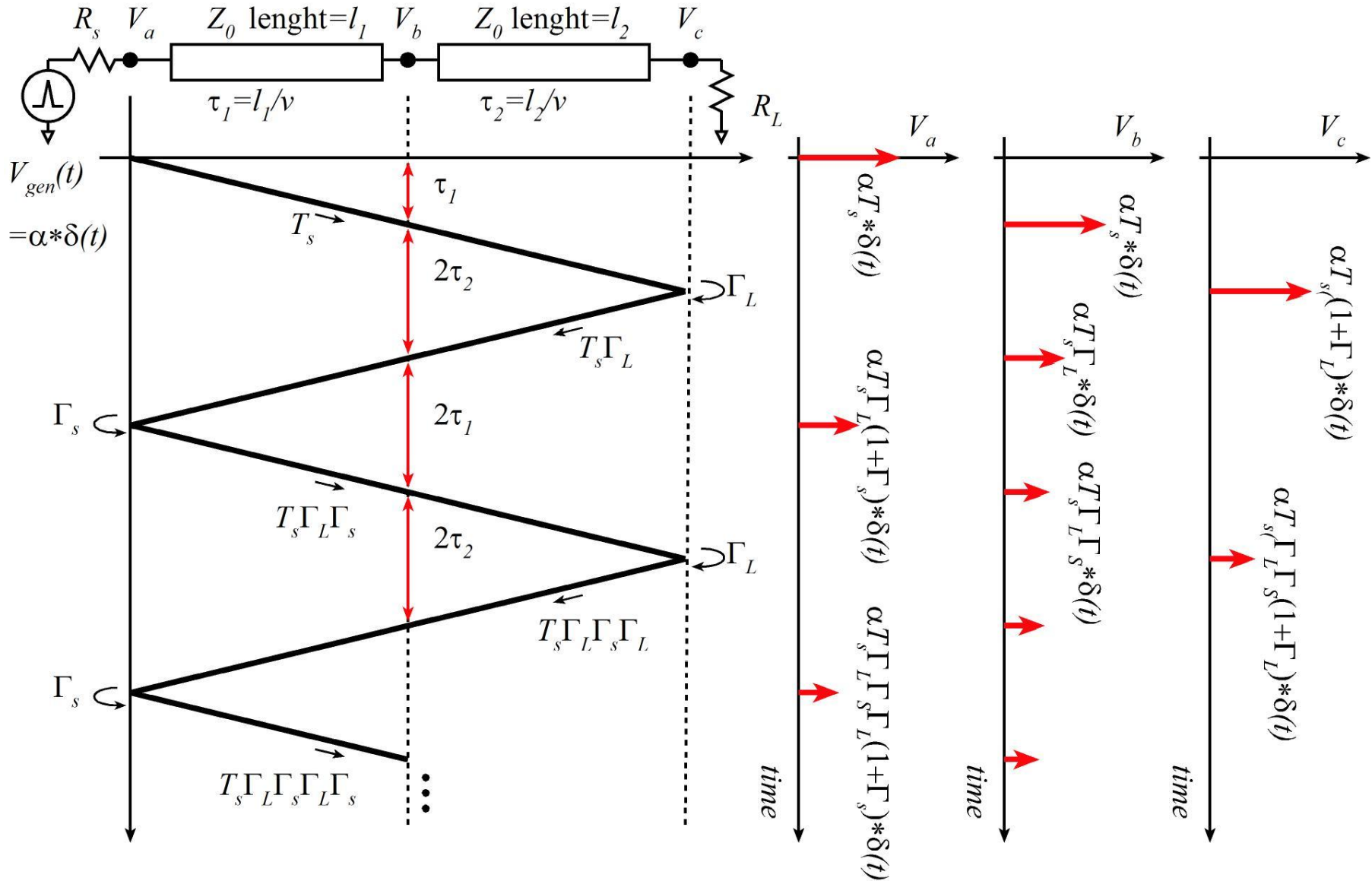


# Lattice Diagrams = Echo Diagrams

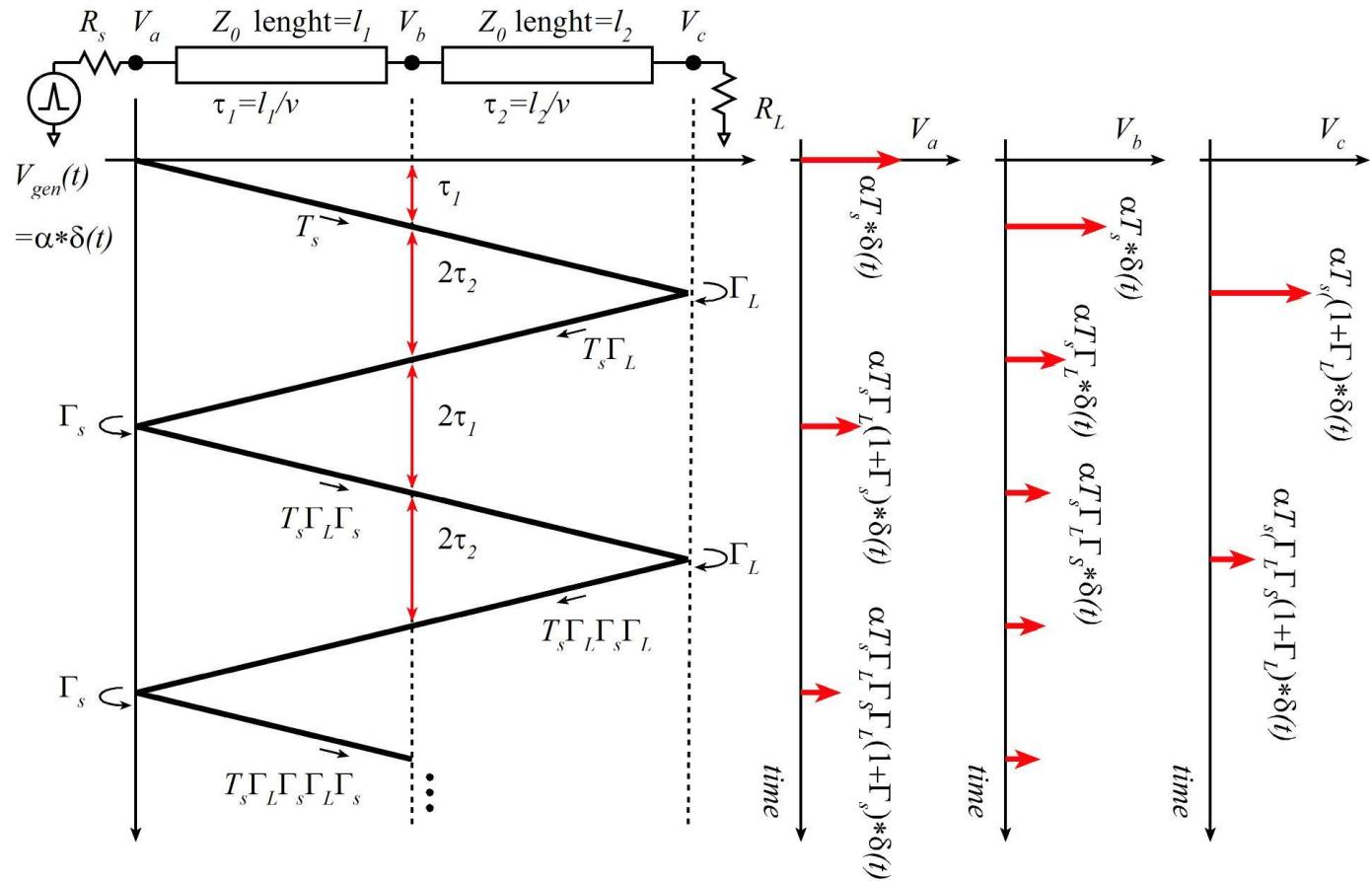


Now please consider how the waveforms would change if the generator were a step-function.
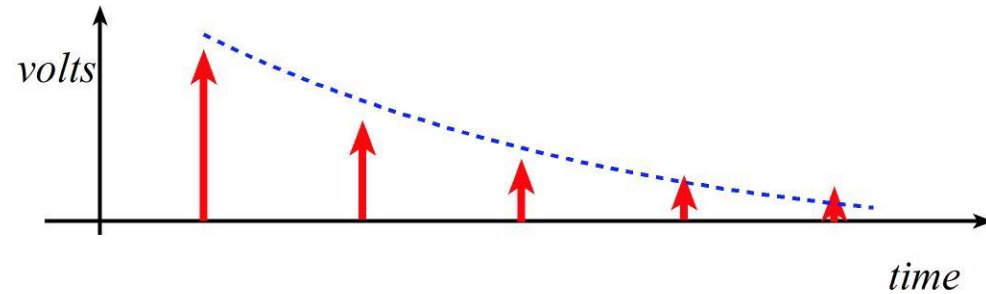
# Repeated Reflections → Ringing or Exponential Decay

If  $\Gamma_L \Gamma_s$  is positive,  
pulse responses decay  
geometrically (exponentially)




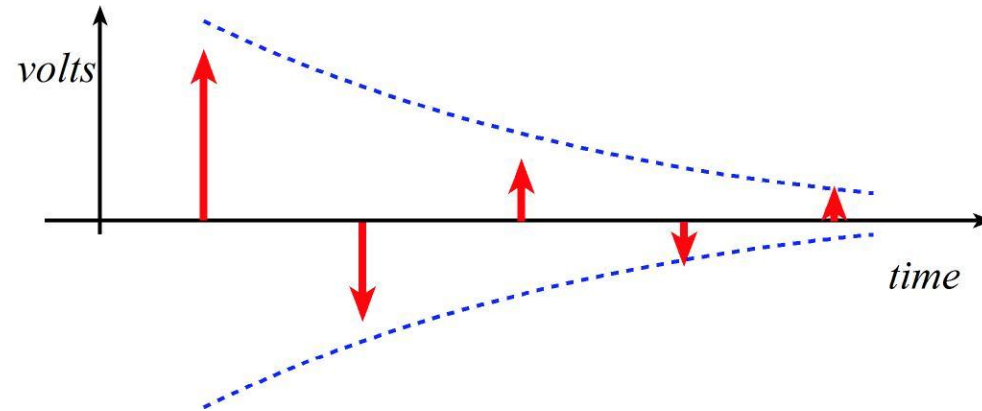If  $\Gamma_L \Gamma_s$  is negative,  
pulse responses also  
alternate in sign - -ringing.





Behavior appears very  
close to RLC ringing.


Why ?

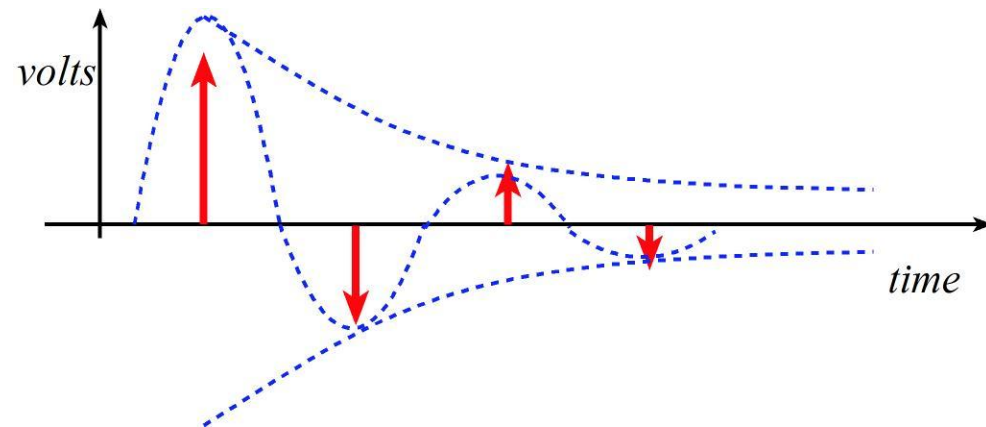


# Time-Domain Analysis

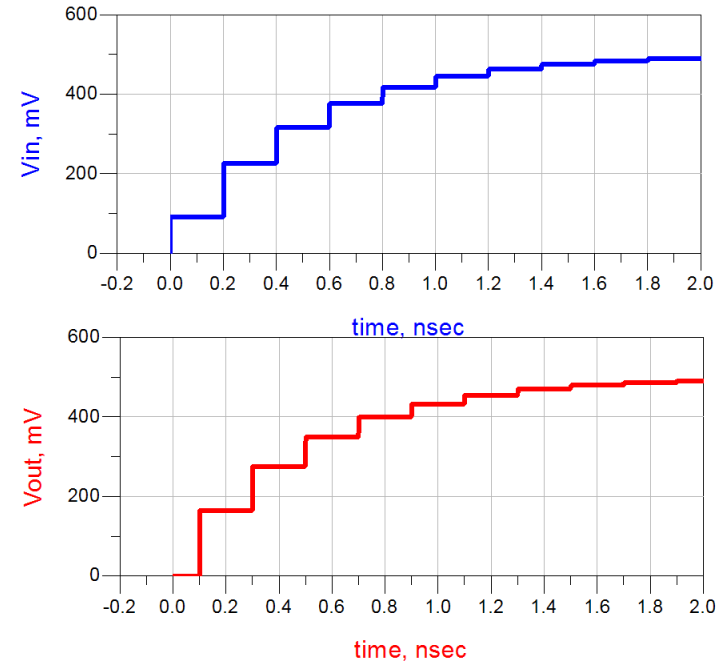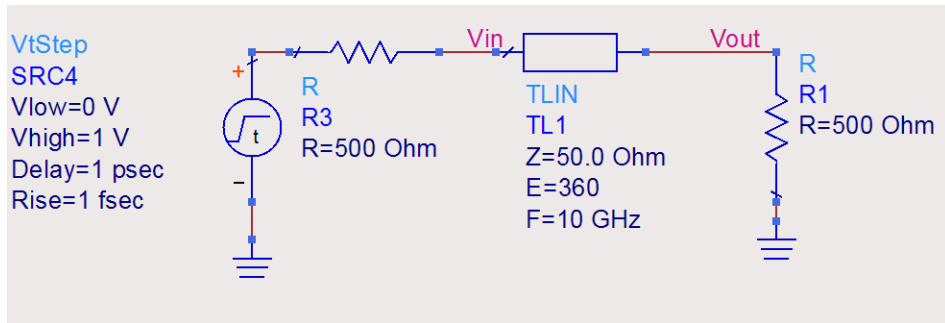

$$L = Z_0 \tau, C = \tau / Z_0$$

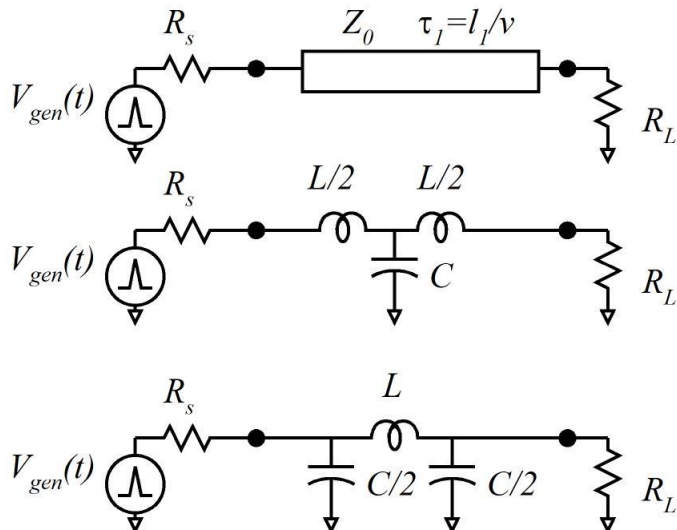

Approximate model

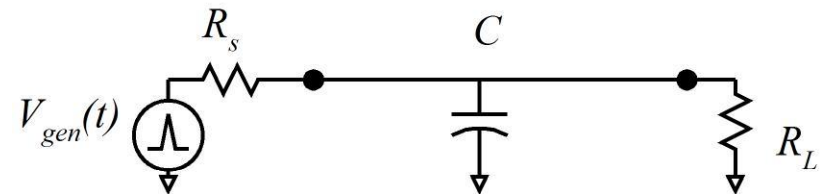




$$L / (R_L + R_s) \ll (R_L \parallel R_s) C$$

→ neglect inductor




RC circuit → charging.




# Time-Domain Analysis

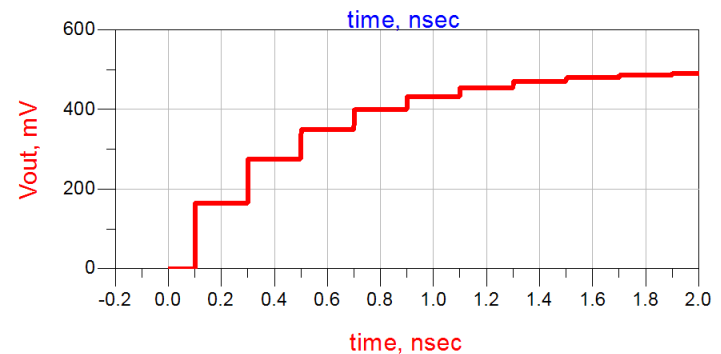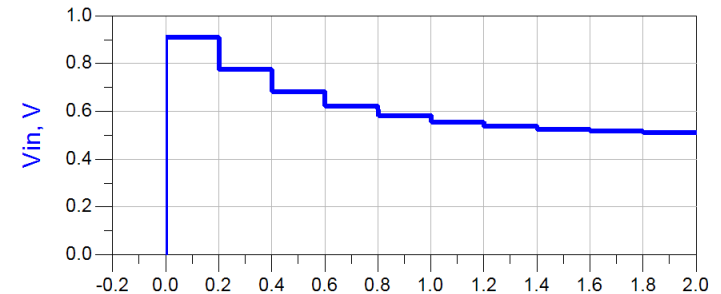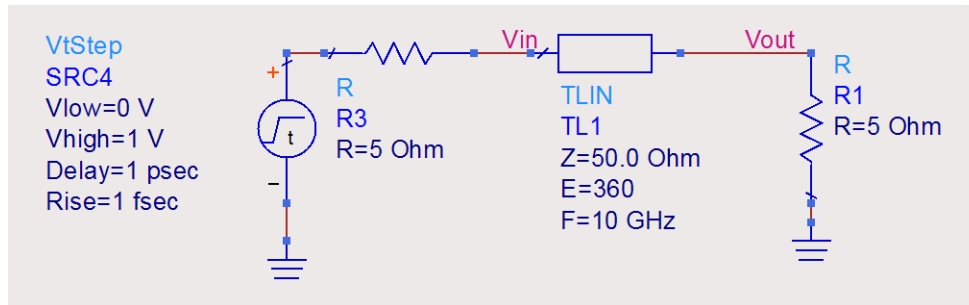

$$L = Z_0 \tau, C = \tau / Z_0$$

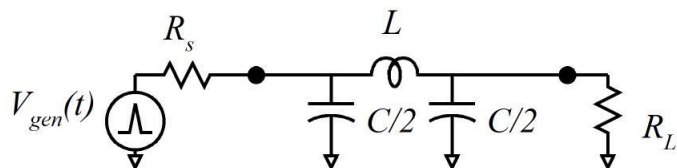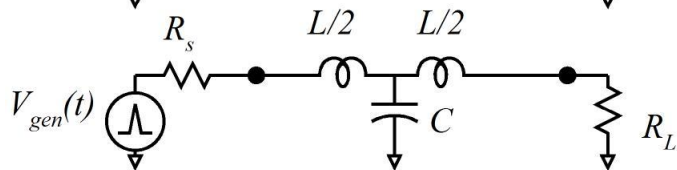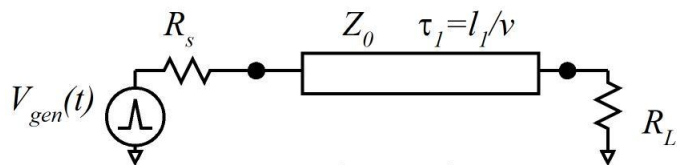

Approximate model



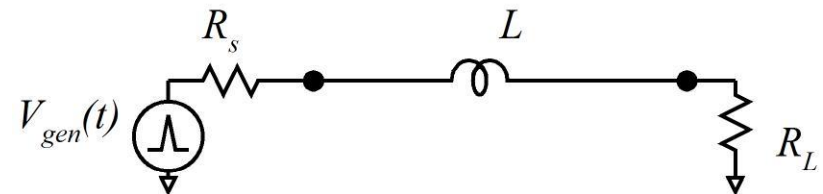


$$L / (R_L + R_s) \gg (R_L \parallel R_s) C$$


→ neglect capacitor

RL circuit → charging.


# Time-Domain Analysis

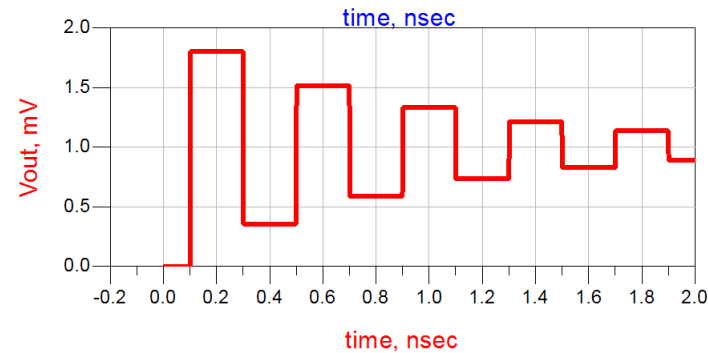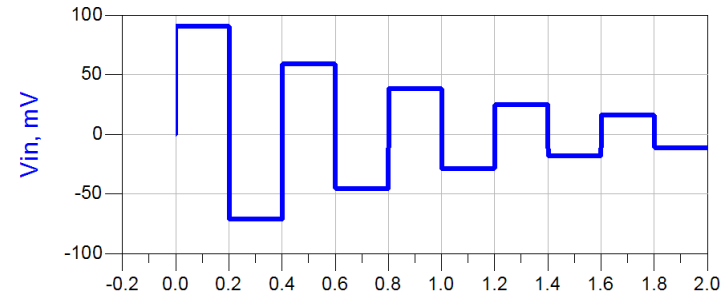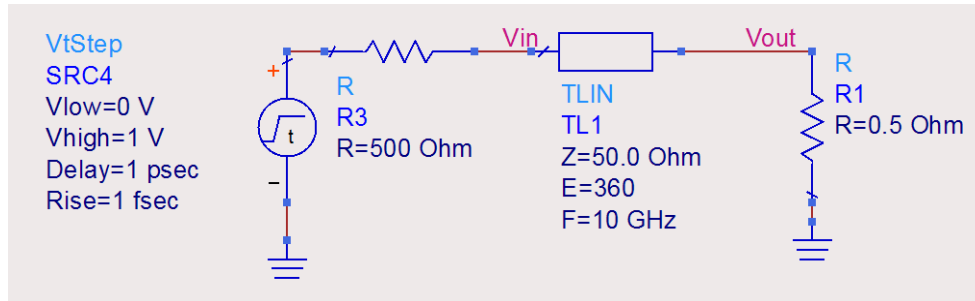

$$L = Z_0 \tau, C = \tau / Z_0$$

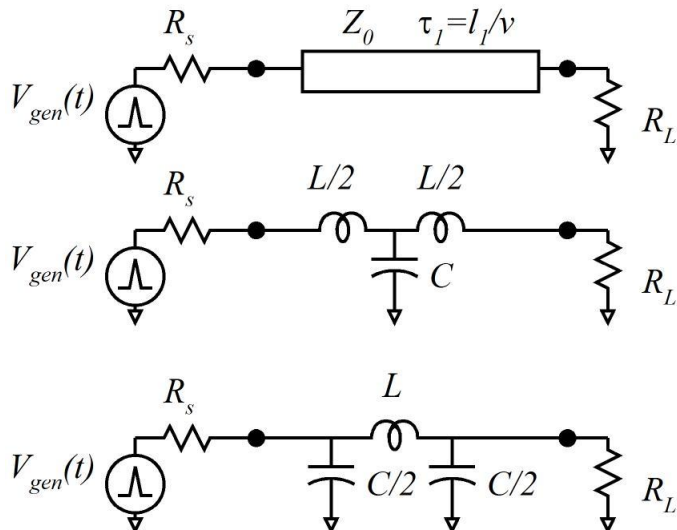

## Approximate model

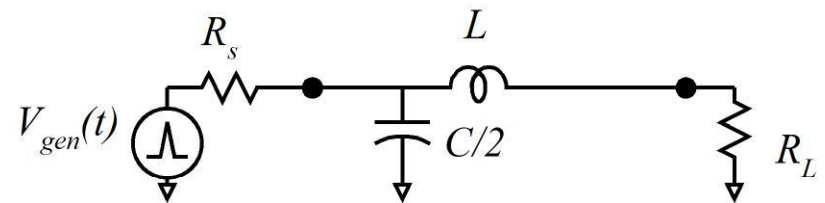

$$R_L C / 2 \ll R_s C / 2$$

→ neglect 2nd capacitor

RLC circuit → ringing

# L and C are Limiting Cases of High- $Z_0$ , low- $Z_0$ lines

$$L = Z_0 \tau, C = \tau / Z_0$$

High -  $Z_0$  line :


large  $L$ , small  $C$ .

→ approximately  
an inductor

Low -  $Z_0$  line :

large  $C$ , small  $L$ .

→ approximately  
a capacitor.

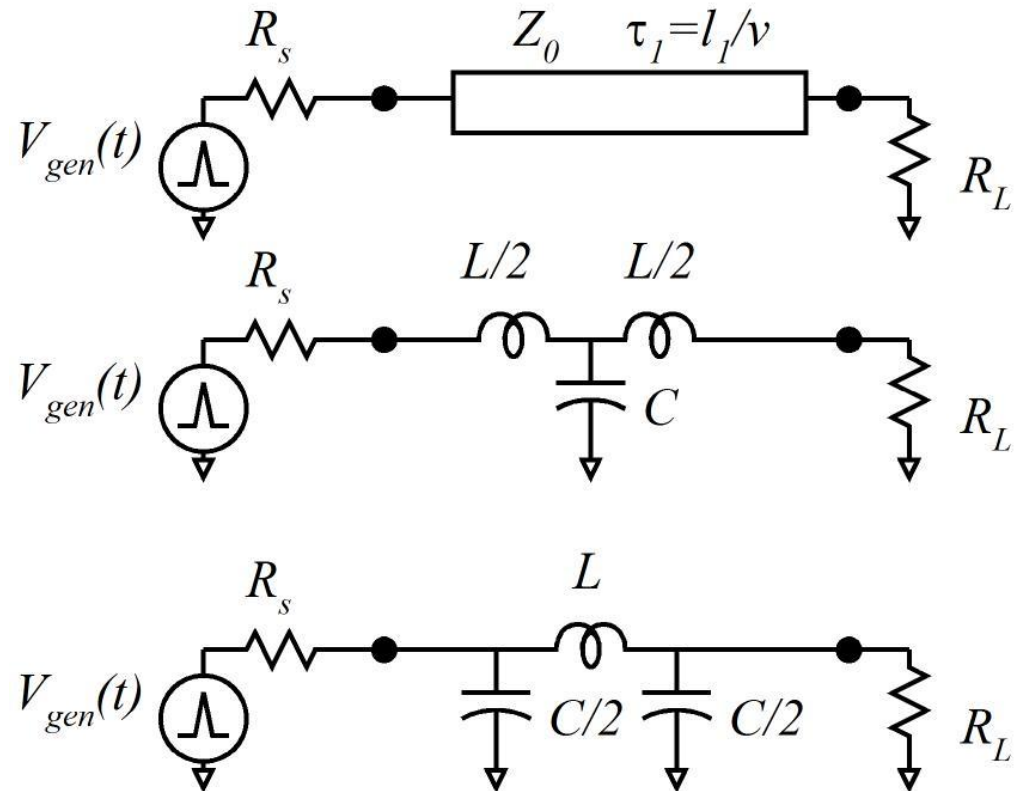

# **Lines in Frequency Domain**

# Line Analysis in Frequency Domain → Smith Chart

---

Time - domain analysis :

intuitive and clear : pulses bouncing back and forth.

very difficult with reactive (L, C) load or generator impedances

Frequency - domain analysis :


less intuitive.

easy with reactive (L, C) load or generator impedances

→ (1) standing waves

→ (2) Smith chart
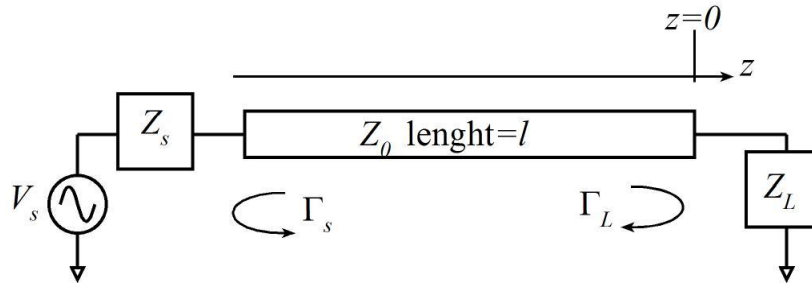
# Line Analysis in Frequency Domain: Phase Constant $\beta$



Phasor notation:  $V_s(t) = \text{Re}[V_0 e^{j\omega t}]$ , where  $V_0 = \|V_0\| e^{j\theta_0}$  is complex.

$$\rightarrow V_s(t) = V_0 \cos(\omega t + \theta_0)$$


On a transmission line, waves travel as  $V^+(t - z/v), V^-(t + z/v)$ .

For a sinusoidal wave traveling at velocity  $v$ ,

$$\cos(\omega(t \pm z/v) + \theta) = \cos(\omega t \pm \omega z/v + \theta) = \cos(\omega t \pm \beta z + \theta).$$

$\beta = \omega/v = 2\pi/\lambda$  is the phase propagation constant.

# Line Analysis: Exponential Waves

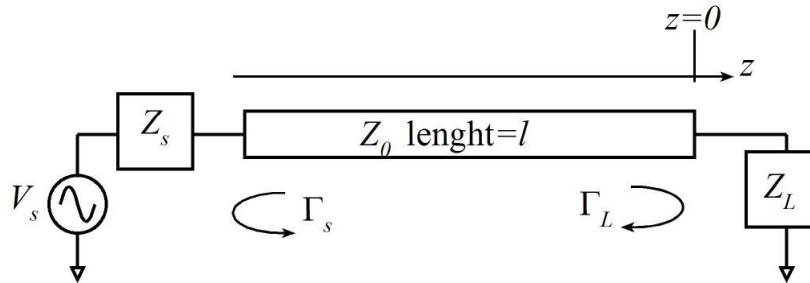

Because  $V_0 \cos(\omega t + \theta_o) = \text{Re}[V_0 e^{j\omega t}]$ , sinusoidal waves are written implicitly as  $V_0 e^{j\omega t}$ .


Exponential waves propagating in the positive  $z$  - direction :

$$V^+ e^{j\omega(t-z/v)} = V^+ e^{j\omega t - j\omega z/v} = V^+ e^{j\omega t} e^{-j\beta z}$$

Exponential waves propagating in the negative  $z$  - direction :

$$V^- e^{j\omega(t+z/v)} = V^- e^{j\omega t + j\omega z/v} = V^- e^{j\omega t} e^{+j\beta z}$$

# Voltages on a Transmission Line

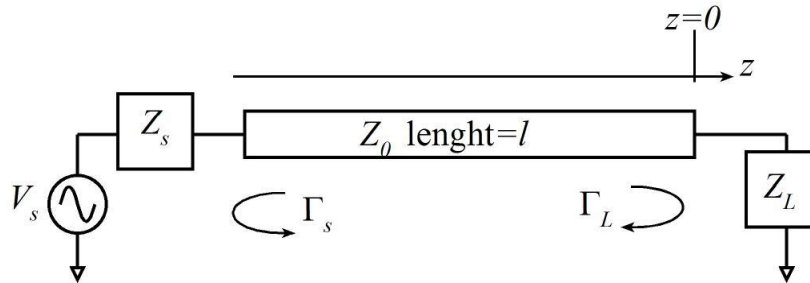

Voltage on line :  $V(z, t) = \text{Re}[V(z)e^{j\omega t}]$


Working with the phasor  $V(z)$  makes  $e^{j\omega t}$  time dependence implicit.

Phasor voltage on the line :

$$\begin{aligned} V(z) &= V^+(z) + V^-(z) \\ &= V^+(0)e^{-j\beta z} + V^-(0)e^{+j\beta z} \end{aligned}$$


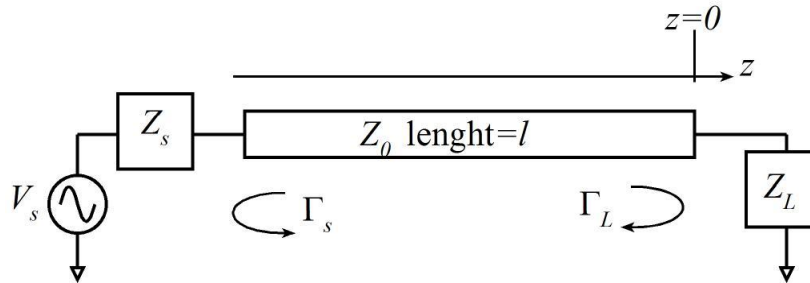
# Voltages and Currents on a Transmission Line




Phasor voltage on the line :

$$V(z) = V^+(z) + V^-(z) = V^+(0)e^{-j\beta z} + V^-(0)e^{+j\beta z}$$

Phasor current on the line :

$$Z_0 I(z) = V^+(z) - V^-(z) = V^+(0)e^{-j\beta z} - V^-(0)e^{+j\beta z}$$

# Wave Parameters

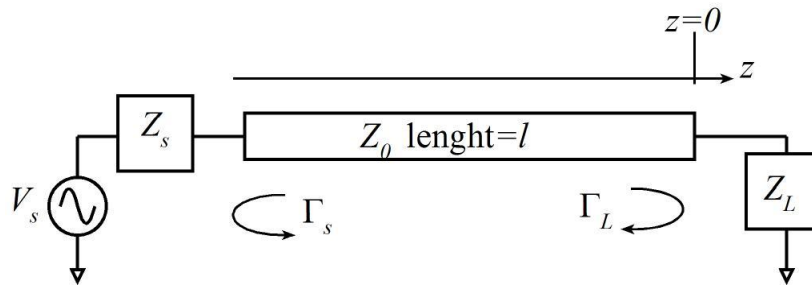

Define wave amplitude  $a$  such that if  $\|a\| = 1$ , then wave power = 1 Watt.

Voltage in forward wave:  $V^+(z)$


Current in forward wave:  $I^+(z) = V^+(z) / Z_0$

Power in forward wave =  $V^+ (I^+)^* = \|V^+(z)\|^2 / Z_0$

Forward wave amplitude:  $a(z) = V^+(z) / \sqrt{Z_0}$

Reverse wave amplitude:  $b(z) = V^-(z) / \sqrt{Z_0}$

# Wave Parameters and Power

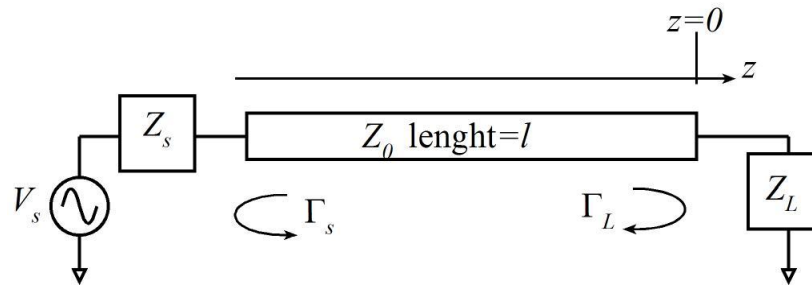


Power in forward wave =  $V^+(I^+)^* = \|V^+(z)\|^2 / Z_0 = a(z)a^*(z)$

Power in reverse wave =  $V^-(I^-)^* = \|V^-(z)\|^2 / Z_0 = b(z)b^*(z)$

Throughout the notes, we use R.M.S. quantities.

# Reflections from the Load

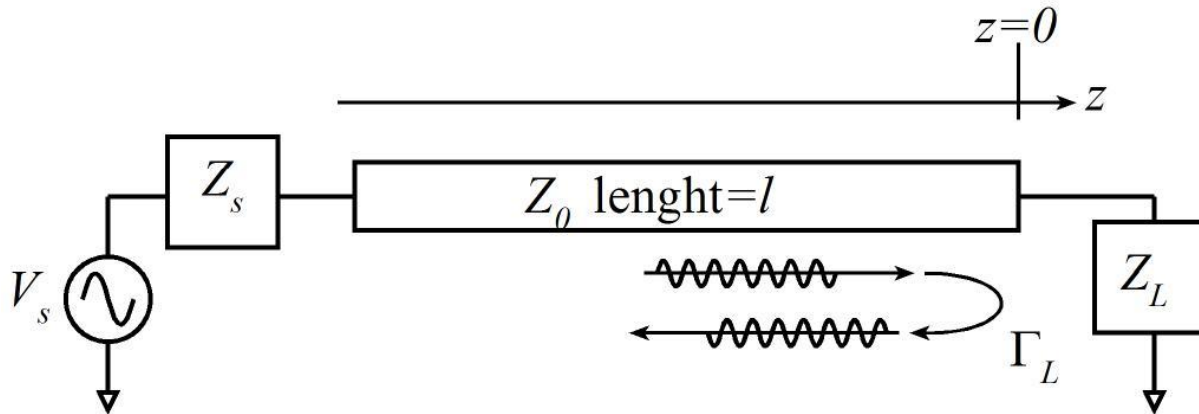


$$V^-(0) = \Gamma_L V^+(0)$$

where  $\Gamma_L = \frac{\mathfrak{Z}_L - 1}{\mathfrak{Z}_L + 1}$  is the load reflection coefficient.

and  $\mathfrak{Z}_L = \frac{Z_L}{Z_0}$  is the \* normalized \* load impedance.

# Reflections from the Generator

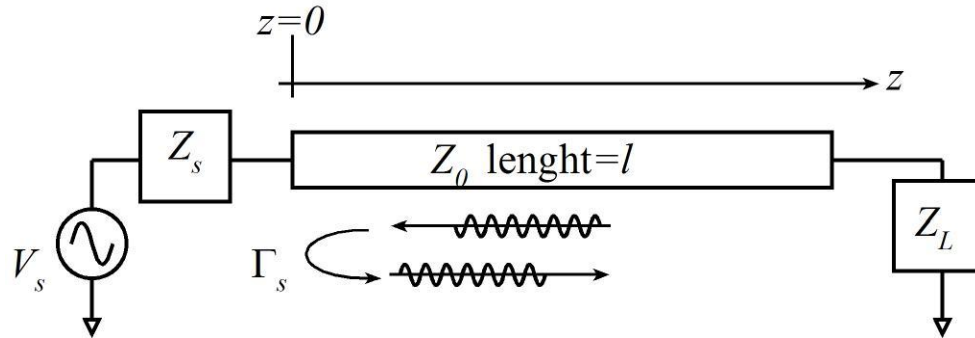

$$V^+(0) = \Gamma_s V^-(0) + T_s V_s$$


where  $T_s = \frac{Z_0}{Z_0 + Z_s}$  is the source transmission coefficient

where  $\Gamma_s = \frac{\mathfrak{Z}_s - 1}{\mathfrak{Z}_s + 1}$  is the source reflection coefficient

and  $\mathfrak{Z}_s = \frac{Z_s}{Z_0}$  is the \* normalized \* source impedance.

Note that the reference plane ( $z = 0$ ) has been moved.

# Movement of Reference Plane

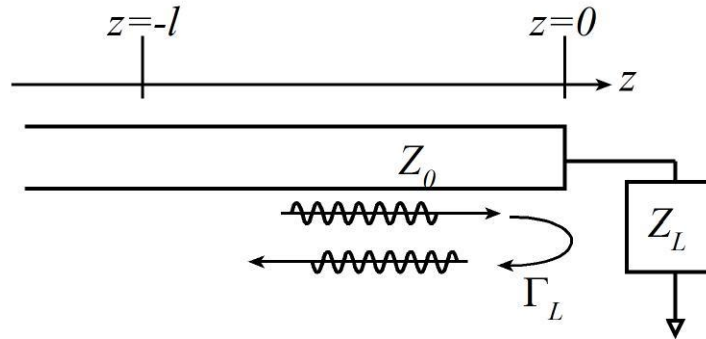

$$V(z) = V^+(z) + V^-(z) = V^+(z) \cdot (1 + \Gamma(z))$$

where  $\Gamma(z) \equiv \frac{V^-(z)}{V^+(z)}$  is the position-dependent reflection coefficient

$$V(z) = V^+(0)e^{-j\beta z} \cdot (1 + \Gamma(0)e^{+2j\beta z})$$

$$\text{because } \Gamma(z) \equiv \frac{V^-(z)}{V^+(z)} = \frac{V^-(0)e^{+j\beta z}}{V^+(0)e^{-j\beta z}} = \Gamma(0)e^{+2j\beta z}$$

# Position-Dependent Reflection Coefficient

Reflection coefficient  $\Gamma$  at a distance  $l$  from load.

$$\Gamma(-l) = \Gamma(0)e^{+2j\beta z}$$

The reflection coefficient has gone through a phase shift of


negative  $\frac{l}{\lambda} \cdot 2 \cdot 2\pi$  radians.

or

negative  $2 \cdot \beta \cdot l$  radians.


or

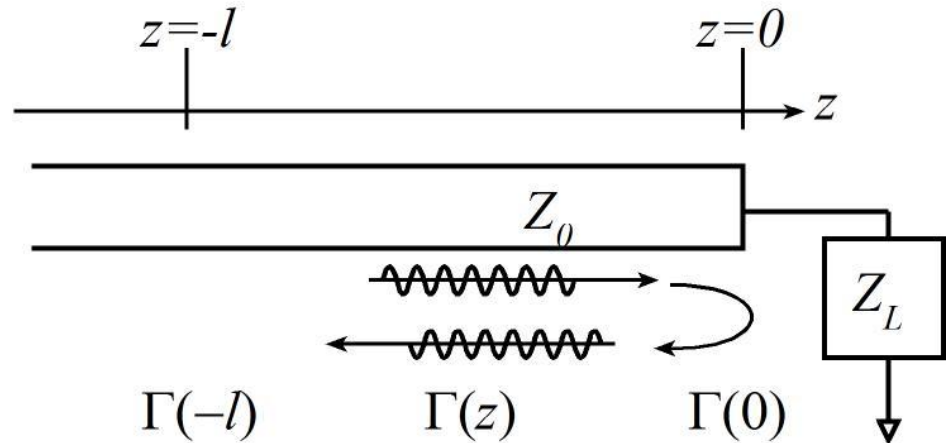negative  $\frac{l}{\lambda} \cdot 2 \cdot 360$  degrees.



...simply because  $V^+$  and  $V^-$  undergo 360 degree phase shifts every wavelength of distance.

# Impedance vs. Position

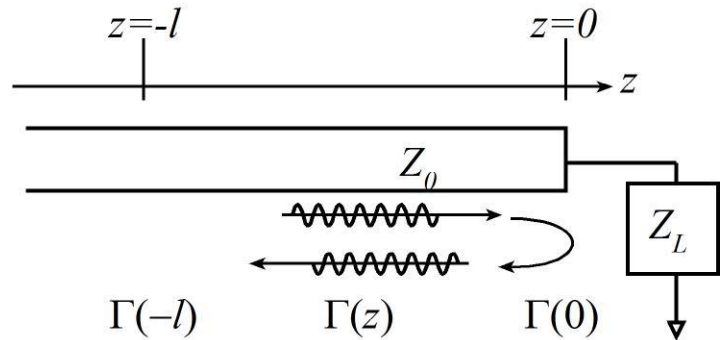

Impedance at any point

$$Z(z) \equiv V(z) / I(z) = (V^+(z) + V^-(z)) / (I^+(z) - I^-(z))$$

$$= Z_0 \cdot (V^+(z) + V^-(z)) / (V^+(z) - V^-(z))$$


$$Z(z) = Z_0 \cdot \frac{1 + \Gamma(z)}{1 - \Gamma(z)}$$

Normalized impedance at any point

$$\mathcal{Z}(z) \equiv Z(z) / Z_0 = \frac{1 + \Gamma(z)}{1 - \Gamma(z)}$$



# Line Input Impedance

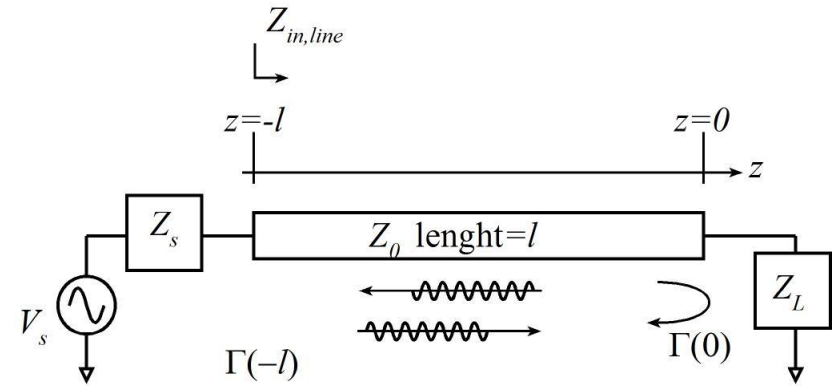


Input impedance at  $z = -l$

$$\mathcal{Z}(-l) = \frac{V(-l)}{I(-l)} = \frac{1 + \Gamma(-l)}{1 - \Gamma(-l)} \text{ normalized.}$$

$$Z(-l) = \frac{V(-l)}{I(-l)} = Z_0 \cdot \frac{1 + \Gamma(-l)}{1 - \Gamma(-l)} \text{ unnormalized.}$$
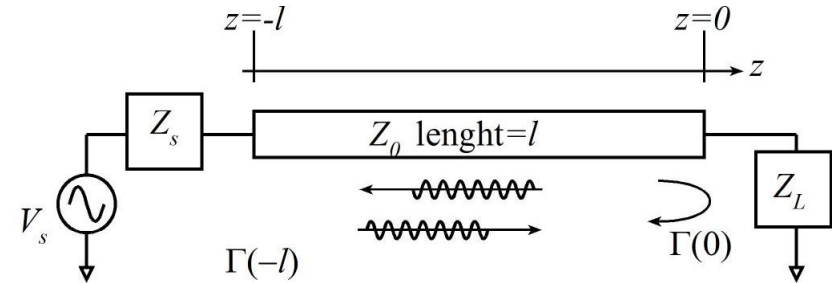
# Impedance and Reflection Coefficient vs Position



$$\left. \begin{aligned} V(z) &= V^+(z) + V^-(z) = V^+(0)e^{-j\beta z} + V^-(z)e^{+j\beta z} \\ Z_0 I(z) &= V^+(z) - V^-(z) = V^+(0)e^{-j\beta z} - V^-(z)e^{+j\beta z} \end{aligned} \right\} \text{ waves}$$


$$\left. \begin{aligned} \Gamma(z) &= V^+(z) / V^-(z) \\ \Gamma(z) &= \Gamma(0) e^{+2j\beta z} \end{aligned} \right\} \text{ reflection coefficients}$$

$$\left. \mathfrak{Z}(z) = \frac{1}{Z_0} \frac{V(z)}{I(z)} = \frac{1 + \Gamma(z)}{1 - \Gamma(z)} \right\} \text{ normalized impedance}$$

Conceptually simple, but tedious math.  $\rightarrow$  Work with a graphical tool.
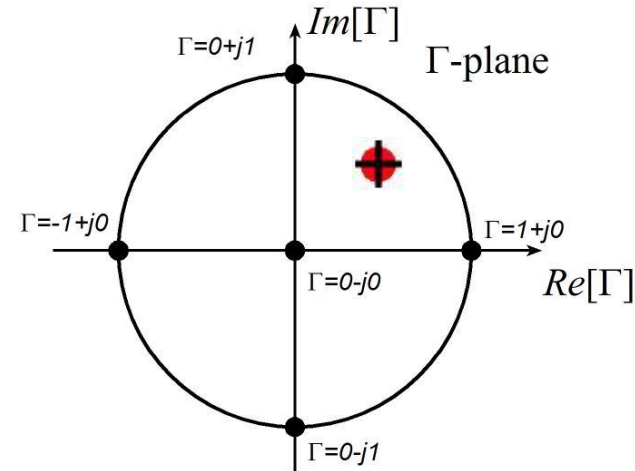
# Developing the Smith Chart

The relationship  $\mathcal{Z} = \frac{1 + \Gamma}{1 - \Gamma} \leftrightarrow \Gamma = \frac{\mathcal{Z} - 1}{\mathcal{Z} + 1}$  is key.




The relationship is a 1 - 1 mapping between the complex #s  $\mathcal{Z}$  and  $\Gamma$ ; a conformal transformation. This relationship can be graphed.

In the 2 - dimensional plane of  $\Gamma$  - the  $\Gamma$  plane - a reflection coefficient is represented by a point (here, a red dot).
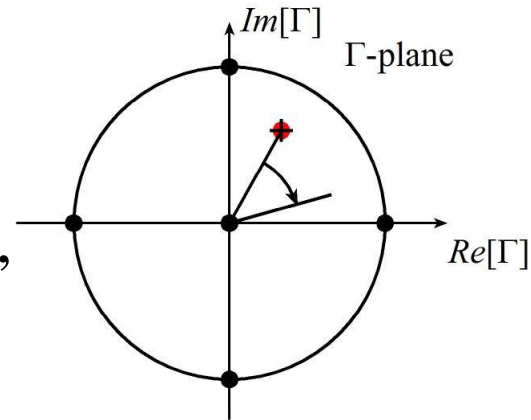
# Moving Reference Planes---on the Smith Chart

As we move a distance  $l$  away from the load, the vector  $\Gamma$  rotates by an angle  $\Delta\theta$




$$\Delta\theta = -2\beta l$$

$$= -360^\circ \cdot \frac{l}{\lambda} \cdot 2$$

= one whole rotation in the  $\Gamma$  plane

for each half - wavelength movement  
on the transmission line.

# Finding Impedances

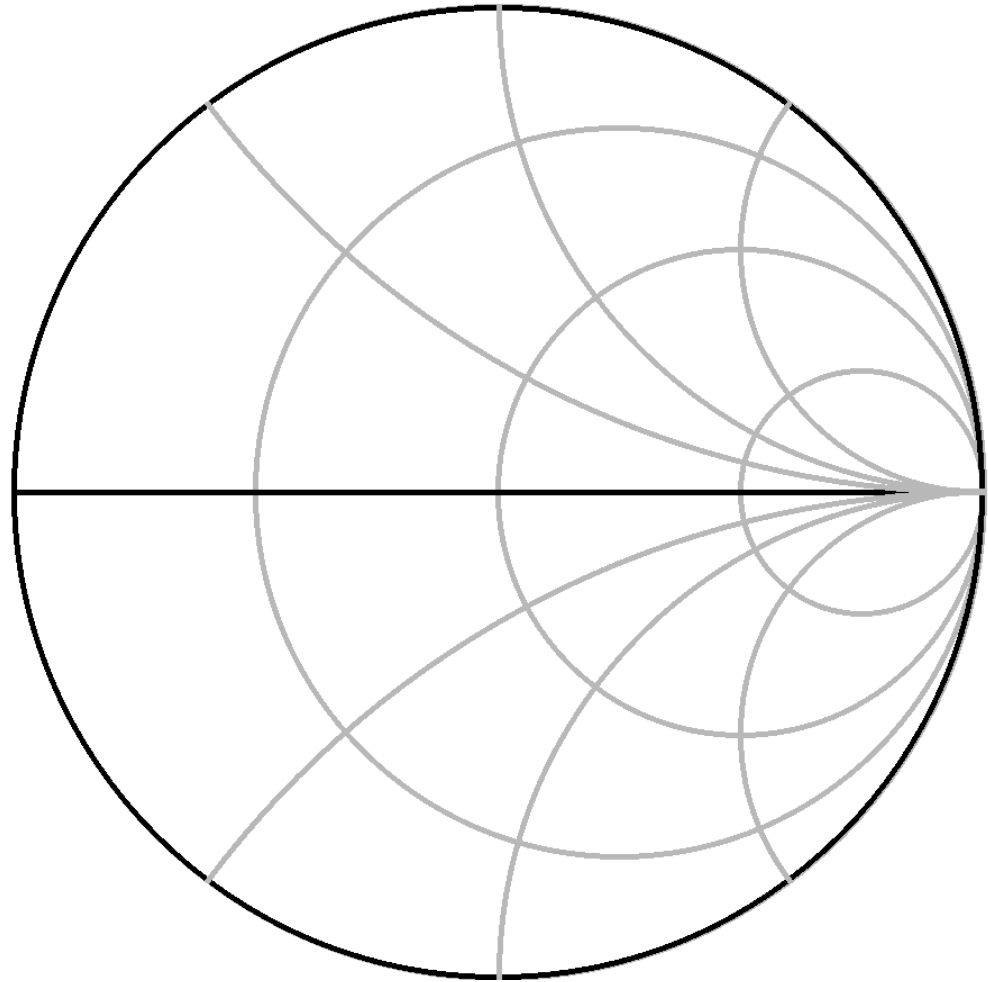

$$\mathfrak{Z}(z) = \frac{1}{Z_0} \frac{V(z)}{I(z)} = \frac{1 + \Gamma(z)}{1 - \Gamma(z)}$$

This is a 1 : 1 relationship

between reflection coefficient  $\Gamma$  (magnitude and phase) and normalized impedance  $\mathfrak{Z}$  (real and imaginary parts).


Plot the units of  $\mathfrak{Z}$  on the  $\Gamma$  plane!

# Finding Impedances

$$\mathfrak{Z} = \frac{1 + \Gamma}{1 - \Gamma} = \frac{Z}{Z_0}$$

$$Z = R + jX$$

$$\mathfrak{Z} = r + jx$$

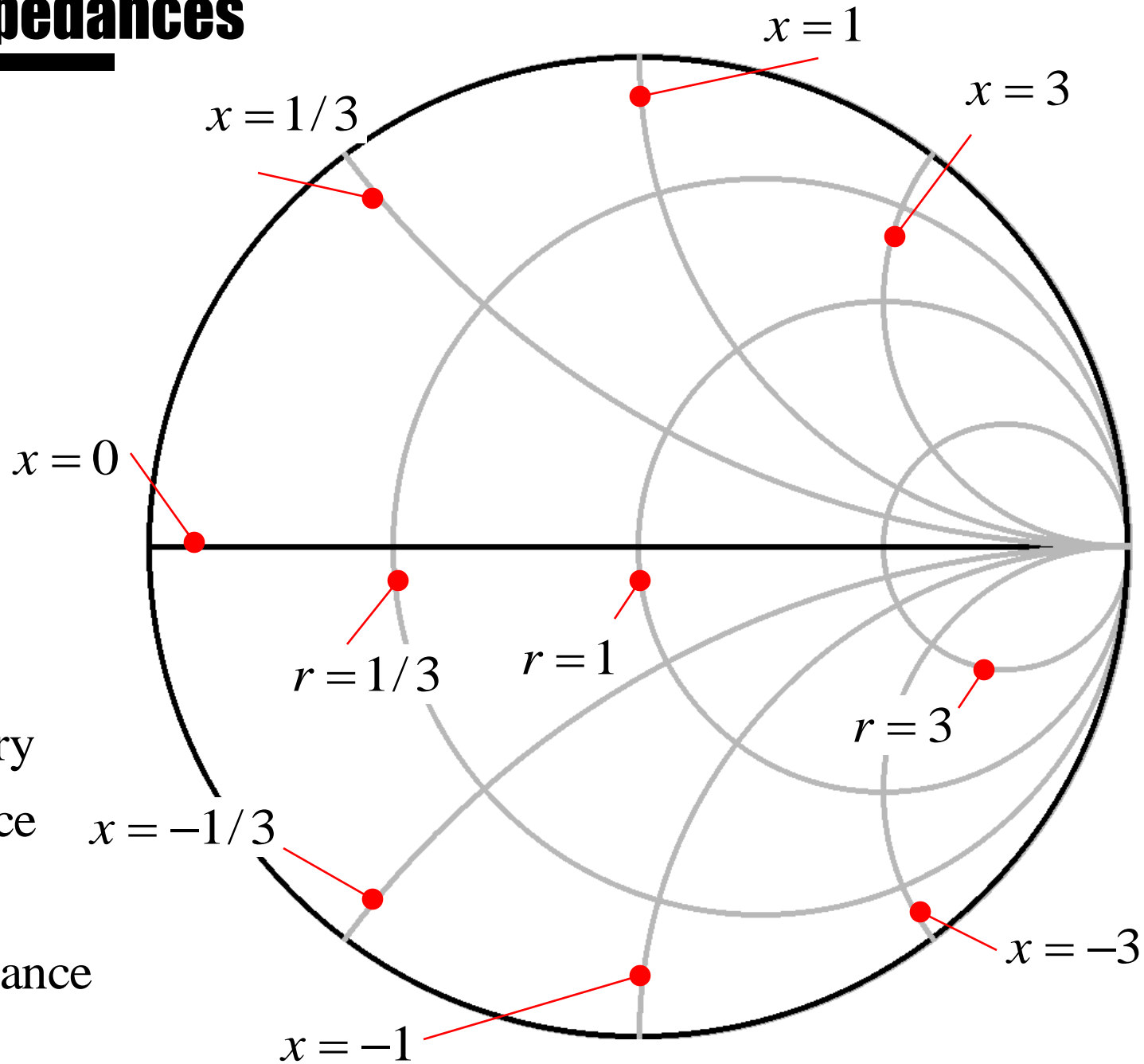


Real and imaginary parts of impedance can be read from the curved impedance axes on the chart.
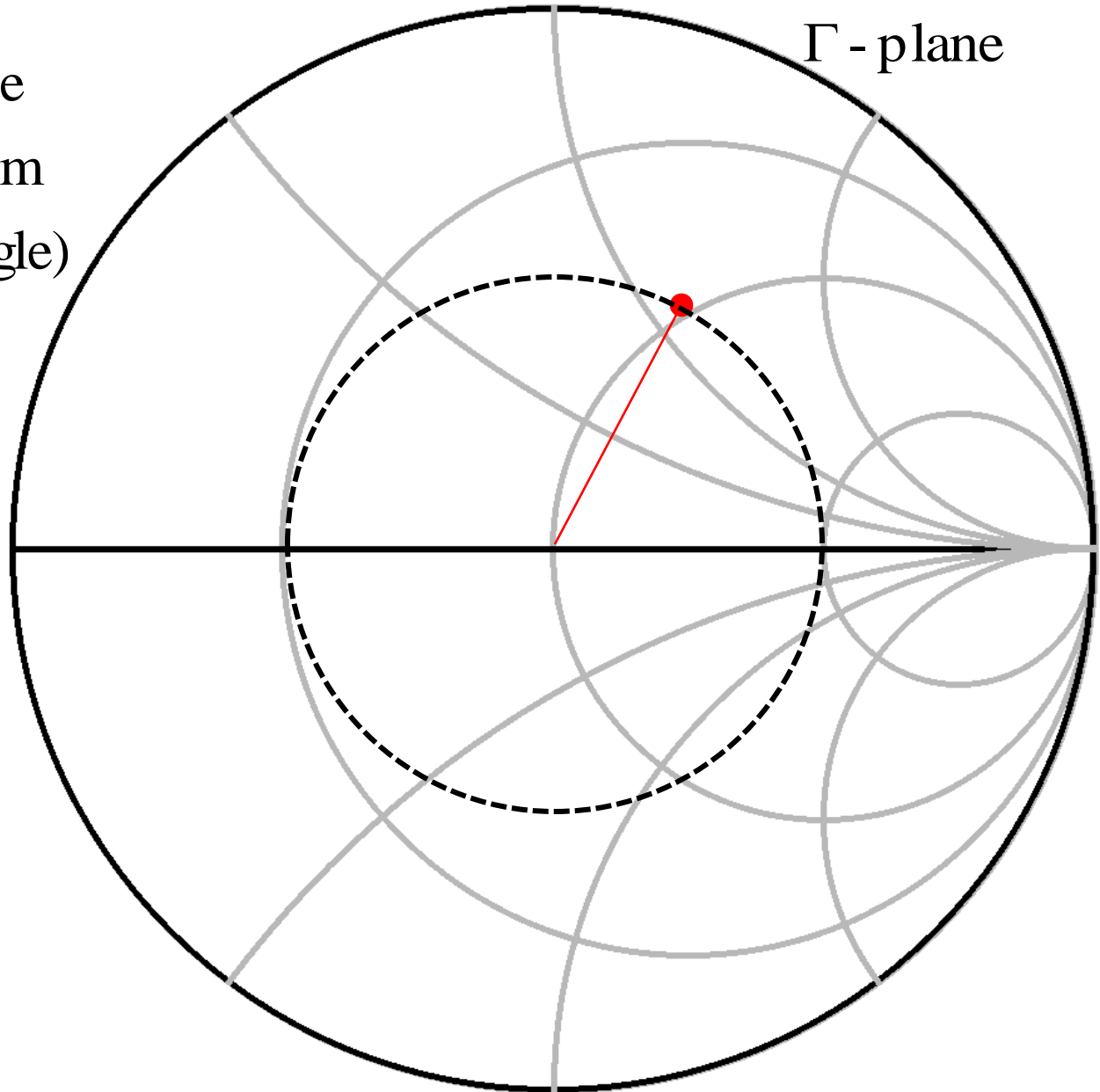
# Finding Reflection Coefficient


The magnitude and angle of  $\Gamma$  are simply read from the chart (radius and angle)

this measurement can be done using a ruler and a protractor\*.



\* though today the CAD software does the measurement from a cursor.


# Using the Smith Chart

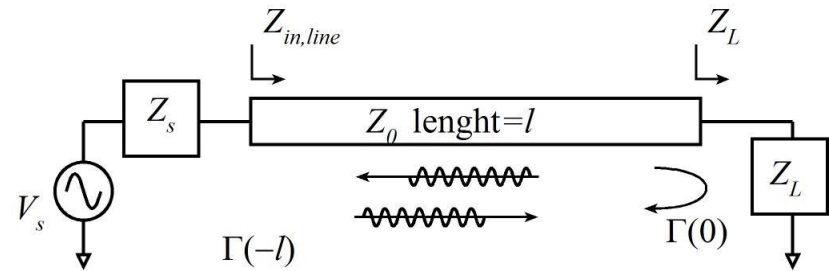

Starting with the load impedance  $Z_L$ ,  
we compute  $\mathfrak{z}_L = Z_L / Z_0$ .

We then find this point on the Smith chart.

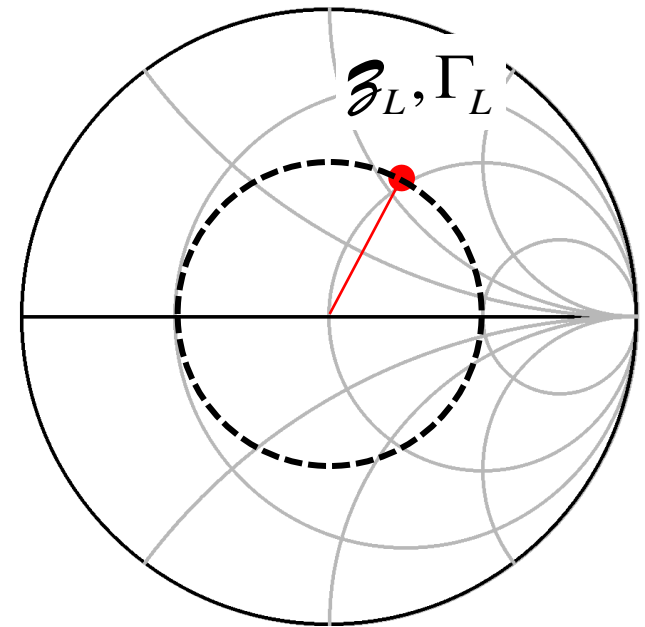This determines the load reflection  
coefficient  $\Gamma_L$ .







# Using the Smith Chart


We then rotate the vector  $\Gamma$  through an angle  $360^\circ \cdot (2l / \lambda)$ .

This locates the input reflection coefficient.

We can now read off the input impedance.

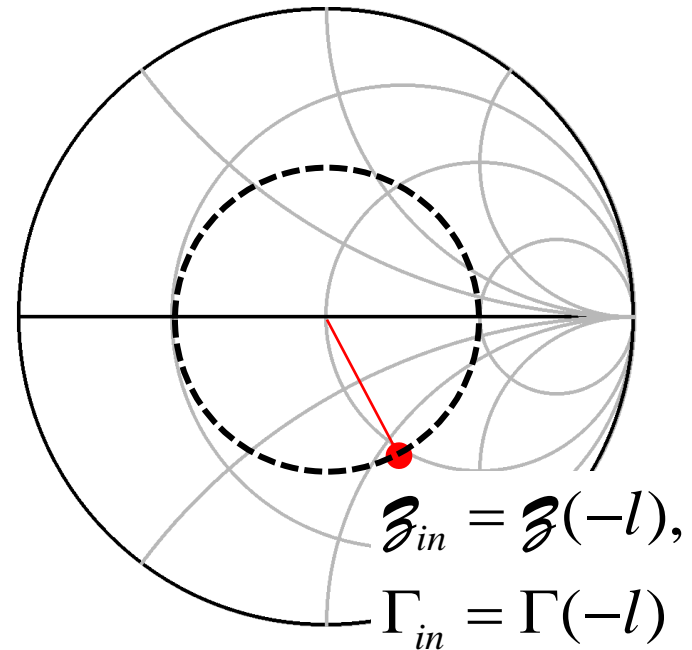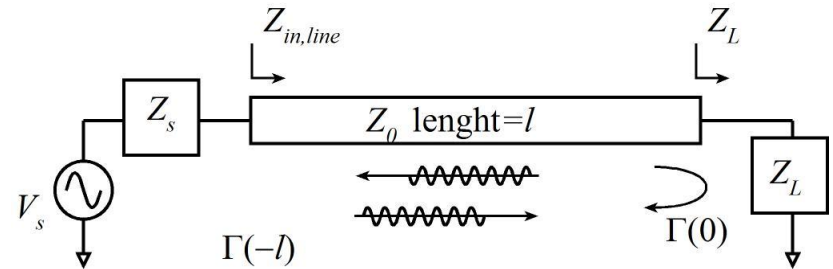

# Impedance-Admittance Chart

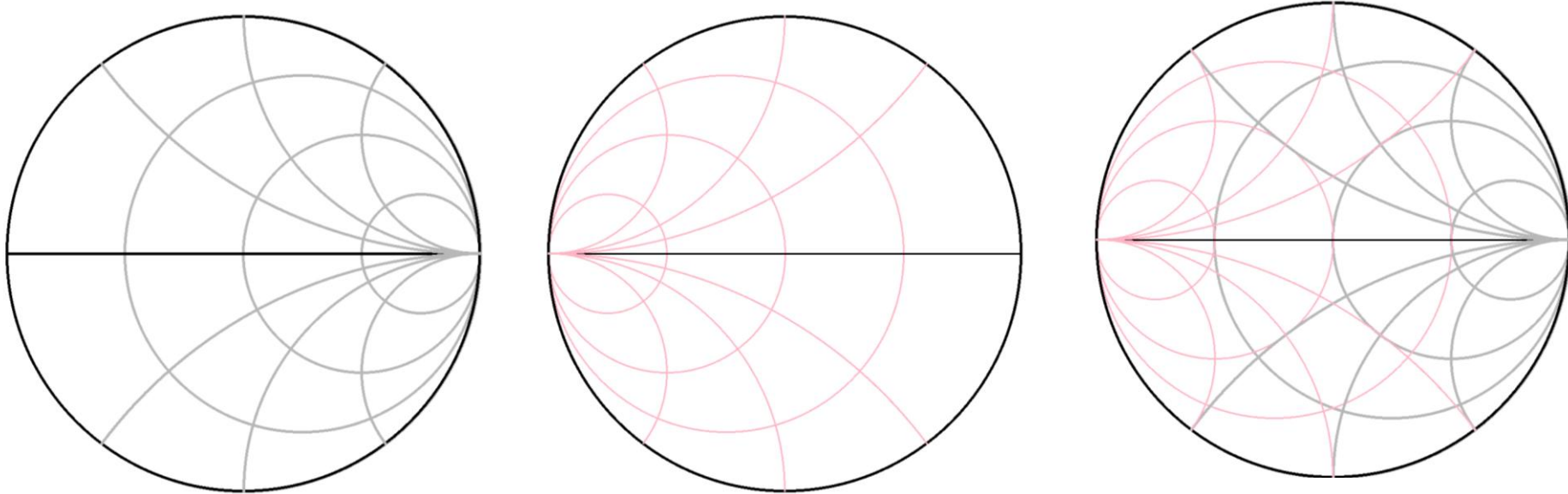

Impedance  $Z = R + jX$

Normalized impedance  $\mathfrak{z} = Z / Z_o = r + jx$

Admittance  $Y = 1 / Z = G + jB$

Normalized admittance  $\mathfrak{y} = YZ_o = Y / Y_o = g + jb$

Smith charts can have axes for  $\mathfrak{z}$ ,  $\mathfrak{y}$ , or both.

# **Solving Wave Equations Quickly**

# Waves and Fourier Transforms (1)

Maxwell's equations give us a wave equation :

$$\nabla^2 \vec{E} = \mu\epsilon \cdot \frac{\partial^2 \vec{E}}{\partial t^2} + \mu \frac{\partial \vec{J}}{\partial t} + \epsilon^{-1} \vec{\nabla} \rho \quad \text{if } \mu \text{ and } \epsilon \text{ are uniform}$$

Assume nonzero conductivity,  $\vec{J} = \sigma \vec{E}$ , assume charge neutrality  $\rho = 0$ .

$$\nabla^2 \vec{E} = \mu\epsilon \cdot \frac{\partial^2 \vec{E}}{\partial t^2} + \mu\sigma \frac{\partial \vec{E}}{\partial t}$$

To solve this easily, assume

$$E_x(x, y, z, t) = E_x e^{j\omega t} e^{-jk_x x} e^{-jk_y y} e^{-jk_z z} \quad (\text{and the same for } E_y, E_z)$$

Sometimes, the  $k$ 's are complex : writing  $\gamma = jk = \alpha + j\beta$

$$E_x(x, y, z, t) = E_x e^{j\omega t} e^{-\gamma_x x} e^{-\gamma_y y} e^{-\gamma_z z}$$

# Waves and Fourier Transforms (2)

So we have :

$$\frac{\partial^2 E_x}{\partial x^2} + \frac{\partial^2 E_x}{\partial y^2} + \frac{\partial^2 E_x}{\partial z^2} = \mu\varepsilon \cdot \frac{\partial^2 E_x}{\partial t^2} + \mu\sigma \frac{\partial E_x}{\partial t} \quad (\text{and the same for } E_y, E_z)$$

Given


$$E_x(x, y, z, t) = E_x e^{j\omega t} e^{-jk_x x} e^{-jk_y y} e^{-jk_z z} \quad (\text{and the same for } E_y, E_z),$$

This becomes simply

$$k_x^2 + k_y^2 + k_z^2 = k^2 \quad \text{where } k^2 = (j\omega\mu)(j\omega\varepsilon + \sigma)$$

This is the wave equation in the sinusoidal steady state

# Waves and Fourier Transforms (3)

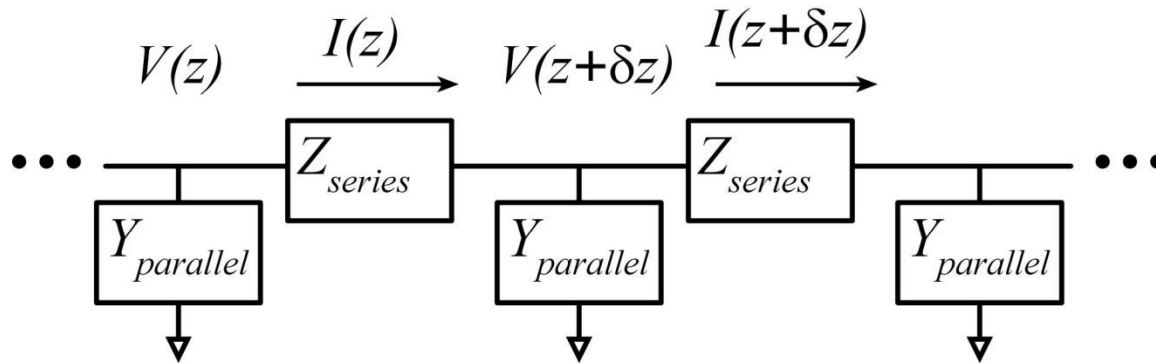

Now consider a 1-dimensional system (transmission - line)

$$\frac{\partial V}{\partial z} = -Z_{series} I \quad \text{and} \quad \frac{\partial I}{\partial z} = -Y_{parallel} V$$


To solve this easily, assume

$$V^{+/-}(z, t) = V^{+/-} e^{j\omega t} e^{-\gamma z} \quad \text{and} \quad I^{+/-}(z, t) = I^{+/-} e^{j\omega t} e^{\gamma z}$$

Then

$$\gamma V = Z_{series} I \quad \text{and} \quad \gamma I = Y_{parallel} V$$

# Waves and Fourier Transforms (4)

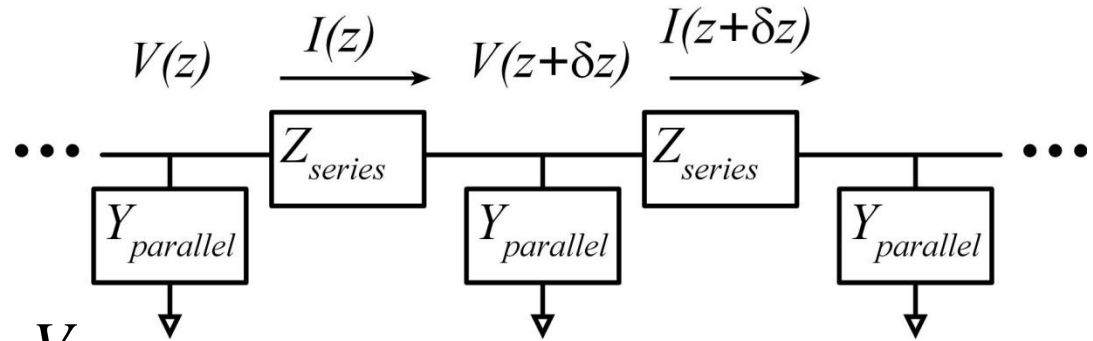

$$\gamma V = Z_{series} I \quad \text{and} \quad \gamma I = Y_{parallel} V$$

Multiply these:


$$\gamma^2 VI = Z_{series} Y_{parallel} VI \rightarrow \gamma = \pm \sqrt{Z_{series} Y_{parallel}}$$

Divide these:

$$V^\pm / I^\pm = Z_{series} I^\pm / Y_{parallel} V^\pm \rightarrow Z_0 \equiv (V^\pm / I^\pm) = \pm \sqrt{Z_{series} / Y_{parallel}}$$

The  $\pm$  before the root indicates that the forward current has the same sign as the forward voltage, while the reverse current has sign opposite that of the reverse voltage.

# Waves and Fourier Transforms (5)

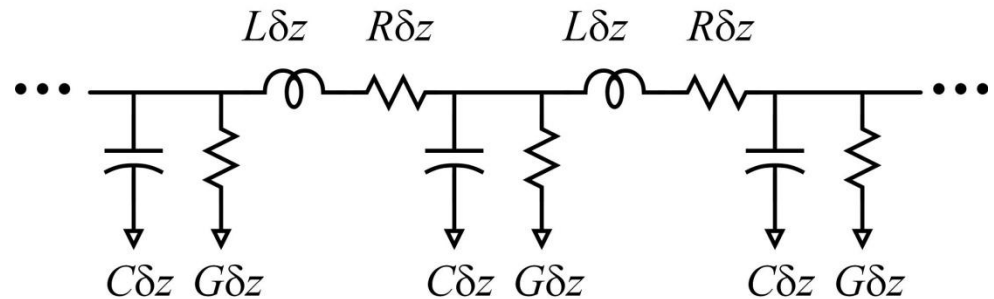

Line has series inductance  $L$  and series  $R$  resistance per unit length.

Line has parallel capacitance  $C$  and parallel conductance  $G$  per unit length.

Then


$$Z_{series} = R + j\omega L \quad Y_{parallel} = G + j\omega C$$

So :

$$\gamma = \pm \sqrt{(R + j\omega L)(G + j\omega C)} \quad Z_0 = \pm \sqrt{(R + j\omega L)/(G + j\omega C)}$$



# Waves and Fourier Transforms (6)

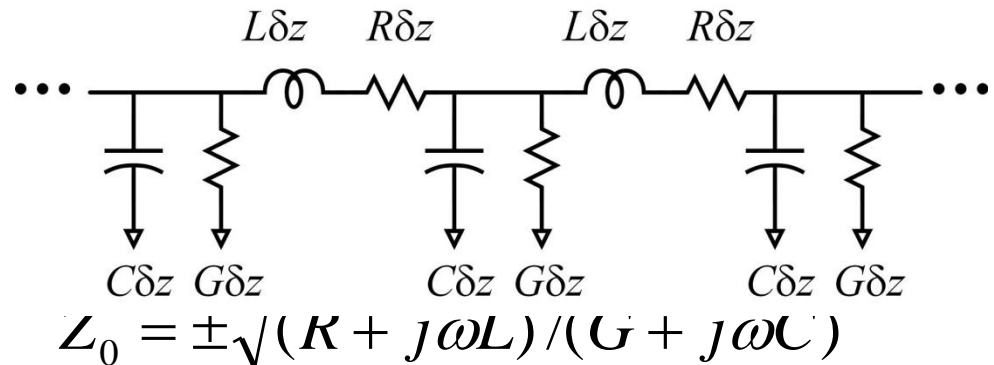

$$\gamma = \pm \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$Z_0 = \pm \sqrt{(R + j\omega L) / (G + j\omega C)}$$

Suppose  $R \ll \omega L$  and  $G \ll j\omega C$ . Use  $(1 + \varepsilon)^N = 1 + N\varepsilon + O(\varepsilon^2)$


$$Z_0 = \pm \sqrt{j\omega L / j\omega C} \sqrt{(1 + R / j\omega L) / (1 + G / j\omega C)}$$

$$Z_0 \cong \pm \left[ \sqrt{\frac{L}{C}} \cdot \frac{1 + R / j2\omega L}{1 + G / j2\omega C} \right]$$

Note that  $Z_0$  becomes slightly complex.

Important sometimes in S - parameter calibration

# Waves and Fourier Transforms (7)

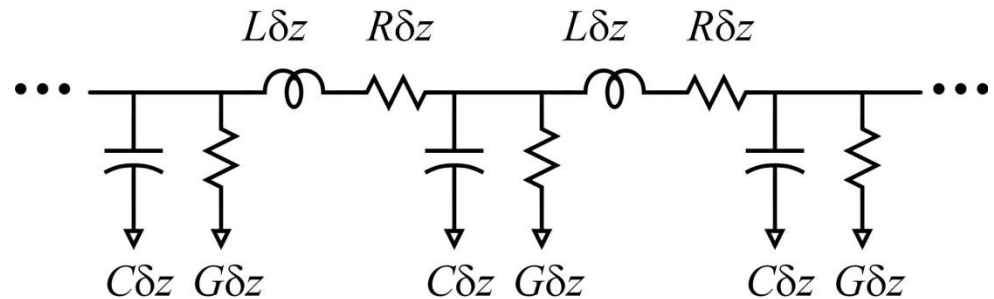

$$\gamma = \pm \sqrt{(R + j\omega L)(G + j\omega C)}$$

Suppose  $R \ll \omega L$  and  $G \ll j\omega C$ . Use  $(1 + \varepsilon)^N = 1 + N\varepsilon + O(\varepsilon^2)$

$$\gamma = \pm \sqrt{(j\omega L)(j\omega C)} \sqrt{1 + R/j\omega L} \sqrt{1 + G/j\omega C}$$

$$\cong \pm j\omega \sqrt{LC} \cdot (1 + R/j2\omega L)(1 + G/j2\omega C)$$

$$\gamma \cong \pm \left[ \frac{R}{2\sqrt{L/C}} + \frac{G\sqrt{L/C}}{2} + j\omega \sqrt{LC} \right]$$

$$\gamma \cong \pm \left[ \frac{R}{2Z_0} + \frac{GZ_0}{2} + j\omega \sqrt{LC} \right] = \pm [\alpha + j\beta]$$