

## ECE 145a /218A problem set 6a

### Power amplifiers

Problem 1:



The FET has a small-signal parameters as below, and large-signal parameters as given to the right.

$$g_m = 1.0 \text{ mS} / \mu\text{m} \cdot W_g \quad R_i = 1.0 / g_m$$

$$C_{gd} = 0.0 \text{ fF} / \mu\text{m} \cdot W_g$$

$$C_{gs} = 1.5 \text{ fF} / \mu\text{m} \cdot W_g$$
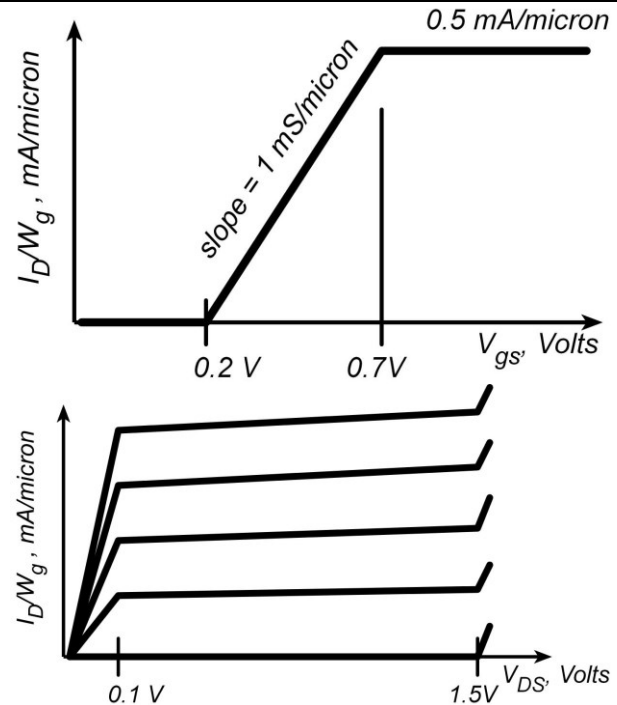 
$$G_{ds} = 0.1 \text{ mS} / \mu\text{m} \cdot W_g$$



The maximum safe drain-source voltage is 1.1 Volts, and the maximum drain current is 1.5mA per micron of gate width  $W_g$ . The maximum gate width *for an individual FET finger* is 2 microns, if we wish to maintain the low input resistance  $R_i$  given above.

a) If we construct a multi-finger FET with \*100\* such fingers, each of 2 microns width, in parallel, find the overall  $g_m$ ,  $R_i$ ,  $C_{gs}$ ,  $R_{ds}$ , of the device. What is the maximum drain current? What are  $f_T$  and  $f_{max}$ ?

b) For this 100-finger device, what is the optimum load impedance for maximum saturated output power? Caution: you should \*not\* include the parallel loading of  $R_{DS}$  in this calculation; this is a subtle point which arises because, in real FETs,  $R_{DS}$  is bias-dependent and becomes infinite at zero drain current.

c) Ignoring  $R_{DS}$  (setting it to infinity), and choosing a design frequency of  $f_{max}/10$ , design a lumped LC matching network to match the input to 50 Ohms. Design a simple quarter-wave microstrip network to load the transistor with the optimum impedance

d) Under the above conditions, calculate by hand the maximum amplifier output power and its power gain. Hint: it is not necessary to know the element values of the matching network to do this.

e) Using Wilkinson Power-combiners, shown above, and \*four\* power amplifiers from

part (c), above, draw the schematic for a 4:1 corporate power-combined power amplifier.  
What would the total maximum saturated output power now ?