

---

# ***ECE145A / 218A Notes : Basic Analysis of Analog Circuits***

***Mark Rodwell***

***University of California, Santa Barbara***

# Comment

---

This (2009) is a transitional year:

Next year 145abc will be reorganized,

145a: fundamentals (devices, analog & RF analysis, models)

145cb: RF systems at IC and system level

This year:

some students have taken 145c:

already have device models

already know analog circuit analysis well

some students have not

must cover device models

must review some circuit analysis methods

These notes: shortened version (2009 only) of device models

# Transistor Circuit Design

---

## *This note set*

- reviews the basics
- starts at the level of a first IC design course
- moves very quickly


## *This will*

- establish a common terminology
- accommodate capable students having minimal background in ICs.

# **DC models**

## **DC bias analysis**

# Large-Signal Model For Bias Analysis

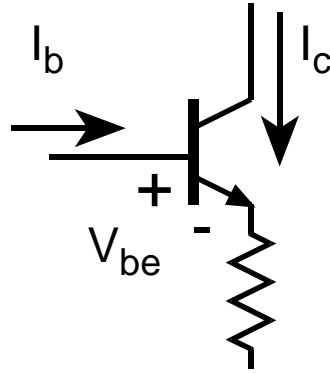


Provided that  $V_{ce} > 0$ ,

$I_c = I_s \exp(V_{be} / V_T)$  and  $I_b = I_c / \beta$ , where  $V_T = kT / q$

...note that  $V_{be}$  is specified internal to the emitter resistance  $R_{ex}$

The  $I_e R_{ex}$  drop is significant for HBTs operating at current densities near that required for peak transistor bandwidth.

# DC Bias Example: Current Mirror

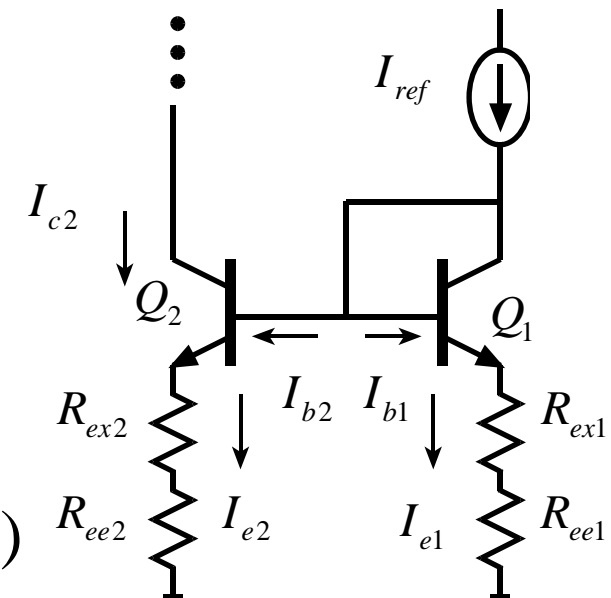

We have  $V_{be1} + I_{e1}(R_{ex1} + R_{ee1}) = V_{be2} + I_{e2}(R_{ex2} + R_{ee2})$

and  $V_{be1} = V_t \ln(I_{c1} / I_{s1})$ ,  $V_{be2} = V_t \ln(I_{c2} / I_{s2})$


Assume that  $\beta \gg 1$ ,  $R_{ee2} = 2R_{ee1}$

& assume that  $A_{E1} = A_{E2}$  ( $A_E$  is the emitter area).

This implies  $R_{ex1} = R_{ex2} / 2$ , and  $I_{s1} = 2I_{s2}$ ,

from which we find  $I_{c2} = I_{c1} / 2$

# Simpler DC Model for Bias Analysis

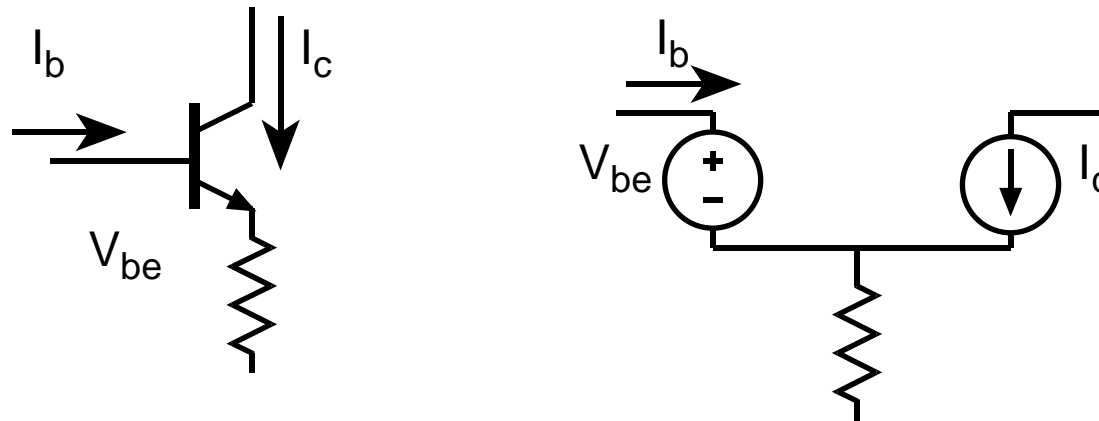


It is often sufficient in bias analysis to ignore the variation of  $V_{be}$  with  $I_c$  and instead take  $V_{be} = V_{be,on} = \phi$ .

$V_{be,on}$  depends upon current density and technology.

Biased at current densities within  $\sim 10\%$  of peak bandwidth bias,

$$V_{be,on} = \phi \sim \begin{cases} 0.9 \text{ V Modern Si/SiGe HBTs} \\ 0.7 \text{ or } 0.9 \text{ V InGaAs/InP HBTs} \\ 1.4 \text{ V GaAs/GaInP HBTs} \end{cases}$$

# Simple DC Bias Example

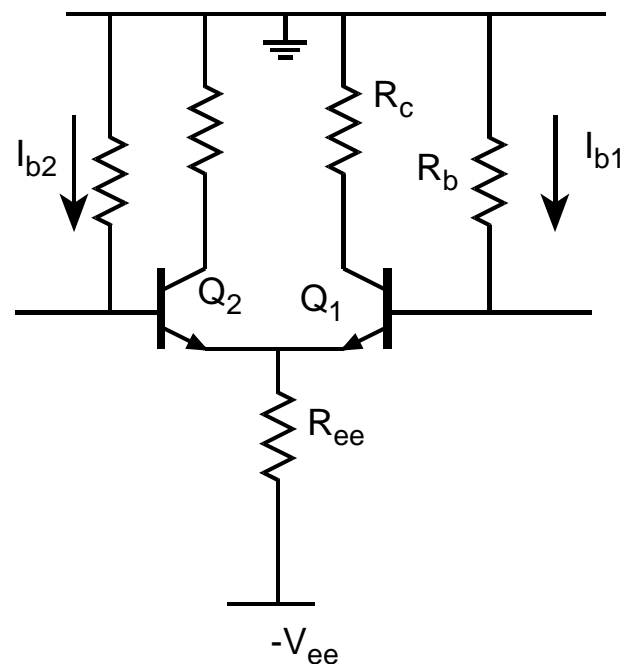

If we neglect the  $I_b R_b$  drops, then  $V_{b1} = V_{b2} = 0$  Volts.

Approximate  $V_{e1} = V_{e2} = -\phi \cong -0.9$  V (SiGe).

$$I_{c1} + I_{c2} = 2I_{c1} = (-V_{ee} - 0.9V) / R_{ee}$$

$$I_{c1} = I_{c2} = (-V_{ee} - 0.9V) / 2R_{ee}$$



# Efficiently Handling Base Currents In Bias Analysis

If  $I_b R_b$  drop is significant,

one can solve simultaneous equations :

$$I_{c1} + I_{c2} = 2I_{c1} = (-V_{ee} - \phi - I_{b1} R_b) / R_{ee}$$

where  $I_{b1} = I_{c1} / \beta$ ,


Quicker : find by iteration :

- 1) solve  $I_{c1} = (-V_{ee} - \phi) / 2R_{ee}$

- 2) solve  $I_{b1} \cong I_{c1} / \beta$

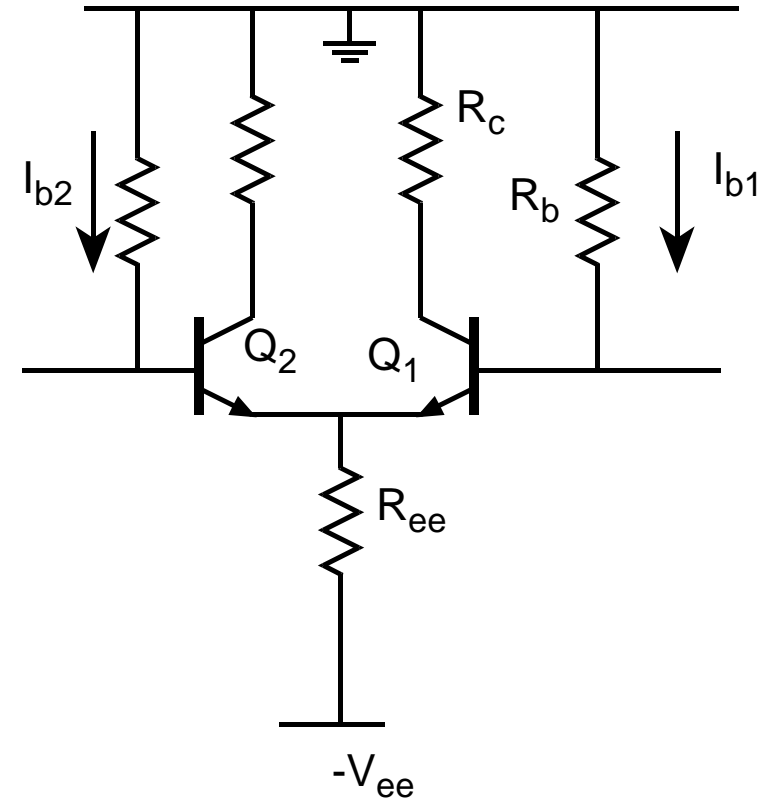- 3) use this value of  $I_b$  to solve  $I_{c1} = (-V_{ee} - \phi - I_{b1} R_b) / 2R_{ee}$

Works because any well - designed circuit has DC bias only weakly dependent upon  $\beta$ .




# **small-signal baseband analysis**

# Hybrid- $\pi$ Bipolar Transistor Model


$$R_{be} = \beta / g_m$$

$$\tau_f = \tau_b + \tau_c$$

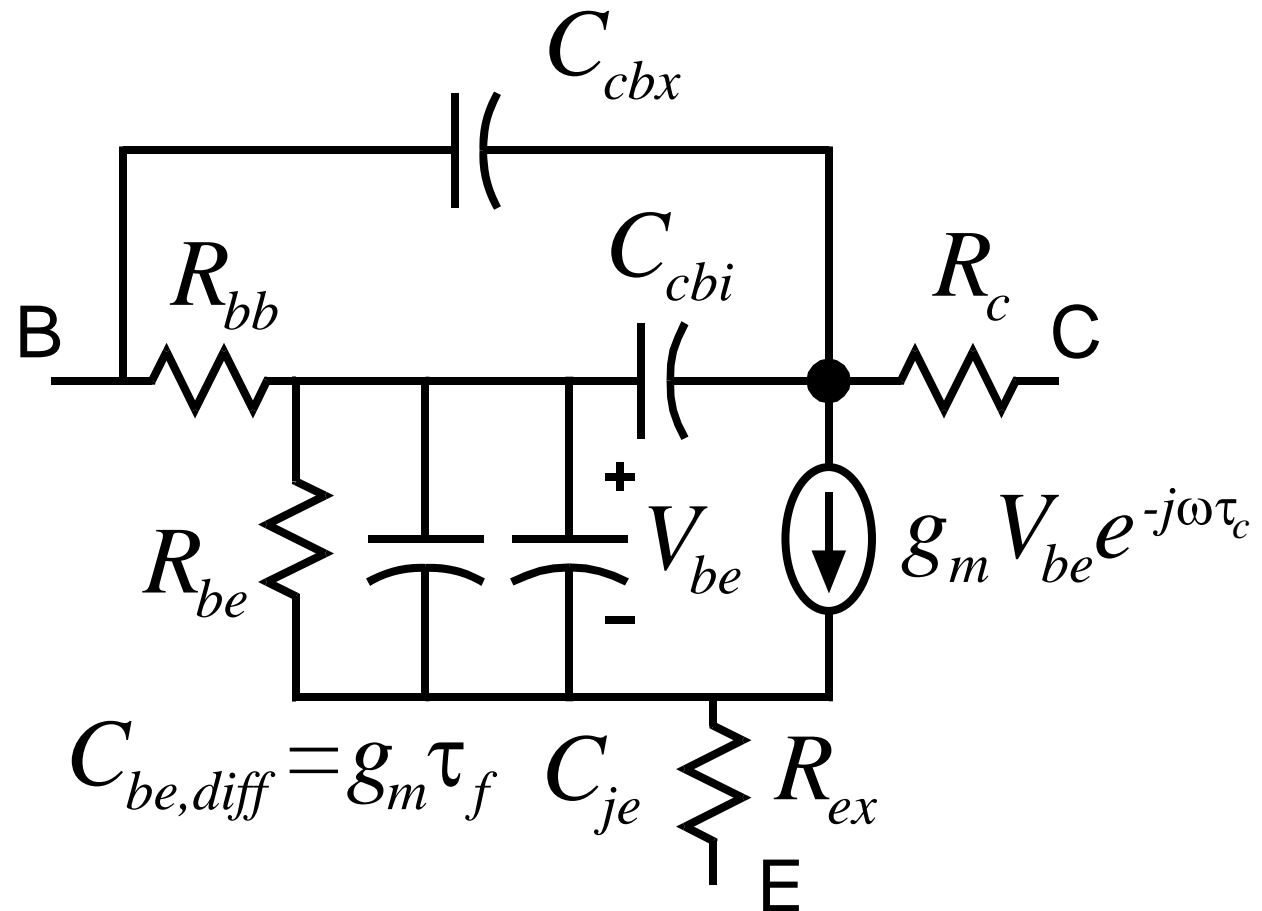

Accurate model, but too detailed for quick hand analysis
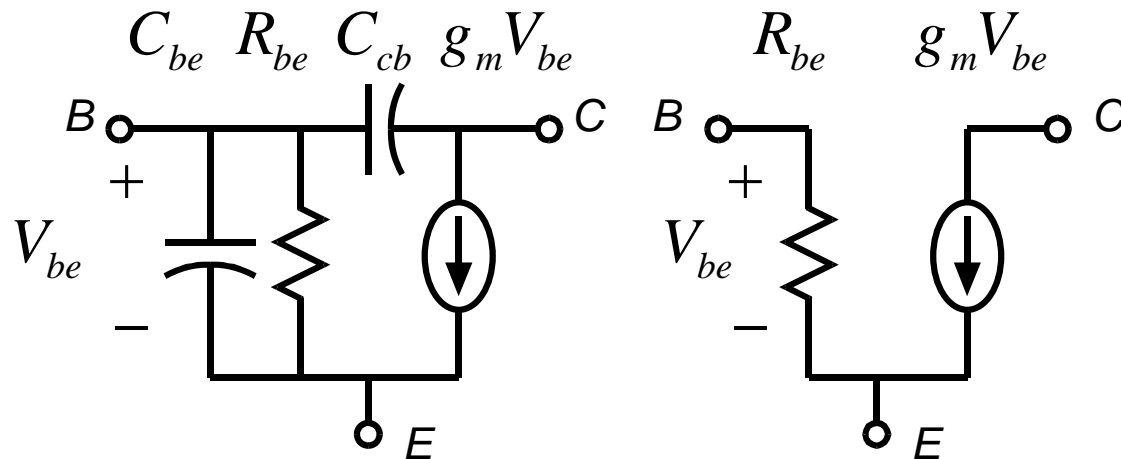
# Oversimplified Model for Quick Hand Analysis




In most high-frequency circuits, the node impedance is low and  $R_{ce}$  is therefore negligible.

Neglecting  $R_{bb}$  in high-frequency analysis is a poor approximation but is nevertheless common in introductory treatments.

The "textbook" analyses which follow use this oversimplified model. These introductory treatments will later be refined.


# Common Emitter Stage: Basics

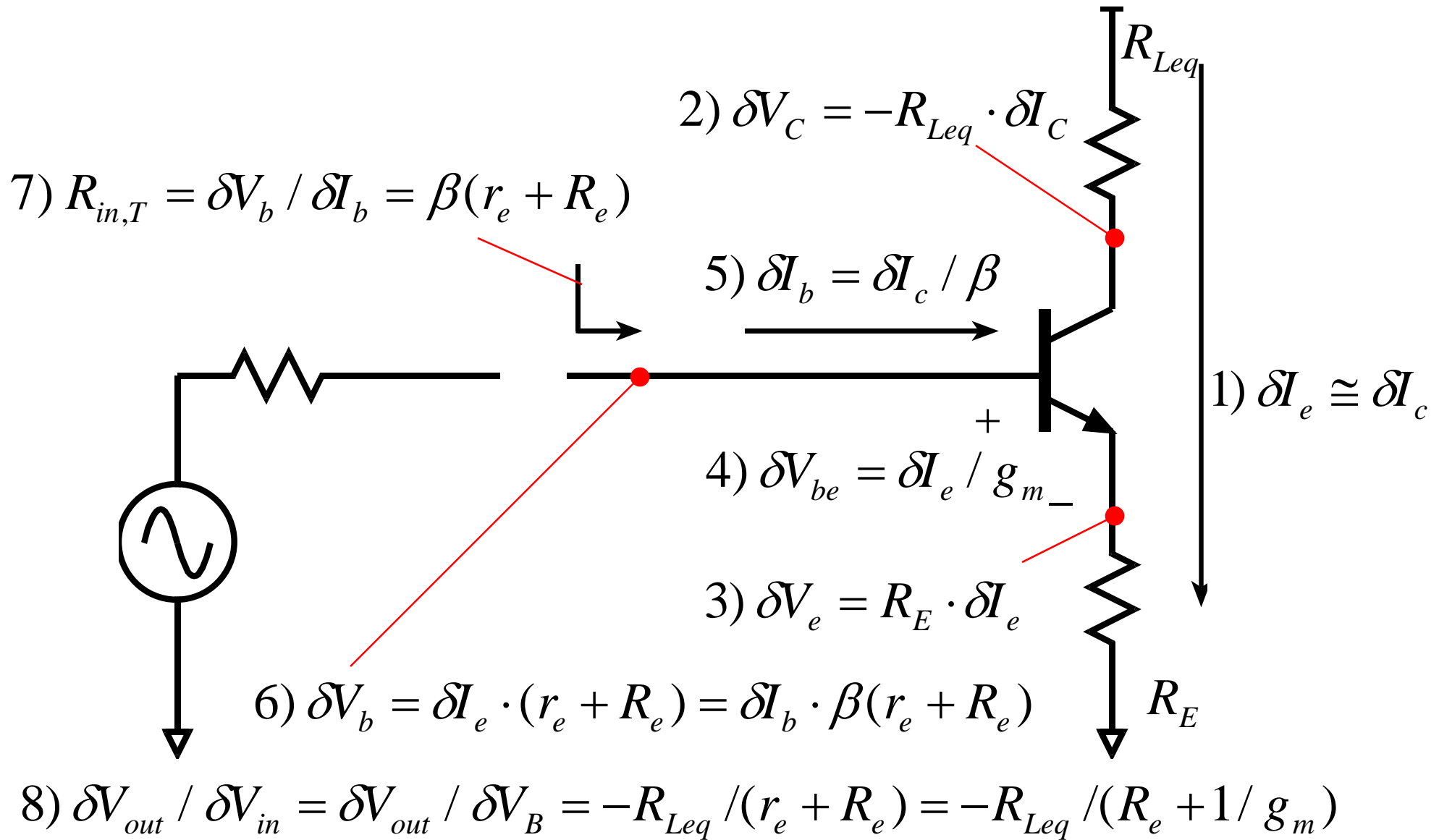

Gain is  $-R_{Leq} / (R_e + 1 / g_m)$ ; Transistor  $R_{in}$  is  $\beta(r_e + R_E)$
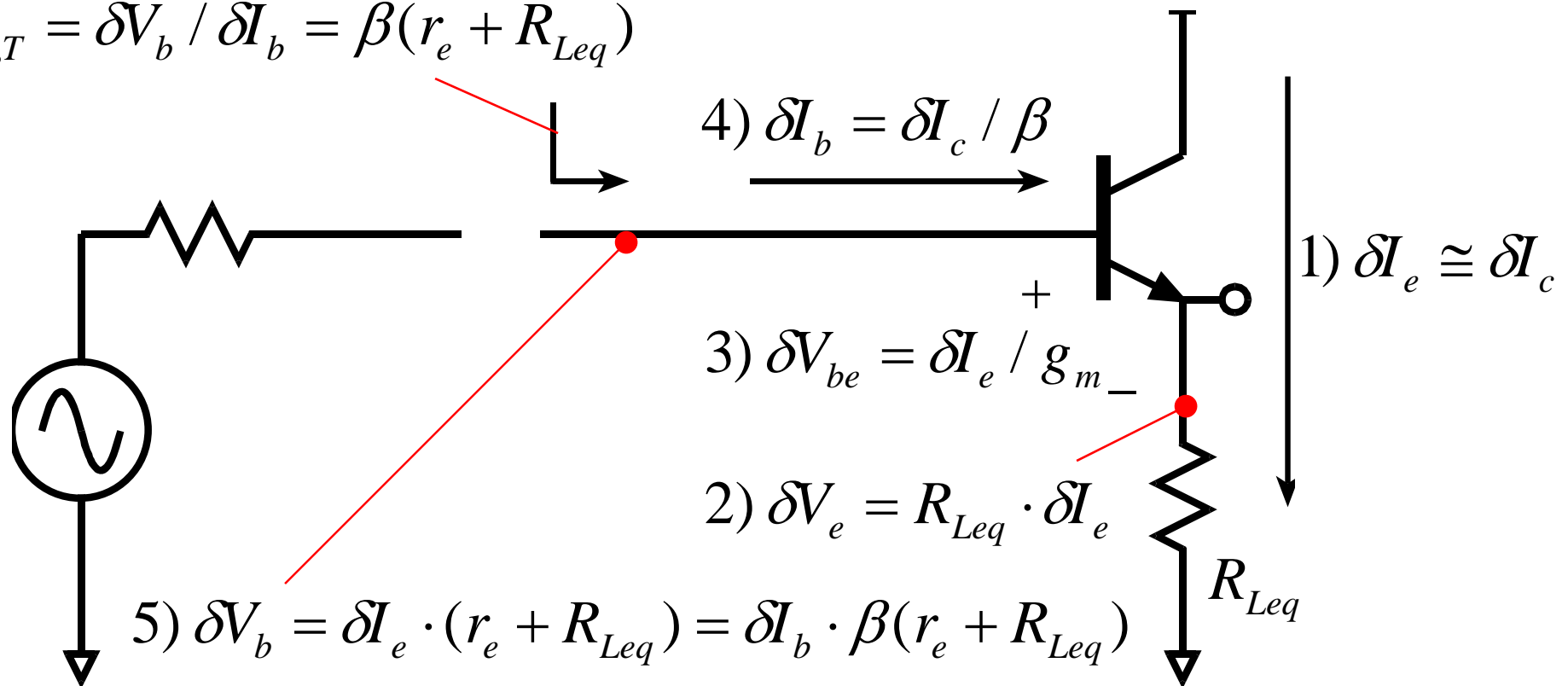
# Emitter Follower Stage: Basics

$$6) R_{in,T} = \delta V_b / \delta I_b = \beta(r_e + R_{Leq})$$



$$7) \delta V_{out} / \delta V_{in} = \delta V_{out} / \delta V_E = R_{Leq} / (r_e + R_{Leq}) = R_{Leq} / (R_{Leq} + 1 / g_m)$$


Gain is  $R_{Leq} / (R_{Leq} + 1 / g_m)$ ; Transistor  $R_{in}$  is  $\beta(r_e + R_E)$

# Common-Base Stage: Basics

$$6) \delta V_{in} = \delta I_e \cdot (r_e + R_b / \beta)$$

$$2) \delta V_{out} = R_{Leq} \cdot \delta I_c$$

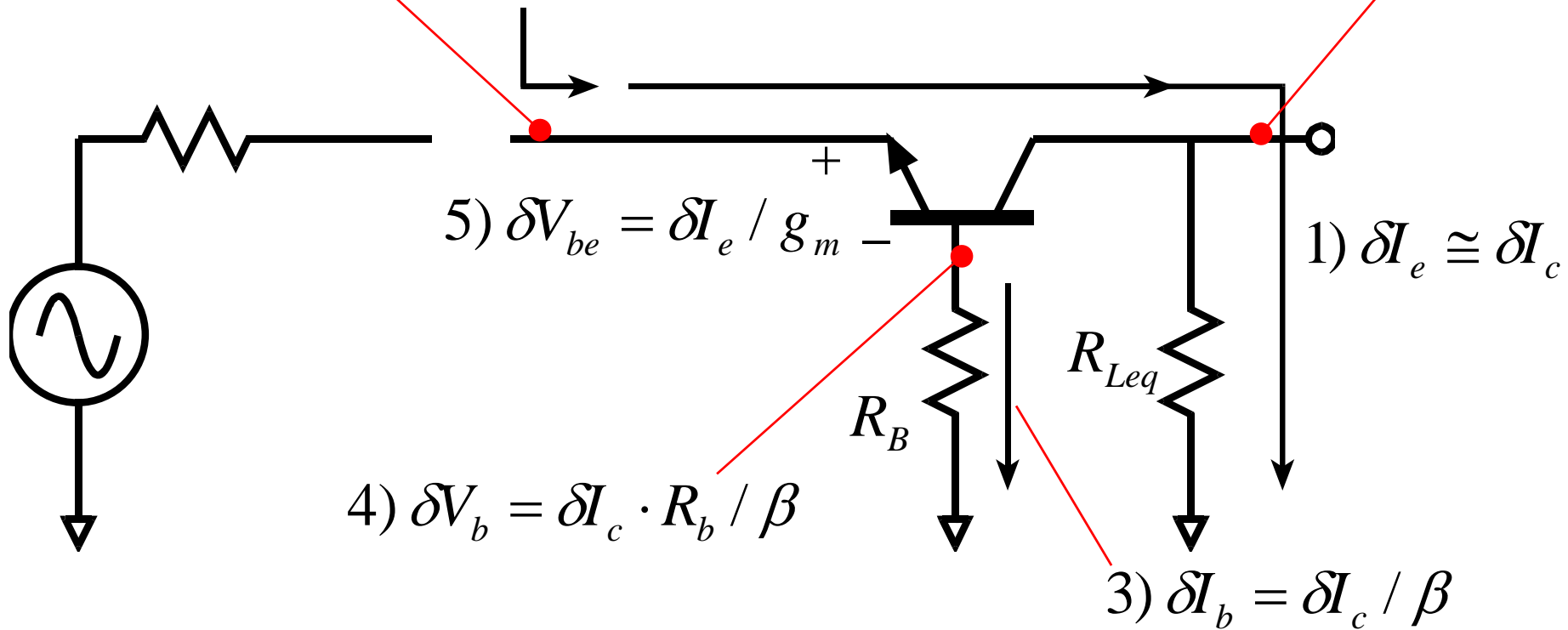
$$7) R_{in,T} = \delta V_e / \delta I_e = r_e + R_B / \beta$$



$$7) \delta V_{out} / \delta V_{in} = R_{Leq} / (r_e + R_b / \beta)$$

Gain is  $R_{Leq} / (r_e + R_b / \beta)$ ; Transistor  $R_{in}$  is  $r_e + R_b / \beta$

# Emitter Follower Output Impedance

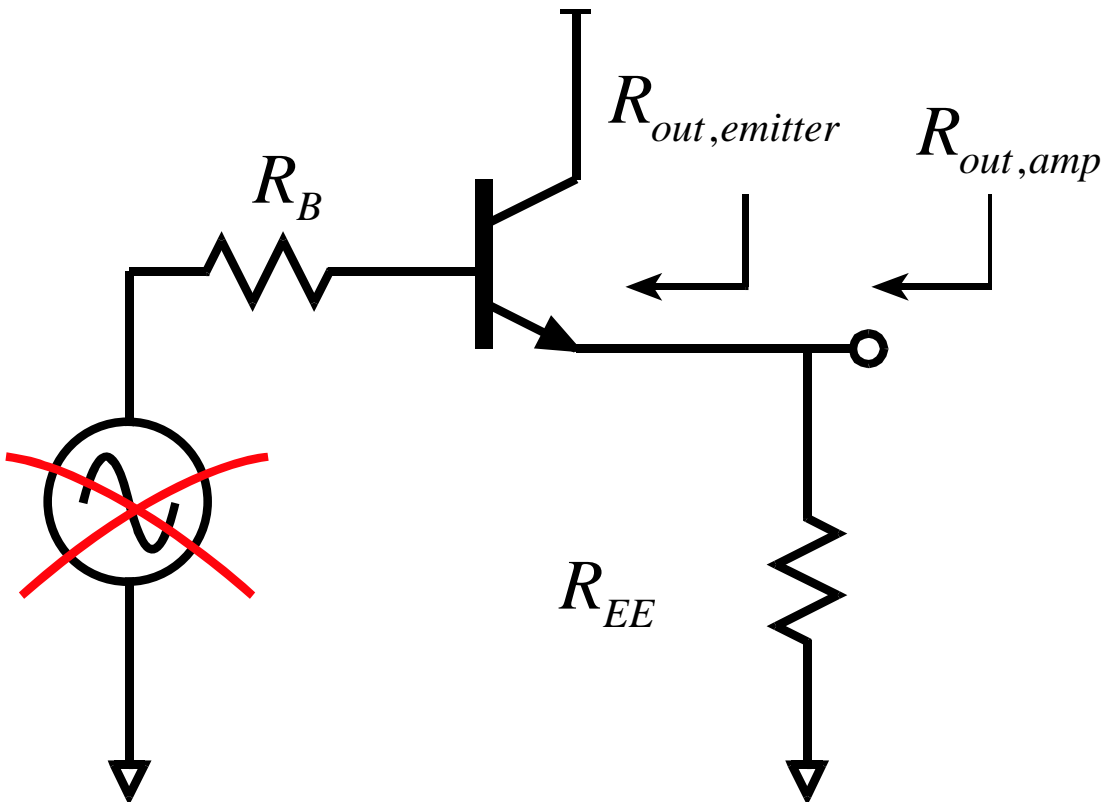


## Common-Base Stage: Basics

$$6) \delta V_{in} = \delta I_e \cdot (r_e + R_b / \beta)$$

$$2) \delta V_{out} = R_{Leq} \cdot \delta I_c$$
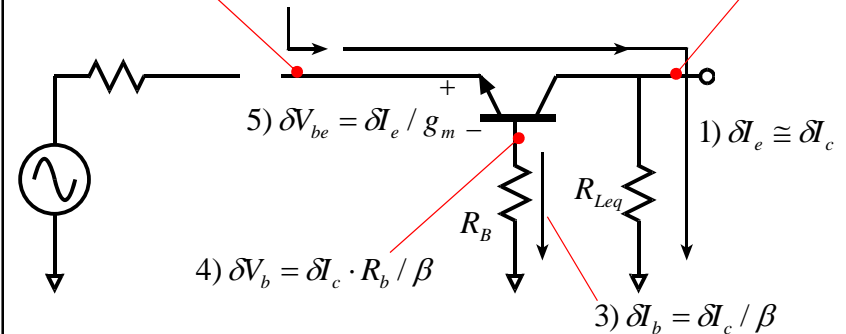
$$7) R_{in,T} = \delta V_e / \delta I_e = r_e + R_B / \beta$$



$$5) \delta V_{be} = \delta I_e / g_m$$

$$1) \delta I_e \cong \delta I_c$$

$$4) \delta V_b = \delta I_c \cdot R_b / \beta$$

$$3) \delta I_b = \delta I_c / \beta$$

$$7) \delta V_{out} / \delta V_{in} = R_{Leq} / (r_e + R_b / \beta)$$

Gain is  $R_{Leq} / (r_e + R_b / \beta)$ ; Transistor  $R_{in}$  is  $r_e + R_b / \beta$


E.F. output impedance is same problem as C.B. input impedance

$$R_{out,emitter} = r_e + R_B / \beta = 1 / g_m + R_B / \beta$$

$$R_{out,amp} = R_{out,emitter} \parallel R_{EE}$$



# Including Bias Circuit Resistances

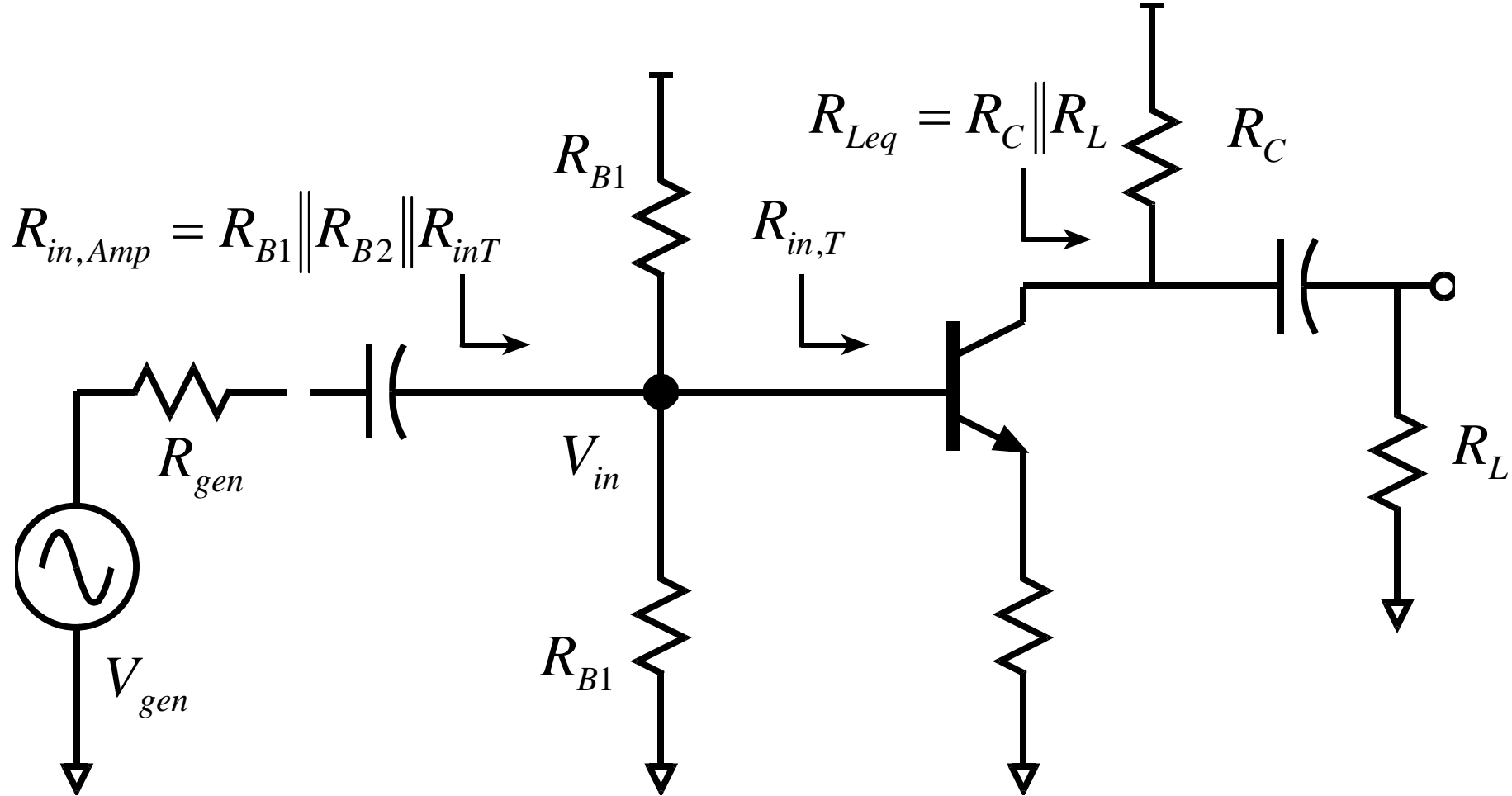

These are (trivially) added in parallel with the transistor terminal impedances to determine the net circuit impedances.


From which,  $V_{in} / V_{gen} = R_{in,amp} / (R_{in,amp} + R_{gen})$ , etc.

# Baseband Analysis Of Multistage Circuits

*For baseband analysis of multi-stage circuits,  
simply break into individual stages.*


*Load impedance of the Nth stage includes the input  
impedance of the (N+1)<sup>th</sup> stage*

*Analysis is then trivial...*

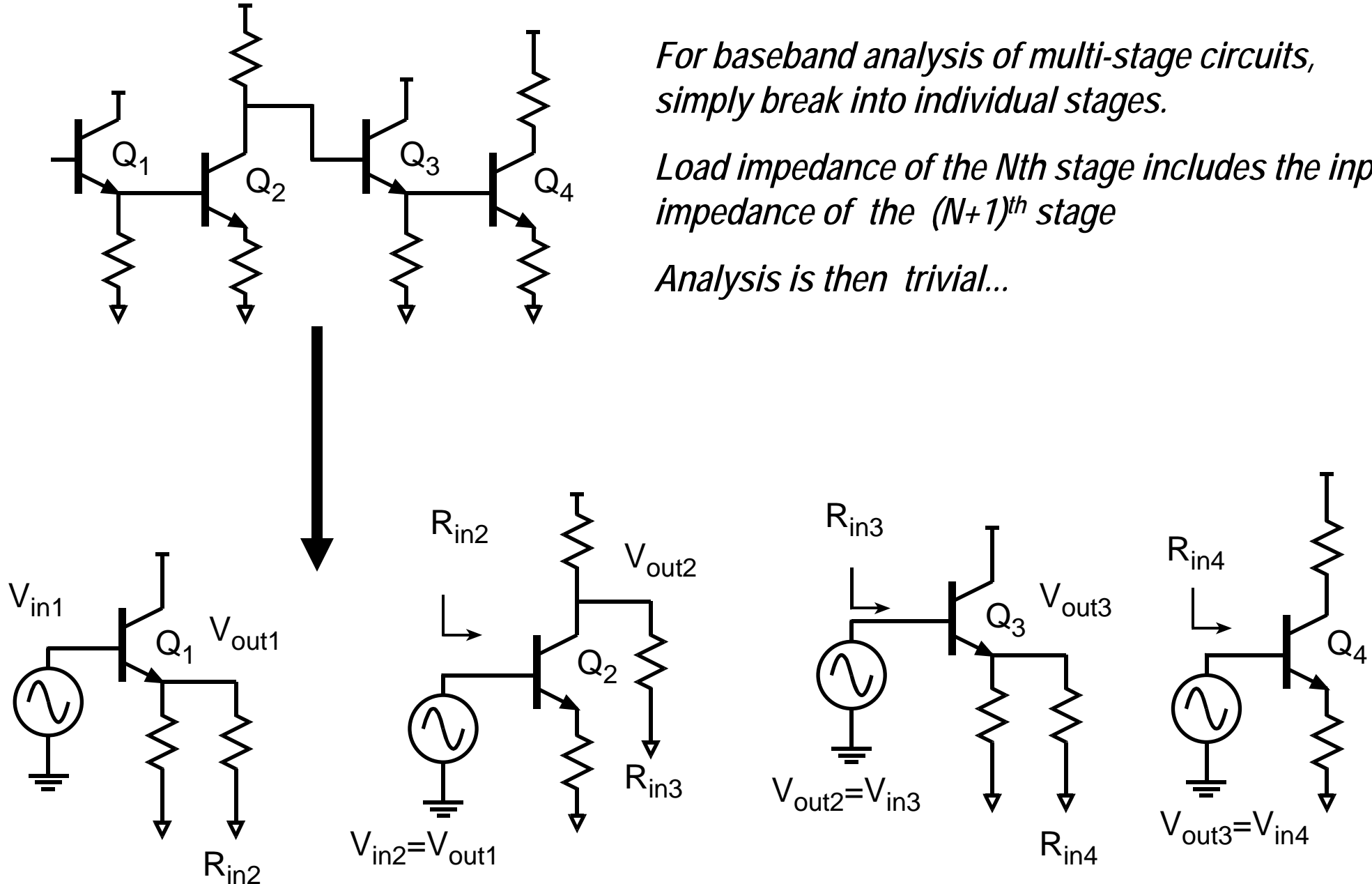

# **small-signal baseband analysis**
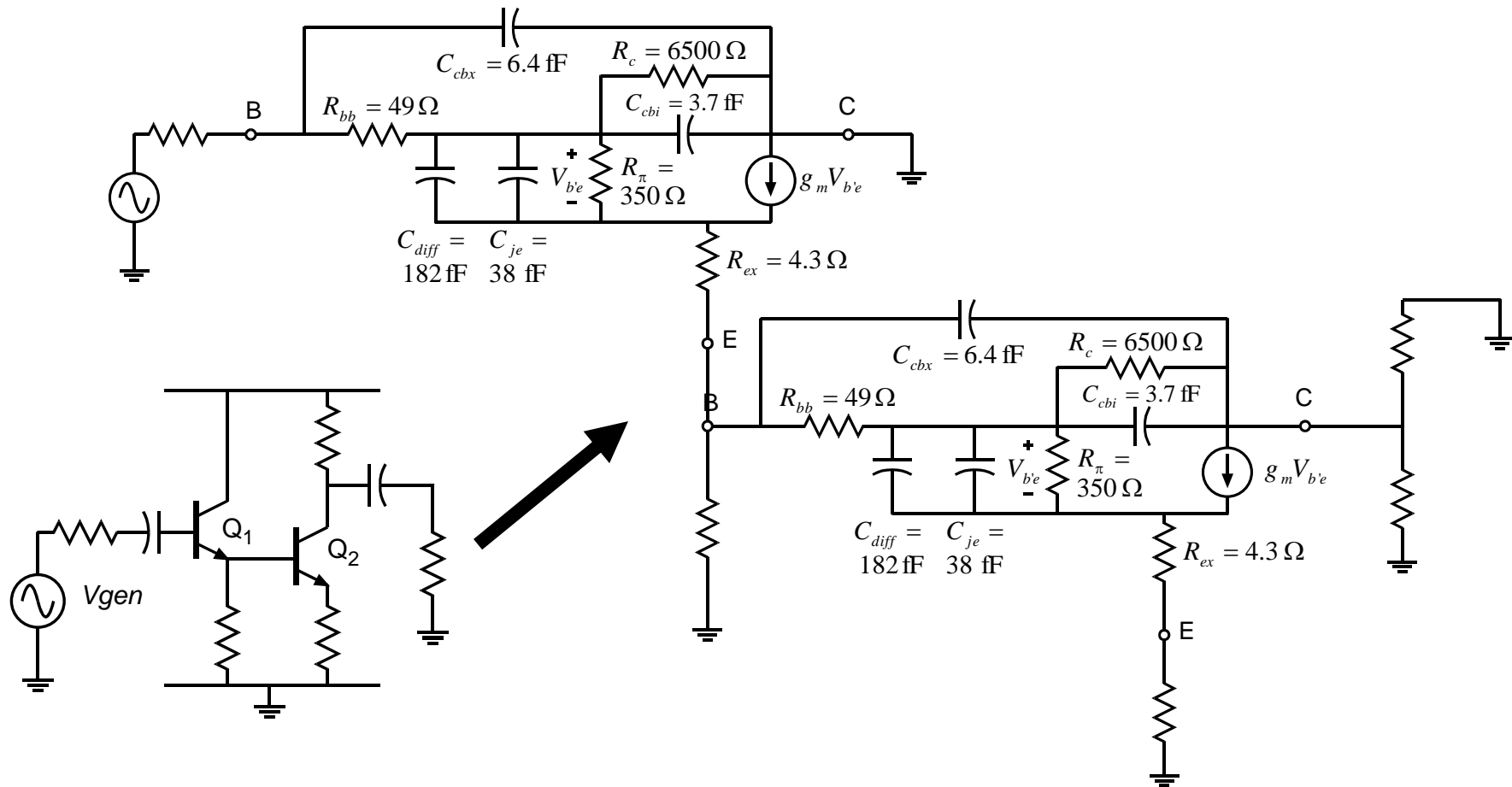
# High-Frequency Analysis: The General Problem



Analyzing frequency response is difficult: cannot separate stage-by-stage


Method #1: nodal analysis: accurate, general, tedious.

Method #2: method of time constants: accurate, limited applicability, quick & intuitive

# Nodal Analysis

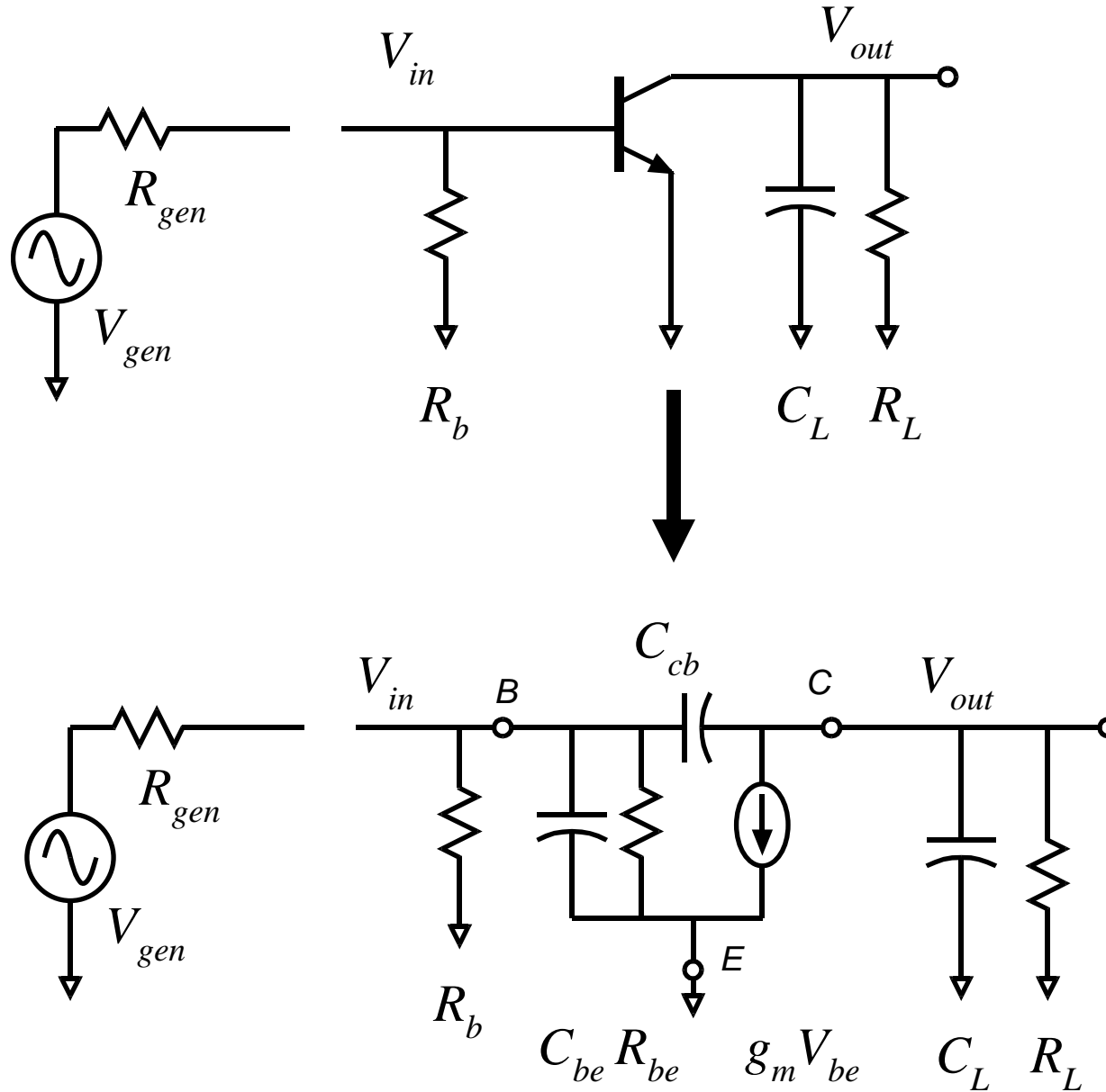
# Tutorial: Transfer Function Analysis: Nodal Analysis I

Simple & very familiar example : common - emitter amplifier.



# Tutorial: Transfer Function Analysis: Nodal Analysis II

Reduced circuit :

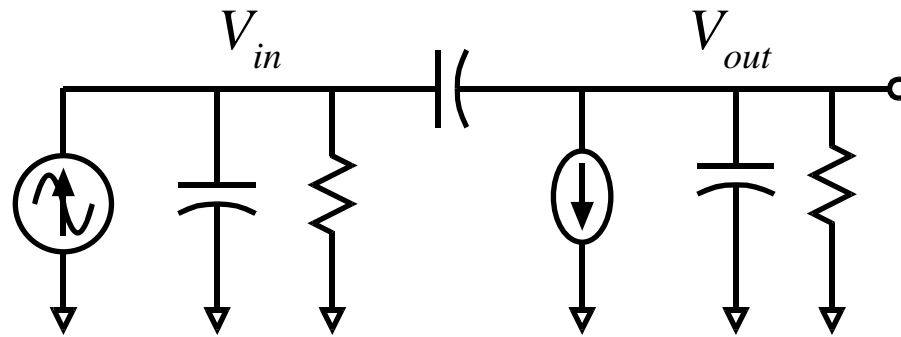

$$(R_i = R_{gen} \parallel R_{be} \parallel R_b)$$

$$I_i = V_{gen}/R_{gen} \quad C_{be} \quad R_i \quad g_m V_{be} \quad C_L \quad R_L$$

Step 1 : Write Nodal Equations from KCL

$$\begin{bmatrix} G_i + sC_{be} + sC_{cb} & -sC_{cb} \\ g_m - sC_{cb} & G_L + sC_L + sC_{cb} \end{bmatrix} \begin{bmatrix} V_{in} \\ V_{out} \end{bmatrix} = \begin{bmatrix} I_i \\ 0 \end{bmatrix}$$

# Tutorial: Transfer Function Analysis: Nodal Analysis III

Step 2: Solve Nodal Equations :

$$V_{out} / I_{in} = N(s) / D(s)$$

$$N(s) = \begin{vmatrix} G_i + sC_{be} + sC_{cb} & 1 \\ g_m - sC_{cb} & 0 \end{vmatrix} = -(g_m - sC_{cb})$$

$$D(s) = \begin{vmatrix} G_i + sC_{be} + sC_{cb} & -sC_{cb} \\ g_m - sC_{cb} & G_L + sC_L + sC_{cb} \end{vmatrix}$$

$$D(s) = (G_i + sC_{be} + sC_{cb})(G_L + sC_L + sC_{cb}) - (g_m - sC_{cb})(-sC_{cb})$$

Step 3: Organize in powers of  $s$

$$\begin{aligned} D(s) &= G_i G_L \\ &+ s(G_i C_L + G_i C_{cb} + G_L C_{be} + G_L C_{cb} + g_m C_{cb}) \\ &+ s^2(C_{be} C_L + C_{be} C_{cb} + C_{cb} C_L + \cancel{C_{cb} C_{cb}} - \cancel{C_{cb} C_{cb}}) \end{aligned}$$



# Tutorial: Transfer Function Analysis: Nodal Analysis IV

Step 4 : Separate into dimensionless ratio - of - polynomials form, separating constants and gains from the transfer function...

$$\frac{V_{out}}{I_{in}} = \frac{V_{out}}{V_{gen} / R_{gen}} = \frac{N(s)}{D(s)}$$

$$= \frac{-(g_m - sC_{cb})}{\left( G_i G_L + s(G_i C_L + G_i C_{cb} + G_L C_{be} + G_L C_{cb} + g_m C_{cb}) + s^2(C_{be} C_L + C_{be} C_{cb} + C_{cb} C_L) \right)}$$

$$\frac{V_{out}}{V_{gen}} = \frac{-(g_m - sC_{cb})R_i R_L / R_{gen}}{\left( 1 + s(R_L C_L + R_L C_{cb} + R_i C_{be} + R_i C_{cb} + g_m R_i R_L C_{cb}) + s^2(C_{be} C_L + C_{be} C_{cb} + C_{cb} C_L)R_i R_L \right)}$$

# Tutorial: Transfer Function Analysis: Nodal Analysis V

note that 
$$\frac{R_i}{R_{gen}} = \frac{(R_{be} \parallel R_b \parallel R_{gen})}{R_{gen}} = \frac{(R_{be} \parallel R_b)}{(R_{be} \parallel R_b) + R_{gen}} = \frac{R_{in,Amp}}{R_{in,Amp} + R_{gen}}$$

SO...

$$\frac{V_{out}}{V_{gen}} = \left( \frac{R_{in,Amp}}{R_{in,Amp} + R_{gen}} \right) (-g_m R_L) \times \frac{-\left(1 - sC_{cb} / g_m\right)}{\left(1 + s(R_L C_L + R_L C_{cb} + R_i C_{be} + R_i C_{cb} + g_m R_i R_L C_{cb}) + s^2(C_{be} C_L + C_{be} C_{cb} + C_{cb} C_L) R_i R_L\right)}$$

$b_1$  (points to  $-g_m R_L$ )  
 $a_1$  (points to  $1 - sC_{cb} / g_m$ )  
 $a_2$  (points to  $s^2(C_{be} C_L + C_{be} C_{cb} + C_{cb} C_L) R_i R_L$ )

$$\Rightarrow \frac{V_{out}(s)}{V_{gen}(s)} = \frac{V_{out}}{V_{gen}} \Big|_{mid-band} \frac{1 + b_1 s}{1 + a_1 s + a_2 s^2}$$

# Tutorial: Transfer Function Analysis: Nodal Analysis VI

Step 5 : Find the roots (poles & zeros) of the polynomial

$$\frac{V_{out}(s)}{V_{gen}(s)} = \frac{V_{out}}{V_{gen}} \Big|_{mid-band} \frac{1 + b_1s}{1 + a_1s + a_2s^2} = \frac{V_{out}}{V_{gen}} \Big|_{mid-band} \frac{1 + b_1s}{(1 - s/s_{p1})(1 - s/s_{p2})}$$

what are efficient methods of finding the poles ?

# **Finding Poles from Transfer Functions**

# Finding Poles and Zeros

---

Ratio - of - Polynomial Form :

$$\frac{V_{out}(s)}{V_{gen}(s)} = \left. \frac{V_{out}}{V_{gen}} \right|_{\text{at mid-band}} * s^m \frac{1 + b_1s + b_2s^2 + \dots}{1 + a_1s + a_2s^2 + \dots}$$

Poles and Zeros :

$$\frac{V_{out}(s)}{V_{gen}(s)} = \left. \frac{V_{out}}{V_{gen}} \right|_{\text{at mid-band}} * s^m \frac{(1 - s/s_{z1})(1 - s/s_{z2})(1 - s/s_{z3})\dots}{(1 - s/s_{p1})(1 - s/s_{p2})(1 - s/s_{p3})\dots}$$

# Finding Poles: Complex Poles

$$\frac{V_{out}}{V_{gen}} = k \frac{1 + b_1s + b_2s^2 + \dots}{1 + a_1s + a_2s^2 + a_3s^3}$$

If  $a_3 / a_2 \ll a_2$  then we can ignore the  $s^3$  at moderate frequencies and


$$\frac{V_{out}}{V_{gen}} \approx k \left( \frac{1 + b_1s + b_2s^2 + \dots}{1 + a_1s + a_2s^2} \right)$$

If the roots of this are complex, then

$$\frac{V_{out}}{V_{gen}} = k \left( \frac{1 + b_1s + b_2s^2 + \dots}{1 + a_1s + a_2s^2} \right) = k \left( \frac{1 + b_1s + b_2s^2 + \dots}{1 + (2\zeta / \omega_n)s + s^2 / \omega_n^2} \right)$$

$$\frac{V_{out}}{V_{gen}} = k \left( \frac{1 + b_1s + b_2s^2 + \dots}{\left(1 - \frac{s}{-\zeta\omega_n + j\omega_d}\right) \left(1 + \frac{s}{-\zeta\omega_n - j\omega_d}\right)} \right)$$
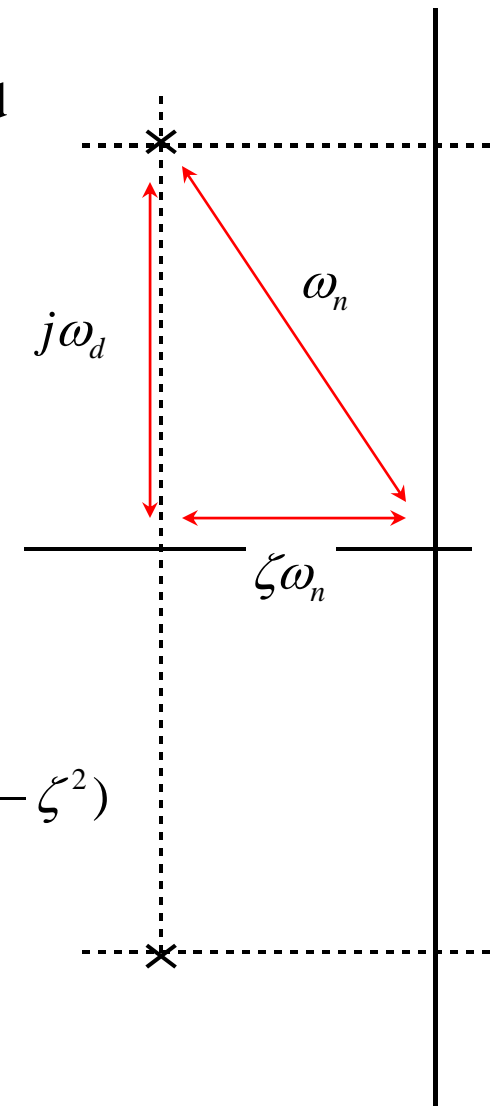
$$\omega_d^2 = \omega_n^2 (1 - \zeta^2)$$




# Finding Poles: Separated Pole Approximation

If the roots are widely separated

e.g.  $(a_2/a_1) \ll a_1$ , then

$$\frac{V_{out}}{I_{in}} = k \left( \frac{1 + b_1s + b_2s^2 + \dots}{1 + a_1s + a_2s^2} \right)$$
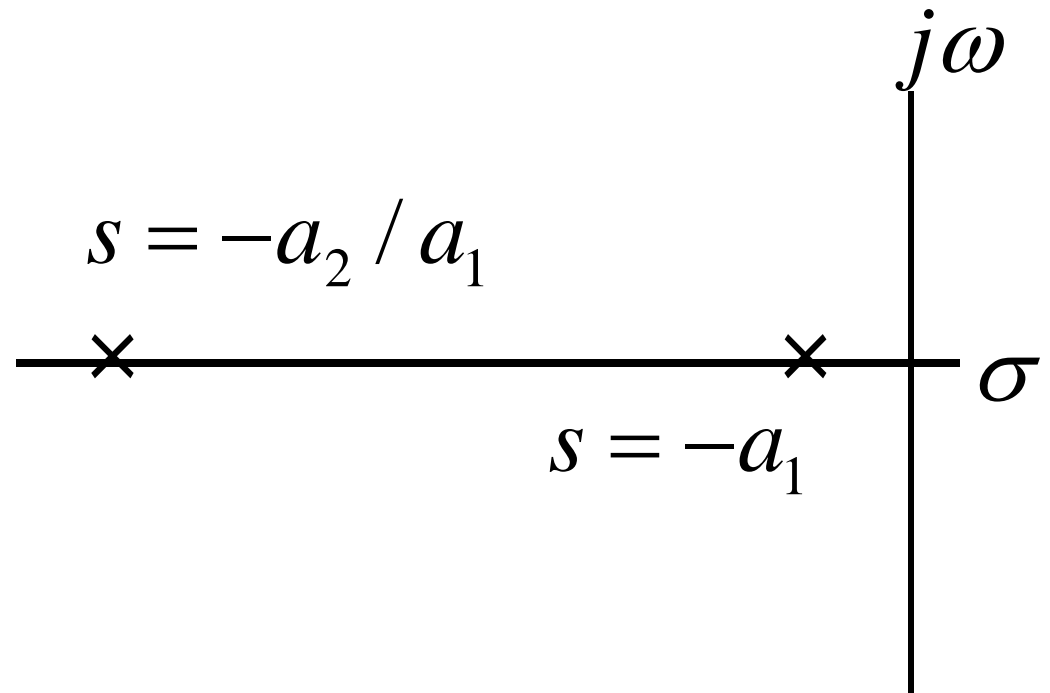
$$\frac{V_{out}}{I_{in}} \cong k \frac{1 + b_1s + b_2s^2 + \dots}{(1 + a_1s) \left( 1 + \left( \frac{a_2}{a_1} \right) s \right)}$$



$a_1$  is the dominant pole.


# **Introductory Circuit Design: summary**



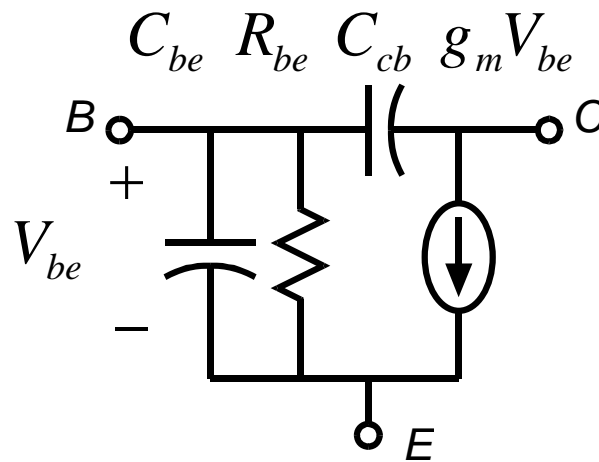
# Gain Stages: Elementary Bandwidth Analysis

---

Using the oversimplified device model below, with  $C_{pi}$  denoting the sum of base-emitter depletion and diffusion capacitances, bandwidth of CE/CB/CC stages can be found....


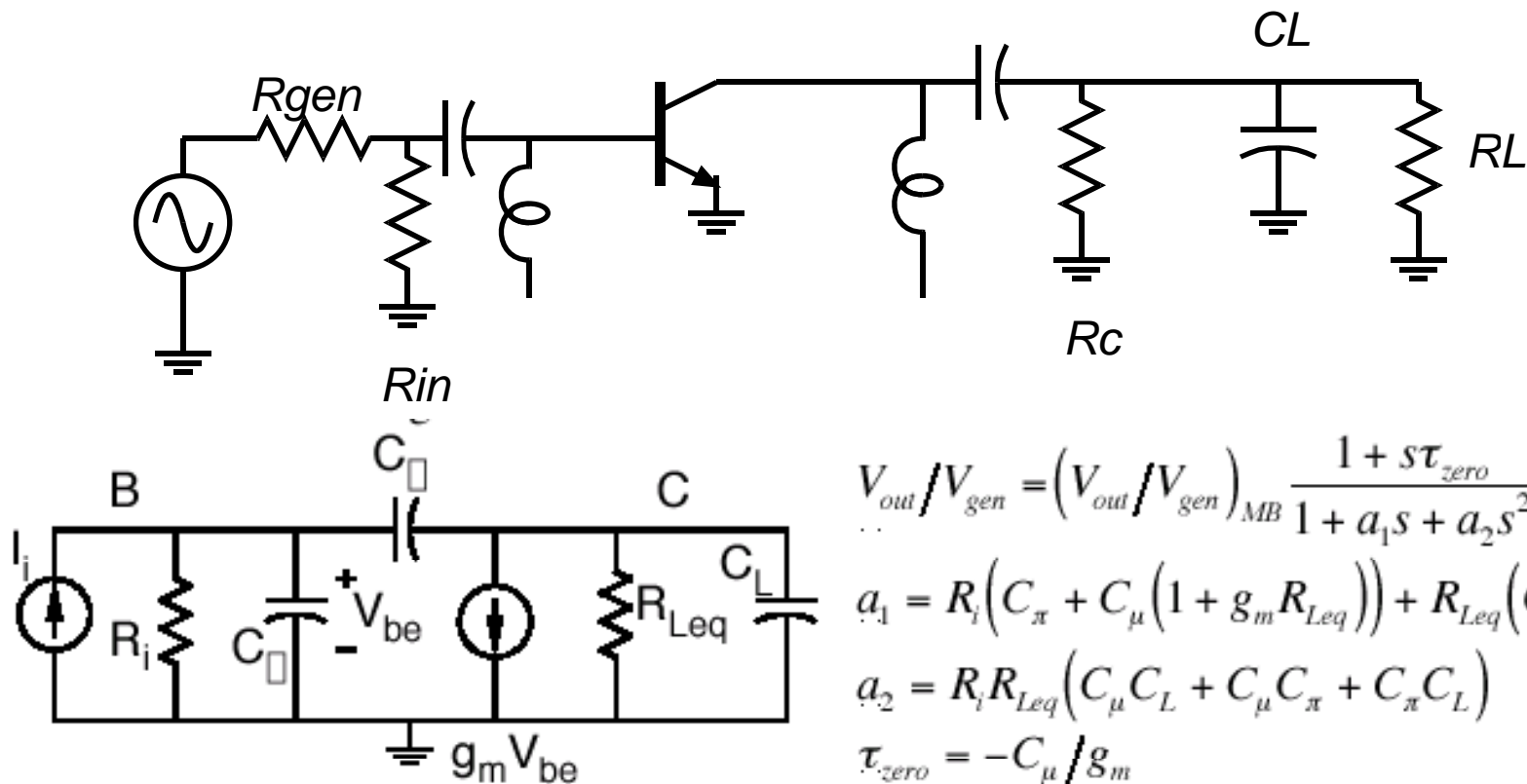
# CE Stage: Elementary Bandwidth Analysis



$$V_{out}/V_{gen} = (V_{out}/V_{gen})_{MB} \frac{1 + s\tau_{zero}}{1 + a_1s + a_2s^2}$$

$$a_1 = R_i \left( C_{\pi} + C_{\mu} (1 + g_m R_{Leq}) \right) + R_{Leq} (C_{\mu} + C_L)$$

$$a_2 = R_i R_{Leq} (C_{\mu} C_L + C_{\mu} C_{\pi} + C_{\pi} C_L)$$



$$\tau_{zero} = -C_{\mu} / g_m$$

$R_i$  is the parallel combination of  $R_{gen}$ ,  $R_{in}$ , and  $R_{\pi}$

$R_{Leq}$  is the parallel combination of  $R_L$ ,  $R_C$ , and  $R_o$

Note in the dominant pole ( $a_1$ ) the miller-multiplication of the collector base capacitance
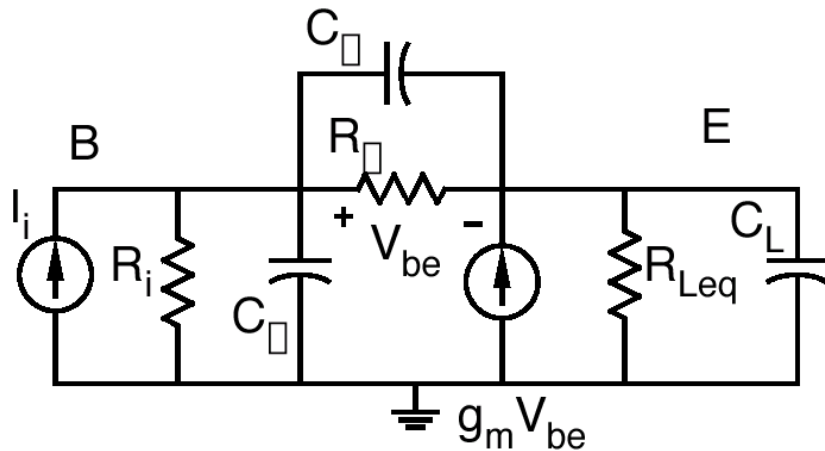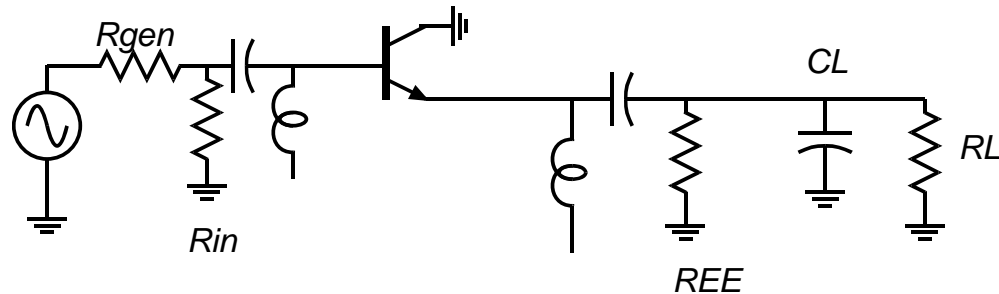
# CC Stage: Elementary Bandwidth Analysis



$$\frac{V_{out}}{V_{gen}} = \left( \frac{V_{out}}{V_{gen}} \right)_{MB} \frac{1 + s\tau_{zero}}{1 + a_1 s + a_2 s^2}$$

given that  $A_{vmb} = \left( r_e / (r_e + R_{Leq}) \right)$ :

$$a_1 = C_\pi \left( R_\pi \left\| \left( r_e \parallel R_{Leq} + R_i (1 - A_{vmb}) \right) \right\| \right)$$

$$+ C_\mu \left( R_i \parallel \text{transistor input resistance} \right)$$

$$+ C_L \left( R_{Leq} \parallel \text{transistor output resistance} \right)$$

$$a_2 = \left( R_i \parallel \text{transistor input resistance} \right) \left( R_{Leq} \parallel r_e \right)$$

$$\times \left( C_\mu C_\pi + C_\mu C_L + C_L C_\pi \right)$$


$$\tau_{zero} = g_m / C_\pi$$

$R_i$  is the parallel combination of  $R_{gen}$ , and  $R_{in}$ ,

$R_{Leq}$  is the parallel combination of  $R_{ee}$  and  $R_L$

Note that the frequency response is a mess. Given  $C_L$ , the transfer function very often has complex poles, and may show strong gain peaking, hence ringing in the pulse response.
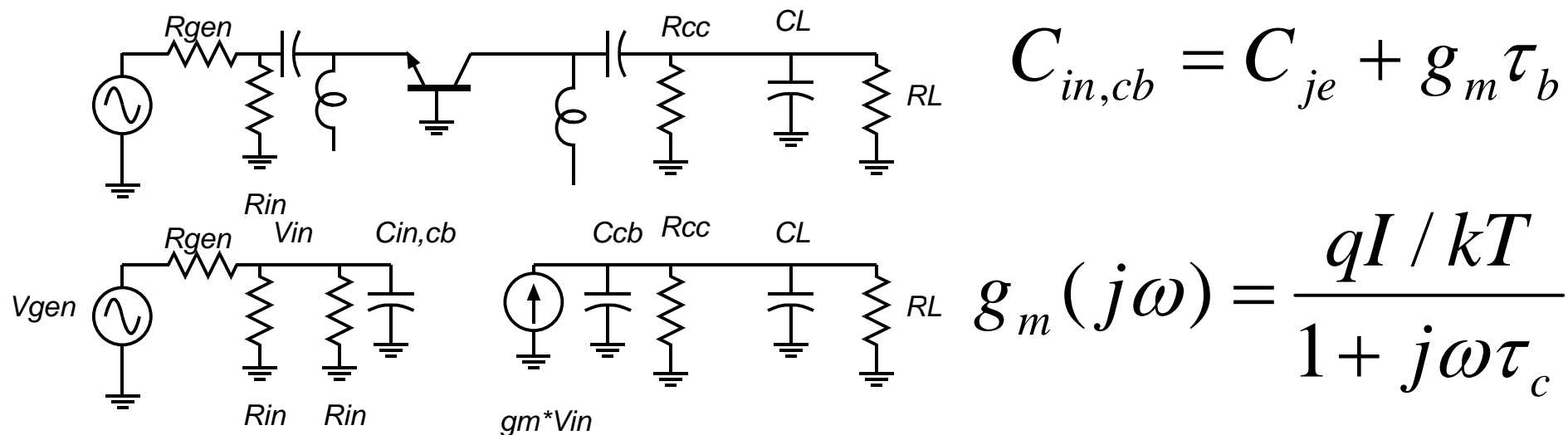
# CB Stage: Elementary Bandwidth Analysis



Here we have a problem. To the extent that the CB stage is modeled by a very very simple hybrid-pi model (explicitly, with zero  $R_{bb}$ ), we find (by very simple analysis) very high bandwidth, with poles having time constants equal to  $\tau_b$ , to  $\tau_c$ , and to the product of the load resistance times  $(C_{cb} + C_L)$ .

## Note that

- 1) **Input capacitance is indeed as noted. Does not include effect of  $\tau_c$**
- 2) **Ignoring  $R_{bb}$  in CB stage analysis, while appealing for simplicity (e.g. undergrad classes) is quite unreasonable, as  $C_{cb}R_{bb}$  often dominates high frequency rolloff.** More regarding this later.

# **Method of Time Constants**

make revision for 2009----first before MOTC, give by summary without derivation the standard stage expressions.

then define MOTC, first and second order  
then show a 1-stage Darlington diff amp, and say caps to ground, caps between inputs and outputs.

Give expression for caps to ground

Give expression for caps between in and out of general block

then use this for CD stage  $C_{gs}$  only

then use this for CC stage  $C_{be}$  only


then do for CE stage  $C_{cb}$  only

then work the full Darlington diff amp

then show how CE (with degen) CB CC are same problem

then re-show stage relationship

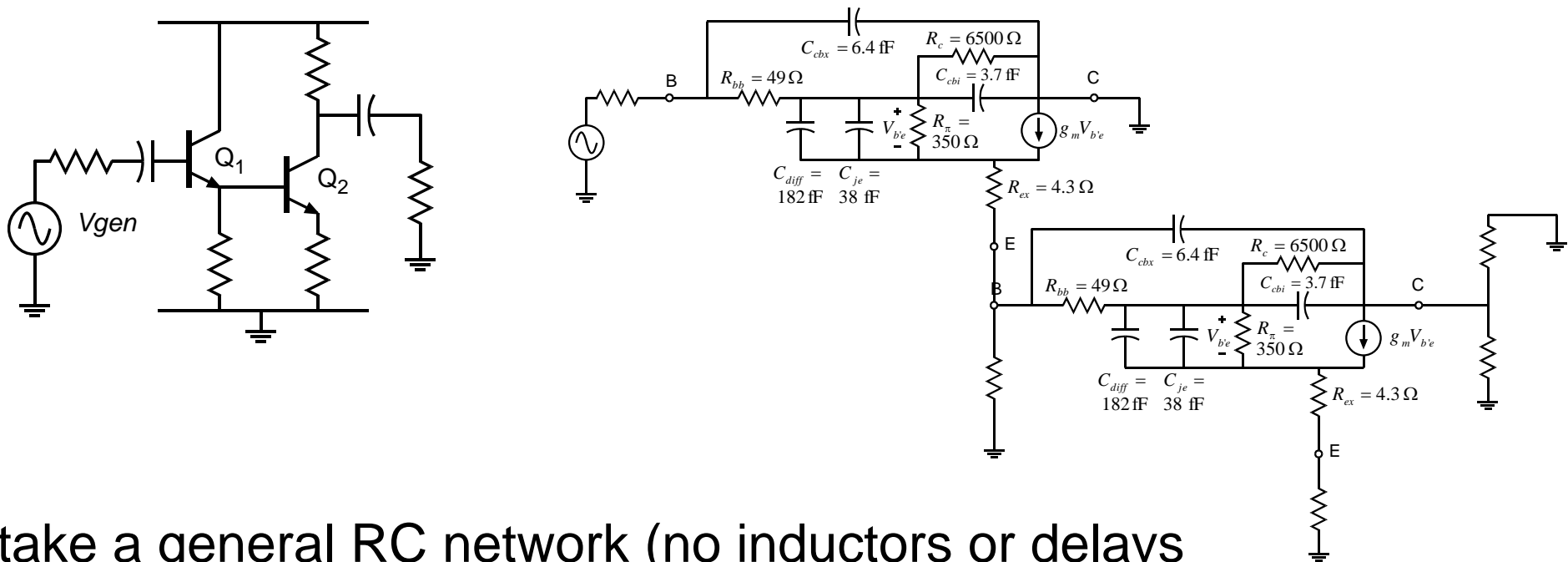
# Finding Bandwidth: Method of Time Constants



take a general RC network (no inductors or delays tau), and separate into 2 parts, network without capacitors, and the capacitors:

# MOTC: Separation into Capacitors & Resistive N-port

---

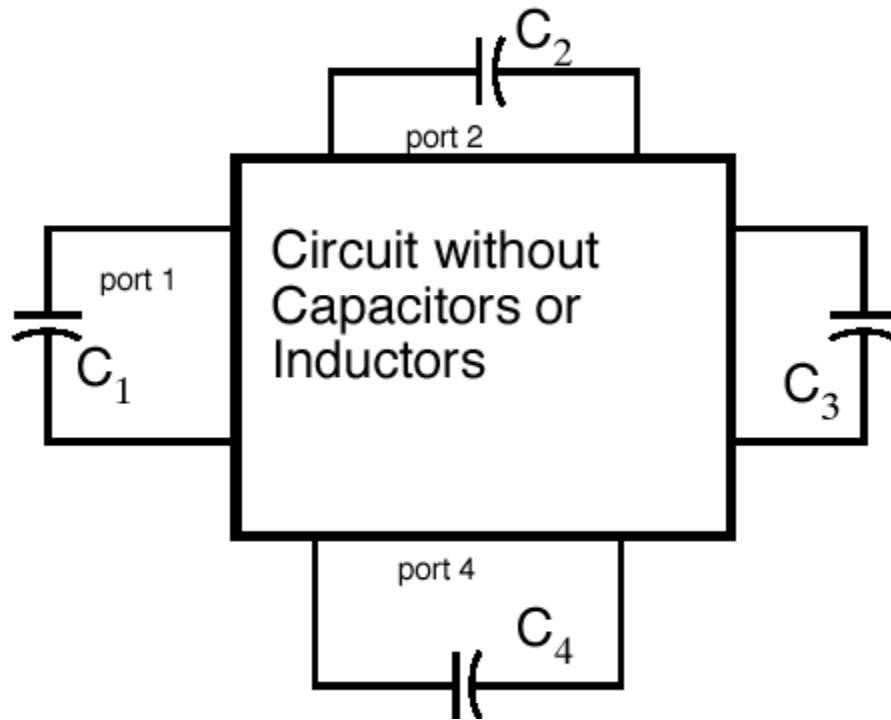


The internal capacitor-free network is now frequency-independent. The MOTC method (not proven here) relies on results from n-port network theory



# MOTC: Open-Circuit Resistances

---

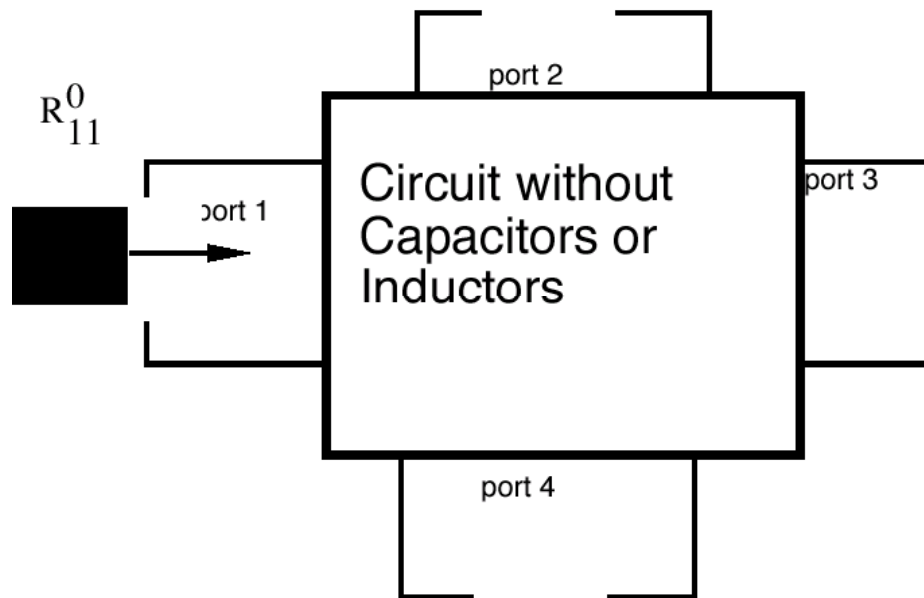

$R_{11}^0$  is the small signal resistance measured at port one with all other ports open - circuited. This is determined by applying a test voltage (or current) at the port and computing from this the resulting current (or voltage)

# MOTC: the Dominant Time Constant

---

$$\frac{V_{out}}{V_{gen}} = \left( \frac{V_{out}}{V_{gen}} \right)_{mb} \frac{1 + b_1s + b_2s^2 + \dots}{1 + a_1s + a_2s^2 + \dots}$$

$$a_1 = R_{11}^0 C_1 + R_{22}^0 C_2 + R_{33}^0 C_3 + R_{44}^0 C_4$$

The MOTC first - order time constants directly give us the dominant time constant  $a_1$  of the circuit. If (and only if) the secondary time constant  $a_2$  is negligible, the 3 - dB bandwidth is  $1 / 2\pi a_1$ . We must use the second - order (short - circuit) time constants to determine  $a_2$ .


# MOTC: Are We Saving Any Work ?

---

Are we saving work relative to brute-force nodal analysis:  
MOTC would be of only moderate value if we had to calculate all the  $R_i$ 's each time. Fortunately, most terms involve quantities ***already found in midband stage analysis: input and output impedances, load impedances, etc.***

# MOTC: Short-Circuit Resistances

---

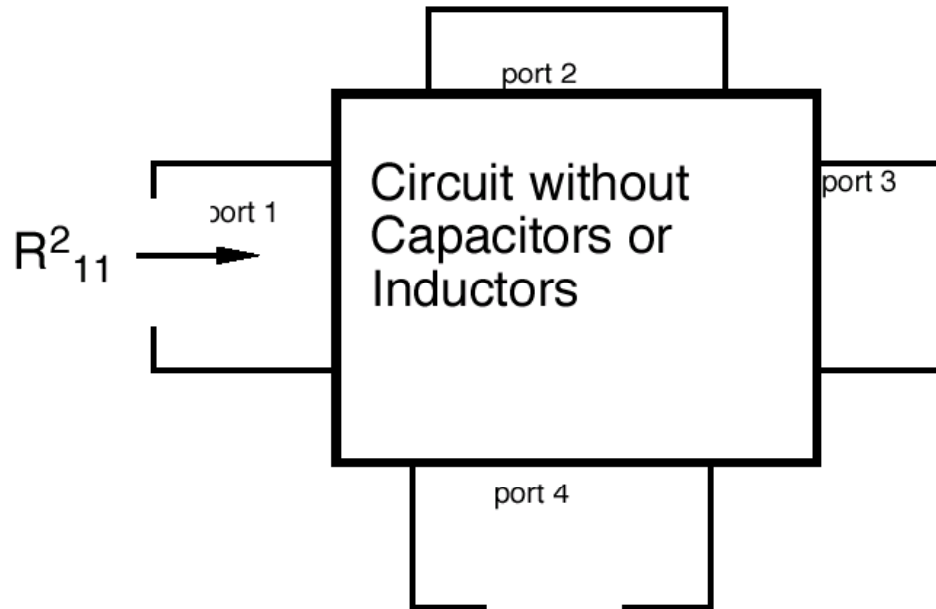

$R_{11}^2$  is the small signal resistance measured at port one with all other ports open - circuited, except for port 2, which is shorted

# MOTC: The Second-Order Time-Constant

---

$$\frac{V_{out}}{V_{gen}} = \left( \frac{V_{out}}{V_{gen}} \right)_{mb} \frac{1 + b_1s + b_2s^2 + \dots}{1 + a_1s + a_2s^2 + \dots}$$

$$a_2 = R_{11}^0 R_{22}^1 C_1 C_2 + R_{11}^0 R_{33}^1 C_1 C_3 + R_{11}^0 R_{44}^1 C_1 C_4 \\ + R_{22}^0 R_{33}^2 C_2 C_3 + R_{22}^0 R_{44}^2 C_2 C_4 + R_{33}^0 R_{44}^3 C_3 C_4$$

notethat  $R_{xx}^0 R_{yy}^x = R_{xx}^y R_{yy}^0$

# MOTC: Working these Efficiently

---



Because  $R_{xx}^y R_{yy}^0 = R_{xx}^0 R_{yy}^x$ , we always have 2 choices in finding each term in the MOTC. The trick is to work the problem so that as much as possible :

- 1) terms are related to input, output, load impedances
- 2) terms are ones found earlier, in  $a_1$  analysis.

There are 2 "funny" cases which arise so often that I will give them on the next 2 pages (note these are intimately related to the well-known Miller effect)


# MOTC and the Miller Effect

$$R_{xx}^y = R_i (1 + A_v) + R_{out}$$

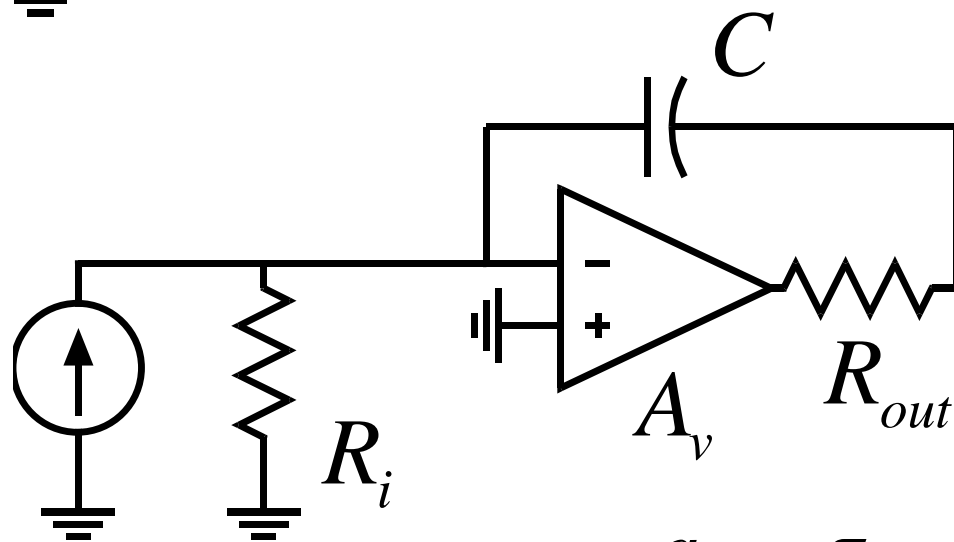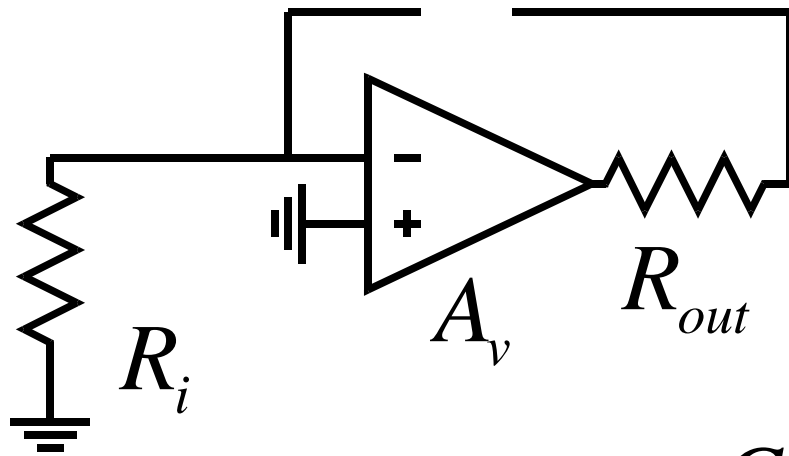

$$a_1 = \tau = [R_i (1 + A_v) + R_{out}] \bullet C$$
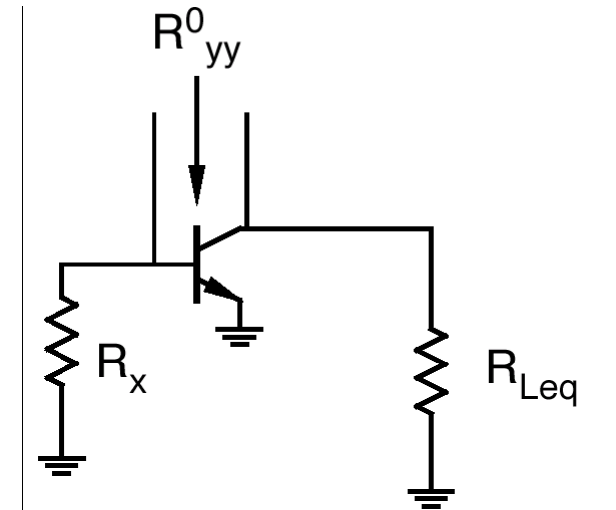
# MOTC: port impedances between collector and base



If we decide explicitly that  $R_x$  is to denote the parallel combination of any external circuit resistances and  $R_{be}$ , and that  $R_{Leq}$  similarly denotes the combined effect of external resistors and  $R_{ce}$ , then



$$R_{yy}^0 = R_x (1 + g_m R_{Leq}) + R_{Leq}$$


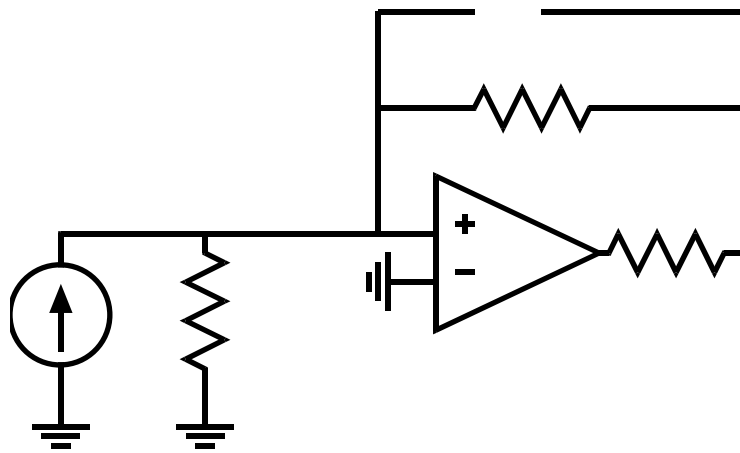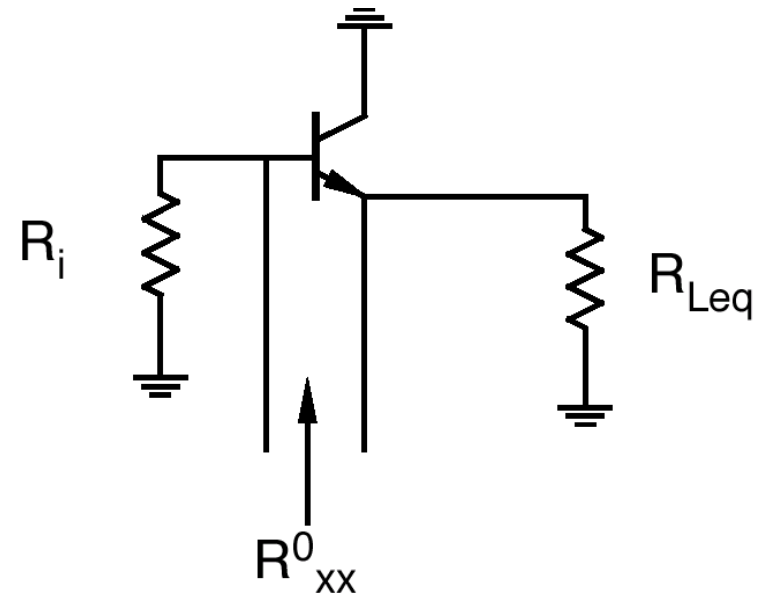
# MOTC: Port Impedances Between Emitter & Base


$$R_{xx}^0 = R_{\pi} \parallel \left( r_e \parallel R_{Leq} + R_i (1 - A_{vmb}) \right)$$

$$A_{vmb} = \left( R_{Leq} / (r_e + R_{Leq}) \right)$$



# MOTC: Multistage Example

*work on the board...*

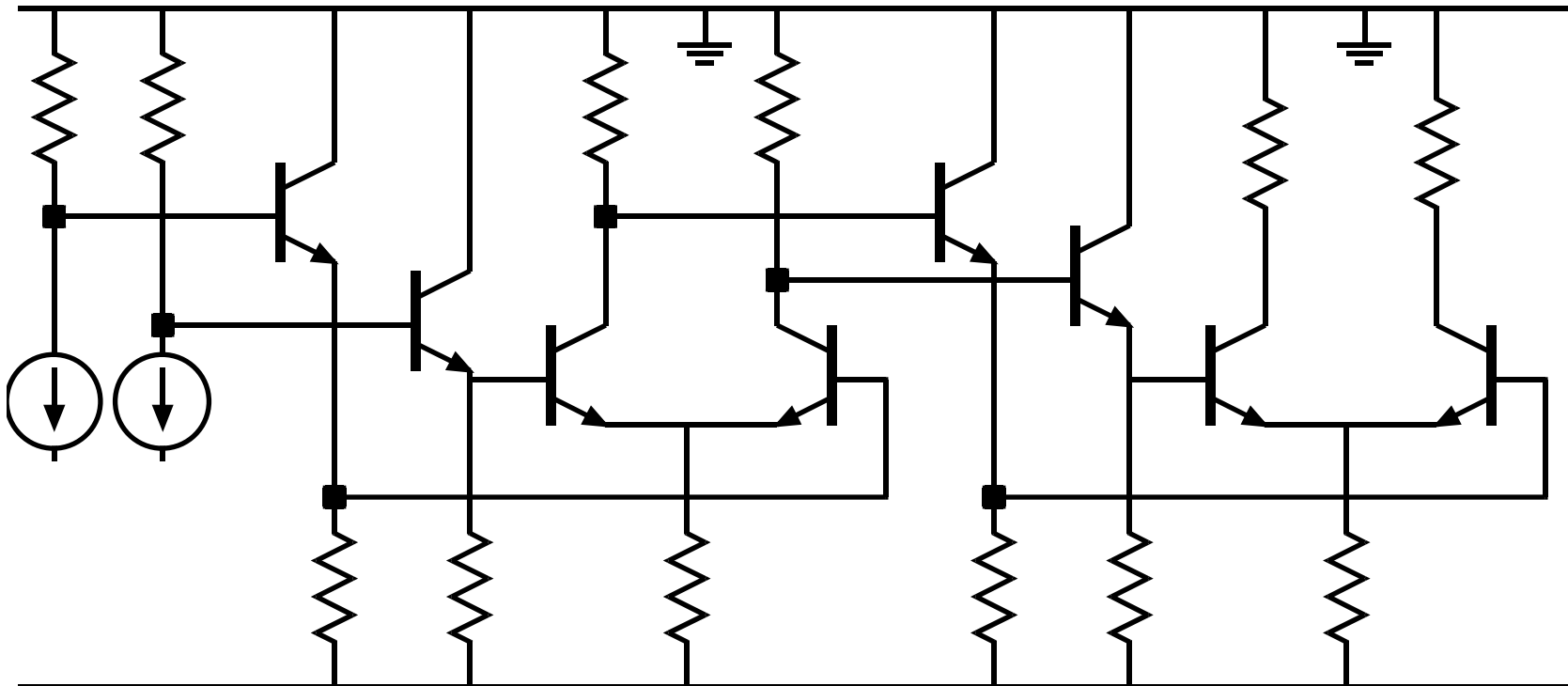

**End**