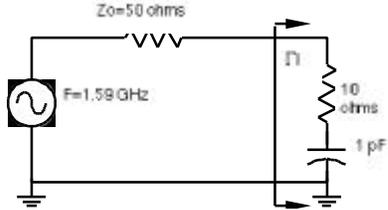



**ECE202A first problem set. Due October 18, 1999 (in class)**

**1) Practice with a Smith Chart:**


a) What are  $Z_l$ ,  $Y_l$ ,  $\Gamma_l$ ?



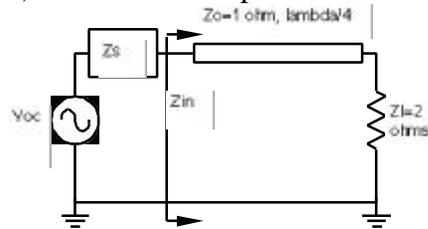
b) What source impedance will match  $Z_{in}$ ?



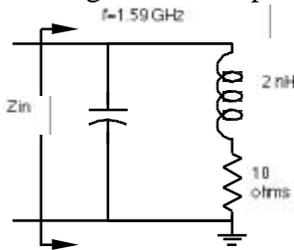c) matching: find the capacitance C required to make  $Z_{in}=50$  ohms.




**2) Lumped-Element Equivalents:**

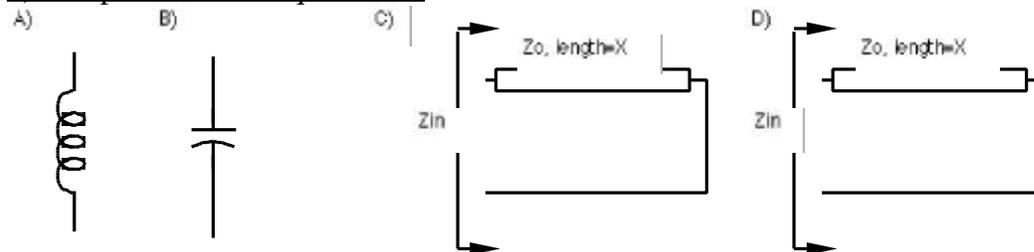


Using the smith chart, determine the reactances for the following elements over the frequency range  $f=0$  to  $f=2f_0$ , where  $L=Z_0\tau$ ,  $C=\tau/Z_0$ ,  $\tau=X/V_p$ , and  $f_0=1/\tau$  where  $V_p$  is the transmission line (phase) velocity, and  $\tau$  is the line electrical time delay. Plot the trajectories of each on the Smith Chart, and also draw two rectangular plots of reactance-(normalized to  $Z_0$ ) vs.-frequency (normalized to  $f_0$ ), one with A) and C), the other with B) and D). Over what range of frequencies does which transmission line reactance approximate which lumped element reactance? This should give a very clear picture
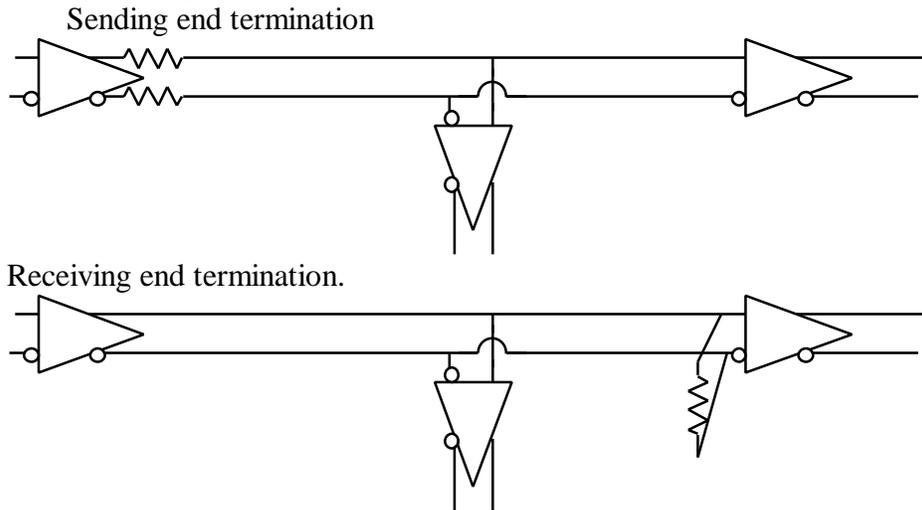
### 3) Lattice Diagrams and Bus Structures



The circuit diagrams above represent logic gates interconnected by a  $200\ \Omega$  balanced transmission line, typical of ECL. The line is one meter long, with a third gate connected at the middle. The line velocity is  $2/3\ c$ . The gates have infinite input impedance and zero output impedance. In the sending-end termination case, the sending end is driven from a total source impedance of  $150\ \Omega$ , while in the receiving end case the receiving end is terminated in  $150\ \Omega$ . The output voltage of the driving gate is a  $300\ \text{mV}$  step-function; use lattice diagrams for the 2 cases to find the input voltages to the two receiving gates; which gates function correctly?
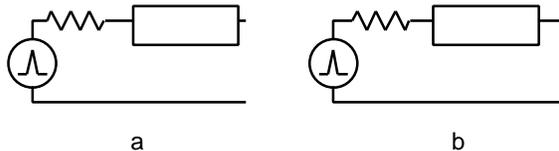
### 4) More on lattice diagrams and pulse responses:



In parts a and b the lines are driven by unit voltage impulses. In case a the line is  $50\ \Omega$  and the generator impedance  $5000\ \Omega$ , while in case b the line is  $50\ \Omega$  and the generator impedance  $0.5\ \Omega$ . In both cases the lines are  $1\ \text{ps}$  long.

First) Use Lattice diagrams to find the input voltage to the lines

Second) Using either pi- or T-equivalent lumped-element approximations to the circuits, again find the input voltage

Third) explain clearly what you have found.

You have worked through 2 of 4 possible cases-what would the other 2 cases be?