

UNIVERSITY OF CALIFORNIA, SANTA BARBARA Dept. of Electrical and Computer Engineering

ECE124A VLSI Principles

Homework #1 Review of Digital Design

Due Date: 10/05/2011 Friday by 5:00pm

Problem 1 Binary and 2-Complement Number

- (A) Convert $(21)_{10}$ and $(26)_{10}$ into Binary
- (B) Convert $(-21)_{10}$ and $(-26)_{10}$ into 2-complement number. Suppose each number has 8 digits and the highest digit is sign digit.
- (C) Calculate $26+(-21)$ and $21+(-26)$ using 2-complement numbers. Show your process. And explain the reason why we use 2-complement number in digital systems.

Problem2 Boolean algebra and Simplification

- (A) Use algebraic manipulation to simplification $F = \overline{AB + C} + \overline{AC} + B$
- (B) Use algebraic manipulation to convert the following equation to sum-of-product and product-of-sum forms: $X(\overline{Y + Z}) + Y\overline{Z}W + \overline{Y}\overline{Z} + Z + X\overline{Y}W$

Hint: don't forget consensus.

- (C) Make use of a Karnaugh Map to simplify:

$$F = \overline{A}B\overline{C}D + \overline{A}B\overline{C}\overline{D} + \overline{A}B\overline{C}D + \overline{A}B\overline{C}\overline{D} + \overline{A}BCD$$

$$d = \overline{A}BCD + \overline{A}B\overline{C}D + \overline{A}B\overline{C}\overline{D} + \overline{A}BCD$$

*Note that d corresponds to the don't cares. Choose the values of the don't cares to minimize the logic function. Be sure to show the values of the d's you choose.***Problem 3 Implement Boolean functions**

- (A) Implement the boolean expression below in a complementary CMOS gate

$$X = \overline{(A+B)(CD + EF)} + G$$


- (B) Realize the following 4-input switching function using an 8-1 multiplexer:

$$F(A, B, C, D) = ABC + AD + AC$$

Hint: Make a truth table. Use D to implement the result F. Connect A, B, C to MUX address lines.

Problem 4 Sequential Circuit

 
- (A) What is this? What are the Input/Output properties?
- (B) If input is changing from (0,0) to (1,1), what will happen?
- (C) How to use it to implement a D-latch with Enable signal?
- (D) How to use two of the latches in (C) to implement an edge-triggered D-Flip-Flop?
- (E) Explain setup time and hold time using a time diagram of D-Flip-Flop.



Problem 5 Finite State Machine

Consider the following state-transition graph which is to be implemented as a clocked, synchronous sequential circuit. If state d is the reset state and the states are encoded as State a = 00, State b = 01, State c = 11, and State d = 10:

- (A) Construct a state transition table for the machine in terms of input X and present-state (Y1 Y2) for output Z and next-state (Y1+ Y2+).
- (B) Use Karnaugh maps to obtain the reduced next-state and output equations for the machine. Show your K-maps.
- (C) Use the reduced set of equations to obtain a circuit diagram for an implementation of the machine. Use the minimum number of logic gates (AND, OR, NAND, NOR, XOR, XNOR, or inverters) and positive-edge-triggered JK flip flops.

 

Problem 6

- (A) Write half page of review for the article listed below. The article can be found in the “Lecture Notes and Reference” section of the [course webpage](#).
[G. E. Moore, “Cramming more components onto integrated circuits,” in Electronics, 38\(8\):114 -- 117, April 1965.](#)

Also answer the following questions based on the paper:

- (B) Why is integrated electronics better than “conventional” electronics?
- (C) According to G. Moore, integration will not change linear systems as radically as digital systems. Explain.
- (D) Search the Web for transistor counts of Intel and AMD’s more recent microprocessors. Make a graph of transistor count vs. year of introduction from their Processors in 1990 to the present on a semilog scale. How many months pass between doubling of transistor counts?