

**UNIVERSITY OF CALIFORNIA, SANTA BARBARA**  
**Department of Electrical and Computer Engineering**

**ECE225 High-Speed Digital IC Design**

**Homework #2**

*Due Date: Feb 23 by 5:00pm*


**1. Reading Assignment:** Chapter 4 and 9 of the book:

*Digital Integrated Circuits: A Design Perspective (2nd Edition), Jan M. Rabaey et al., Prentice Hall, 2003.*

**2. Draw the transistor level schematic of a 4-1 Multiplexer with;**


- a) transmission gate
- b) pass transistor logic
- c) pass transistor with restoring logic
- d) static CMOS
- e) Implement all above logic families in Hspice, use 65 nm technology. Compare power, delay and power-delay product of different multiplexers in room temperature.
- f) Change temperature to 100° C and repeat part (e).

 **3. A dynamic logic gate is shown below. During the pre-charge phase ( $\phi = 0$ ) output F is charged to VDD and it is given that  $A = B = C = D = 0V$ . During the evaluate phase ( $\phi = 1$ ), any of these inputs may or may not change.**



- a) What is the worst-case combination of input transitions in terms of charge sharing? That is, what input combination will corrupt F the most when the output is supposed to remain high?
- b) For the worst-case identified in part (a), what is the final voltage at node F? Use  $V_{DD} = 1.5V$ , NMOS model  $V_{TH0} = 0.5V$ ,  $\gamma = 0.4V$ ,  $2\phi_F = 0.6V$ , assume that  $C_{db} = C_{sb} = 1fF$  for all transistors and ignore gate capacitance.
- c) In addition to the charge sharing calculated in part (b), now assume that there is also a constant leakage current of  $2nA$  discharging node F to ground. What is that *minimum* clock speed that this gate can operate at if the next gate has  $V_{IH} = 1.0V$ ? Assume that clock  $\phi$  is high and low for equal periods of time.

 4. Consider the CMOS logic circuit in figure below, which is a simple Domino circuit. Node X is connected to a CMOS inverter so that the output of the inverter can be directly fed to the next stage of the domino circuit.



- Explain how the voltage level at node X, after it is pre-charged to 5 V, can be affected during “evaluate” by the charge sharing between node X and node Y. Express the final voltage at node X in terms of the initial voltage at node Y, when the charge sharing is completed following the full pre-charge operation. During pre-charge, the gate terminal of the transistor M2 is fixed at 0 V.
  - Determine the ratio between device transconductance parameters,  $k_p$  and  $k_n$ , of the inverter to prevent any logic error due to charge sharing between nodes X and Y under all circumstances. Assume that the magnitudes of threshold voltages in the inverter are equal to 1.0 V.
5. Multi-core designs are being adopted for future generations of high-performance ICs including microprocessors (see [www.intel.com](http://www.intel.com)). For multi-core architectures, which alleviate power dissipation problems, interconnects are going to play a key role in determining the design and performance of such ICs. Write a report (6 page, IEEE style) detailing the main philosophy behind multi-core designs and its various challenges. In particular, discuss the role of interconnects. Include a comprehensive list of all previous and related works in the literature. Discuss (and quantify, if possible) various implications of interconnect variations on multi-core architectures.