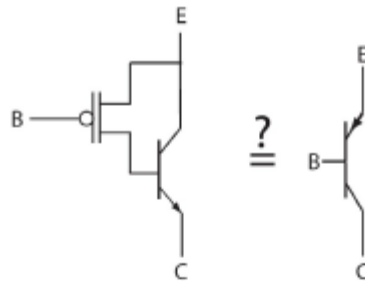


Problem Set 4

Additional Problems

1.



a) The definition of a transistor (Transfer Resistor) is a device that has transconductance, in other words, the device takes an input voltage, and gives an output current. To operate a PNP bipolar device in the forward active region, we need to forward bias the Emitter-base junction, and reverse bias the Base-collector junction. In terms of terminal voltages, $V_e - V_b > V_{bi}$, and $V_b > V_c$. Looking at our PMOS/NPN composite device, if we make V_{eb} greater than the threshold voltage of the PMOS device (V_{thp}), i.e., $V_e - V_b > V_{thp}$, assuming the initial drain voltage V_d is at zero Volt, then the device is in strong inversion, and a current will flow, charging up node V_d , as soon as V_d goes above V_{bi} of the NPN device, the NPN transistor turns on, giving rise to a current I_c . At this point, V_d is pinned at V_{bi} of the NPN device, because any additional current will now go to the emitter. At least operation wise, the composite device operates as an PNP bipolar transistor.

b) Assuming PMOS is in saturation

$$I_d = K_p (V_{eb} - V_{thp})^2 = I_{b_{NPN}}$$

$$I_{c_{NPN}} = \beta \cdot I_{b_{NPN}}$$

$$I_c = \beta \cdot K_p (V_{eb} - V_{thp})^2$$


c) The device will show linear¹ and saturation behaviors like that of a PMOS transistor

d) V_{beon} on the device is the threshold voltage of the PMOS device, v_{thp}

e) The device does not take any input current, so β is infinite

f) compared to a normal PMOS, the output current of the composite device is increased by factor of $(\beta+1)$.

2. (a)

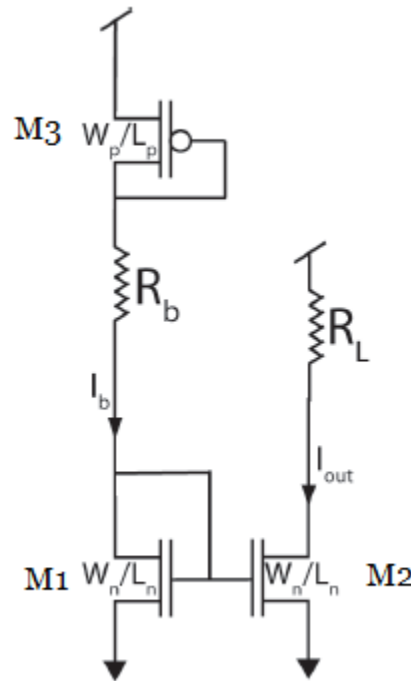

The drain and gate of M1 and M3 are connected. So you can think of the two transistors as nonlinear resistors. Then I_b is determined by the three resistors (M1, R_b , and M3). Now we have M1 and M2 current mirror, which means I_b of M1 is copied to I_{out} of M2. Depending on the size ratio of M1 and M2, I_{out} is proportional to I_b .

$$I_b = \frac{K_n}{2} \left(\frac{W}{L} \right)_{n1} (V_{gsn} - V_{Tn})^2$$

$$I_{out} = \frac{K_n}{2} \left(\frac{W}{L} \right)_{n2} (V_{gsn} - V_{Tn})^2$$

$$\Rightarrow I_{out} = \frac{\left(\frac{W}{L} \right)_{n2}}{\left(\frac{W}{L} \right)_{n1}} I_b$$

$$\text{If } \left(\frac{W}{L} \right)_{n1} = \left(\frac{W}{L} \right)_{n2}, I_{out} = I_b$$

(b)

$$I_{out} = 25 \mu A = I_b$$

$$\text{Assume, } \left(\frac{W}{L}\right)_n = 10, \left(\frac{W}{L}\right)_p = 20$$

$$V_{DD} = V_{gsn} + I_b R_b + V_{sgp}$$

$$\Rightarrow V_{DD} = V_{Tn} + \sqrt{\frac{2I_b}{\mu_n C_{ox} \left(\frac{W}{L}\right)_n}} + I_b R_b + |V_{Tp}| + \sqrt{\frac{2I_b}{\mu_p C_{ox} \left(\frac{W}{L}\right)_p}}$$

$$\Rightarrow 5 = 1.5 + 25 \times 10^{-6} R_b + 0.16 + 0.18$$

$$\Rightarrow 3.16 = 25 \times 10^{-6} R_b$$

$$\Rightarrow R_b = 126 \text{ k}\Omega$$

(c)

Since the circuit works as a current source, I_{out} should not depend on R_L

The circuit does not work for all values of R_L


$$V_{DD} - I_{out} R_L = V_{gsn} - V_{Tn}$$

$$\Rightarrow 5 - 25 \times 10^{-6} R_L = 0.16$$

$$\Rightarrow R_L = 193.6 \text{ k}\Omega$$

When $R_L > 193.6 \text{ k}\Omega$, M2 will operate in linear region and therefore, it becomes a linear resistor.

3.

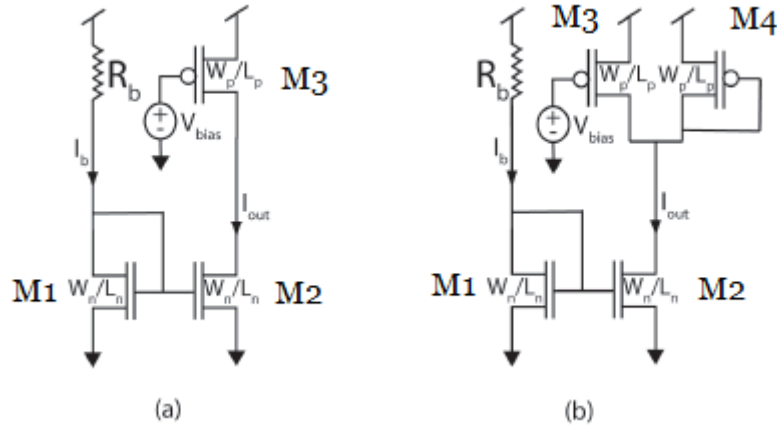

(a)

$$\left(\frac{W}{L}\right)\left(\frac{100\mu\text{A}}{V^2}\right)(V_{gs} - V_T)^2 = \frac{V_{DD} - V_{gs}}{R_b}$$

$$\Rightarrow \frac{W}{L} = \frac{V_{DD} - V_{gs}}{\left(\frac{100\mu\text{A}}{V^2}\right)(V_{gs} - V_T)^2 R_b} \geq 1$$

$$\Rightarrow V_{DD} - V_{gs} \geq 100R_b(V_{gs}^2 - 2V_{gs}V_T + V_T^2)$$

$$\Rightarrow 100R_bV_{gs}^2 - (200R_bV_T - 1)V_{gs} + 100R_bV_T^2 - V_{DD} \leq 0$$

$$\Rightarrow V_{gs} \leq \frac{(200R_bV_T - 1) \pm \sqrt{400R_b(V_{DD} - V_T) + 1}}{200R_b}$$

So the maximum value of V_{gs} is

$$V_{gs} = \frac{(200R_bV_T - 1) + \sqrt{400R_b(V_{DD} - V_T) + 1}}{200R_b}$$

(b)

Assume, $\left(\frac{W}{L}\right)_n = 1$

$$I_b = \left(\frac{W}{L}\right)_n \left(\frac{100\mu A}{V^2}\right) (V_{gsn} - V_T)^2$$

$$\Rightarrow 100\mu A = 1 \left(\frac{100\mu A}{V^2}\right) (V_{gsn} - 0.75)^2$$

$$\Rightarrow V_{gsn} = 1.75V$$

$$R_b = \frac{V_{DD} - V_{gsn}}{I_b} = \frac{5 - 1.75}{100\mu A} = 32.5k\Omega$$

(c)

Assume, $V_{bias} = 2V$

$$R_3 = R_b$$

$$\Rightarrow \frac{1}{40 \times 10^{-6} A/V^2 \left(\frac{W}{L}\right)_p (V_{DD} - V_{bias} - |V_{Tp}|)} = 32.5 \times 10^3$$

$$\Rightarrow \left(\frac{W}{L}\right)_p = \frac{1}{40 \times 10^{-6} A/V^2 (5 - 2 - 0.75) \times 32.5 \times 10^3} = 0.34$$

(d)

R4 is diode connected device, the small-signal resistance of R4 is given by $1/gm4$.

$$R_4 = \frac{1}{\mu_p C_{ox} \left(\frac{W}{L}\right)_p (V_{DD} - V_{out} - |V_{Tp}|)}$$

R3 is working in linear region, but if V_{sd} is large, the square term in its current equation takes effect. Let's write its current equation in linear region first. Then find its output resistance by taking derivative over V_{out} .

$$I_3 = \mu_p C_{ox} \left(\frac{W}{L}\right)_p \left[(V_{DD} - V_{bias} - |V_{Tp}|)(V_{DD} - V_{out}) - \frac{1}{2}(V_{DD} - V_{out})^2 \right]$$


$$R_3 = \left(\frac{\partial I_3}{\partial (V_{DD} - V_{out})} \right)^{-1} = \frac{1}{\mu_p C_{ox} \left(\frac{W}{L} \right)_p (V_{out} - V_{bias} - |V_{Tp}|)}$$

$$R_3 \parallel R_4 = \frac{1}{\mu_p C_{ox} \left(\frac{W}{L} \right)_p (V_{DD} - V_{out} - |V_{Tp}| + V_{out} - V_{bias} - |V_{Tp}|)}$$

$$= \frac{1}{\mu_p C_{ox} \left(\frac{W}{L} \right)_p (V_{DD} - V_{bias} - 2|V_{Tp}|)}$$

Hence, adding another diode connected PMOS transistor in parallel with M3 eliminate nonlinearity or in other words remove the dependence on V_{out} .

4.

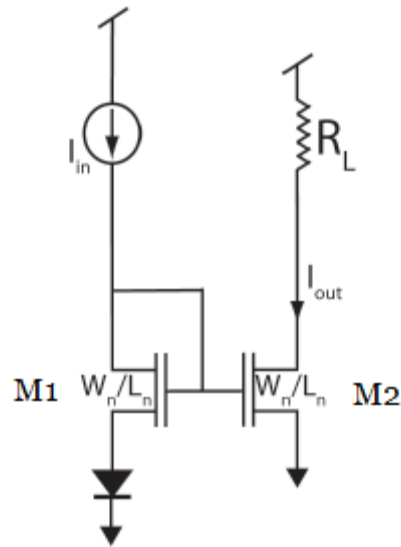

(a)

$$V_{gs2} = V_{gs1} + V_{on}$$

$$V_{gs1} = V_{Tn} + \sqrt{\frac{2I_{in}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_n}}$$

$$V_{gs2} = V_{Tn} + \sqrt{\frac{2I_{out}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_n}}$$

$$V_{gs2} = V_{gs1} + V_{on}$$

$$\Rightarrow \sqrt{\frac{2I_{out}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_n}} = \sqrt{\frac{2I_{in}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_n}} + V_{on}$$

(b)

If the voltage across the diode is V_1


$$I_{in} = I_s \left(e^{\frac{qV_1}{kT}} - 1 \right)$$

$$\Rightarrow V_1 = \frac{kT}{q} \ln \left(\frac{I_{in}}{I_s} + 1 \right)$$

$$V_{gs2} = V_{gs1} + V_1$$

$$\Rightarrow \sqrt{\frac{2I_{out}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_n}} = \sqrt{\frac{2I_{in}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_n}} + \frac{kT}{q} \ln \left(\frac{I_{in}}{I_s} + 1 \right)$$

5.

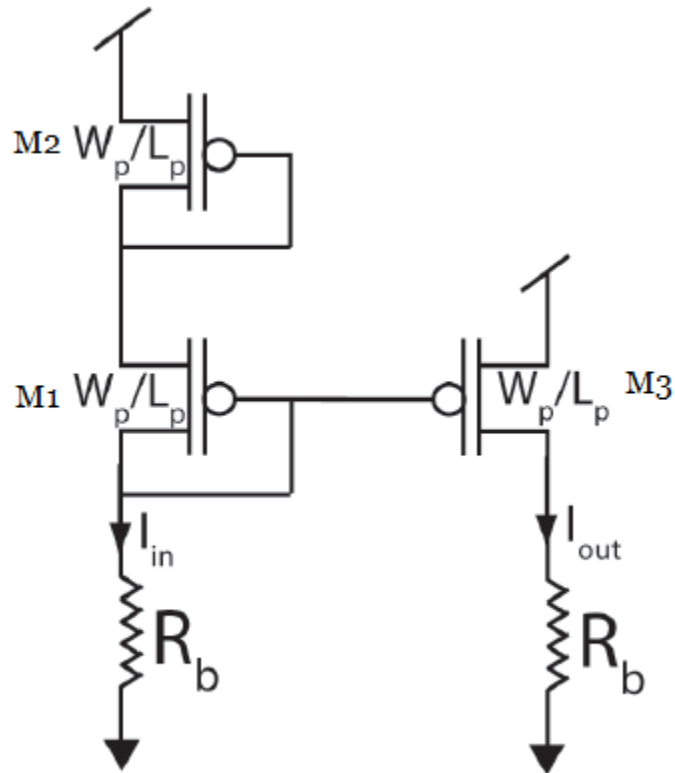

(a)

$$V_{sg1} + V_{sg2} = V_{sg3}$$

$$\Rightarrow |V_{Tp}| + \sqrt{\frac{2I_{in}}{\mu_p C_{ox} \left(\frac{W}{L}\right)_1}} + |V_{Tp}| + \sqrt{\frac{2I_{in}}{\mu_p C_{ox} \left(\frac{W}{L}\right)_2}} = |V_{Tp}| + \sqrt{\frac{2I_{out}}{\mu_p C_{ox} \left(\frac{W}{L}\right)_3}}$$

$$\Rightarrow \Rightarrow |V_{Tp}| + \sqrt{\frac{2I_{in}}{\mu_p C_{ox} \left(\frac{W}{L}\right)_1}} + \sqrt{\frac{2I_{in}}{\mu_p C_{ox} \left(\frac{W}{L}\right)_2}} = \sqrt{\frac{2I_{out}}{\mu_p C_{ox} \left(\frac{W}{L}\right)_3}}$$


(b) Assume, $\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = 20$

$$|V_{Tp}| + \sqrt{\frac{2I_{in}}{\mu_p C_{ox} \left(\frac{W}{L}\right)_1}} + |V_{Tp}| + \sqrt{\frac{2I_{in}}{\mu_p C_{ox} \left(\frac{W}{L}\right)_2}} + I_{in} R_b = V_{DD}$$

$$\Rightarrow 1.5 + 0.176 + 0.176 + 25 \times 10^{-6} R_b = 5$$

$$\Rightarrow R_b = 125.6 \text{ k}\Omega$$

6.

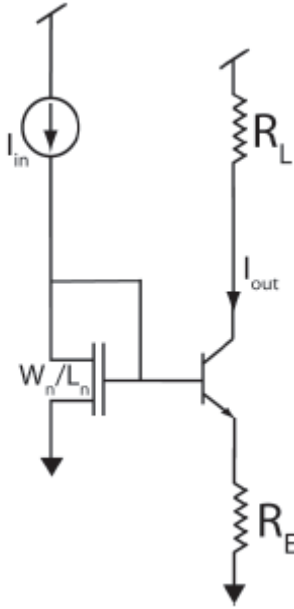


$$V_{gsn} = V_{on} + I_{out} R_E$$

$$\Rightarrow V_{Tn} + \sqrt{\frac{2I_{in}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_n}} = V_{on} + I_{out} R_E$$

$$\Rightarrow R_E = \frac{V_{Tn} + \sqrt{\frac{2I_{out}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_n}} - V_{on}}{I_{out}} \quad [\text{since, } I_{in} = I_{out}]$$

#7

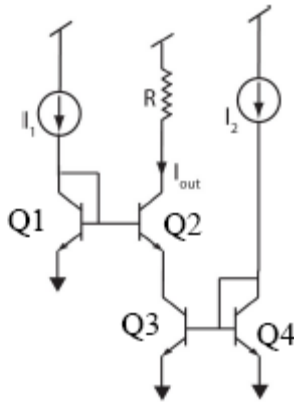

$$V_{be1} = \frac{kT}{q} \ln\left(\frac{I_1}{I_s}\right)$$

$$I_{out} = I_s \exp\left(q \frac{(V_{be1} - V_x)}{kT}\right)$$

$$I_{out} = I_s \exp\left(\frac{qV_{be1}}{kT}\right) \exp(-qV_x/kT) = I_1 \exp(-qV_x/kT)$$

$$V_x = \frac{-kT}{q} \ln\left(\frac{I_{out}}{I_1}\right)$$

$$I_3 = I_{out} = I_s \exp\left(\frac{qV_{be1}}{kT}\right) \left(1 - \exp\left(\frac{-qV_x}{kT}\right)\right) = I_2 \left(1 - \exp\left(\frac{-qV_x}{kT}\right)\right)$$

$$I_{out} = I_2 - I_2 \exp\left(\frac{-qV_x}{kT}\right)$$

plugging in V_x to the preceding equation, we have

$$I_{out} = I_2 - I_2 \exp\left(\ln\left(\frac{I_{out}}{I_1}\right)\right)$$

$$I_{out} = I_2 - I_2 \frac{I_{out}}{I_1}$$

$$I_{out} = \frac{I_1 I_2}{I_1 + I_2}$$