

ECE 137A Winter 2009

Homework 4 Solutions

4.33

(a) Since $V_{DS} = V_{GS}$ and $V_{TN} > 0$ for both transistors, both devices are saturated.

$$\text{Therefore } I_{D1} = \frac{K'_n W}{2 L} (V_{GS1} - V_{TN})^2 \quad \text{and} \quad I_{D2} = \frac{K'_n W}{2 L} (V_{GS2} - V_{TN})^2.$$

From the circuit, however, I_{D2} must equal I_{D1} since $I_G = 0$ for the MOSFET:

$$I = I_{D1} = I_{D2} \quad \text{or} \quad \frac{K'_n W}{2 L} (V_{GS1} - V_{TN})^2 = \frac{K'_n W}{2 L} (V_{GS2} - V_{TN})^2$$

which requires $V_{GS1} = V_{GS2}$. Using KVL:

$$V_{DD} = V_{DS1} + V_{DS2} = V_{GS1} + V_{GS2} = 2V_{GS2}$$

$$V_{GS1} = V_{GS2} = \frac{V_{DD}}{2} = 5V$$

$$I = \frac{K'_n W}{2 L} (V_{GS1} - V_{TN})^2 = \frac{100 \mu A}{2} \frac{10}{V^2} \frac{1}{1} (5 - 0.75)^2 V^2 = 9.03 \text{ mA}$$

(b) The current simply scales by a factor of two (see last equation above), and $I_D = 18.1 \text{ mA}$.

(c) For this case,

$$I_{D1} = \frac{K'_n W}{2 L} (V_{GS1} - V_{TN})^2 (1 + \lambda V_{DS1}) \quad \text{and} \quad I_{D2} = \frac{K'_n W}{2 L} (V_{GS2} - V_{TN})^2 (1 + \lambda V_{DS2}).$$

Since $V_{GS} = V_{DS}$ for both transistors

$$I_{D1} = \frac{K'_n W}{2 L} (V_{GS1} - V_{TN})^2 (1 + \lambda V_{GS1}) \quad \text{and} \quad I_{D2} = \frac{K'_n W}{2 L} (V_{GS2} - V_{TN})^2 (1 + \lambda V_{GS2})$$

and $I_{D1} = I_{D2} = I$

$$\frac{K'_n W}{2 L} (V_{GS1} - V_{TN})^2 (1 + \lambda V_{GS1}) = \frac{K'_n W}{2 L} (V_{GS2} - V_{TN})^2 (1 + \lambda V_{GS2})$$

which again requires $V_{GS1} = V_{GS2} = V_{DD}/2 = 5V$.

$$I = \frac{K'_n}{2} \frac{W}{L} (V_{GS1} - V_{TN})^2 (1 + \lambda V_{DS}) = \frac{100 \mu A}{2} \frac{10}{V^2} \frac{1}{1} (5 - 0.75)^2 V^2 (1 + (0.04)5) = 10.8 \text{ mA}$$

4.54

(a) For $V_{IN} = 0$, the NMOS device is on with $V_{GS} = 5$ and $V_{SB} = 0$, and the PMOS transistor is off with $V_{GS} = 0$, $V_O = 0$, and $V_{SB} = 0$.

$$R_{on} = \frac{1}{(100 \times 10^{-6})(10)(5 - 0.75)} = 235 \Omega$$

(b) For $V_{IN} = 5V$, the NMOS device is off with $V_{GS} = 0$, and the PMOS transistor is on with $V_{GS} = -5V$, $V_O = 5V$, and $V_{SB} = 0$.

$$R_{on} = \frac{1}{(40 \times 10^{-6})(25)(-5 + 0.75)} = 235 \Omega$$

4.103

(a) The transistor is saturated by connection.


$$V_{GS} = 12 - 10^5 I_D \quad \text{and} \quad I_D = \frac{100 \times 10^{-6}}{2} \left(\frac{10}{1} \right) \left(\frac{A}{V^2} \right) (V_{GS} - 0.75V)^2$$

$$50V_{GS}^2 - 74V_{GS} + 16.13 = 0 \Rightarrow V_{GS} = 1.214V, \quad -0.266V \Rightarrow V_{GS} = 1.214 \text{ V since } V_{GS} \text{ must}$$

$$\text{exceed the threshold voltage.} \quad | \quad I_D = \frac{100 \times 10^{-6}}{2} \left(\frac{10}{1} \right) \left(\frac{A}{V^2} \right) (1.214 - 0.75V)^2$$

$$I_D = 104 \mu A \quad | \quad \text{Checking: } I_D = \frac{12 - 1.21}{10^5} = 108 \mu A \quad | \quad \text{Q-Point: } (108 \mu A, 1.21 \text{ V})$$

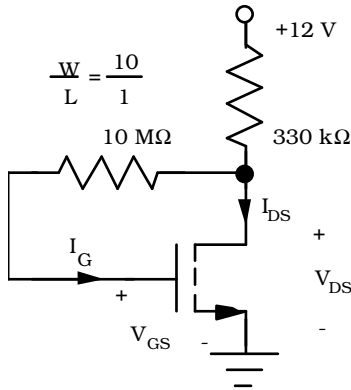(b) Using KVL, $V_{DS} = 10^7 I_G + V_{GS}$. But, since $I_G = 0$, $V_{GS} = V_{DS}$. Also $V_{TN} = 0.75 \text{ V} > 0$, so the transistor is saturated by connection.



$$\frac{W}{L} = \frac{10}{1}$$

$$I_D = \frac{K'_n W}{2 L} (V_{GS} - V_{TN})^2 = \left(\frac{100 \mu A}{2 V^2} \right) \left(\frac{10}{1} \right) (V_{GS} - 0.75)^2$$

$$V_{GS} = 12 - 330 k\Omega (I_D + I_G) - 10 M\Omega (I_G) \quad \text{but } I_G = 0$$

$$V_{GS} = 12 - 330 k\Omega (I_D)$$

$$V_{GS} = 12 - (3.30 \times 10^5) \left(\frac{1.00 \times 10^{-3} A}{2 V^2} \right) (V_{GS} - 0.75)^2$$

$$165 V_{GS}^2 - 246.5 V_{GS} + 80.81 = 0 \quad \text{yields } V_{GS} = 1.008 V, 0.486 V$$

V_{GS} must be 1.008 V since 0.486 V is below threshold.

$$I_D = \left(\frac{100 \mu A}{2 V^2} \right) \frac{10}{1} (1.008 - 0.75)^2 = 33.3 \mu A \quad \text{and } V_{DS} = V_{GS}$$

Q-Point: (33.3 μA , 1.01 V) Checking: $I_D = (12 - 1.01) V / 330 k\Omega = 33.3 \mu A$. ✓

4.121

For $V_{GS} = 5 V$ and $V_{DS} = 0.5 V$, the transistor will be in the triode region.

$$I_D = \frac{(5 - 0.5) V}{82 k\Omega} = 54.88 \mu A \quad | \quad 54.88 \times 10^{-6} = 100 \times 10^{-6} \left(\frac{W}{L} \right) \left(5 - 0.75 - \frac{0.5}{2} \right) 0.5 \quad | \quad \frac{W}{L} = \frac{0.274}{1} = \frac{1}{3.64}$$

4.122

For $V_{GS} = 3.3 V$ and $V_{DS} = 0.25 V$, the transistor will be in the triode region.

$$I_D = \frac{(3.3 - 0.25) V}{180 k\Omega} = 16.94 \mu A \quad | \quad 16.94 \times 10^{-6} = 100 \times 10^{-6} \left(\frac{W}{L} \right) \left(3.3 - 0.75 - \frac{0.25}{2} \right) 0.25 \quad | \quad \frac{W}{L} = \frac{0.280}{1} = \frac{1}{3.57}$$

4.123

(a) The transistor is saturated by connection. For this circuit,

$$V_{GS} = V_{DD} + I_D R = -15 + 75000 I_D$$

$$I_D = \frac{4 \times 10^{-5}}{2} \left(\frac{1}{1} \right) (-15 + 75000 I_D + 0.75)^2 \Rightarrow 153 \mu A$$

$$V_{GS} = -15 + 75000 I_D = -3.525 V$$

$$V_{DS} = V_{GS} = -3.525 V \quad | \quad \text{Q-point: } (153 \mu A, -3.53 V)$$

(b) Here the transistor has $V_{GS} = -15 \text{ V}$, a large value, so the transistor is most likely operating in the triode region.

$$I_D = \frac{V_{DS} - (-15)}{75000} = 4 \times 10^{-5} \left(-15 - (-0.75) - \frac{V_{DS}}{2} \right) V_{DS} \Rightarrow V_{DS} = -0.347 \text{ V and } I_D = 195 \mu\text{A}.$$

Checking: $I_D = \frac{15 - 0.347}{785 \text{ k}\Omega} \text{ V} = 195 \mu\text{A}$ Q - point : $(195 \mu\text{A}, -0.347 \text{ V})$

Checking the region of operation: $V_{DS} = -0.347 \text{ V} > V_{GS} - V_{TP} = -15 + 0.75 = -14.25 \text{ V}$

Triode region is correct

4.142

Note: The answers are very sensitive to round-off error and are best solved iteratively using MATLAB, a spreadsheet, HP solver, etc. Hand calculations using the quadratic equation will generally yield poor results.

Saturated by connection with $V_{TP} = -1$

$$I_D = \frac{4 \times 10^{-5}}{2} \left(\frac{10}{1} \right) \left[3.3 \times 10^5 I_D - 12 - (-1) \right]^2 \rightarrow 121 - 7.265 \times 10^6 I_D + 1.089 \times 10^{11} I_D^2 = 0$$

$$I_D = 34.6 \mu\text{A}, 32.1 \mu\text{A} \mid V_{DS} = 3.3 \times 10^5 I_D - 12 = -0.582 \text{ V}, -1.407 \text{ V} \mid \text{Q - point : } (32.1 \mu\text{A}, -1.41 \text{ V})$$

since the transistor would not be conducting for $V_{GS} = -0.582 \text{ V}$.


5.9

Using $v_{BC} = 0$ in Eq. 5.13 and recognizing that $i = i_C + i_B = i_E$:

$$i = i_E = I_S \left(1 + \frac{1}{\beta_F} \right) \left[\exp\left(\frac{v_{BE}}{V_T}\right) - 1 \right], \text{ and the reverse saturation current}$$

$$\text{of the diode connected transistor is } I'_S = I_S \left(1 + \frac{1}{\beta_F} \right) = (2 \text{ fA}) \left(1 + \frac{1}{100} \right) = 2.02 \text{ fA}$$

5.17

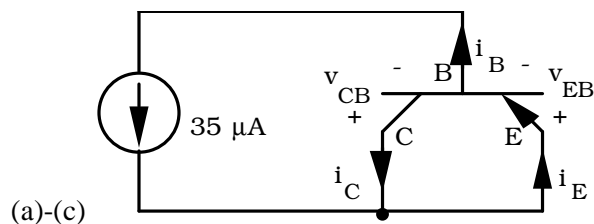

(b) pnp transistor(d)

$$v_{EB} = v_{CB} \quad i_C = -\frac{I_S}{\beta_R} \left[\exp\left(\frac{v_{EB}}{V_T}\right) - 1 \right] \quad i_E = +\frac{I_S}{\beta_F} \left[\exp\left(\frac{v_{EB}}{V_T}\right) - 1 \right] \quad i_B = +I_S \left(\frac{1}{\beta_F} + \frac{1}{\beta_R} \right) \left[\exp\left(\frac{v_{EB}}{V_T}\right) - 1 \right]$$

$$\frac{I_E}{I_B} = \frac{\frac{1}{\beta_F}}{\frac{1}{\beta_F} + \frac{1}{\beta_R}} = \frac{\beta_R}{\beta_F + \beta_R} = \frac{4}{79} = 0.0506 \quad \frac{I_E}{I_B} = -\frac{\beta_R}{\beta_F} = -\frac{4}{75} = -0.0533$$

$$I_B = 35 \mu A \quad I_E = \frac{4}{79} I_B = 1.77 \mu A \quad I_C = -\frac{75}{4} I_E = -33.2 \mu A$$

$$V_{EB} = V_T \ln\left(1 - \frac{\beta_R I_C}{I_S}\right) \quad V_{CB} = V_{EB} = 0.025V \ln\left(1 - \frac{4(-33.2 \times 10^{-6} A)}{2 \times 10^{-15} A}\right) = 0.623 V$$

5.37

(a) I_B is forced to be negative by the current source, and the largest negative base current according to the Transport model is

$$I_B = -I_S \left(\frac{1}{\beta_F} + \frac{1}{\beta_R} \right) = -10^{-15} A \left(\frac{1}{50} + \frac{1}{0.5} \right) = -2.02 fA$$

(b) I_B is forced to be -1 mA by the current source. One or both of the junctions must enter the breakdown region in order to supply this current. For the case of a normal BJT, the base-emitter junction will break down and supply the current since it has the lower reverse breakdown voltage.

5.65

Both transistors are in the forward - active region. For simplicity, assume $V_A = \infty$.

$I = I_{C1} + I_{B1} + I_{B2}$ | Since the transistors are identical and have the same V_{BE} ,

$$I_{C2} = I_{C1} \text{ and } I_{B1} = I_{B2} \quad | \quad I = I_{C1} + 2I_{B1} = (\beta_F + 2)I_{B1} \quad | \quad I_{C2} = \beta_F I_{B2} = \beta_F I_{B1}$$

$$I_{C2} = \frac{\beta_F}{\beta_F + 2} I = \frac{25}{25 + 2} 25 \mu A \quad | \quad I_{C2} = 23.2 \mu A \quad | \quad \text{See the Current Mirror in Chapter 15.}$$

5.96

$$V_{CE} = 1.5 - (I_C + I_B)R_C \rightarrow R_C = \frac{1.5 - 0.9}{20\mu A + \frac{20\mu A}{50}} = 29.4k\Omega \rightarrow 30k\Omega$$

$$R_B = \frac{V_{CE} - V_{BE}}{I_B} = \frac{0.9 - 0.65}{\frac{20\mu A}{50}} = 625k\Omega \rightarrow 620k\Omega$$

$$\text{For } R_C = 30k\Omega: V_{CE} = 1.5 - 30k\Omega(I_C + I_B)R_C = 1.5 - 30k\Omega(126)I_B \mid I_B = \frac{V_{CE} - 0.65}{620k\Omega}$$

$$V_{CE} = 1.5 - 30k\Omega(126)\frac{V_{CE} - 0.65}{620k\Omega} \rightarrow V_{CE} = 0.770V$$

$$I_C = 125I_B = 125\frac{0.770 - 0.65}{620k\Omega} = 24.2\mu A \mid Q\text{-point} : (24.2\mu A, 0.770V)$$

5.97

$$12 = R_C(I_C + I_B) + V_Z + V_{BE} = 500(I_E) + 7.7 \mid I_E = \frac{12 - 7.7}{500} = 8.60mA$$

$$I_B = \frac{I_E}{\beta_F + 1} = \frac{8.60mA}{101} = 85.2\mu A \mid I_C = \beta_F I_B = 8.52mA \mid V_{CE} = 7.70V$$

$$Q\text{-point} = (8.52mA, 7.70V)$$

5.98

$$V_{EQ} = 6 + 100\frac{15 - 6}{7800 + 100} = 6.114V \mid R_{EQ} = 100\Omega \parallel 7800\Omega = 98.73\Omega$$

$$I_B = \frac{20mA}{51} + \frac{V_O}{51(4700\Omega)} = \frac{20mA}{51} + \frac{6.14 - 98.7I_B - V_{BE}}{51(4700\Omega)} \rightarrow I_C = 50I_B = 50\frac{101.1 - V_{BE}}{2.398 \times 10^5}$$

$$V_{BE} = 0.025 \ln \frac{I_C}{10^{-16}}$$

Using MATLAB: fzero('IC107',.02) ---> ans =0.0207

function f=IC107(ic)

vbe=0.025*log(ic/1e-16);

f=ic-50*(101.1-vbe)/2.398e5;

$$V_O = 6.14 - 98.7\frac{20.7mA}{51} - .025 \ln \frac{20.7mA}{10^{-16}} = 5.276V$$

5.100

$$v_o = 7 - 100i_B - v_{BE} = 7 - 100i_B - V_T \ln \frac{i_C}{I_S} = 7 - 100i_B - V_T \ln \frac{\alpha_F i_L}{I_S}$$

$$v_o = 7 - 100i_B - V_T \ln i_L - V_T \ln \frac{\alpha_F}{I_S}$$

$$R_o = -\frac{dv_o}{di_L} = -\left(-100\Omega \frac{di_B}{di_L} - \frac{V_T}{i_L}\right) = \frac{100\Omega}{51} + \frac{0.025V}{0.02A} = 3.21\Omega$$

5.101

Since the voltage across the op - amp input must be zero, $v_o = V_Z = 10 \text{ V}$.

Since the input current to the op amp is zero, $I_E = \frac{V_o}{100} = 100 \text{ mA}$

$$I_{+15} = I_Z + I_C = I_Z + \alpha_F I_E = \frac{15V - 10V}{47k\Omega} + \frac{60}{61} 100mA = 98.5 \text{ mA}$$

11.42

(a) $A_v(s) = -\frac{Z_2(s)}{Z_1(s)}$ $Z_2 = \frac{1}{sC}$ $Z_1(s) = R$ $A_v(s) = -\frac{1}{sRC}$, an inverting integrator.

(b) $\frac{V_s - V_+}{R} + \frac{V_o - V_+}{KR} = sCV_+$ and $V_+ = V_- = V_o \frac{R_1}{R_1 + KR_1} = \frac{V_o}{1+K}$


Combining these expressions yields: $A_v(s) = \frac{V_o}{V_s} = +\frac{1+K}{sRC}$, a noninverting integrator.


11.79

For $C_1 = C = C_2$: $\omega_o = \frac{1}{C\sqrt{R_1R_2}}$ | $Q = \frac{1}{2}\sqrt{\frac{R_2}{R_1}}$ | $\omega_o = \frac{1}{2R_1CQ}$

$$S_{\omega_o}^{\omega_o} = \frac{Q}{\omega_o} \frac{\partial \omega_o}{\partial Q} = \frac{Q}{\omega_o} \left(-\frac{1}{2R_1CQ^2}\right) = \frac{Q}{\omega_o} \left(-\frac{\omega_o}{Q}\right) = -1 \quad | \quad S_Q^{\omega_o} = -1$$

11.91

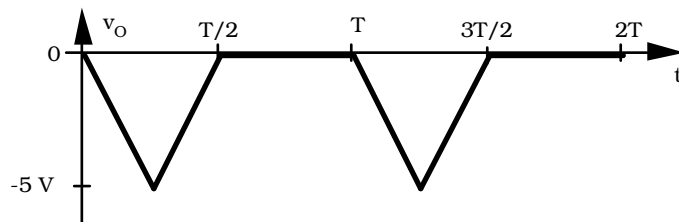

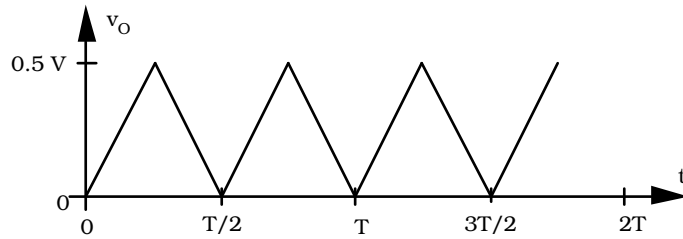11.94**11.98**

$$\frac{V_1}{10k\Omega} = I_s \exp \frac{-V_{o1}}{V_T} \quad | \quad V_{o1} = -V_T \ln \frac{V_1}{10^4 I_s} \quad | \quad V_{o2} = -V_T \ln \frac{V_2}{10^4 I_s}$$

$$V_{o3} = -(V_{o1} + V_{o2}) = V_T \left(\ln \frac{V_1}{10^4 I_s} + \ln \frac{V_2}{10^4 I_s} \right) = V_T \ln \frac{V_1 V_2}{10^8 I_s^2}$$

$$V_o = -10^4 I_D = -10^4 I_s \exp \frac{V_D}{V_T} = -10^4 I_s \exp \left(\ln \frac{V_1 V_2}{10^8 I_s^2} \right) = -\frac{V_1 V_2}{10^4 I_s}$$

The End