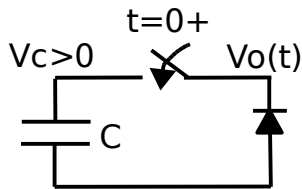


ECE 137A
 Quiz #2 Solution
 Luis Chen



$N_a = 10^{17}$
 $N_d = 10^{15}$
 Lossless switch
 $V_o(t) = 0$ for $t < 0$

1. Calculate total energy before switch closes
2. Calculate total energy after switch closes
3. Is $E_i = E_f$, if not, why not

Here, we assume ideal diode, i.e. No reverse current. Initially,

$$E_i = \frac{1}{2} C \cdot V_c^2$$

At $t > 0$, switch closes, charges flow from the capacitor to the diode. The diode is reverse biased, and has depletion capacitance C_{depl} .

To calculate, E_f , we need to find $V_o(t)$ in steady state (V_f).

$$Q_i = C V_c$$

$$Q_f = Q_i = (C + C_{Depl}) V_f$$

$$C V_c = (C + C_{Depl}) V_f$$

$$\text{so } V_f = V_c \frac{C}{C + C_{Depl}}$$

$$\text{where } C_{Depl} = \frac{C_{j0}}{\sqrt{1 - V_f / \phi_i}}, \quad C_{j0} = \sqrt{\frac{q \epsilon_s}{2 \phi_i} \frac{N_a \cdot N_d}{N_a + N_d}}$$

$$V_f = V_c \frac{C}{C + \frac{C_{j0}}{\sqrt{1 - V_f / \phi_i}}}$$

V_f is difficult to solve symbolically, Had we been given the values of C , V_c and Area, then we can solve it easily.

Let's take some numbers and see what we get,

Assume $C = 20\text{fF}$, $V_c = 1\text{V}$, and $A = 1\text{e-}6 \text{ cm}^2$,

$$\phi_i = \frac{kT}{q} \ln\left(\frac{NaNd}{n_i^2}\right) = 26\text{mV} \cdot \ln\left(\frac{10^{15} \cdot 10^{17}}{(1.5 \times 10^{10})^2}\right) = 0.7\text{V}$$

$$C_{j0} = \sqrt{\frac{1.6 \times 10^{-19} \cdot 11.7 \cdot 8.85 \times 10^{-14}}{2 \cdot 0.7\text{V}} \times \left(\frac{10^{15} \cdot 10^{17}}{10^{15} + 10^{17}}\right)} = \frac{10.8\text{nF}}{\text{cm}^2} \times 1 \times 10^{-6} \text{cm}^2 = 10.8 \text{fF}$$

$$V_f = V_c \frac{C}{C + C_{Depl}} = \frac{1\text{V} \times 20\text{fF}}{20\text{fF} + \frac{10.8\text{fF}}{\sqrt{1 - \frac{V_f}{0.7\text{V}}}}}$$

Solving for V_f ,

$$V_f = 0.498\text{V}$$

This is consistent, from the equation for C_{depl} , we know that $V_f < 0.7\text{V}$, and we assume that there is some final voltage, hence, $0 < V_f < 0.7\text{V}$

Now that we found V_f , we can calculate E_f

$$E_f = \frac{1}{2}(C + C_{Depl})V_f^2$$

Plugging in V_f

$$E_f = \frac{1}{2}(C + C_{Depl}) \cdot V_c^2 \frac{C^2}{(C + C_{Depl})^2} = E_i \frac{C}{C + C_{Depl}}$$

Clearly, E_f is less than E_i , where did the rest of the energy go?

The energy we calculated is the electric energy stored in the capacitors. Movement of charges (current) converts some of the initial energy into magnetic energy, and it is radiated into space in the form of magnetic field (Ampere's law).