

Midterm 1 Practice Questions

Razavi, **2.10, 2.18, 2.26, 3.21,4.16, 4.22, 5.22**

Review the following topics:

- Differential Amplifiers
- Cascode
- Current sources
- Feedback
- Opamp circuits
- MOS in Linear Region
- 2nd Order systems
- Dynamics