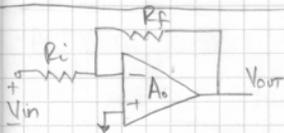


Notes 29 Mar 10

2 Midterms, 1 Final, 2-3 projects


137B → Dynamics
 Integrated Circuit Design
 Switched Capacitor Design (z-transforms)



$$A_v = -\frac{R_f}{R_i}$$

lets say

$$A_v = \frac{A_0}{1 + Ts}$$

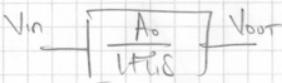


$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{A_0}{1 + Ts}$$

→ pole at $\frac{1}{p}$

Any transfer function can be written as

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{a_n s^n + a_{n-1} s^{n-1} + \dots + a_0}{b_m s^m + b_{m-1} s^{m-1} + \dots + b_0} = \frac{(s + \delta z_1)(s + \delta z_2)(\dots)}{(s + \delta p_1)(s + \delta p_2)(\dots)}$$

Bode plot $\left| \frac{V_{out}}{V_{in}} \right|$

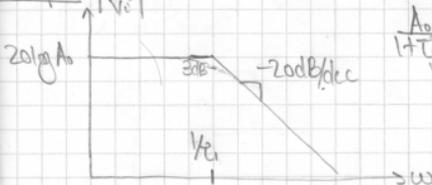

$$\frac{A_0}{1 + Ts}$$

$$20 \log A_0 - 20 \log(1 + Ts)$$

$$\frac{A_0}{1 + Ts} \approx \frac{A_0}{\sqrt{1 + \omega^2 \tau^2}} \approx \frac{A_0}{\omega \tau}$$

- plot of the Fourier transform
 not the Laplace transform

- Apply a signal to a stable system and allow transients to settle, then report what happens!

- look at sinusoidal steady state, not concerned with transients

- Must be stable! (LHP only)

when $\omega = \omega_c \rightarrow \sim \sqrt{2}$ (-3dB drop)



Phase

All systems I care about are BIBO stable

considered → bounded input bounded output


- Why is phase important?

new representation

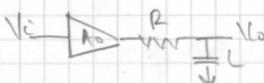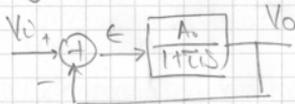

$$\tau = RC$$

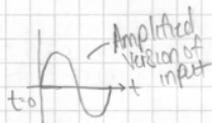
At DC, input & output has same phase with some time delay between input & output



$$\omega = \frac{1}{RC}$$

↳ both the resistor and the capacitor are the same impedance

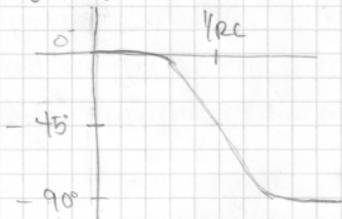- As system gets faster & faster, phase changes



- In response to the need to go faster it will reduce the output amplitude


- 45° implies a lag of 45° with respect to the input

↳ So, at 45°

- As frequency increases, it will asymptotically approach -90°

- Every pole adds 90°, signs on the summation change with delay

Example → 3 poles (270°)

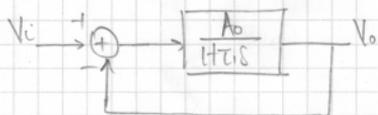


Why do systems have 270°

Single Stage $A_v = 200$ $\xrightarrow{\text{need multiple stages}}$ 30,000

Gain-Bandwidth relationship

$$\omega_0 \gg \omega_c \quad \omega_0 = A\omega_c$$

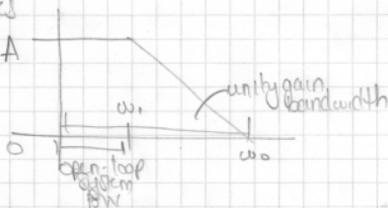- either have high gain, low bandwidth or low gain, high bandwidth



- Cascade many low gain, high bandwidth systems to get a system that is high gain, high bandwidth

$$A_v = \frac{\omega^2}{\delta^2 + 2\zeta\omega\delta + \omega_n^2} \quad \zeta = \text{Damping factor}$$

Resonance



- convert all potential energy to kinetic energy & vice versa at a particular point is resonant energy (perfect exchange of energy - resonance)

- Add resistor and energy is lost over time


- If you impose a voltage, cap has no say in dynamics

- Want to impose a current instead to get Bode plot


$$\begin{aligned} \frac{V_o(s)}{I_o(s)} &= \text{Impedance of system} = \frac{1}{\frac{1}{R} + \frac{1}{j\omega L} + j\omega C} \\ &= \frac{j\omega RL}{j\omega L + R - \omega^2 LC} = \frac{j\omega RL}{j\omega L + R - \omega^2 LC} \\ &= \frac{j\omega L}{j\omega(L/R) + 1 - \omega^2 LC} = \frac{j\omega C}{j\omega(1/R) + 1/C - \omega^2} \\ &= \frac{j\omega/C}{1/C - \omega^2 + j\omega(1/R)} \end{aligned}$$

Second Order System

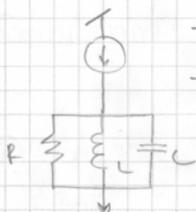
$$H(s) = \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2} = \frac{1}{\frac{s^2}{\omega_n^2} + \frac{2\zeta s}{\omega_n} + 1}$$



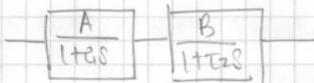- Generally, don't use inductors except in RF
- What behavior can you get without inductors?




cascade 2 first order systems

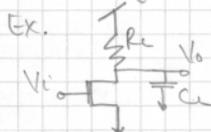

$$A_v = -g_m Z_{out} = -g_m \left(\frac{R_L}{1+sR_L C_L} \right)$$

DC response

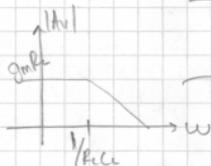
$$Z_{out} = R_L \parallel r_o \parallel C_L$$



Add second stage

$$Z_{out} = R_L \parallel r_o \parallel C_L$$

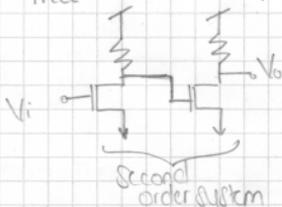$r_o \gg R_L$
 $\approx R_L \parallel C_L = \frac{R_L}{1+sR_L C_L}$
 $R_L \parallel (r_o \parallel C_L) \rightarrow \frac{R_L r_o}{R_L + r_o} \parallel C_L$



both poles are real and negative



$$\frac{K}{(s+\alpha)(s+\beta)}$$

$$\frac{AB}{(1+Ts)(1+Ts)}$$

$$\frac{AB/L^2}{(1/L_1 + s)(1/L_2 + s)}$$

$$h(t) = c e^{-\alpha t} + d e^{-\beta t}$$

system is stable
always decays

form of eqn is good for partial fractions & getting inverse Laplace transforms

cascading can only give you a second order system that is stable


Step response $u(t) \xrightarrow{\mathcal{L}} \frac{1}{s}$

$$H(s) = \frac{K}{(s+\alpha)(s+\beta)}$$

$$Y(s) = \frac{H(s)}{s} = \frac{K}{s(s+\alpha)(s+\beta)} \xrightarrow{\mathcal{L}^{-1}}$$


$$y(t) = 1 - (K_1 e^{-\alpha t} + K_2 e^{-\beta t})$$

Similar to an RC

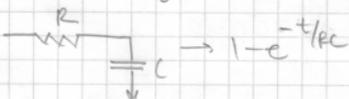


Difference in step response between first & second order system

In time:

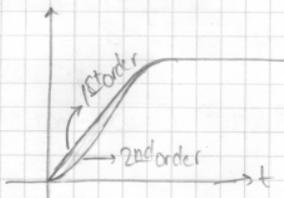

- 2nd order begins as a square function
- 1st order begins linear

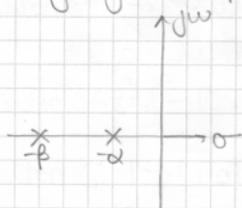
- Can you get a complex system from two real poles?



$$g_m(s) = sL \quad \left(g_m(s) = \frac{1}{sC} \right)$$

- make inverse to $\frac{1}{sC}$
- making C look like an L

Ideal opamp ex.:

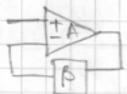

$$= \frac{A}{1+\beta A} \approx \frac{1}{\beta}$$

$$i = C \frac{dV}{dt} \quad V = L \frac{di}{dt}$$

- place integrator in feed back path to get an inductor


$$V_e = V_0 \sin \omega t \quad i_c = V_0 \omega C \cos \omega t$$

- Voltage | current out of phase by 90° (Voltage leads)



- Exactly opposite in an inductor

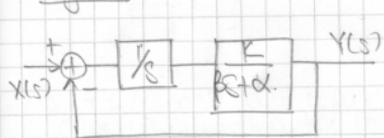- To make one look like the other, you must shift one by 180°
- Negative feedback accomplished this



$$H(s) = \frac{Y(s)}{X(s)} = \frac{\text{feed forward gain}}{1 + \text{loop gain}}$$

$$\text{feed forward gain} = \frac{1}{s} \left(\frac{K}{s+\alpha} \right)$$

$$\text{loop gain} = \frac{1}{s} \left(\frac{K}{s+\alpha} \right)$$

$$H(s) = \frac{\frac{1}{s} \frac{K}{s+\alpha}}{1 + \frac{1}{s} \left(\frac{K}{s+\alpha} \right)} = \frac{K}{s(s+\alpha) + K} = \frac{K}{s^2 + \alpha s + K}$$

want system to look like $\frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$

$$\omega_n^2 = K/\beta$$

$$2\zeta\omega_n = \alpha/\beta$$

damping ratio: actual

roots of denominator

$$\frac{-2\zeta\omega_n \pm \sqrt{4\zeta^2\omega_n^2 - 4(\omega_n^2)}}{2} = \frac{-2\zeta\omega_n \pm 2\omega_n \sqrt{\zeta^2 - 1}}{2}$$

$$= -\zeta\omega_n \pm \omega_n \sqrt{\zeta^2 - 1} = -\zeta\omega_n \pm j\omega_n \sqrt{1 - \zeta^2}$$


① when $\zeta^2 = 1 \rightarrow -\zeta\omega_n$ (double root \rightarrow critically damped case)

$$\alpha = 2\omega_n\beta$$

② when $0 < \zeta^2 < 1 \rightarrow$ (complex roots \rightarrow underdamped)

③ when $\zeta^2 > 1 \rightarrow$ (real poles \rightarrow overdamped)

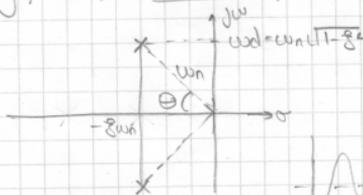
- integrator delays, the loop gain delay more; the closer to 180° delay, the more underdamped



$$\theta = \tan^{-1} \left[\frac{\omega_n \sqrt{1 - \zeta^2}}{\zeta \omega_n} \right]$$

$$= \tan^{-1} \left[\frac{\sqrt{1 - \zeta^2}}{\zeta} \right]$$

phase delay of one wave going back

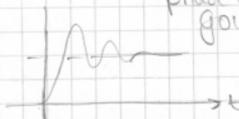



a step response will result in amplification of selected sine waves within the range of the band pass filter

Notes 04-05-2010

Order of poles given order of system

real poles $p_1, p_2 \rightarrow$ must be complex conjugates of each other if they are the only poles

$e^{st} \rightarrow$ eigenfunction only scaled by a linear function can only change amplitude and phase

$$s = -\sigma \pm j\omega_d \quad H(s) = \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2} = \frac{\omega_n^2}{(s + \sigma - j\omega_d)(s + \sigma + j\omega_d)}$$

$$= \frac{\omega_n^2}{(s + \sigma)^2 + \omega_d^2} = \frac{\omega_n^2}{s^2 + \sigma^2 + 2\sigma s + \omega_d^2} = \frac{\omega_n^2}{s^2 + 2\sigma s + \sigma^2 + \omega_d^2}$$

$$\sigma = \zeta\omega_n \quad \omega_n^2 = \sigma^2 + \omega_d^2 = (\zeta\omega_n)^2 + \omega_d^2$$

$$\omega_n^2(1 - \zeta^2) = \omega_d^2 \quad \omega_d = \omega_n \sqrt{1 - \zeta^2}$$

$$\mathcal{L}^{-1} \left\{ \frac{b}{(s+a)^2 + b^2} \right\} = e^{-at} \sin(bt) u(t)$$

$$H(s) = \frac{\omega_n^2}{(s + \sigma)^2 + \omega_n^2(1 - \zeta^2)} = \frac{\frac{\omega_n^2}{\sqrt{1 - \zeta^2}} \sqrt{1 - \zeta^2}}{(s + \sigma)^2 + \omega_n^2(1 - \zeta^2)}$$

$$= \frac{\omega_n}{\sqrt{1 - \zeta^2}} \left[\frac{\omega_n \sqrt{1 - \zeta^2}}{(s + \sigma)^2 + \omega_n^2(1 - \zeta^2)} \right] = \frac{\omega_n}{\sqrt{1 - \zeta^2}} \left[\frac{\omega_d}{(s + \sigma)^2 + \omega_d^2} \right]$$


Impulse response - homogeneous response (unforced)



$$\frac{dV(t)}{dt} = \frac{V_{in}(t) - V(t)}{R}$$

zero-input response $\rightarrow V_{in}(t) = 0$
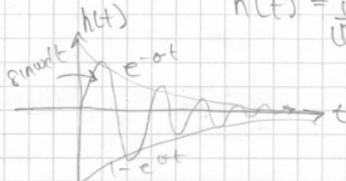
$$h(t) = \frac{\omega_n}{\sqrt{1 - \zeta^2}} e^{-\sigma t} \sin(\omega_d t) u(t)$$






Step Response (edge contains all frequencies)

- Integral of the impulse response
- Multiply $t(s)$ by $1/s$ which is the Laplace transform of the step

$$\mathcal{L}^{-1} \left\{ \frac{a^2 + b^2}{(s(s+a) + b^2)} \right\} \rightarrow 1 - e^{-at} \left(\cos bt + \frac{a}{b} \sin bt \right)$$
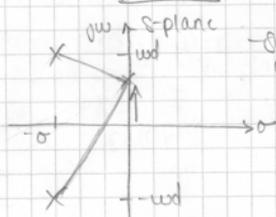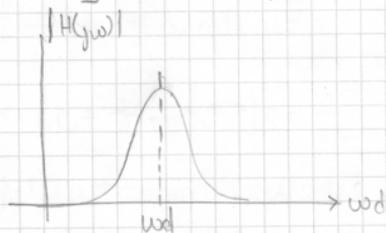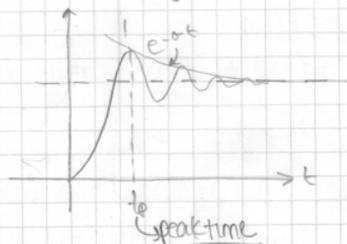
$$V_{out}(t) = 1 - e^{-\sigma t} \left[\cos \omega_d t + \frac{\sigma}{\omega_d} \sin \omega_d t \right] \leftarrow \text{Step response}$$



- sweeping frequencies means you are walking along the $j\omega$ -axis
- measuring resultant vector
- shorter vector dominates the response

Example: includes steady state + transient (most general form)



$$a = 1/RC$$


$$h(t) = e^{-t/RC} u(t)$$

$$h(t) = e^{-at} u(t)$$


$$H(s) = \frac{1}{s+a}$$

$$H(j\omega) = \frac{1}{j\omega + a}$$

$$\text{To find } |H(j\omega)| = \frac{1}{\sqrt{\omega^2 + a^2}}$$

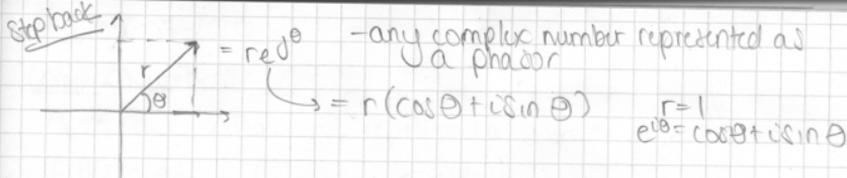

Back to RC response

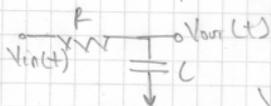


$$C \frac{dV_{out}(t)}{dt} + \frac{V_{out}(t)}{R} = \frac{V_{in}(t)}{R}$$

$$V_{out}(t) = A e^{st} \rightarrow \text{ble it's a real system}$$

Substitute: $C \frac{dA e^{st}}{dt} + \frac{A e^{st}}{R} = 0$

$$s(CA e^{st}) + \frac{A}{R} e^{st} = 0 \rightarrow sC + \frac{1}{R} = 0 \rightarrow \boxed{s = -\frac{1}{RC}}$$

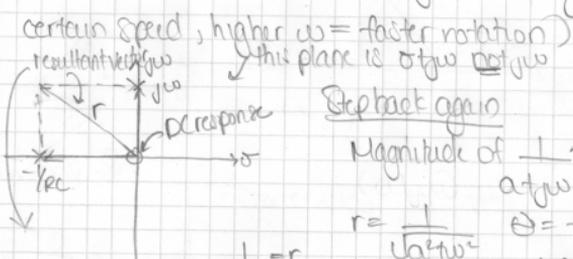- Assuming response is of the form $A e^{st}$, but to find sinusoidal $V_{out}(t) = A e^{j\omega t}$ instead. $\theta = j\omega$ (rotating in s-plane at a certain speed, higher $\omega =$ faster rotation)



Step back again

Magnitude of $\frac{1}{a + j\omega}$ $\rightarrow r e^{j\theta}$

$$r = \frac{1}{\sqrt{a^2 + \omega^2}} \quad \theta = \tan^{-1}\left(\frac{\omega}{a}\right)$$

$$\sqrt{a^2 + \omega^2} = \text{root of denominator}$$

$$= \frac{1}{\sqrt{a^2 + \omega^2}} e^{j \tan^{-1}\left(\frac{\omega}{a}\right)}$$

- as $\omega \uparrow$, response is attenuated, gets smaller

how did you get this?

$$= e^{\sigma t} e^{j\omega t} = e^{\sigma t} (\cos\omega t + j\sin\omega t)$$


$$H(s) = \frac{1}{s + a} \quad \text{if } s = -a \rightarrow H(s) \rightarrow \infty$$

in reality only manipulating $j\omega$, not σ

Notes 04-07-2010


Complex Numbers

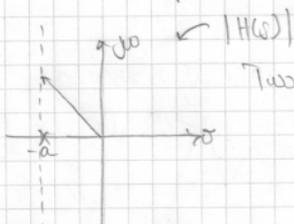$s = \sigma + j\omega$ also can be represented as a vector in the s -plane
 if $H(s) = \frac{1}{s+a}$




Two vectors $\rightarrow \frac{1}{(s+a)(s+a)}$

multiplication of two vectors

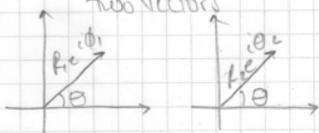


- In the s -plane is only the variable plane

Back to first order system:

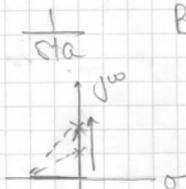


Bole: $|H(j\omega)|$

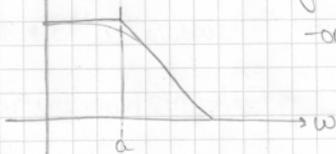

Scaling and rotation
 (magnitude) (angle)

- only varying ω
 (move along $j\omega$ -axis
 in s -plane)

Two poles? :

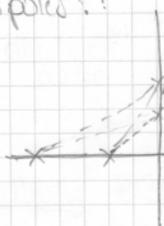

- Character of two dominants

Second-order system:

$$H(s) = \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

roots @ $\sigma \pm j\omega_d$


Step response: $H(s) = \frac{\omega_n}{s} \frac{1}{s(s^2 + 2\zeta\omega_n s + \omega_n^2)}$

$$\mathcal{L}^{-1} \left\{ \frac{a^2 + b^2}{s(s^2 + a^2 + b^2)} \right\} = 1 - e^{-at} \left(\cos bt + \frac{a}{b} \sin bt \right)$$

$$= \frac{\omega_n^2}{(\sigma^2 + \omega_d^2)^2 + \omega_d^2} = \frac{\omega_n^2 (\sigma^2 + \omega_d^2)}{(\sigma^2 + \omega_d^2) [(\sigma^2 + \omega_d^2)^2 + \omega_d^2]}$$

$$= \frac{\omega_n^2}{\omega_n^2 \zeta^2 + \omega_n^2 (1 - \zeta^2)} = \frac{(\sigma^2 + \omega_d^2)^2}{\delta ((\sigma^2 + \omega_d^2)^2 + \omega_d^2)}$$
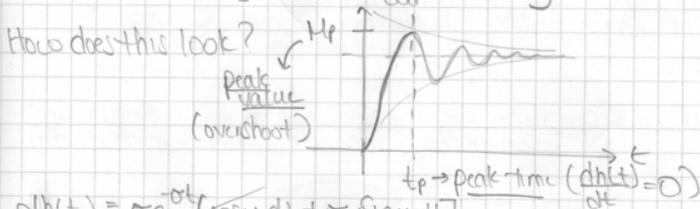
$$h(t) = 1 - e^{-\sigma t} \left[\cos \omega_d t + \frac{\sigma}{\omega_d} \sin \omega_d t \right]$$



$$\frac{dh(t)}{dt} = \cancel{\sigma e^{-\sigma t} [\cos \omega_d t + \frac{\sigma}{\omega_d} \sin \omega_d t]} - e^{-\sigma t} [-\omega_d \sin \omega_d t + \sigma \cos \omega_d t]$$

$$= \frac{\sigma e^{-\sigma t}}{\omega_d} \sin \omega_d t + e^{-\sigma t} \omega_d \sin \omega_d t$$

$$= e^{-\sigma t} \left[\frac{\sigma}{\omega_d} \sin \omega_d t + \omega_d \sin \omega_d t \right] = 0$$

- goes to zero when $\omega_d t \rightarrow \pi$

$$\boxed{\omega_d t = \pi} \quad t = t_p$$


$$\boxed{t_p = \frac{\pi}{\omega_d}}$$

M_p due to $e^{-\sigma t}$
at t_p

$$1 - e^{-\sigma t} \left[\cos \omega_d t + \frac{\sigma}{\omega_d} \sin \omega_d t \right]$$

$$M_p = 1 - e^{-\sigma t} \left[1 + \frac{\sigma}{\omega_d} \right] = M_p$$

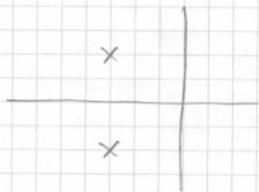Stability: BIBO stable (Bounded Input - Bounded Output)



- system with two complex poles in LHP
is BIBO stable

- LHP is always stable due to damping exponential

- if poles on jw-axis, then you have an oscillation

- Minimum number of poles for oscillation $\rightarrow \underline{3}$

Simplest oscillator



ideal - not real (all real systems must have a dissipative term)

but you can never get to jw axis




- must have some element to replace energy lost through dissipative term to sustain oscillation

- Once another element is added, the third pole is added which moves other two poles to jw axis

$$H(s) = \frac{1}{(s+a)(s+b)}$$

most of time we do this


$$\frac{K}{(s+a)(s+b)}$$

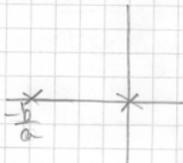

- amplifiers/circuits are typically not used in open loop

- In open loop, signal must be very small or bias will be upset
for BJT $\rightarrow \ll \frac{V_T}{\beta}$ for MOS $\rightarrow \ll V_{ov}$

Closed loop:

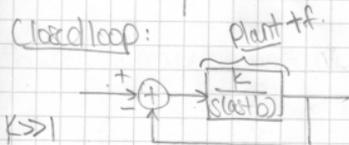


- feedback typically take out large disturbances

- How will the poles of the closed loop system change when open loop gain changes?


Root Locus Method: plot pole locations as K varies

- if loop is open, poles do not move

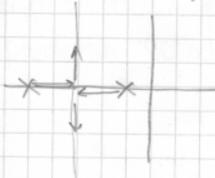- As loop is closed, one pole gets faster, one gets slower





Step Response:

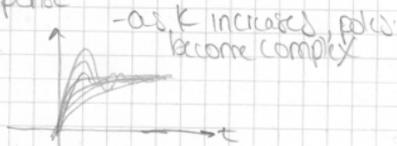

- as K increased, poles become complex

Bode plot method:

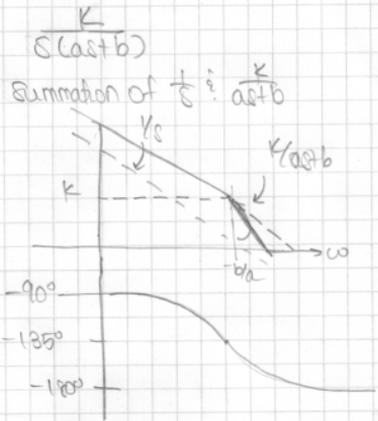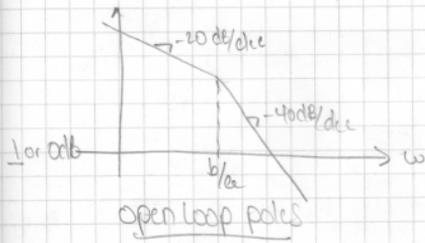


- Anything fed back over 90° will result in ringing
- If you lower K , get less gain at same point so you get a first-order crossover. (proportional)

- Called Reduced-gain compensation - loading system to make stable
- get steady-state error and smaller bandwidth




how close you get to V_{in} depends entirely on A

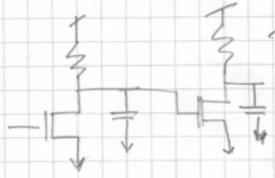How can we make an unstable system stable?



two poles $(s+a)(s+b)$

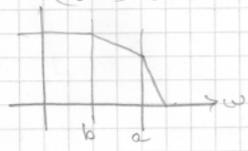

if poles at same point phase is at -90° at the break point