



Notes 04-12-10

COMPENSATION

Reduced Gain

New gain = $(A_0 - 1)$ dB
 Reduced gain \rightarrow Lower DC gain + Lower bandwidth

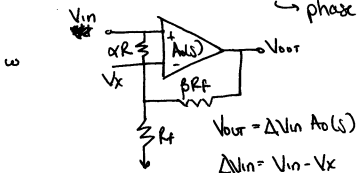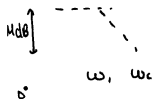Want P.M. of 50°
 \rightarrow phase margin



originally 0° P.M., changed to approximately 60° P.M.

$$\frac{V_{in} - V_x}{\alpha R} - \frac{V_x}{R_f} - \frac{V_x - V_{out}}{\beta R_f} = 0$$

$$\times \left[\frac{1}{\alpha R} + \frac{1}{R_f} + \frac{1}{\beta R_f} \right] = \frac{V_{in}}{\alpha R} + \frac{V_{out}}{\beta R_f}$$

$$\frac{V_{in} - V_{out}}{A_0(s)} \left[\frac{1}{\alpha R} + \frac{1}{R_f} + \frac{1}{\beta R_f} \right] = \frac{V_{in}}{\alpha R} + \frac{V_{out}}{\beta R_f}$$


\uparrow
 ΔV_{in}

- Amount of input applied is smaller than original \rightarrow reducing original gain


$$(V_{in} - \frac{V_{out}}{A_0(s)}) \left[\frac{1}{\alpha R} + \frac{1}{R_f} + \frac{1}{\beta R_f} \right] = \frac{V_{in}}{\alpha R} + \frac{V_{out}}{\beta R_f}$$

$$V_{in} \left[\frac{1}{\alpha R} + \frac{1}{R_f} + \frac{1}{\beta R_f} - \frac{1}{\alpha R} \right] = \frac{V_{out}}{A_0(s)} \left[\frac{1}{\alpha R} + \frac{1}{R_f} + \frac{1}{\beta R_f} \right] + \frac{V_{out}}{\beta R_f}$$

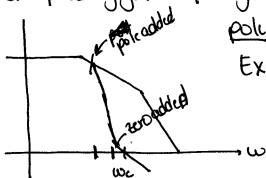- Is there a way to compensate without killing the gain?
 (keep unity gain frequency at ω_c)




pole followed by a zero

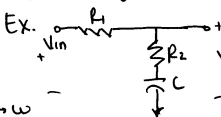


$$\frac{R_2 + 1/sC}{R_1 + R_2 + 1/sC}$$

$$= \frac{1 + sR_2C}{1 + s(R_1 + R_2)C}$$

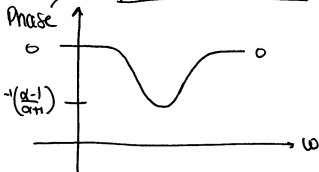
Generic TF:
$$\frac{V_{out}}{V_{in}} = \frac{K(s+1)}{as^2 + 1}$$



Opamp example

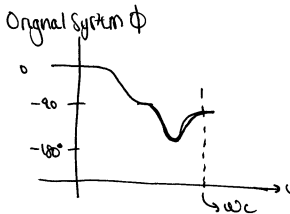


Compensation called LAG compensation

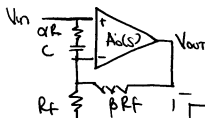

- can live with reduced bandwidth in certain applications

Example:

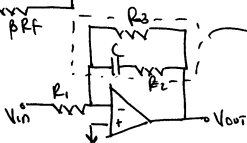


$$z_{fb} = R_3 \parallel R_2 + 1/sC$$

$$= \frac{1+sR_2R_3C}{1+s(R_2+R_3)C}$$

$$\frac{V_{out}}{V_{in}} = \frac{z_{fb}}{R_1} = \frac{1+sR_2R_3C}{R_1(1+s(R_2+R_3)C)} = a_0 \left[\frac{s+1}{as^2+1} \right]$$

If $R_2=0 \rightarrow$ proportional integral controller (P.I. controller)

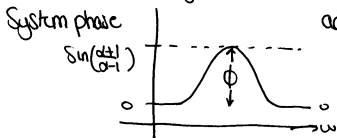Another option? Kill gain, keep bandwidth




added ϕ at crossover to get desired phase margin


- still want to keep original unity gain frequency ω_0

- Instead add zero first, pole second
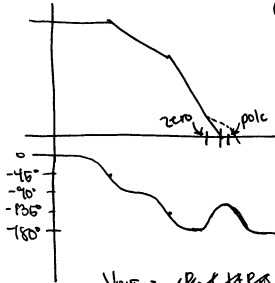
$$\text{General TF} = \frac{1}{s} \left(\frac{\alpha Ts + 1}{Ts + 1} \right)$$



Example network:

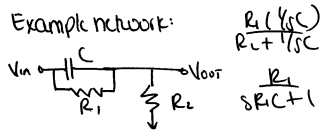


$$\frac{V_{out}}{V_{in}} = \frac{R_2}{R_2 + \frac{R_1}{1 + TsC}}$$

$$\frac{R_2 (1 + TsC)}{R_1 + R_2 + TsR_1C}$$

$$\frac{V_{out}}{V_{in}} = \frac{R_2}{R_1 + R_2} \left[\frac{1 + Ts \frac{R_1 C}{R_1 + R_2}}{1 + Ts \frac{R_1 R_2}{R_1 + R_2} C} \right]$$


if $R_1 = 0 \rightarrow$ proportional derivative controller (PD-controller) parallel combination smaller

Op Amp Example

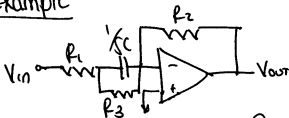



compensation is called LEAD compensation

How do you stabilize the plant itself?

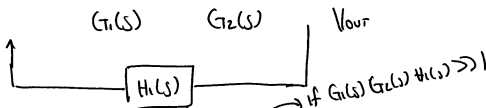

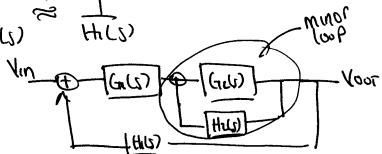
$$\frac{V_{out}}{V_{in}} = \frac{G_1(s)G_2(s)}{1 + G_1(s)G_2(s)H_1(s)} \approx \frac{1}{H_1(s)}$$




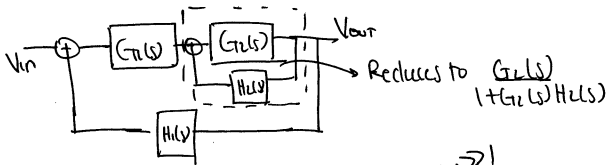

Rewrite as

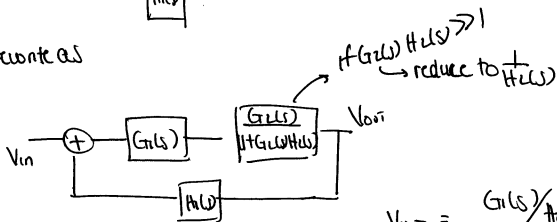



Now \rightarrow

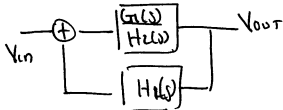

$$\frac{V_{out}}{V_{in}} = \frac{G_1(s) / H_2(s)}{1 + \frac{G_1(s)H_1(s)}{H_2(s)}}$$

$\frac{1}{H_2(s)}$ reduction $\rightarrow \frac{V_{out}}{V_{in}} = \frac{G_1(s)G_2(s)}{1 + G_2(s)H_2(s) + G_1(s)G_2(s)H_1(s)}$

Bodeplot perspective:

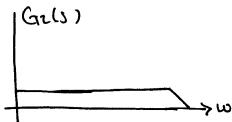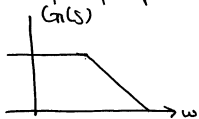


$$G_1(s) =$$

$$G_2(s) = \frac{A_1}{\tau_b s + 1}$$

A.A


ω

Consider $G(s)$ in feedback (unity gain)

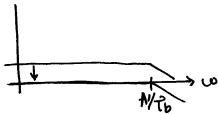


-extending bwo but lowered gain

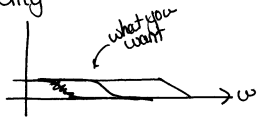-instead of unity gain at all frequencies
want unity gain at high frequencies
only





Real example:

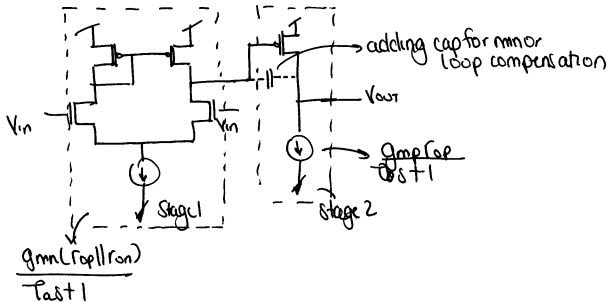

Notes 04-14-10


Compensation: LAG - P.I \rightarrow high DC gain, lower bandwidth
 LEAD - P.D \rightarrow high + high bandwidth
 REDUCED GAIN - Proportional (low gain, low bw)
 MINOR LOOP

Dominant Pole

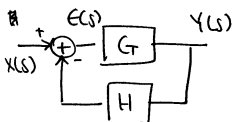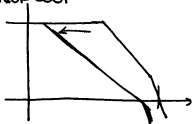



Input	Output	Feedback Transfer
V	V	K - Series-shunt
V	I	G - Series-series
I	I	K - Shunt-series
I	V	R - Shunt-shunt

Ex. Series-shunt

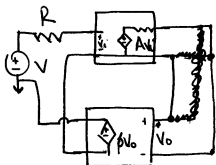


- Understand how to properly feedback different variables


Ex. Voltage-Voltage (Op-Amp)

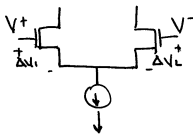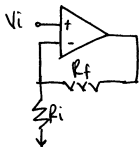

Ex. Voltage-Current

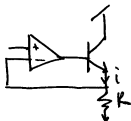

Ex. Current-Current

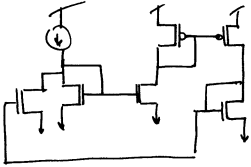


Simpler Choice : cascode




input current
output current

Ex. Current-Voltage

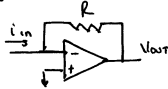

input current, output voltage



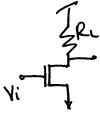
- Most circuits respond in voltage rather than current



- Device always picks free Φ variable to ~~no~~ respond with. If current is fixed with a current source, transistor will respond in voltage and vice versa

- Resistor is between current & voltage source, so it will respond with both current & voltage \rightarrow softer gain

Capacitance :

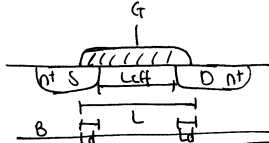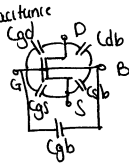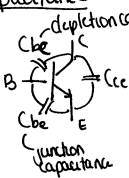

$$L_{eff} = L_{drawn} - 2L_d$$

- When referring to a layout

design this length is

~~the drawn length~~




ω

E


Analog	Digital
3-5x L_{drawn}	L_{drawn}

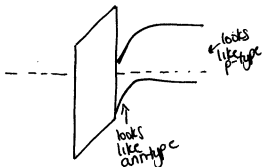Physics of Inversion / Accumulation Concepts



- just by applying a potential, change material from p-type to n-type

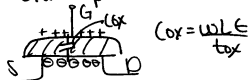- In inversion, you will only see the C_{ox} - oxide capacitance



$$C_{ox} = \frac{\epsilon_0 \epsilon_r}{t_{ox}}$$

In Linear:

$$C_{gs} = \frac{1}{2} C_{ox} \omega L$$

$$C_{gd} = \frac{1}{2} C_{ox} \omega L$$

partition half to each junction



Diagram

Only in linear region b/c continuous charge from source to drain

In Saturation (channel pinched off)

$$C_{gd} = 0$$

$$C_{gs} = \frac{2}{3} C_{ox} \omega L$$

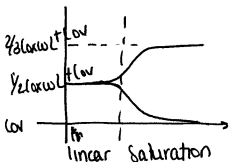
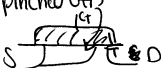


- still must include C_{ov} → overlap capacitance

Area Actually $C_{gd} = C_{ov}$ or $\frac{1}{2} C_{ox} \omega L + C_{ov}$

$$C_{gs} = \frac{2}{3} C_{ox} \omega L + C_{ov} \quad \text{or} \quad \frac{1}{2} C_{ox} \omega L + C_{ov}$$

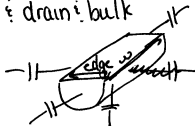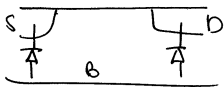Also have diodes b/c source & bulk & drain & bulk



$$C_j + 2(L+2W)C_{jsw}$$

Small-signal model

