 


Problem 18

(40 points) In this problem, you will get practice with tri-state buffers.



(a) Why is it called a "tri-state buffer"? What are the 3 values that F can take?

(b) Implement a 2:1 mux using only tristate buffers.


(c) Implement a 4:1 mux using only tristate buffers.

(d) Now, we would like to implement a 2:4 decoder using only tristate buffers.

A	B	F3	F2	F1	F0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

Fig: Truth table for a 2:4 decoder.

 A possible implementation is as follows: Let us examine $F3$: We want to route the logic value 1 to $F3$ when A and B are both 1; and route the logic value of 0 to $F3$ otherwise.



Note how the tristate buffers are used above to build a "switching network". The AND of two inputs is implemented as two tristate buffers in series, and the OR of two inputs is implemented as two tristate buffers in parallel.

- Using a similar approach, implement F_2 , F_1 , and F_0 .
- How many tri-state buffers have you used in total to implement a 2:4 decoder?

(e) What is the advantage of using tri-state buffers rather than AND, OR, NOT gates?

What might be the disadvantage?

(f) Can every Boolean function be implemented using only tri-state buffers? If so, give the sketch of a proof. If not, give a counterexample.