


LECTURE : CMOS TECHNOLOGY

AIM: Examine how the logic gates (and memory) are implemented using transistors.


Transistor: basically a switch

CMOS: Complementary MOS (used in integrated circuits)

Two types of transistors

 


N-MOS

 

P-MOS


Basic operation :

N-mos

 

← passes the signal (current) through

||| equivalent to


 


X
signal blocked

|||
equivalent to





N-Mos passes "0" well:

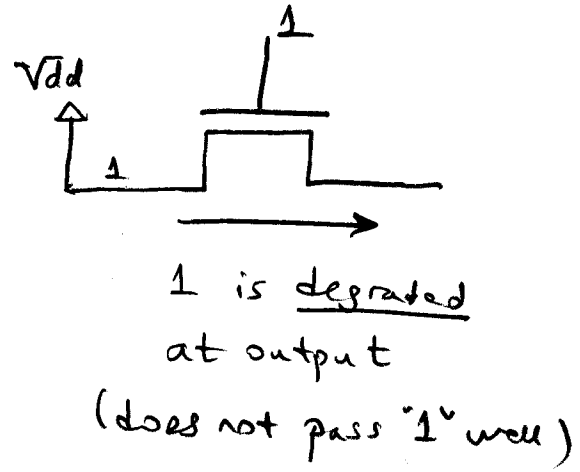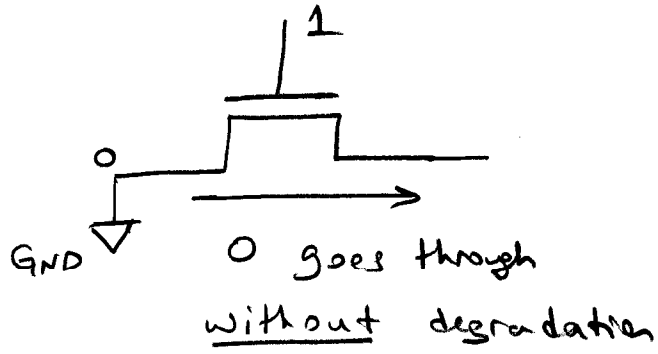


Basic operation :



P-MOS :

 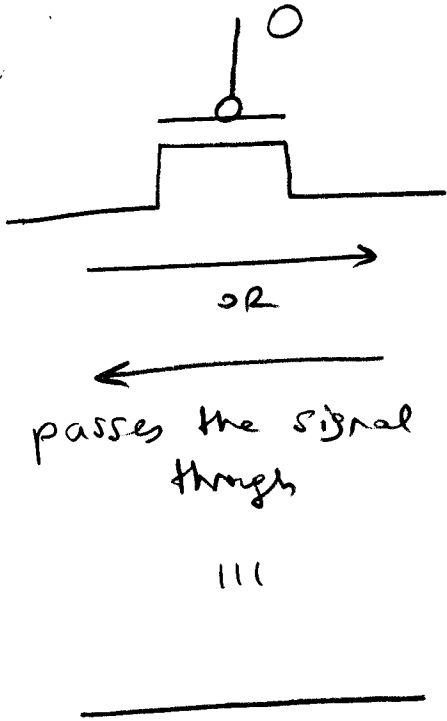

|||

 


P-mos passes "1" well ;

  

(does not pass 0 well)

- ALL Boolean functions can be implemented in CMOS.

Main idea: (chip layout)

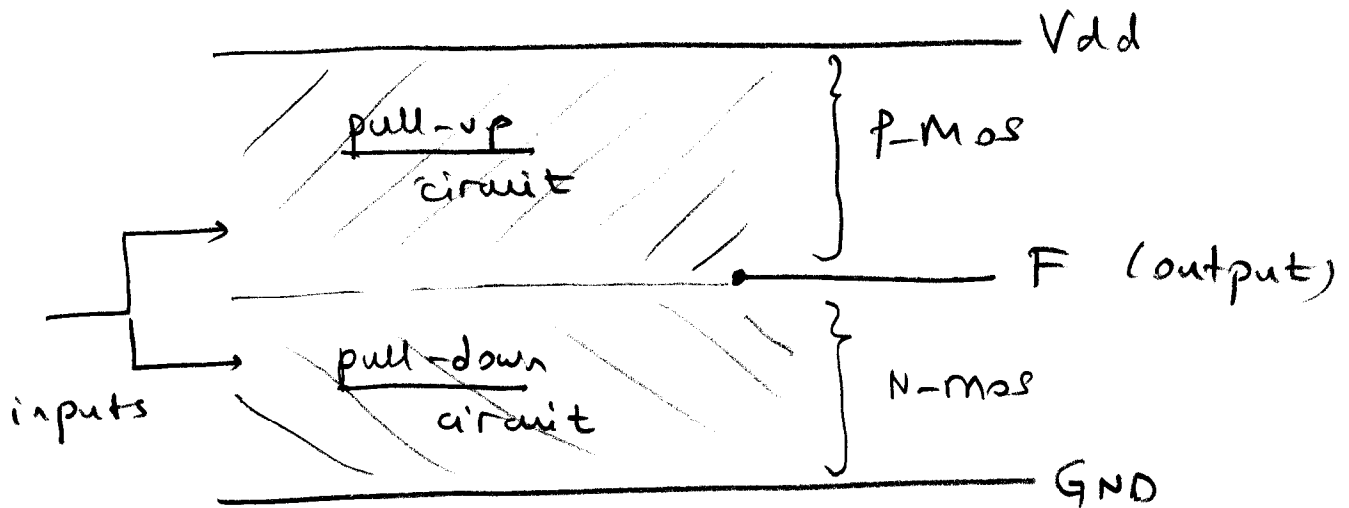


- Pull-up circuit implements the "1"s (ON-TERMS) of F , using only P-MOS transistors
- Pull-down circuit implements the "0"s (OFF-TERMS) of F , using only N-MOS transistors.

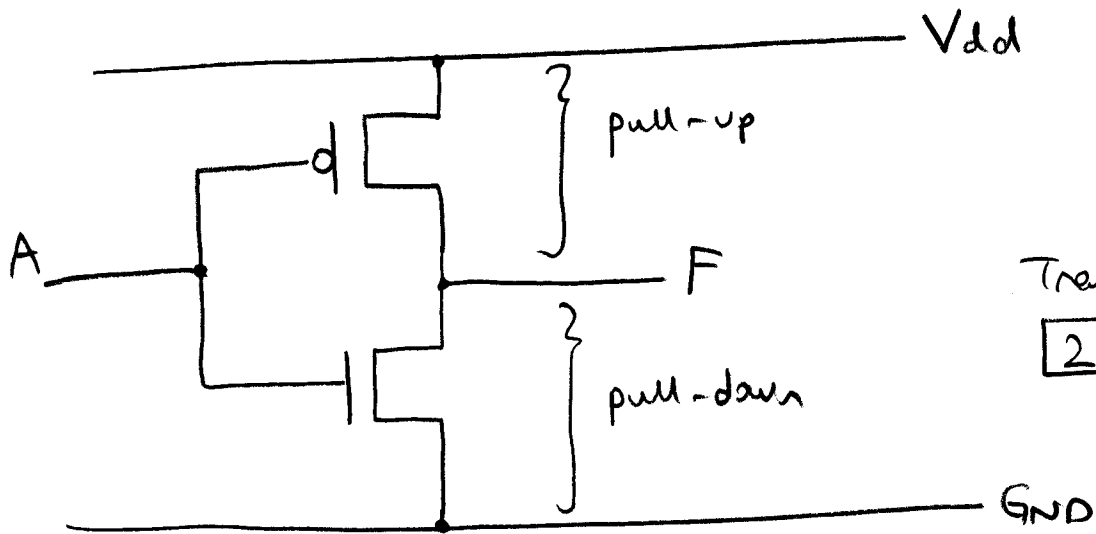Example 1; Implement an inverter in CMOS



Solution: $F = A'$ \longrightarrow implement in P-MOS

$F' = A$ $\xrightarrow[\text{TRANS}]{\text{OFF}}$ implement in N-MOS




Transistor count:

2T

 Example 2: Implement a NAND gate in CMOS.

Solution: $F = (A \cdot B)' = A' + B'$ → OR: implement as a parallel network of switches

$F' = A \cdot B$ ← Series network of switches.



Key Observations:

1 - CMOS does not leave the Boolean fn output floating. F is connected either to Vdd or GND. (network is either pulling up to Vdd or down to GND).


2 - Energy is consumed only when the output is switching from Vdd \rightarrow GND or GND \rightarrow Vdd. After circuit stabilizes, no static energy

Assumption, \rightarrow CMOS used widely for low-power designs

Example 3 : Implement a NOR gate in CMOS

Solution : $F = (A+B)' = A' \cdot B'$


$$F' = A + B$$

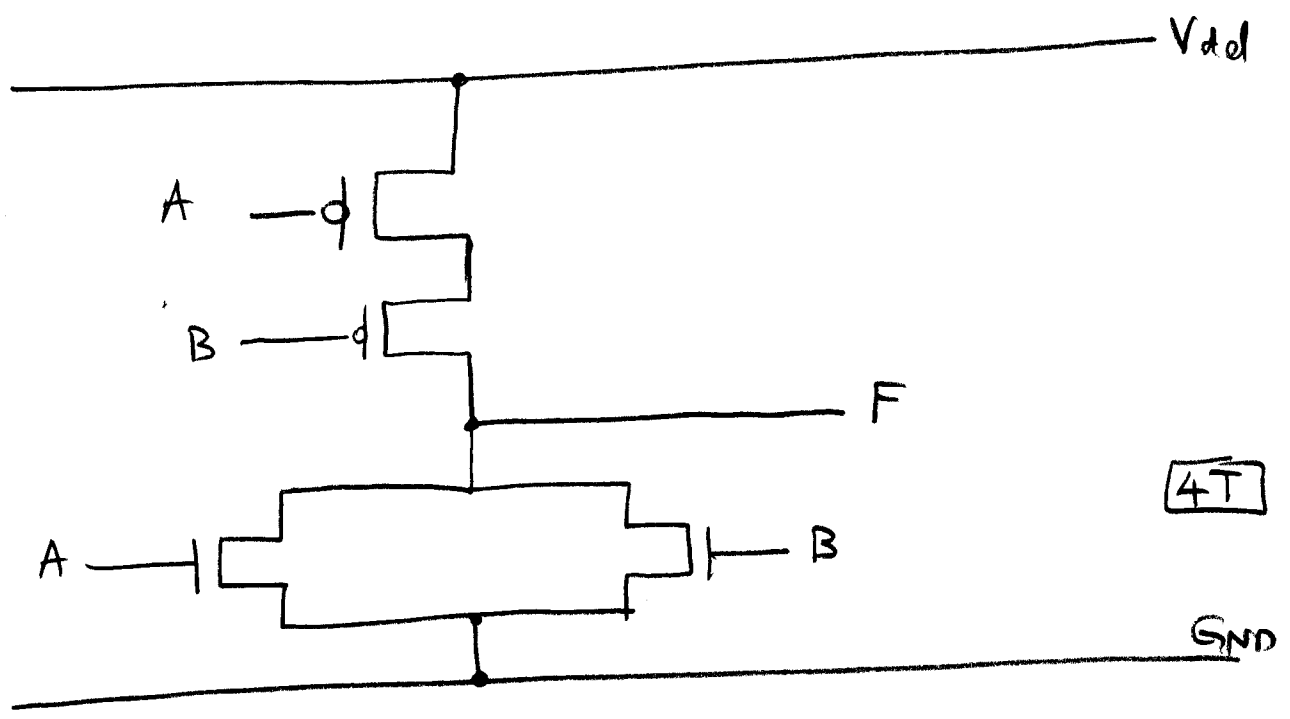

Example 4 : Implement an AND gate in CMOS.

Solution : $F = A \cdot B$

$$F' = (A \cdot B)' = A' + B'$$

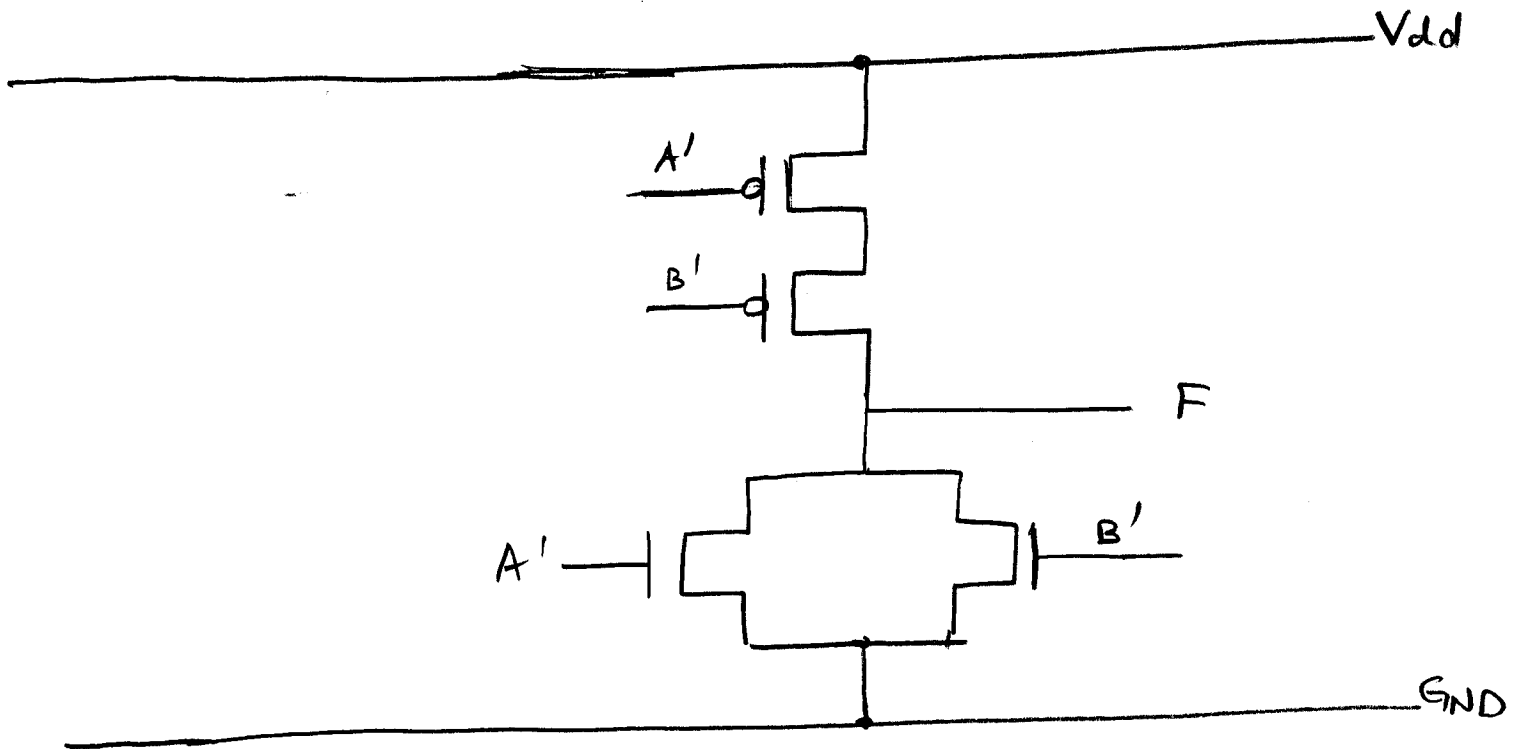


$$\text{Transistor count} = 4 + \underbrace{2}_{\text{to invert } A} + \underbrace{2}_{\text{to invert } B} = \boxed{8T}$$

[Contrast with NAND gate: 4T]

Example 5: Implement an OR gate in CMOS

Solution: $F = A + B$

$$F' = (A + B)' = A' \cdot B'$$

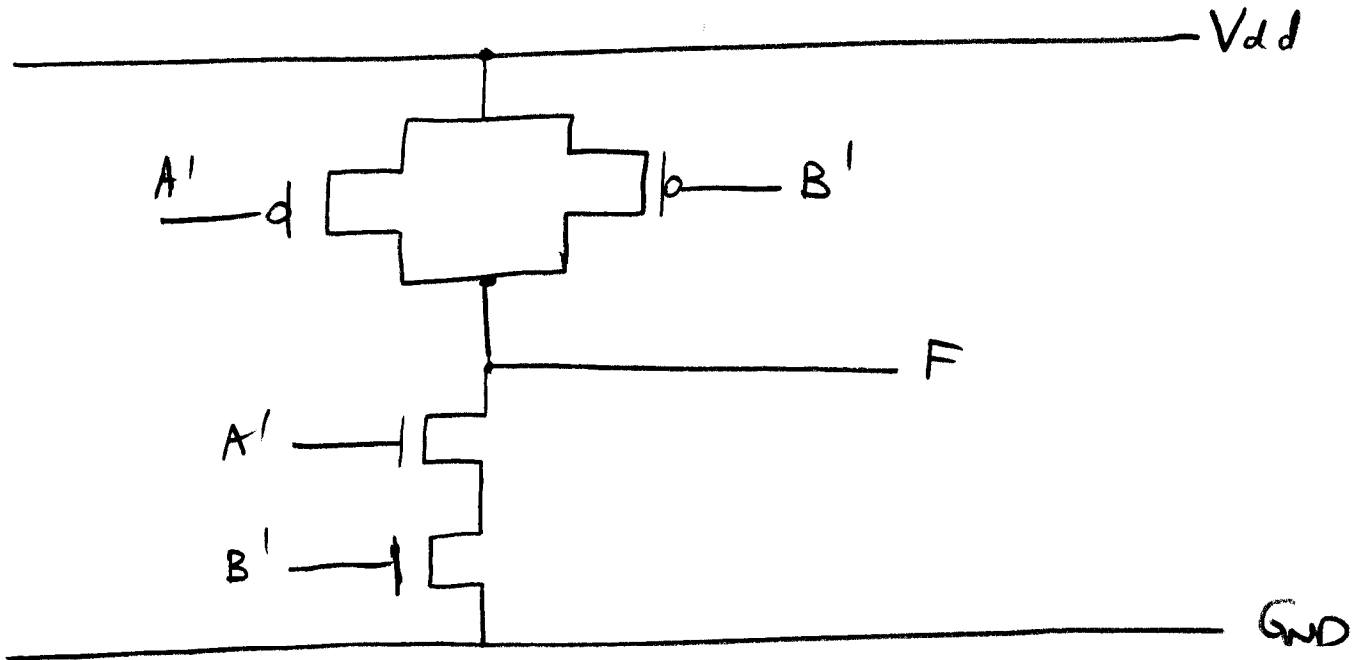

Transistor count = $4 + 2 + 2 = \boxed{8T}$


Example 6: Implement $F = A \cdot B + C$

[This shows the general procedure to implement any Boolean function.]

Solution: $F = (A \cdot B) + C$] pull-up

$$F' = (A \cdot B + C)' = (A \cdot B)' \cdot C' \\ = (A' + B') \cdot C'$$


pull-down

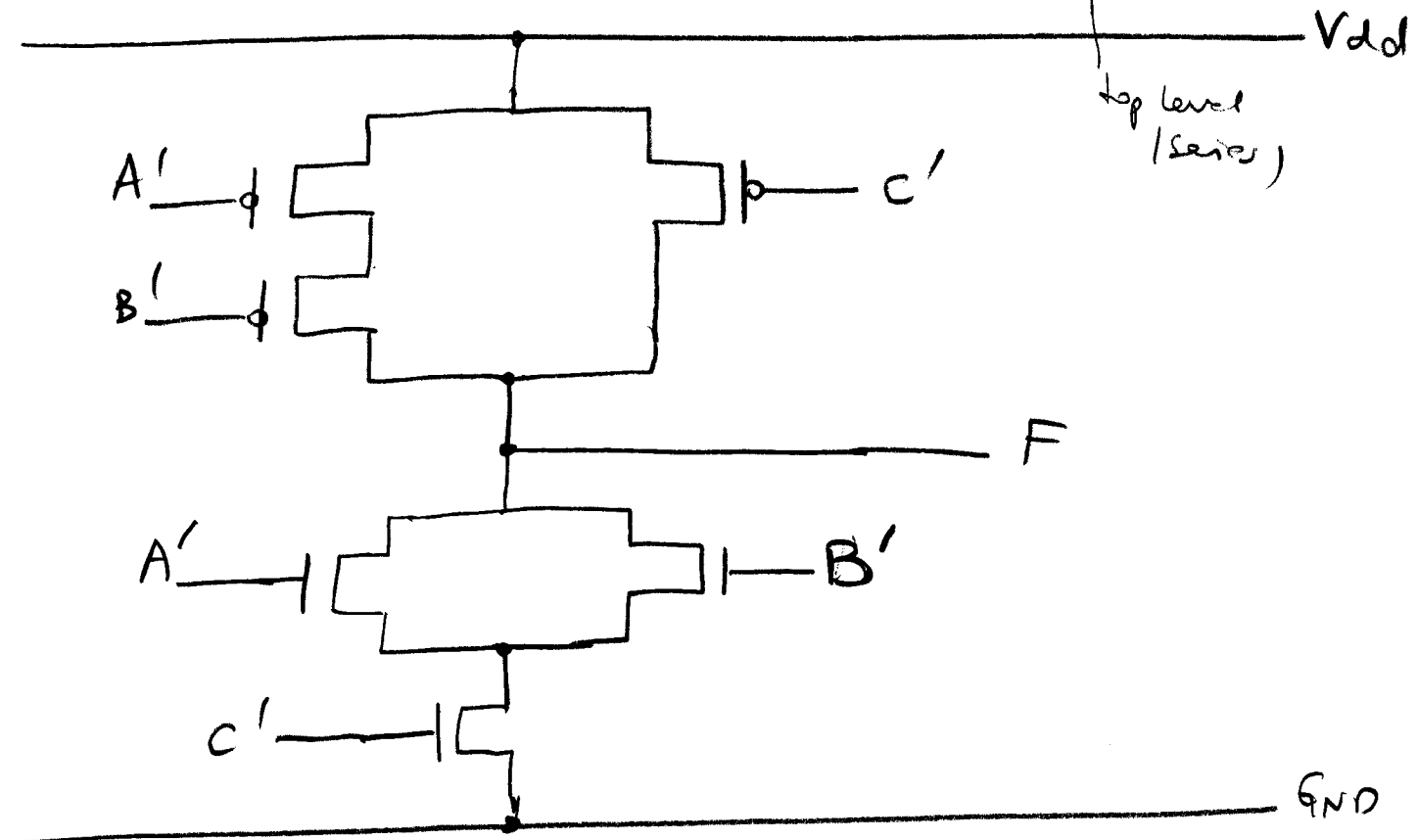

Transistor count = $6 + \underbrace{2}_{A'} + \underbrace{2}_{B'} + \underbrace{2}_{C'} = \boxed{12T}$

Memory elements in CMOS

- Cross-coupled NOR gates:

 


- Transistor count in CMOS = $2 \times \underbrace{(4T)}_{\text{per NOR Gate}} = \boxed{8T}$

- For integrated memories, we need high integration density (i.e. a high # of bits stored per unit area of silicon).
- ∴ Must reduce the area of a "cell" (a storage unit that holds 1 bit).
- Area: depends on # transistors + wiring complexity.

S-RAM cell (6 T S-RAM cell)


→ Random Access memory

 [Static RAM: static means that V_{dd}, GND used to reinforce the value stored inside. ∴ will hold the bit as long as power is on.]



- Holds 1 bit.
- cross coupled inverters
- $(2T/inverter) \times 2 \text{ inverters} + 2 \text{ n-Mos} = \boxed{6T}$

Operation of S-RAM cell :

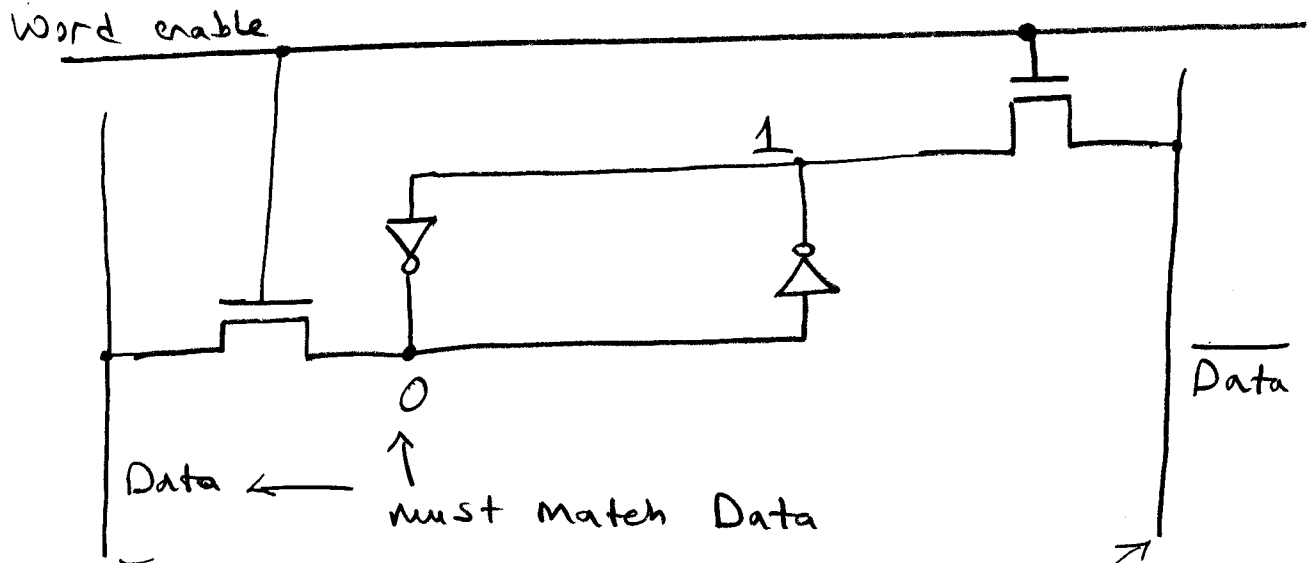

- Assume the cell is initially storing a "0".
Sense amplifier detects difference.
(Reading)

READING from the S-RAM cell:

- ① Both Data and $\overline{\text{Data}}$ are pre-charged to 1.
 - (Word Enable originally low)
- ② Word Enable put high.
 - The "0" in the cell pulls the Data line to 0 (since N-MOS passes 0 well.)
- ③ The sense amplifier senses the difference between Data and $\overline{\text{Data}}$.
 - If Data has voltage $\overset{\text{sufficiently less than}}{<} \overline{\text{Data}}$, then a value of "0" declared.
 - Otherwise a "1" is declared.

WRITE : to the S-RAM cell.

Example: writing a "0".

① Data = 0 and $\overline{\text{Data}} = 1$ (driven by external circuitry)


② Word Enable = 1

- The external circuitry drives these values into the cell.

③ Word Enable = 0.

S-RAM chip:

Example:

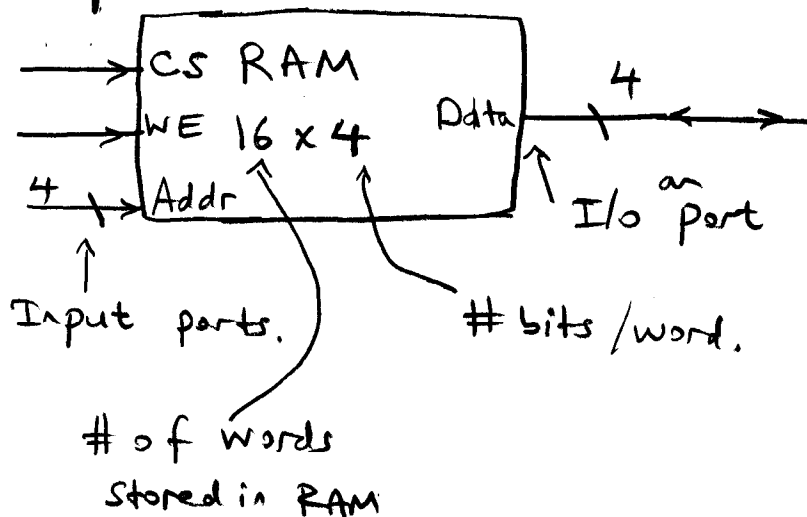

CS: Chip Select (if low, cannot read or write)


WE: Write Enable (if CS == 1, and WE == 1 write
CS == 1, and WE == 0 read.)

Address: Need $\log_2(16) = 4$ bits to address each word.


Conceptual organization:16 x 4 RAM:

- $16 \cdot 4 = \underline{\underline{64}}$
cells in total

 - Idea: Address
one of the 16
words (to write in)
or (read out) an
entire word.




Conceptual organization:

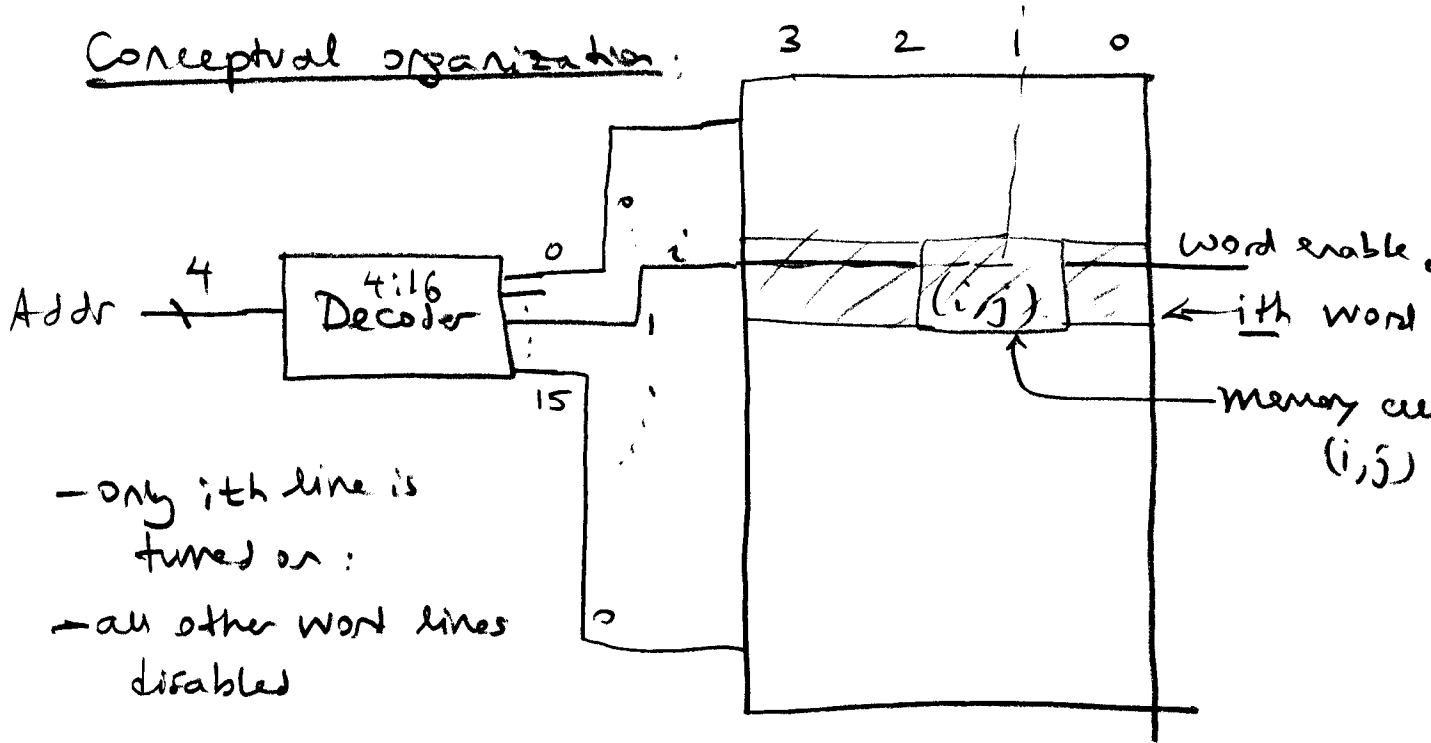


- only i th line is turned on:
- all other word lines disabled

SRAM Read Cycle Sequencing

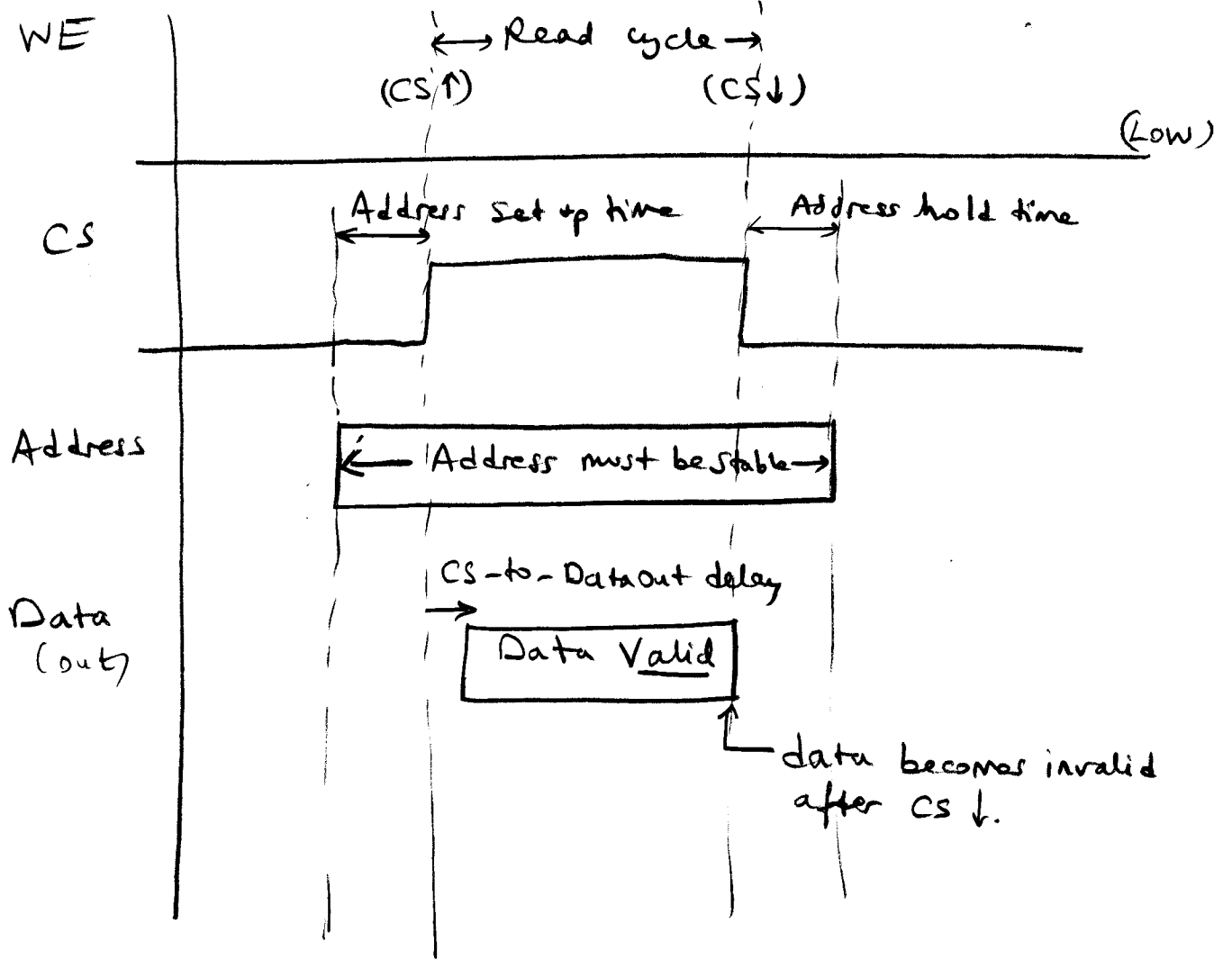


S-RAM WRITE CYCLE SEQUENCING

 

Wider, S-RAM's have a more efficient ^{internal} organization


Example; 1024 x 4 SRAM.

not a good idea to:

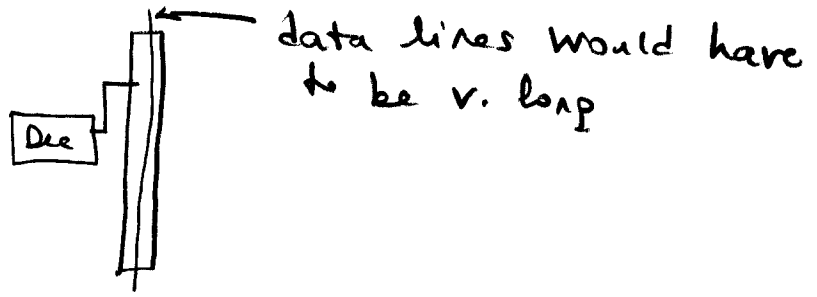


Preferred organization; uses a square storage matrix.

 $1024 \times 4 = 64 \times 64$. (square)
 $(2^{10}) \times (2^2) = 2^6 \times 2^6 \leftarrow \text{internal}$



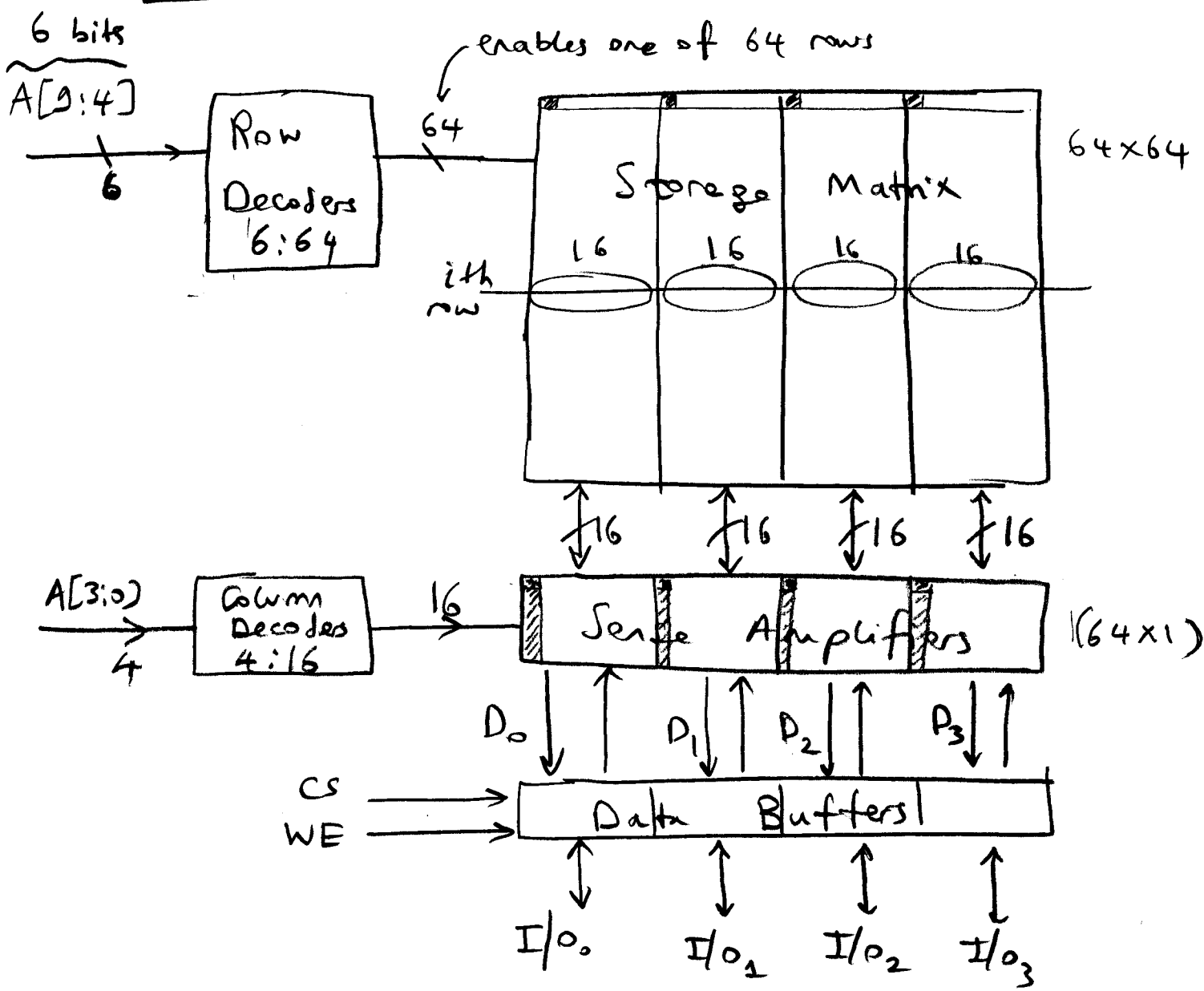Internal organization with STORAGE MATRIX




- Note that the 4 bits of a word do not sit next to each other in storage matrix (i.e., physical storage location different from that in conceptual diagram.)

- The word at address 0000000000 is shown shaded above.

Dynamic RAM

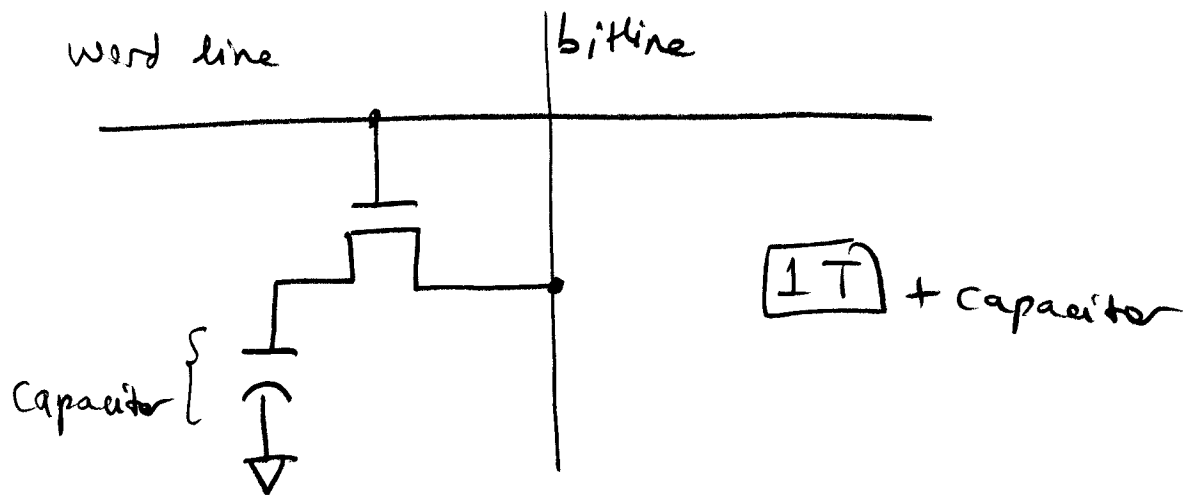- smaller space per cell \rightarrow higher integration density
- slower than S-RAM
- needs refreshing (\therefore dynamic memory)



- Capacitor holds the charge
- Charge leaks over time \therefore need to read out all content & write them back in ("refresh")