 



Implementation of intermediate combinational logic building blocks

**I** Mux: (multiplexer)




2 inputs  
2:1 mux  
1 output  
[mux symbol]

operations:

 

If  $S=0$ ,  $F=A$

 


If  $S=1$ ,  $F=B$


- How can we implement a 2:1 mux using AND, OR and NOT gates? [Implementations]

• First, write down the Boolean expression for  $F$ . [ask class]

$$F = S' \cdot A + S \cdot B$$

 

4:1 mux

 


Ask how many control inputs we need.

$$F = S_1' \cdot S_0' \cdot A + S_1' \cdot S_0 \cdot B + S_1 \cdot S_0' \cdot C + S_1 \cdot S_0 \cdot D$$

Emphasize interface & implementation:
 
## II Design of Adder:

- Half-adders create Interface: (schematic):



Behavior/operation:


A	B	Sum	cout
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$\text{Sum} = A'B + AB' (= A \oplus B)$$

$$\text{cout} = A \cdot B$$

give discussion of unsigned numbers.


習

 


Half-adder

[Reading: ch 4.1-4.4, 4.4, ch 6.1]


\* Implementation

 

- Full-adder:

 

A	B	Cin	Sum	cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 

$$\begin{aligned}
 \text{sum} &= A'B'C + A'B \cdot C' + AB'C' + ABC \\
 &= A' \underbrace{(B'C + BC')}_{(B \oplus C)} + A \underbrace{(B'C' + BC)}_{(B \oplus C)'}
 \end{aligned}$$

$$= A \oplus (B \oplus C) = A \oplus B \oplus C_{in}$$

(XOR is associative)  
 (you will show this in your next assignment)

• XOR: basic operation ~~for~~ binary addition, (but ~~has~~ ~~no~~ cannot track carries)

Ex)  $1 \oplus 0 \oplus 1 \oplus 1 \oplus 1 = 0$

XOR of an odd number of 1's is 1,  
 even 1's is 0

$$\text{Sum} = A \oplus B \oplus C_{in}$$

$$\text{Carry} = A'B'C + AB'C + ABC' + ABC$$

$$= BC(A+A') + A(B'C+BC')$$

$$= BC + A \cdot (B \oplus C)$$

$$= C(A'B+AB') + AB(C+C')$$


$$= C(A \oplus B) + AB$$

$$\text{Carry} = C_{in} \cdot (A \oplus B) + A \cdot B$$

[Note:

$$C_{in}(A \oplus B) + A \cdot B$$


Also possible implementation

 


- How do we implement n-bit addition?

A3 A2 A1 A0

B3 B2 B1 B0

 

Implementation:

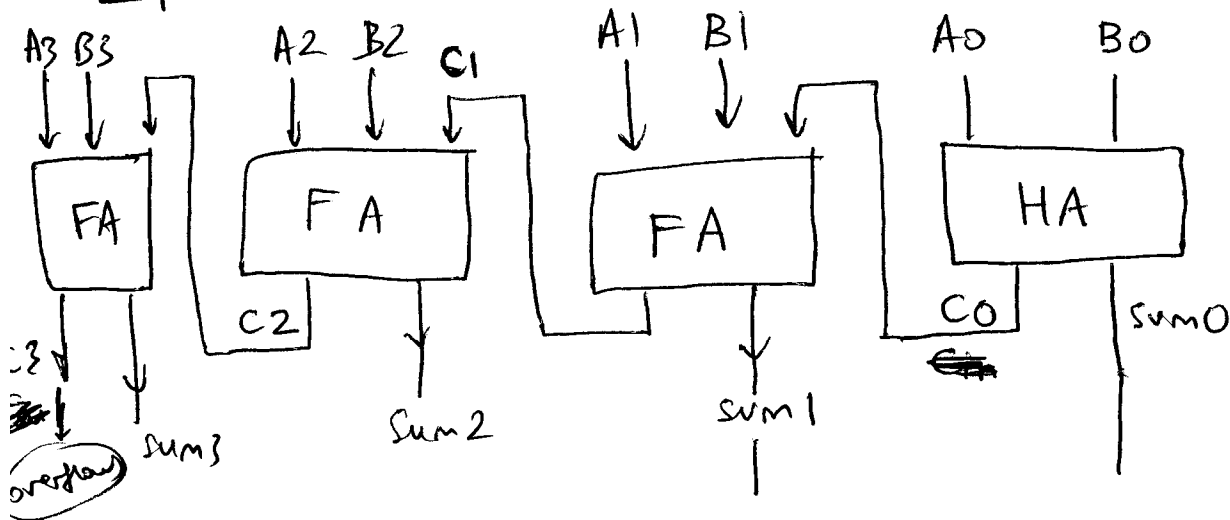

- Ripple-carry adder

(slow: as  $n \uparrow$ , the delay scales linearly with  $n$ )  
 $\rightarrow$  ~~target~~

~~Does not~~

- does not handle overflow.

~~Does not~~

(Ask class: How can I detect the overflow in the addition of 2 unsigned numbers?)


Answer: carryout from the last stage indicates overflow. for unsigned numbers.)  
 Overflow Detected = C3 (above.)

ECE 152A Lecture # 2

- Boolean minimization (K-maps <sup>using</sup>)

~~(Reading for this week: Ch 5 & 8 skip 5-6  
variable k-maps.)~~

 Recall our full adder example from last lecture  
go back to 3



A	B	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

→ to page 5

Last time: we did algebraic ~~method~~ simplification,





This time: understand geometrically what we're doing when simplifying & design a <sup>better</sup> ~~fast~~ method for simplification.

Boolean cube:

represent the input vectors in a vector space:

Sum

Count

    

$$\text{Count} = A'BC + AB'C + ABC' + ABC$$

$$\textcircled{1} = (A' + A)BC + AB'C + ABC'$$

OR do:  $\textcircled{2}$

$$= A'BC + AB'C + AB(C' + C)$$


OR do:  $\textcircled{3}$

$$= A'BC + A(B' + B)C + ABC'$$

- Hence, main insight is: Algebraic simplification by grouping corresponds to grouping of 'minterms' on Boolean cube.

- If the number of inputs is ~~not~~ not very high (well address  $\leq 4$ ), then grouping by visualization tools ~~may be faster~~ is faster/easier.

- Karnaugh map

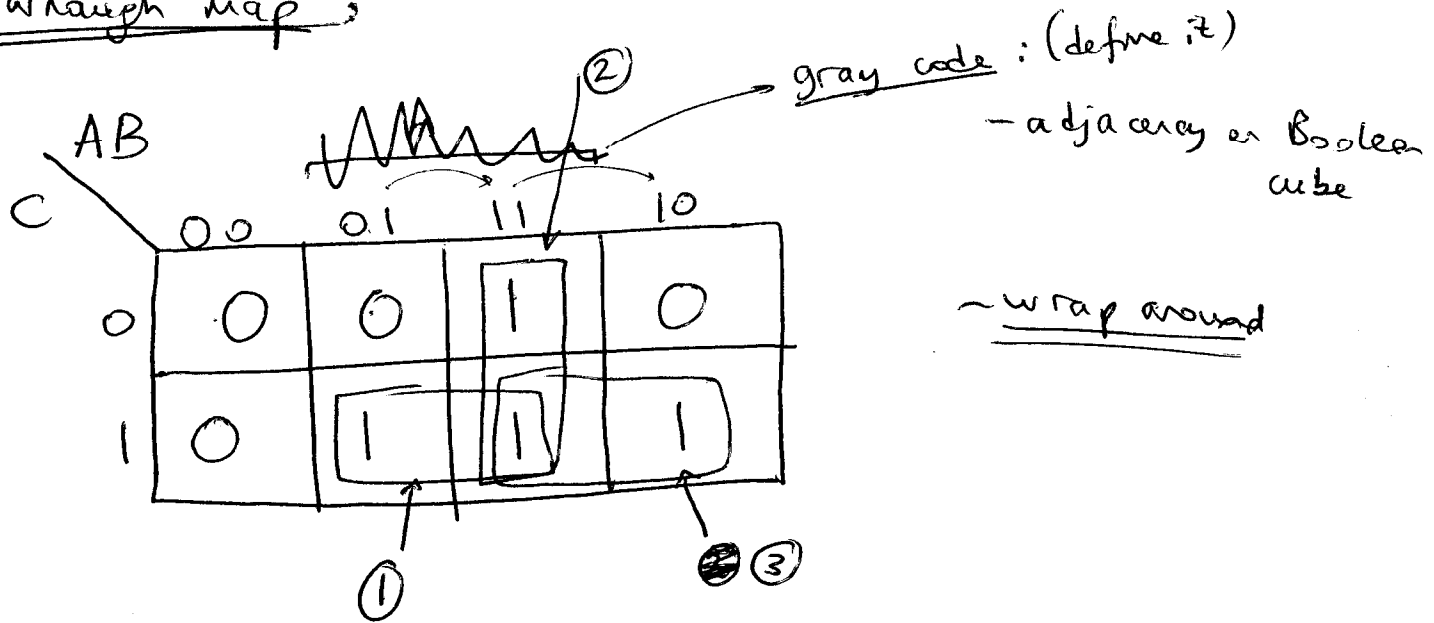


- In the future: we will go directly from the truth table to the K-map.

- An important skill is to be able write down the resulting algebraic expression after minimization (grouping) on the K-map.



~S<sub>0</sub>, above:

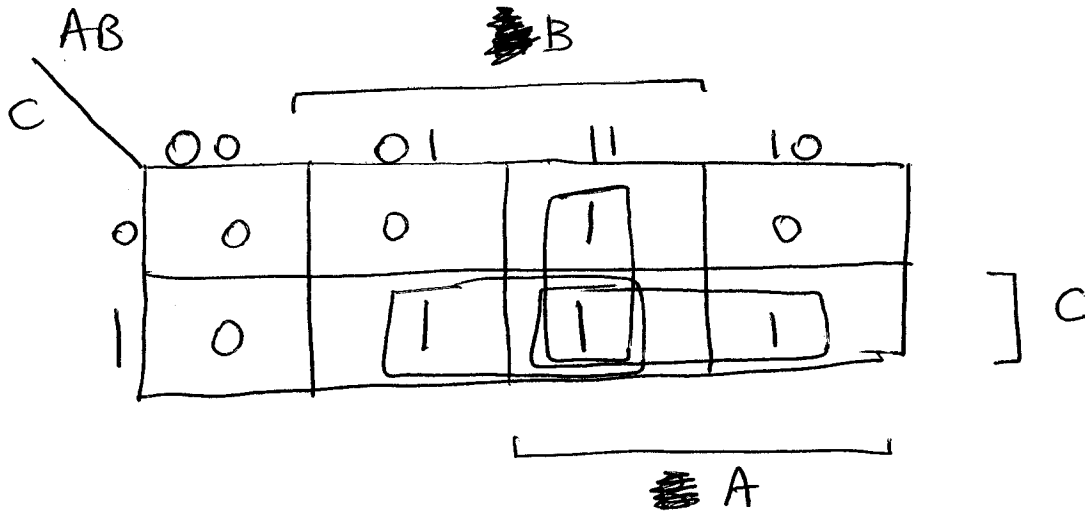

$$\text{Count} = AB + BC + AC.$$


$$= (C_{in} (A+B) + AB)$$


← the "majority function" (3-inputs) (is equal to 1 iff the majority of the inputs is 1)

I have illustrated above how to do simplification using

K-maps

 Answer Example: K-map of a 4-variable function



 

(all p.i.'s  
here are  
essential)

$$F = C + A'BD + B'D'$$

Rigorous treatment of these concepts:

- Two-level <sup>logic</sup> Canonical forms:

• Any Boolean function <sup>write</sup> in a unique canonical form:

2 forms  $\left\{ \begin{array}{l} \text{Sum of products (minterm expansion)} \\ \text{Product of sums (maxterm expansion)} \end{array} \right.$

Sum of products :

A	B	C	<del>Σ</del> <u>Minterms</u>
0	0	0	<del>Σ</del> $A'B'C' = m_0$
0	0	1	$A'B'C = m_1$
0	1	0	$A'BC' = m_2$
1	1	1	$ABC = m_7$

an ANDed product of literals in which each variable appears exactly once either in true or complemented form.

ex)  $AB$  is not a minterm.  
 $ABB'C$  is not a minterm.

then lastly

~~Σ~~  
↑

$$\text{cout} = A'BC + AB'C + ABC' + ABC$$

(~~canonical~~) <sup>canonical</sup> Sum of products form

- minterm expansion

$$= \sum m_3 + m_5 + m_6 + m_7$$

Product of Sums :  
(maxterm expansion)

maxterm:  
an ORed sum of literals in which each variable appears exactly once in true or complemented form

A	B	C	maxterms
0	0	0	$A + B + C = M_0$
0	0	1	$A + B + C' = M_1$
0	1	0	$A + B' + C = M_2$
0	1	1	$A' + B + C = M_3$
1	0	0	$A' + B + C = M_4$
1	0	1	$A' + B + C' = M_5$
1	1	0	$A' + B' + C = M_6$

$$\text{cout} = m_3 + m_5 + m_6 + m_7.$$

$$(\text{cout})' = m_0 + m_1 + m_2 + m_4 \quad (\text{ASK class})$$

$$= A'B'C' + A'B'C + A'BC' + AB'C'$$

$$\boxed{\text{cout} = ((\text{cout})')'}$$

$$= (A'B'C' + A'B'C + A'BC' + AB'C')'$$

$$= \underbrace{(A+B+c)}_{M_0} \cdot \underbrace{(A+B+c')}_{M_1} \cdot \underbrace{(A+B'+c)}_{M_2} \cdot \underbrace{(A'+B+c)}_{M_4}$$

$$= \boxed{M_0 \cdot M_1 \cdot M_2 \cdot M_4} \quad (\text{maxterm expansion})$$

hence:

$$\text{cout} = m_3 + m_5 + m_6 + m_7 = M_0 \cdot M_1 \cdot M_2 \cdot M_4$$

$$\text{cout}' = m_0 + m_1 + m_2 + m_4 = M_3 \cdot M_5 \cdot M_6 \cdot M_7$$

Two-level simplification: go to the Boolean cube example

now

& come back

"minimum sum of products" : Sum of products with the minimum number of product terms and out of ~~all the sum~~ all such ones, ~~there are with~~ one with the minimum number of literals.

(not a unique expansion)

"minimum product of sums" : — defined similarly

implicant : is an ANDed expression (product) that makes the function true. (So a single 1 or a group of 1's in a K-map).


prime implicant : ~~is~~ an implicant that cannot be combined with other terms ~~to~~ ~~be~~ ~~simplified~~ ~~further~~.

essential prime implicant : ~~one in which~~ a prime implicant that is ~~not~~ necessary in the expansion in order to cover a "1".

(go to example on p. 5)


Example: 2-bit comparator:  
(see sheets)

Go back to:  
Example: 2-1 mux: example:

 

$$F = I \cdot B + I' \cdot A$$

A	B	I	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

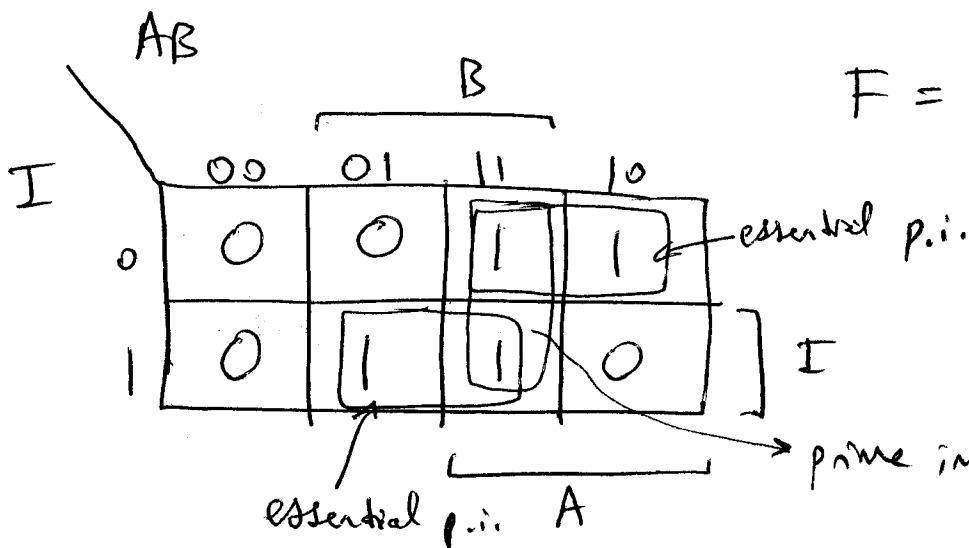


$$F = I \cdot B + I' \cdot A$$

$\textcircled{IAB}$   
↑  
consensus term,  
essential.
 
# Incompletely Specified Functions:

Ex) Design a combinational circuit that takes as input a Binary-Decimal-Coded ~~2~~ (BCD) digit  $X$  (ie.  $0 \dots 9$ ) and outputs  $X+1 \pmod{10}$ , (ie.  $0 \rightarrow 1, 1 \rightarrow 2, \dots, 8 \rightarrow 9, 9 \rightarrow 0$ ). The input is guaranteed (by external circuitry) to be in range  $0 \dots 9$ .

Design: Need 4 bits to represent the input



So, we use the numbers  $0000 \rightarrow 1001$  (0) (9) ; Note that

the input values "10"  $\rightarrow$  "15" will never occur, ~~but we~~

We can actually use this fact to our advantage when we do logic minimization,


— Let's write down the truth table for the "increment by 1" circuit.

A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X

← note wrap-around

don't care!

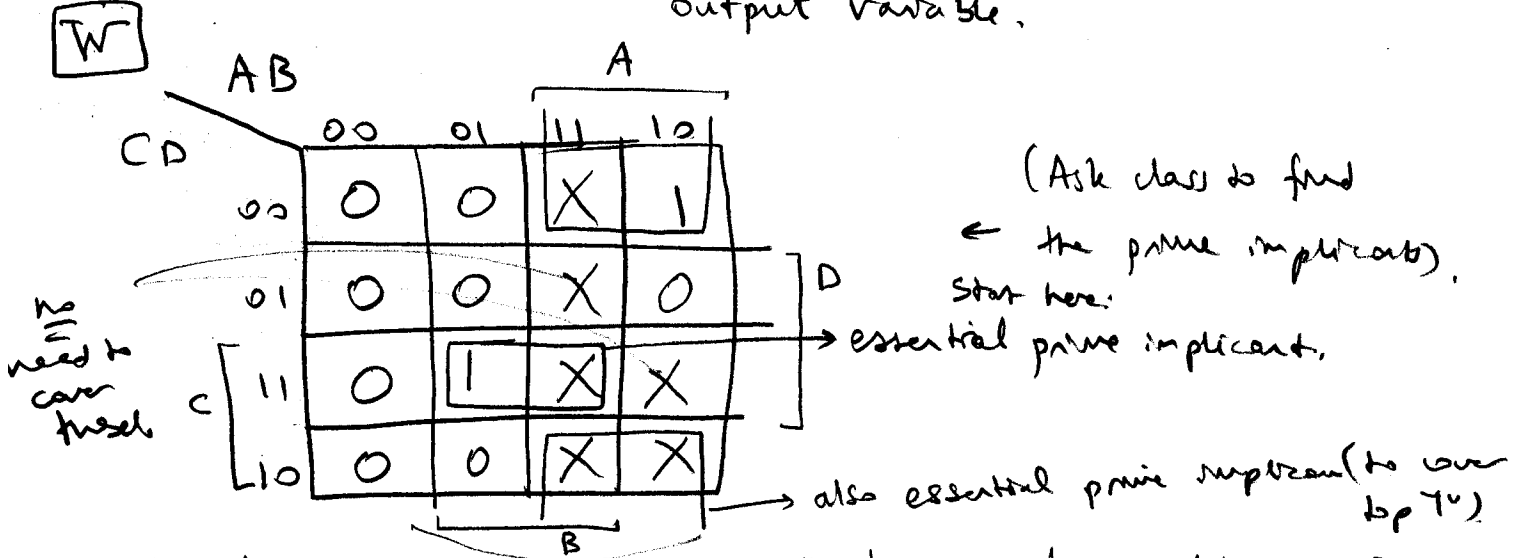Logic minimization: — need to draw a K-map for each output variable.



— The key is that I can use "X's" as 0's or 1's as I wish because those <sup>input</sup> values will not occur anyway.


— But: I don't need to care all X's!

• Hence, above, we have to draw two 1's.

$$W = BCD + AD'$$

(a minimum SOP expression for W.)

**X**

 



$$X = B'CD + BC' + BD'$$

~~Do Y and Z as <sup>exercise</sup> ~~homework~~.~~

Similarly, we find the following for Y & Z.

Answers:

**Y**

		A			
		00	01	11	10
C	00	0	0	X	0
	01	1	1	X	0
	11	0	0	X	X
	10	1	1	X	X
		B			

D

$$Y = A'c'D + CD'$$

**Z**

		A			
		00	01	11	10
C	00	1	1	X	1
	01	0	0	X	0
	11	0	0	X	X
	10	1	1	X	X
		B			

D

$$Z = D'$$