

Sequential Circuit Design with Verilog

ECE 152A – Fall 2006

Reading Assignment

- **Brown and Vranesic**
 - 6 Combinational – Circuit Building Blocks
 - 6.6 Verilog for Combinational Circuits
 - 6.6.1 The Conditional Operator
 - 6.6.2 The If-Else Statement
 - 6.6.3 The Case Statement

Reading Assignment

- **Brown and Vranesic (cont)**
 - 7 Flip-Flops, Registers, Counters, and a Simple Processor
 - 7.12 Using Storage Elements with CAD Tools
 - 7.12.2 Using Verilog Constructs for Storage Elements
 - 7.12.3 Blocking and Non-Blocking Assignments
 - 7.12.4 Non-Blocking Assignments for Combinational Circuits
 - 7.12.5 Flip-Flops with Clear Capability
 - 7.13 Using Registers and Counters with CAD Tools
 - 7.13.3 Using Verilog Constructs for Registers and Counters

The Gated D Latch

- Transparent on high phase of clock

```
module D_latch(D, Clk, Q);
  input D, Clk;
  output Q;
  reg Q;

  always @(D or Clk)
    if (Clk)
      Q = D;
endmodule
```

The Gated D Latch

- The “if” construct
 - When D or CLK change value:
 - if CLK = 1, set Q = D
 - Since there is no else, assignment occurs only when CLK = 1
 - Q follows D when CLK = 1
 - Q remains latched on CLK = 0
 - “Always” construct triggered by change in value of D or CLK
 - Either change can cause the output to change

The Gated D Latch

- The “always” construct
 - Responds to changes in the signals on the sensitivity list
 - always @ (D or Clk)
 - Example above is “level sensitive”
 - When D or Clk changes value
 - Make edge triggered by using Verilog keywords posedge and negedge
 - i.e., always @ (posedge Clk)

The Edge Triggered D Flip-Flop

- Positive edge triggered

```
module flipflop(D, Clock, Q);
    input D, Clock;
    output Q;
    reg Q;

    always @(posedge Clock)
        Q = D; // Q+ = D, characteristic function

endmodule
```

The Edge Triggered D Flip-Flop

- D is not included on sensitivity list since it cannot cause output (Q) to change
 - No transparent phase with edge triggered flip-flops
- Characteristic function used in assignment statement
 - Defining next state (Q⁺) of the flip-flop

The Edge Triggered JK Flip-Flop

- Assign characteristic function to Q on rising clock edge ($Q^+ = JQ' + K'Q$)

```
module JKflipflop(J,K, Clock, Q);
  input J,K, Clock;
  output Q;
  reg Q;

  always @(posedge Clock)
    Q = J && ~Q || ~K && Q; // Q+ = JQ' + K'Q

endmodule
```


November 2, 2006

ECE 152A - Digital Design Principles

9

The Edge Triggered JK Flip-Flop

- Functional Simulation

 

November 2, 2006

ECE 152A - Digital Design Principles

10


The Edge Triggered T Flip-Flop

- Assign characteristic function to Q on rising clock edge ($Q^+ = T \text{ XOR } Q$)

```
module Tflipflop(T, Clock, Q);  
  input T, Clock;  
  output Q;  
  reg Q;  
  
  always @(posedge Clock)  
    Q = T ^ Q; // Q = T XOR Q  
  
endmodule
```

The Edge Triggered T Flip-Flop

- Functional Simulation

 

Blocking and Non-Blocking Assignments

- $Q = D$
 - Equal sign (=) signifies a blocking assignment
- Statements are evaluated in the order in which they are written
 - If a variable is given a value by a blocking assignment, the new value is used in evaluating all subsequent statements in the block

Blocking and Non-Blocking Assignments

■ Blocking Assignment Statement Example

```
module example1(D, Clock, Q1, Q2);
  input D, Clock;
  output Q1, Q2;
  reg Q1, Q2;

  always @(posedge Clock)
  begin
    Q1 = D;
    Q2 = Q1;
  end


endmodule
```

Blocking and Non-Blocking Assignments

 - Example synthesizes two positive edge triggered D flip-flops
 - Both flip-flops triggered by same clock edge
- Both assignments in always block are blocking
 - Q1 gets the value D
 - Q2 then gets the new value of Q1
 - Q1+, which is now D

Blocking and Non-Blocking Assignments

- The synthesized circuit with blocking assignment statements




Blocking and Non-Blocking Assignments

- Non-Blocking Statements (\leq)
 - Non-blocking assignment statements in an always block are evaluated using the values of the variables when the block is entered

```
always @(posedge Clock)
begin
    Q1 <= D; // substitute
    Q2 <= Q1; // non-blocking assignments
end
```

Blocking and Non-Blocking Assignments

 - Q2 gets the value of Q1 when the always block is entered
 - The synthesized circuit with non-blocking assignment statements
 - Flip-flops connected in cascade



Blocking and Non-Blocking Assignments

■ Blocking Assignment Statement Example

```
module example3(x1, x2, x3, Clock, f, g);
  input x1, x2, x3, Clock;
  output f, g;
  reg f, g;

  always @(posedge Clock)
  begin
    f = x1 & x2;
    g = f | x3;
  end


endmodule
```

Blocking and Non-Blocking Assignments

- Both f and g are implemented as the outputs of D flip-flops
 - Synthesized as flip-flops because the sensitivity list of the always block specifies posedge Clock
- “g” gets the new value (Q^+) of “f” OR’d with x_3

Blocking and Non-Blocking Assignments

 - The synthesized circuit
 - Blocking assignment statements



November 2, 2006

ECE 152A - Digital Design Principles

21

Blocking and Non-Blocking Assignments

- If assignment statements changed to non-blocking

```
always @(posedge Clock)
begin
  f <= x1 & x2;
  g <= f | x3;
end
```

- “g” gets the previous value of “f” (the value when the always block is entered, i.e., Q)


November 2, 2006

ECE 152A - Digital Design Principles

22

Blocking and Non-Blocking Assignments

 - The synthesized circuit
 - Non-blocking assignment statements



Blocking and Non-Blocking Assignments

- General Rule
 - The results of non-blocking assignments are visible only after all of the statements in the always block have been evaluated
 - When there are multiple assignments to the same variable inside an always block, the result of the last assignment is maintained

Flip-Flops with Clear

■ Asynchronous Clear

```
module flipflop(D, Clock, Resetn, Q);
  input D, Clock, Resetn;
  output Q;
  reg Q;

  always @(negedge Resetn or posedge Clock)
    if (!Resetn)
      Q <= 0;
    else
      Q <= D;

endmodule
```

Flip-Flops with Clear

■ Synchronous Clear

```
module flipflop(D, Clock, Resetn, Q);
  input D, Clock, Resetn;
  output Q;
  reg Q;

  always @(posedge Clock)
    if (!Resetn) // check value of reset on clock edge
      Q <= 0;
    else
      Q <= D;

endmodule
```

4-Bit Binary Counter

■ Counter includes reset and enable

```
module upcount(Resetn, Clock, E, Q);
  input Resetn, Clock, E;
  output [3:0] Q;
  reg [3:0] Q;

  always @(negedge Resetn or posedge Clock)
    if (!Resetn)
      Q <= 0; // asynchronous reset overrides enable
    else if (E)
      Q <= Q + 1; // synthesizes adder circuit

endmodule
```


November 2, 2006

ECE 152A - Digital Design Principles

27

4-Bit Binary Counter

■ Functional Simulation

 


November 2, 2006

ECE 152A - Digital Design Principles

28

Finite State Machine (FSM) Design

 - Recall state diagram for JK flip-flop counter from previous lecture



November 2, 2006

ECE 152A - Digital Design Principles

29

Finite State Machine (FSM) Design

- The State Table

PS			NS		
A	B	C	A ⁺	B ⁺	C ⁺
0	0	0	1	0	0
0	0	1	X	X	X
0	1	0	0	1	1
0	1	1	0	0	0
1	0	0	1	1	1
1	0	1	X	X	X
1	1	0	X	X	X
1	1	1	0	1	0

November 2, 2006

ECE 152A - Digital Design Principles

30

Finite State Machine (FSM) Design

- Can't use addition operator because sequence is not binary count
 - See previous example
- Use parameter statement to define states

```
parameter [2:0] A = 3'b000, B = 3'b100, C = 3'b111,  
                D = 3'b010, E = 3'b011;
```

Finite State Machine (FSM) Design

- Use case statement to implement state transitions

```
always @ (posedge clock)  
case(count)  
  A: count <= B;  
  B: count <= C;  
  C: count <= D;  
  D: count <= E;  
  E: count <= A;  
  default: count <= A;  
endcase
```


Finite State Machine (FSM) Design

■ The complete module

```
module jk_counter(count, clock);  
  
    input clock;  
    output [2:0] count;  
  
    reg [2:0] count;  
    parameter [2:0] A = 3'b000, B = 3'b100, C = 3'b111,  
                  D = 3'b010, E = 3'b011;  
  
    always @ (posedge clock)  
    case(count)  
        A: count <= B;  
        B: count <= C;  
        C: count <= D;  
        D: count <= E;  
        E: count <= A;  
        default: count <= A;  
    endcase  
  
endmodule
```


November 2, 2006

ECE 152A - Digital Design Principles

33

Finite State Machine (FSM) Design

■ Functional Simulation

 

November 2, 2006

ECE 152A - Digital Design Principles

34