

Combinational Logic Building Blocks and Bus Structure

ECE 152A – Summer 2009

Reading Assignment

- Brown and Vranesic
 - 3 Implementation Technology
 - 3.8 Practical Aspects
 - 3.8.7 Passing 1s and 0s Through Transistor Switches
 - 3.8.8 Fan-In and Fan-Out in Logic Gates
 - Tri-State Buffers (only this section of 3.8.8)
 - 3.9 Transmission Gates
 - 3.9.2 Multiplexer Circuit

Reading Assignment

- Brown and Vranesic (cont)
 - 6 Combinational-Circuit Building Blocks
 - 6.1 Multiplexers
 - 6.1.1 Synthesis of Logic Functions Using Multiplexers
 - 6.1.2 Multiplexer Synthesis Using Shannon's Expansion
 - 6.2 Decoders
 - 6.2.1 Demultiplexers
 - 6.3 Encoders
 - 6.3.1 Binary Encoders
 - 6.3.2 Priority Encoders
 - 6.4 Code Converters

Reading Assignment

- Roth
 - 9 Multiplexers, Decoders and Programmable Logic
 - 9.1 Introduction
 - 9.2 Multiplexers
 - 9.3 Three State Buffers
 - 9.4 Decoders and Encoders

Multiplexer


- Passes one of several data inputs to output
 - Generally 2^n data inputs and always a single data output
 - n control lines determine which input is “steered” to the output
- Allows logical (not “tri-state” or electrical) implementation of buses
 - Buses and register transfer operations fundamental to digital system design

Multiplexer

- Also possible to implement arbitrary combinational logic with multiplexers
 - Universal, combinational logic element
- Also known as “Data Selector” and “Mux”
- In sequential operation, provides parallel to serial conversion

Two-to-One Multiplexer

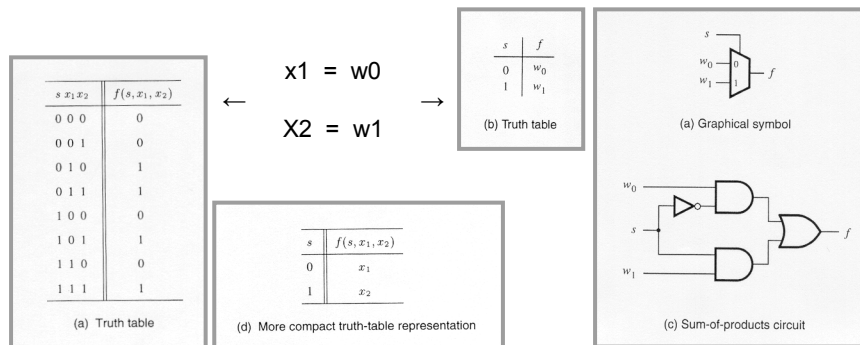■ $F = \text{Select}' \cdot x_0 + \text{Select} \cdot x_1$



August 24, 2009

ECE 152A - Digital Design Principles


7

Four-to-One Multiplexer

- i^{th} data input ANDed with minterm m_i
 - Embedded circuit generating minterms will become known as a decoder

$$f = \bar{s}_1 \bar{s}_0 w_0 + \bar{s}_1 s_0 w_1 + s_1 \bar{s}_0 w_2 + s_1 s_0 w_3$$

$m_0 w_0$ $m_1 w_1$ $m_2 w_2$ $m_3 w_3$

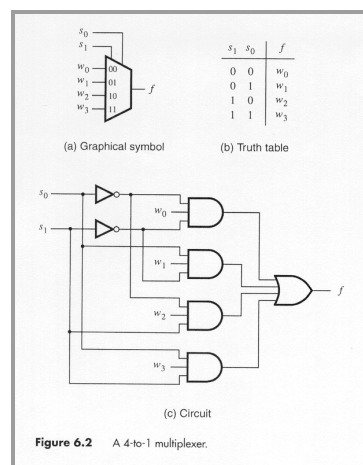


August 24, 2009

ECE 152A - Digital Design Principles

8

Building Larger Multiplexers

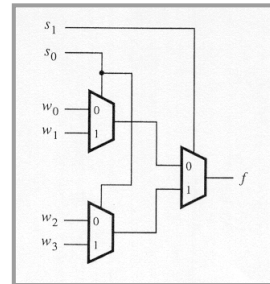- 4-to-1 (4:1) Mux using 2-to-1 (2:1) Muxes
 - Simple and modular
 - Adds 2 levels of gate (propagation) delay




August 24, 2009

ECE 152A - Digital Design Principles

9

Building Larger Multiplexers

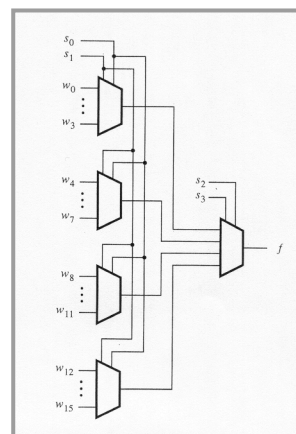- 16:1 Mux constructed from 4:1 Muxes
 - Expandable to 32:1 and 64:1 with additional 2:1 and/or 4:1 Muxes
 - With additional levels of propagation delay




August 24, 2009

ECE 152A - Digital Design Principles

10

Multiplexer Application

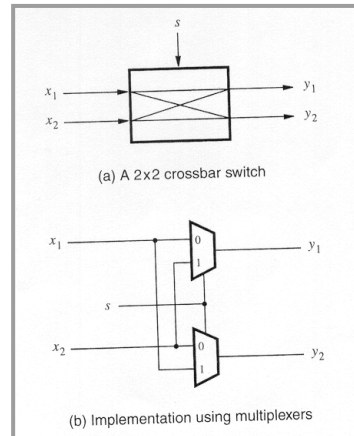- Crossbar Switch
 - In general, n-inputs by n-outputs
 - Connectivity is any input to any output
 - Important component of networking hardware
 - The bigger, the faster, the better...



August 24, 2009

ECE 152A - Digital Design Principles

11

Combinational Design Using Multiplexers

- Input variables applied to Mux select lines
 - “Steer” (constant) value of function to output
 - Allows implementation of n-variable function with 2^n -to-1 multiplexer
 - “Steer” derived function (a variable, its complement, the constant 1 or the constant 0) to the output
 - Allows implementation of n-variable function with 2^{n-1} -to-1 multiplexer

August 24, 2009




ECE 152A - Digital Design Principles

12

Combinational Design Using Multiplexers

■ Example 1: XOR Function

  
 
- Using a 4:1 Mux
- The modified Truth Table
 - Possibilities are $x, x', 0, 1$
- The 2-input XOR using a 2:1 Mux



Combinational Design Using Multiplexers

■ Example 2 : Three input majority function

  - Three input function with $(2^{n-1}$ -to-1) 4:1 Mux



Combinational Design Using Multiplexers

- Multiplexer Synthesis Using Shannon's Expansion
 - By adding gate level circuitry to Mux inputs, an arbitrary combinational function can be realized with a 2-to-1 Mux
 - Externally generating a function of one of the variables

Shannon's Expansion Theorem Any Boolean function $f(w_1, \dots, w_n)$ can be written in the form

$$f(w_1, w_2, \dots, w_n) = \bar{w}_1 \cdot f(0, w_2, \dots, w_n) + w_1 \cdot f(1, w_2, \dots, w_n)$$

Combinational Design Using Multiplexers

- Example 3 : Three input majority function with 2:1 Mux
 - Algebraic expansion

$$f(w_1, w_2, w_3) = (w_1 w_2 + w_1 w_3 + w_2 w_3)$$

$$f(w_1, w_2, w_3) = (w_1 w_2 + w_1 w_3 + w_2 w_3)(w_1' + w_1)$$

$$f = w_1'(w_1 w_2 + w_1 w_3 + w_2 w_3) + w_1(w_1 w_2 + w_1 w_3 + w_2 w_3)$$


... and from Shannon

$$f = w_1'(0w_2 + 0w_3 + w_2 w_3) + w_1(1w_2 + 1w_3 + w_2 w_3)$$

$$f = w_1'(w_2 w_3) + w_1(w_2 + w_3)$$

Combinational Design Using Multiplexers

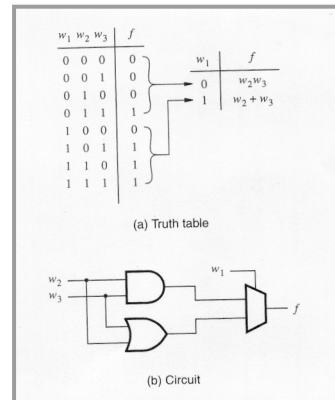- Example 3: Three input majority function with 2:1 Mux
 - Truth Table and circuit implementation



August 24, 2009

ECE 152A - Digital Design Principles

17

Combinational Design Using Multiplexers

- Shannon's Expansion with 4:1 Mux
 - Three input majority function
 - Expansion in terms of w_1 and w_2
 - Verifies earlier (heuristic) solution

$$f(w_1, w_2, w_3) = (w_1 w_2 + w_1 w_3 + w_2 w_3)$$

$$f = w_1' w_2' (00 + 0w_3 + 0w_3) + w_1' w_2 (01 + 0w_3 + 1w_3)$$

$$+ w_1 w_2' (10 + 1w_3 + 0w_3) + w_1 w_2 (11 + 1w_3 + 1w_3)$$

$$f = w_1' w_2' (0) + w_1' w_2 (w_3) + w_1 w_2' (w_3) + w_1 w_2 (1)$$

August 24, 2009

ECE 152A - Digital Design Principles

18

Multiplexers and Buses

- Bus allows data transfers between multiple sources and single or multiple destinations over a shared path (wires)
 - Bus includes multiple bits
 - Parallel data bus
 - Only one source on the bus at any time
 - Bus contention


August 24, 2009

ECE 152A - Digital Design Principles

19

Multiplexers and Buses

 - Example below illustrates two, four-bit words (X and Y) multiplexed onto the Z bus
 - Register transfer operations
 - $A' : Z \leftarrow X$, $A : Z \leftarrow Y$




August 24, 2009

ECE 152A - Digital Design Principles

20



Tri-State Outputs

 - Utilizes third, high impedance output state
 - In Hi-Z state, output appears as an open circuit to bus connection
 - Mux disconnects from bus logically, tri-state output device disconnects electrically




Tri-State Outputs (cont)

  - Flavors of tri-state outputs and control
- Bus implementation



NMOS and PMOS Transistors

 - Recall static CMOS circuits
 - Logic high output passed to output through PMOS transistor(s)
 - PMOS transistor passes “good” 1 and “bad” 0
 - Logic low output passed to output through NMOS transistor(s)
 - NMOS transistor passes “good” 0 and “bad” 1
 - “Good” 0s and 1s are GND and V_{DD}
 - “Bad” 0s and 1s have degraded DC voltage (logic) levels



August 24, 2009

ECE 152A - Digital Design Principles

23

NMOS and PMOS Transistors

- Degradation of DC signal levels is a result of the “threshold voltage” (V_T) of transistor and the “body effect”
 - To “turn on” the transistor, the gate to source voltage (V_{GS}) must exceed the transistor’s threshold voltage (V_T)
 - An NMOS transistor has a positive V_T
 - A PMOS transistor has a negative V_T
 - The threshold voltage itself is increased by the body effect by a factor of ~ 1.5


August 24, 2009

ECE 152A - Digital Design Principles

24

NMOS and PMOS Transistors

 - For the inverter below, assume the NMOS device has a V_T of 1V ($V_{GS} > 1V$) and the PMOS device has a V_T of -1V ($V_{GS} < -1V$) and $V_{DD} = 5V$




Input = 5V, $V_{GS}(T1) = 5V$ (off), $V_{GS}(T2) = 5V$ (on)
Output = 0V (GND)

Input = 0V, $V_{GS}(T1) = -5V$ (on), $V_{GS}(T2) = 0V$ (off),
Output = 5V (V_{DD})


NMOS and PMOS Transistors

 - Bad 1s (NMOS) and Bad 0s (PMOS)
 - $V_A = V_{DD} - V_T$ (NMOS)
 - Input going high; turns off at $V_{GS} = V_T$
 - $V_B = -V_T$ (PMOS)
 - Input going low; turns off at $V_{GS} = V_T$




CMOS AND Gate

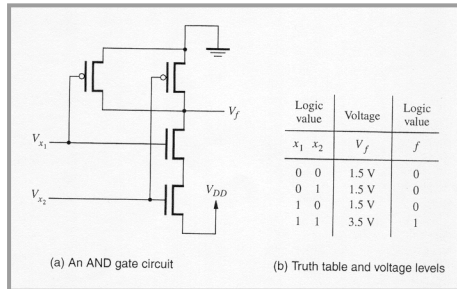- Note degradation in DC signal (logic) levels
 - AND Gates are never built this way in CMOS




The CMOS Transmission Gate

 - When enabled, the CMOS Transmission Gate:
 - Passes “good” 1s (through the PMOS transistor)
 - Passes “good” 0s (through the NMOS transistors)
- When disabled, the CMOS Transmission gate acts like a Tri-State Buffer



CMOS Transmission Gate MUX

 - 2:1 Multiplexer implementation with transmission gates




August 24, 2009

ECE 152A - Digital Design Principles

29

Decoders

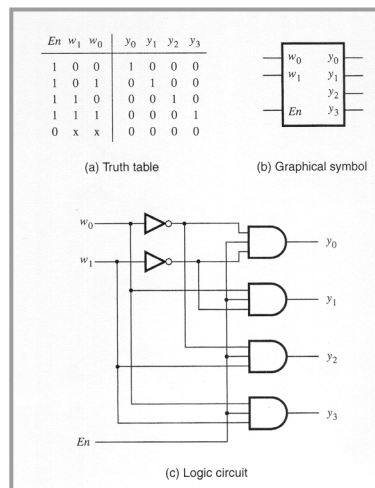- 2-to-4 Decoder shown
 - 2-to- 2^n in general
 - Enable input allows construction of decoder tree and demultiplexer
 - Generates all minterms when enabled
 - Multiple output circuits
 - One hot decoding




August 24, 2009

ECE 152A - Digital Design Principles

30

Decoder Tree

 - One-bit expansion (3-to-8) by adding external decoding circuitry




August 24, 2009

ECE 152A - Digital Design Principles

31

Decoder Tree

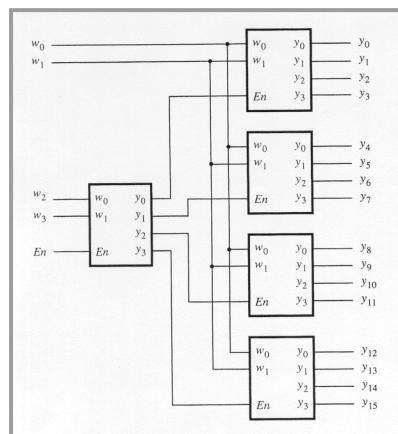- Two-bit expansion (4-to-16) by adding another 2-to-4 decoder




August 24, 2009

ECE 152A - Digital Design Principles

32

Decoder Applications

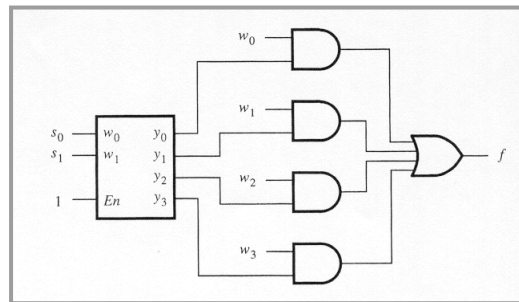- Multiplexer from decoder
 - Recall “embedded decoder”




August 24, 2009

ECE 152A - Digital Design Principles

33

Decoder Applications

 - Multiple Output Circuits
 - Full Adder using 3 X 8 Decoder



$$\begin{aligned} \text{Sum} &= m1 + m2 + m4 + m7 \\ &= x'y'z + x'yz' + xy'z' + xyz \end{aligned}$$

$$\begin{aligned} \text{Carry} &= m3 + m5 + m6 + m7 \\ &= x'yz + xy'z + xyz' + xyz \end{aligned}$$


August 24, 2009

ECE 152A - Digital Design Principles

34

Decoder Applications

■ Decoder Bus Control/Multiplexer

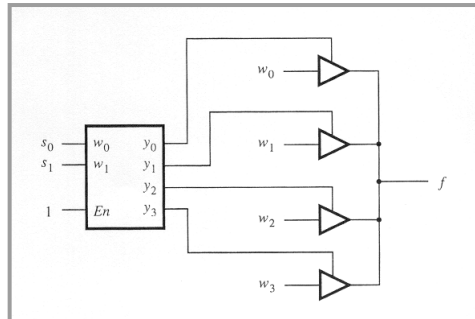



Demultiplexers

- Serial to parallel conversion
 - Send a single data bit to a specific address
- A 1-to- 2^n demultiplexer is implemented using an n -to- 2^n decoder
 - The (value of) the data is applied via the enable input
- Valuable circuit in sequential circuits
 - Not so much in combinational circuits
- Also referred to as Dmux's

Encoders

Binary Encoders

  
- “One hot” input, binary (or other code) representation output
 - Reverse of decoder



Encoders


Priority Encoders

 - Used in prioritizing interrupts (or other events)



Code Converters

 ■ BCD to 7-Segment Display Code Converter



w_3	w_2	w_1	w_0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1

(c) Truth table