

# Latches, the D Flip-Flop & Counter Design

ECE 152A – Summer 2009

## Reading Assignment

- Brown and Vranesic
  - 7 Flip-Flops, Registers, Counters and a Simple Processor
    - 7.1 Basic Latch
    - 7.2 Gated SR Latch
      - 7.2.1 Gated SR Latch with NAND Gates
    - 7.3 Gated D Latch
      - 7.3.1 Effects of Propagation Delays

## Reading Assignment

- Brown and Vranesic (cont)
  - 7 Flip-Flops, Registers, Counters and a Simple Processor (cont)
    - 7.4 Master-Slave and Edge-Triggered D Flip-Flops
      - 7.4.1 Master-Slave D Flip-Flop
      - 7.4.2 Edge-Triggered D Flip-Flop
      - 7.4.3 D Flip-Flop with Clear and Preset
      - 7.4.4 Flip-Flop Timing Parameters (2<sup>nd</sup> edition)

## Reading Assignment

- Roth
  - 11 Latches and Flip-Flops
    - 11.1 Introduction
    - 11.2 Set-Reset Latch
    - 11.3 Gated D Latch
    - 11.4 Edge-Triggered D Flip-Flop

## Reading Assignment


- **Roth (cont)**
  - 12 Registers and Counters
    - 12.1 Registers and Register Transfers
    - 12.2 Shift Registers
    - 12.3 Design of Binary Counters
    - 12.4 Counters for Other Sequences

## Combinational vs. Sequential Logic

- **Combinational logic**
  - Function of present inputs only
    - Output is known if inputs (some or all) are known
- **Sequential logic**
  - Function of past and present inputs
    - Memory or “state”
    - Output known if present input and present state are known
      - Initial conditions often unknown (or undefined)
 
# Gate Delays

- Recall from earlier lecture
  - When gate inputs change, outputs don't change instantaneously




July 20, 2009

ECE 152A - Digital Design Principles

7
 
# Feedback

- Outputs connected to inputs
  - Single inverter feedback
    - If propagation delay is long enough, output will oscillate




July 20, 2009

ECE 152A - Digital Design Principles

8


 
# Feedback

- If the propagation delay is not long enough, the output will settle somewhere in the middle
  - $V_{in} = V_{out}$



  
# Feedback

- Ring Oscillator
  - Any odd number of inverters will oscillate
    - $\frac{1}{2}$  period = total prop delay of chain



 
## Feedback

- What about an even number of inversions?
  - Two inverter feedback
    - Memory (or State)
    - Static 1 or 0 “stored” in memory




## The Latch

- Replace inverters with NOR gates

 
 
## The Set-Reset (SR) Latch

- NOR implementation
  - Inverted feedback



July 20, 2009

ECE 152A - Digital Design Principles

13

## The SR Latch

- R = Reset (clear)
  - $Q \rightarrow 0, Q^* \rightarrow 1$
- S = Set (preset)
  - $Q \rightarrow 1, Q^* \rightarrow 0$
- NOR gate implementation
  - Either input = 1 forces an output to 0

July 20, 2009

ECE 152A - Digital Design Principles

14

## The SR Latch (cont)

- Terminology
  - Present state, Q
    - Current value of Q and Q\*
  - Next state, Q<sup>+</sup>
    - Final value of Q and Q\* after input changes

## The SR Latch (cont)


- Operation
  - S=1, R=0 : set to 1, Q<sup>+</sup> = 1
  - S=0, R=1 : reset to 0, Q<sup>+</sup> = 0
  - S=0, R=0 : hold state, Q<sup>+</sup> = Q
  - S=1, R=1 : not allowed
    - Q<sup>+</sup> = Q<sup>\*\*</sup> = 0, lose state


 
## The SR Latch (cont)

- Timing Diagram

- RS inputs are “pulses”
  - Temporarily high, but normally low



July 20, 2009

ECE 152A - Digital Design Principles

17


## The SR Latch (cont)

- Characteristic Equation

- Algebraic expression of flip-flop behavior
- Plot characteristic table on map, find  $Q^+$ 
  - $Q^+ = S + R'Q$  ( $S = R = 1$  not allowed)

S(t)	R(t)	Q(t)	Q(t + Δ)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	—
1	1	1	—

— inputs not allowed

 

July 20, 2009

ECE 152A - Digital Design Principles

18

## The SR Latch (cont)

### ■ Characteristic Equation

- $Q^+ = S + R'Q$  ( $S = R = 1$  not allowed)
  - Q becomes 1 when  $S = 1, R = 0$
  - Stays Q when  $S = R = 0$
  - Q becomes 0 when  $S = 0, R = 1$


## The SR Latch (cont)

### ■ State Table

PS (Q)	NS (Q <sup>+</sup> )			
	SR=00	01	10	11
0	0	0	1	X
1	1	0	1	X

## The SR Latch (cont)

### ■ State Diagram

 

July 20, 2009


ECE 152A - Digital Design Principles

21

## The SR Latch with NANDS
 
### ■ NAND Based S'R' Latch

- S' = R' = 0 not allowed
- Either input = 0 forces output to 1




July 20, 2009

ECE 152A - Digital Design Principles

22

 
## The Gated SR Latch

- Also known as “transparent” latch
  - Output follows input (transparent) when enabled




## The Gated SR Latch (cont)

- Timing Diagram

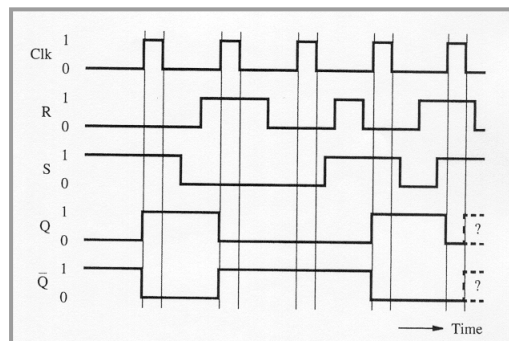


## The Gated SR Latch (cont)

- NAND Implementation

 

 
## The Gated Data (D) Latch

- NAND Implementation of transparent D latch



# The Gated D Latch


## ■ Timing Diagram

 

# The Edge Triggered D Flip-Flop

 
## ■ The D Flip-Flop

- Input D, latched and passed to Q on clock edge
- Rising edge triggered or falling edge triggered
  - Characteristic table and function


 
## The Edge Triggered D Flip-Flop

- Most commonly used flip-flop
- Output follows input after clock edge
  - Q and Q\* change only on clock edge
  - Timing diagram for negative edge triggered flip-flop



July 20, 2009

ECE 152A - Digital Design Principles

29

## The D Flip-Flop

- State Table

PS (Q)	NS (Q <sup>+</sup> )	
	D = 0	D = 1
0	0	1
1	0	1


July 20, 2009

ECE 152A - Digital Design Principles

30

## The D Flip-Flop (cont)

### ■ State Diagram

 


July 20, 2009

ECE 152A - Digital Design Principles

31
 
## The Master-Slave D Flip-Flop

- Construct edge triggered flip-flop from 2 transparent latches
  - Many other topologies for edge triggered flip-flops
  - Falling edge triggered (below)



July 20, 2009


ECE 152A - Digital Design Principles

32


 
## The Master-Slave D Flip-Flop (cont)

- Timing Diagram
  - Falling edge triggered




July 20, 2009

ECE 152A - Digital Design Principles

33
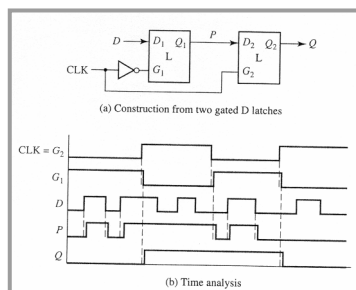
## The Master-Slave D Flip-Flop (cont)

- A Second Timing Diagram
  - Rising edge triggered




July 20, 2009

ECE 152A - Digital Design Principles

34

 
# The Edge Triggered D Flip-Flop

- “True” Edge Triggered D Flip-Flop
  - Never transparent (unlike Master Slave)




# The Edge Triggered D Flip-Flop

- Operation of Flip-Flop

 

# Types of D Flip-Flops

- Gated, Positive Edge and Negative Edge

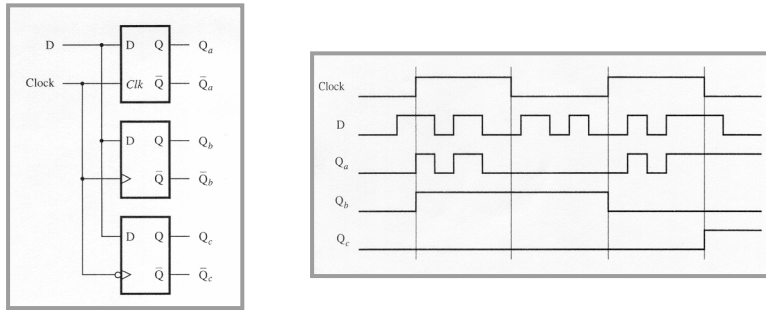


July 20, 2009

ECE 152A - Digital Design Principles

37
 
# Timing Parameters

- CLK → Q
  - Delay from clock edge (CLK) to valid (Q, Q\*) output
- Setup time  $t_{su}$ 
  - Stable, valid data (D) before clock edge (CLK)
- Hold time  $t_{hold}$ 
  - Stable, valid data (D) after clock edge (CLK)





July 20, 2009

ECE 152A - Digital Design Principles

38
  
## Maximum Frequency

- Maximum frequency (minimum clock period) for a digital system
  - $\text{CLK} \rightarrow \text{Q} + \text{propagation delay} + t_{su}$




## Counter Design with D Flip-Flops

- Design Example #1: Modulo 3 counter
  - $00 \rightarrow 01 \rightarrow 10 \downarrow$   
 $\uparrow \leftarrow \leftarrow \leftarrow \leftarrow \leftarrow$
- Requires 2 flip-flops
  - One for each "state variable"

# Counter Design with D Flip-Flops

## ■ State Diagram

 

July 20, 2009

ECE 152A - Digital Design Principles

41

# Counter Design with D Flip-Flops

## ■ State Table

PS		NS	
A	B	A <sup>+</sup>	B <sup>+</sup>
0	0	0	1
0	1	1	0
1	0	0	0
1	1	X	X

July 20, 2009

ECE 152A - Digital Design Principles

42

## Counter Design with D Flip-Flops

### ■ Next State Maps

	B	0	1
A	0	0	1
1	0	0	X

$$A^+ = B$$

	B	0	1
A	0	1	0
1	0	0	X


$$B^+ = A'B'$$

## Counter Design with D Flip-Flops

- Implementation with D Flip-Flops
- What are the D inputs to flip-flops A and B?
  - Recall characteristic equation for D flip-flop
    - $Q^+ = D$
    - Therefore,  $A^+ = B \rightarrow D_A = B$
    - and...  $B^+ = A'B' \rightarrow D_B = A'B'$
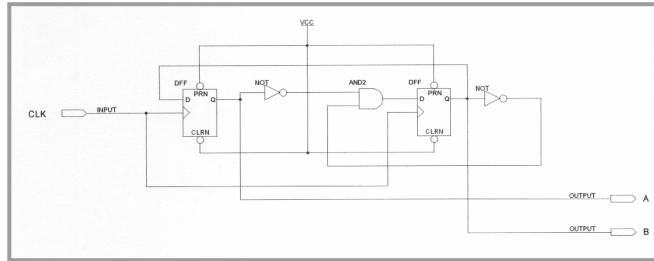
# Counter Design with D Flip-Flops

- Implementation with positive edge triggered flip-flops




July 20, 2009

ECE 152A - Digital Design Principles

45
 
# Counter Design with D Flip-Flops

- Implementation with positive edge triggered flip-flops
  - Timing diagram



July 20, 2009

ECE 152A - Digital Design Principles

46

## Counter Design with D Flip-Flops

- Design Example #2:
  - Modulo 3 counter with up/down\* input
    - Counter counts up with input = 1 and down with input = 0
  - Implement with D flip-flops


July 20, 2009

ECE 152A - Digital Design Principles

47

## Counter Design with D Flip-Flops

- State diagram

 

July 20, 2009

ECE 152A - Digital Design Principles

48



# Counter Design with D Flip-Flops

## ■ State table

U	A	B	A <sup>+</sup>	B <sup>+</sup>
0	0	0	1	0
0	0	1	0	0
0	1	0	0	1
0	1	1	X	X
1	0	0	0	1
1	0	1	1	0
1	1	0	0	0
1	1	1	X	X

# Counter Design with D Flip-Flops

## ■ Next state maps and flip-flop inputs

U \ AB	00	01	11	10
0	1		X	
1		1	X	

$$A^+ = D_A = UB + U'A'B'$$

U \ AB	00	01	11	10
0			X	1
1	1		X	

$$B^+ = D_B = U'A + UA'B'$$