

University of California, Santa Barbara
Department of Electrical and Computer Engineering

ECE 152A – Digital Design Principles

Homework #1
Solution

Problem #1:

Demonstrate by means of truth tables the validity of the following identities:

1. DeMorgan's theorem for three variables: $(xyz)' = x' + y' + z'$

x	y	z	xyz	$(xyz)'$	x'	y'	z'	$x' + y' + z'$
0	0	0	0	1	1	1	1	1
0	0	1	0	1	1	1	0	1
0	1	0	0	1	1	0	1	1
0	1	1	0	1	1	0	0	1
1	0	0	0	1	0	1	1	1
1	0	1	0	1	0	1	0	1
1	1	0	0	1	0	0	1	1
1	1	1	1	0	0	0	0	0

2. The second distributive law: $x + yz = (x + y)(x + z)$

x	y	z	yz	$x + yz$	$(x + y)$	$(x + z)$	$(x + y)(x + z)$
0	0	0	0	0	0	0	0
0	0	1	0	0	0	1	0
0	1	0	0	0	1	0	0
0	1	1	1	1	1	1	1
1	0	0	0	1	1	1	1
1	0	1	0	1	1	1	1
1	1	0	0	1	1	1	1
1	1	1	1	1	1	1	1

3. The consensus theorem: $xy + x'z + yz = xy + x'z$

<u>x</u>	<u>y</u>	<u>z</u>	<u>xy</u>	<u>x'z</u>	<u>yz</u>	<u>xy + x'z + yz</u>	<u>xy + x'z</u>
0	0	0	0	0	0	0	0
0	0	1	0	1	0	1	1
0	1	0	0	0	0	0	0
0	1	1	0	1	1	1	1
1	0	0	0	0	0	0	0
1	0	1	0	0	0	0	0
1	1	0	1	0	0	1	1
1	1	1	1	0	1	1	1

Problem #2:

Simplify the following Boolean expressions to a minimum number of literals:

1. $x'y' + xy + x'y$

$$x'(y' + y) + xy$$

$$x' + xy$$

$$(x' + x)(x' + y)$$

$$= \mathbf{x' + y}$$

2. $(x + y)(x + y')$

$$(x + y)$$

$$\underline{(x + y') \{ \text{multiply out} \}}$$

$$xx + xy + xy' + yy'$$

$$x + xy + xy'$$

$$= \mathbf{x}$$

$$3. x'y + xy' + xy + x'y'$$

$$(x' + x)y + (x' + x)y'$$

$$y + y'$$

$$= \mathbf{1}$$

$$4. x' + xy + xz' + xy'z'$$

$$x' + xy + xz'$$

$$x' + x(y + z')$$

$$= \mathbf{x' + y + z'}$$
 { by $A + A'B = A + B$ }

$$5. xy' + y'z' + x'z'$$

$$= \mathbf{xy' + x'z'}$$
 { by consensus theorem }

Problem #3:

Simplify the following Boolean expressions to a minimum number of literals:

$$1. ABC + A'B + ABC'$$

$$AB(C + C') + A'B$$

$$AB + A'B$$

$$(A + A')B$$

$$= \mathbf{B}$$

$$2. x'yz + xz$$

$$z(x'y + x)$$

$$= \mathbf{z(y + x)}$$

$$3. (x + y)'(x' + y')$$

$$x'y'(x' + y')$$

$$x'y'x' + x'y'y'$$

$$= x'y'$$

$$4. xy + x(wz + wz')$$

$$xy + x(w(z + z'))$$

$$xy + xw$$

$$= x(y + w)$$

$$5. (BC' + A'D)(AB' + CD')$$

$$\underline{(AB' + CD')} \text{ \{ multiply out \}}$$

$$A(BB')C' + (AA')B'D + B(CC')D' + A'C(DD')$$

$$= 0$$

Problem #4:

Reduce the following Boolean expressions to the indicated number of literals:

$$1. A'C' + ABC + AC' \quad \text{to three literals}$$

$$C'(A' + A) + ABC$$

$$C' + ABC$$

$$= AB + C'$$

$$2. (x'y' + z)' + z + xy + wz \quad \text{to three literals}$$

$$(x + y)z' + z + xy \quad \{z + wz = z\}$$

$$(x + y) + z + xy \quad \{z + z'() = z + ()\}$$

$$= x + y + z$$

$$3. A'B(D' + C'D) + B(A + A'CD) \quad \text{to one literal}$$

$$A'BD' + A'BC'D + AB + A'BCD$$

$$A'BD(C + C') + A'BD' + AB$$

$$A'B(D + D') + AB$$

$$A'B + AB$$

$$= B$$

$$4. (A' + C)(A' + C')(A + B + C'D) \quad \text{to four (or fewer?) literals}$$

$$\underline{A' + C'} \quad \{ \text{multiply out} \}$$

$$(A'A' + A'C + A'C' + CC')(A + B + C'D)$$

$$A'(A + B + C'D)$$

$$= A'(B + C'D)$$

Problem #5:

Find the complement of $F = x + yz$; then show that $F(F') = 0$ and $F + F' = 1$;

$$F' = (x + yz)' = (x')(y' + z') = x'y' + x'z'$$

$$F(F') = 0 =$$

$$(x + yz)(x'y' + x'z')$$

$$xx'y' + xx'z' + x'yy'z + x'yyz'$$

$$= 0$$

$$F + F' = 1 =$$

$$x + yz + x'y' + x'z'$$

$$x + yz + y' + x'z'$$

$$x + yz + y' + z'$$

$$x + y' + y + z'$$

$$= 1$$

Problem #6:

Find the complement of the following expressions:

$$1. F = xy' + x'y$$

$$F' = (x' + y) (x + y') = xy + x'y'$$

$$2. F = (AB' + C)D' + E$$

$$= AB'D' + CD' + E$$

$$F' = (A' + B + D) (C' + D) E'$$

$$3. F = AB(C'D + CD') + A'B'(C' + D)(C + D')$$

$$ABC'D + ABCD' + A'B(CD + C'D')$$

$$= ABC'D + ABCD' + A'BCD + A'BC'D'$$

$$F' = (A' + B' + C + D') (A' + B' + C' + D) \\ (A + B' + C' + D') (A + B' + C + D)$$

$$4. (x + y' + z)(x' + z')(x + y)$$

$$= x'yz' + xz + x'y'$$

Problem #7:


Given the following Boolean function:

$$F = xy'z + x'y'z + w'xy + wx'y + wxy$$

1. Obtain the truth table for the function

	<u>w</u>	<u>x</u>	<u>y</u>	<u>z</u>	<u>xy'z</u>	<u>x'y'z</u>	<u>w'xy</u>	<u>wx'y</u>	<u>wxy</u>	<u>F=y'z+yw+xy</u>
0	0	0	0	0	0	0	0	0	0	0
1	0	0	0	1	0	1	0	0	0	1
2	0	0	1	0	0	0	0	0	0	0
3	0	0	1	1	0	0	0	0	0	0
4	0	1	0	0	0	0	0	0	0	0
5	0	1	0	1	1	0	0	0	0	1
6	0	1	1	0	0	0	1	0	0	1
7	0	1	1	1	0	0	1	0	0	1
8	1	0	0	0	0	0	0	0	0	0
9	1	0	0	1	0	1	0	0	0	1
10	1	0	1	0	0	0	0	1	0	1
11	1	0	1	1	0	0	0	1	0	1
12	1	1	0	0	0	0	0	0	0	0
13	1	1	0	1	1	0	0	0	0	1
14	1	1	1	0	0	0	0	0	1	1
15	1	1	1	1	0	0	0	0	1	1

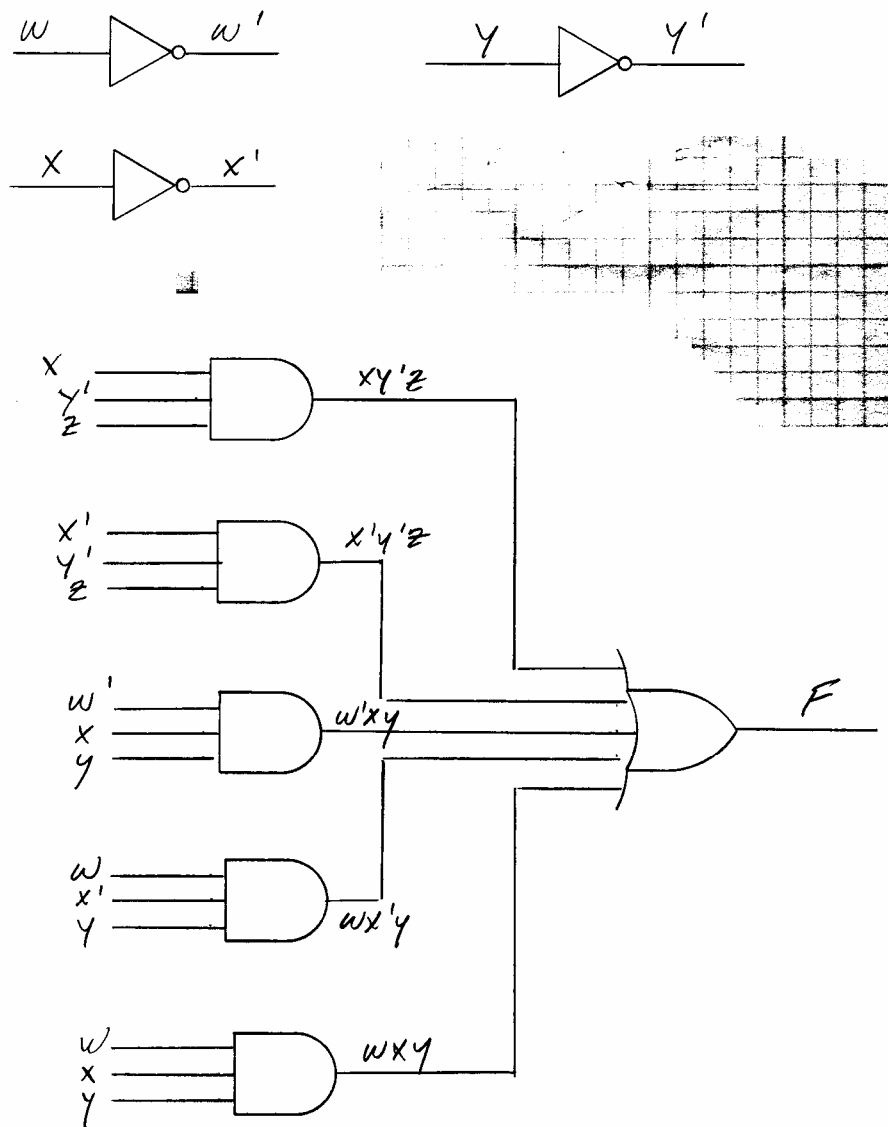2. Draw the logic diagram using the original Boolean expression



3. Simplify the function to a minimum number of literals using Boolean algebra

$$xy'z + x'y'z + w'xy + wx'y + wxy$$

$$(x + x') y'z + (w' + w) xy + wx'y$$

$$y'z + xy + wx'y$$


$$y'z + y(x + x'w)$$

$$= y'z + y(x + w)$$

4. Obtain the truth table of the function from the simplified expression and show that it is the same as the one in part 1

See truth table above

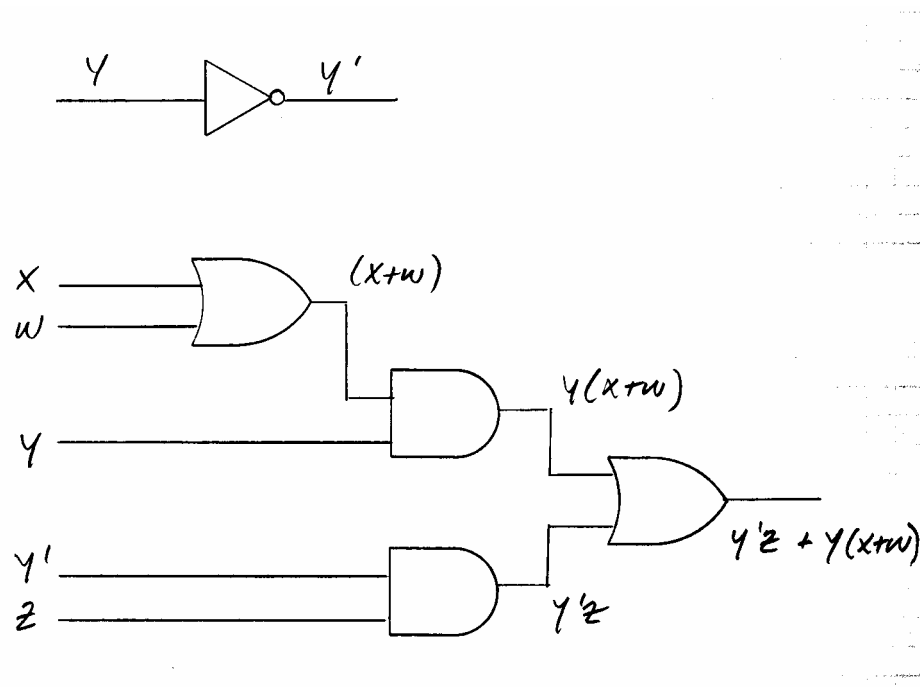5. Draw the logic diagram from the simplified expression and compare the total number of gates with the diagram of part 2



Problem #8:

Convert the following expressions into sum of products and product of sums:

$$1. (AB + C)(B + C'D)$$

$$= AB + BC \quad (SOP)$$

$$= B(A + C) \quad (POS)$$


$$2. x' + x(x + y')(y + z')$$

$$= x' + y + z' \quad (SOP)$$

$$= x' + y + z' \quad (POS)$$

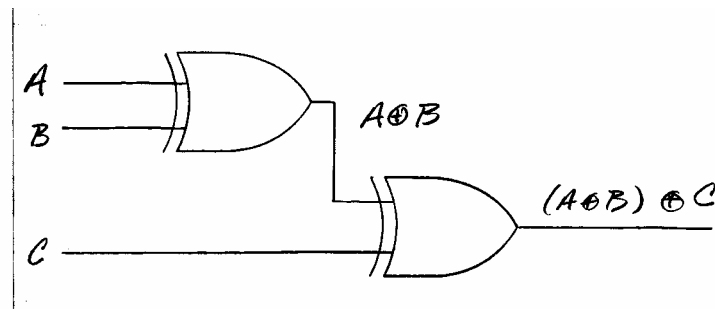Problem #9:

A 3-input exclusive OR gate can be constructed from 2, 2-input gates as shown below:



1. Generate the truth table for the 3 input XOR gate

A	B	C	$A \oplus B$	$\oplus C$
0	0	0	0	0
0	0	1	0	1
0	1	0	1	1
0	1	1	1	0
1	0	0	1	1
1	0	1	1	0
1	1	0	0	0
1	1	1	0	1

2. Generate the Boolean expression for the 3 input XOR gate

$$\mathbf{A \oplus B \oplus C = A'B'C + A'BC' + AB'C' + ABC}$$

Problem #10:

Show (using Boolean algebra) that the dual of the 2-input exclusive-OR function is equal to its complement.

$$\text{XOR} = x'y + xy'$$

$$\begin{aligned} \text{Dual (XOR)} &= (x' + y)(x + y') = x'x + x'y' + xy + yy' \\ &= \mathbf{xy + x'y'} \end{aligned}$$

$$\begin{aligned} \text{Complement (XOR)} &= (x'y + xy')' = (x + y')(x' + y) \\ &= x'x + x'y' + xy + yy' \\ &= \mathbf{xy + x'y'} \end{aligned}$$

Problem #11:

1) $(xy+z)(y+xz)$

$$\begin{array}{r} (xy+z) \\ (y+xz) \\ \hline \end{array}$$

$$xyy + yz + xxy + xzz$$

$$xy + yz + x\cancel{y}z + xz$$

$$= xy + yz + x'yz + xy'z$$

$$= m_7 + m_6 + m_3 + m_5$$

x	y	z	$(xy+z)(y+xz)$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Problem #11 (cont):

$$= \sum m(3, 5, 6, 7)$$

$$= \prod M(0, 1, 2, 4)$$

$$1.2) \quad (A' + B)(B' + C)$$

$$A' + B$$

$$B' + C$$

$$A'B' + \cancel{B'B'} + A'C + BC$$

EXPAND ALGEBRAICALLY:

$$A'B'C + A'B'C' + A'BC + ABC$$

$$= m_1 + m_0 + m_3 + m_7$$


A	B	C	$(A'+B)(B'+C)$
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

Problem #11 (cont):

$$= \sum m(0, 1, 3, 7)$$

$$= \prod M(2, 4, 5, 6)$$
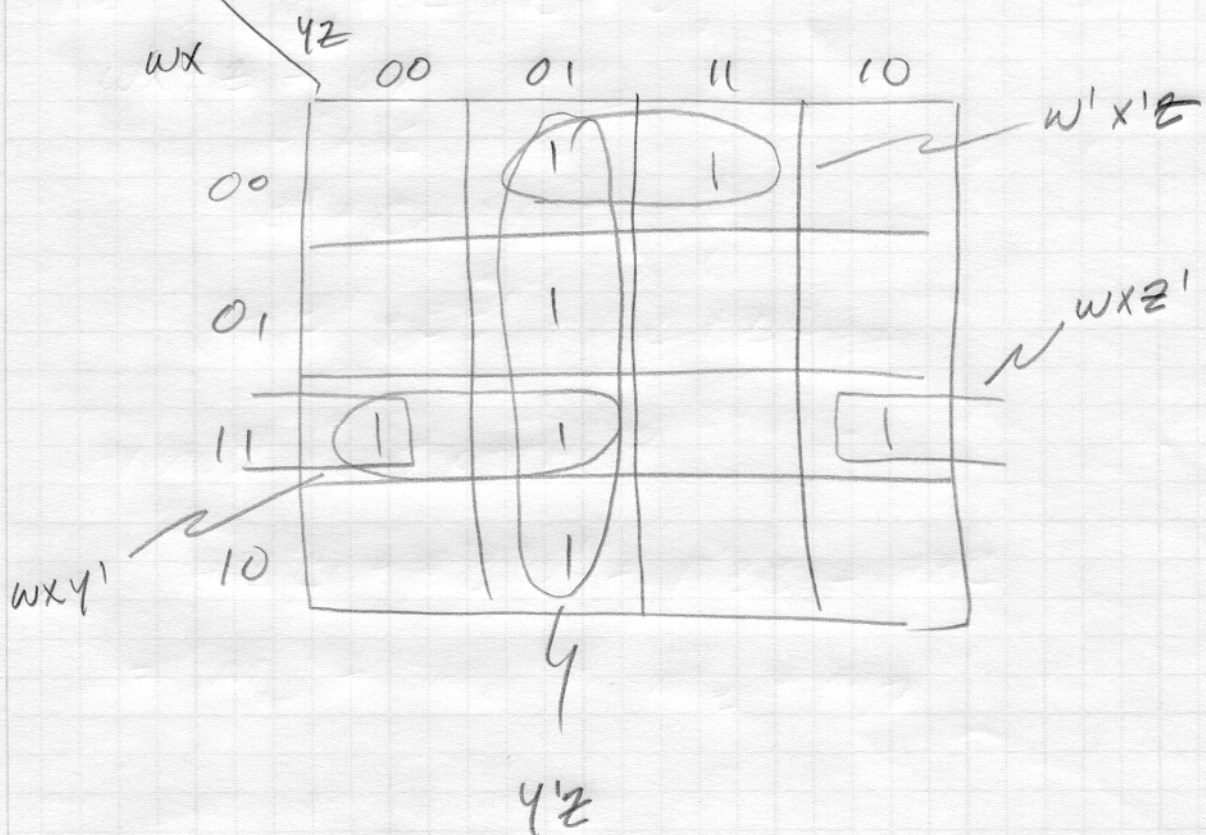
$$(1.3) \quad y'z + wx y' + wx z' + w'x'z$$



$$= \sum m(1, 3, 5, 9, 12, 13, 14)$$

$$= \prod M(0, 2, 4, 6, 7, 8, 10, 11, 15)$$

Problem #12:

2.1) MINTERMS: m_2, m_3, m_6, m_7
 $(x'yz', x'yz, xyz', xyz)$

2.2) MINTERMS OF F'
 m_0, m_1, m_4, m_5
 $(x'y'z', x'y'z, xy'z', xy'z)$

2.3) SUM OF MINTERMS:
 $= \sum m(2, 3, 6, 7)$

2.4) SIMPLIFY FUNCTION
 $= x'yz' + x'yz + xyz' + xyz$
 $= y(x'z' + x'z + xz' + xz)$
 $= y(x'(z'/z) + x(z'/z))$
 $= y(x' + x)$
 $= \underline{\underline{y}}$

Problem #13:

1) $B'D + A'D + BD$

AB \ CD	00	01	11	10
00		1	1	
01		1	1	
11		1	1	
10		1	1	

$= D$
 $= \sum m(1, 3, 5, 7, 9, 11, 13, 15)$
 $= \prod M(0, 2, 4, 6, 8, 10, 12, 14)$

Problem #13 (cont):

2) $(xy+z)(xz+y)$

$xy+z$
 $xz+y$

$xyx + xz + xy + yz$

$x \begin{array}{c} yz \\ 00 \quad 01 \quad 11 \quad 10 \\ 0 \\ 1 \end{array}$


	00	01	11	10	
0			1	1	yz
1		1	1	1	xy

$\sum xz$

$= \sum m(3, 5, 6, 7)$

$= \prod M(0, 1, 2, 4)$

Problem #14:

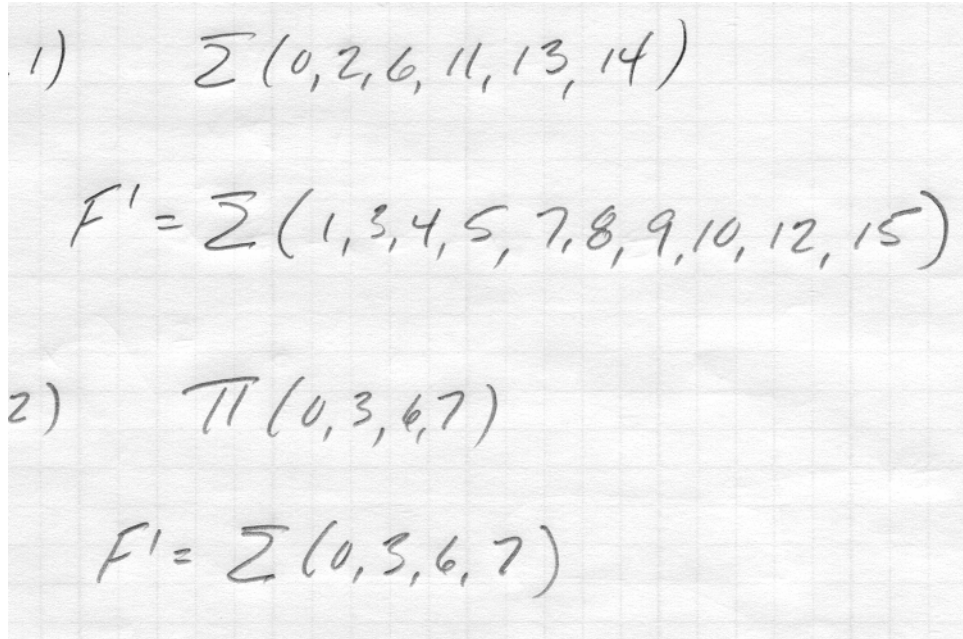

1) $\Sigma(0, 2, 6, 11, 13, 14)$

$F' = \Sigma(1, 3, 4, 5, 7, 8, 9, 10, 12, 15)$

2) $\Pi(0, 3, 6, 7)$

$F' = \Sigma(0, 3, 6, 7)$

Problem #15:

1) $\Sigma(0,1,5,7)$

x \ yz	00	01	11	10
0	1	1		
1		1	1	

$= x'y' + xz$

Problem #15 (cont):

2) $\Sigma(1, 2, 3, 6, 7)$

x \ yz	00	01	11	10
0		1	1	1
1			1	1

$= y + x'z$

3) $\Sigma(3, 5, 6, 7)$

x \ yz	00	01	11	10
0			1	
1		1	1	1

$= xz + yz + xy$

Problem #15 (cont):

(5.4)

$\Sigma(0, 2, 3, 4, 6)$

A \ BC	00	01	11	10
0	1		1	1
1	1			1

$\underline{= C' + A'B}$

Problem #16:

(6.1) $xy + x'y'z' + x'yz'$

x \ yz	00	01	11	10
0	1			1
1			1	1

$\underline{= x'z' + xy}$

Problem #16 (cont):

2) $X'Y' + YZ + X'YZ'$

X \ YZ	00	01	11	10
0	1	1	1	1
1			1	

$= X' + YZ$

3) $A'B + BC' + B'C'$

A \ BC	00	01	11	10
0	1		1	1
1	1			1

$= C' + A'B$

Problem #17:

$$(7.1) \quad F(A, B, C, D) = \sum (4, 6, 7, 15)$$

$AB \setminus CD$	00	01	11	10
00				
01	1		1	1
11			1	
10				


$$= \underline{A'B'D' + BCD}$$

$$(7.2) \quad F(w, x, y, z) = \sum (2, 3, 12, 13, 14, 15)$$

$wx \setminus yz$	00	01	11	10
00			1	1
01				
11	1	1	1	1
10				

$$= \underline{wx + w'x'y}$$

Problem #17 (cont):

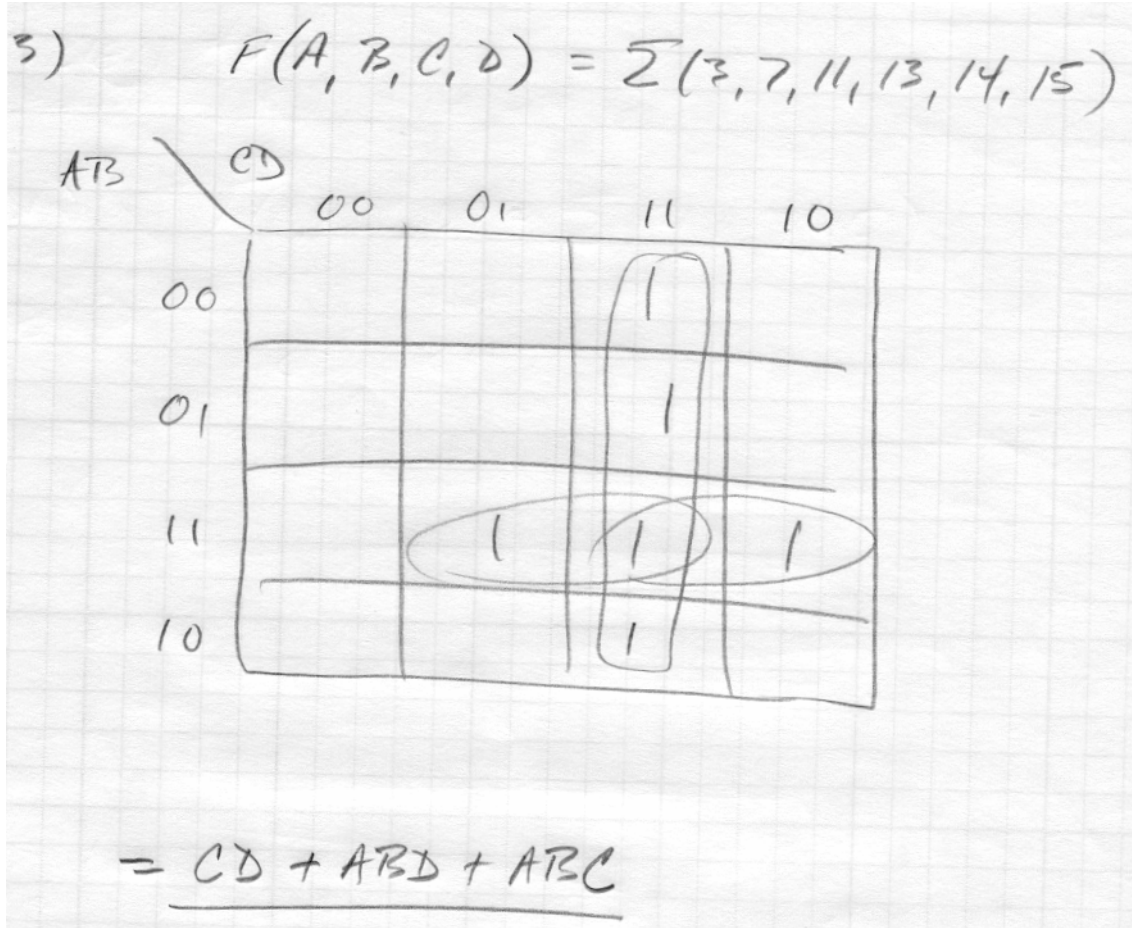

Problem #18:

1) $F(w, x, y, z) = \sum (1, 4, 5, 6, 12, 14, 15)$

wx \ yz	00	01	11	10
00		1		
01	1	1		1
11	1		1	1
10				

$= \underline{xz' + w'y'z + wxy}$

Problem #18 (cont):

2) $F(A, B, C, D) = \sum(0, 1, 2, 4, 5, 7, 11, 15)$

AB \ CD	00	01	11	10
00	1	1		1
01	1	1	1	
11			1	
10			1	

$= \underline{A'C' + AB'D' + A'BD + ACD}$

3) $F(W, X, Y, Z) = \sum(2, 3, 10, 11, 12, 13, 14, 15)$

WX \ YZ	00	01	11	10
00			1	1
01				
11	1	1	1	1
10			1	1

$= \underline{WX + X'Y}$

Problem #18 (cont):

8, 4) $F(A, B, C, D) = \sum(0, 2, 4, 5, 6, 7, 8, 10, 13, 15)$

AB \ CD	00	01	11	10
00	1			1
01	1	1	1	1
11		1	1	
10				1

$= \underline{B'D' + A'B + BD}$

Problem #19:

1) $w'z + xz + x'y + wx'z$

wx \ yz	00	01	11	10
00		1	1	1
01		1	1	
11		1	1	
10		1	1	1

$= z + x'y$

Problem #19 (cont):

2) $B'D + A'BC' + AB'C + ABC'$

	00	01	11	10
00		1	1	
01	1	1		
11	1	1		
10		1	1	1

$= \underline{BC' + B'D + AB'C}$

3) $AB'C + B'C'D' + BCD + ACD' + A'BC' + A'BC'D$

AB \ CD	00	01	11	10
00	1		1	1
01		1	1	
11			1	1
10	1		1	1

$= B'D' + AC + B'C + A'BD \rightarrow$

Problem #19 (cont):

3 (CONT)

OK: $B'D' + AC + CD + A'BD$

4) $wxy + yz + xy'z + x'y$

		yz			
	wx	00	01	11	10
00				1	1
01			1	1	
11			1	1	1
10				1	1

$= xz + wy + x'y$

Problem #20:

10.1) $xy + yz + xy'z$

$x \backslash yz$	00	01	11	10
0			1	
1		1	1	1

$= \sum (3, 5, 6, 7)$

2) $C'D + ABC' + ABD' + A'B'D$

$AB \backslash CD$	00	01	11	10
00		1	1	
01		1		
11	1	1		1
10		1		

$= \sum (1, 3, 5, 9, 12, 13, 14)$

Problem #20 (cont):

10.3) $wxy + x'z' + w'xz$

wx \ yz	00	01	11	10
00	1			1
01		1	1	
11			1	1
10	1			1

$= \sum (0, 2, 5, 7, 8, 10, 14, 15)$