 


Blocking vs non-blocking (procedural) assignments:

1

Example 1: 2-bit shift register:



Behavior:

```
module SR (D, CLK, Q);
```

```
  input D, CLK;
```

```
  output [1:0] Q;
```

```
  reg [1:0] Q;
```

```
  always @ (posedge CLK)
```

```
  begin
```

```
    Q[0] <= D;
```

```
    Q[1] <= Q[0];
```

```
  end
```

```
endmodule
```

- ① Nonblocking assignments
- ② Synchronized to positive edge of CLK


[a 2-bit SR will correctly be synthesized from this code.]

— What would be ^{synthesized} if we wrote instead blocking assignments?


```

always @ (posedge CLK)
begin
    Q[0] = D;
    Q[1] = Q[0];
end
    
```

} blocking assignments

 

 [Synthesis tools will likely eliminate one of these flip-flops (since one of them is redundant) in the optimizer, and create:



as the result of synthesis.

— What happens when we are dealing with combinational logic?

```


EX2
reg f;
always @ (A)
begin
    f = A[1] & A[0]; (1)
    f = f | (A[2] & A[1]); (2)
end
    
```

} blocking assignments.

* Note that if you interchange lines (1) and (2), the result will be different.

— Just like in the previous example, blocking assignments will evaluate to

$$f = (A[1] \& A[0]) | (A[2] \& A[1]);$$

 

∴ The correct combinational logic circuit is synthesized. (intended)

- Other ways to write this circuit: ^(describing)

• Continuous assignments: [least error-prone way]

wire c, d, f;

assign c = A[1] & A[0];

assign d = A[1] & A[2];

assign f = c | d;

} these are
concurrent
(interchangeable)
lines.

[• Non-blocking assignments:

reg c, d, f;

always @ (A[1] or A[0])

c <= A[1] & A[0];

always @ (A[1] or A[2])

d <= A[1] & A[2];

always @ (c or d)

f <= c | d;

]

ADVICE:

① For sequential machine behavior

[procedural assignments within always block
triggered by posedge —, or inputs]


use NON-BLOCKING assignments

② For combinational logic:

-safest way: continuous assignments

-if using procedural assignments, use BLOCKING
assignments.

EX3)

 

reg C, F;

always @ (A or B)

begin

C = A & B;

F = A & C;

end

✓