

# Propagation Delay, Circuit Timing & Adder Design

ECE 152A – Fall 2006

## Reading Assignment

- Brown and Vranesic
  - 2 Introduction to Logic Circuits
    - 2.9 Introduction to CAD Tools
      - 2.9.1 Design Entry
      - 2.9.2 Synthesis
      - 2.9.3 Functional Simulation
      - 2.9.4 Summary
    - 3 Implementation Technology
      - 3.3.1 Speed of Logic Circuits
      - 3.5 Standard Chips
        - 3.5.1 7400-Series Standard Chips

## Reading Assignment

- **Brown and Vranesic** (cont)
  - 5 Number Representation and Arithmetic Circuits
    - 5.1 Positional Number Representation
      - 5.1.1 Unsigned Numbers
      - 5.1.2 Conversion Between Decimal and Binary Systems
      - 5.1.3 Octal and Hexadecimal Representations
    - 5.2 Addition of Unsigned Numbers
      - 5.2.1 Decomposed Full-Adder
      - 5.2.2 Ripple-Carry Adder
      - 5.2.3 Design Example


## Reading Assignment

- **Roth**
  - 1 Introduction Number Systems and Conversion
    - 1.2 Number Systems and Conversion
    - 1.3 Binary Arithmetic
  - 8 Combinational Circuit Design and Simulation Using Gates
    - 8.3 Gate Delays and Timing Diagrams
 
## Propagation Delay

- When gate inputs change, outputs don't change instantaneously
  - This delay is known as “gate” or “propagation” delay

$$\begin{aligned}\epsilon_1 &= t_{PHL} \\ \epsilon_2 &= t_{PLH}\end{aligned}$$



October 12, 2006

ECE 152A - Digital Design Principles

5

## Propagation Delay

- $\epsilon_1$  is the propagation delay from input going high to output going low (inverting logic)
  - $t_{PHL}$
- $\epsilon_2$  is the propagation delay from input going low to output going high (inverting logic)
  - $t_{PLH}$
- Terminology ( $t_{PHL}$  and  $t_{PLH}$ ) always refers to the transition on the output (whether circuit is inverting or not)

October 12, 2006


ECE 152A - Digital Design Principles

6

## Propagation Delay

### ■ Multiple Gate Delays

 - Example assumes that  $t_{PLH}$  and  $t_{PHL}$  equal 20 ns for both AND and NOR gate
  - Not always the case for different transitions or different gate types



October 12, 2006

ECE 152A - Digital Design Principles

7

## Propagation Delay

- Maximum propagation delay is the longest delay between an input changing value and the output changing value
- The path that causes this delay is called the critical path
  - The critical path imposes a limit on the maximum speed of the circuit
    - Max frequency =  $f$  (clk to q + critical path + setup time)  
... much more on this later

October 12, 2006

ECE 152A - Digital Design Principles


8

## Propagation Delay

- For example circuit, critical path is from any change in the A input resulting in a change in  $G_2$ 
  - Circuit is inverting (from A to  $G_2$ )
    - With  $B = 1$  and  $C = 0$ ,  $A \uparrow$  causes  $G_2 \downarrow$  ( $t_{PHL} = 20$  ns) and  $A \downarrow$  causes  $G_2 \uparrow$  ( $t_{PLH} = 20$  ns)
  - Maximum propagation delay
    - $20$  ns +  $20$  ns =  $40$  ns
      - Same for either  $A \uparrow$  or  $A \downarrow$
      - Not always the case

 
## Propagation Delay

- Definitions of transitions and delay times for (inverting) digital circuits



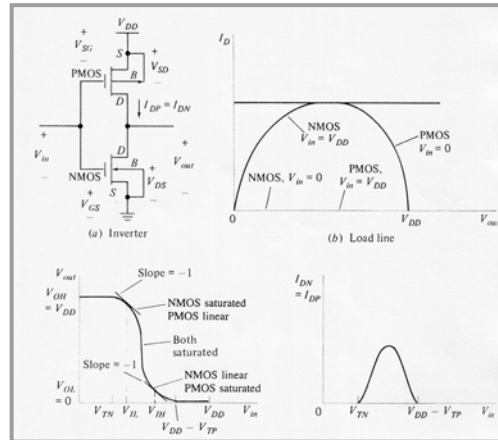
# The CMOS Inverter

- Alternate symbol and more details
  - Current flows only when output switching
  - Power is frequency dependent



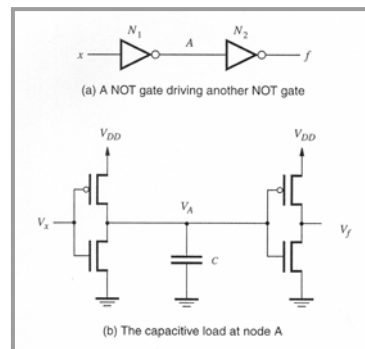
# The CMOS Inverter

- Output switching requires charging (or discharging) parasitic and gate capacitance through a resistor(s)
  - Transistor "on resistance"
  - Wire capacitance and resistance
  - Gate capacitance


 
## The CMOS Inverter

- SPICE Simulation of CMOS inverter pair
  - First inverter driven by ideal source
  - Full (distributed) and lumped RC loads



October 12, 2006

ECE 152A - Digital Design Principles

13

## Transistor-Transistor Logic (TTL)

- Bipolar Junction Transistor (BJT) based technology and logic family
- Both input and output stages implemented with transistors (hence, TTL)
  - Earlier logic families used resistors (RTL) or diodes (DTL) in the input stage
- TTL first commercialized in mid 1960's
  - Driven by many issues, not the least of which was the need for an on-board computer for the Lunar Excursion Module (LEM) in NASA's Apollo program

October 12, 2006

ECE 152A - Digital Design Principles

14

## Transistor-Transistor Logic (TTL)

- First “complete” family of digital integrated circuits
  - Small and medium scale integration (SSI and MSI)
    - SSI < 10 gates per device
    - MSI > 10 and < 100 gates per device
    - LSI and VLSI followed
  - Commercial and military temperature ranges
    - 74XX – Commercial temperature range
      - 0 – 70° C
    - 54XX – Military temperature range
      - -55 – 125° C


## Transistor-Transistor Logic (TTL)

- “Significant” evolution of Texas Instruments’ TTL technology
  - Standard TTL (1965) 54/74XX
  - Schottky-Clamped TTL (1970) 54/74SXX
  - Low Power, Schottky-Clamped TTL (1975) 54/74LSXX
  - Advanced, Low Power, Schottky-Clamped TTL (1980) 54/74ALSXX
  - TTL compatible CMOS (1985) 54/74ACTXX
- Compatible TTL families from other vendors
  - Fairchild, Intel, Motorola, National and others



# Transistor-Transistor Logic (TTL)

## ■ Standard TTL, 2-input NAND Gate

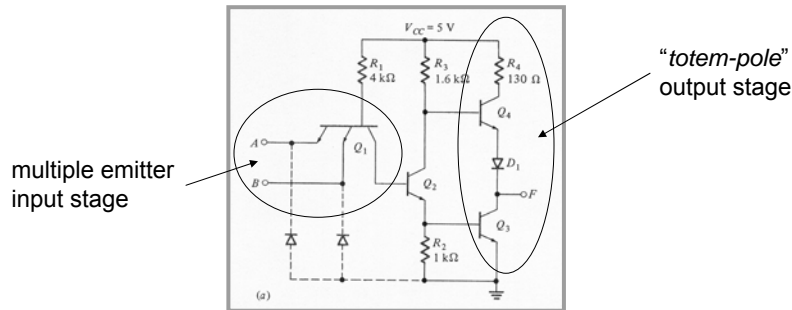

October 12, 2006

ECE 152A - Digital Design Principles

17

# Binary Numbers

- Unsigned and Signed Integers
  - Unsigned integers represent all positive values in the range  $0$  to  $2^n - 1$
  - Signed integers in several flavors
    - Sign magnitude
    - One's complement
    - Two's complement
- We will be concerned with unsigned binary integers for this discussion of adders

October 12, 2006

ECE 152A - Digital Design Principles

18

# Conversion Between Binary and Decimal

## Binary to Decimal

$$1011.11_2 = 1 \times 2^3 + 0 \times 2^2 + 1 \times 2^1 + 1 \times 2^0 + 1 \times 2^{-1} + 1 \times 2^{-2}$$

$$= 8 + 0 + 2 + 1 + \frac{1}{2} + \frac{1}{4} = 11\frac{3}{4} = 11.75_{10}$$

## Decimal to Binary

Convert 53<sub>10</sub> to binary.


|        |                           |
|--------|---------------------------|
| 2 / 53 |                           |
| 2 / 26 | rem. = 1 = a <sub>0</sub> |
| 2 / 13 | rem. = 0 = a <sub>1</sub> |
| 2 / 6  | rem. = 1 = a <sub>2</sub> |
| 2 / 3  | rem. = 0 = a <sub>3</sub> |
| 2 / 1  | rem. = 1 = a <sub>4</sub> |
| 0      | rem. = 1 = a <sub>5</sub> |

53<sub>10</sub> = 110101<sub>2</sub>

Convert .625<sub>10</sub> to binary.

|                       |                       |                       |                      |
|-----------------------|-----------------------|-----------------------|----------------------|
| $F = .625$            | $F_1 = .250$          | $F_2 = .500$          |                      |
| $\times 2$            | $\times 2$            | $\times 2$            | $.625_{10} = .101_2$ |
| 1.250                 | 0.500                 | 1.000                 |                      |
| (a <sub>-1</sub> = 1) | (a <sub>-2</sub> = 0) | (a <sub>-3</sub> = 1) |                      |

# Octal and Hexadecimal Representation

 


**Table 5.1** Numbers in different systems.

| Decimal | Binary | Octal | Hexadecimal |
|---------|--------|-------|-------------|
| 00      | 00000  | 00    | 00          |
| 01      | 00001  | 01    | 01          |
| 02      | 00010  | 02    | 02          |
| 03      | 00011  | 03    | 03          |
| 04      | 00100  | 04    | 04          |
| 05      | 00101  | 05    | 05          |
| 06      | 00110  | 06    | 06          |
| 07      | 00111  | 07    | 07          |
| 08      | 01000  | 10    | 08          |
| 09      | 01001  | 11    | 09          |
| 10      | 01010  | 12    | 0A          |
| 11      | 01011  | 13    | 0B          |
| 12      | 01100  | 14    | 0C          |
| 13      | 01101  | 15    | 0D          |
| 14      | 01110  | 16    | 0E          |
| 15      | 01111  | 17    | 0F          |
| 16      | 10000  | 20    | 10          |
| 17      | 10001  | 21    | 11          |
| 18      | 10010  | 22    | 12          |
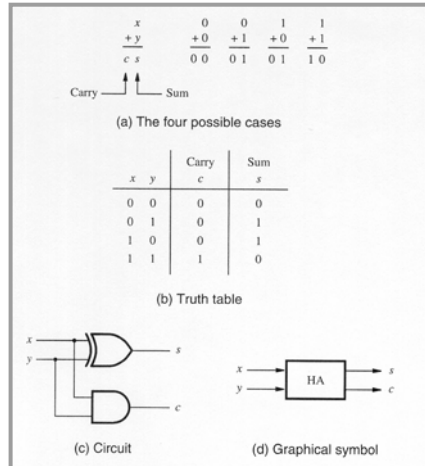
# Addition of Unsigned Numbers


- Half Adder

- 2 input bits
  - x
  - y
- 2 output bits
  - s (sum)
  - c (carry)



 
# TTL Implementation

- SN7400 : Quad, 2-input, positive NAND gates with totem pole outputs
  - SN indicates Texas Instruments
  - Pin assignments (top view) for dual-in-line package (DIP)


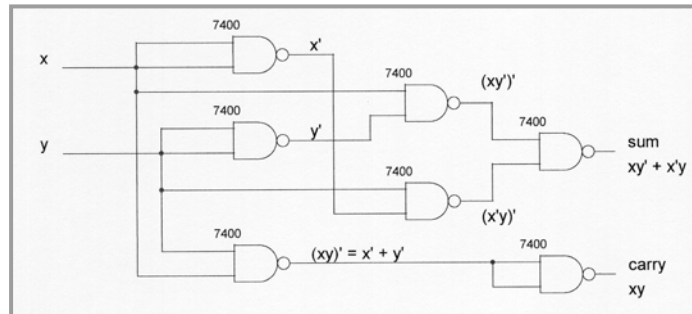
# TTL Implementation

- Schematic with SN7400's
  - 2 IC's, 1 spare NAND gate



October 12, 2006

ECE 152A - Digital Design Principles

23

# TTL Implementation

- SN7400
  - Switching characteristics (propagation delays)
    - $t_{PLH}$  (max) = 22 ns
    - $t_{PHL}$  (max) = 15 ns

switching characteristics at  $V_{CC} = 5\text{ V}$ ,  $T_A = 25^\circ\text{C}$

| TYPE     | TEST CONDITIONS#                           | $t_{PLH}$ (ns)<br>Propagation delay time,<br>low-to-high-level output |     |     | $t_{PHL}$ (ns)<br>Propagation delay time,<br>high-to-low-level output |     |     |
|----------|--|---|-----|-----|---|-----|-----|
|          |  | MIN   | TYP | MAX | MIN   | TYP | MAX |
| '00, '10 | $C_L = 15\text{ pF}$ , $R_L = 400\ \Omega$ |   | 11  | 22  |   | 7   | 15  |
| '04, '20 |  |   | 12  | 22  |   | 8   | 15  |
| '30      |  |   | 13  | 22  |   | 8   | 15  |

October 12, 2006

ECE 152A - Digital Design Principles

24

## TTL Implementation

- Worst case propagation delay
  - Critical path is x (or y) to sum
  - Three levels of gate delay and three levels of inversion
    - Two possibilities
      - $t_{PLH} + t_{PHL} + t_{PLH}$
      - $t_{PHL} + t_{PLH} + t_{PHL}$
    - Max delay is  $t_{PLH} + t_{PHL} + t_{PLH}$ 
      - $22 \text{ ns} + 15 \text{ ns} + 22 \text{ ns} = 59 \text{ ns}$
      - Max frequency =  $1 / (\text{clk to } q + 59 \text{ ns} + \text{setup time})$


## Programmable Logic Devices

- A Programmable Logic Device (PLD) is a single, programmable device capable of replacing multiple, discrete TTL chips
  - PLD is comprised of “uncommitted” gates and programmable switches to interconnect the gates
  - Simple PLD’s can realize 2 to 10 functions of 4 to 16 input variables
  - Complex PLD’s can implement circuits requiring 100’s of thousands of gates

## Half Adder Implementation with a Programmable Logic Device (PLD)
 
### ■ Schematic Capture (Design Entry)

- Using “Primitive” library of logic elements
  - Specify logic function using generic logic gates rather than selecting physical devices (e.g., 7400 TTL)
  - CAD tool will determine actual implementation



October 12, 2006


ECE 152A - Digital Design Principles

27

## PLD Implementation of Half Adder

### ■ Functional Simulation

- All propagation delays set to zero

 

October 12, 2006

ECE 152A - Digital Design Principles

28

## PLD Implementation of Half Adder


- Map logical design onto a target architecture and physical device using CAD tool
  - Logical function is specified via the primitive library and implemented using logical structures incorporated into the target architecture
  - The physical device is a single chip hardware implementation of the design incorporating the structures of the target architecture
    - Altera MAX 7000 Complex Programmable Logic Device (CPLD) family for this example

## PLD Implementation of Half Adder

- Timing Simulation
  - Must know specific device and package combination in PLD environment
    - Both contribute to performance
  - Simulation of physical implementation of design
    - Logical (gate) delays
    - Physical (interconnect) delays
    - I/O (package input/output) delay

 
# PLD Implementation of Half Adder

- Approximately 6ns delay from input to output
  - $t_{PLH}$  and  $t_{PHL}$


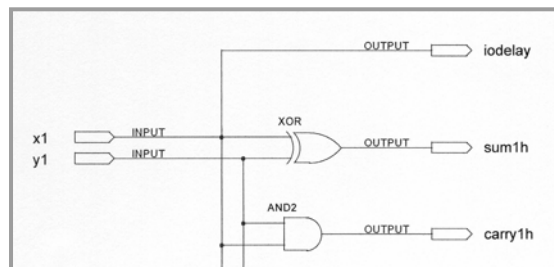
# I/O Delays

- Circuit to measure I/O delay
  - X1 to iodelay path through input receiver and output driver
    - Allows I/O delay to be separated from internal (core) delays






# I/O Delays
 
## ■ Timing Simulation


- Simulation indicates I/O delay dominates logic circuit delays for this (very small) design



# Full Adder

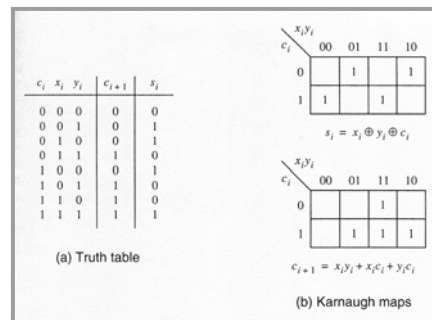
## □ Full Adder

- By adding a *carry in* input, multiple-bit numbers can be added by cascading full adder stages
- The sum and carry out become functions of three variables  $x$ ,  $y$  and  $c_{in}$




# Full Adder

- Generic Circuit Implementation

 

# Full Adder Implementation


- Schematic Capture

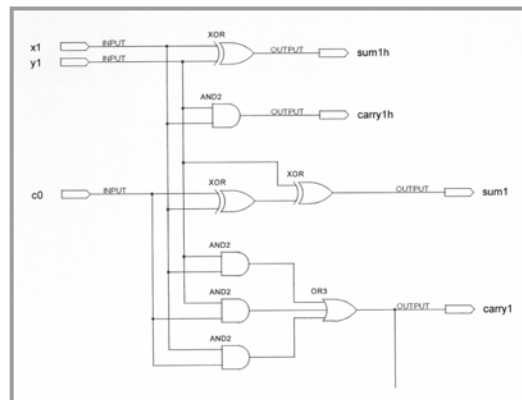
 
# Full Adder Implementation

- Timing Simulation

- As with the half adder, I/O delays dominate



October 12, 2006


ECE 152A - Digital Design Principles

37
 
# Ripple Carry Adder

- n-bit, Ripple Carry Adder

- By cascading full adders, carry “ripples” from least to significant bit toward most significant bit
    - Critical path becomes input to full adder 0 to output of full adder n




October 12, 2006

ECE 152A - Digital Design Principles

38
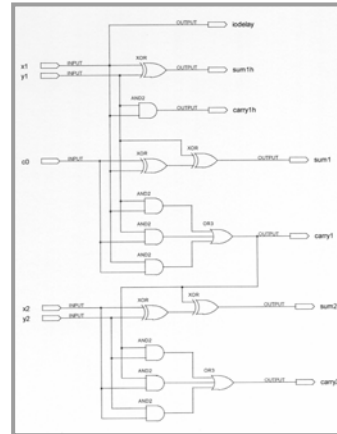
# Two-Bit Ripple Carry Adder

- Schematic with I/O test circuit, half-adder, full adder and two-bit ripple carry adder




October 12, 2006

ECE 152A - Digital Design Principles

39

# CPLD Implementation

- Timing Simulation

 

October 12, 2006

ECE 152A - Digital Design Principles

40

## CPLD Implementation

### ■ Timing Simulation

- Note propagation delay from y1 to carry2 is measured at 9.5 ns
  - Greater than simulated I/O delay of 6ns
  - Internal delays now visible (and measurable) at device pins
- Note also 3.5 ns “glitch” at 66ns
  - Resolution of simulation implied to be 3.5ns