

Combinational Logic Design with Verilog

ECE 152A – Fall 2006

Reading Assignment

- Brown and Vranesic
 - 2 Introduction to Logic Circuits
 - 2.10 Introduction to Verilog
 - 2.10.1 Structural Specification of Logic Circuits
 - 2.10.2 Behavioral Specification of Logic Circuits
 - 2.10.3 How *Not* to Write Verilog Code

Reading Assignment

- Brown and Vranesic (cont)
 - 4 Optimized Implementation of Logic Functions
 - 4.12 CAD Tools
 - 4.12.1 Logic Synthesis and Optimization
 - 4.12.2 Physical Design
 - 4.12.3 Timing Simulation
 - 4.12.4 Summary of Design Flow
 - 4.12.5 Examples of Circuits Synthesized from Verilog Code

Design Entry

- In previous examples, design entry is schematic based
 - TTL implementation using standard, discrete integrated circuits
 - PLD implementation using library of primitive elements
- Code based design entry uses a hardware description language (HDL) for design entry
 - Code is synthesized and implemented on a PLD

Verilog Design

- **Structural Verilog**
 - Looks like the gate level implementation
 - Specify gates and interconnection
 - Text form of schematic
 - Referred to as “netlist”
 - Allows for “bottom – up” design
 - Begin with primitives, instantiate in larger blocks

October 17, 2006

ECE 152A - Digital Design Principles

5

Verilog Design

- **RTL (Register Transfer Level) Verilog**
 - Allows for “top – down” design
 - No gate structure or interconnection specified
 - Synthesizable code (by definition)
 - Emphasis on synthesis, not simulation
 - vs. high level behavioral code and test benches
 - No timing specified in code
 - No initialization specified in code
 - Timing, stimulus, initialization, etc. generated in testbench (later)


October 17, 2006

ECE 152A - Digital Design Principles

6

Half Adder - Structural Verilog Design

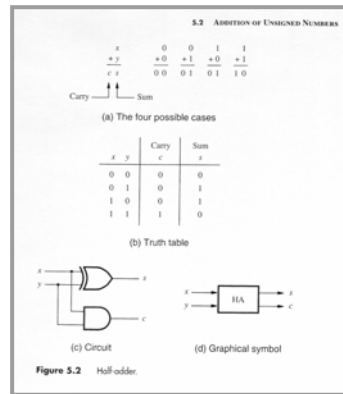- Recall Half Adder description from schematic based design example
 - Operation
 - Truth table
 - Circuit
 - Graphical symbol



Verilog Syntax

- Modules are the basic unit of Verilog models
 - Functional Description
 - Unambiguously describes module's operation
 - Functional, i.e., without timing information
 - Input, Output and Bidirectional ports for interfaces
 - May include instantiations of other modules
 - Allows building of hierarchy

Verilog Syntax

- **Module declaration**
 - module ADD_HALF (s,c,x,y);
 - Parameter list is I/O Ports
- **Port declaration**
 - Can be input, output or inout (bidirectional)
 - output s,c;
 - input x,y;

October 17, 2006

ECE 152A - Digital Design Principles

9

Verilog Syntax

- **Declare nodes as wires or reg**
 - Wires assigned to declaratively
 - Reg assigned to procedurally
 - More on this later
 - In a combinational circuit, all nodes can, but don't have to be, declared wires
 - Depends on how code is written
 - Node defaults to wire if not declared otherwise
 - wire s,c,x,y;

October 17, 2006

ECE 152A - Digital Design Principles

10

Verilog Syntax

■ Gates and interconnection

- xor G1(s,x,y);
- and G2(c,x,y);
 - Verilog gate level primitive
 - Gate name
 - Internal (local) name
 - Instance name
 - Parameter list
 - Output port, input port, input port...

Gate Instantiation

■ Verilog Gates

- Note: *notif* and *bufif* are tri-state gates

Table A.2 Verilog gates.

Name	Description	Usage
and	$f = (a \cdot b \cdot \dots)$	and (<i>f</i> , <i>a</i> , <i>b</i> , ...)
nand	$f = \overline{(a \cdot b \cdot \dots)}$	nand (<i>f</i> , <i>a</i> , <i>b</i> , ...)
or	$f = (a + b + \dots)$	or (<i>f</i> , <i>a</i> , <i>b</i> , ...)
nor	$f = \overline{(a + b + \dots)}$	nor (<i>f</i> , <i>a</i> , <i>b</i> , ...)
xor	$f = (a \oplus b \oplus \dots)$	xor (<i>f</i> , <i>a</i> , <i>b</i> , ...)
xnor	$f = (a \odot b \odot \dots)$	xnor (<i>f</i> , <i>a</i> , <i>b</i> , ...)
not	$f = \bar{a}$	not (<i>f</i> , <i>a</i>)
buf	$f = a$	buf (<i>f</i> , <i>a</i>)
notif0	$f = (e ? \bar{a} : 'bz)$	notif0 (<i>f</i> , <i>a</i> , <i>e</i>)
notif1	$f = (e ? a : 'bz)$	notif1 (<i>f</i> , <i>a</i> , <i>e</i>)
bufif0	$f = (e ? a : 'bz)$	bufif0 (<i>f</i> , <i>a</i> , <i>e</i>)
bufif1	$f = (e ? \bar{a} : 'bz)$	bufif1 (<i>f</i> , <i>a</i> , <i>e</i>)

Verilog Syntax


- Close the module definition with
 - endmodule
- Comments begin with //

Half Adder - Structural Verilog Design

```
module ADD_HALF (s,c,x,y);  
  
    output s,c;  
    input x,y;  
  
    wire s,c,x,y;  
        // this line is optional since nodes default to wires  
  
    xor G1 (s,x,y); // instantiation of XOR gate  
    and G2 (c,x,y); // instantiation of AND gate  
  
endmodule
```

Half Adder – PLD Implementation

■ Functional Simulation

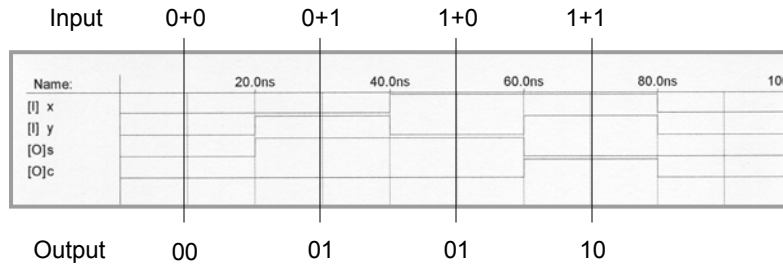

Full Adder – Structural Verilog Design

- Recall Full Adder description from schematic based design example
 - Truth table
 - Karnaugh maps
 - Circuit


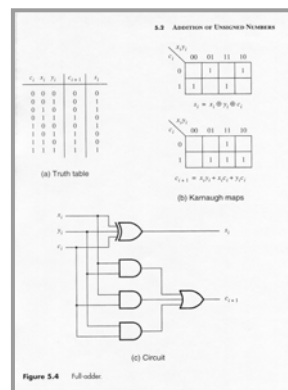


Figure 5.4 Full-adder

Full Adder from 2 Half Adders

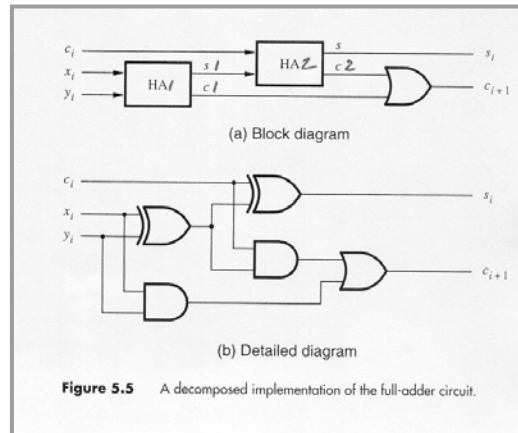

October 17, 2006

ECE 152A - Digital Design Principles

17

Full Adder – Structural Verilog Design

```
module ADD_FULL (s,cout,x,y,cin);  
  
    output s,cout;  
    input x,y,cin;  
  
    //internal nodes also declared as wires  
    wire cin,x,y,s,cout,s1,c1,c2;  
  
    ADD_HALF HA1(s1,c1,x,y);  
    ADD_HALF HA2(s,c2,cin,s1);  
    or (cout,c1,c2);  
  
endmodule
```


October 17, 2006

ECE 152A - Digital Design Principles

18

Full Adder – PLD Implementation

■ Functional Simulation

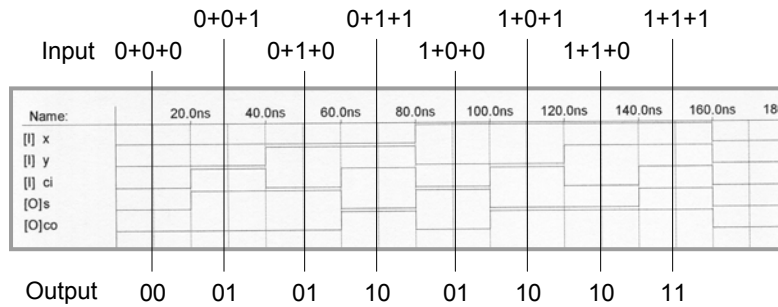

Verilog Operators

- The Verilog language includes a large number of logical and arithmetic operators
 - Bit length column indicates width of result

Category	Examples	Bit Length
Bitwise	$\sim A$, $+A$, $-A$ $A \& B$, $A B$, $A \sim\sim B$, $A \wedge\sim B$	$L(A)$ $\text{MAX}(L(A), L(B))$
Logical	$\&A$, $\&\&A$, $A B$	1 bit
Reduction	$\&A$, $\sim\&A$, $ A$, $\sim A$, $\wedge\sim A$, $\sim\wedge A$	1 bit
Relational	$A == B$, $A' = B$, $A > B$, $A < B$ $A >= B$, $A <= B$ $A ==\sim B$, $A' == B$	1 bit
Arithmetic	$A + B$, $A - B$, $A * B$, A / B $A \% B$	$\text{MAX}(L(A), L(B))$
Shift	$A << B$, $A >> B$	$L(A)$
Concatenate	$\{A, \dots, B\}$	$L(A) + \dots + L(B)$
Replication	$\{B[A]\}$	$B * L(A)$
Condition	$A ? B : C$	$\text{MAX}(L(B), L(C))$

Behavioral Specification of Logic Circuits

■ Continuous Assignment Operator

- assign sum = a ^ b;
 - “Assign” to a wire (generated declaratively)
 - Equivalent to
 - xor (sum,a,b);
- Continuous and concurrent with other wire assignment operations
 - If a or b changes, sum changes accordingly
 - All wire assignment operations occur concurrently
 - Order not specified (or possible)

Full Adder from Logical Operations

```
module ADD_FULL_RTL (sum,cout,x,y,cin);  
  
    output sum,cout;  
    input x,y,cin;  
  
    //declaration for continuous assignment  
    wire cin,x,y,sum,cout;  
  
    //logical assignment  
    assign sum = x ^ y ^ cin;  
    assign cout = x & y | x & cin | y & cin;  
  
endmodule
```

Full Adder from Arithmetic Operations

```
module ADD_FULL_RTL (sum,cout,x,y,cin);

    output sum,cout;
    input x,y,cin;

    //declaration for continuous assignment
    wire cin,x,y,sum,cout;

    // concatenation operator and addition
    assign {cout, sum} = x + y + cin;

endmodule
```

Procedural Verilog Statements

- Recall:
 - Wires assigned to declaratively
 - Continuous / concurrent assignment
 - Reg “variables” assigned to procedurally
 - Value is “registered” until next procedural assignment
 - Continuous assignment (wires) occurs immediately on input change
 - Enables clocked (synchronous) timing

Procedural Verilog Statements

- The “always” block
 - Syntax is “always at the occurrence (@) of any event on the *sensitivity list*, execute the statements inside the block (in order)”

```
always @ (x or y or cin)
    {cout, sum} = x + y + cin;
```

RTL Design of Full Adder

```
module ADD_FULL_RTL (sum,cout,x,y,cin);

    output sum,cout;
    input x,y,cin;

    //declaration for behavioral model
    wire cin,x,y;
    reg sum,cout;

    // behavioral specification
    always @ (x or y or cin)
        {cout, sum} = x + y + cin;

endmodule
```

Two-bit, Ripple Carry Adder – Structural Verilog

```

module TWO_BIT_ADD (S,X,Y,cin,cout);

    input cin;
    input [1:0]X,Y; // vectored input
    output [1:0]S; // and output signals
    output cout;

    wire cinternal;

    ADD_FULL AF0(S[0],cinternal,X[0],Y[0],cin);
    ADD_FULL AF1(S[1],cout,X[1],Y[1],cinternal);

endmodule

```


October 17, 2006

ECE 152A - Digital Design Principles

27

Two-bit, Ripple Carry Adder – PLD Implementation

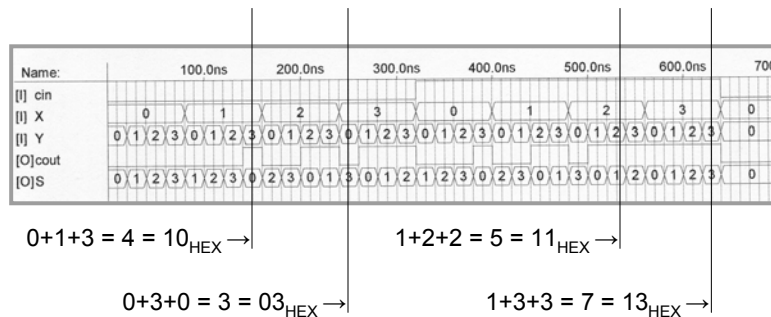- Functional Simulation
 - HEX Bus Representation of X, Y and Sum



October 17, 2006

ECE 152A - Digital Design Principles

28

Verilog Test Bench

- Device Under Test (DUT)
 - Circuit being designed/developed
 - Full adder for this example
- Testbench
 - Provides stimulus to DUT
 - Like test equipment on a bench
- Instantiate DUT in testbench
 - Generate all signals in testbench
 - No I/O (parameter list) in testbench

Full Adder Testbench Example

```
module ADDFULL_TB;
    reg a,b,ci;
    wire sum,co;

    initial begin
        a = 0;
        b = 0;
        ci = 0;
    end

    always begin
        #5 a = ~a;
    end

    always begin
        #10 b = ~b;
    end

    always begin
        #20 ci = ~ci;
    end

    ADD_FULL AF1(sum,co,a,b,ci);
endmodule
```