

OVERVIEW OF ECE 152A LABS

- Lab 1
 - Display A-J on a 7-segment LED display
- Lab 2
 - 3 Adders in Verilog
- Lab 3
 - Up/Down Counter
- Lab 4
 - Ford Thunderbird Tail lights


LAB 1: COMBINATIONAL LOGIC To Display Letters on 7-segment LED

Design Process:

Word problem->Logic Equations->Logic
Minimization (K-maps)->TTL Design



LAB 1 IMPLEMENTATION

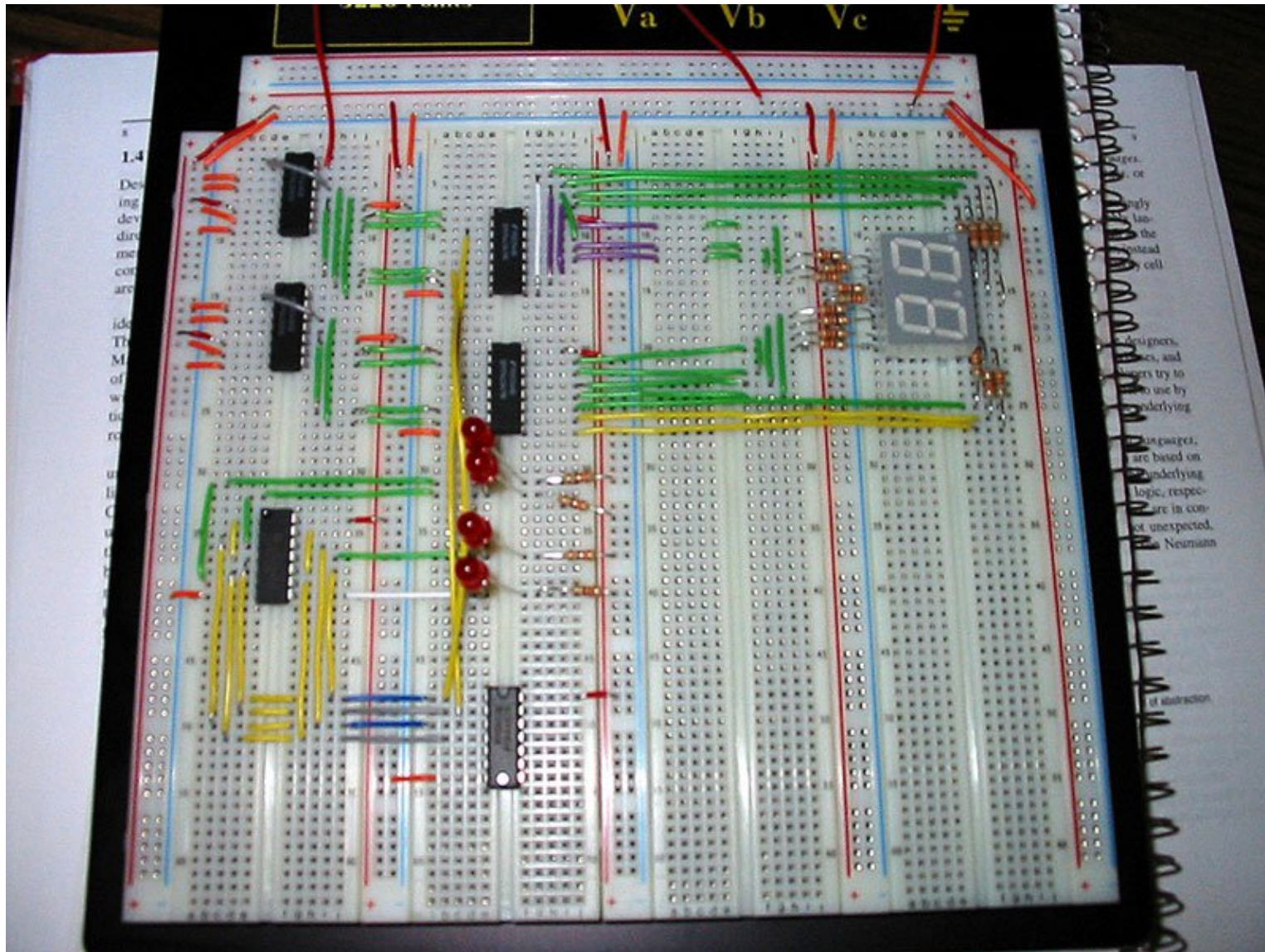


LAB 2: ADDERS


SPACE COMPLEXITY VS. DELAY

- Types


- Ripple carry
- And-Or
- 2-bit pairs

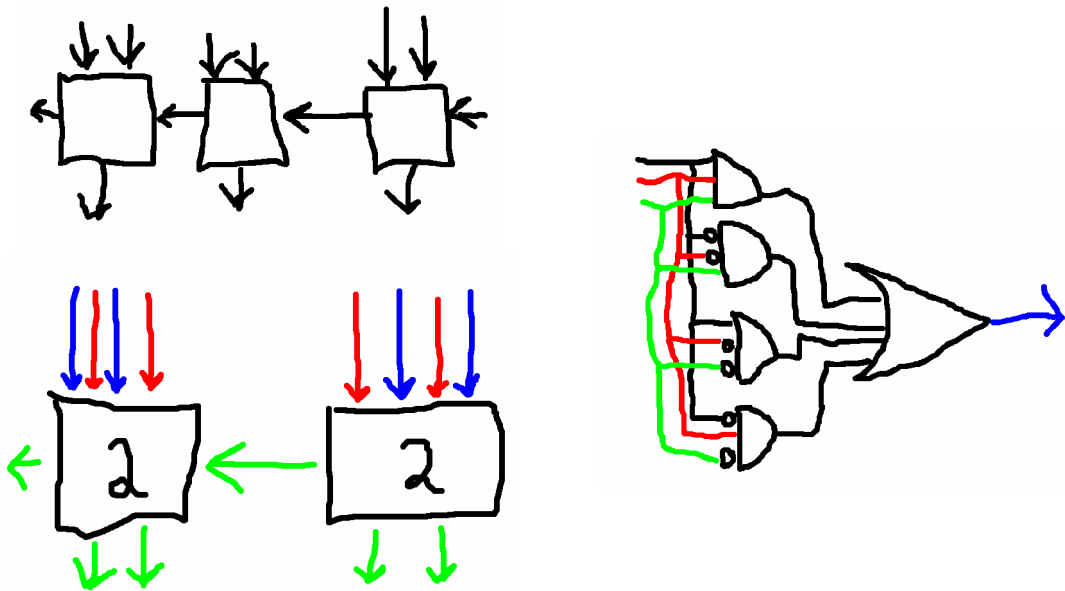

- Implemented in Verilog

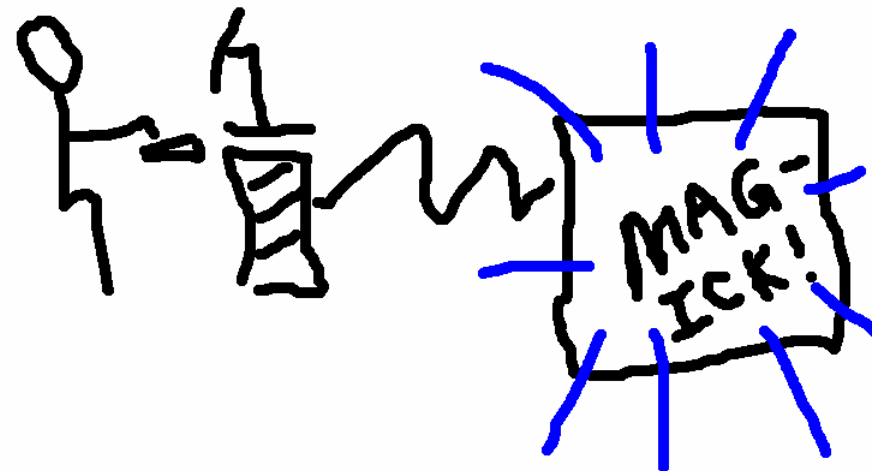

ECE DIGILAB FPGA BOARD

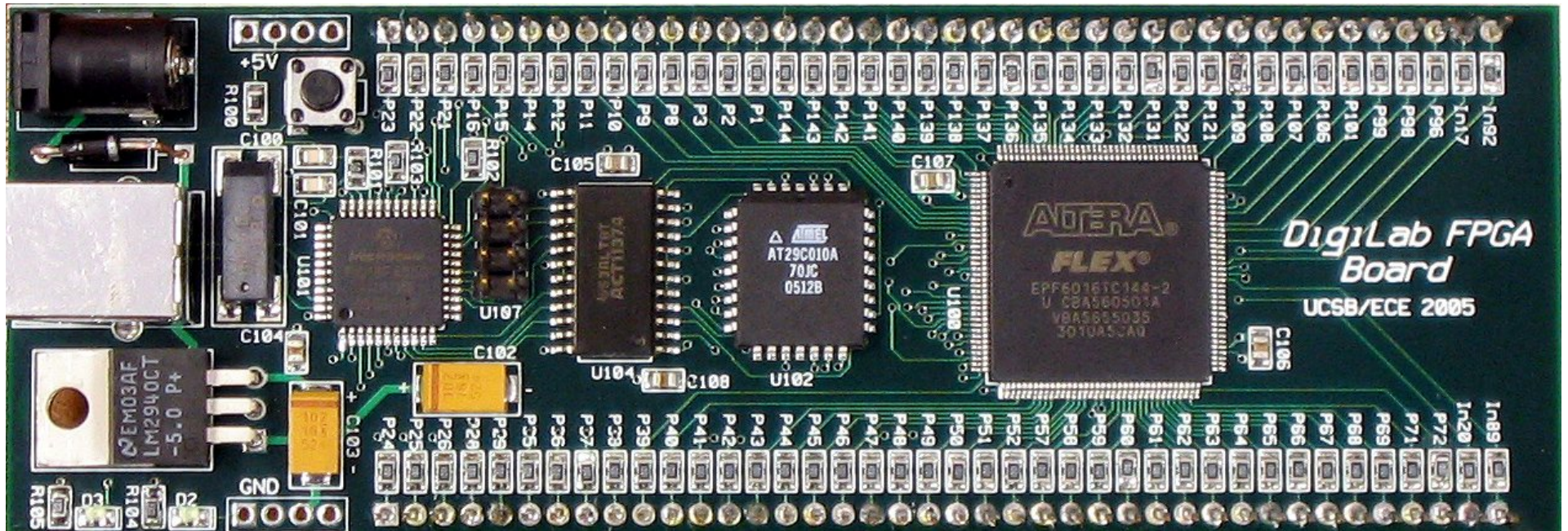


You will be using this FPGA board in Lab 2 (& 4).

Design process:

Design in Verilog->FPGA download

LAB 3: COUNTERS

UP-DOWN COUNTER

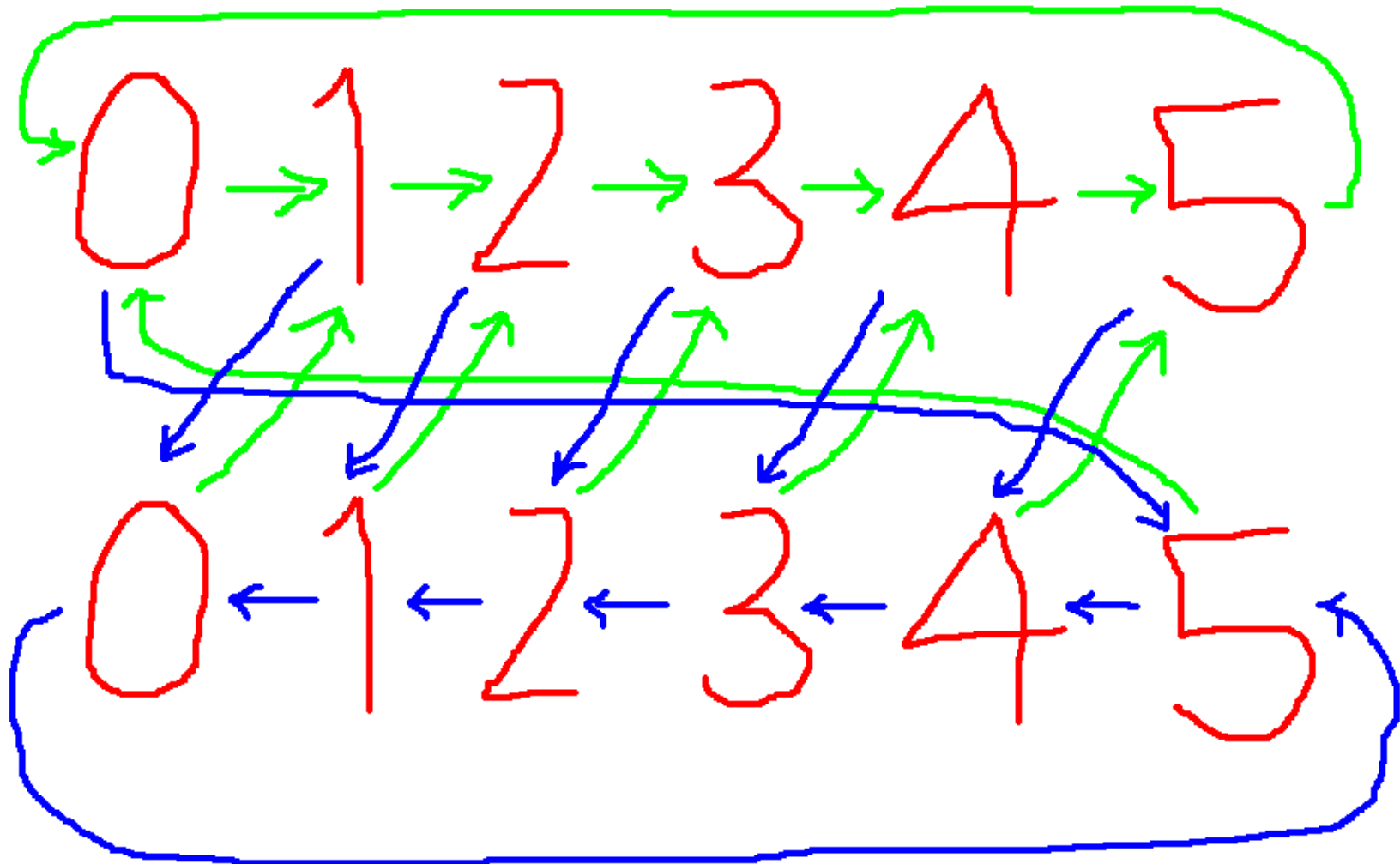

LAB 4: FINITE STATE MACHINE DESIGN: Tail-lights of an Automobile



LAB 4: FINITE STATE MACHINE DESIGN: Tail-lights of an Automobile



Left Turn



LAB 4 IMPLEMENTATION

