 


LECTURE #13


① CMOS Technology;

transistor: a basic switch,

two types in CMOS: [complementary Mos] of transistors




N-Mos

 

P-Mos


Basic idea;

N-mos: Apply

 

passes the signal (current) through.



||| equivalent to;

 



|||



N-MOS passes "0" well,

  


p-MOS passes "1" well,

  


— Boolean functions can be implemented in a technology (CMOS) that uses p-MOS & n-MOS transistors

Main idea:

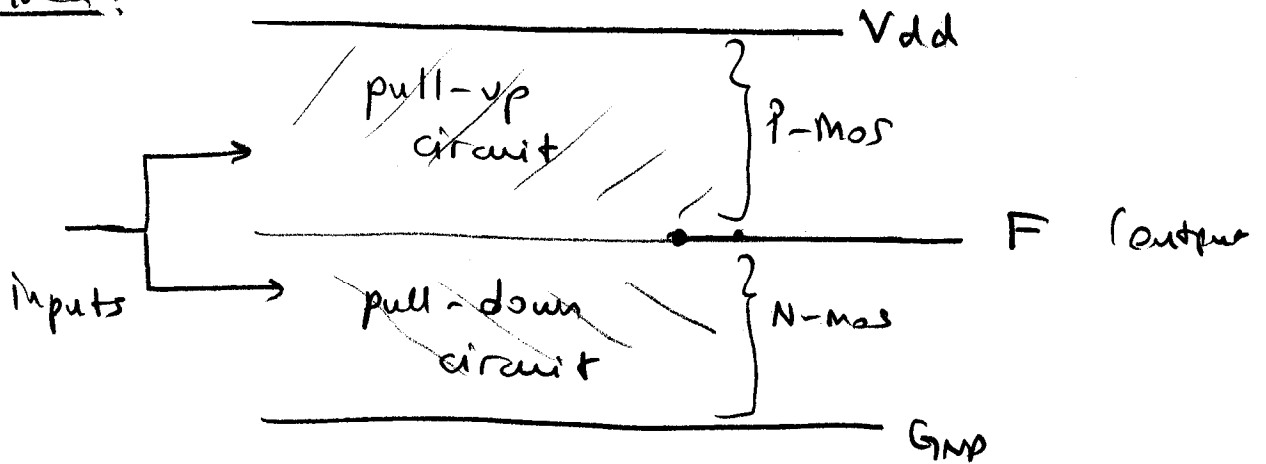


- Pull-up circuit implements the "1"s of F (the "1"s, i.e. ON-SETS or K-map of F .)
- Pull-down circuit implements the "0"s of F .

 Example 1: Implement an inverter in CMOS.



Solution: $F = A'$ → implement in P-mos


$F' = A$. → implement in N-mos

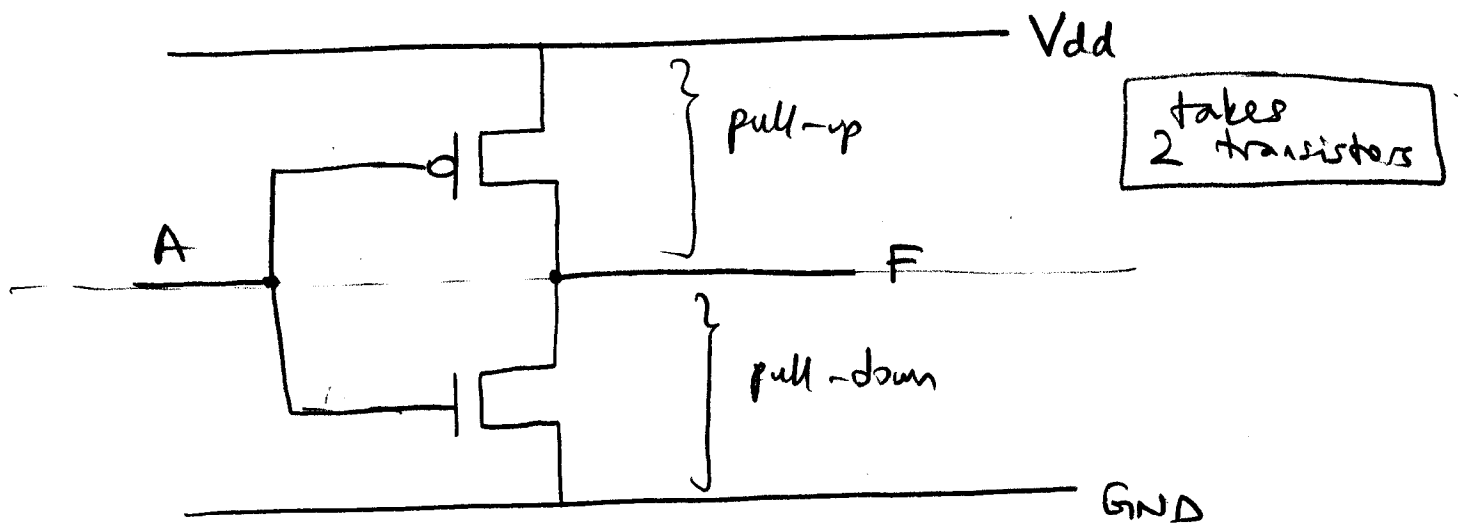

Example 2: Implement a NAND gate in CMOS.

Solution: $F = (A \cdot B)'$ $= A' + B'$ → OR: Implement as a parallel network of switches


$F' = A \cdot B$ → AND: series network of switches

 

Example 3: Implement a NOR gate in CMOS.

Solution: $F = (A + B)' = A' \cdot B'$


$$F' = A + B.$$

 

Example 4: Implement an AND gate in CMOS.

Solution: $F = A \cdot B$

$$F' = (A \cdot B)' = A' + B'$$

 


- The above is one ^{of the} reasons that NAND gates are more frequently used in CMOS implementations (ie. NAND gate does not require any complements of inputs)

Example 5: OR gate in CMOS

Solution: $F = A + B$

$$F' = (A + B)' = A' \cdot B'$$

 

Example 6: Implement $F = A \cdot B + C$ in CMOS.
[This shows the general procedure to implement any Boolean function.]

Solution:


$$F = A \cdot B + C$$

pull-up


$$F' = (A \cdot B + C)' = (A \cdot B)' \cdot C'$$

$$= (A' + B') \cdot C'$$

pull-down

 

Where :

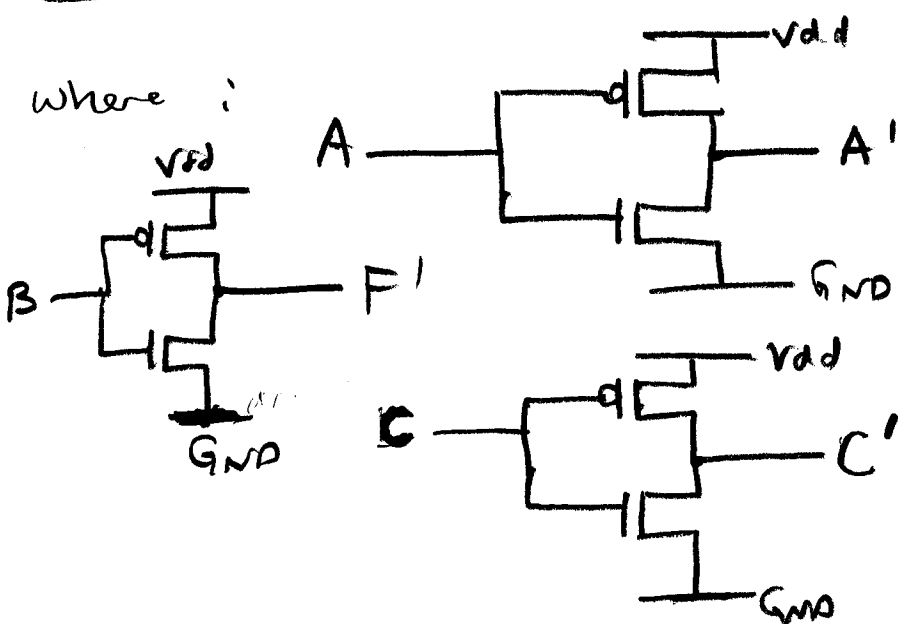


A total of 12 transistors needed for this F.

So far! Combinational logic. Now!

- Memory elements:

 • cross-coupled NOR gates: (basic latch),



• How many transistors used if implemented in CMOS?

$$2 \times \underset{\substack{\uparrow \\ \text{for NOR gate}}}{4} = \boxed{8 T} \quad (8 \text{ transistors})$$


- So far, we used memory elements in discrete components

- For, integrated memories, need high density (i.e., a high # bits stored per area). - So, reduce the area of a "cell" (a storage unit to hold one bit).

↑
(dependent on the # transistors & the wiring complexity),

- A "memory cell" that uses 6T (6 transistors)

[6T S-RAM cell]:

 


- This cell holds 1 bit.

- cross coupled inverters.

- $(2T / \text{inverter} \times 2 \text{ inverters}) + 2 \text{ (n-mos T for access)} = \boxed{6T}$.

Operation:

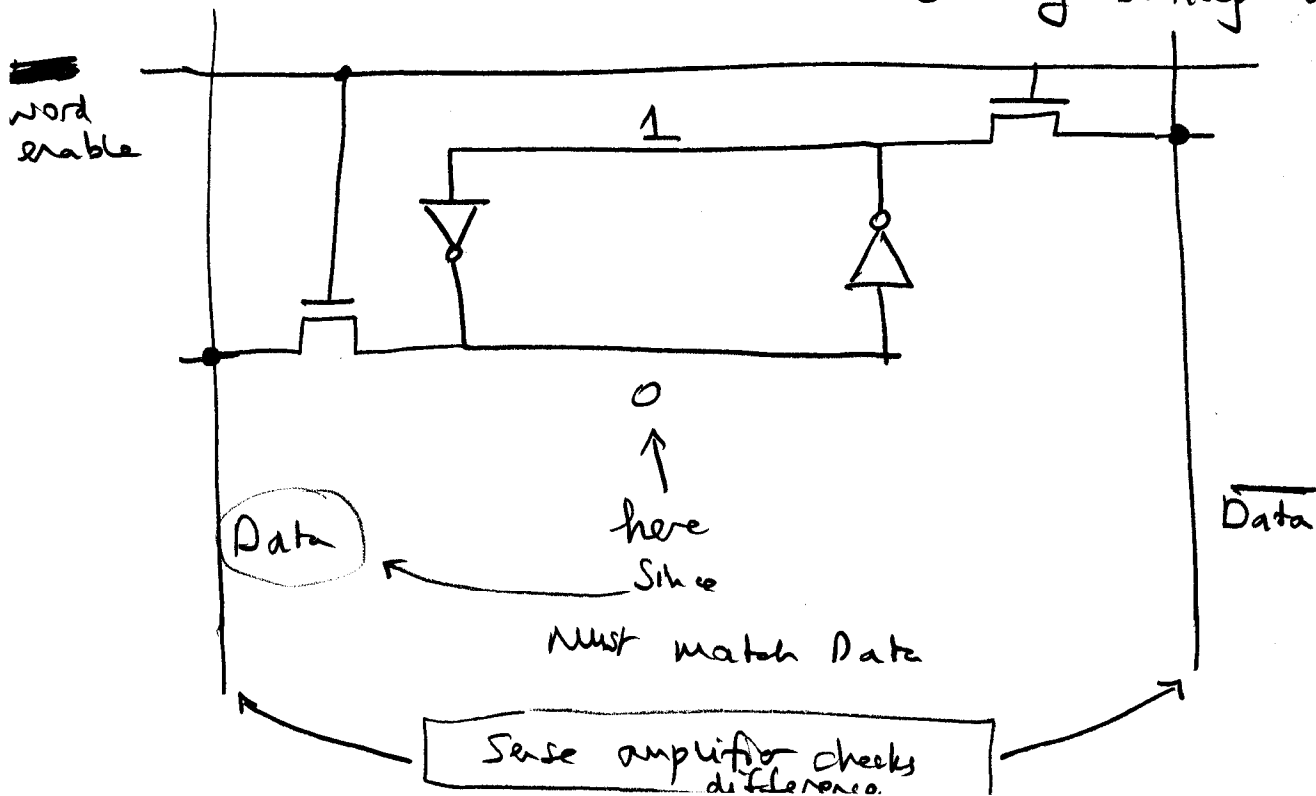Assume that the cell is originally storing a "0".



READ :

- Now, to read from the cell, first the

W ① Both Data and $\overline{\text{Data}}$ are pre-charged to 1,

② Word Enable is put to high.

- The "0" in the cell pulls the Data line to 0 (since N-Mos passes 0 well.)

③ The sense amplifier senses the difference between Data and $\overline{\text{Data}}$.

- If Data has a voltage \downarrow sufficiently less than $\overline{\text{Data}}$, then a value of "0" is declared.

- otherwise "1" is declared.

WRITE :

- To write to the cell: (e.g. write a "0".)

① Data = 0 and $\overline{\text{Data}} = 1$ by external circuitry

② Word Enable = 1.

- The external circuitry drives these values into the cell (0 to lower part of cell). The driving

- How is the cell used?

S-RAM: static RAM

(x dynamic RAM)
 ↑
 requires refresh to leakage

means: will hold the contents as long as power is ON, with no refresh needed.

Ex 1


1024 x 4 S-RAM.

↑
 # of words

↑
 # of bits per word.


Conceptual organization:

 ($2^{10} \cdot 2^2 = 2^{12}$ memory cells required here.)



- Idea: Address one of the 1024 (by a 10-bit address) and read out (or write in) an entire word.

Conceptually:

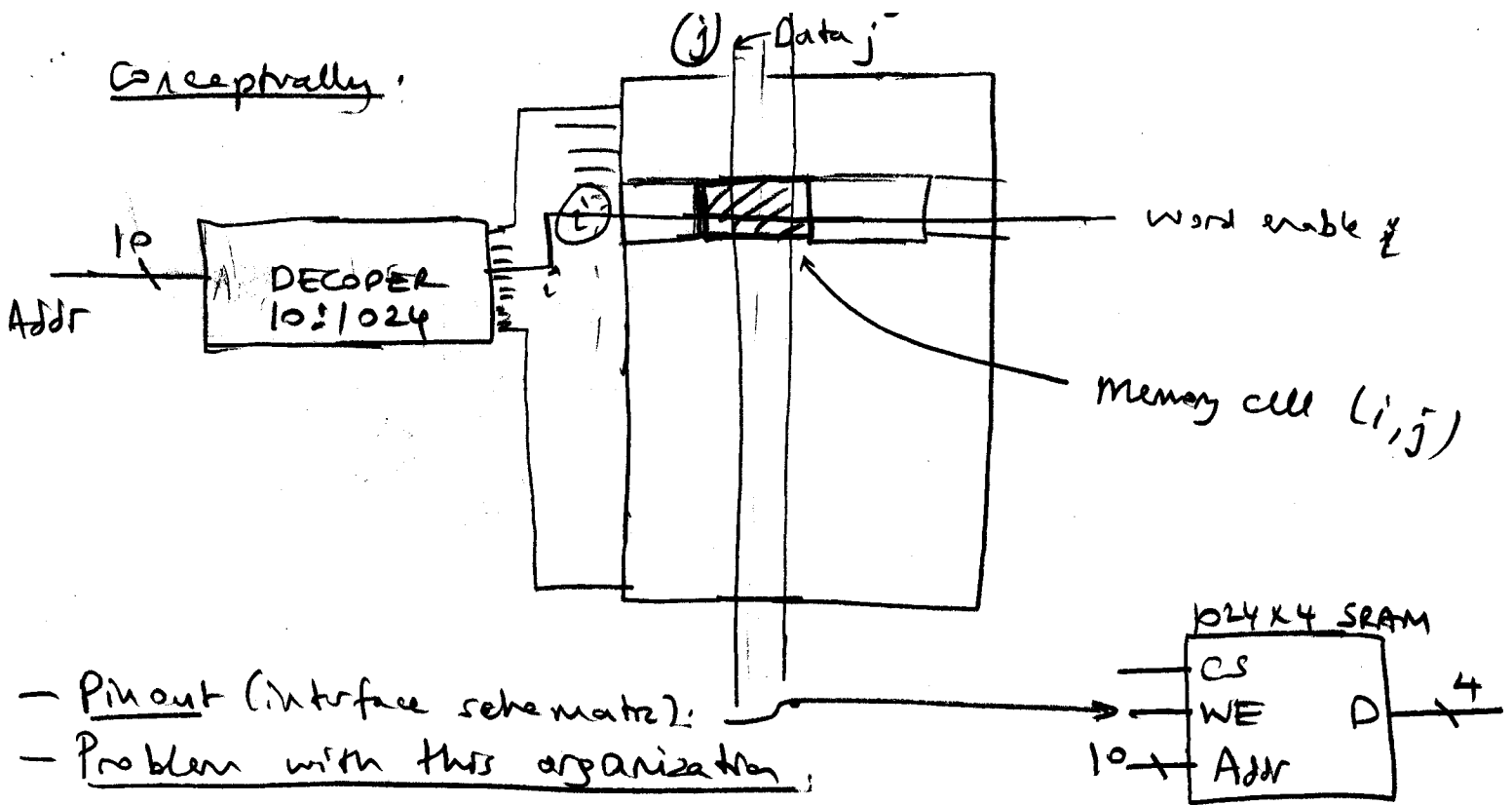


- Pinout (interface schematic):
- Problem with this organization:

- Long Data (and Addr) wires:
 - increase delay (due to wire length)


Better internal organization uses a "storage matrix" that is square: $1024 \times 4 = 64 \times 64$

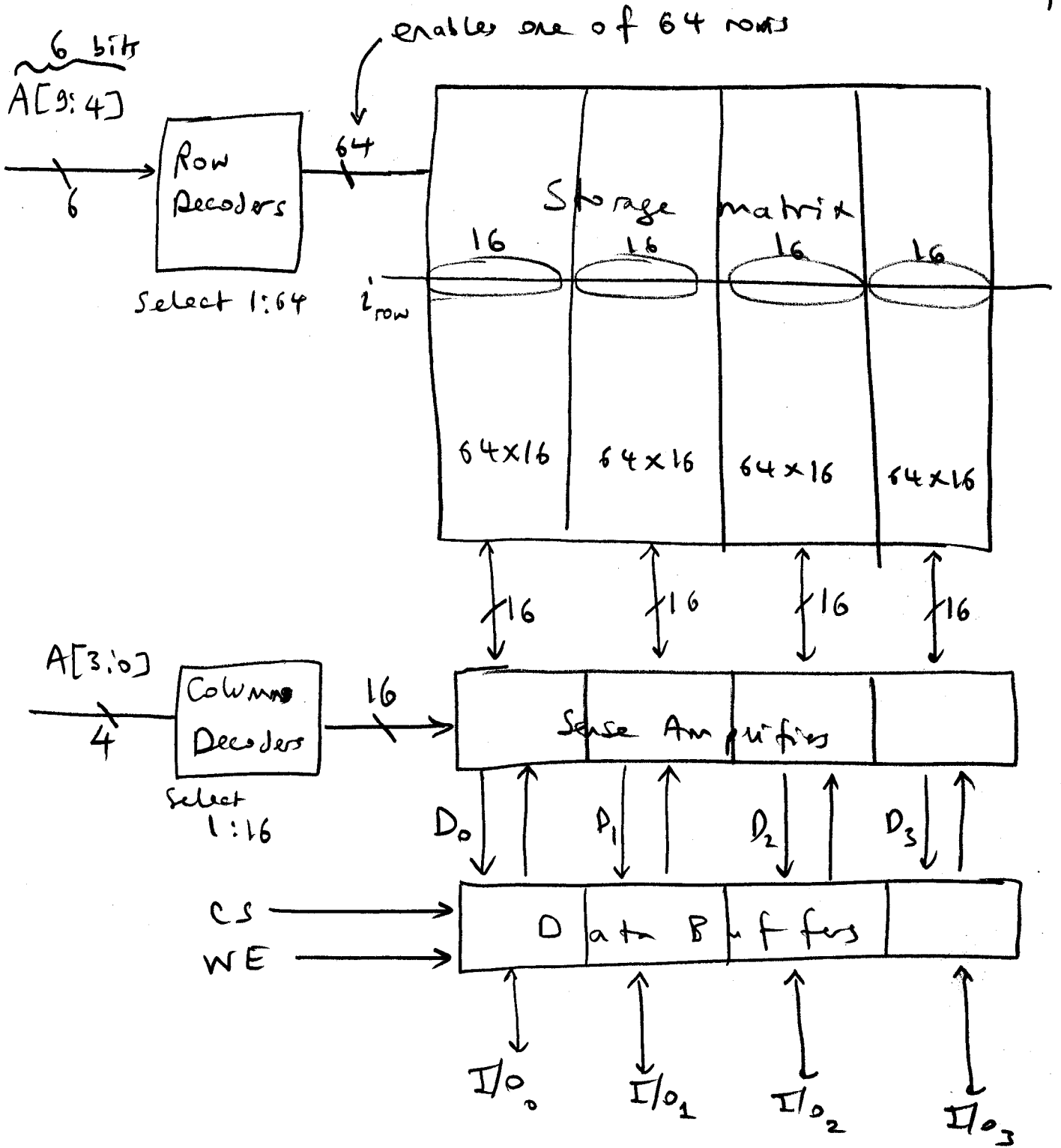- This organization is shown on the next page:




- Note that the 4 bits in a ^{RAM} word do not sit next to each other in the storage matrix. (ie the physical storage location is different from that in the conceptual organization)

SRAM Read Cycle Sequence

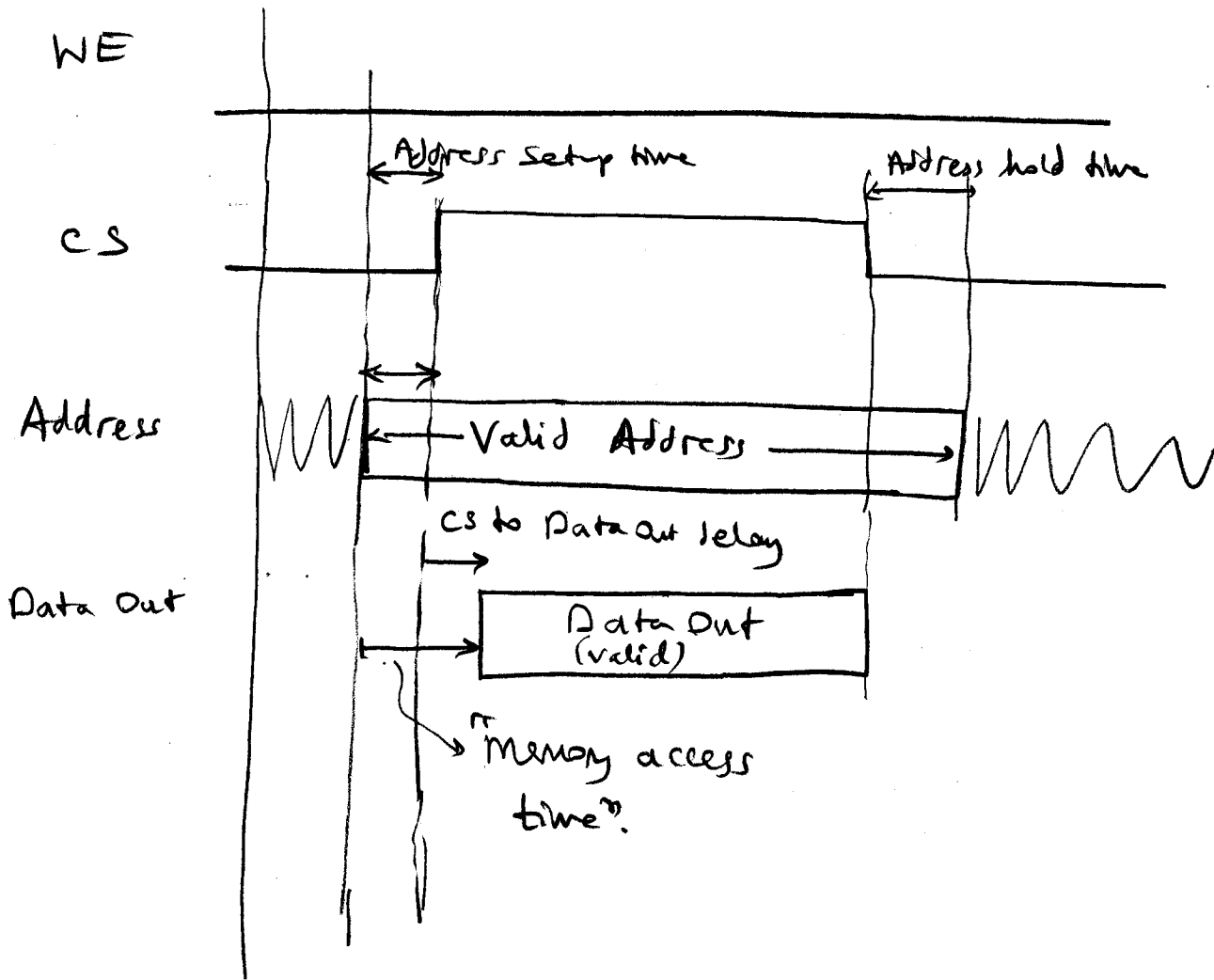

- Keys • the address has to settle to the correct value a setup time before the CS (or WE) goes high. (otherwise you read out junk.)
- WE must be kept low the entire time CS is high. (for reading)


SRAM write cycle sequencing:

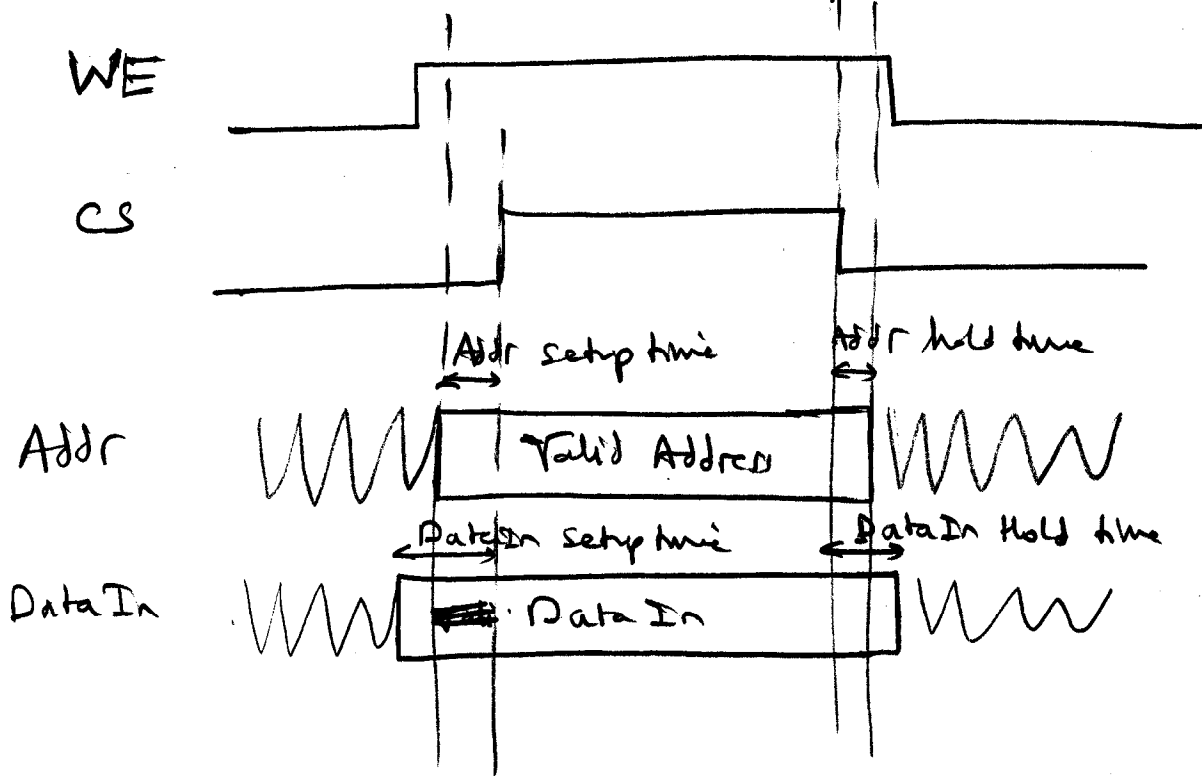

- Keys:
- Both the Addr and the DataIn have to have settled to their correct values, respective setup times, before the CS goes high.
 - Note that write cycle begins when both WE and CS are high.

Dynamic RAM :

 - smaller space per cell \rightarrow higher integrable density
- slower than SRAM.
- needs refreshing ($\approx 1-4$ MS or so.)



- capacitor leaks the charge over time (\approx milliseconds)
So need to read out contents & write them back in,
("refresh operation")