

# Problem Set 2

Prof. Luke Theogarajan  
ECE 194A/594A  
Department of Electrical & Computer Engineering,  
University of California, Santa Barbara

Due October 24, 2008

## Problem 1

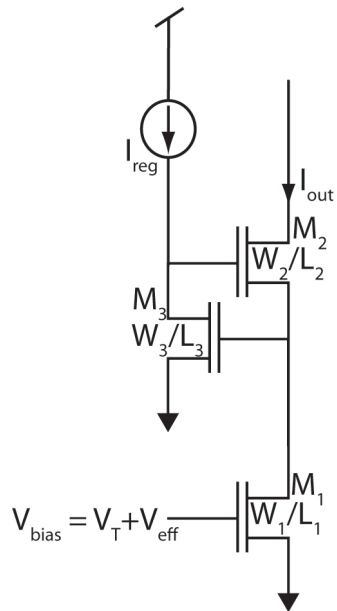


Figure 1: Figure for Problem 1

The circuit in figure 1 is called the *regulated cascode*, since the  $V_{ds1}$  of transistor  $M_1$  is regulated by the common source amplifier.

- a What is the gate voltage of transistor  $M_2$ ? Confirm your answer with an appropriate derivation.

- b Calculate the output impedance of this circuit. Assume all transistors are biased in the saturation region (*Hint*: It will be easier if you use a feedback block diagram approach)
- c What is the minimum voltage the o/p of this stage can swing to?
- d One of the problems with this circuit is that  $V_{ds1}$  needs to be at least  $V_T + V_{eff3}$ , one of your friends suggest that why don't you change the current in the common source to operate in the subthreshold thereby enabling  $V_{ds1} < V_T$ , will this work? If so are there any problems with this circuit?

**Problem 2** One of the problems of the regulated cascode was the o/p swing.

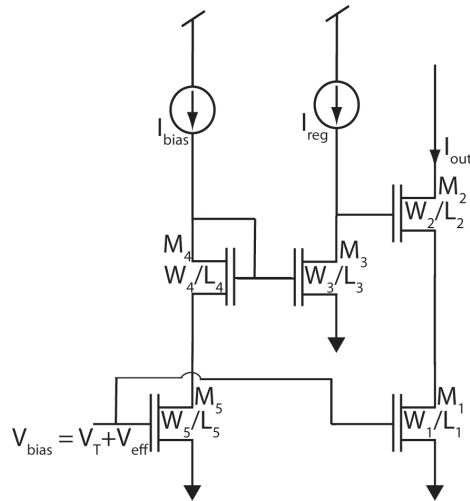


Figure 2: Figure for Problem 2

Your friend Smar T. Pants comes up with the circuit shown in figure 2. While you were looking at his notes in Goleta beach park, the sheet which has the explanation of how the circuit works, the size and current relationships gets swept by a gust of wind into the ocean. You decide that you would like to figure out how the circuit works and how to size it.

- a Give a *qualitative* description of how the circuit works
- b Assume that transistor  $M_1$  and  $M_2$  are sized the same. One of the supposed advantages of this circuits is that it gives the maximum output swing i.e.  $2V_{eff}$  from each supply rail. From your knowledge of current mirror design
- what is the gate voltage of transistor  $M_2$  have to be for this to be satisfied?



- b Assume that  $I_1$  and  $I_2$  are now operated above threshold, calculate  $I_{out}$ .
- c From your answers to a & b how does the circuit behave according to you.

**Problem 4**

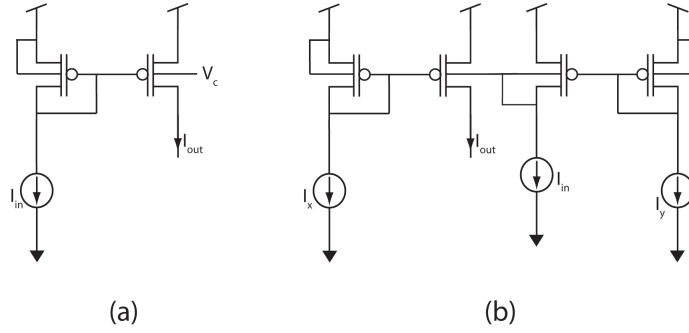


Figure 4: Figure for problem 4

Consider the circuit shown in figure 4(a), assume that all the transistors operate in the subthreshold regime i.e. the input current is a subthreshold current.

- a Calculate  $I_{out}$  as a function of  $I_{in}$  and  $V_c$ .
- b Consider the circuit shown in figure 4(b) Using your answer from (a) derive a relationship between  $I_{out}$ ,  $I_x$ ,  $I_y$  and  $I_{in}$ .
- c Would these circuits work similarly in the above threshold regime? Explain
- d Are there any precautions that must be taken when operating this circuit?