

**ECE 137 A Mid-Term Exam**

**Thursday February 6, 2014**

Do not open exam until instructed to.

Closed book: Crib sheet and 1 page personal notes permitted

There are 2 problems on this exam, and you have 75 minutes.


Use any and all reasonable approximations (5% accuracy is fine.) , **AFTER STATING and approximately Justifying them.**

Name: Solution I

Part	Points Received	Points Possible
1a	7	
1b	7	
1c	6	
1d	15	
1e	15	
1f	6	
1g	14	
2a	12	
2b	13	
2c	5	
TOTAL	100	

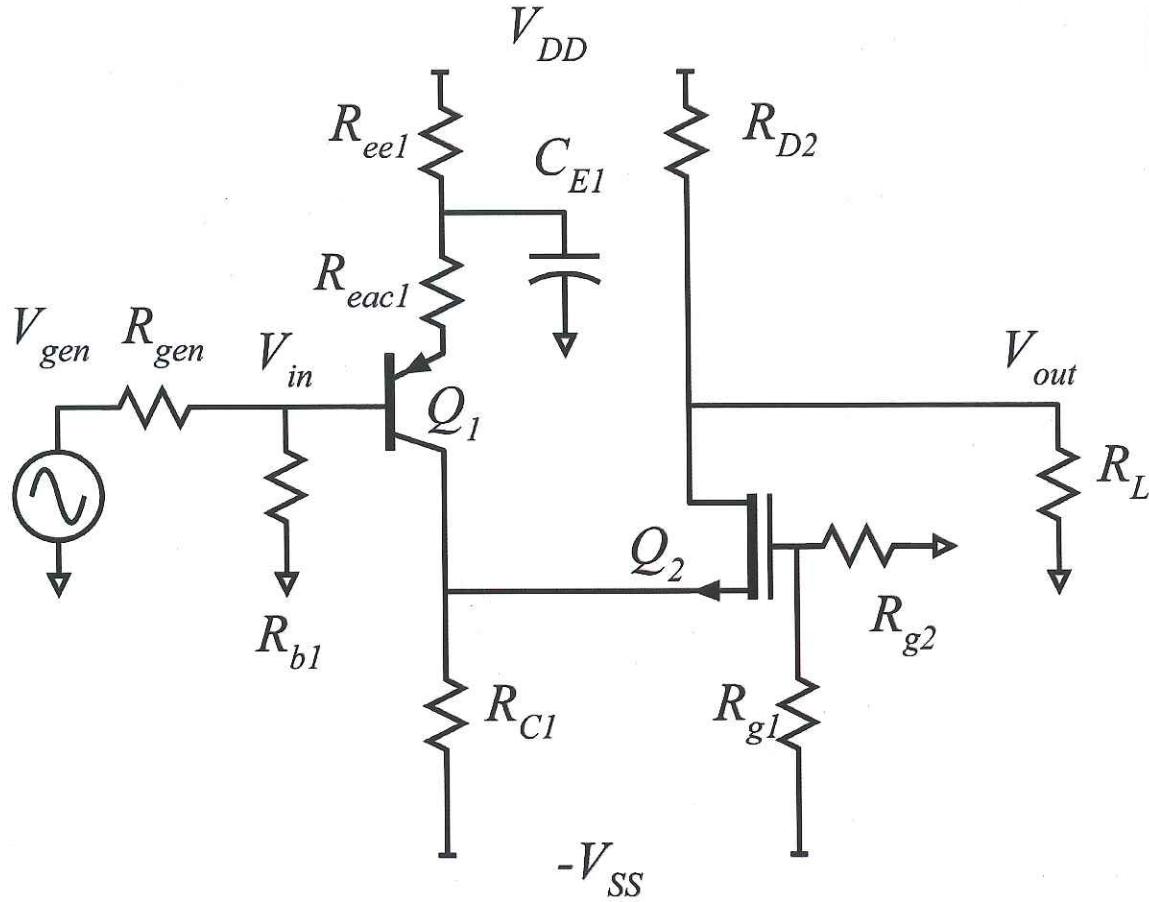**Problem 1, 70 points**

You will be working on the circuit below:



$$Q1: \beta = 100, V_A = 100 \text{ V}$$

$$Q2: \text{Velocity-limited } V_{th} = 0.2V, 1/\lambda = \text{infinity}, \Delta V = L_g v_{th} / \mu = 0.1V, c_{ox} v_{th} W_g = 5\text{mA/V}$$

The supplies are +3V and -3 V

Rgen=1000 Ohms, RL=10,000 Ohms, Rg2=100kOhms, Reac1=74 Ohms, Rb1=10kOhms  
Ce1 is very large (AC short-circuit)

Part a, 7 points

DC bias.

$V_{in}$  is at (approximately) zero volts DC.

The gate of Q2 is to be biased at -1.5 Volts

The drain is to be biased at zero volts.

Q1 is to be biased at 1 mA emitter current

Q2 is to be biased at 2 mA drain current.

Find the following:

$$R_{c1} = \underline{267\Omega} \quad R_{g1} = \underline{100k\Omega} \quad R_{e1} = \underline{2.26k\Omega}$$

$$R_{g1} = \underline{100k\Omega}$$

$$\begin{aligned} \textcircled{1} \quad & \left[ \begin{aligned} I_{D2} &= 2 \text{mA} = (5 \text{mA/V}) (V_{GS1} - V_{th} - \Delta V) \\ 2 \text{mA} &= (5 \text{mA/V}) (V_{GS1} - 0.2V - 0.1V) \\ V_{GS1} &= 0.2V + 0.1V + 2 \text{mA}/(5 \text{mA/V}) = 0.7V \end{aligned} \right] \\ \textcircled{1} \rightarrow & V_{S1} = -0.7V - 1.5V = \underline{-2.2V} \end{aligned}$$

$$\begin{aligned} \textcircled{1} \quad & \left[ \begin{aligned} R_{c1} &\text{ carries } 3 \text{mA } (I_{c1} + I_{D2}) \\ R_{c1} &= \frac{3V - 2.2V}{3 \text{mA}} = 267\Omega. \end{aligned} \right] \end{aligned}$$

$$\textcircled{1} \quad \underline{\text{Base of Q1 @ } 0 \text{V} \rightarrow V_{B1} \approx 0.7V}$$

$$\textcircled{1} \quad \underline{R_{e1} = \frac{3V - 0.7V}{1 \text{mA}} - R_{eaci} = 2.3k\Omega - 74\Omega = 2.226k\Omega}$$

$$\textcircled{1} \quad \underline{R_{D2} = \frac{3V - 0V}{2 \text{mA}} = 1.5k\Omega}$$

$$\textcircled{1} \quad \underline{R_{g2} \text{ carries } 1.5V/100k\Omega = 15 \mu A}$$

$$\textcircled{1} \quad \underline{R_{g1} = \frac{3V - 1.5V}{15 \mu A} = 100k\Omega.}$$


$$\alpha_2 : V_{TL} = 0.2V \quad I = 0, \quad \Delta V = 0.1V$$

~~$\frac{5mA}{V}$~~

$$Q_1 : \beta = 100, \quad V_A = 100V$$

Part b, 7 points

DC bias

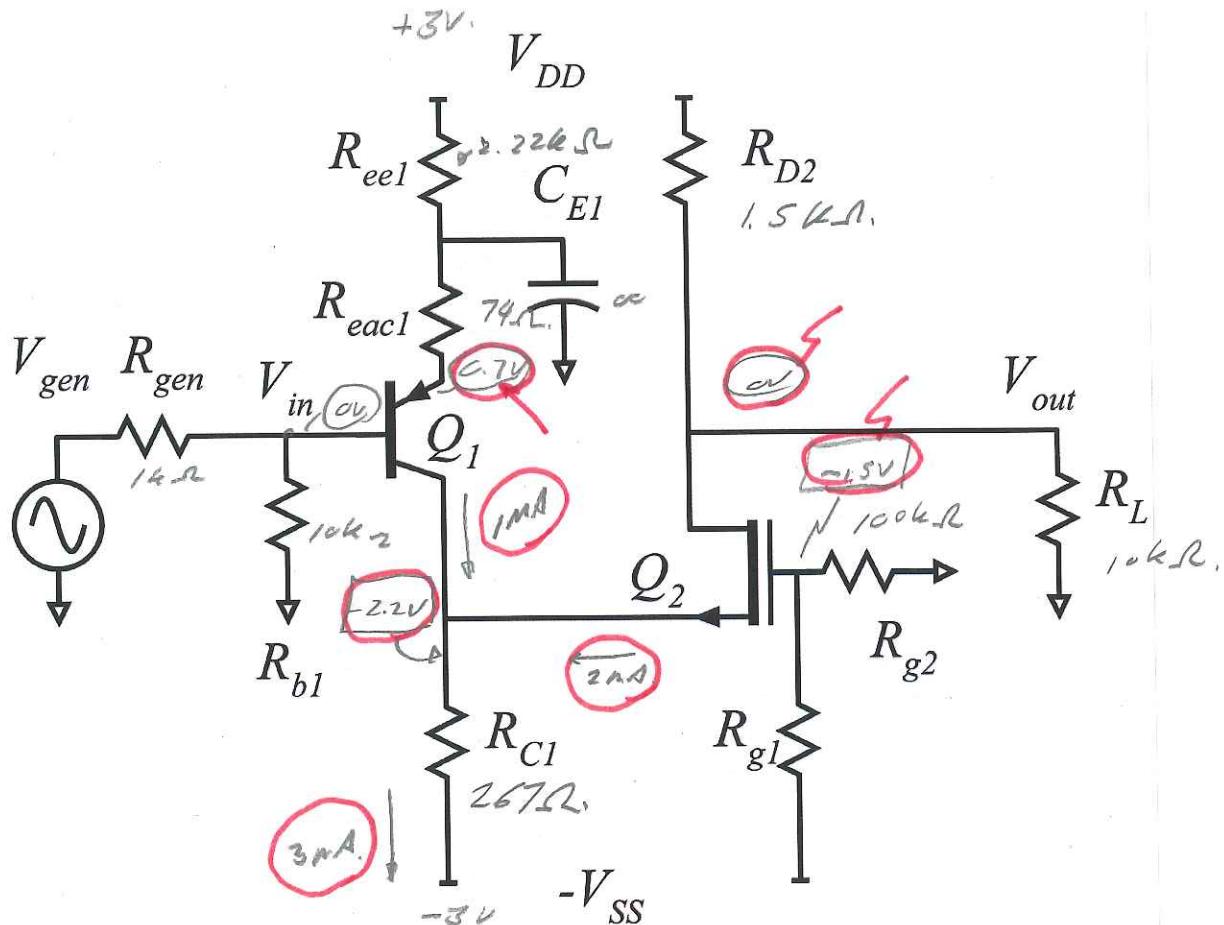

On the circuit diagram above, label the DC voltages at **ALL** nodes and the DC currents through **ALL** resistors

Part c, 6 points

Find the small signal parameters of Q1 and Q2.

Transistor Q1:  $gm = \frac{38.5mS}{1mA}$   $R_{ce} = 100k\Omega$   $R_{be} = 2.6k\Omega$

Transistor Q2:  $gm = \frac{5mS}{1mA}$   $R_{ds} = \infty \Omega$

Q1:  $I_C = 1mA$ ,  $V_A = 100V$ ,  $\beta = 100$

1.5  $[g_m = \frac{1mA}{26mV} = 38.5mS = \frac{1}{26\Omega}]$

1.5  $[R_{se} = \beta/g_m = 100 \cdot 26\Omega = 2.6k\Omega]$

1.  $[R_{ce} = \frac{V_{CE} + V_A}{I_C} \approx \frac{V_A}{I_C} = \frac{100V}{1mA} = 100k\Omega]$

Q2:  $I_D = 2mA$  velocity limited

1.  $[g_m = 5mS/V]$

1.  $[R_{ds} = \infty \text{ because } \lambda = 0V^{-1}]$

Part d, 15 points.

Find the small signal voltage gain ( $V_{d2}/V_{s2}$ ) of Q2 and Q2's small-signal input resistance.

$$V_{d2}/V_{s2} = \underline{+6.5.}$$

$$R_{in,q2} = \underline{200\Omega.}$$

3.5 [Q2: common-gate.

3.5 [Because  $R_{DSS} = \infty$ ,  $R_{in2} = 1/g_m2 = \frac{1}{5ms} = 200\Omega$ .

3.5 [ $R_{Leq2} = R_{D2} \parallel R_L = 1.5k\Omega \parallel 10k\Omega = 1.3k\Omega$

$$3.5 \left[ \frac{V_{d2}}{V_{s2}} = \frac{R_{Leq2}}{R_{in2}} = \frac{1.3k\Omega}{200\Omega} = 6.5 \right]$$

Part e, 15 points

Find the small signal voltage gain ( $V_{c1}/V_{b1}$ ) of Q1 and the \*\*\* amplifier \*\*\* input resistance.

$$V_{c1}/V_{b1} = \underline{-1.14}$$

$$R_{in, \text{amplifier}} = \underline{5k\Omega}$$

2 [Q1  $\rightarrow$  common-emitter with degeneration]

$$1/g_m = 26\Omega, R_{eqc} = 74\Omega$$

$$2 [R_{out, d1} = R_{ce}(1 + g_m R_{eqc}) = 100\Omega(1 + 74/26\Omega)] \\ = \underbrace{\text{very large}}_{\downarrow}, \text{can neglect.}$$

$$3 [R_{eq1} = R_{c1} \parallel R_{in2} \parallel R_{out2}] \\ \approx 267\Omega \parallel 200\Omega = 114\Omega$$

$$3 [A_{v1} = -\frac{R_{eq}}{r_{eqc} + 1/g_m} = -\frac{114\Omega}{26\Omega + 74\Omega} = -1.14]$$

$$3 [R_{in1} = \beta(1/g_m + R_{eqc}) = 100 \cdot (74\Omega + 26\Omega) \\ = 10,000\Omega]$$

$$2 [R_{inA} = R_0 \parallel R_{in1} = 10k\Omega \parallel 10k\Omega = 5k\Omega]$$

Part f, 6 points

Find  $(V_{out}/V_{in})$ ,  $(V_{in}/V_{gen})$  and  $(V_{out}/V_{gen})$

$$(V_{out}/V_{in}) = \underline{-7.41}$$

$$(V_{in}/V_{gen}) = \underline{0.833}$$

$$(V_{out}/V_{gen}) = \underline{-6.17}$$

2

$$\left[ \frac{V_{in}/V_{gen}}{V_{out}/V_{in}} = \frac{R_{in} + R_{ga}}{R_{out}} = \frac{5k\Omega}{5k\Omega + 1k\Omega} = 0.833 \right]$$

2

$$\left[ V_{out}/V_{in} = A_{v1} A_{v2} = -1.14 \cdot 6.5 = -7.41 \right]$$

2

$$\left[ \begin{aligned} V_{in}/V_{gen} &= V_{out}/V_{in} \cdot V_{in}/V_{gen} \\ &= -7.41 \cdot 0.833 \\ &= -6.17 \end{aligned} \right]$$

Part g, 14 points

Now you must find the maximum signal swings. Find the output voltage due to saturation and cutoff in Q2. Give the sign (+ or -) in your answers below.

Cutoff of Q1; Maximum  $\Delta V_{out}$  resulting = - 0.741V.

Saturation of Q1; Maximum  $\Delta V_{out}$  resulting = + 15.6V

Cutoff of Q2; Maximum  $\Delta V_{out}$  resulting = + 2.6V.

Knee voltage of Q2; Maximum  $\Delta V_{out}$  resulting = - 2.1V.

Note:  $A_{v2} = +6.5$

Cutoff Q1:

$$1 [ \Delta I_{C1\max} = 1mA - 0mA = 1mA \text{ (decrease)} ]$$

$$1 [ R_{Ceq1} = 114 \Omega ]$$

$$1 [ \Delta V_{C1\max} = 1mA \cdot 114\Omega = 114mV, \text{ negative-going} ]$$

$$1 [ \Delta V_{out} = 114mV \cdot A_{v2} = 114mV \cdot (6.5) = 7.40741V ]$$

Saturation of Q1

$$1 [ V_{CEQ} = 0.7V + 2.2V = 2.9V, V_{CEsat} \approx 0.5V ]$$

$$1 [ \Delta V_{CE\max} = 2.4V; \text{ neglecting } \Delta V_E, \Delta V_{C1\max} = 2.4V ]$$

$$1 [ \Delta V_{out} = 2.4V \cdot (6.5) = +15.6V ]$$

Cutoff Q2

$$1.5 [ I_{DQ2} = 2mA, \Rightarrow \Delta I_{D\max} = 2mA \text{ (decrease)} ]$$


$$2 [ \Delta V_{out} = 2mA \cdot R_{Ceq2} = 2mA \cdot 1.3k\Omega = 2.6V ]$$

Knee Q2

$$1 [ V_{DSQ} = 2.2V, \Delta V_{D\max} = 0.1V \cdot (\text{velocity-saturated}) ]$$

$$1 [ \Delta V_{DS} \approx \Delta V_{out} = 2.1V ]$$

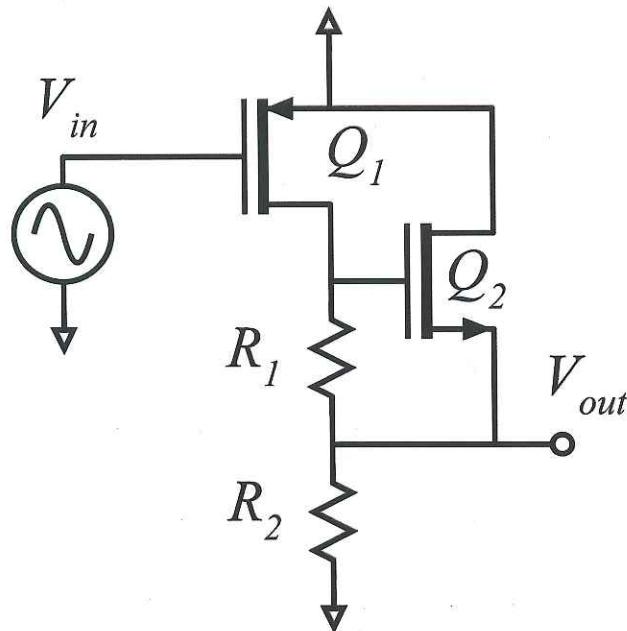**Problem 2, 30 points**  
**nodal analysis**



You will be working on the circuit to the left.

Ignore DC bias analysis. You don't need it.


Transistor 1 has transconductance  $gm_1$ .

Transistor 2 has transconductance  $gm_2$ .

The drain-source resistances  $R_{ds}$  of both transistors are infinity (so you don't need to draw it!)

Part a, 12 points

Draw the small-signal equivalent circuit

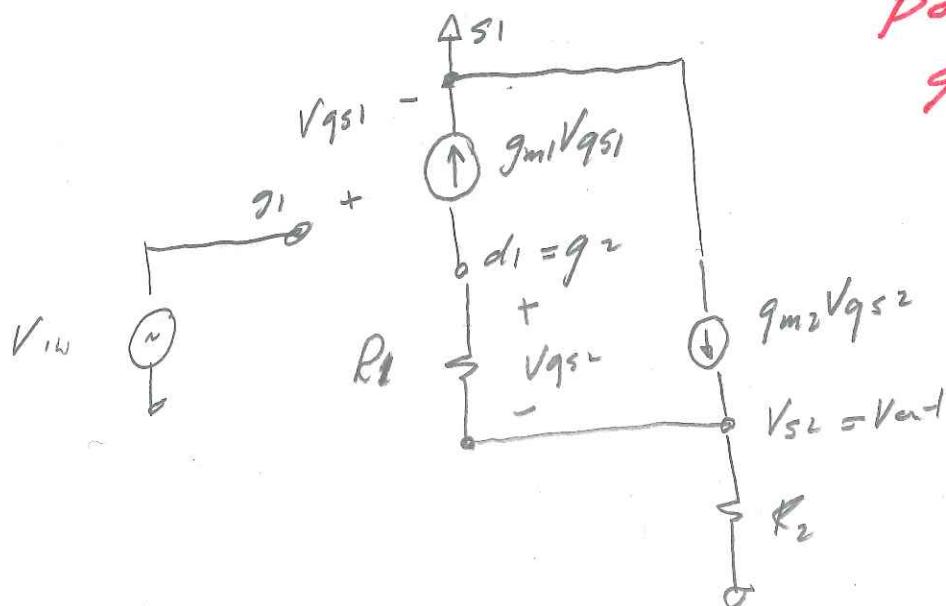

points off if  
 $gm$  generators are  
 not labelled  
 or controlling voltage  
 not identified

Part b, 13 points

Find, by nodal analysis, a small-signal expression for  $V_{out}/V_{in}$ .

$$V_{out}/V_{in} = \underline{\hspace{10mm}}$$

there are two unknowns:  $V_{d1} = V_{g2}$  and  $V_{out}$ .

$$\sum I = 0 \text{ @ } V_{g2} \quad (+ = \text{leaving})$$

$$4 \left[ + g_{m1} V_{g2} + (V_{g2} - V_{out}) / R_2 = 0 \right]$$

$$+ g_{m1} (V_{in}) + V_{g2} / R_2 - V_{out} / R_2 = 0$$

$$\boxed{V_{g2} (-1/R_2) + V_{out} (1/R_2) = -g_{m1} V_{in}}$$

$$\sum I = 0 \text{ @ } V_{out} \quad (+ = \text{leaving})$$

$$4 \left[ (V_{out} - V_{g2}) / R_2 + V_{out} / R_2 - g_{m2} V_{g2} = 0 \right]$$

$$(V_{out} - V_{g2}) / R_1 + V_{out} / R_2 - g_{m2} (V_{g2} - V_{out}) = 0$$

$$\boxed{V_{g2} (-1/R_1 + g_{m2}) + V_{out} (1/R_1 + 1/R_2 + g_{m2}) = 0}$$

$$\begin{bmatrix} 1/R_1 & -1/R_1 \\ -1/R_1 - q_{m2} & 1/R_1 + 1/R_2 + q_{m2} \end{bmatrix} V_{out} = \begin{bmatrix} -q_{m1} \\ 0 \end{bmatrix} V_{in}$$

so  $\frac{V_{out}}{V_{in}} = \frac{N}{D}$  where

$$D = \begin{vmatrix} 1/R_1 & -1/R_1 \\ -1/R_1 - q_{m2} & 1/R_1 + 1/R_2 + q_{m2} \end{vmatrix}$$

$$= (1/R_1)(1/R_1 + 1/R_2 + q_{m2}) - (1/R_1)(-1/R_1 - q_{m2})$$

$$N = \begin{vmatrix} 1/R_1 & -q_{m1} \\ -1/R_1 - q_{m2} & 0 \end{vmatrix} = -q_{m1}(1/R_1 + q_{m2})$$

$$\frac{V_{out}}{V_{in}} = \frac{-q_{m1}(1/R_1 + q_{m2})R_1}{(1/R_1 + 1/R_2 + q_{m2}) - (1/R_1 + q_{m2})}$$

$$\boxed{\frac{V_{out}}{V_{in}} = -q_{m1}(1 + q_{m2}R_1)R_2} \leftarrow s.$$

Part c, 5 points

$gm_1 = 1 \text{ mS}$     $gm_2 = 10 \text{ mS}$  ,  $R_1 = 1\text{k}\Omega$ ,  $R_2 = 2\text{k}\Omega$   
Give a numerical value for  $V_{out}/V_{in}$ .

$V_{out}/V_{in} = \underline{-22.}$

$$\begin{aligned} \frac{V_{out}}{V_{in}} &= -1\text{mS} (1 + 10\text{mS} \cdot 1\text{k}\Omega) 2\text{k}\Omega \\ &= -1\text{mS} (11) 2\text{k}\Omega \\ &= -11\text{mS} \cdot 2\text{k}\Omega \\ &= -22 \end{aligned}$$