

Final Exam, ECE 137A

Wednesday March 19, 2014 7:30-10:30 PM

Name: Solafon B.

Closed Book Exam: Class Crib-Sheet and 3 pages (6 surfaces) of student notes permitted
 Do not open this exam until instructed to do so. Use any and all reasonable approximations (5% accuracy), *after stating & justifying them.*

Show your work:

Full credit will not be given for correct answers if supporting work is missing.


Good luck

Time function	LaPlace Transform
$\delta(t)$ impulse	1
$U(t)$ unit step-function	$1/s$
$e^{-\alpha t} U(t)$	$\frac{1}{s + \alpha}$
$e^{-\alpha t} \cos(\omega_d t) U(t)$	$\frac{s + \alpha}{(s + \alpha)^2 + \omega_d^2}$
$e^{-\alpha t} \sin(\omega_d t) U(t)$	$\frac{\omega_d}{(s + \alpha)^2 + \omega_d^2}$

Part	Points Received	Points Possible	Part	Points Received	Points Possible
1a		5	2c		15
1b		6	2d		10
1c		4	3a		7
1d		10	3b		8
1e		10	3c		7
2a		10	3d		8
2b		10			
total		100			

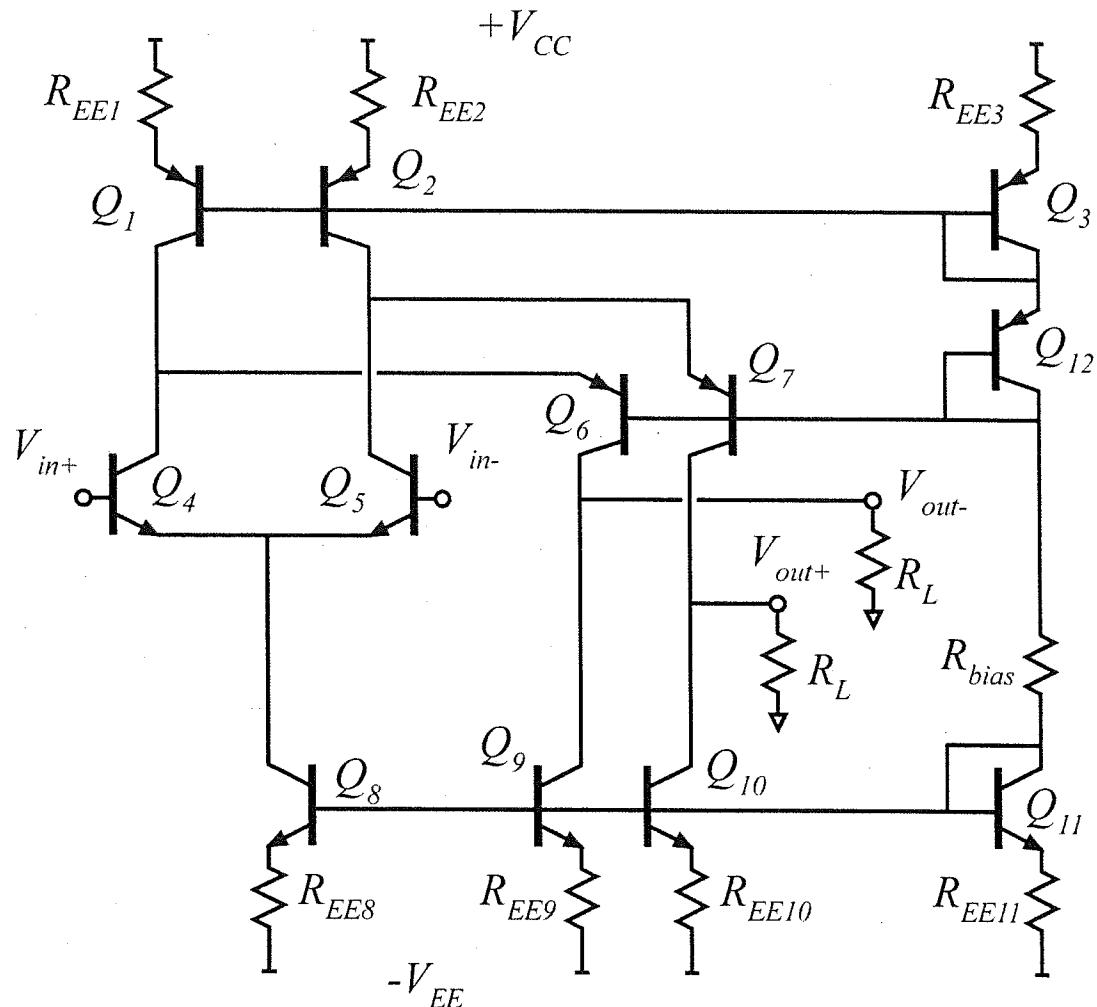Problem 1, 35 points

This is an NOT an Op-Amp: Analyze under the assumption that the differential and common mode input voltages are at zero volts



All the transistors have the same (matched) I_S , have $\beta = \infty$, and $V_A = \infty$ Volts .


$V_{CE(sat)} = 0.5V$. V_{be} is roughly 0.7 V, but use $V_{be} = (kT/q) \ln(I_E / I_S)$ when necessary and appropriate. The supplies are +4.5 Volts and -4.5 Volts. The DC voltage drops across R_{EE3} and R_{EE11} are both 500mV.

The DC collector currents of $Q_3, 4, 5, 6, 7, 11, 12$ are all 2.0 mA. $R_L = 250\Omega$

• 1/3 pt each.

Part a, 5 points

DC bias:

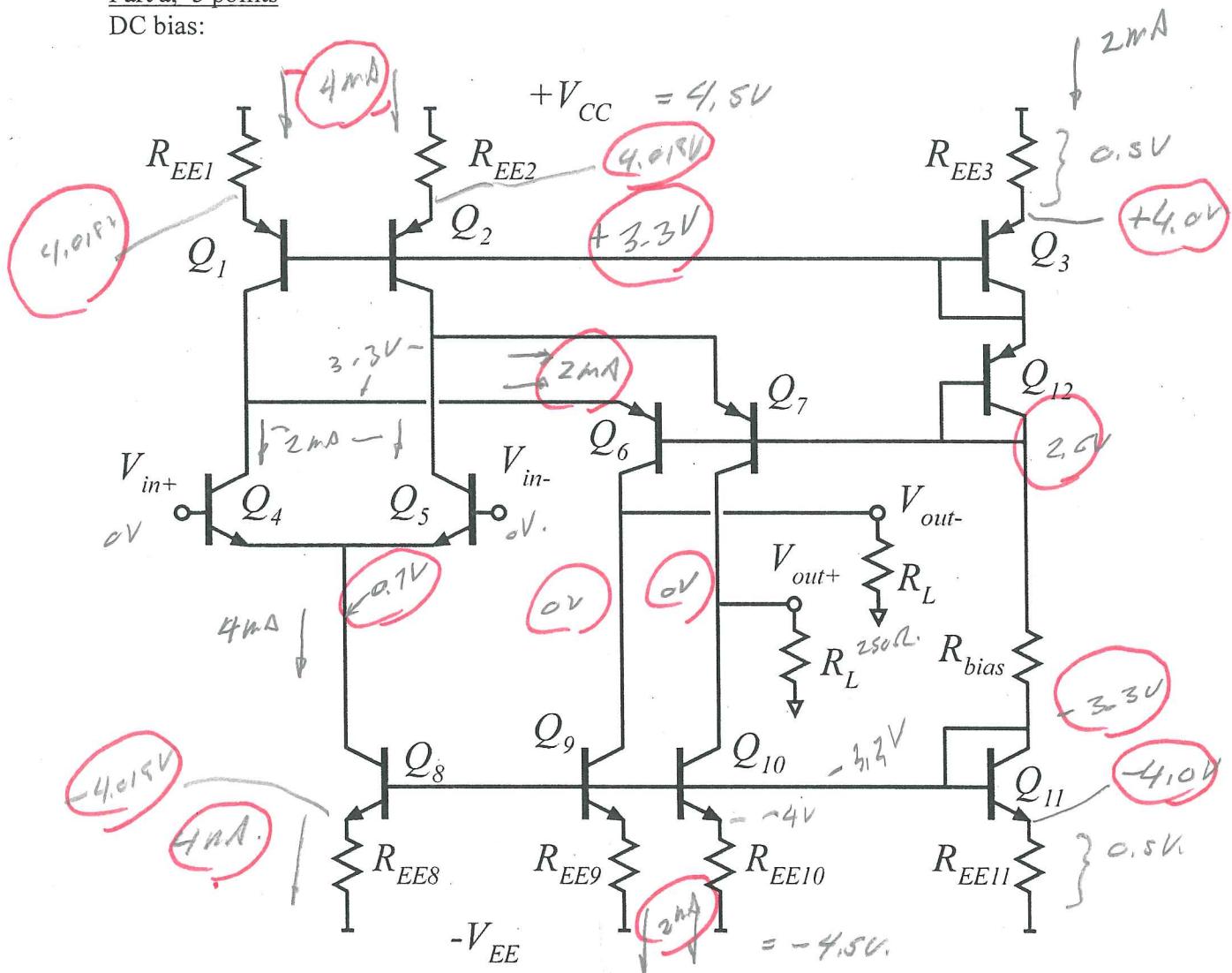

On the circuit diagram above, label the DC voltages at ALL nodes, the DC currents through ALL resistors, and the DC drain currents of all transistors.

note that $V_{BE9} = V_{BE10} = V_{SE11} = 0.5V$] 0.5

note that $V_{BE8} = V_{SD11} + V_{Thn(2)} = 0.7V + 18mV$.] 1

→ Drop across R_{EE8} is 500mV - 18mV = 482mV] 0.5

Note that $V_{BE1} = V_{BE2} = V_{BE3} + V_{Thn(2)} = 0.7V + 18mV$.] 1

Drops across R_{EE1,2} are 482mV.] 0.5

Part a total

Part b, 6 points

DC bias:

Find the value of all resistors.

$$R_{bias} = \frac{2.95\text{mV}}{170\mu\text{A}} \quad R_{ee1} = \frac{120\Omega}{170\mu\text{A}} \quad R_{ee2} = \frac{120\Omega}{170\mu\text{A}} \quad R_{ee3} = \frac{250\Omega}{170\mu\text{A}}$$
$$R_{ee8} = \frac{170\Omega}{170\mu\text{A}} \quad R_{ee9} = \frac{250\Omega}{170\mu\text{A}} \quad R_{ee10} = \frac{250\Omega}{170\mu\text{A}} \quad R_{ee11} = \frac{250\Omega}{170\mu\text{A}}$$

$$R_{EE1} = 5.9V / 2mA = 2.95k\Omega \quad] 0.5$$

$$R_{EE1} = R_{EE2} = 482mV / 4mA = 120.5\Omega \quad] 0.5$$

$$R_{EE3} = 0.5V / 2mA = 250\Omega \quad] 0.5$$

$$R_{EE8} = R_{EE9} = 482mV / 4mA = 120.5\Omega \quad] 0.5$$

$$R_{EE11} = R_{EE9} = R_{EE10} = 0.5V / 2mA = 250\Omega \quad] 0.5$$

Part c, 4 points

Find the transconductance of the transistors below:

gm4=____ gm5=____ gm6=____ gm7=____

\Rightarrow all 76.9 mS .

$$\frac{1}{g_{m4}} = \frac{1}{g_{m5}} = \frac{1}{g_{m6}} + \frac{1}{g_{m7}} = \frac{26 \text{ mV}}{2 \text{ mV}} = 13 \Omega \quad] \text{, } 1 \text{ pF each}$$


$$1/13 \Omega = 76.9 \text{ mS}$$

Part d, 10 points.

The circuit is fully differential. Assuming a differential input signal, $V_{in,diff} = V_{i+} - V_{i-}$, and defining a differential output signal $V_{out,diff} = V_{o+} - V_{o-}$, compute the differential gain

$$A_d = V_{out,diff} / V_{in,diff}$$

$$A_d = \underline{+19.2}$$

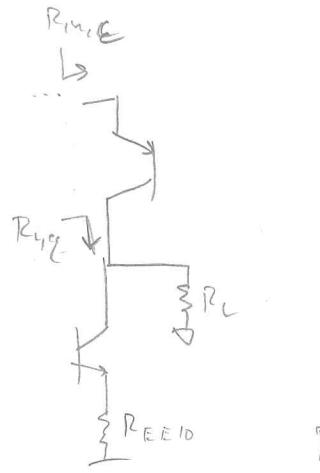

$$R_{L,eq} = R_L \parallel R_{CE} \left(1 + g_m R_{EE10} \left(\frac{r_{be}}{r_{ce} + r_{BE} + R_B} \right) \right)$$

$\Leftarrow R_L = 250\Omega$

$$A_{V,Q6} = \frac{R_L}{r_c} = g_m R_L = \frac{250\Omega}{13\Omega} = 19.2] 4$$

$$R_{in,2} = \left(r_e + \frac{r_{ce}}{\beta+1} \right) \left(\frac{r_{ce} + r_{ee}}{r_{ce}} \right) = r_e = \frac{1}{g_m}$$

$$\Rightarrow A_{V,Q7} = -g_m \cdot R_{Q7} = -\frac{g_{m,qs}}{g_{m,Q7}} = -1] 4$$


$$A_{V,1,0+} = -A_{V,1,Q4} \cdot A_{V,1,ab} = +19.2] 2$$

Part e, 10 points

Maximum peak-peak output voltage at the positive output V_{o+} (*show all your work*)

	magnitude and sign of maximum output signal swing due to <i>cutoff</i>	magnitude and sign of maximum output signal swing due to <i>saturation</i>
Transistor Q1	N/A (current mirror)] 1	$-3.84V$] 2
Transistor Q4	$-500mV$] 2	$+67.2V$] 1
Transistor Q6	$+500mV$] 1	$-2.8V$] 1
Transistor Q9	N/A (current mirror)] 1	$+3.5V$] 1

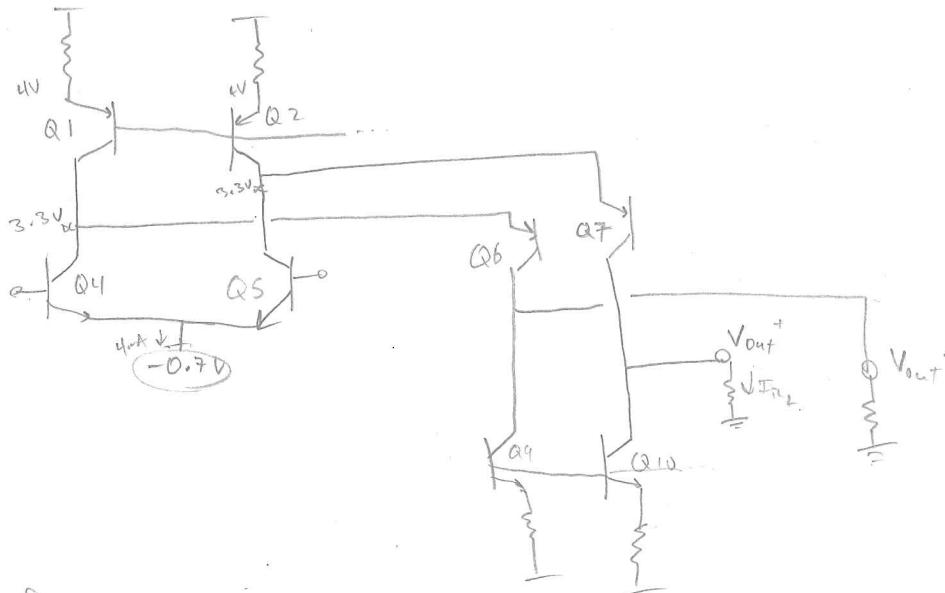Be warned: In some cases a limit is not relevant at all. Mark those answers "not relevant". But, give a 1-sentence statement below as to why it is not relevant.



Cutoff

$$Q4: I_{c,4} = 0mA \Rightarrow I_{c,5} = 4mA \Rightarrow I_{c,7} = 0mA \text{ from } 2mA$$

$$\Rightarrow V_{out}^+ = -R_L \cdot 2mA = -500mV$$

$$Q6: I_{c,6} = 0mA \Rightarrow I_{c,4} = 4mA \Rightarrow I_{c,5} = 0mA \Rightarrow I_{c,7} = 4mA \Rightarrow I_{R_L} = 2mA$$

$$\Rightarrow V_{out}^+ = (2mA) (250\Omega) = +500mV$$

Q1 & Q9: no cutoff since these are part of current mirrors.

Saturation

Q1: $V_{CQ1,a} = 0.7V$, $V_{CE1,sat} = 0.5V \Rightarrow \Delta V_{C1} = 0.2$
 $\Rightarrow \Delta V_{out, Q1 sat}^- = 0.2 \times 19.2 = 3.84V$
 $\Rightarrow \Delta V_{out, Q1 sat}^+ = -3.84V$

Q4

$V_{CQ4,a} = 4V$, $V_{CE4,sat} = 0.5V \Rightarrow \Delta V_{C4} = -3.5V$
 $\Rightarrow \Delta V_{out, Q4 sat}^- = (19.2)(-3.5V) = -67.2V$
 $\Rightarrow \Delta V_{out, Q4 sat}^+ = +67.2V$

Q6


$V_{CQ6,a} = 3.3V$, $V_{CE,sat} = 0.5V$, $V_B^{fixed} \Rightarrow |\Delta V_C| = \Delta V_U$
 $\Delta V_{C6} = +2.8V$
 $\Rightarrow \Delta V_{out, Q6 sat}^- = +2.8V \Rightarrow \Delta V_{out, Q6 sat}^+ = -2.8V$

Q9

$V_{out}^- = -3.5V \Rightarrow \Delta V_{out, Q9}^- = +3.5V$

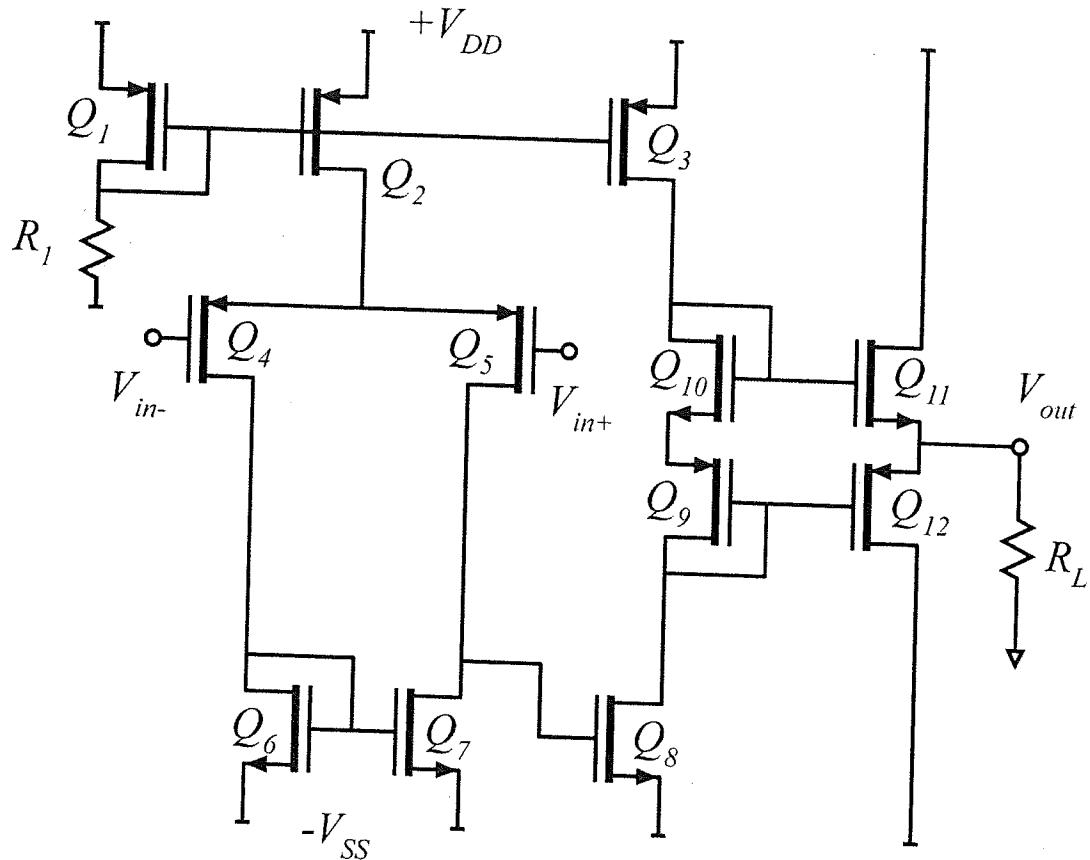Problem 2, 35 points

This is an Op-Amp---analyze the bias under the assumption that DC output voltage is zero volts, that the positive input V_{i+} is zero volts, and that we must determine the DC value of the negative input voltage (V_{i-}) necessary to obtain this.



$$\text{All NMOS: } I_D = 1(\text{mA/V})(W_g / 1\mu\text{m})(V_{gs} - V_{th} - \Delta V)(1 + \lambda V_{DS})$$

$$\Delta V = 0.1\text{V}, V_{th} = 0.2\text{V}, 1/\lambda = 5\text{V}$$

$$\text{All PMOS: Also velocity-limited, with } g_m = 0.5(\text{mA/V})(W_g / 1\mu\text{m})$$

$$\Delta V = -0.1\text{V}, V_{th} = -0.2\text{V}, 1/\lambda = 5\text{V}$$

$$V_{DD} = +1\text{ V}, -V_{SS} = -1\text{ V}, \text{ The load resistor is } R_L = 10\text{ k}\Omega$$

Part a, 10 points

DC bias.

Approximation: ignore the term $(1 + \lambda V_{DS})$ in DC bias analysis.

Analyze the bias under the assumption that DC output voltage is zero volts, that the positive input V_{i+} is zero volts, and that we must determine the DC value of the negative input voltage (V_{i-}) necessary to obtain this.

Q1 is to be biased at 0.2 mA drain current.

The transistor gate widths are as follows

Q1	Q2	Q3	Q4	Q5	Q6	Q7	Q8	Q9	Q10	Q11	Q12
2μm	4μm	4μm	2μm	2μm	1μm	1μm	2μm	4μm	2μm	10μm	20μm

Find:

$$ID_1 = \underline{0.2 \text{ mA}} \quad ID_2 = \underline{0.4 \text{ mA}} \quad ID_3 = \underline{0.4 \text{ mA}} \quad ID_4 = \underline{0.2 \text{ mA}} \quad ID_5 = \underline{0.2 \text{ mA}} \quad ID_6 = \underline{0.2 \text{ mA}} \\ ID_7 = \underline{0.2 \text{ mA}} \quad ID_8 = \underline{0.4 \text{ mA}} \quad ID_9 = \underline{0.4 \text{ mA}} \quad ID_{10} = \underline{0.4 \text{ mA}} \quad ID_{11} = \underline{2 \text{ mA}} \quad ID_{12} = \underline{2 \text{ mA}} \\ R_1 = \underline{7.5 \text{ k}\Omega}$$

$$I_{D_1} = 0.2 \text{ mA} = (0.5 \text{ mA/V}) \left(\frac{2 \mu\text{m}}{1 \mu\text{m}} \right) (|V_{as_1}| - |V_{th}| - |\Delta V|) \quad] +1 \\ |V_{as_1}| = 0.2 \text{ V} + 0.2 \text{ V} + 0.1 \text{ V} = 0.5 \text{ V}$$

$$R_1 = \frac{1.5 \text{ V}}{0.2 \text{ mA}} = 7.5 \text{ k}\Omega \quad] +1$$

$$|V_{as_2}| = |V_{as_3}| = 0.5 \text{ V}$$

$$+2 \quad [I_{D_2} = \frac{W_{g_2}}{N_{g_1}} I_{D_1} = 2 \times 0.2 \text{ mA} = 0.4 \text{ mA} = I_{D_3}] +1$$

$$+1.5 \quad [I_{D_4} = I_{D_5} = I_{D_2}/2 = 0.2 \text{ mA} = (0.5 \text{ mA/V}) \left(\frac{2 \mu\text{m}}{1 \mu\text{m}} \right) (|V_{as_4}| - |V_{th}| - |\Delta V|) \\ |V_{as_4}| = |V_{as_5}| = 0.2 \text{ V} + 0.3 \text{ V} = 0.5 \text{ V}$$

$$+1.5 \quad [I_{D_6} = I_{D_4} = I_{D_7} = I_{D_5} ; \quad W_{g_6} = \frac{1}{2} W_{g_4} ; \quad g_{m_6} = 2 g_{m_4} \\ |V_{as_6}| = |V_{as_7}| = |V_{as_4}| = |V_{as_5}| = 0.5 \text{ V}$$

$$I_{D_{10}} = \left(1 \text{ mA/V}\right) \left(\frac{2 \mu\text{m}}{1 \mu\text{m}}\right) \left(|V_{G_{S10}}| - |V_{T+}| - |\Delta V|\right) = 0.4 \text{ mA}$$

$$|V_{G_{S10}}| = 0.2 \text{ V} + 0.3 \text{ V} = 0.5 \text{ V}$$

$$W_{gq} = 2 W_{g_{10}} ; \quad g_{m_q} = \frac{1}{2} g_{m_{10}} ; \quad I_{D_{10}} = I_{D_q}$$

$$\Rightarrow |V_{G_{S10}}| = |V_{G_{S9}}|$$

$$I_{D_8} = I_{D_{10}} ; \quad W_{g_8} = W_{g_{10}} ; \quad g_{m_8} = g_{m_{10}}$$

$$\Rightarrow |V_{G_{S8}}| = |V_{G_{S10}}|$$

$$I_{D_{11}} = \left(1 \text{ mA/V}\right) \left(\frac{10 \mu\text{m}}{1 \mu\text{m}}\right) \left(0.5 \text{ V} - 0.2 \text{ V} - 0.1 \text{ V}\right) = 2 \text{ mA}$$


+2

$$I_{D_{11}} = I_{D_{12}} = 2 \text{ mA}$$

$\frac{2}{3}$ pt each

Part b, 10 points

DC bias

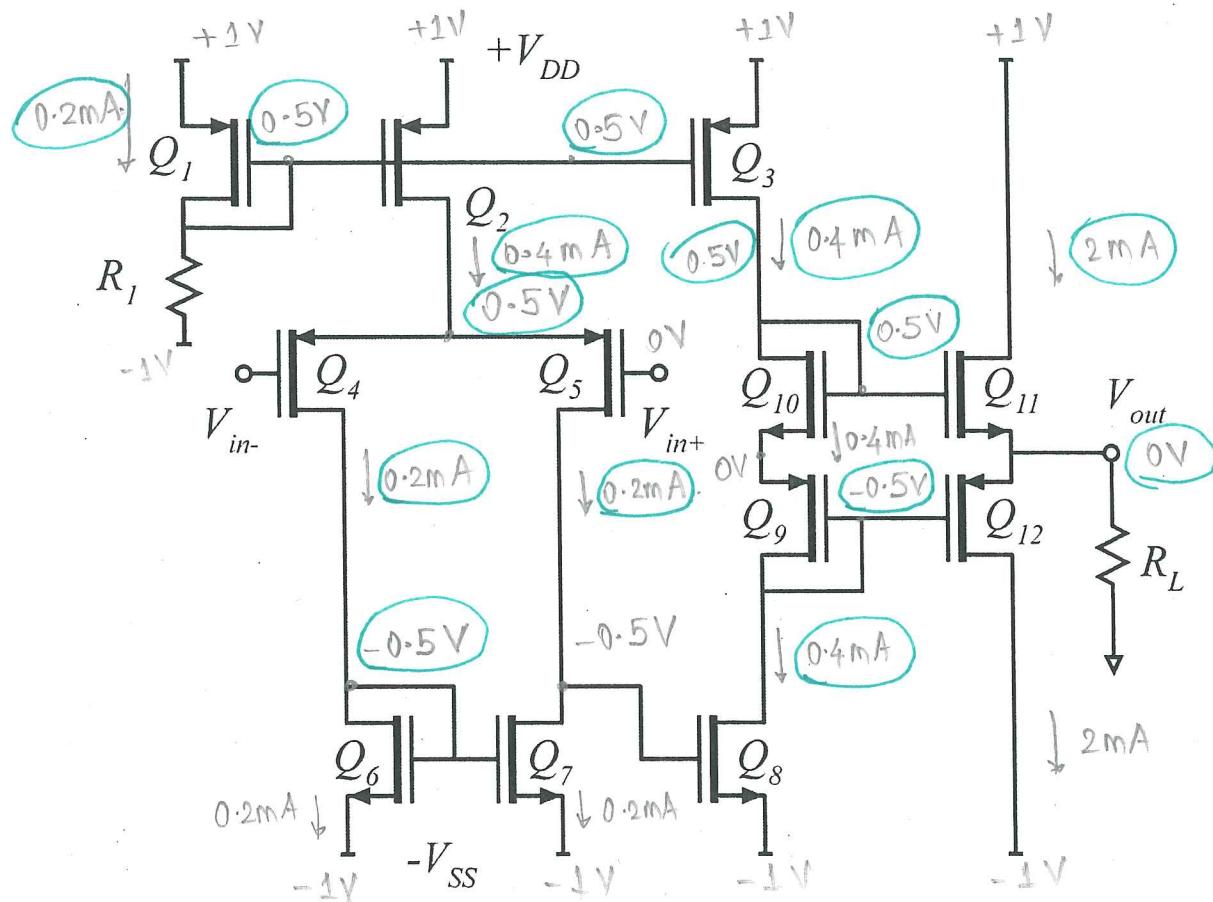


On the circuit diagram above, label the DC voltages at **ALL nodes** and the drain currents of **ALL transistors**

$$\text{Define gain : } \frac{V_{out}}{V_{in^+} - V_{in^-}}$$

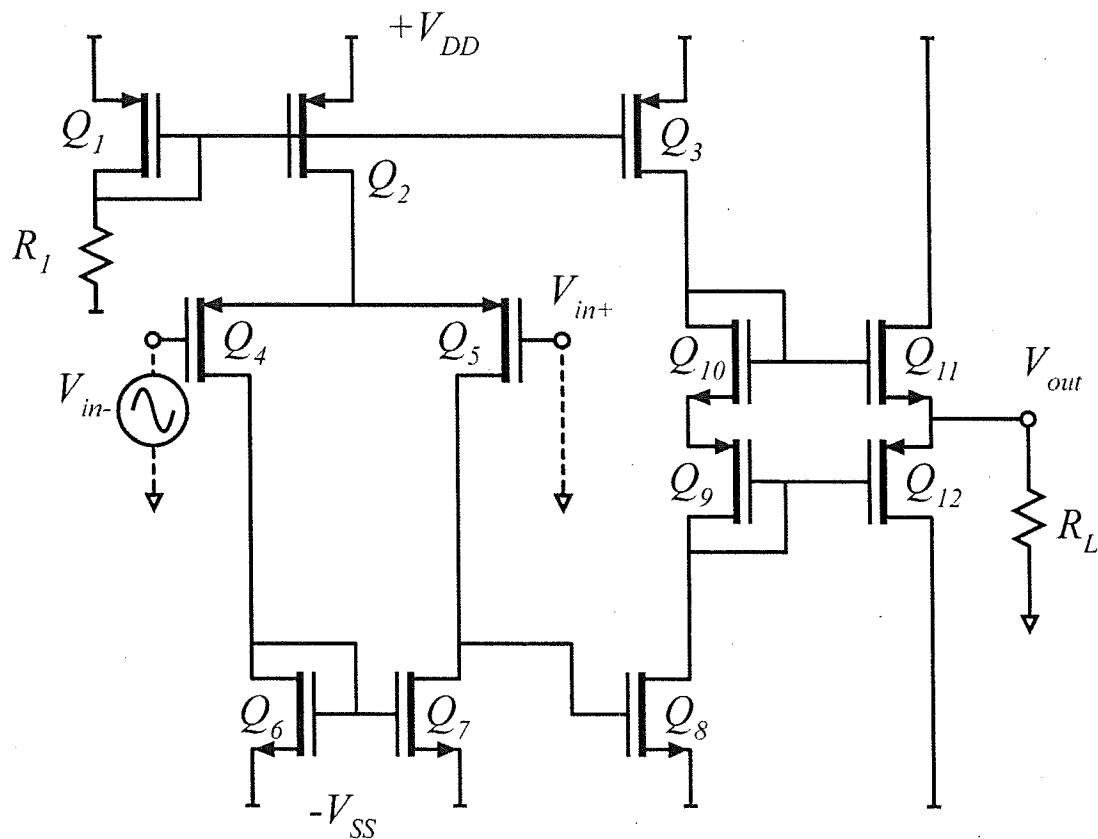Part c, 15 points.

To compute the op-amp differential gain, we will ground the positive input and apply a signal to the negative input. Assume that the DC bias conditions do not change when we do this.



Find the following

	Voltage Gain	Input impedance
Transistor combination Q4,5,6,7	- ± 15	∞ Ω
Transistor Q8	- 13.75	∞ Ω
Transistor combination Q11,12	1 (or) 0.5	∞ Ω
Overall differential Vout/Vin	- ± 103.125	∞ Ω

$A_{V,4,5,6,7}$

$$A_{V,4567} = \pm g_{m_5} R_{L_{eq}}$$

$$R_{L_{eq}} = R_{DS_7} \parallel R_{DS_5} \quad [+1.5]$$

$$R_{DS_7} = \frac{1}{2I_{DS_7}} = \frac{5V}{0.2mA} = 25k\Omega = R_{DS_5} \quad \text{[+1.5]}$$

$$R_{L_{eq}} = 12.5k\Omega$$

$$+1.5 \quad \left[g_{m_5} = (0.5mA/V) \left(\frac{2\mu m}{1\mu m} \right) \left(1 + \frac{1V}{5V} \right) = 1mS \quad (1.2) = 1.2mS \right]$$

$$A_{V,4567} = \pm 15 \quad [+1.5]$$

$A_{V,8}$

$$A_{V,8} = -g_{m_8} R_{L_{eq}}$$

$$R_{L_{eq}} = R_{DS_8} \parallel R_{DS_3}$$

$$R_{DS_8} = \frac{1}{2I_{DS_8}} = \frac{5V}{0.4mA} = 12.5k\Omega \quad [+1.5]$$

$$R_{DS_3} = R_{DS_8} = 12.5k\Omega$$

$$R_{L_{eq}} = 12.5k\Omega \parallel [12.5k\Omega]$$

$$R_{L_{eq}} = 6.25k\Omega \quad [+1.5]$$

$$g_{m_8} = (1mA/V) \left(\frac{2\mu m}{1\mu m} \right) \left(1 + \frac{0.5}{5} \right) = 2.2mS$$

$$A_{V,8} = -2.2mS \times 6.25k\Omega = -13.75 \quad [+1.5]$$

$A_{V_{11,12}}$ (Assuming Q_{11}, Q_{12} as 'ON')

$$R_{\text{Leg}} = R_L \parallel \left(\frac{1}{g_{m_{11}}} \right) \parallel (R_{DS_{11}} \parallel R_{DS_{12}})$$

$$g_{m_{11}} = (1 \text{ mA/V}) \left(\frac{10 \mu\text{m}}{1 \mu\text{m}} \right) \left(1 + \frac{1}{5} \right) = 12 \text{ mS}$$

+1.5

$$R_{DS_{11}} = \frac{1}{2 \cdot I_{D_{11}}} = \frac{5 \text{ V}}{2 \text{ mA}} = 2.5 \text{ k}\Omega = R_{DS_{12}}$$

$$R_{\text{Leg}} = 10 \text{ k}\Omega \parallel (83.3 \Omega) \parallel (1.25 \text{ k}\Omega)$$

$$R_{\text{Leg}} = 83 \Omega$$

+1.5

$$A_{V_{11,12}} = \frac{R_{\text{Leg}}}{R_{\text{Leg}} + \frac{1}{g_{m_{12}}}} = \frac{83 \Omega}{83 \Omega + 83.3 \Omega} \approx 0.5$$

+1.5

Overall gain: $A_{V_{4567}} \times A_{V_{12}} \times A_{V_{11,12}} = (\pm 15)(-13.75)(0.5)$

$$\boxed{A_{V_{\text{overall}}} = \mp 103.125}$$

+1.5

{ The difference in the value of $A_{V_{11,12}}$ comes from assuming both 11 & 12 as being 'ON' (or) either of them being 'OFF'. BOTH ARE OK

Ambiguity in the signs of the overall gain

comes from the definition of the gain for the first stage (i) wrt V_{in} signal input @ V_{in}
(ii) wrt $20(V_{in}^+ - V_{in}^-)$

Part d, 10 points (Assuming $\text{Q}_{11}, \text{Q}_{12}$ are both 'ON')

Maximum peak-peak output voltage at the positive output $V_{\text{O}+}$ (*show all your work*)
Recall that the FETs are velocity-limited, hence $V_{DS,\text{knee}} = \Delta V = 0.1\text{V}$.

	magnitude and sign of maximum output signal swing due to <i>cutoff</i>	magnitude and sign of maximum output signal swing due to: <i>knee voltage</i> (saturation)
Transistor Q3	N/A current mirror	(+0.2V↑) (0) (+0.4V↑)
Transistor Q8	(+1.25V↑) (0) (+2.5V↑)	(-0.2V↓) (0) (-0.4V↓)
Transistor Q11	(+1) N/A push-pull	+0.9V↑
Transistor Q12	(+1) N/A push-pull	-0.9V↓

Be warned: in some cases a limit is not relevant. Mark those answers "not relevant". But, give a 1-sentence statement why below.

$$\begin{aligned} \text{Q}_{11} : (\text{knee}) \quad V_{DS,Q_{11}} &= 1\text{V} \\ \Delta V_{\text{out}} &= V_{DS,Q_{11}} - \Delta V = +0.9\text{V}^{\uparrow} \end{aligned} \quad] \quad (+1)$$

$$\text{Q}_{12} : (\text{knee}) \quad \text{Same as } \text{Q}_{11} \quad] \quad (+1)$$

$$\begin{aligned} \text{Q}_8 : (\text{cutoff}) \quad I_{C_{Q_8}} &= 0.4\text{mA} \\ \Delta V_{Q_8} &= I_{C_{Q_8}} \times R_{\text{leg}} = (0.4\text{mA})(6.25\text{k}\Omega) \\ &= +2.5\uparrow \Rightarrow \Delta V_{\text{out}} = +1.25\text{V}^{\uparrow} \end{aligned}$$

$$\begin{aligned} \text{Q}_8 : (\text{knee}) \quad V_{DS,Q_8} &= 0.5\text{V} \\ \Delta V_{Q_8} &= V_{DS,Q_8} - V_{DS,\text{knee}} = 0.5\text{V} - 0.1\text{V} = 0.4\text{V}^{\downarrow} \\ \Delta V_{\text{out}} &= -0.2\text{V}^{\uparrow} \end{aligned}$$


$$Q3 : V_{DS,Q} = 0.5V$$

$$\Delta V_{DS} = 0.5V - 0.1V = 0.4V$$

$$\Delta V_{out} = +0.2V \uparrow$$


[+2]

Problem 3, 30 points

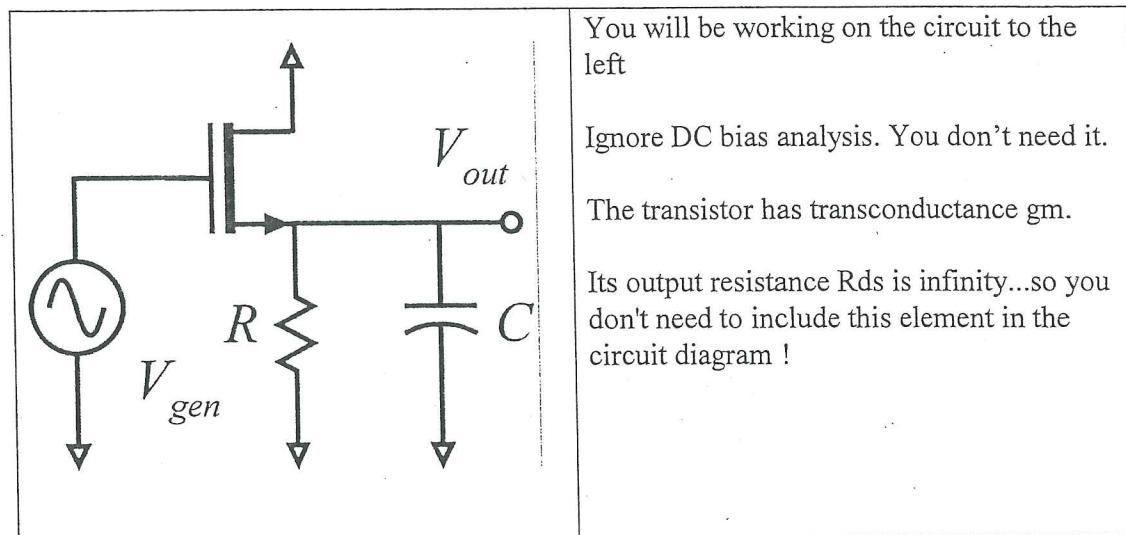

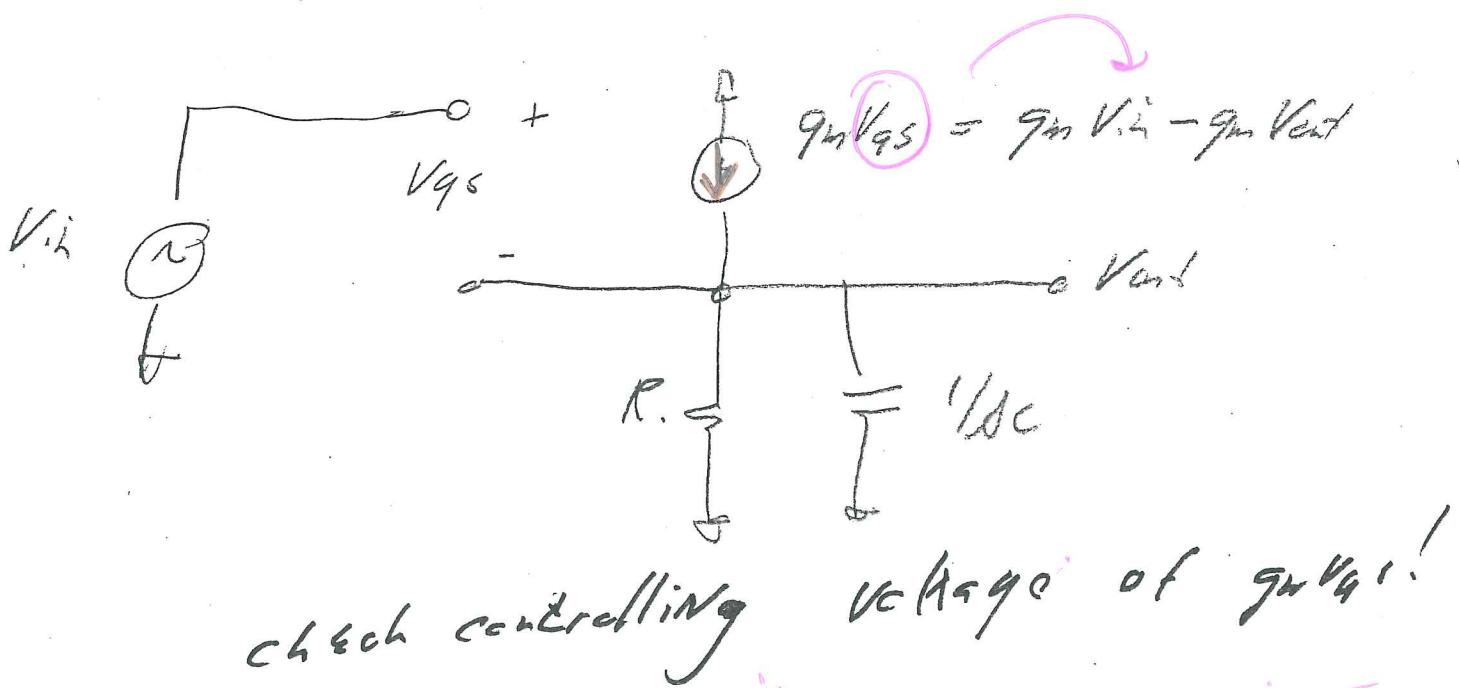Part a, 7 points

Draw a small-signal equivalent circuit of the circuit.



Part b, 8 points

gm=9 mS. C=1 nF. R= 1000 Ohms

Find, by nodal analysis, a small-signal expression for Vout/Vin. Be sure to give the answer with **correct units** and in ratio-of-polynomials form, i.e.

$$\frac{V_{out}(s)}{V_{gen}(s)} = K \cdot \frac{1 + b_1 s + b_2 s^2 + \dots}{1 + a_1 s + a_2 s^2 + \dots} \text{ or (as appropriate)} \frac{V_{out}(s)}{V_{gen}(s)} = K \cdot (s\tau)^n \cdot \frac{1 + b_1 s + b_2 s^2 + \dots}{1 + a_1 s + a_2 s^2 + \dots}$$

Note that an expression like

$$\frac{V_{out}(s)}{V_{gen}(s)} = \frac{1}{1 + (3 \cdot 10^{-6})s} \text{ is dimensionally wrong, } \frac{1}{1 + (3 \cdot 10^{-6} \text{ seconds})s} \text{ is dimensionally correct}$$

$$V_{out}(s)/V_{in}(s) = \underline{\hspace{2cm}}$$

$$\boxed{\sum I = 0 @ V_{at}}$$

$$4 \left[-g_m V_{in} + g_m V_{out} + V_{at}/R + AC \cdot V_{at} = 0 \right]$$

$$g_m V_{in} = V_{at} [g_m + 1/(R + AC)]$$

$$\frac{V_{at}}{V_{in}} = \frac{g_m}{g_m + 1/R + AC}$$

$$g_m = g_{ms} \approx 1 \text{ mS}, R_o = 1 \text{ k}\Omega$$

$C = 10^{-9} \mu\text{F}$

$$\underline{V_{out}} = \frac{\underline{g_m}}{\underline{|g_m + 1/R|}} \frac{\underline{g_m A_{MOS} + V_R}}{\underline{g_m + 1/R} + SC}$$

$$= \frac{g_m}{g_m + 1/R} \frac{1}{1 + SC(g_m + 1/R)^{-1}}$$

4

$$\Rightarrow 0.9 \cdot \frac{1}{1 + ST}$$

where $T = (1/g_{ms})10^{-9}F = 100 \text{ n} \cdot 10^{-9} \mu\text{F}$
 $\approx 10^{-7} \text{ seconds}$

$$f_0 = \frac{1}{2\pi T} \approx 1.59 \text{ MHz} \approx 1.6 \text{ MHz}$$


Part c, 7 points

Find any/all pole and zero frequencies of the transfer function, in Hz:

pole @ 10 m/s [2]

Draw a clean Bode Plot of V_{out}/V_{in} ,

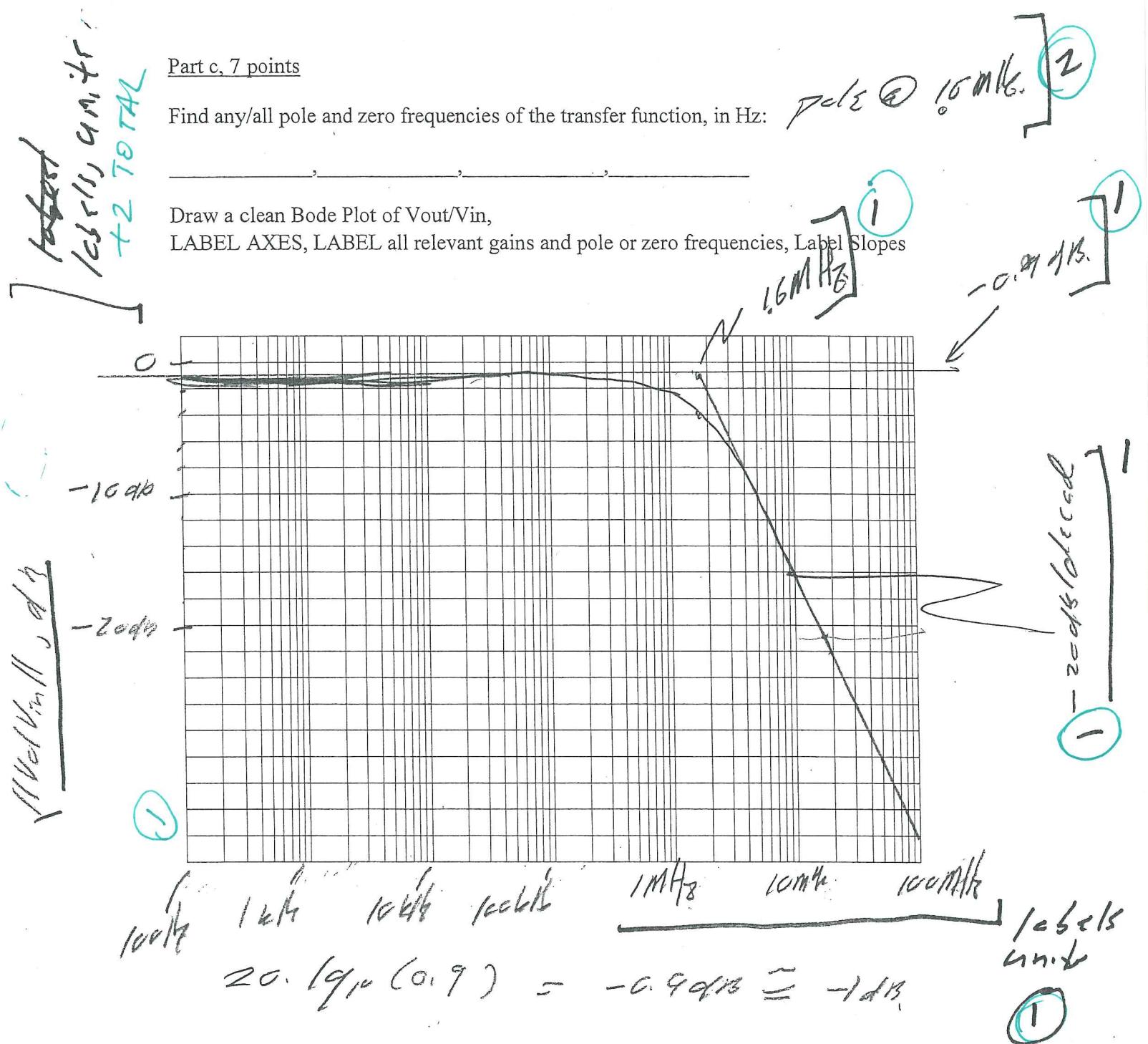LABEL AXES, LABEL all relevant gains and pole or zero frequencies, Label Slopes




100% marks

Part d, 8 points

$V_{in}(t)$ is a 0.2 V amplitude step-function.

$$\text{Find } V_{out}(t) = \underline{0.18V \cdot u(t) [1 - e^{-t/100ns}]} \quad \boxed{2}$$

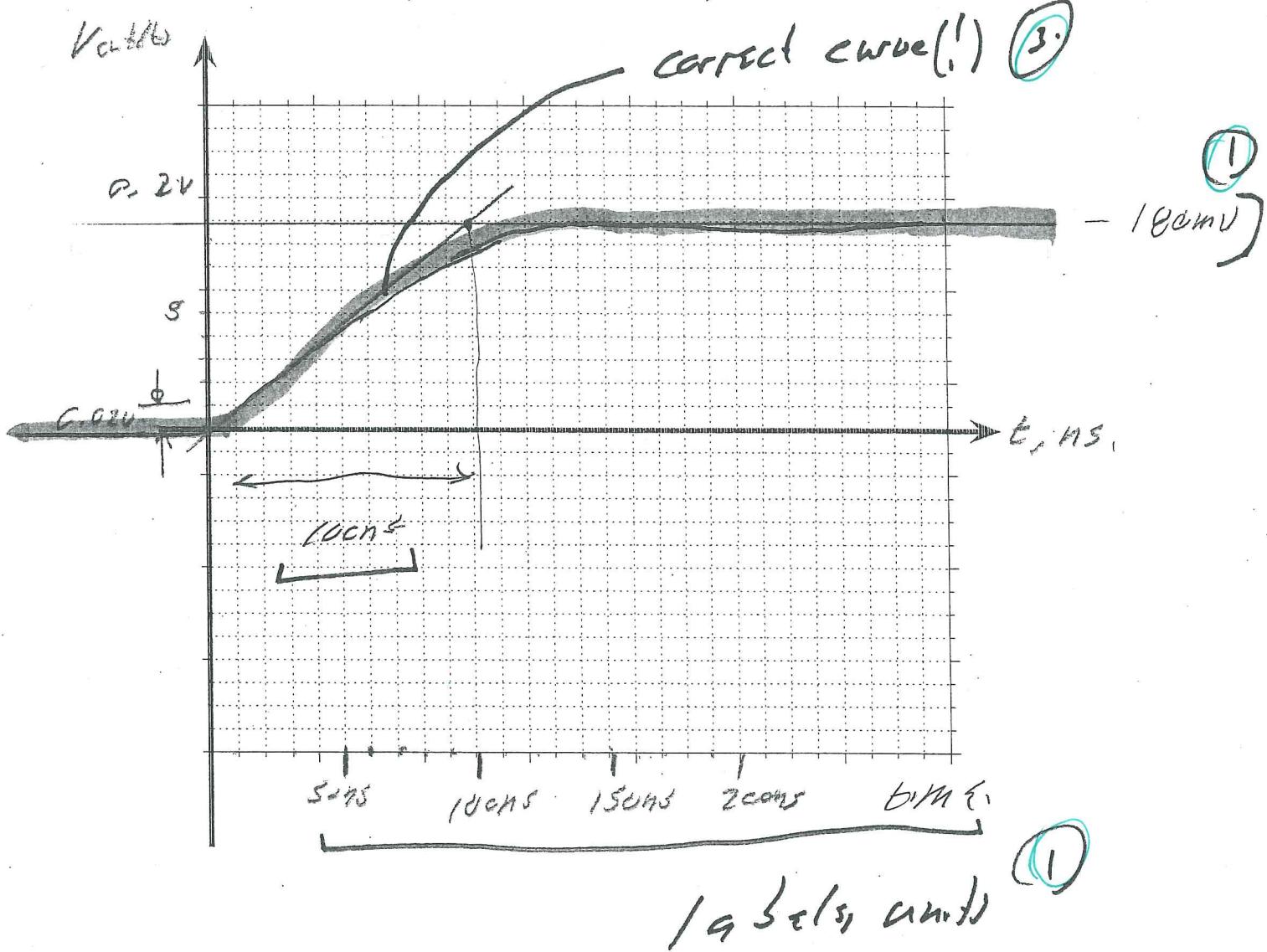Plot it below. Label axes, show initial and final values, show time constants.



$$h(s) = \frac{0.9}{1+sT} \quad \text{where } T = 10^{-7} \text{ sec}$$

$$V_{in}(s) = \frac{0.2V}{s}$$

$$V_{out}(s) = \frac{0.18V}{s} \frac{1}{1+sT}$$

$$V_{out}(t) = 0.18V \cdot 0.60 [1 - e^{-t/T}]$$

where $T = 10^{-7} \text{ sec} = 100 \text{ ns}$