

ECE 137 A Mid-Term Exam

Thursday, February 9, 2017

Do not open exam until instructed to.

Closed book: Crib sheet and 1 page personal notes permitted

There are 3 problems on this exam, and you have 75 minutes.


Use any and all reasonable approximations (5% accuracy is fine.),
AFTER STATING and approximately Justifying them.

Name: _____

Part	Points Received	Points Possible	Part	Points Received	Points Possible
1a		10	2f		15
1b		5	3a		8
1c		5	3b		8
1d		10	3c		4
1e		15			
2a		10			
2b		5			
2c		5			
2d		10			
2e		5			
TOTAL					100

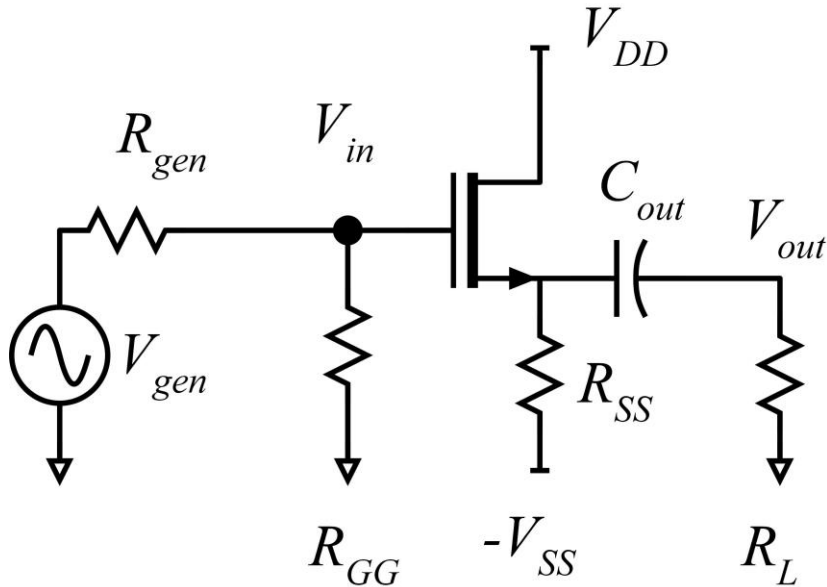Problem 1, 30 points

You will be working on the circuit below:



The transistor has

$$L_g = 22 \text{ nm}, \mu = 180 \text{ cm}^2/\text{V}\cdot\text{s}, \epsilon_{r,ox} = 3.8, T_{ox} = 1 \text{ nm}, v_{sat} = 10^7 \text{ cm/s}, V_{th} = 0.3 \text{ V}, 1/\lambda = 10 \text{ V},$$

From which we calculate:

$$c_{ox} v_{sat} = 3.36 \text{ mA/V}/\mu\text{m}, \mu c_{ox} / 2L_g = 13.8 \text{ mA/V}^2/\mu\text{m}, \Delta V = L_g v_{th} / \mu = 0.122 \text{ V},$$

The supplies are +2V and -2 V

You are to bias the transistor at 2mA drain current, and with -0.5 V DC source voltage.

$$R_{GG} = 10 \text{ M}\Omega, R_{gen} = 100 \text{ k}\Omega, R_L = 1 \text{ k}\Omega$$

C_{out} are is very large (AC short-circuit)

Part a, 10 points

DC bias.


Use this approximation: Ignore (i.e. set to zero) the FET λ parameter in the DC bias calculation.

Find the following:

FET gate width W_g =_____ R_{ss} =_____

Part b, 5 points

DC bias

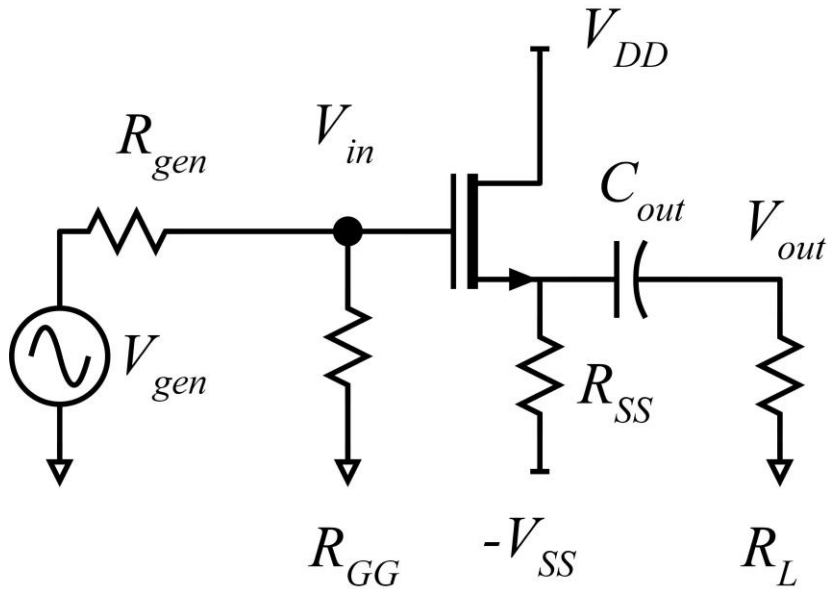

On the circuit diagram above, label the DC voltages at **ALL nodes** and the DC currents through **ALL resistors**

Part c, 5 points

Using the actual (nonzero) FET λ parameter, find the FET small signal parameters
gm=_____ Rds=_____

Part d, 10 points.


Find the small signal voltage gain V_{out}/V_{in} and the amplifier small-signal input resistance.

$V_{out}/V_{in} =$ _____

$R_{in, \text{ amplifier}} =$ _____

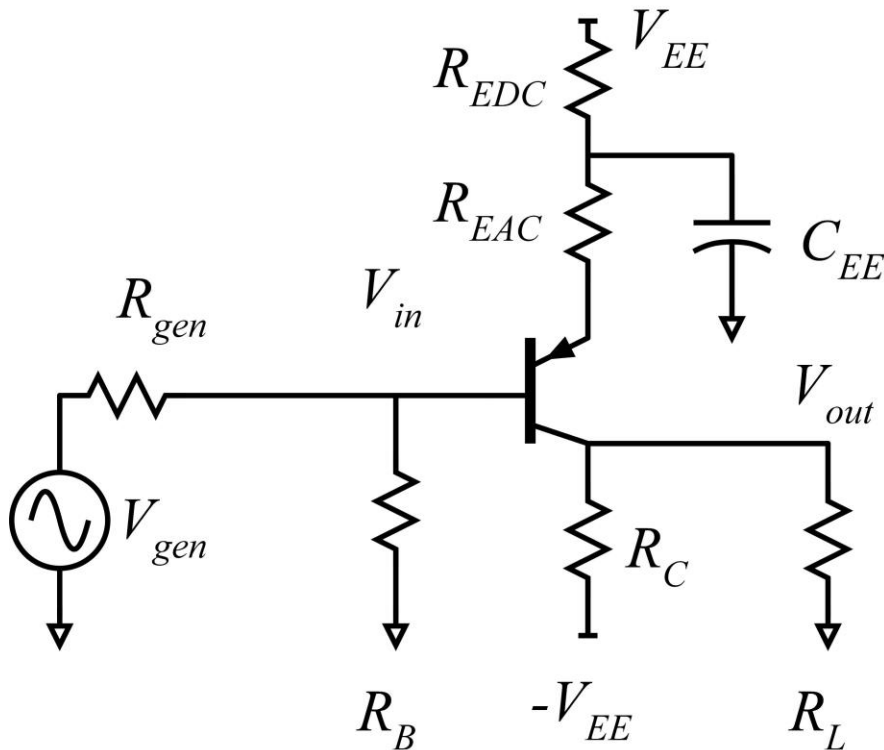Problem 2, 50 points

You will be working on the circuit below:



Q1: $\beta = 100$, $V_A = \text{infinity V}$

The supplies are +5V and -5 V.

You will bias the transistor with 10mA collector current.

The DC collector bias voltage is 0V.

R_L is 500Ω , R_{gen} is 100Ω , R_b is $1\text{ k}\Omega$, R_{EAC} is 25Ω

C_{EE} is very large. Assume that it is an AC short-circuit.

Part a, 10 points


DC bias.

Find the following:

$$R_{EE} = \underline{\hspace{2cm}} \quad R_C = \underline{\hspace{2cm}} \quad R_{EDC} = \underline{\hspace{2cm}}$$

Part b, 5 points

DC bias

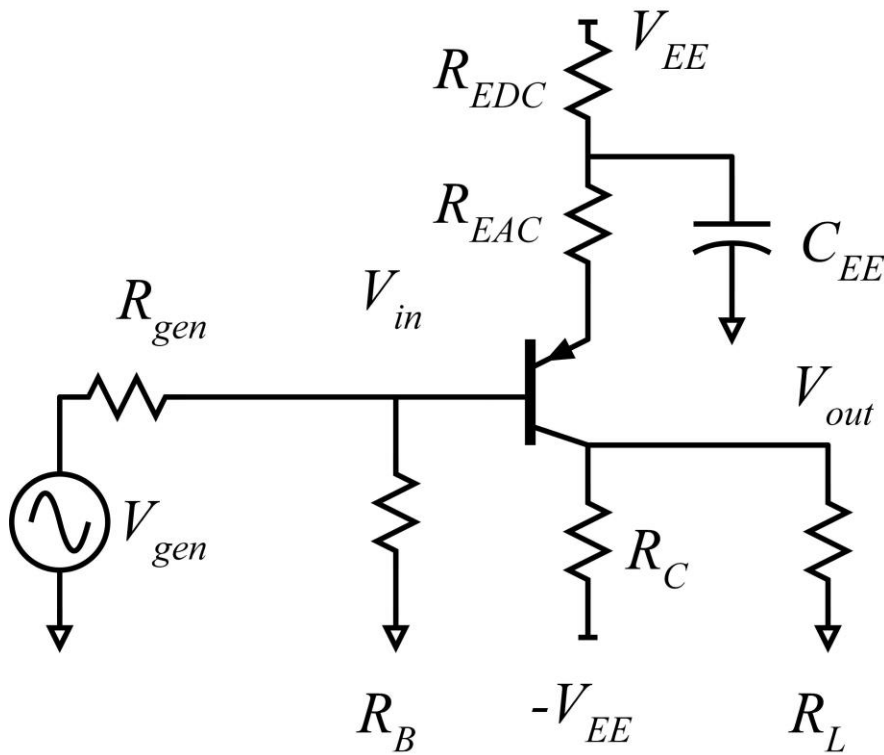

On the circuit diagram above, label the DC voltages at **ALL nodes** and the DC currents through **ALL resistors**

Part c, 5 points

Find the small signal parameters of Q1.

$g_m =$ _____ $R_{ce} =$ _____ $R_{be} =$ _____

Part d, 10 points.

Find the small signal voltage gain (V_{out}/V_{in}) of Q1 and the amplifier small-signal input resistance.

$V_{out}/V_{in} =$ _____

$R_{in,amp} =$ _____

Part e, 5 points

Find (V_{in}/V_{gen}) and (V_{out}/V_{gen})

$(V_{in}/V_{gen}) =$ _____

$(V_{out}/V_{gen}) =$ _____


Part f, 15 points

Now you must find the maximum signal swings. Find the output voltage due to saturation and cutoff in Q2. **Give the sign (+ or -) in your answers below.**

Cutoff of Q1; Maximum ΔV_{out} resulting = _____

Saturation of Q1; Maximum ΔV_{out} resulting = _____

Problem 3, 20 points
nodal analysis

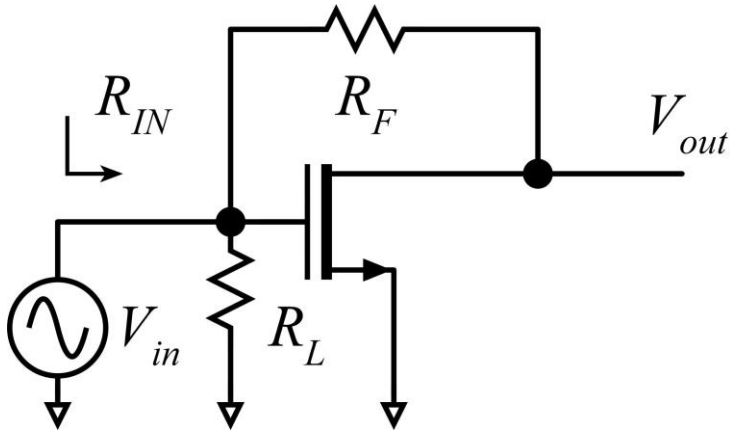

You will be working on the circuit to the left.

Ignore DC bias analysis. You don't need it.

The transistor has transconductance g_m .

The drain-source resistance R_{ds} of the transistor is infinity (so you don't need to draw it!)

Part a, 8 points

Draw the small-signal equivalent circuit

Part b, 8 points

Find, by nodal analysis, a small-signal expression for R_{in} .

$R_{in} =$ _____

Part c, 4 points

$g_m = 1 \text{ mS}$, $R_L = 3 \text{ k}\Omega$, $R_f = 2 \text{ k}\Omega$.

Give a numerical value for R_{in} .

$R_{in} = \underline{\hspace{2cm}}$