

Final Exam, ECE 137A

Wednesday March 22, 2017, 7:30 - 10:30pm

Name: Solution.

Closed Book Exam:

Class Crib-Sheet and 3 pages (6 surfaces) of student notes permitted

Do not open this exam until instructed to do so. Use any and all reasonable approximations (5% accuracy), *after stating & justifying them.*

Show your work:

Full credit will not be given for correct answers if supporting work is missing.


Good luck

Time function	LaPlace Transform
$\delta(t)$ impulse	1
$U(t)$ unit step-function	$1/s$
$e^{-\alpha t} U(t)$	$\frac{1}{s + \alpha}$
$e^{-\alpha t} \cos(\omega_d t) U(t)$	$\frac{s + \alpha}{(s + \alpha)^2 + \omega_d^2}$
$e^{-\alpha t} \sin(\omega_d t) U(t)$	$\frac{\omega_d}{(s + \alpha)^2 + \omega_d^2}$

Part	Points Received	Points Possible	Part	Points Received	Points Possible
1a		5	2c		15
1b		6	2d		10
1c		4	3a		7
1d		10	3b		8
1e		10	3c		7
2a		10	3d		8
2b		10			
total		100			

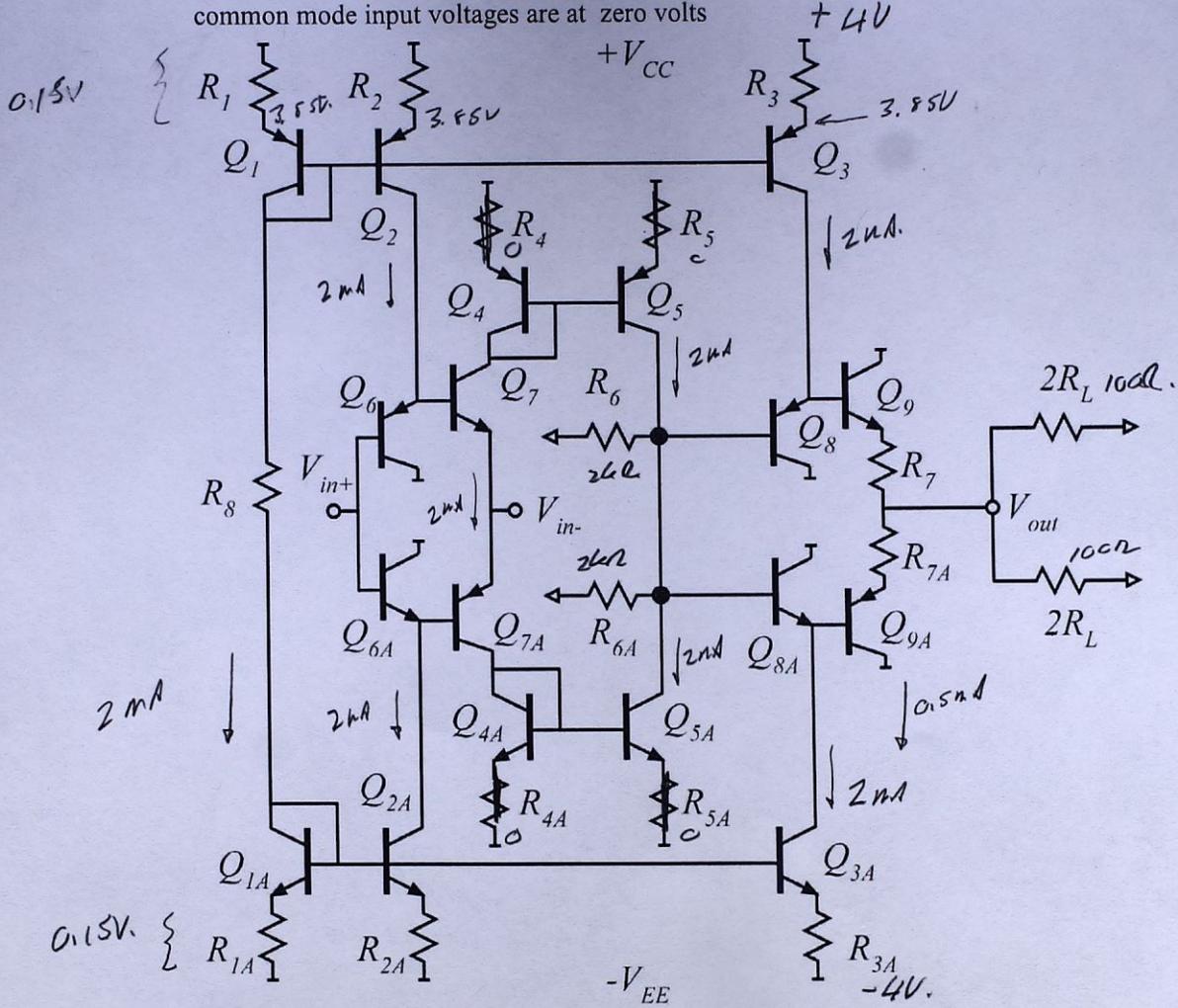Problem 1, 35 points

This is an NOT an Op-Amp: Analyze under the assumption that the differential and common mode input voltages are at zero volts



All the transistors have the same (matched) I_S , have $\beta = 100$, and $V_A = \infty$ Volts.

$$V_{CE(sat)} = 0.5V$$

V_{be} is roughly 0.7 V, but use $V_{be} = (kT/q) \ln(I_E/I_S)$ when necessary and appropriate.

The supplies are +4 Volts and -4 Volts.

R1=R1A, R2=R2A, R3=R3A, R6=R6A, R7=R7A.

The voltage drops across R1 and R1A are both 150mV.

Q1, Q1A, Q6, Q6A, Q7, Q7A, Q5, Q5A, Q8, Q8A : $I_C = 2\text{mA}$.

Q9, Q9A: $I_C = 0.5 \text{ mA}$.

$RL = 50 \text{ Ohms}$, $R6 = R6A = 2000 \text{ Ohms}$. $R4 = R4A = R5 = R5A = 0 \text{ Ohms}$.


$$\frac{kT}{q} / h = R_7 \cdot 0.5\text{mA} -$$

$R_7 = 3672$

$$\beta = 100, V_A = 0V$$

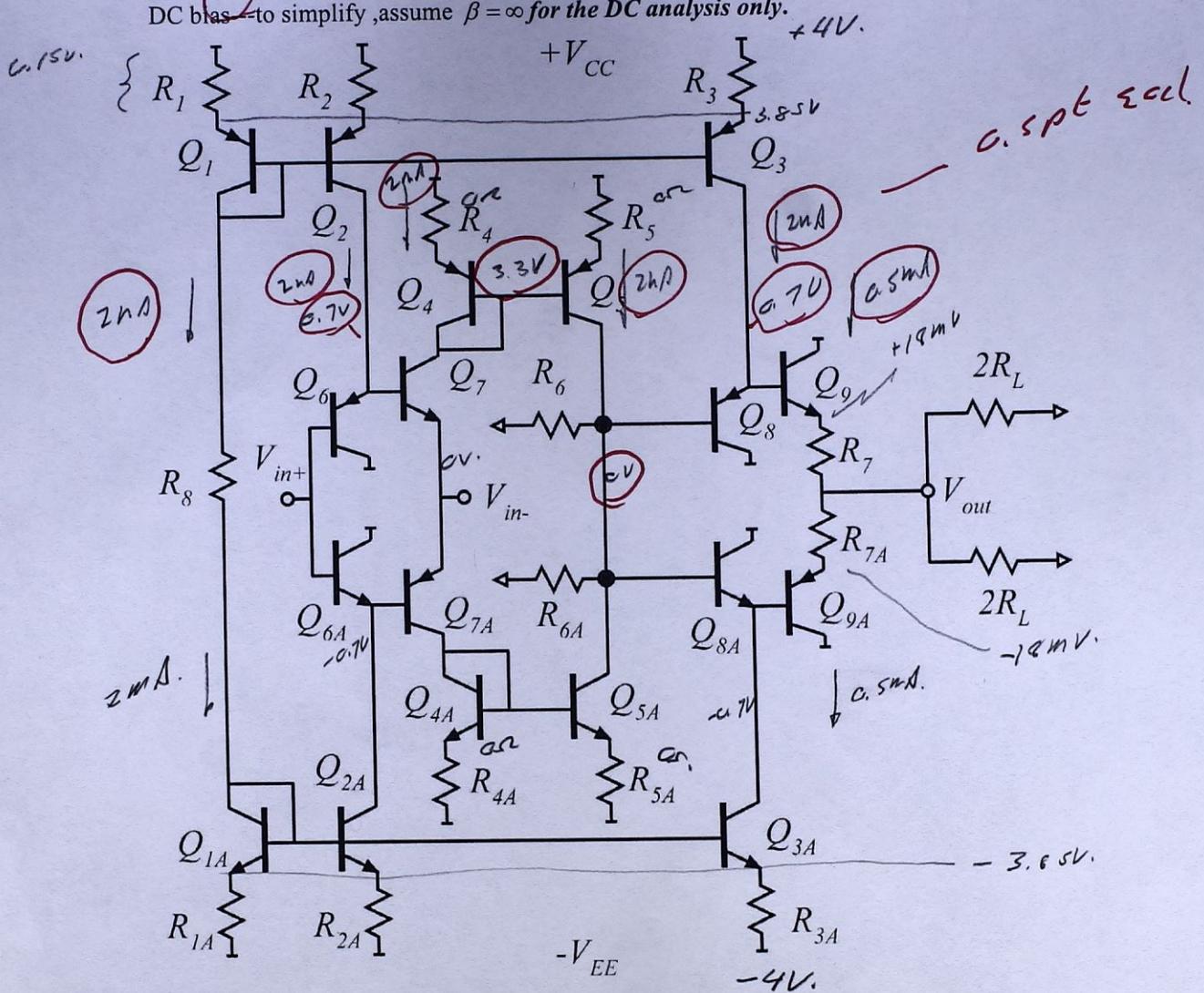Part a. 5 points

DC bias - to simplify ,assume $\beta = \infty$ for the DC analysis only.



On the circuit diagram above, label the DC voltages at ALL nodes, the DC currents through ALL resistors, and the DC collector currents of all transistors.

Part b, 6 points

DC bias:

Find the value of all resistors.

$$\begin{aligned} R_1/R_{1A} &= \underline{75} & R_2/R_{2A} &= \underline{75} & R_3/R_{3A} &= \underline{7.5} & R_4/R_{4A} &= \underline{0.5} \\ R_5/R_{5A} &= \underline{0.2} & R_6/R_{6A} &= \underline{2k\Omega} & R_7/R_{7A} &= \underline{3.85} & R_8 &= \underline{3.85k\Omega} \\ &&&&\uparrow && \\ &&&&72\Omega && \end{aligned}$$

2 $R_1/R_{1A} = 1/2A/3/3A : R = \frac{0.15V}{2mA} = 75\Omega$

2 $R_7/R_{7A} : V_{be8} + V_{be80} - V_{beq} - V_{be91} = 2 \cdot R_7 \cdot 0.5mA$

$$2 \frac{kT}{8} \ln(4) = 2R_7 \cdot 0.5mA$$

$$R_7 = 72\Omega$$

2 $R_8 : V_{drop} \text{ is } (4V - 0.15V) \cdot z, \text{ current is } 2mA$

$$R = \frac{(4V - 0.15V) \cdot z}{2mA} = 3.85k\Omega$$

Part c, 4 points

find the following

device	Q1/1A	2/2A	3/3A	4/4a	5/5A	6/6A	7/7A	8/8A	9/9A
gm, S									
R _{ce} , Ω	∞	∞	∞	∞	∞	∞	∞	∞	∞

76.9ms

19ms.

1

$$R_{ce} = \frac{V_A + \frac{V_{CE}}{\infty}}{I_C} \rightarrow \infty \text{ or } R_c$$

1.5

All to except Q9/9A:

$$I_C = 2 \text{ mA} \rightarrow 1/g_m = 132 \rightarrow g_m = 76.9 \text{ ms}$$


1.5

Q9/9A

$$I_C = 1/2 \text{ mA} \rightarrow 1/g_m = 522 \rightarrow g_m = 19.2 \text{ ms}$$

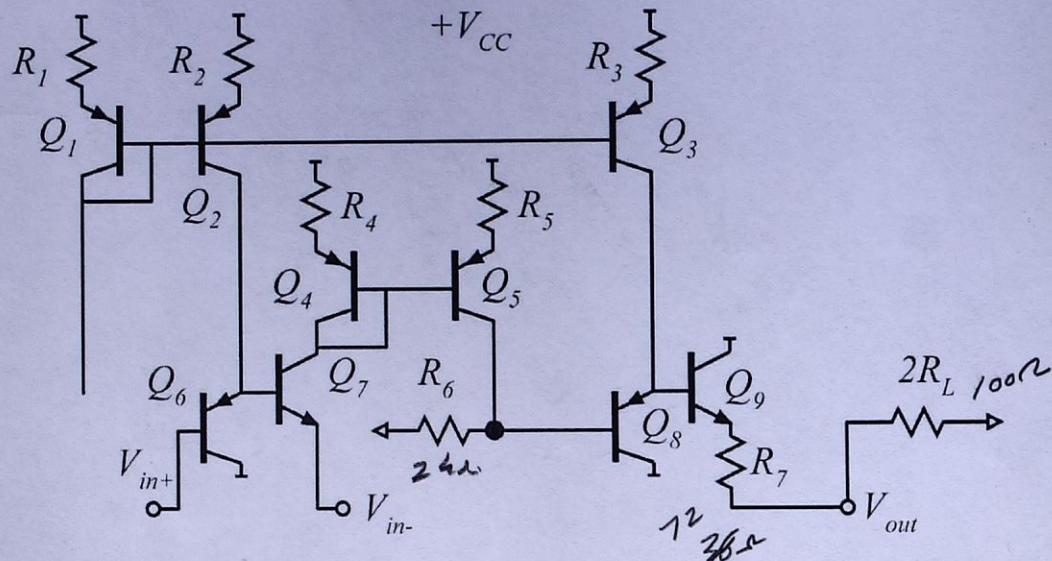Part d, 10 points.

The circuit is 100% symmetric, and can be represented by the simpler small-signal diagram below;



Find the following, *using the actual value of β , i.e. $\beta=100$*

	Voltage Gain	Input impedance
Q9	0.45	22 k\Omega
Q8	1	2.2 M\Omega
Q5	-154	1.3 k\Omega
Q7	-1	1.3 k\Omega
Q6	1	130 \mu\Omega
Overall differential Vout/Vin	69	130 k\Omega

Note: with some insight, you can find the combined gain of Q7/Q4/Q5 in a single step. If you would like to do so, omit the separate answers for Q5 and Q7 in the table above, and instead fill in the table below,

	Voltage Gain	Input impedance
Q7/Q4/Q5 combination.	154	13 k\Omega

Q9 / $R_7, 2R_L$ divider

$$1 \left. \begin{aligned} V_{out}/V_{reg} &= \frac{100\Omega}{172\Omega} \\ Q9: Av &= \frac{172\Omega}{172\Omega + 52\Omega} = 0.71 \end{aligned} \right\} 0.45: \text{overall}$$

$$1/2 \left[R_{in} = \beta(172\Omega + 52\Omega) = 22.4 \text{ k}\Omega \right]$$

Q8: $1/2 \left[R_{leg} = R_{in} = 22.4 \text{ k}\Omega \right]$

$$\underline{\underline{5}} \quad 1/I_{gm} = 13\Omega$$

$$1/2 \left[Av = \frac{22.4 \text{ k}\Omega}{22.4 \text{ k}\Omega + 13\Omega} = 0.999 \approx 1 \right]$$

$$1/2 \left[R_{in} = \beta(22.4 \text{ k}\Omega) = 2.24 \text{ M}\Omega \right]$$

Q5 $1/2 \left[R_{leg5} = R_6 \parallel R_{in8} = 2\text{k}\Omega \parallel 2.24 \text{ M}\Omega = 1.995 \text{ M}\Omega \right. \\ \left. \approx 2\text{k}\Omega \right]$

$$1/2 \left[Av = -g_m \cdot R_{leg5} = -\frac{2\text{k}\Omega}{13\Omega} = -153.8 \right]$$

$$1/2 \left[R_{in5} = \beta/I_{gm} = 100 \cdot 13\Omega = 1.3 \text{ k}\Omega \right]$$

Q7 $1/2 \left[R_{leg} = 1/I_{gm4} \parallel R_{in5} = 13\Omega \parallel 1.3 \text{ k}\Omega = 0.99 \cdot 13\Omega \right. \\ \left. \approx 13\Omega \right]$

$$1 \left[Av_7 = -g_m R_{leg7} = -13\Omega / 13\Omega = -1 \right]$$

$$1 \left[R_{in7} = \beta/I_{gm} = 1.3 \text{ k}\Omega \right]$$

Q6/1 $1 \left[R_{leg} = R_{in7} = 1.3 \text{ k}\Omega \right] \quad 1 \left[Av = \frac{1.3 \text{ k}\Omega}{1.3 \text{ k}\Omega + 13\Omega} = 0.99 \right]$

$$1 \left[R_{in} = \beta \cdot R_{leg} = 1.3 \cdot 1.3 \text{ k}\Omega \approx 1.3 \text{ M}\Omega \right]$$

Alternative: for the Q7/4/5 comb. not.a.

$$\begin{array}{c} \text{Ar} = {}^+g_m \tau R_s = \frac{2kR}{13R} \\ \text{Ar} = 153.8 \end{array}$$

Note: QXA answers are the negative of Qx answers.

Part e, 10 points


Maximum peak-peak output voltage (*show all your work*)

For this, you must use the full circuit diagram, not the half circuit diagram.


	magnitude and sign of maximum output signal swing due to <i>cutoff</i>	magnitude and sign of maximum output signal swing due to <i>saturation</i>
Transistor Q9	+1.43V	N/A
Transistor Q9A	-1.43V	N/A
Transistor Q8	-1.84V	+10V
Transistor Q8A	+1.84V	-10V
Transistor Q5	1.43V	N/A
Transistor Q5A	-1.43V	N/A
Transistor Q7	N/A	N/A
Transistor Q7A	N/A	N/A

Be warned: In some cases a limit is not relevant at all. Mark those answers "not relevant". But, give a 1-sentence statement below as to why it is not relevant. Q9/9A form a push pull stage, so be careful about your answer there. **Hint:** There is, effectively, another push-pull stage in the circuit, which will affect two of the other answers.


Q9 cutoff - not relevant - push pull

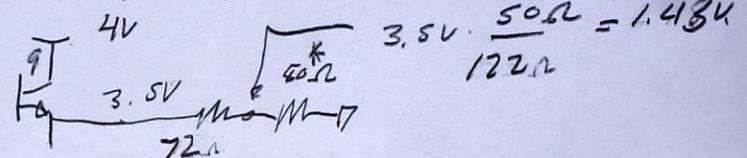

Q9 saturation

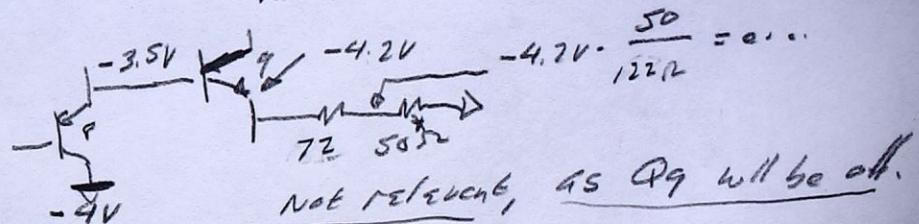


Actual limit

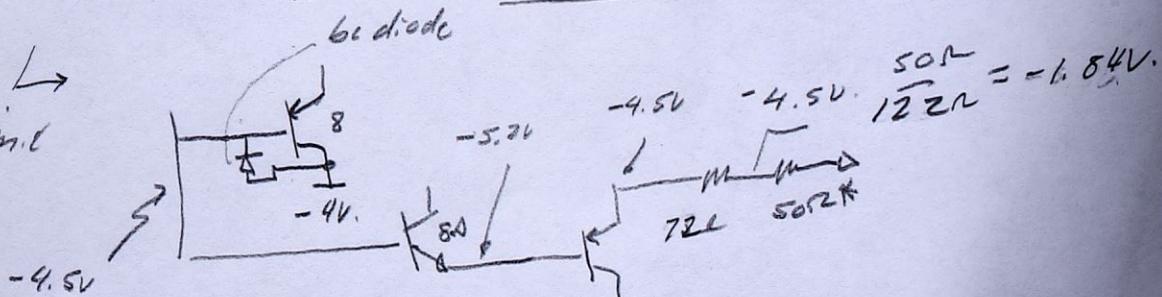


*note - we will accept $\frac{100\Omega}{100\Omega + 72\Omega}$ as acceptable.

and will accept use of $\frac{11}{100\Omega}$ for load.

Cutoff Q9

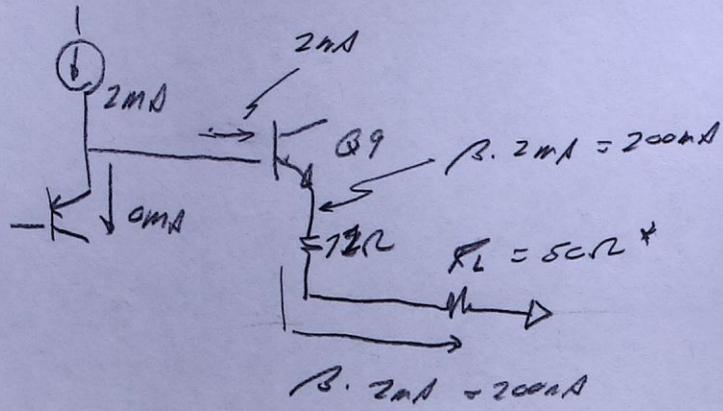


Sat Q5

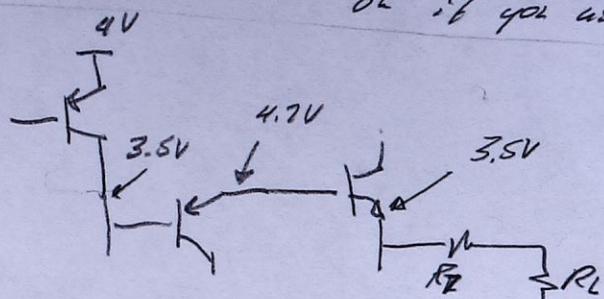


$$3.5V \cdot \frac{R_L}{R_L + R_2} = 3.5V \cdot \left(\frac{50\Omega}{122.62} \right) * = 1.43 \text{ V.}$$

Cutoff Q5

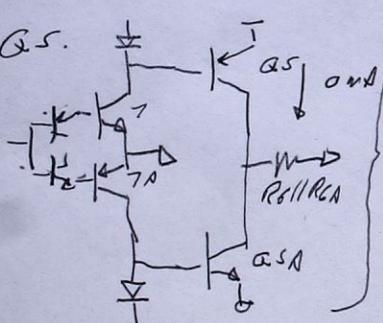


cutoff of Q5 is not relevant
as Q5/Q5A form another
push-pull pair

Sat Q7

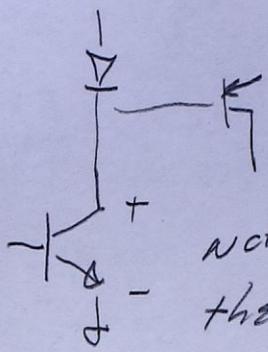

not relevant - if $V_{CE} \geq 0.8V$
then I_{C7} would be VERY large.


Cutoff Q7

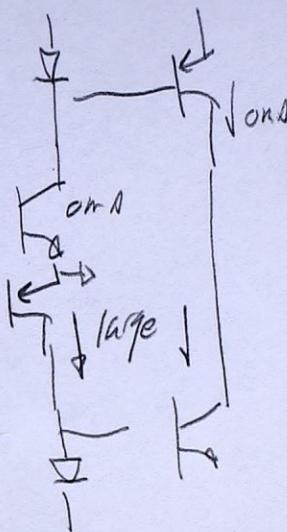

Again - not relevant
as Q7 / 7A
& Q5 / 5A
form push pull pair

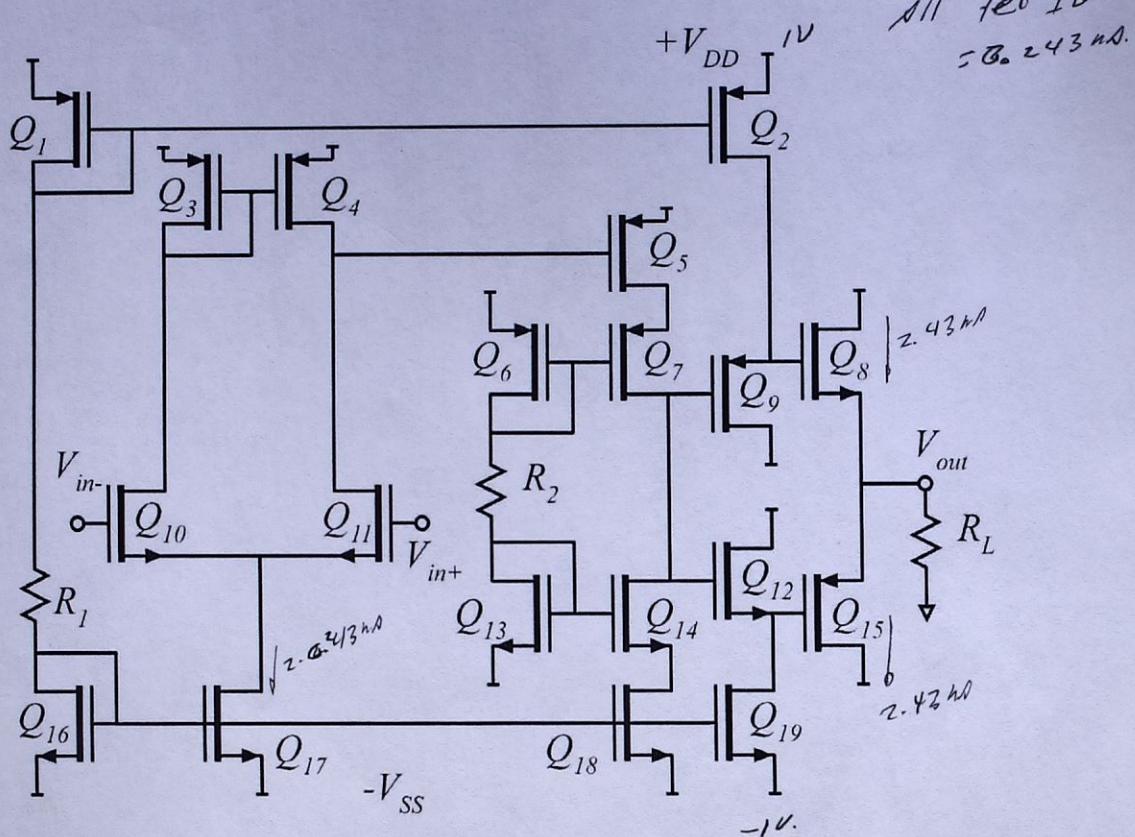Problem 2, 35 points

This is an Op-Amp---analyze the bias under the assumption that DC output voltage is zero volts, that the positive input V_{in+} is zero volts, and that we must determine the DC value of the negative input voltage (V_{in-}) necessary to obtain this.



The NMOSFETs and the PMOSFETs have a 0.20 V threshold, a 22nm gate length, 200 cm²/Vs mobility, a 10⁷cm/s injection velocity, and $1/\lambda=4$ Volts. The gate oxide thickness is 0.8nm and the dielectric constant is 3.8. This gives

$$\mu c_{ox} W_g / 2L_g = 19.1 \text{ mA/V}^2 \cdot (W_g / 1\mu\text{m}) \text{ and}$$

$$v_{sat} c_{ox} W_g = 4.21 \text{ mA/V} \cdot (W_g / 1\mu\text{m}) \text{ (both are a bit unrealistic for a real technology).}$$

$$\text{and } v_{sat} L_g / \mu = 0.110 \text{ V}$$

$$V_{DD} = +1 \text{ V}, \quad -V_{SS} = -1 \text{ V}, \quad R_L = 10 \text{ kOhm}$$

Part a, 10 points

DC bias.

Approximation: ignore the term $(1 + \lambda V_{DS})$ in DC bias analysis.

Analyze the bias under the assumption that DC output voltage is zero volts, that the positive input V_{i+} is zero volts, and that we must determine the DC value of the negative input voltage (V_{i-}) necessary to obtain this.

All transistors *except Q6, Q13* have $|V_{gs}|=0.25V$.

Q6 and Q13 have $V_{gs}=0.30V$.

All transistors *except Q8, Q15, Q17* have $|I_D|=0.243mA$.

Q8 and Q15 have $|I_D|=2.43mA$.

You can figure out $|I_D|$ for Q17.

Find the gate widths of all transistors, plus R1 and R2.

Find:

$$Wg_1 = \underline{\hspace{2cm}} \quad Wg_2 = \underline{\hspace{2cm}} \quad Wg_3 = \underline{\hspace{2cm}} \quad Wg_4 = \underline{\hspace{2cm}}$$

$$Wg_5 = \underline{\hspace{2cm}} \quad Wg_6 = \underline{\hspace{2cm}} \quad Wg_7 = \underline{\hspace{2cm}} \quad Wg_8 = \underline{\hspace{2cm}}$$

$$Wg_9 = \underline{\hspace{2cm}} \quad Wg_{10} = \underline{\hspace{2cm}} \quad Wg_{11} = \underline{\hspace{2cm}} \quad Wg_{12} = \underline{\hspace{2cm}}$$

$$Wg_{13} = \underline{\hspace{2cm}} \quad Wg_{14} = \underline{\hspace{2cm}} \quad Wg_{15} = \underline{\hspace{2cm}} \quad Wg_{16} = \underline{\hspace{2cm}}$$

$$Wg_{17} = \underline{\hspace{2cm}} \quad Wg_{18} = \underline{\hspace{2cm}} \quad Wg_{19} = \underline{\hspace{2cm}}$$

$$R_1 = \underline{\hspace{2cm}} \quad R_2 = \underline{\hspace{2cm}}$$

1 [$|V_{gs}| = 0.25V \rightarrow$ less than $V_{th} + \Delta V \rightarrow$ mob, I_f limited.

$$0.243mA = \frac{19.1mA}{\sqrt{2}} \cdot \frac{Wg}{1\mu m} (0.25V - 0.2V)^2 \rightarrow Wg = 5\mu m$$

$$\approx 5\mu m$$

2 [$Wg = 5\mu m$ for all Fets except Q8, 15, 17, 6, 13.

1 [For Q8/15 $\rightarrow Wg = 5\mu m$ (10x more I_d , same V_{gs}).

2 [For Q17 $= 0.486mA = \frac{19.1mA}{\sqrt{2}} \cdot \frac{Wg}{1\mu m} (0.25V - 0.2V)^2 \rightarrow Wg = 10.1\mu m$

1 [$R_1 // I = 0.243mA, V = 2(IV - 0.25V) \rightarrow R = 6.17k\Omega$

1 [$R_2 // I = 0.243mA, V = 2(IV - 0.3V) \Rightarrow R = 5.76k\Omega$


$$\left. \begin{array}{l} Q_1, Q_{13} \\ V_{GS} = 0.3V \\ V_{EL} + \Delta V = 0.2V + 0.11V \end{array} \right\} \text{still mobility limited}$$

2

$$0.243 \text{ m} = 19.1 \frac{\text{m}}{\text{s}^2} \cdot \frac{V_g}{\mu\text{m}} (0.3V - 0.2V)^2$$

$$V_g = 1.27 \mu\text{m}$$

Part b, 10 points

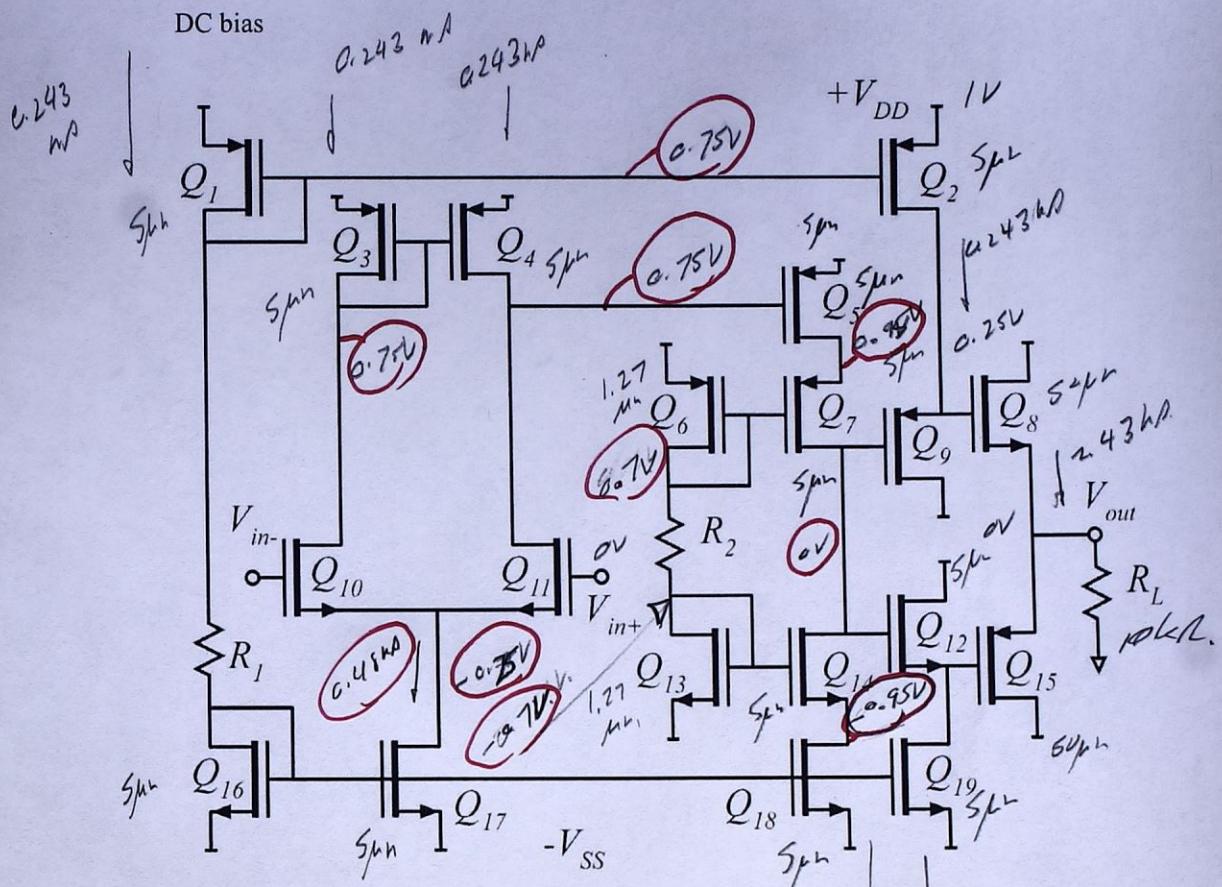

On the circuit diagram above, label the DC voltages at **ALL nodes**, the drain currents of **ALL transistors**, and the gate widths of **ALL transistors**

$$\frac{1}{\lambda} = 4V$$

Part c, 15 points.

You will now compute the op-amp differential gain. **You must consider the $(1 + \lambda V_{DS})$ term in the FET IV characteristics when you do this.**

Find the following

	Voltage Gain	Input impedance
Transistor combination Q3,4,10,11	157.6	$\infty \Omega$
Q5,7	13,300	$\infty \Omega$
Q9 or Q12.	0.996	$\infty \Omega$
Q8 or Q15	0.99	$\infty \Omega$
Overall differential Vout/Vin	$1.94 \cdot 10^6$	$\infty \Omega$


Notes:

- 1) You can analyze Q5 and Q7 as separate stages, or as a combined stage using Norton/Thevenin methods. Don't ask for hints as to how to do this.
- 2) For Q9/12 and for Q8/15, you can assume that Q9 and Q12 are on for the positive signal swing and Q8 and Q15 are on for the negative signal swing. More accurately, you can assume, for the signal swing near zero volts, that all are on. If you take the latter approach (and do it correctly), you will receive a couple of extra credit points. One hint (don't ask for any other hints): use symmetry.

o- work for 2 stages

or work as 2 stages.

Let's analyze this by Norton method

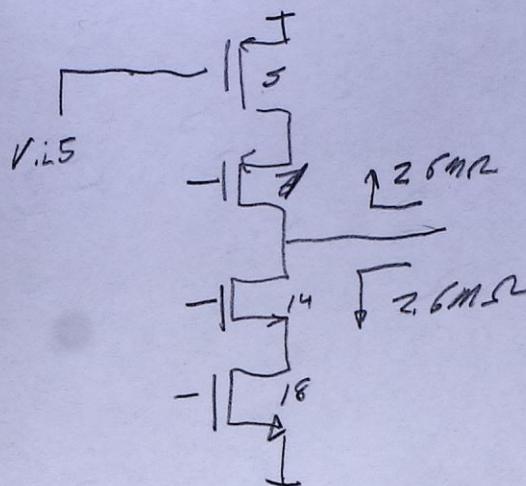

Node impedance is

$$2.6M\Omega \parallel 2.6M\Omega = 1.3M\Omega$$

Short-circuit current is

$$g_{m5} v_{in5} \cdot \frac{R_{DS5}}{R_{DS5} + 1/g_{m7}}$$

$$\rightarrow \text{Voltage gain} = g_{m5} \cdot 1.3M\Omega \cdot \frac{R_{DS5}}{R_{DS5} + 1/g_{m7}}$$

$$\left[\begin{array}{l} \text{voltage gain of } Q5 \text{ & } Q7 \\ = \frac{1.3M\Omega}{104.7\Omega} \cdot \frac{16.5k\Omega}{16.5k\Omega + 104.7\Omega} = \underline{\underline{12,300}} \\ 12,400 \quad \underbrace{104.7\Omega}_{0.994} \end{array} \right]$$

Q10/11/13/14 -

$$1 \left[R_{L\text{eq}} = R_{DS9} \parallel R_{DS11} \right]$$

$$R_{DS} = 1/\lambda I_D = 16.5k\Omega$$

$$1 \left[A_v = g_m R_{L\text{eq}} = 16.5k\Omega (104.7\Omega)^{-1} = 157.1 \right]$$

2

$$g_a = 2 \left(\overbrace{V_{GS} - V_{EL}}^{0.05V} \right) \cdot \frac{19.1mA}{V^2} \cdot Wg$$

$$= 9.55 \text{ ms for all } T_c \text{ except Q8/15} = 1/104.7\Omega$$

$$= 95.5 \text{ ms for Q8/15} = 1/10.47\Omega$$

Q8

$$\text{assume } Q15 \text{ off}$$

$$A_{v8} = \frac{10kR_{DS8}}{R_{DS8} + 1/g_m} = 0.993 \approx 1$$

$$R_{DS8} = 1/g_m = 1.65k\Omega$$

$$R_{DS8} = 104.7\Omega$$

$$R_i = \infty \Omega$$

Q9

$$R_{DS9} = R_{DS2} = \frac{R_{DS2}}{R_{DS9}} = \frac{1/\lambda I_D}{8.25k\Omega} = 4V/0.243mA = 16.5k\Omega$$

$$A_{v9} = \frac{16.5k\Omega}{8.25k\Omega + 1/g_m} = 0.988 \approx 1$$

$$R_i = \infty \Omega$$

Q7 and Q5.

$$R_{DS9} = R_{in \text{ drain } 14} = (g_{m14} R_{DS14} + 1) R_{DS19}$$

$$R_{DS14} = R_{DS14} = 1/\lambda I_D = 4V/0.243mA = 16.5k\Omega$$

$$= (16.5k\Omega / 104.7\Omega + 1) 16.5k\Omega = 2.6M\Omega$$

two options to work

- 1) stage by stage.
- 2) Norton analysis of Q5/7 combination.

Part d, 10 points

Maximum peak-peak output voltage at the positive output V_{O+} (*show all your work*)

	magnitude and sign of maximum output signal swing due to <i>cutoff</i>	magnitude and sign of maximum output signal swing due to: <i>knee voltage (saturation)</i>
Transistor Q8	not relevant - posh-poll	+0.95V
Transistor Q15	" " "	-0.95V
Transistor Q9	+4V (or large ignore)	+1.2V
Transistor Q12	-4V (or "large")	-1.2V
Transistor Q2	N/A	0.7V
Transistor Q19	N/A	-0.7V
Transistor Q7	-630V or irrelevant	+0.9V
Transistor Q14	N/A	-0.9V

Be warned: in some cases a limit is not relevant. Mark those answers "not relevant".

1 [Q8 - cutoff - not relevant - posh-poll
Q15 - " " " " "

1 [Q8 knee voltage $\frac{+0.2V}{+0.05V}$ | $+0.05V$. knee is $\textcircled{Q} V_{BS} = 0.05V$.
 $+0.25V$ | $V_{out} = 1V - 0.05 = 0.95V$

1/2 [Q15 knee voltage - identical calculation.

1/2 [Q9 cutoff $\Delta I_O = 0.243mA$ but R_{DS2} is $R_{DS2} - \text{large}$.
 $\Delta V = 0.243mV$. $R_{DS2} = +4V \rightarrow \text{large} \rightarrow \text{ignore}$.


1/2 [Q12 cutoff identical calculation / reg

1 [Q9 knee voltage $\frac{-0.05V}{+0.05V}$ | $+0.95V$ | $+0.2V$ | $-1.2V$ - beyond supply
- not relevant

1/2 [Q12 knee voltage identical calculation $\rightarrow +1.2V$.

10s [α_2 knee voltage]

$$V_{out} = 0.65V$$

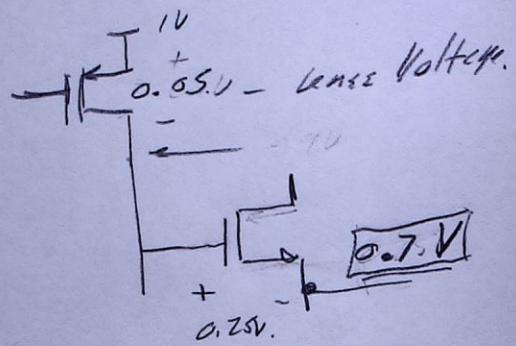

1/2 [α_{19} knee voltage \rightarrow identical calculation]

$$\Rightarrow V_{out} = -0.70V.$$

1/2 [α_2/α_{19} cutoff - not relevant - I_C doesn't turn off.]


1 [α_7 knee voltage]

1/2 [α_{14} knee voltage \rightarrow identical calculation - $V_{out} = -0.9V$]

1 [α_7 cutoff: $\Delta I = 0.243 \text{ mA}$] $dV = \text{product}$
 $R_{\text{leg}} = 2.6M\Omega$ $= -630V$
Very large (not relevant)


1/2 [α_{14} cutoff - not relevant - I_D does not vary]

Problem 3, 30 points

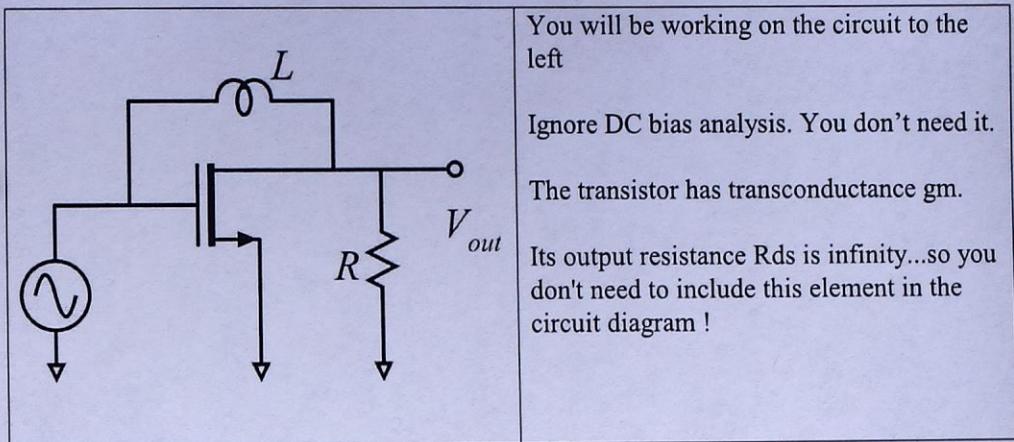

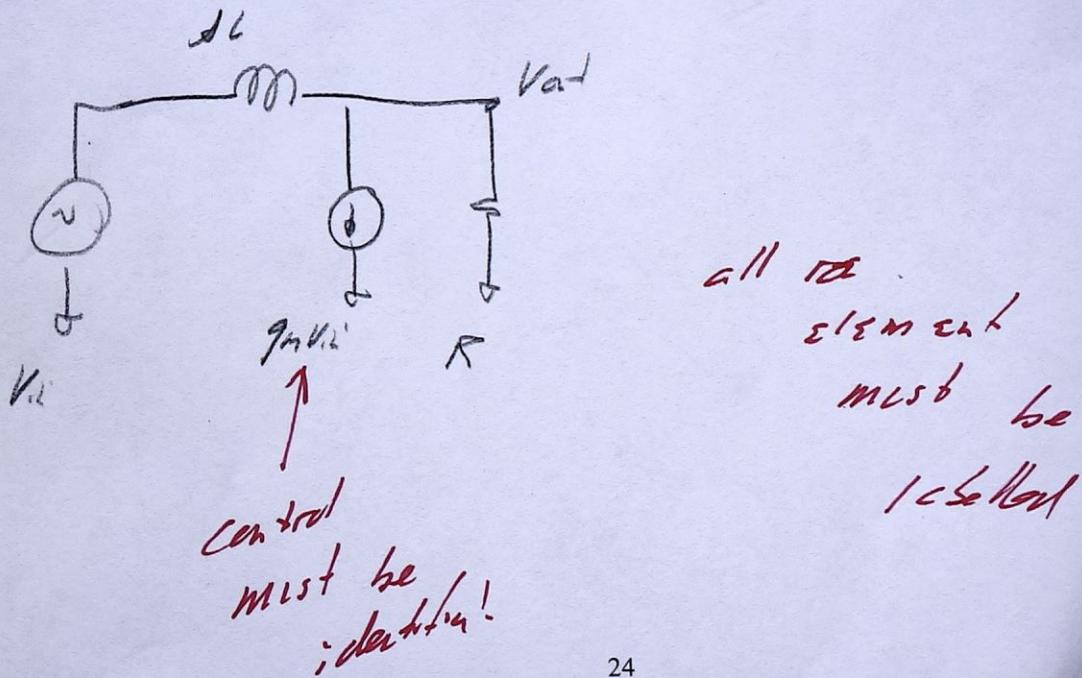Part a, 7 points

Draw a small-signal equivalent circuit of the circuit.



Part b, 8 points

$g_m = 20 \text{ mS}$, $L = 1 \text{nH}$, $R = 1000 \text{ Ohms}$

Find, by nodal analysis, a small-signal expression for V_{out}/V_{in} . Be sure to give the answer with **correct units** and in ratio-of-polynomials form, i.e.

$$\frac{V_{out}(s)}{V_{gen}(s)} = K \cdot \frac{1 + b_1 s + b_2 s^2 + \dots}{1 + a_1 s + a_2 s^2 + \dots} \text{ or (as appropriate)} \frac{V_{out}(s)}{V_{gen}(s)} = K \cdot (s\tau)^n \cdot \frac{1 + b_1 s + b_2 s^2 + \dots}{1 + a_1 s + a_2 s^2 + \dots}$$

Note that an expression like

$$\frac{V_{out}(s)}{V_{gen}(s)} = \frac{1}{1 + (3 \cdot 10^{-6})s} \text{ is dimensionally wrong; } \frac{1}{1 + (3 \cdot 10^{-6} \text{ seconds})s} \text{ is dimensionally correct}$$

$$V_{out}(s)/V_{in}(s) = \underline{\hspace{10em}}$$

$$= 1 @ V_{out} = 0$$

$$\rightarrow \left[\frac{(V_{out} - V_{in})}{sL} + g_m V_{in} + V_{out}/R = 0 \right] 4$$

$$V_{in} (1/sL - g_m) = V_{out} (1/sL + 1/R)$$

$$\frac{V_{out}}{V_{in}} = \frac{1/sL - g_m}{1/sL + 1/R} = \frac{1 - sL g_m}{1 + sL/R}$$

$$= \frac{1 - s(20 \mu S)}{1 + s(1 \mu S)}$$


4

Part c, 7 points

Find any/all pole and zero frequencies of the transfer function, in Hz:

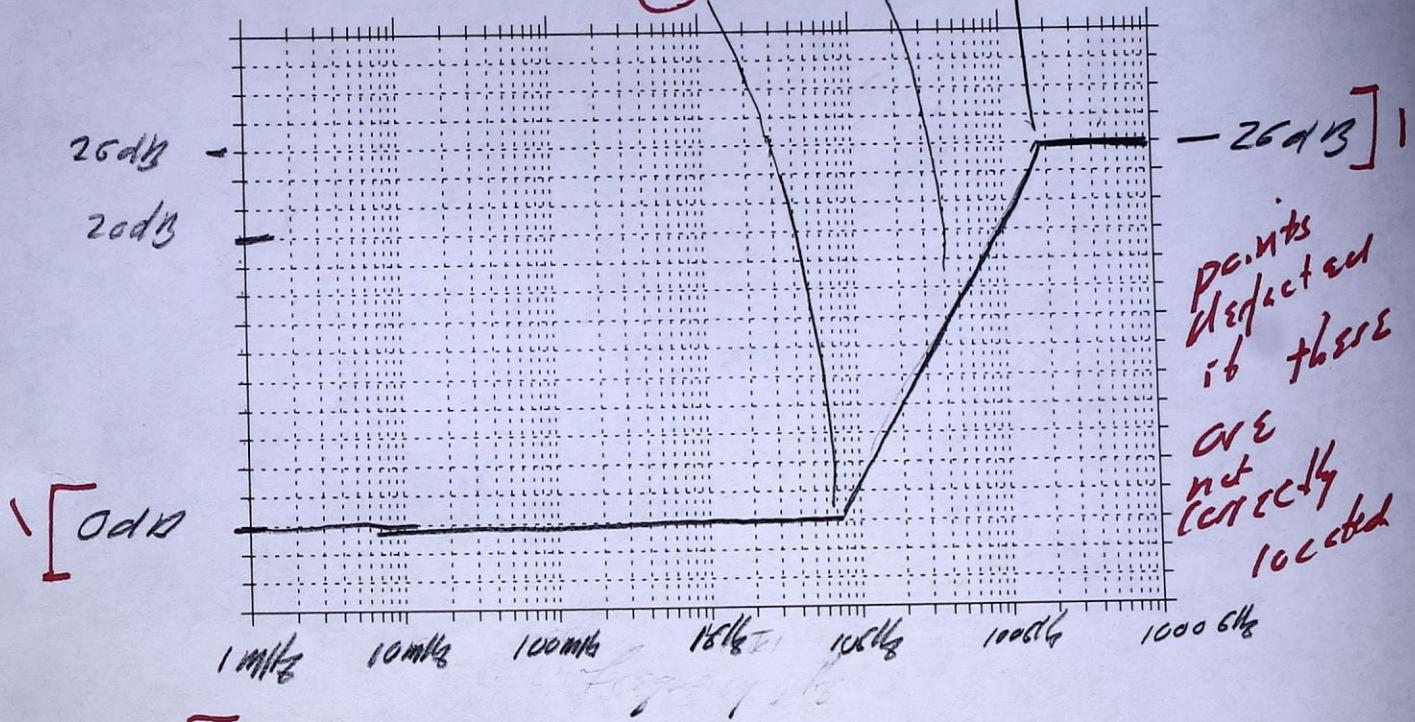_____ , _____ , _____ , _____

Draw a clean Bode Plot of Vout/Vin,
LABEL AXES, LABEL all relevant gains and pole or zero frequencies, Label Slopes



$$f_p = \frac{1}{2\pi(160)} = 160 \text{ kHz}$$


$$f_z = \frac{1}{2\pi(8)} = 8 \text{ kHz}$$

Part d, 8 points

$V_{in}(t)$ is a 0.1 V amplitude step-function.

Find $V_{out}(t) =$ _____

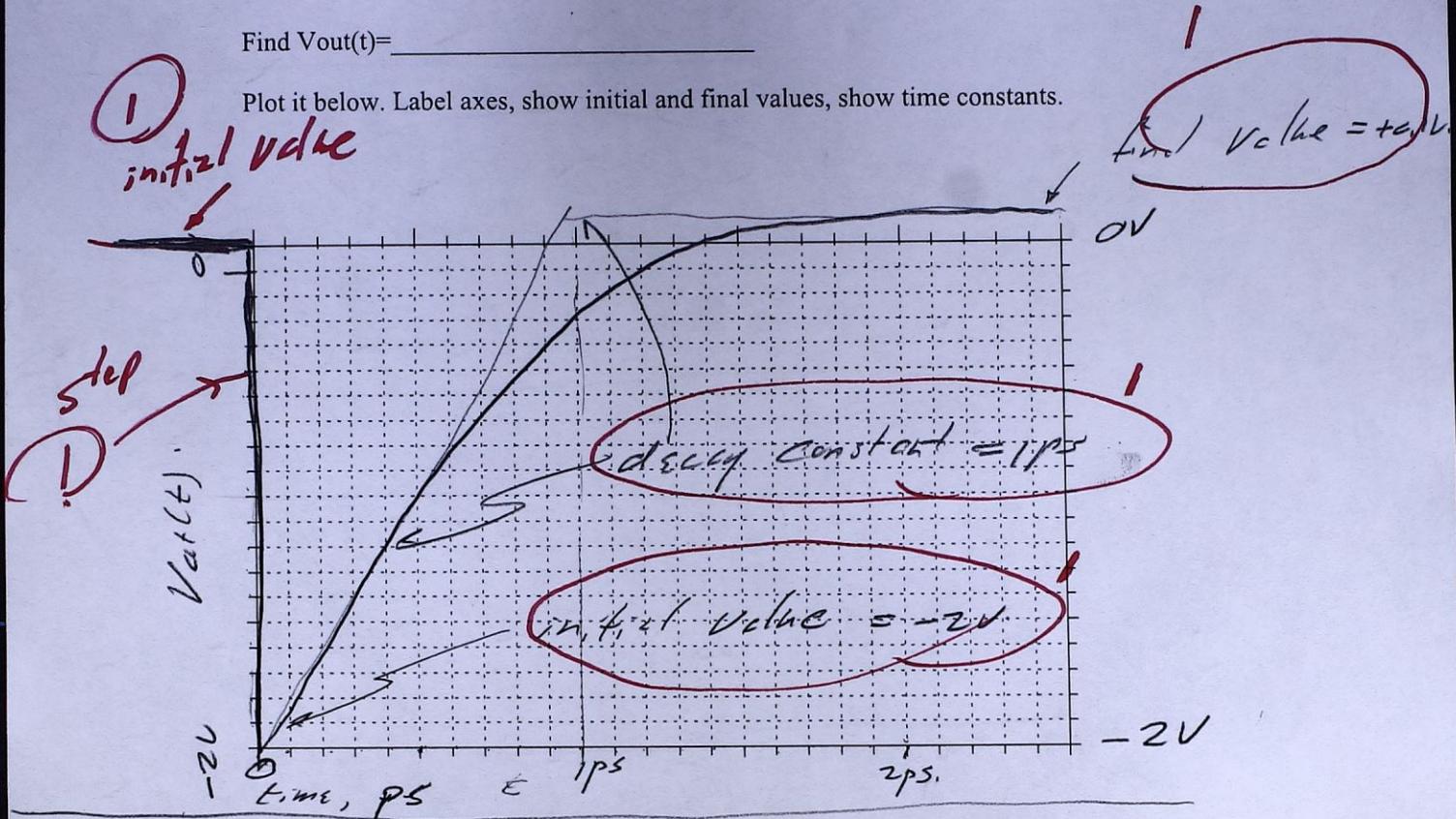Plot it below. Label axes, show initial and final values, show time constants.



$$U(s) = 0.1V / s$$

$$\begin{aligned} V_o(s) &= \frac{0.1V}{s} \frac{1 - s\gamma_p}{1 + s\gamma_p} = \frac{0.1V}{s} \left[1 + \frac{s(-\gamma_p - \gamma_p)}{1 + s\gamma_p} \right] \\ &= \frac{0.1V}{s} + \frac{0.1V(-\gamma_p - \gamma_p)}{\gamma_p} \frac{1}{1 + s\gamma_p} = \frac{0.1V}{s} + \frac{0.1V(-z_1)}{1 + s\gamma_p} \frac{1}{1 + s(1/\gamma_p)} \end{aligned}$$

$$V_o(t) = 0.1V \cdot u(t) - 2.1V u(t) \cdot e^{-t/1\text{ps}}$$