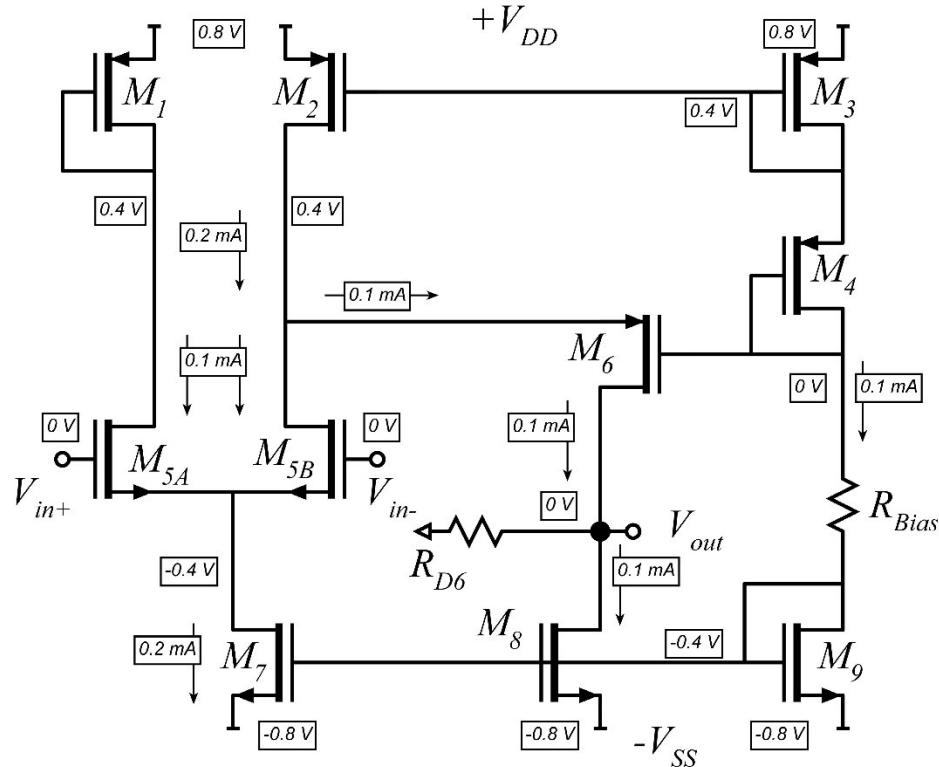


# ECE137A, Notes Set 11: MOS Multi-stage example

***Mark Rodwell,  
Dolucha Family Chair, ECE Department  
University of California, Santa Barbara  
rodwell@ece.ucsb.edu***

# Multistage CMOS example

Differential pair with single-ended folded cascode.



FETs:

$$K_\mu = 10 \text{ mA/V}^2 (W_g / 1 \mu\text{m})$$

$$K_v = 2 \text{ mA/V} (W_g / 1 \mu\text{m})$$

$$\Delta V = 0.1 \text{ V}$$

$$V_{th} = \pm 0.3 \text{ V}$$

$$1/\lambda = 4 \text{ V}$$


DC bias:  $V_{gs} = 0.4 \text{ V}$  for all FETs  $\rightarrow$  boundary of velocity- and mobility-limited regions.

All FETs except M5A, M5B, M8:  $|V_{DS}| = 0.4 \text{ V}$ .

M5A, M5B, M8:  $|V_{DS}| = 0.8 \text{ V}$ .

M1 forces an equal  $V_{DS}$  for M5A, M5B

# DC bias analysis

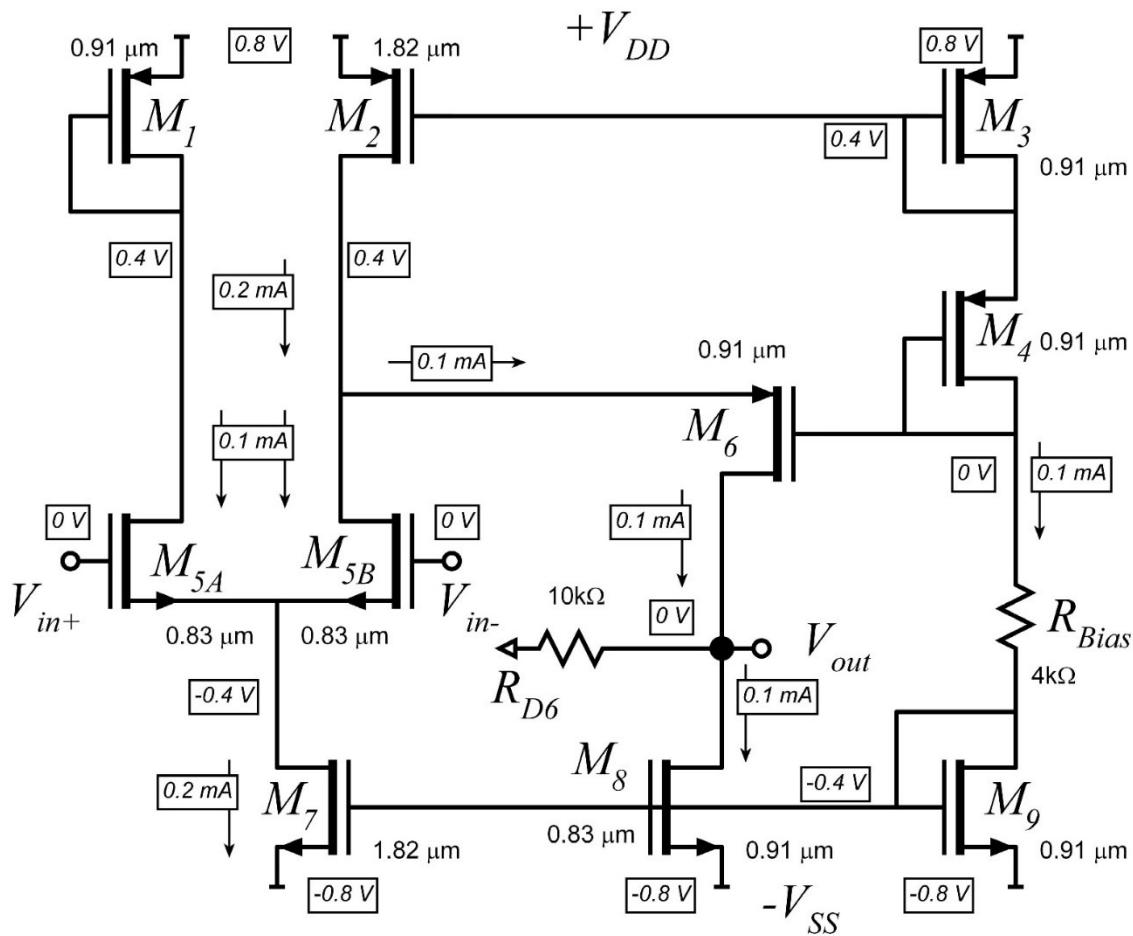

FET widths are calculated from

$$I_D = K_\mu (V_{gs} - V_{th})^2 (1 + \lambda V_{DS})$$


where  $K_\mu = 10 \text{ mA/V}^2 (W_g / 1 \mu\text{m})$

FET small-signal parameters from  $g_m|_{mobility} = 2I_D / (V_{gs} - V_{th})$ ,  $R_{DS} = 1 / \lambda I_D$

M5A,B:  $g_m = 2 \text{ mS}$ ,  $R_{DS} = 40 \text{ k}\Omega$ . M2:  $R_{DS} = 20 \text{ k}\Omega$

M6 :  $g_m = 2 \text{ mS}$ ,  $R_{DS} = 40 \text{ k}\Omega$ . M8:  $R_{DS} = 40 \text{ k}\Omega$

# Small signal analysis

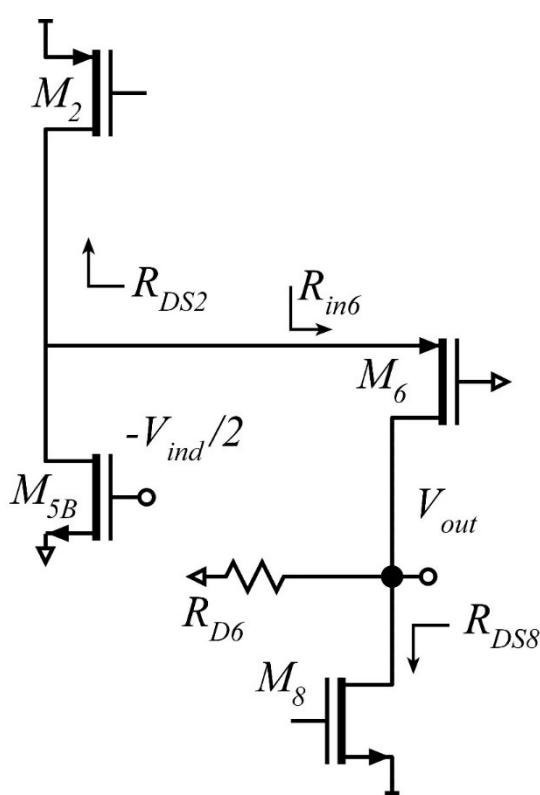

$M6$ : Common-gate

$$R_{Leq6} = R_{D6} \parallel R_{DS8} = 10\text{k}\Omega \parallel 40\text{k}\Omega = 8\text{k}\Omega$$

$$\begin{aligned} R_{in6} &= (1/g_m)(1 + R_{Leq6}/R_{DS6}) \\ &= 500\Omega \cdot (1 + 8\text{k}\Omega / 40\text{k}\Omega) = 600\Omega \end{aligned}$$

$$A_{v6} = R_{Leq6} / R_{in6} = 8\text{k}\Omega / 600\Omega = 13.333$$

$M5B$ : Common-source

$$R_{Leq5B} = R_{in6} \parallel R_{DS2} \parallel R_{DS5B} = 600\Omega \parallel 20\text{k}\Omega \parallel 40\text{k}\Omega = 574\Omega$$

$$A_{v5B} = -g_{m5B} R_{Leq5B} = 2\text{mS} \cdot 574\Omega = -1.15$$


$$V_{out} / V_d = -A_{v6} A_{v5B} / 2 = 15.333 / 2 = 7.6666$$

Alternatively, tracking currents:

$$\begin{aligned} A_{v6} A_{v5B} &= -g_{m5B} \left( \frac{R_{DS2} \parallel R_{DS5B}}{R_{DS2} \parallel R_{DS5B} + R_{in6}} \right) R_{Leq6} = -2\text{mS} \cdot \left( \frac{13.33\text{k}\Omega}{13.33\text{k}\Omega + 600\Omega} \right) 8\text{k}\Omega \\ &= -2\text{mS} \cdot (0.957) 8\text{k}\Omega = -15.333 \end{aligned}$$

# Maximum signal swings

---

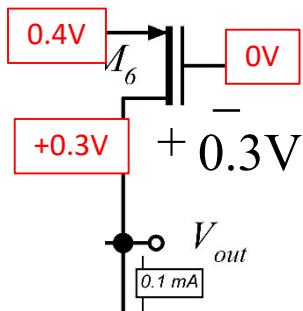


Knee voltage of M6:

Transistor is biased at  $V_G = 0.4\text{V}$  and  $V_S = 0.0\text{V}$

Knee (saturation): when  $V_{DG} = V_{th} = 0.3\text{V}$ .

Voltages as indicated on drawing

Output can swing to +0.3V.

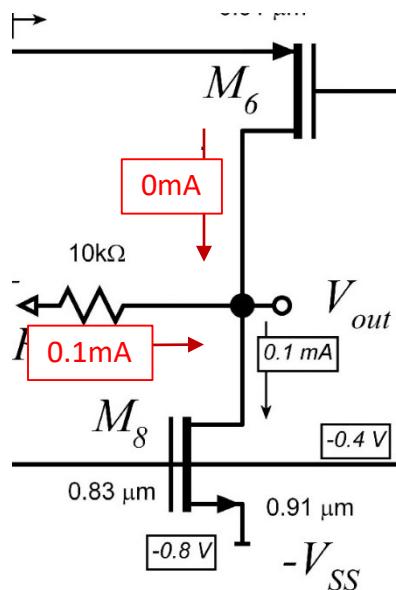

M6 cutoff:

We can decrease  $I_{D6}$  from  $100\mu\text{A}$  to  $0\mu\text{A}$ .

$$R_{Leq6} = 10\text{k}\Omega \parallel R_{DS8} = 8\text{k}\Omega$$


$$\Delta V_{out} = -100\mu\text{A} \cdot 8\text{k}\Omega = -0.8\text{V}.$$

Output can swing to -0.8V.

note:  $R_{DS8}$  accounts for the variation of  $I_{D8}$  with  $V_{out}$ ; as  $V_{out}$  goes negative,  $I_{D8}$  decreases due to  $(1+\lambda V_{DS})$ .

# Maximum signal swings

---

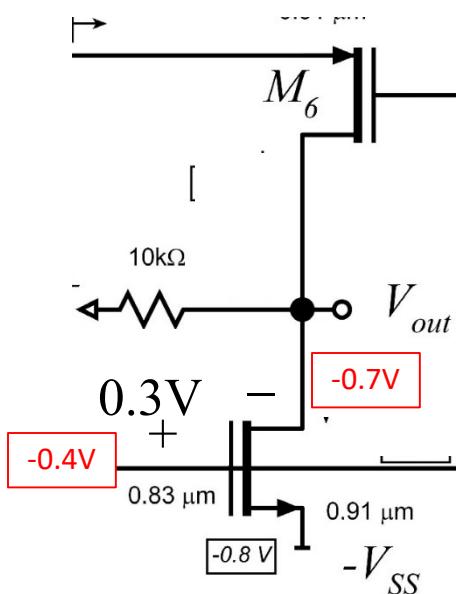

Knee voltage of  $M_8$ :


Transistor is biased at  $V_G = -0.4\text{ V}$  and  $V_S = -0.8\text{ V}$

Knee (saturation): when  $V_{DG} = -V_{th} = -0.3\text{ V}$ .

Voltages as indicated on drawing

Output can swing to  $-0.7\text{ V}$ .

# Maximum signal swings: M5A cutoff

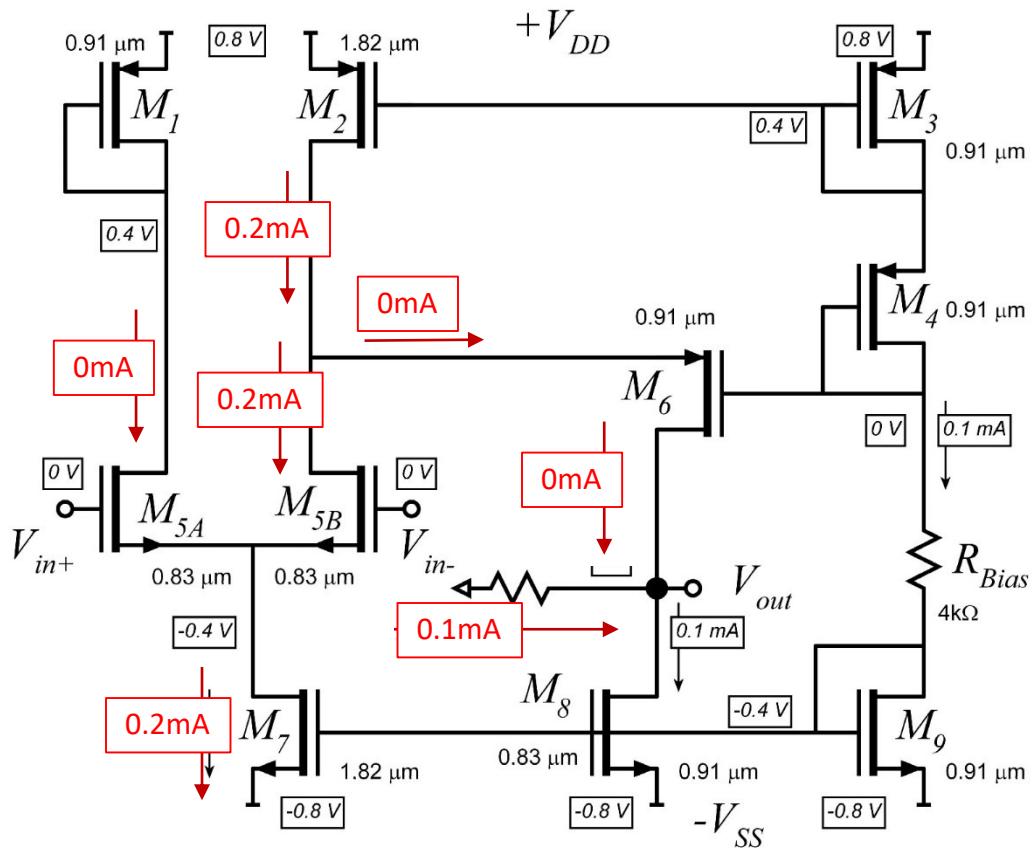

Can be calculated approximately by tracking the currents as shown to the right.

$$\Delta V_{out} = -0.1\text{mA} \cdot 10\text{k}\Omega = -1\text{V}?$$

We are ignoring the effect of  $R_{DS8}, R_{DS6}, R_{DS2}, R_{DS5B}$


More carefully:

$$\Delta I_{D5A} = 100\mu\text{A} \text{ to } 0\mu\text{A} = -100\mu\text{A} \rightarrow \Delta I_{D5B} = +100\mu\text{A}$$

$$\Delta I_{D6} = -\Delta I_{D5A} \left( \frac{R_{DS2} \parallel R_{DS5B}}{R_{DS2} \parallel R_{DS5B} + R_{in6}} \right) = -100\mu\text{A} \cdot (0.957) = 95.7\mu\text{A}$$

$$\Delta V_{out} = -\Delta I_{D6} R_{Leq6} = -95.7\mu\text{A} \cdot 8\text{k}\Omega = -0.768\text{V}. V_{out} \text{ can swing to } -0.77\text{V}.$$

# Maximum signal swings: M5B cutoff

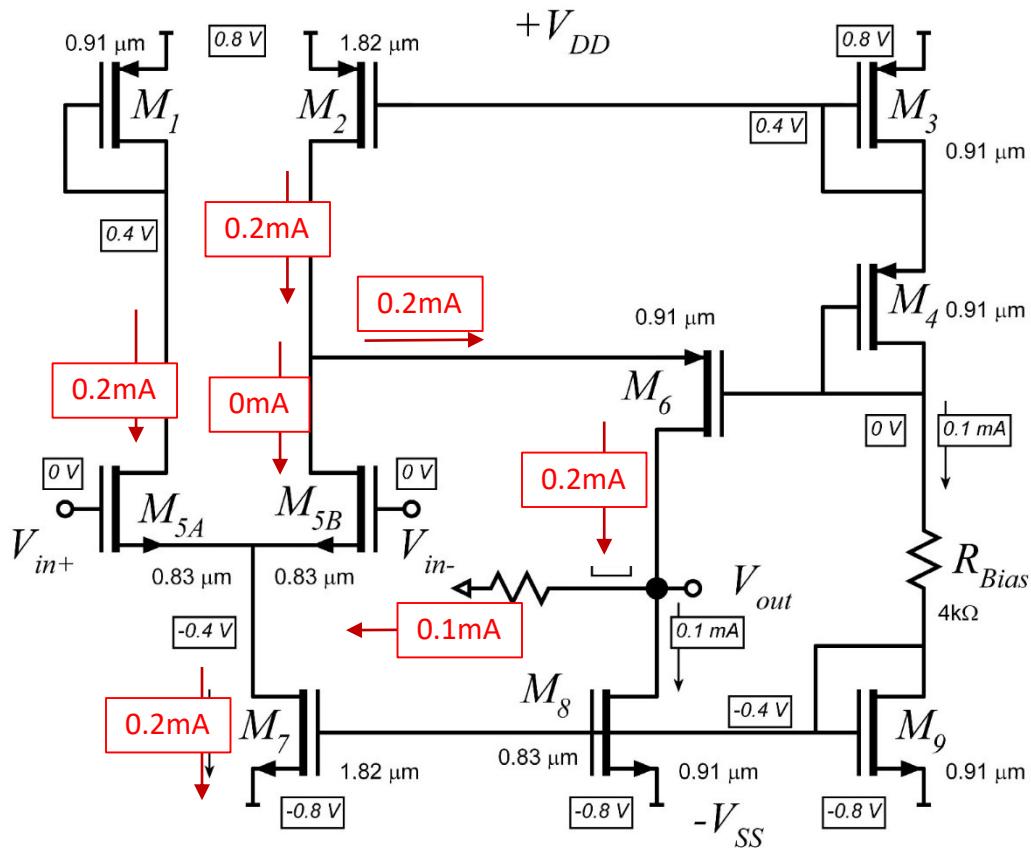

Can be calculated approximately by tracking the currents as shown to the right.

$$\Delta V_{out} = 0.1\text{mA} \cdot 10\text{k}\Omega = +1\text{V}?$$

We are ignoring the effect of  $R_{DS8}, R_{DS6}, R_{DS2}, R_{DS5B}$

More carefully:

$$\Delta I_{D5B} = -100\mu\text{A}$$

$$\Delta I_{D6} = -\Delta I_{D5A} \left( \frac{R_{DS2} \parallel R_{DS5B}}{R_{DS2} \parallel R_{DS5B} + R_{in6}} \right) = +100\mu\text{A} \cdot (0.957) = 95.7\mu\text{A}$$

$$\Delta V_{out} = \Delta I_{D6} R_{Leq6} = 96\mu\text{A} \cdot 8\text{k}\Omega = 0.768\text{V}. \text{ Output can swing to } 0.77\text{V}.$$