 


ECE137A, Notes Set 14: Op-Amps

***Mark Rodwell,
Doluca Family Chair, ECE Department
University of California, Santa Barbara
rodwell@ece.ucsb.edu***

Operational Amplifier




$$V_{out} = A_D (V^+ - V^-)$$

Characteristics of op-amp:

A_d is very large. Very large CMRR

Large R_{in} . Small R_{out}

 


Example of feedback network:

$$V^- = \beta V_{out} \text{ where } \beta = R_2 / (R_1 + R_2)$$

Operational Amplifier with Feedback

Combine these:

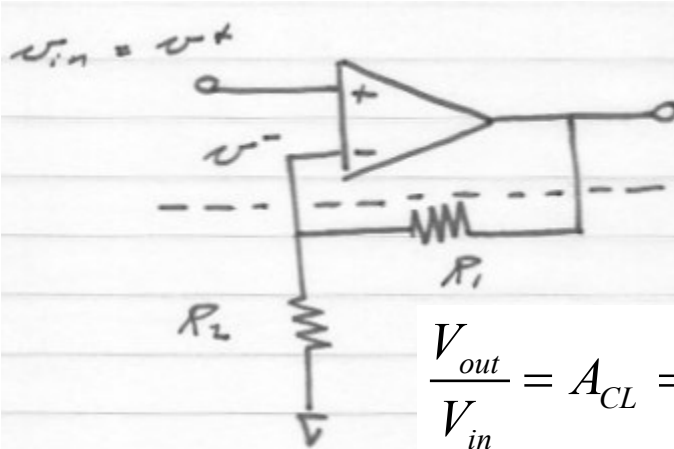

$$\frac{V_{out}}{V_{in}} = A_{CL} = \frac{1}{\beta} \cdot \frac{A_d \beta}{1 + A_d \beta} = \frac{1}{\beta} \cdot \frac{T}{1 + T}$$

where A_d = differential gain or open-loop gain, a.k.a. A_{OL}

β = feedback factor. A_{CL} = closed-loop gain.

T = loop transmission

$$\frac{V_{out}}{V_{in}} = A_{CL} = \begin{cases} 1/\beta & \text{if } T \gg 1 \\ A_d & \text{if } T \ll 1 \end{cases}$$

If the loop transmission is very large,

the closed-loop gain is precisely set by the feedback factor

Negative feedback

Feedback can provide precise control of circuit gain.

If $A_d\beta$ is large, then the gain is controlled by the feedback resistors

Note that the external feedback components also set the DC bias.

Op-amp bias is almost always set by the feedback network:

For now, analyze by assuming that $V_{out}=0V$,
and work back to the input to find (V^+-V^-) .

An op-amp is an amplifier that:

is designed for use with feedback

operates usually over a range of supply voltages

has a very large voltage gain

usually (not always) has a large input impedance

usually (not always) has a small output impedance

is designed to not oscillate when feedback is applied (see ece137B)

Bias analysis of op-amps

There will be a small mismatch between input transistors, and possibly also of their load, etcetera. As a result:

$$V_{out} = A_d (V_d + V_{os}) = A_d (V_{in}^+ - V_{in}^- + V_{os})$$

V_{os} is called the offset voltage, and might be 0.1-10mV.



If $A_d=10^6$ and $V_{os}=1\text{mV}$, then a zero-volt input would force the output to clipping.

Consequently, op-amps are always used with feedback

DC analysis is performed by assuming that $V_{out}=0\text{V}$, and working backward to find the required V_d to obtain this. This value of V_d is the offset voltage V_{os} .

Finding V_{out} given an offset voltage

$$V_{out} = A_d (V_d + V_{os})$$

  


$$V_{out} = A_d [V_{in} + V_{os} - \beta V_{out}]$$

$$V_{out} = \frac{1}{\beta} \frac{T}{1+T} (V_{in} + V_{os}) \quad ; \quad T = A_d \beta$$

V_{os} is simply amplified by the closed-loop gain.

How to get high voltage gain ?

 We seek $A_D \beta \gg 1$, so large op-amp gain is desired.




Suppose $V_{CQ} \ll V_{CC} \rightarrow R_L \cong V_{CC} / I_C$

$$-A_V = g_m R_{Leq} = g_m (R_L \parallel R_{CE}) < g_m R_L = (I_C / V_T)(V_{CC} / I_C) = V_{CC} / V_T$$

If $V_{CC} = 10\text{V}$, then $\|A_V\| < 10\text{V}/26\text{mV} \cong 400$

 \rightarrow gain is limited by the power supply




Suppose $V_{A1} = V_{A2}$ Then $R_{CE1} = R_{CE2} = V_A / I_C$

$$-A_V = g_{m1} R_{Leq} = g_{m1} (R_{CE1} \parallel R_{CE2}) = (I_C / V_T)(V_A / 2I_C) = V_A / 2V_T$$

If $V_A = 100\text{V}$, then $\|A_V\| = 50\text{V}/26\text{mV} \cong 2000$

\rightarrow gain is limited by the Early voltage

How to get high voltage gain ?

 


Suppose $V_{DQ} \ll V_{DD} \rightarrow R_L \cong V_{DD} / I_D$

$$-A_V = g_m R_{Leq} = g_m (R_L \parallel R_{DS}) < g_m R_L ; \text{ now assume mobility-limited} \\ = (2I_D / (V_{GS} - V_{TH})) (V_{DD} / I_D) = 2V_{DD} / (V_{GS} - V_{TH})$$

but only if $(V_{GS} - V_{TH}) > 2V_T$; otherwise $g_m = I_D / nV_T$

If $V_{CC} = 1\text{V}$, then $\|A_V\| \leq 1\text{V} / (n \cdot 26\text{mV}) \leq 1\text{V} / 26\text{mV} \cong 40$

 \rightarrow gain is limited by the power supply. Need low $(V_{GS} - V_{TH})$



Suppose $\lambda_1 = \lambda_2$ Then $R_{DS1} = R_{DS2} = 1 / \lambda I_D$


$$-A_V = g_{m1} R_{Leq} = g_{m1} (R_{DS1} \parallel R_{DS2}); \text{ now assume mobility-limited} \\ = (2I_D / (V_{GS} - V_{TH})) (1 / 2\lambda I_D) = 1 / (\lambda (V_{GS} - V_{TH}))$$

but only if $(V_{GS} - V_{TH}) > 2V_T$; otherwise $g_m = I_D / nV_T$

If $1 / \lambda = 4\text{V}$, then $\|A_V\| \leq 4\text{V} / (2 \cdot n \cdot 26\text{mV}) \leq 4\text{V} / 52\text{mV} \cong 80$

\rightarrow gain is limited by $(1 / \lambda)$. Need low $(V_{GS} - V_{TH})$.

Cascodes for high voltage gain

 

Approximate: Assume impedances presented to bases are small

Note: $g_{m1} = g_{m2} = g_{m3} = g_{m1}$ and $R_{CE1} = R_{CE2} = R_{CE3} = R_{CE4}$

$Q2$: common gate

$$R_{out3} = R_{CE} (1 + g_m R_{CE}) \cong g_m R_{CE}^2$$

$$R_{Leq2} = R_{out3}$$

$$R_{in2} = (1 / g_m) (1 + R_{Leq3} / R_{CE}) \cong R_{CE} (!)$$

$$A_{V2} = R_{Leq2} / R_{in2} = g_m R_{CE}$$

$Q1$: common-source


$$R_{Leq1} = R_{CE1} \parallel R_{in2} = R_{CE} \parallel R_{CE} = R_{CE} / 2$$

$$A_{V1} = -g_m R_{Leq1} = -g_m R_{CE} / 2 (!)$$

$$\text{Overall: } A_V = A_{V1} A_{V2} = -(g_m R_{CE})^2 / 2 = -(V_A / V_T)^2 / 2$$

$$\text{If } V_A = 100\text{V then } -A_V = (100\text{V}/26\text{mV})^2 / 2 \cong (4000)^2 / 2 = 8 \cdot 10^6$$



Cascode: alternate analysis

 

Norton (output) resistance

$$R_{out2} = R_{out3} \cong g_m R_{CE}^2$$

  
$$R_{out} = R_{out3} \parallel R_{out2} \cong g_m R_{CE}^2 / 2$$



Norton (output) current

R_{in2} is now $1/g_m$, so $R_{in2} \ll R_{CE1}$, so


$$I_{out} \cong g_m V_{in}$$

 

Norton and Thevenin models:

voltage gain is $-(g_m R_{DS})^2 / 2$

FET Cascode

 

By the same analysis (either method)

$$A_V = A_{V1} A_{V2} = -(g_m R_{DS})^2 / 2$$

If we assume mobility-limited operation,


$$\text{take } R_{DS} = 1 / \lambda I_D$$

$$\text{and } g_m = 2I_D / (V_{GS} - V_{TH}) < I_D / nV_T,$$

$$\text{then } A_{V1} A_{V2} = (2 / \lambda (V_{GS} - V_{TH}))^2 / 2 \leq (1 / \lambda nV_T)^2$$


$$\text{Example: } 1 / \lambda = 4\text{V}, (V_{GS} - V_{TH}) = 0.1\text{V} \rightarrow |A_{V1} A_{V2}| = 800$$

A simple op-amp

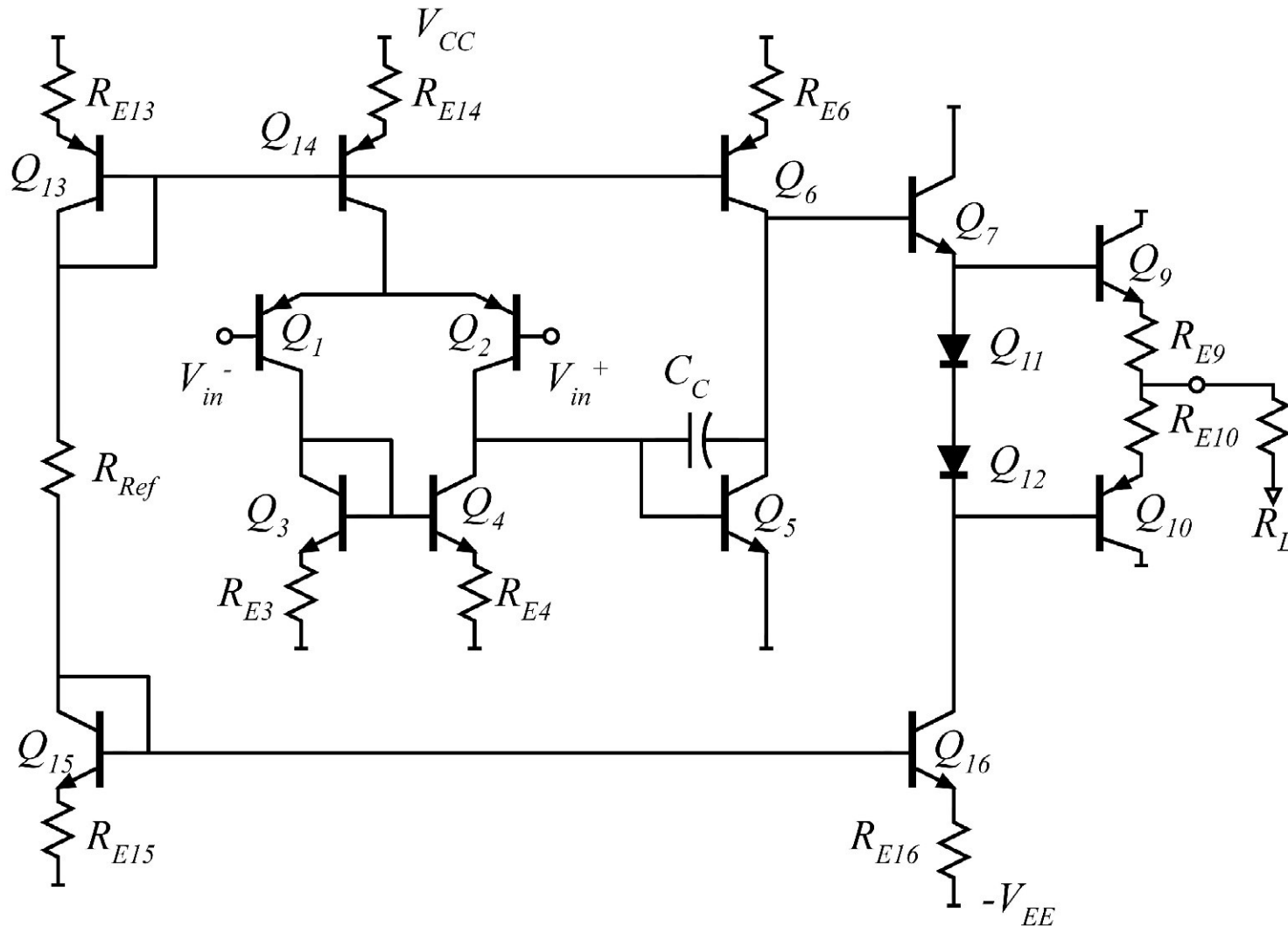

The compensation capacitor C_C will be explained in ece137B


A simple op-amp: DC bias

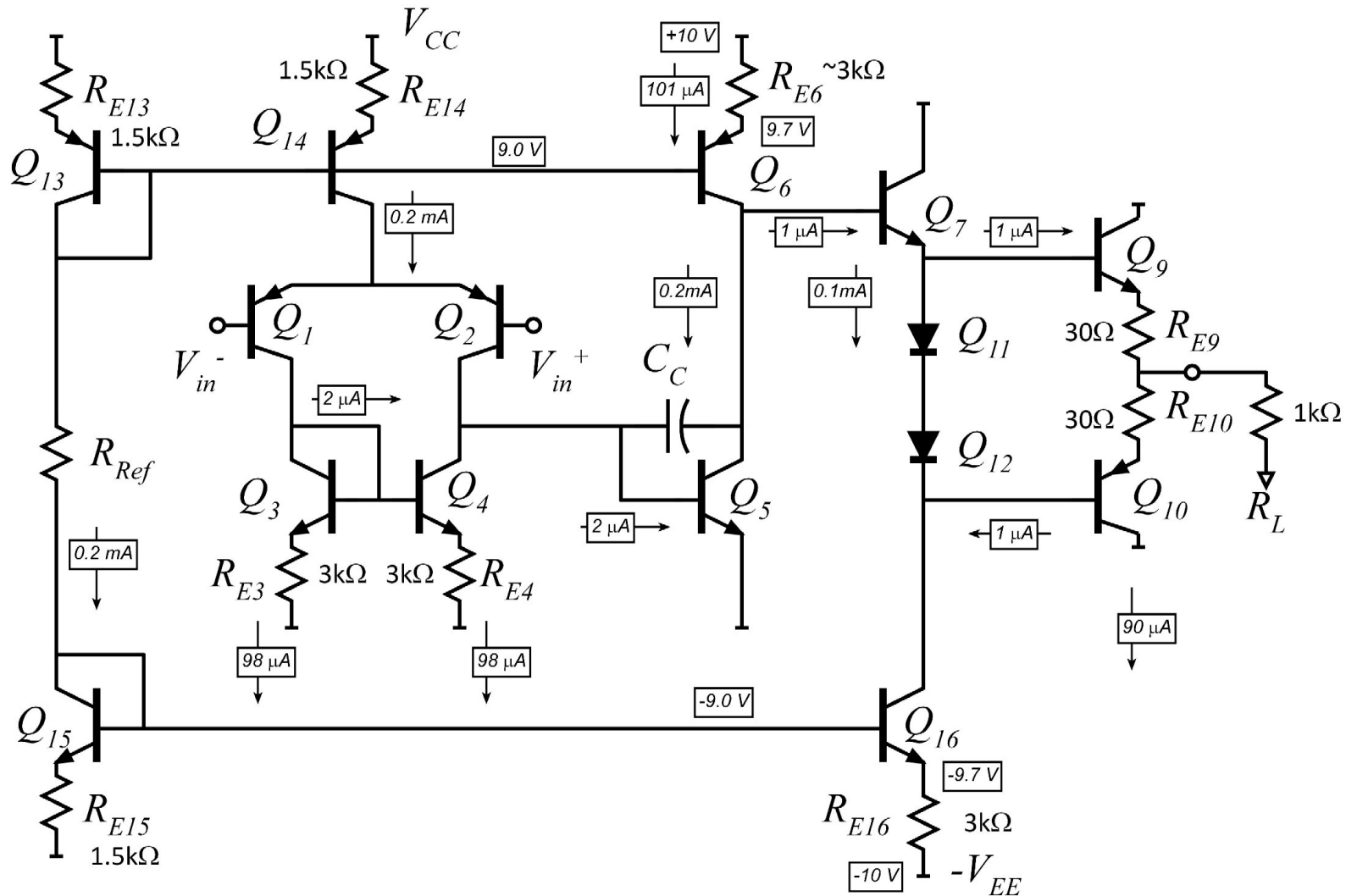

Assume that all transistors have identical I_S

$\beta = 100$, $V_A = 100\text{V}$

A simple op-amp: Small-signal (1)

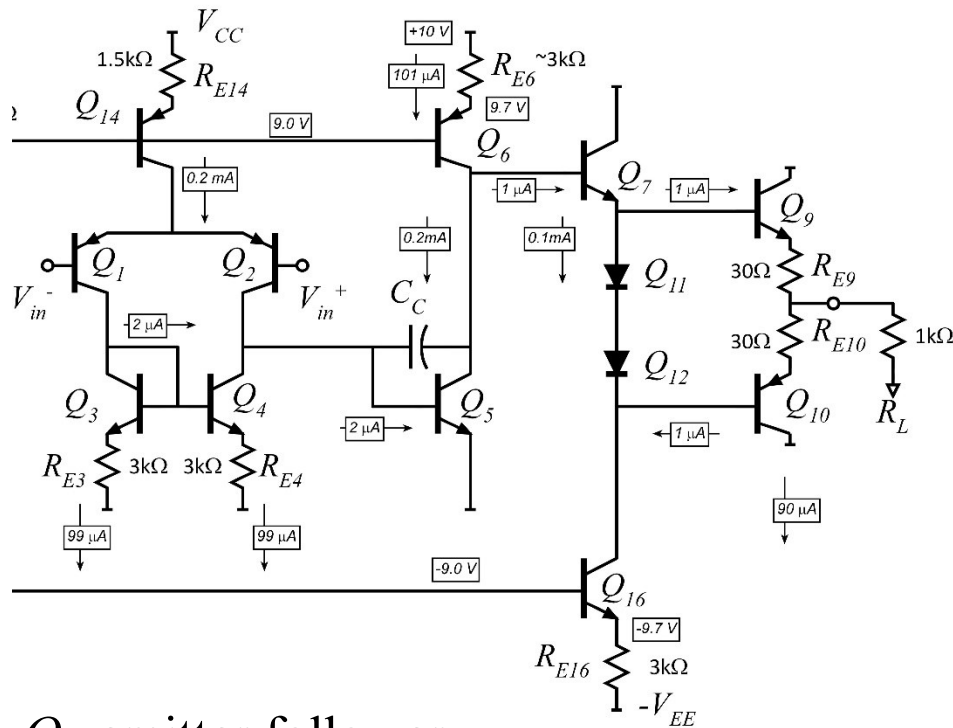

Q_9 / Q_{10} : push-pull. Assume Q_9 is on.

Assume $V_{out} = 1V \rightarrow I_{E9} = 1mA$.

$$g_{m9} = 1 / 26\Omega$$

$$R_{Leq9} \cong 1030\Omega$$

$$A_{v9} = R_{Leq9} / (R_{Leq9} + 1 / g_m)$$

$$= 1000\Omega / (1030\Omega + 26\Omega) = 0.947$$

$$R_{in9} = \beta(R_{Leq9} + 1 / g_{m9}) = 100 \cdot 1056\Omega$$

$$\cong 100k\Omega$$

Q_7 emitter follower.

$$g_{m7} = 1 / 260\Omega$$

$$R_{CE7} \cong R_{CE16} = V_A / I_C \cong 100V / 0.1mA = 100k\Omega$$


$$R_{Leq7} = R_{CE7} \parallel R_{CE16} \parallel R_{in9} = 33.3k\Omega.$$

$$A_{v7} = R_{Leq7} / (R_{Leq7} + 1 / g_m) = 33.3k\Omega / (33.3k\Omega + 260\Omega) = 0.992$$

$$R_{in7} = \beta(R_{Leq7} + 1 / g_{m7}) = 100 \cdot 33.6k\Omega$$

$$\cong 3.3M\Omega$$

A simple op-amp: Small-signal (2)

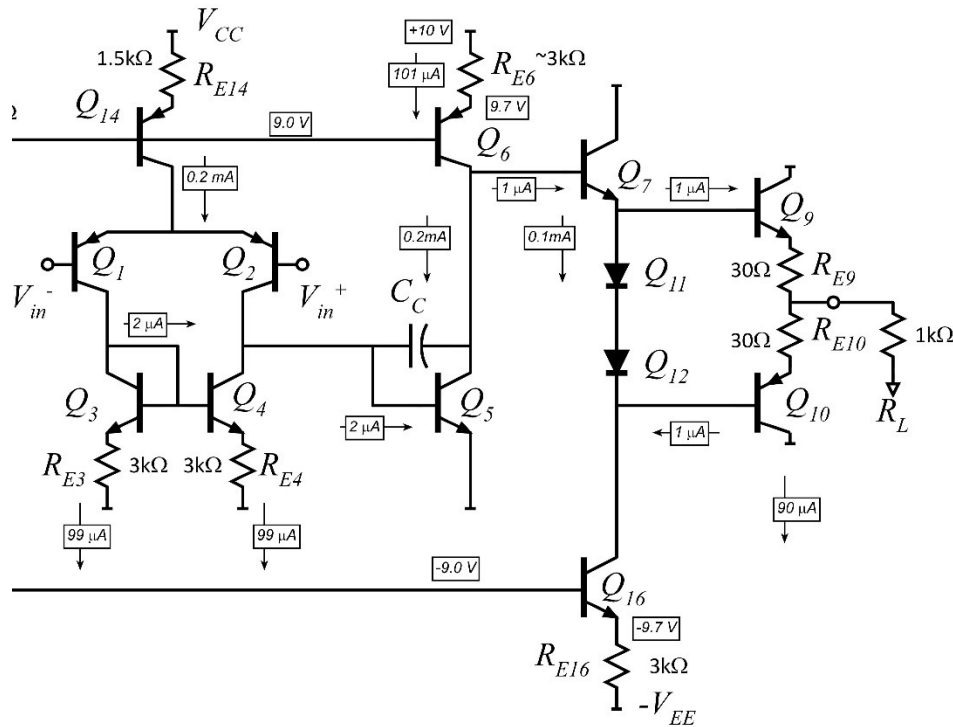

Q_5 common emitter

$$g_{m5} = 1 / 130\Omega$$

$$R_{CE5} \cong R_{CE16} = V_A / I_C$$

$$\cong 100V / 0.2mA = 500k\Omega$$

$$R_{out6} \cong R_{CE6} (1 + g_{m6} R_{E6})$$

$$= 500k\Omega (1 + 3k\Omega / 130\Omega) = 12M\Omega$$

$$R_{Leq5} = R_{CE5} \parallel R_{out6} \parallel R_{in7} =$$


$$= 500k\Omega \parallel 12M\Omega \parallel 3.3M = 419k\Omega$$

$$A_{v5} = -g_{m5} R_{Leq5} = -419k\Omega / 130\Omega$$

$$= -3200$$

$$R_{in5} = \beta / g_{m5} = 100 \cdot 130\Omega = 13k\Omega$$

A simple op-amp: Small-signal (3)

 

$$g_{m1,2,4,3} = 1 / 260\Omega$$

$$R_{CE1,2,3,4} = V_A / I_C \cong 100\text{V} / 0.1\text{mA} = 1\text{M}\Omega$$

$$R_{out4} \cong R_{CE4} (1 + g_{m4} R_{E4}) = 1\text{M}\Omega (1 + 3\text{k}\Omega / 260\Omega) = 12.5\text{M}\Omega$$

$$R_{Leq1,2,3,4} = R_{CE2} \parallel R_{out4} \parallel R_{in5} = 1\text{M}\Omega \parallel 12.5\text{M}\Omega \parallel 13\text{k}\Omega \cong 13\text{k}\Omega$$


$$A_{v1,2,3,4} = g_{m1,2} R_{Leq} = 13\text{k}\Omega / 260\Omega = 50$$

$$R_{in,diff} = 2\beta / g_{m1,2} = 2 \cdot 100 \cdot 260\Omega = 52\text{k}\Omega$$

Overall differential gain:

$$A_d = 50 \cdot 3200 \cdot 0.992 \cdot 0.947 = 150,000$$


Common-mode gain (?)

 

The above analysis suggests infinite CMRR.

It needs to be repeated given assumed mismatches between $Q1-Q2$ and $Q3-Q4$.

Low-voltage CMOS Amplifier: Comments

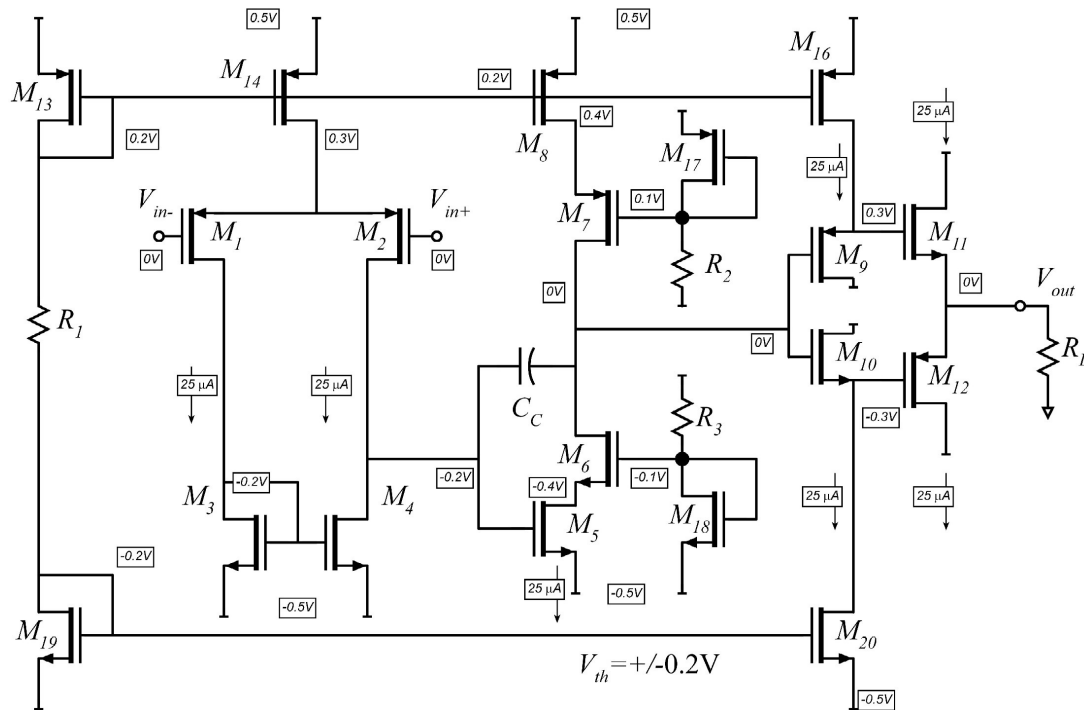

FETs:

$$K_{\mu} = 10\text{mA/V}^2 (W_g / 1\mu\text{m})$$

$$K_v = 2\text{mA/V} (W_g / 1\mu\text{m})$$

$$\Delta V = 0.1\text{V}$$


$$V_{th} = \pm 0.2\text{V}$$

$$1 / \lambda = 4\text{V}$$

Despite the cascode gain stage and the push-pull output stage, this design can operate with +/- 0.5V supplies and yet provide +/- 0.1V output

Most on-wafer CMOS op-amps do not need to drive significant output current and therefore have no source-follower output stage. Much larger voltage swings are then possible.

Low-voltage CMOS Amplifier

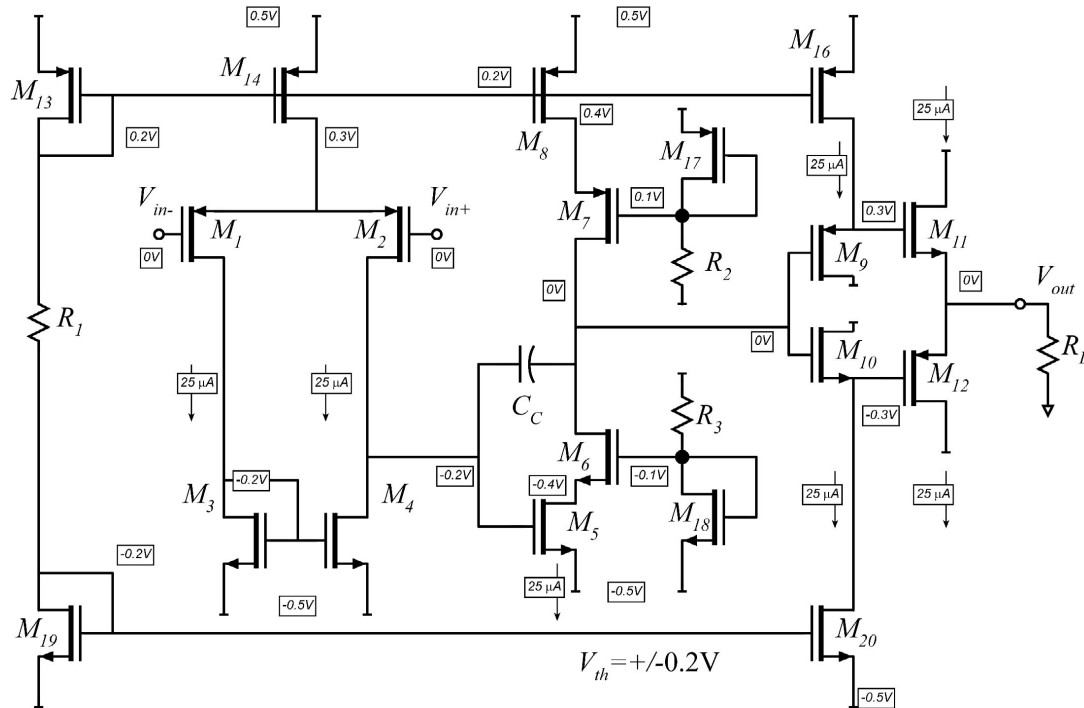

With all FETs except M17,18 operating at $V_{gs} = \pm 0.3\text{V}$ and $V_{th} = \pm 0.2\text{V}$, the FET saturation voltage is $V_{DS,sat} = 0.1\text{V}$.


Note carefully that all FETs are biased with $V_{DS} \geq 0.1\text{V}$.

All FET widths can be calculated from

$$I_D = K_\mu (V_{gs} - V_{th})^2 (1 + \lambda V_{DS})$$

where $K_\mu = 10\text{mA/V}^2 (W_g / 1\mu\text{m})$.

Diamond driver output stage

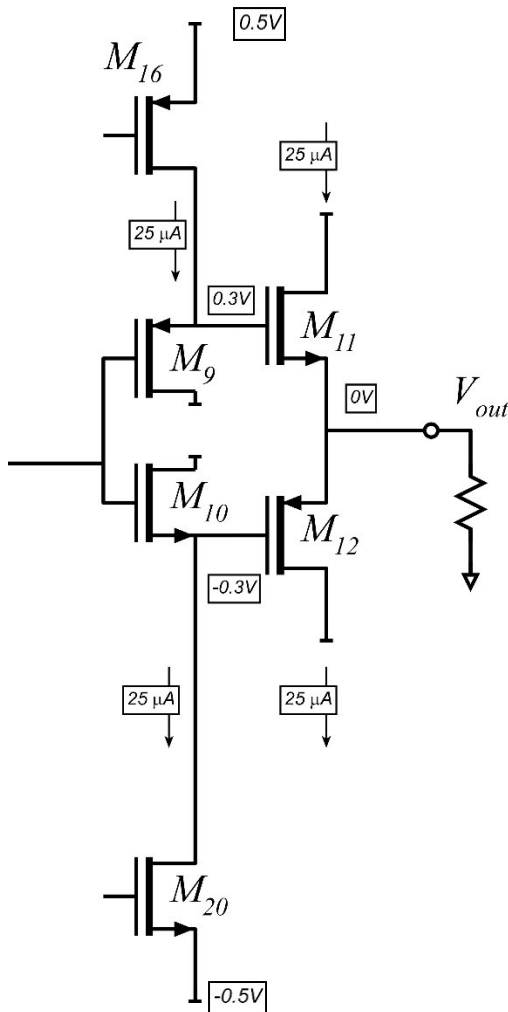

This is a different form of a push-pull output stage.

DC bias design is similar to a current mirror.

$$V_{gs9} + V_{gs10} = V_{gs11} + V_{gs12}.$$

If $I_{D16,9} = I_{D10,20}$, and if $W_{g11}/W_{g9} = W_{g12}/W_{g10}$

then $I_{D11,12} / I_{D9,10,16,20} = W_{g11}/W_{g9}$

For large output signals,

M9 and M11 carry the positive swing

while M10 and M12 carry the negative swing

Voltage gain is calculated in the usual way.


Close to 1 if $R_L \gg (1/g_{m11,12})$

M16 and M20 are biased with $|V_{DS}| = 0.2V$,

while $|V_{DS,sat}| = 0.1V$, so the maximum

output is $\pm 0.1V$. Not very large.

Differential Input stage

 

$$g_m = 2I_D / (V_{gs} - V_{th}) = 2(25\mu A) / (0.1V) = 0.5mS.$$

$$R_{DS} = 1 / \lambda I_D = 4V / 25\mu A = 160k\Omega$$


As derived earlier,

$$A_{v1,2,3,4} = (g_m R_{DS}) / 2 = 40$$

Overall op-amp gain:

$$A_D = A_{v1,2,3,4} A_{V5} A_{V6} A_{V9} A_{V11} \cong 40 \cdot 3200 = 128,000$$

Op-amp with no output buffer

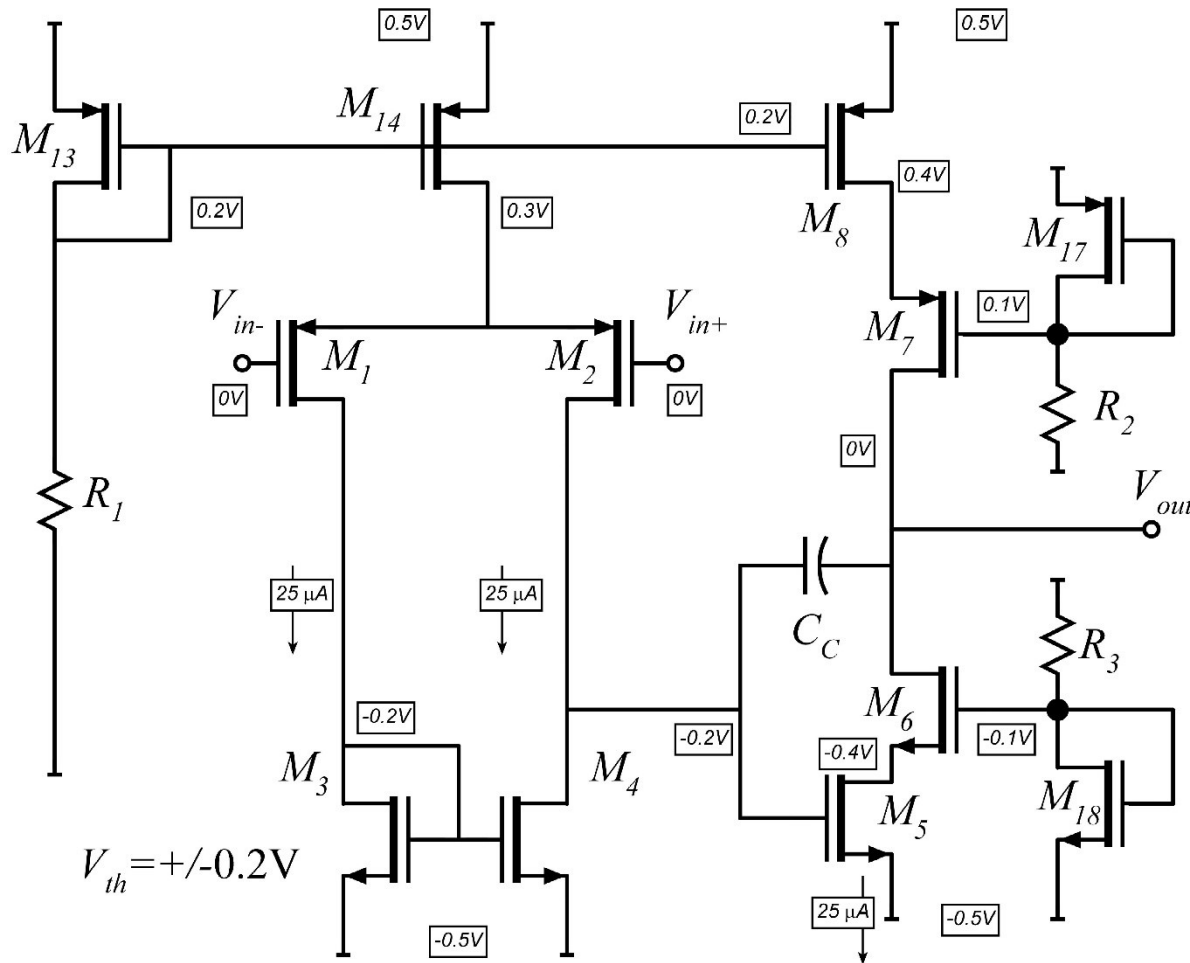

If the load impedances are always very high, then we can remove the output buffer

The output can then swing $\pm 0.3V$

More on op-amp design

Please see the documents associated with lab project 3