
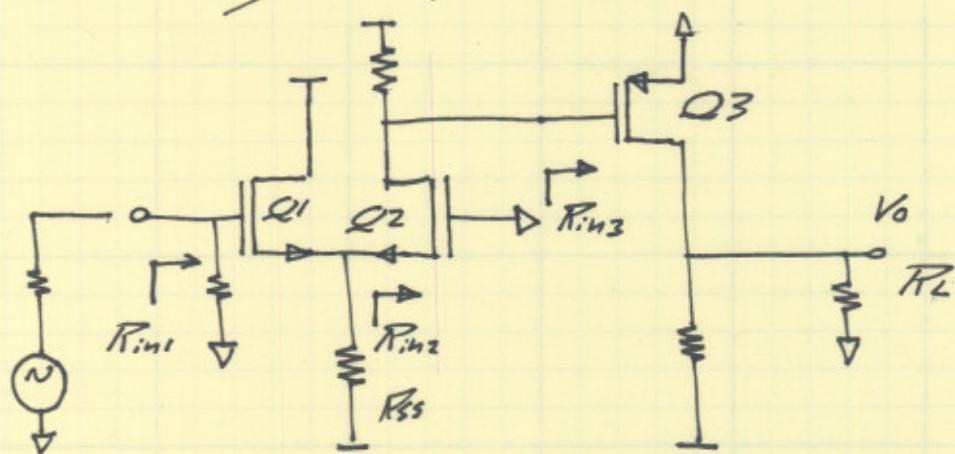


Multistage amplifiers

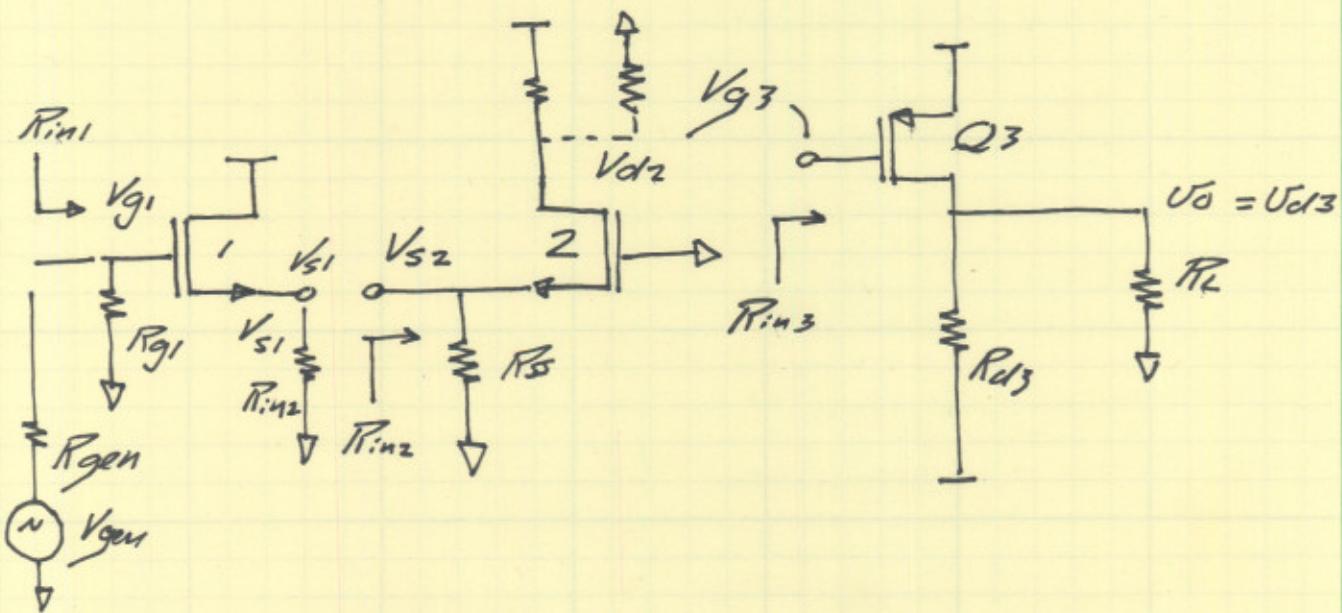

To analyze

- 1) Find bias, working from input to output
- 2) Separate into individual stages



- = First find V_{d3}/V_{g3} and find R_{in3}
- = Then find V_{d2}/V_{s2} and R_{in2}
 - Note that R_{in3} enters into the above calculation
- = Then find V_{s1}/V_{g1} and R_{in1}
 - Note that R_{in2} enters into the above calculation.
- = Then find V_{g1}/V_{gen}
 - depends upon R_{gen} and R_{in1}

we can then find

$$\frac{V_o}{V_{gen\text{ overall}}} = \frac{V_{in}}{V_{gen}} \cdot \frac{V_{s1}}{V_{g1}} \cdot \frac{V_{d2}}{V_{s2}} \cdot \frac{V_{d3}}{V_{g3}}$$

explicitly:

Q3:

$$R_{\text{load}} = R_L \parallel R_{D3} \parallel R_{S3}$$

$$Av = V_{d3}/V_{g3} = -g_{m3} R_{\text{load}}$$

$$R_{in3} = \infty$$

Q2/

$$R_{\text{load}} = R_{in3} \parallel R_{D2} = \infty \parallel R_{D2} = R_{D2}$$

$$R_{in, \text{source}, 2} = (1/g_{m2}) \left(\frac{R_{\text{load}} + R_{S2}}{R_{D2}} \right)$$

$$Av = V_{d2}/V_{S2} = R_{\text{load}} / R_{in, \text{source}, 2}$$

$$R_{in2} = R_{in, \text{source}, 2} \parallel R_S$$


Q1/

$$R_{\text{load}} = R_{S1} \parallel R_{in2}$$

$$Av_1 = V_{S1}/V_{g1} = \frac{R_{\text{load}}}{R_{\text{load}} + 1/g_{m1}}$$

$$R_{in1} = R_{g1}$$
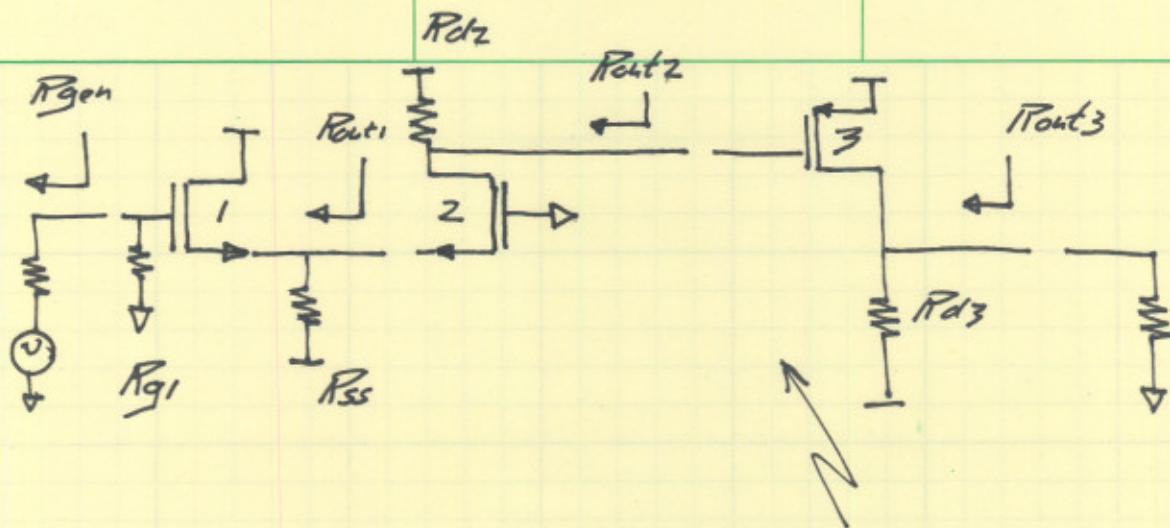
$$\text{generator/ } V_{th}/V_{gen} = R_{in1} / (R_{in1} + R_{gen})$$





To find output impedances, we must work in the opposite direction...

$$R_{out1} = R_{ss} \parallel \frac{1}{g_{m1}}$$

$$R_{out2} = R_{d3} \parallel \left\{ R_{ss} \cdot \left(1 + g_{m2} \cdot R_{out1} \right) \right\}$$

$$R_{out3} = R_{d3} \parallel R_{d53}$$

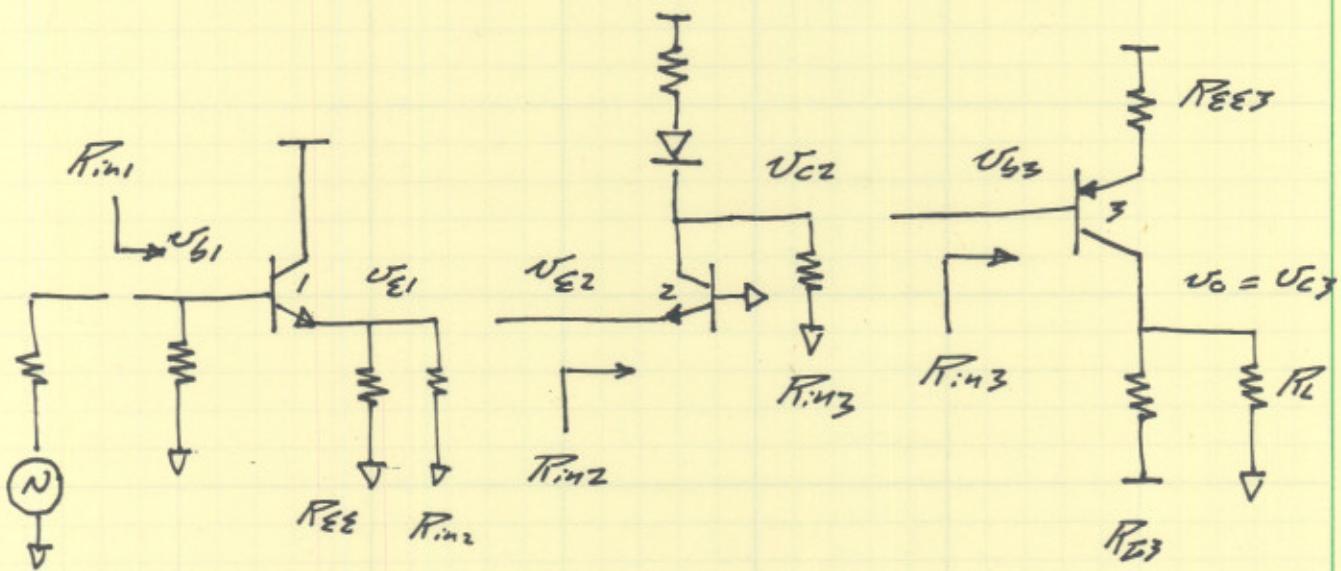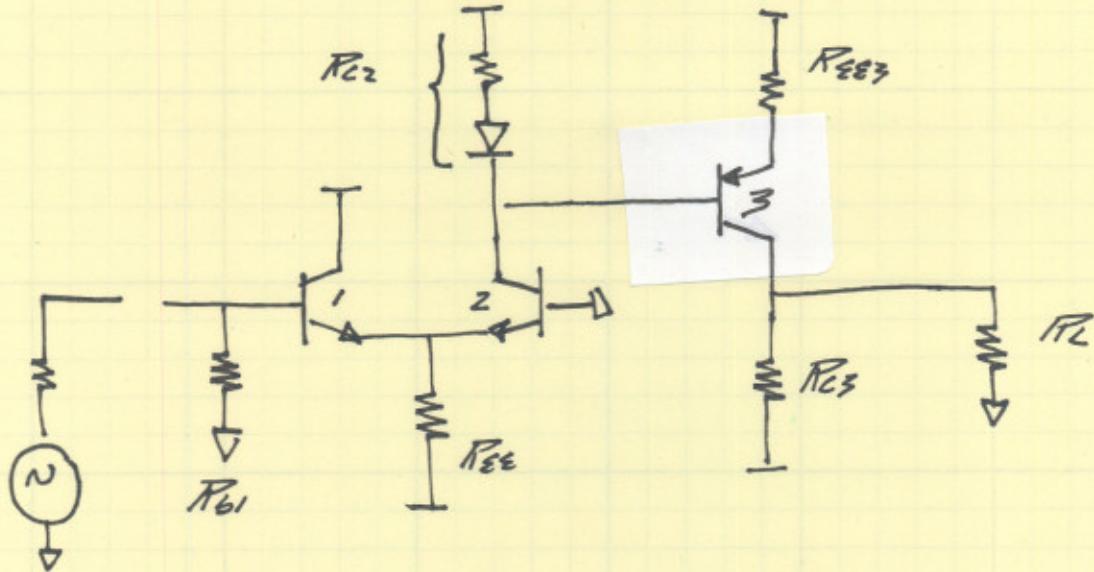The stage-stage interactions are much more significant with bipolar transistors.



for this bipolar example:

Q_3 / Common-emitter with degeneration.

$$R_{\text{leg}_3} = R_{C_3} \parallel R_L \parallel R_{\text{out}, \text{collectors}}$$

$$\left(\sim r_{E3} \cdot (1 + P_{EE3}/r_{E3}) \right)$$

$$A_v = V_{C_3} / V_{S_3} = -R_{\text{leg}_3} / (r_{E3} + P_{EE3})$$

$$R_{in,3} = \beta (r_{E3} + P_{EE3})$$

Q_2 / Common-base

$$R_{\text{leg}_2} = R_{L_2} \parallel R_{C_2} \parallel R_{\text{out}, \text{collectors}}$$

$$R_{in, \text{emitter}_2} = r_{E2} (1 + R_{\text{leg}_2}/R_{C_2}) = R_{in,2}$$

$$A_v = V_{C_2} / V_{E_2} = R_{\text{leg}_2} / R_{in, \text{emitter}_2}$$

Q_1 / common-collector

$$R_{\text{leg}_1} = R_{C_1} \parallel R_{E1} \parallel R_{in,1}$$

$$A_v = V_{E_1} / V_{S_1} = R_{\text{leg}_1} / (R_{\text{leg}_1} + r_{E1})$$

$$R_{in,1} = \beta (R_{\text{leg}_1} + r_{E1}) \parallel R_{S_1}$$