
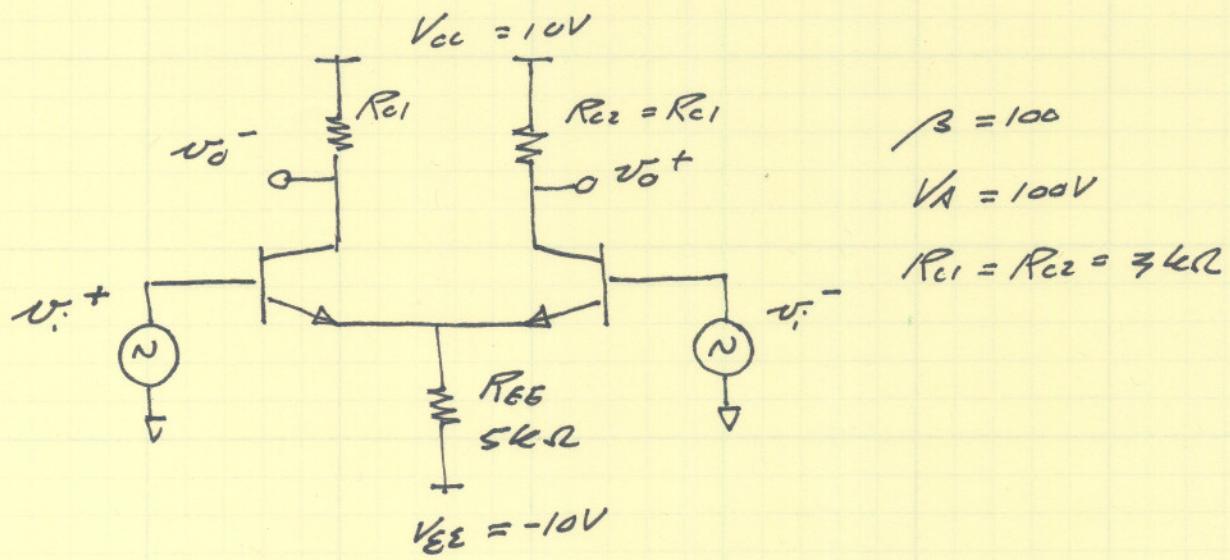



Differential Amplifiers

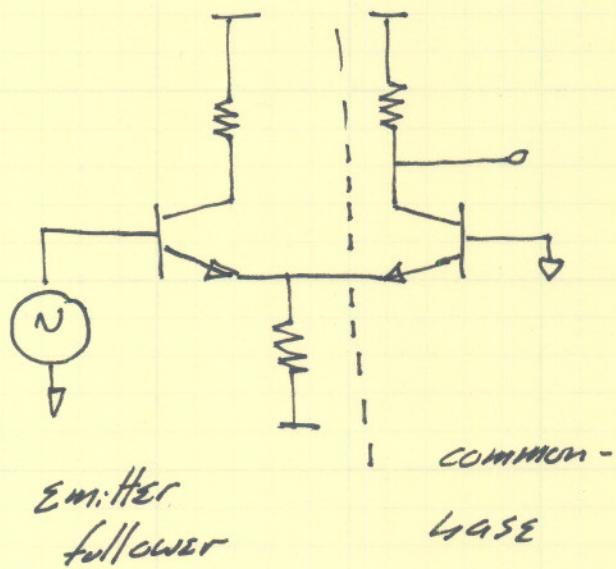

First consider "single-ended input" $\Rightarrow v_i^- = 0V$



Stage 2

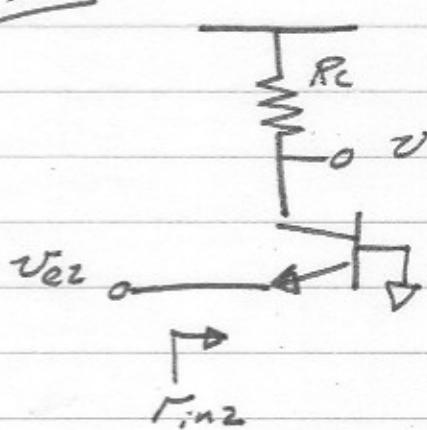


Common base

$$\frac{v_{c2}}{v_{e2}} \approx \frac{R_o}{r_e(1 + R_C/R_o)}$$

$$\approx \frac{R_o // R_C}{r_e}$$

$$r_{in2} = r_{e2}(1 + R_C/R_o) \approx r_{e2}$$

Stage 1

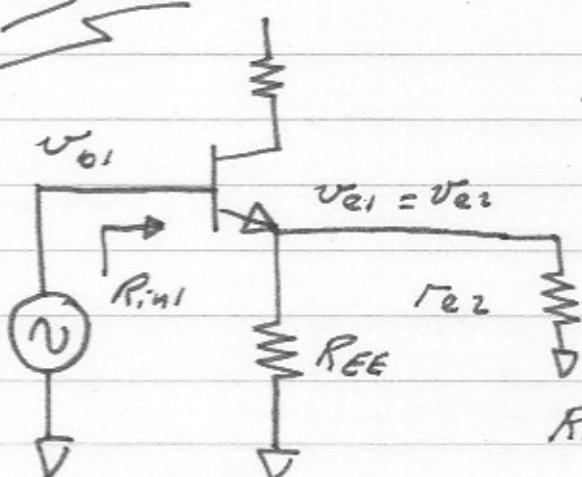

$$\frac{v_{e1}}{v_{o1}} = \frac{R_{leg}}{R_{leg} + r_{e1}} \approx \frac{R_{EE} // r_{e2}}{r_{e1} + R_{EE} // r_{e2}}$$

$$\approx \frac{r_{e2}}{r_{e1} + r_{e2}} = 1/2$$

$$R_{in1} = (\beta + 1)(r_{e1} + R_{leg})$$



$$= (\beta + 1)(r_{e1} + r_{e2} // R_{EE})$$

$$\approx (\beta + 1)(r_{e1} + r_{e2})$$

overall

$$\frac{v_{c2}}{v_i^+} = \frac{v_{out}^+}{v_i^+} \approx \frac{R_C}{r_{e2}} \frac{r_{e2}}{r_{e1} + r_{e2}} = \frac{R_C}{r_{e1} + r_{e2}}$$

Now consider case when $V_o^+ = 0$

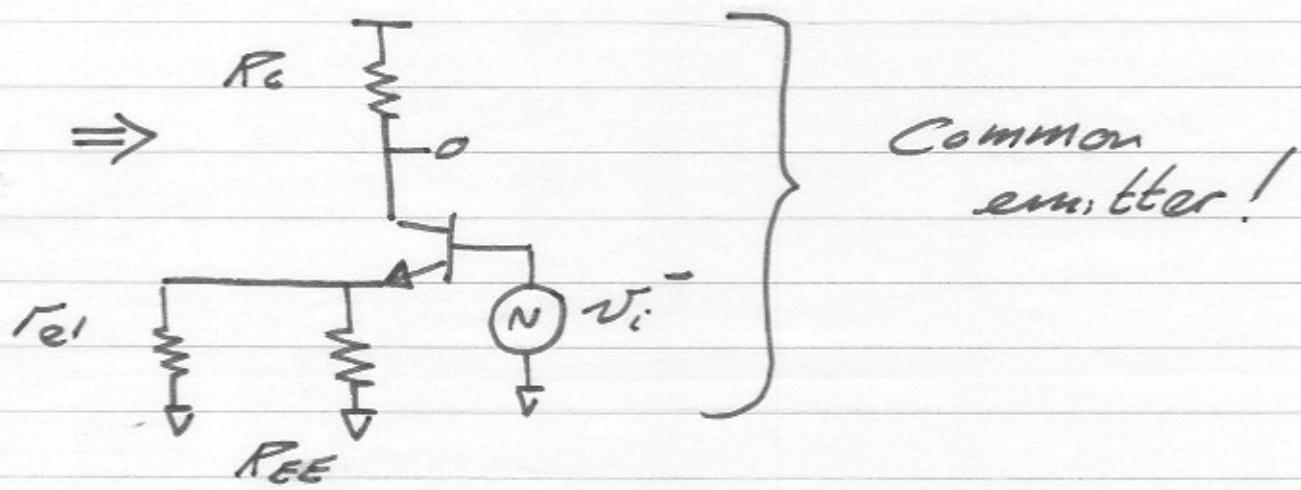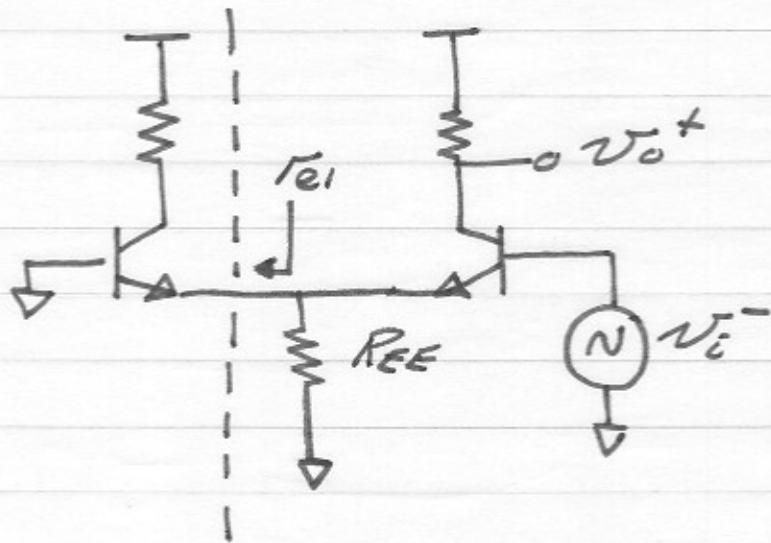

$R_C \parallel R_{out}$, neglect r_{out}

$$\frac{V_o^+}{V_o^-} = -\frac{R_{Ceq}}{r_{e2} + r_{e1} \parallel R_{EE}} \approx -\frac{R_C}{r_{e1} + r_{e2}}$$

We thus get the same gain, except for a reversal of signs

$$\Rightarrow V_{out}^+ \approx \frac{R_C}{r_{e1} + r_{e2}} (V_o^+ - V_o^-)$$

Another - easier - way to analyse the differential amplifier:

Differential and Common-Mode gains:


Differential signal: $v_d = v_i^+ - v_i^-$

Common-mode (average) signal: $v_{cm} = (v_i^+ + v_i^-)/2$

We want to amplify the differential signal
not the common-mode signal.


Differential

$$v_d/2$$

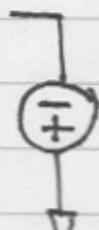

$$v_d/2$$

Common-Mode

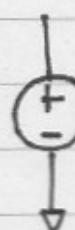


$$v_{cm}$$

$$v_{cm}$$


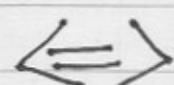
$$\left. \begin{aligned} v_d &= v_i^+ - v_i^- \\ v_{cm} &= \frac{v_i^+ + v_i^-}{2} \end{aligned} \right\}$$



$$\left. \begin{aligned} v_i^+ &= v_{cm} + v_d/2 \\ v_i^- &= v_{cm} - v_d/2 \end{aligned} \right\}$$



Differential Gain

$$\frac{V_o}{(-V_d/2)} = \frac{-R_{L_{eq}}}{r_{e2}}$$

Hence

$$\frac{V_o}{V_d} = \frac{R_{L_{eq}}}{2r_{e2}} = \frac{R_{L_{eq}}}{(r_{e1} + r_{e2})}$$

Because $r_{e1} = r_{e2}$

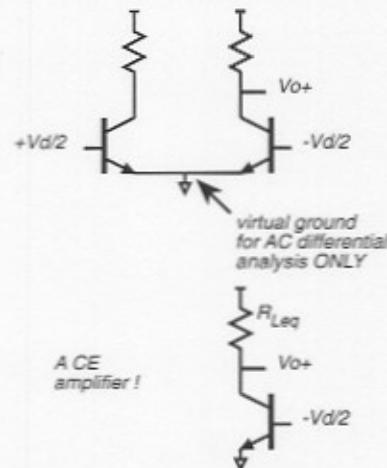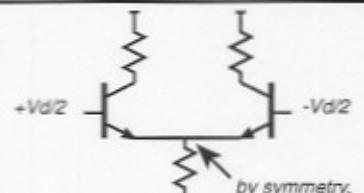

Common-Mode Gain

$$A_{CM} = \frac{V_o}{V_{CM}} = \frac{-R_{L_{eq}}}{r_{e2} + 2R_{EE}} \cong \frac{-R_{L_{eq}}}{2R_{EE}}$$


But we have already found that

$$A_D = \frac{V_o}{V_d} = \frac{R_{L_{eq}}}{2r_{e2}} = \frac{R_{L_{eq}}}{(r_{e1} + r_{e2})}$$

So the common-mode rejection ratio :


$$CMRR = \frac{A_D}{A_{CM}} = \frac{R_{EE}}{r_e}$$

where $r_e = r_{e1} = r_{e2}$

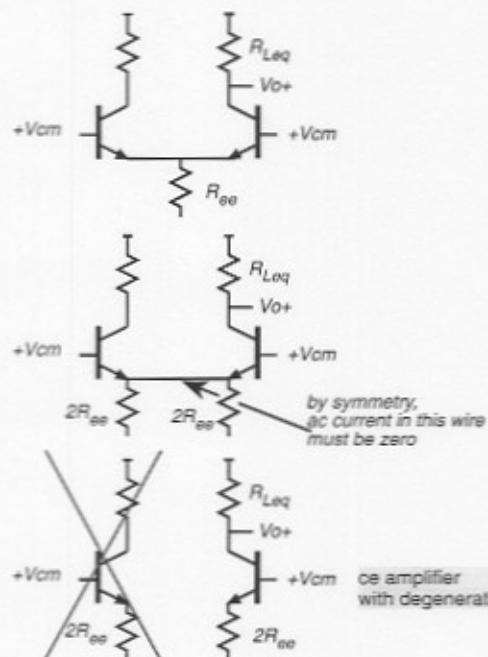


Constant-current source for increased CMRR

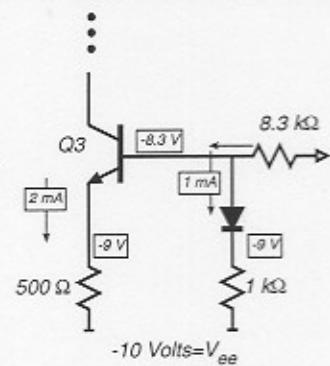The simple voltage divider + diode forces 1.0 Volts across the emitter resistor → pick r_{ee} for desired current.



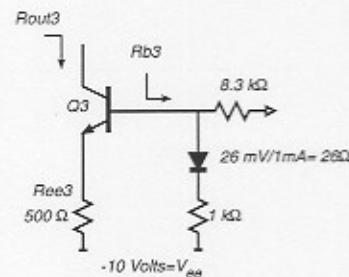
$$R_{out3} = r_{ce3} \left[1 + \frac{R_{EE3}}{r_{e3}} \frac{R_{be3}}{R_{be3} + R_{E3} + R_{b3}} \right] = 994 \text{ k}\Omega$$




Constant-current source for increased CMRR
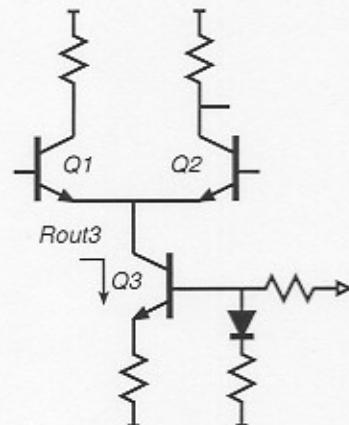
$$CMRR = \frac{R_{out3}}{r_{e1,2}} = \frac{994 \text{ k}\Omega}{26\Omega}$$




Differential pair with degeneration:

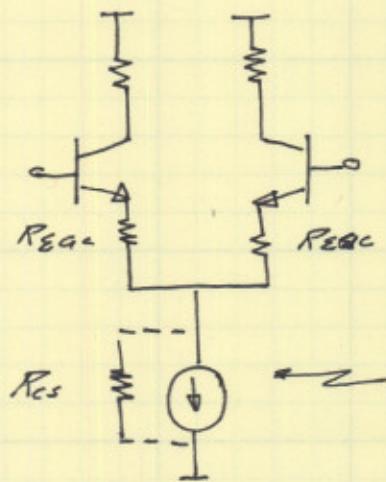


Norton equivalent of
active or passive
current source


Common-mode:

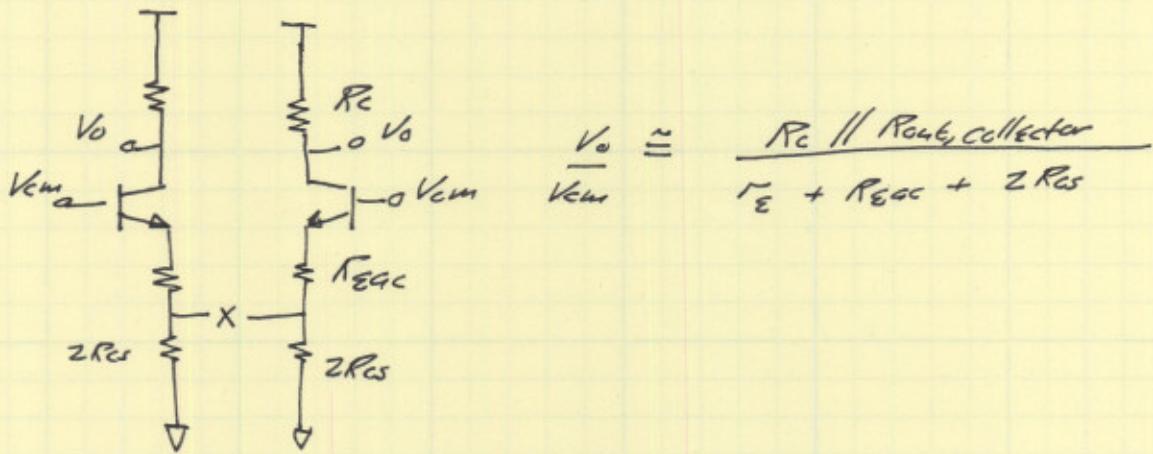

Differential:

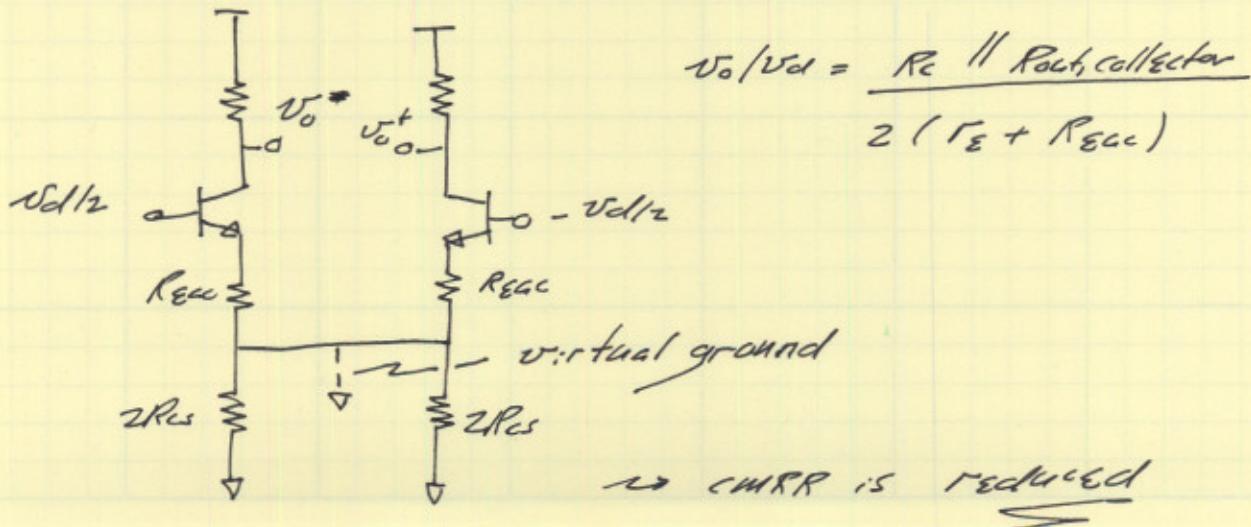


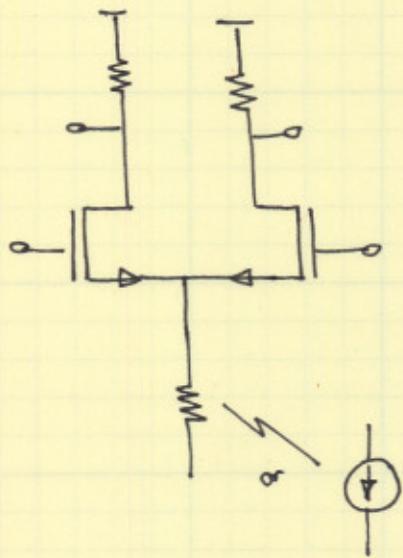WE CAN ALSO CONSTRUCT DIFFERENTIAL AMPLIFIERS
FROM MOSFETS, thus



... and the analysis is identical to that
of the bipolar implementation.

Differential stage input impedances

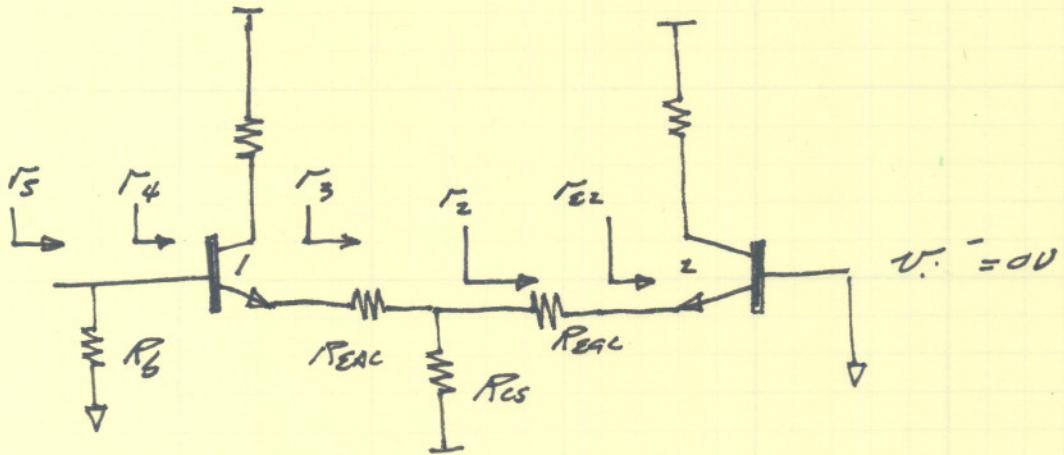

$$r_2 = r_{e2} + R_{EAC}$$

$$r_3 = R_{EAC} + r_2 \parallel R_{CS} \approx zR_{EAC} + r_{e2}$$


... if \$R_{CS}\$ is large

$$r_4 = \beta(r_{e1} + r_3) \approx z\beta(r_{e1} + R_{EAC})$$


$$r_5 = R_6 \parallel r_4.$$

This is the single-ended input impedance.


Differential input impedance

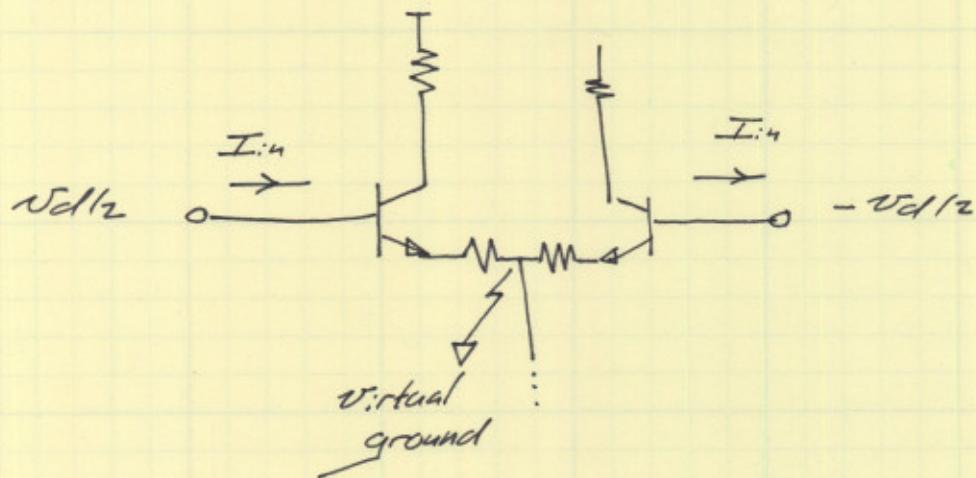


again use symmetry:

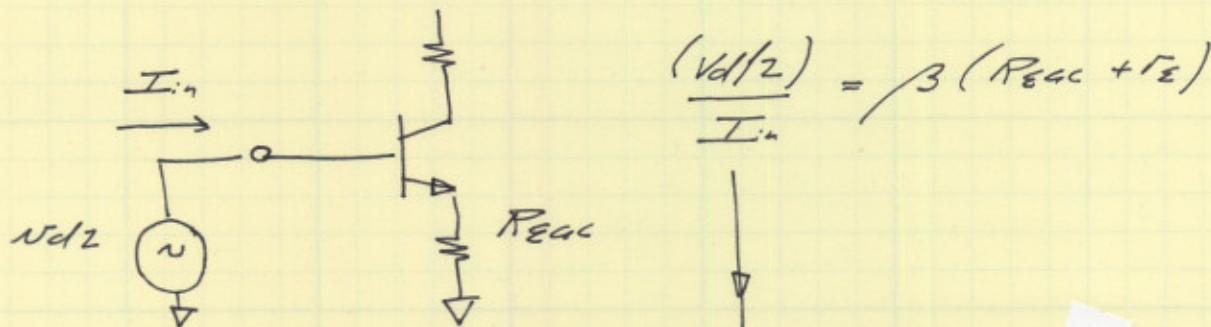
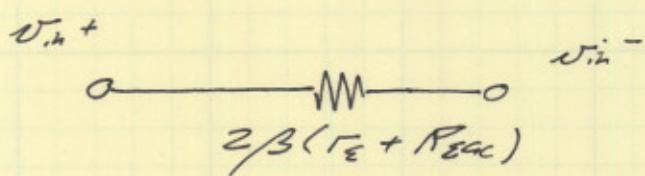
$$\begin{aligned} V_{d1/2}/I_{in} &= 2/\beta (r_e + R_{EAC}) \\ &= R_{in, \text{differential}} \end{aligned}$$




Common-Mode input impedance:

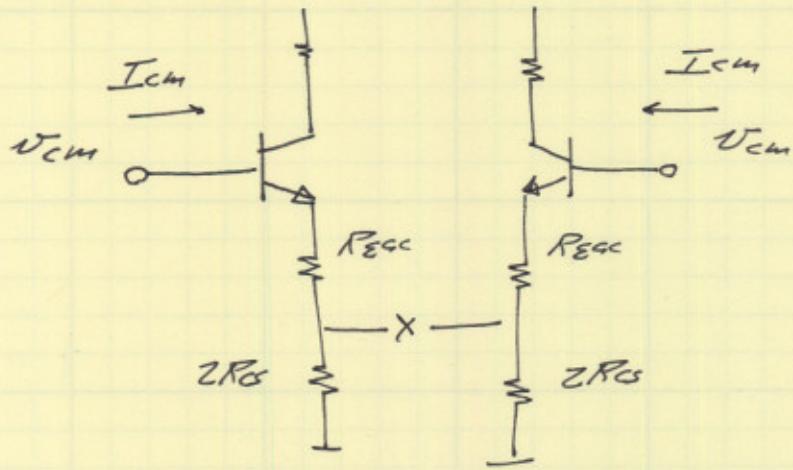

$$\frac{V_{cm}}{I_{cm}} = \beta (\tau_e + R_{ECC} + Z_{RCS}) \approx 2\beta R_{CS}$$

$$= R_{in, cm}$$

Total input model:

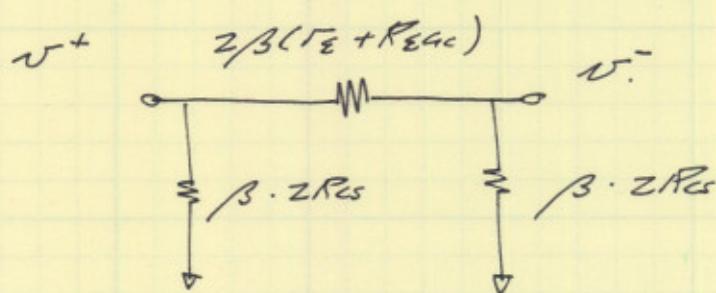

the input impedance must be modelled by
3 resistors

because there are three